

Benha University
Faculty Of Engineering at Shoubra



ECE 122
Electrical Circuits (2)(2017/2018)
Lecture (02)
Parallel Resonance

Prepared By :

Dr. Moataz Elsherbini

motaz.ali@feng.bu.edu.eg

Remember

Series Resonance

$$\boxed{1} \quad \omega_0 = \frac{1}{\sqrt{LC}} \quad , \quad f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$\boxed{2} \quad Z = R + j\left(\omega L - \frac{1}{\omega C}\right) \rightarrow \text{total series Res.}$$

$Z = R$ (at resonance).

$$\boxed{3} \quad BW = \omega_2 - \omega_1 = \frac{R}{L} = \frac{\omega_0}{Q}$$

$$\boxed{4} \quad \left. \begin{aligned} \omega_{1 \text{ actual}} &= \frac{-R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)} \approx \omega_0 - B/2 \\ &\rightarrow \text{from half power} \\ \omega_{2 \text{ actual}} &= \frac{+R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)} \approx \omega_0 + B/2 \\ &\rightarrow \text{from half power} \end{aligned} \right\} \text{at } Z = \sqrt{2}R$$

$$\boxed{5} \quad \omega_0 = \sqrt{\omega_1 \omega_2}$$

$$\boxed{6} \quad Q = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 RC}$$

Series Resonance Circuit (Cont.)

EXAMPLE 20.5 A series R - L - C circuit is designed to resonant at $\omega_s = 10^5$ rad/s, have a bandwidth of $0.15f_s$, and draw 16 W from a 120-V source at resonance.

- Determine the value of R .
- Find the bandwidth in hertz.
- Find the nameplate values of L and C .
- Determine the Q_s of the circuit.

$$BW = f_2 - f_1 = \frac{R}{2\pi L}$$

a. $P = \frac{E^2}{R}$ and $R = \frac{E^2}{P} = \frac{(120 \text{ V})^2}{16 \text{ W}} = \mathbf{900 \ \Omega}$

b. $BW = 0.15f_s$ $f_s = \frac{\omega_s}{2\pi} = \frac{10^5 \text{ rad/s}}{2\pi} = 15,915.49 \text{ Hz}$

$$BW = 0.15f_s = 0.15(15,915.49 \text{ Hz}) = \mathbf{2387.32 \text{ Hz}}$$


c. $BW = \frac{R}{2\pi L}$ and $L = \frac{R}{2\pi BW} = \frac{900 \ \Omega}{2\pi(2387.32 \text{ Hz})} = \mathbf{60 \text{ mH}}$

$$f_s = \frac{1}{2\pi\sqrt{LC}} \text{ and } C = \frac{1}{4\pi^2 f_s^2 L} = \frac{1}{4\pi^2 (15,915.49 \text{ Hz})^2 (60 \times 10^{-3} \text{ H})} = \mathbf{1.67 \text{ nF}}$$

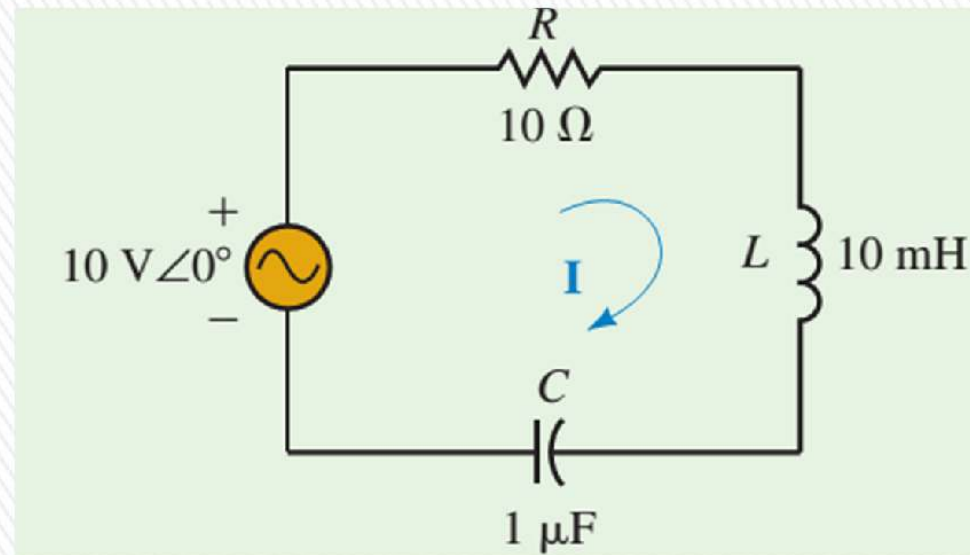d. $Q_s = \frac{X_L}{R} = \frac{2\pi f_s L}{R} = \frac{2\pi(15,915.49 \text{ Hz})(60 \text{ mH})}{900 \ \Omega} = \mathbf{6.67}$

Ex 2

- Determine the maximum power dissipated by the circuit.
- Use the results obtained from Example 21–1 to determine the bandwidth of the resonant circuit and to arrive at the approximate half-power frequencies, ω_1 and ω_2 .
- Calculate the actual half-power frequencies, ω_1 and ω_2 , from the given component values. Show two decimal places of precision.
- Solve for the circuit current, I , and power dissipated at the lower half-power frequency, ω_1 , found in part (c).



Solution

a.
$$P_{\max} = \frac{E^2}{R} = 10.0 \text{ W}$$

b. From Example 21–1, we had the following circuit characteristics:

$$Q_S = 10, \omega_S = 10 \text{ krad/s}$$

The bandwidth of the circuit is determined to be

$$\text{BW} = \omega_S Q_S = 1.0 \text{ krad/s}$$

If the resonant frequency were centered in the bandwidth, then the half-power frequencies occur at approximately

$$\omega_1 = 9.50 \text{ krad/s}$$

and

$$\omega_2 = 10.50 \text{ krad/s}$$

$$\begin{aligned}
 \text{c. } \omega_1 &= -\frac{R}{2L} + \sqrt{\frac{R^2}{4L^2} + \frac{1}{LC}} \\
 &= -\frac{10 \Omega}{(2)(10 \text{ mH})} + \sqrt{\frac{(10 \Omega)^2}{(4)(10 \text{ mH})^2} + \frac{1}{(10 \text{ mH})(1 \mu\text{F})}} \\
 &= -500 + 10\,012.49 = 9512.49 \text{ rad/s} \quad (f_1 = 1514.0 \text{ Hz}) \\
 \omega_2 &= \frac{R}{2L} + \sqrt{\frac{R^2}{4L^2} + \frac{1}{LC}} \\
 &= 500 + 10\,012.49 = 10\,512.49 \text{ rad/s} \quad (f_2 = 1673.1 \text{ Hz})
 \end{aligned}$$

d. At $\omega_1 = 9.51249 \text{ krad/s}$, the reactances are as follows:

$$X_L = \omega L = (9.51249 \text{ krad/s})(10 \text{ mH}) = 95.12 \Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{(9.51249 \text{ krad/s})(1 \mu\text{F})} = 105.12 \Omega$$


The current is now determined to be

$$\begin{aligned}
 \mathbf{I} &= \frac{10 \text{ V} \angle 0^\circ}{10 \Omega + j95.12 \Omega - j105.12 \Omega} \\
 &= \frac{10 \text{ V} \angle 0^\circ}{14.14 \Omega \angle -45^\circ} \\
 &= 0.707 \text{ A} \angle 45^\circ
 \end{aligned}$$

and the power is given as

$$P = I^2 R = (0.707 \text{ A})^2 (10 \text{ V}) = 5.0 \text{ W}$$

Ex 3

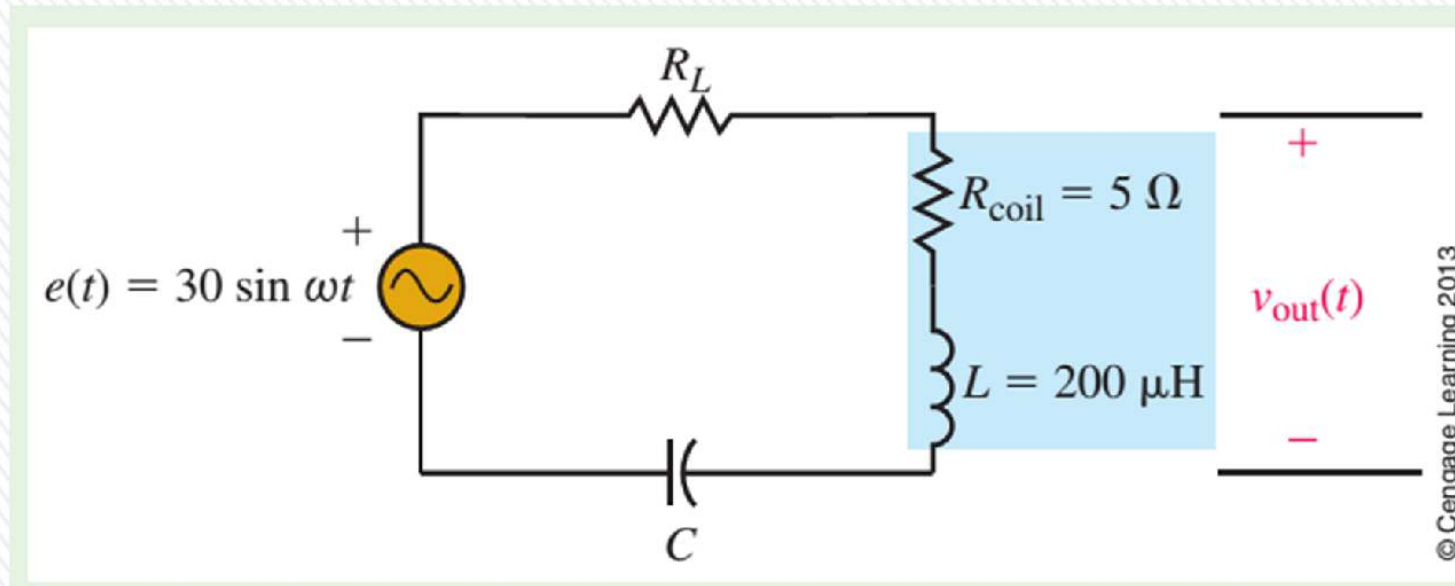

- Calculate the values of R_L and C for the circuit to have a resonant frequency of 200 kHz and a bandwidth of 16 kHz.
- Use the designed component values to determine the power dissipated by the circuit at resonance.
- Solve for $v_{\text{out}}(t)$ at resonance.

a. Because the circuit is at resonance, we must have the following condition:

$$\begin{aligned}Q_s &= \frac{f_s}{\text{BW}} \\ &= \frac{200 \text{ kHz}}{16 \text{ kHz}} \\ &= 12.5\end{aligned}$$

$$\begin{aligned}X_L &= 2\pi fL \\ &= 2\pi(200 \text{ kHz})(200 \mu\text{H}) \\ &= 251.3 \Omega\end{aligned}$$

$$\begin{aligned}R &= R_L + R_{\text{coil}} = \frac{X_L}{Q_s} \\ &= 20.1 \Omega\end{aligned}$$

and so R_L must be

$$R_L = 20.1 \Omega - 5 \Omega = 15.1 \Omega$$

Since $X_C = X_L$, we determine the capacitance as

$$\begin{aligned}C &= \frac{1}{2\pi f X_C} \\&= \frac{1}{2\pi(200 \text{ kHz})(251.3 \ \Omega)} \\&= 3.17 \text{ nF} (\equiv 0.00317 \ \mu\text{F})\end{aligned}$$

b. The power at resonance is found from Equation 21–20 as

$$\begin{aligned}P_{\max} &= \frac{E^2}{R} = \frac{\left(\frac{30 \text{ V}}{\sqrt{2}}\right)^2}{20.1 \ \Omega} \\&= 22.4 \text{ W}\end{aligned}$$

$$\begin{aligned} \mathbf{V}_{\text{out}} &= \frac{(R_1 + j\omega L)}{R} \mathbf{E} \\ &= \frac{(5 \Omega + j251.3 \Omega)}{20.1 \Omega} 21.21 \text{ V} \angle 0^\circ \\ &= (251.4 \Omega \angle 88.86^\circ)(1.056 \text{ A} \angle 0^\circ) \\ &= 265.5 \text{ V} \angle 88.86^\circ \end{aligned}$$

which in time domain is given as

$$v_{\text{out}}(t) = 375 \sin(\omega t + 88.86^\circ)$$

Ex 4

It is required to broadcast a shoubra radio station to be detected through your FM radio. Design a suitable series RLC circuit to verify this mission. The station must be heard within bandwidth of 2MHz, while the most purity sound heard at 90MHz.

$$\text{Sol/ } \omega \text{ BW} = \frac{R}{L} \text{ (rad/sec)}$$

$$\therefore (2 \times 10^6 \times 2\pi) = \frac{R}{L}$$

Let $R = 100 \Omega$ $\therefore L = \frac{100}{2 \times 10^6 \times 2\pi}$
series RLC circuit $\cong 7.95 \mu\text{H}$


$$\omega = \frac{1}{\sqrt{LC}} \quad \therefore 2\pi \times 90 \times 10^6 = \frac{1}{\sqrt{7.95 \times 10^{-6} \times C}}$$

$$\therefore C = 0.39 \mu\text{F}$$

Ex 5

Refer to the circuit of Figure 2.

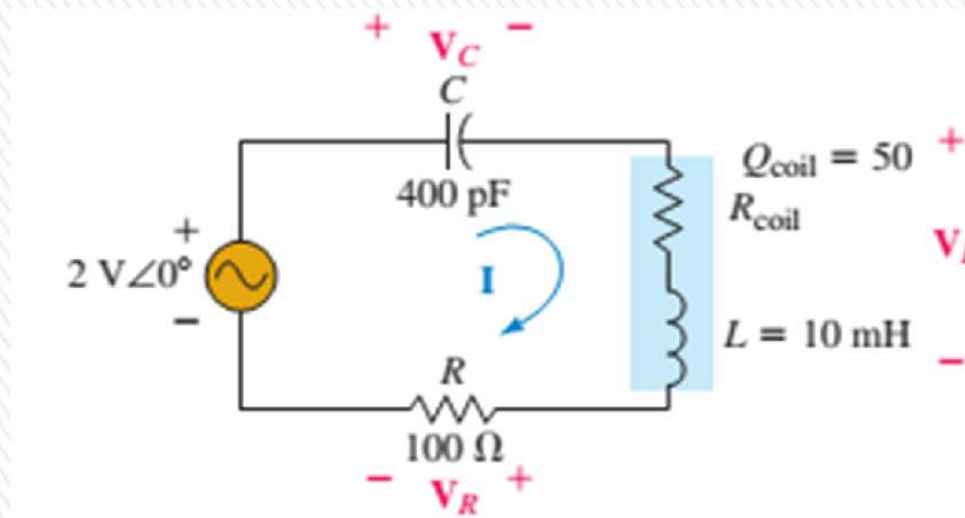- Determine the resonant frequency expressed as ω (rad/s) and f (Hz).
- Calculate the total impedance, Z_T , at resonance.
- Solve for current I at resonance.
- Solve for V_R , V_L , and V_C at resonance.
- Calculate the power dissipated by the circuit and evaluate the reactive powers, Q_C and Q_L .
- Find the quality factor, Q_S , of the circuit.



$$a - \omega = \frac{1}{\sqrt{LC}} = \frac{501}{\sqrt{(400 \times 10^{-12})(10 \times 10^{-3})}} = 500 \text{ krad/s}$$

$$f = \frac{\omega}{2\pi} = 79.617 \text{ kHz}$$

$$b - Z_{t|res} = R + R_{crit} = 100 + R_{crit}$$

$$Q = \frac{\omega L}{R_{crit}} \Rightarrow R_{crit} = \frac{\omega L}{Q} = \frac{500 \times 10^3 \times 10 \times 10^{-3}}{5} = 100$$

$$\therefore Z_t = R = 100 + 100 = 200 \Omega$$

$$c - I_m = \frac{V}{Z_{t|res}} = \frac{2}{200} = 0.01 \text{ A} = 10 \text{ mA}$$

$$d - V_R = I R = (0.01)(100) = 1 \text{ V}$$

$$V_C = I X_C = (0.01) \left(\frac{1}{\omega C} \right) \angle -90^\circ = 0.01 \frac{1}{(500)(10^3)(10 \times 10^{-6})} \angle -90^\circ = 50 \angle -90^\circ$$

$$V_L = I(X_L + R) = (0.01)(R + jX_L)$$

$$= (0.01)(100 + j(500 \times 10^3)(10 \times 10^{-3})) = (0.01)(100 + j5000)$$

$$= 1 + j50 = \sqrt{1^2 + 50^2} \angle \tan^{-1}\left(\frac{50}{1}\right) = 50.01 \angle 88.85^\circ$$

$$e - P = VI = (2)(0.01) = 0.02 = 20 \text{ mW}$$

$$P_C = I^2 X_C = (0.01)^2 (50) \angle -90^\circ = 0.5 \text{ VAR}$$

$$P_L = I^2 X_L = (0.01)^2 (5000) = 0.501 \text{ VAR}$$

$$Q = \frac{\omega L}{R} = \frac{(500 \times 10^3)(10 \times 10^{-3})}{200} = 25$$

Thank You

