

Benha University
Faculty Of Engineering at Shoubra



ECE 122
Electrical Circuits (2)(2017/2018)
Lecture (03)
Parallel Resonance

Prepared By :

Dr. Moataz Elsherbini

motaz.ali@feng.bu.edu.eg

Remember

Series Resonance

$$\boxed{1} \quad \omega_0 = \frac{1}{\sqrt{LC}} \quad , \quad f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$\boxed{2} \quad Z = R + j\left(\omega L - \frac{1}{\omega C}\right) \rightarrow \text{total series Res.}$$

$Z = R$ (at resonance).

$$\boxed{3} \quad BW = \omega_2 - \omega_1 = \frac{R}{L} = \frac{\omega_0}{Q}$$

$$\boxed{4} \quad \left. \begin{aligned} \omega_{1 \text{ actual}} &= \frac{-R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)} \cong \omega_0 - B/2 \\ \omega_{2 \text{ actual}} &= \frac{+R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)} \cong \omega_0 + B/2 \end{aligned} \right\} \begin{array}{l} \text{at} \\ Z = \\ \sqrt{2} R \end{array}$$

\rightarrow from half power

$$\boxed{5} \quad \omega_0 = \sqrt{\omega_1 \omega_2}$$

$$\boxed{6} \quad Q = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 RC}$$

Parallel Resonance Circuit

It is usually called tank circuit

Ideal Circuits

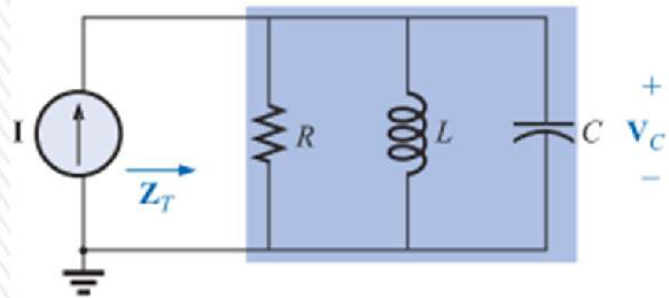


FIG. 20.21

Ideal parallel resonant network.

Practical Circuits


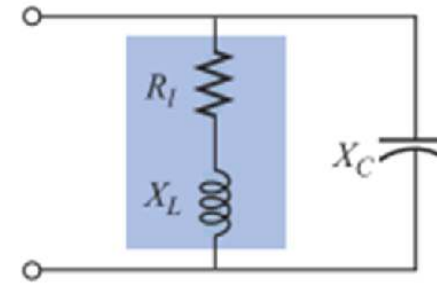


FIG. 20.22

Practical parallel L-C network.

Complex Configuration

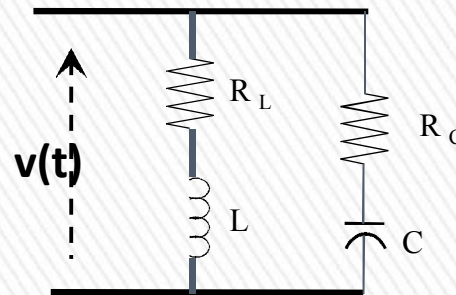

Ideal Parallel Resonance Circuit


The total admittance

$$Y = Y_1 + Y_2 + Y_3$$

$$Y = \frac{1}{R} + \frac{1}{(j\omega L)} + \frac{1}{(-j/\omega C)}$$

$$Y = \frac{1}{R} + \frac{-j}{\omega L} + j\omega C$$
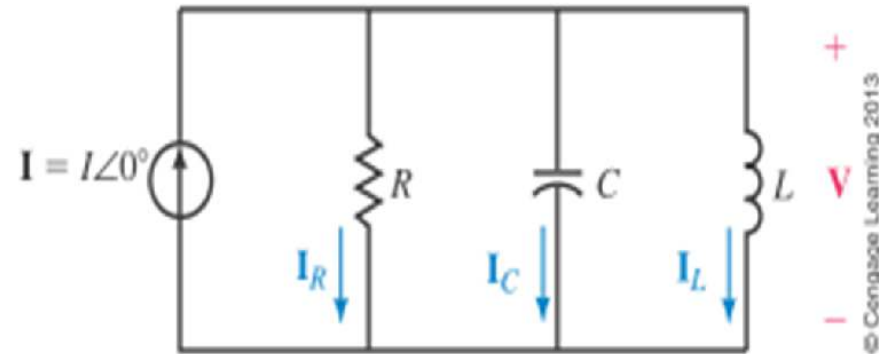
$$Y = \frac{1}{R} + j(\omega C - 1/\omega L)$$



Condition for Ideal Parallel Resonance

Resonance occurs when the imaginary part of Y is zero

$$\omega C - \frac{1}{\omega L} = 0$$

$$X_C = X_L$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \text{ rad/s}$$


Ideal Parallel Resonance Circuit

At parallel resonance:


- ✓ At resonance, the admittance consists only conductance $G = 1/R$.
- ✓ The value of current will be minimum since the total admittance is minimum.
- ✓ The voltage and current are in phase (Power factor is unity).
- ✓ The inductor reactance and capacitor reactance canceled, resulting in a circuit voltage simply determined by Ohm's law as:

$$V = IR = IR \angle 0^\circ$$

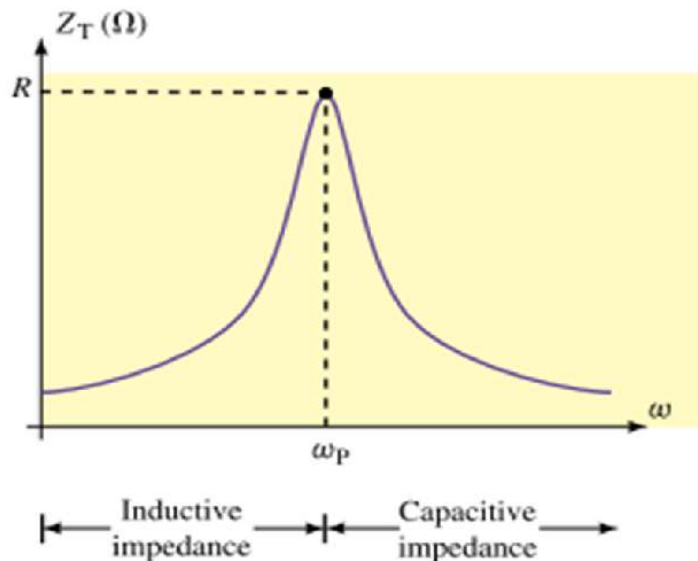- ✓ The frequency response of the impedance of the parallel circuit is shown



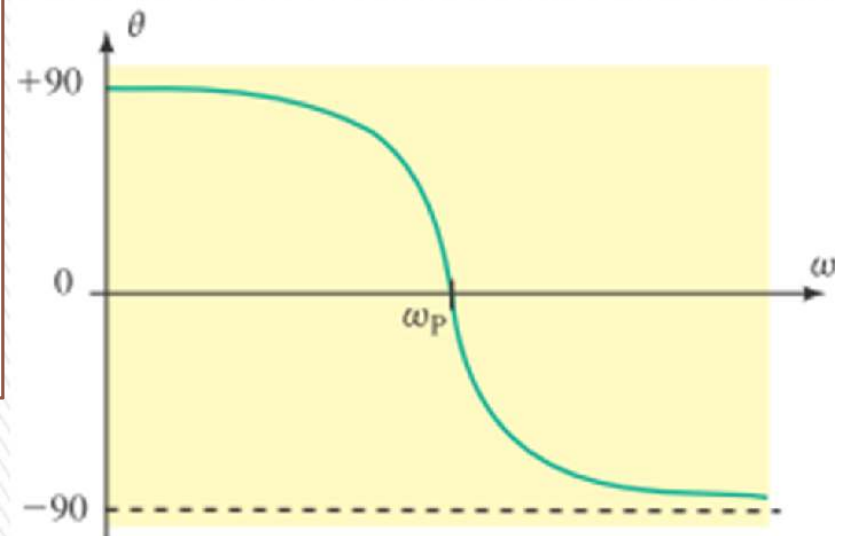exactly
opposite to
that in
series
resonant
circuits,



Ideal Parallel Resonance Circuit

The Q of the parallel circuit is determined from the definition as

$$Q_P = \frac{\text{reactive power}}{\text{average power}} \\ = \frac{V^2/X_L}{V^2/R}$$

$$Q_P = \frac{R}{X_{LP}} = \frac{R}{X_C}$$

Reciprocal of series case

The current

$$I_R = \frac{V}{R} = I$$

$$I_L = \frac{V}{X_L \angle 90^\circ} \\ = \frac{V}{R/Q_P} \angle -90^\circ \\ = Q_P I \angle -90^\circ$$

$$I_C = \frac{V}{X_C \angle -90^\circ} \\ = \frac{V}{R/Q_P} \angle 90^\circ \\ = Q_P I \angle 90^\circ$$

- ✓ The currents through the inductor and the capacitor have the same magnitudes but are 180 out of phase.
- ✓ Notice that the magnitude of current in the reactive elements at resonance is Q times greater than the applied source current.

Ideal Parallel Resonance Circuit

➤ Parallel resonant circuit has same parameters as the series resonant circuit.

Resonance frequency:

$$\omega_p = \frac{1}{\sqrt{LC}} \text{ rad/s}$$

Half-power frequencies:

$$\omega_1 = -\frac{1}{2RC} + \sqrt{\frac{1}{4R^2C^2} + \frac{1}{LC}} \text{ (rad/s)}$$

$$\omega_2 = \frac{1}{2RC} + \sqrt{\frac{1}{4R^2C^2} + \frac{1}{LC}} \text{ (rad/s)}$$

Bandwidth and Q-factor:

$$BW = \omega_2 - \omega_1 = \frac{1}{RC} \text{ (rad/s)}$$


$$BW = \frac{\omega_p}{R(\omega_p C)} = \frac{X_C}{R} \omega_p$$

$$BW = \frac{\omega_p}{Q_p} \text{ (rad/s)}$$

$$Q = \frac{\omega_0}{B} = \omega_0 RC = \frac{R}{\omega_0 L}$$

ملخص قوانين المحاضرة


↓ Ideal circuit

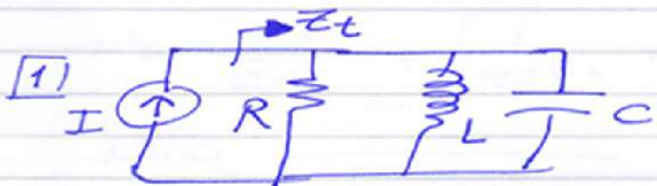

[2] $X_L = X_C$ at Resonance
 $\therefore \omega_p = \frac{1}{\sqrt{LC}}$ rad/s

[3] $Y = \frac{1}{Z} = Y_1 + Y_2 + Y_3$
 $= \frac{1}{R} + j(\omega C - \frac{1}{\omega L})$

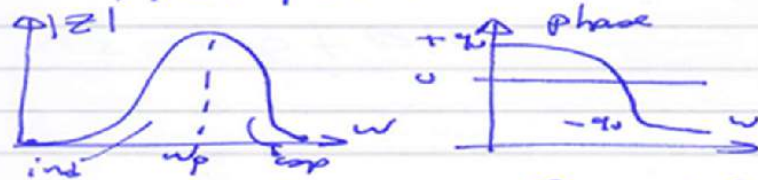[4] at Resonance $G = \frac{1}{R}$
 $\angle V, I$ in phase. \leftarrow admittance



[5] $Q_p = \frac{R}{X_C} = \frac{R}{\cancel{X_L}} = \frac{\omega_p}{BW}$
 $= R/\omega L = \omega RC$

[6] $BW = \omega_2 - \omega_1 = \frac{1}{RC}$ rad/s
 $= \omega_p / Q_p$

[7] $\omega_1 = \frac{-1}{2RC} + \sqrt{\frac{1}{4R^2C^2} + \frac{1}{LC}}$

$\omega_2 = \frac{+1}{2RC} + \sqrt{\frac{1}{4R^2C^2} + \frac{1}{LC}}$ rad/s

Note for Midband


$\omega_1 = \omega_p - BW/2$

$\omega_2 = \omega_p + BW/2$

Example

Example (1)

Consider the circuit shown in Figure

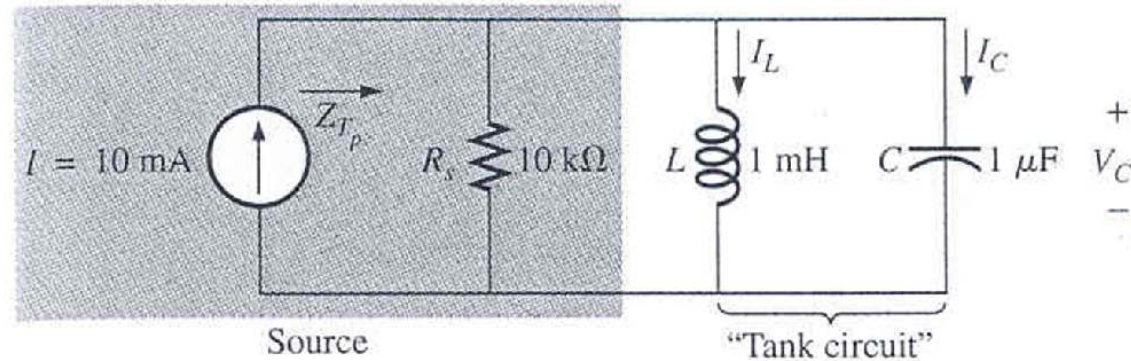

Given the parallel resonant circuit of Fig.16 composed of ideal elements:

- Determine the resonant frequency f_p
- Find the total impedance at resonance
- Calculate the quality factor and bandwidth of the system
- Find the voltage V_C at resonance
- Determine current I_L and I_C
- Calculate the cut-off frequencies f_1 and f_2

Example (1)

Solution

$$\begin{aligned} \text{a)} \quad f_p &= \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{(1 \times 10^{-3})(1 \times 10^{-6})}} \\ &= 5.03 \text{ kHz} \end{aligned}$$

$$\text{b)} \quad Z_T = R_s \square Z_L \square Z_C = R_s = 10 \text{ k}\Omega$$

c)

$$\begin{aligned} Q_p &= \frac{R_s}{X_L} = \frac{R_s}{2\pi f_p L} = \frac{10 \times 10^3}{2\pi(5.03 \times 10^3)(1 \times 10^{-3})} \\ &= 316.41 \end{aligned}$$

$$BW = \frac{f_p}{Q_p} = \frac{5.03 \times 10^3}{316.41} = 15.9 \text{ Hz}$$

Example (1)

d) $V_C = IZ_T = (10 \times 10^{-3})(10 \times 10^3) = 100 \text{ V}$

e)

$$I_L = \frac{V_L}{X_L} = \frac{V_C}{2\pi f_p L} = \frac{100}{2\pi(5.03 \times 10^3)(1 \times 10^{-3})} = \frac{100}{31.6} =$$

$$I_C = \frac{V_C}{X_C} = \frac{100}{31.6} = 3.16$$

f)


$$f_2 = \frac{f_p}{2Q_p} + f_p \sqrt{\left(\frac{1}{2Q_p}\right)^2 + 1}$$
$$= \frac{5030}{2 \times 316.4} + 5030 \sqrt{\left(\frac{1}{2 \times 316.4}\right)^2 + 1} = 5041.9 \text{ Hz}$$

$$f_1 = -\frac{f_p}{2Q_p} + f_p \sqrt{\left(\frac{1}{2Q_p}\right)^2 + 1}$$
$$= 5026.02 \text{ Hz}$$

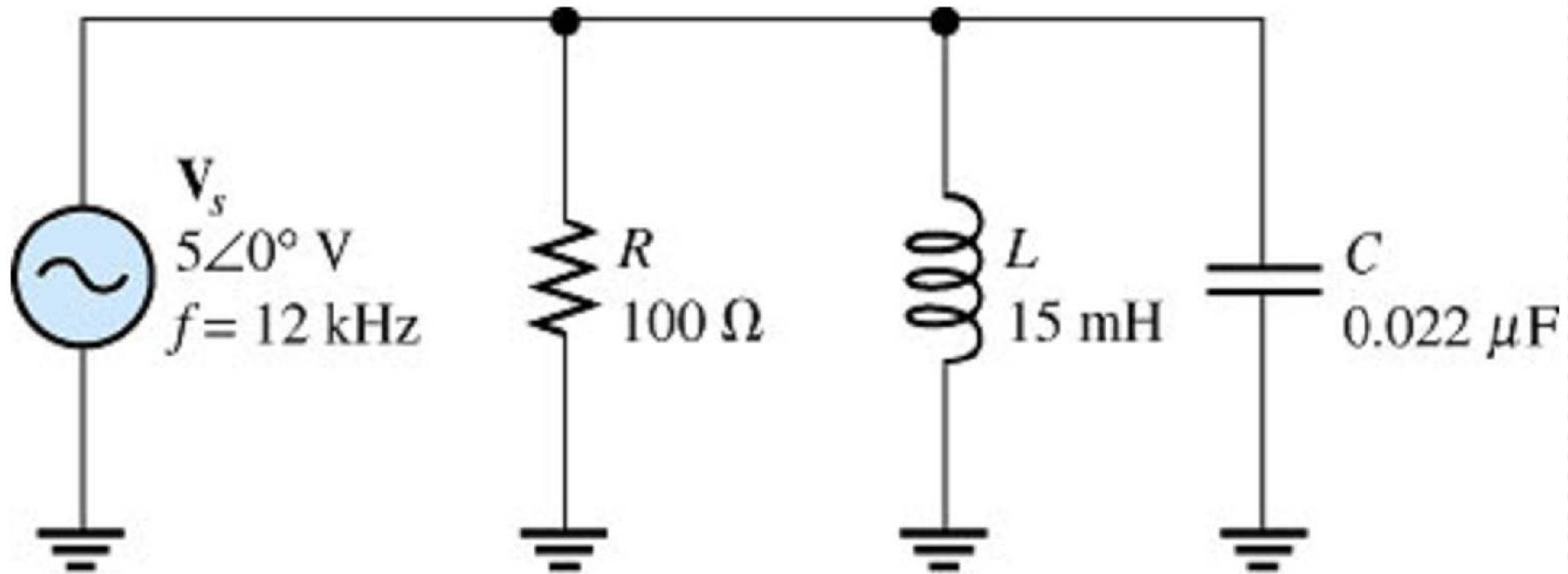Example (2)

Find the following parameters:

- Circuit Impedance in polar form.
- Is the circuit more inductive or more capacitive?
- At what frequency does the circuit change its reactive characteristic from inductive to capacitive or vice-versa?



Example (2)

a). Circuit Impedance in polar form.

$$X_L = 2\pi fL = 2\pi(12 \text{ kHz})(15 \text{ mH}) = 1131 \Omega$$

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi(12 \text{ kHz})(0.022 \mu\text{F})} = 603 \Omega$$

$$\begin{aligned} \mathbf{Z} &= \frac{1}{\frac{1}{100 \angle 0^\circ \Omega} + \frac{1}{1131 \angle 90^\circ \Omega} + \frac{1}{603 \angle -90^\circ \Omega}} \\ &= \frac{1}{10 \text{ mS} - j0.884 \text{ mS} + j1.66 \text{ mS}} = 99.7 \angle -4.43^\circ \Omega \end{aligned}$$


$$Y_T = 10\text{mS} + j0.776\text{mS} = 0.01003\text{S} \angle 4.43^\circ$$

$$Z_T = 1/Y_T = 1/(.01003\text{S} \angle 4.43^\circ) = 99.7\text{ohms} \angle -4.43^\circ$$

Example (2)

b). Since θ of $Z_T = -4.43^\circ$, the circuit is slightly capacitive.

c).

$$X_L < X_C$$

$$2\pi fL < \frac{1}{2\pi fC}$$


$$f^2 < \frac{1}{4\pi^2 LC}$$

$$f < \frac{1}{\sqrt{4\pi^2 LC}}$$

$$f < \frac{1}{2\pi\sqrt{LC}}$$

$$f < \frac{1}{2\pi\sqrt{(15 \text{ mH})(0.022 \mu\text{F})}}$$


$$f < \mathbf{8.76 \text{ kHz}}$$

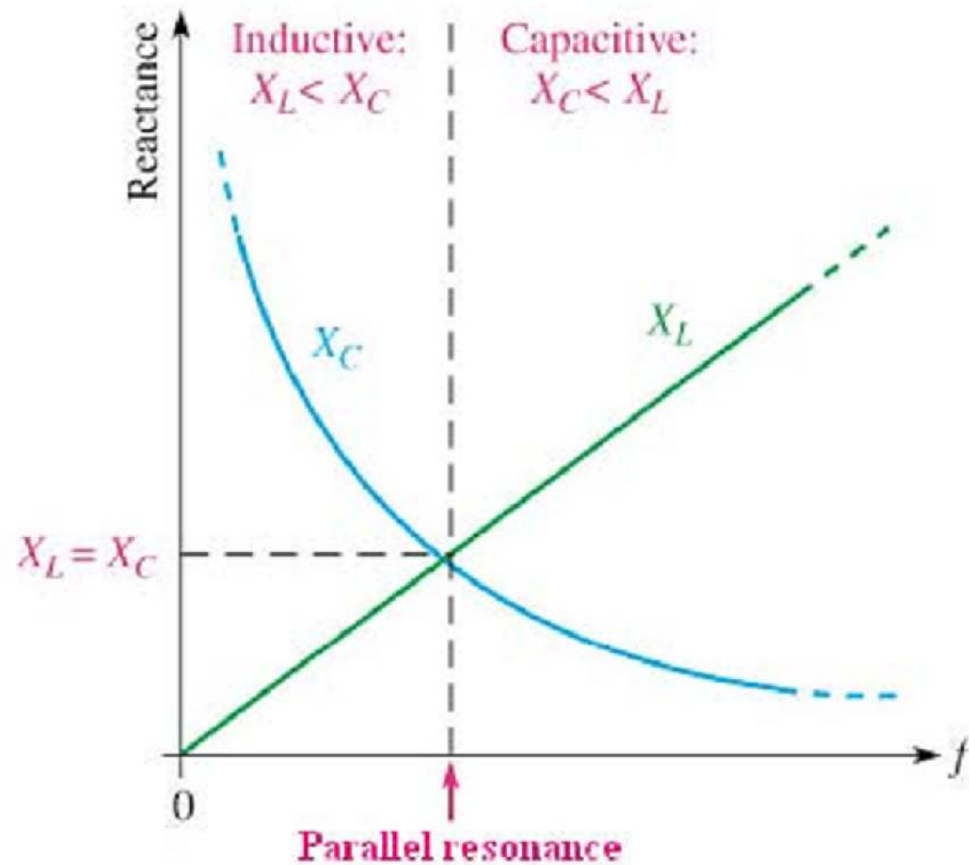

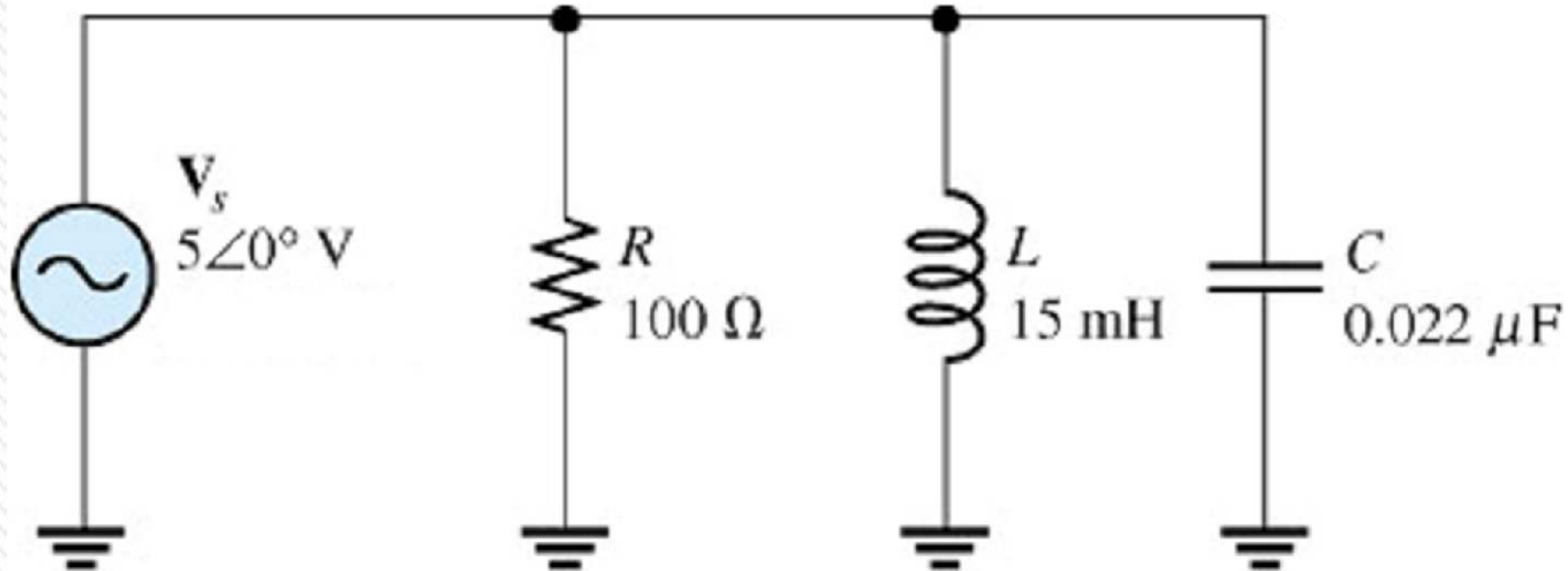Example (3)

Find the following parameters:

- All currents and voltages in polar form if the source frequency is 12KHz.
- The current phasor diagram.



Example (3)

a). All currents and voltages in polar form.

$$\mathbf{I_T} = \frac{\mathbf{V_s}}{\mathbf{Z}} = \frac{5\angle 0^\circ \text{ V}}{99.7\angle -4.43^\circ \Omega} = \mathbf{50.2\angle 4.43^\circ \text{ mA}}$$

$$\mathbf{I_R} = \frac{\mathbf{V_s}}{\mathbf{R}} = \frac{5\angle 0^\circ \text{ V}}{100\angle 0^\circ \Omega} = \mathbf{50\angle 0^\circ \text{ mA}}$$


$$\mathbf{I_L} = \frac{\mathbf{V_s}}{\mathbf{X_L}} = \frac{5\angle 0^\circ \text{ V}}{1131\angle 90^\circ \Omega} = \mathbf{4.42\angle -90^\circ \text{ mA}}$$

$$\mathbf{I_C} = \frac{\mathbf{V_s}}{\mathbf{X_C}} = \frac{5\angle 0^\circ \text{ V}}{603\angle -90^\circ \Omega} = \mathbf{8.29\angle 90^\circ \text{ mA}}$$

$$\mathbf{V_R} = \mathbf{V_L} = \mathbf{V_C} = \mathbf{5\angle 0^\circ \text{ V}}$$


Example (3)

b). Current phasor diagram:

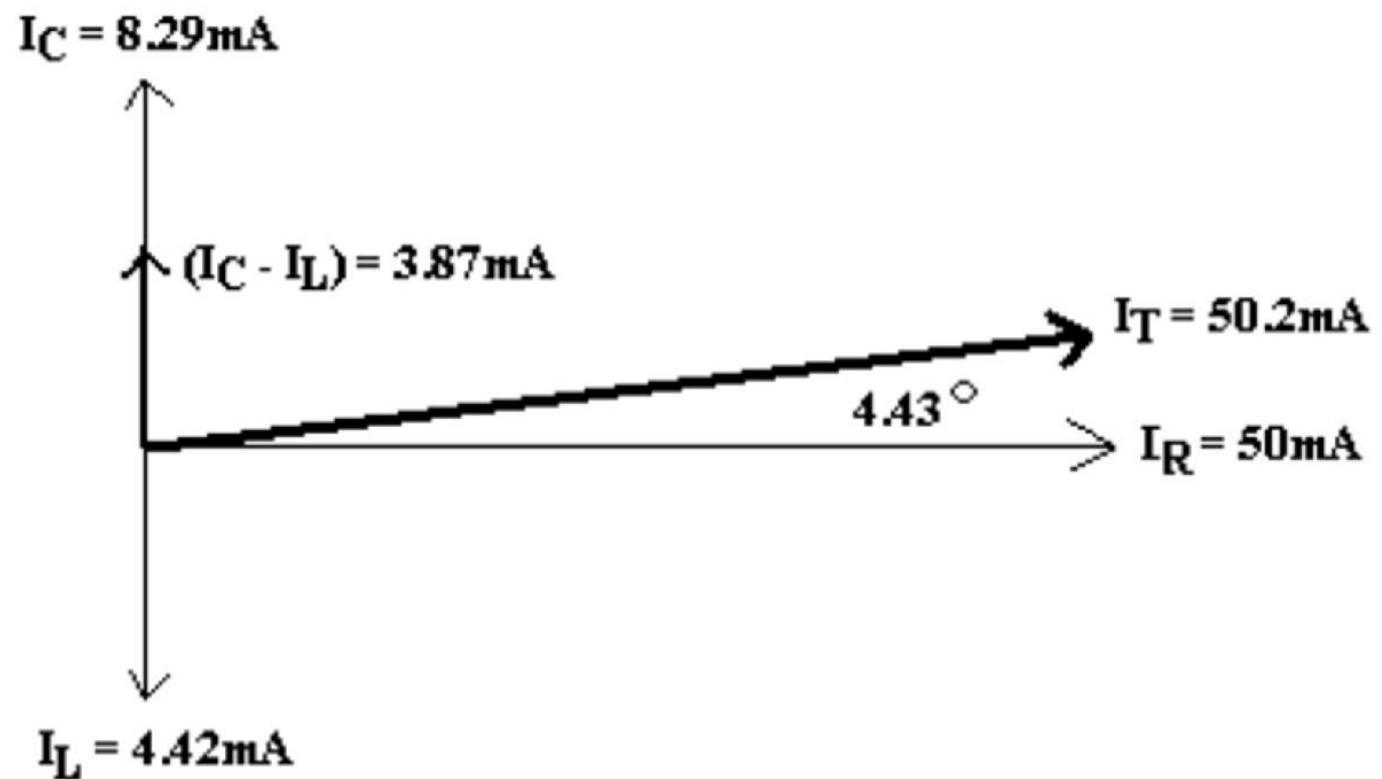

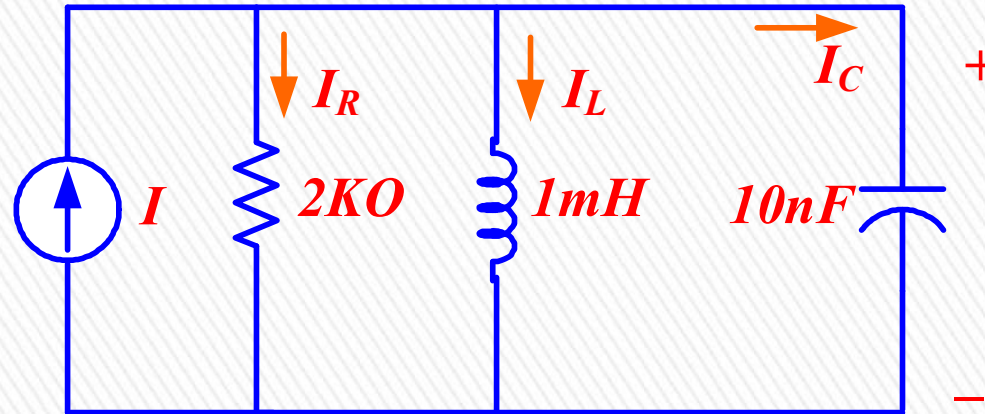Example (4)

Consider the parallel RLC resonant circuit with “ideal” elements given below.



1) The total impedance seen by the source at resonance is

- (a) 0 (b) $2K\Omega$ (c) $2M\Omega$ (d) infinity

Ans: (b)


2) The resonant frequency approximately is

- (a) 10 Hz (b) 100 KHz (c) 160 KHz (d) 500 KHz

Ans: (c)

SELF-TEST

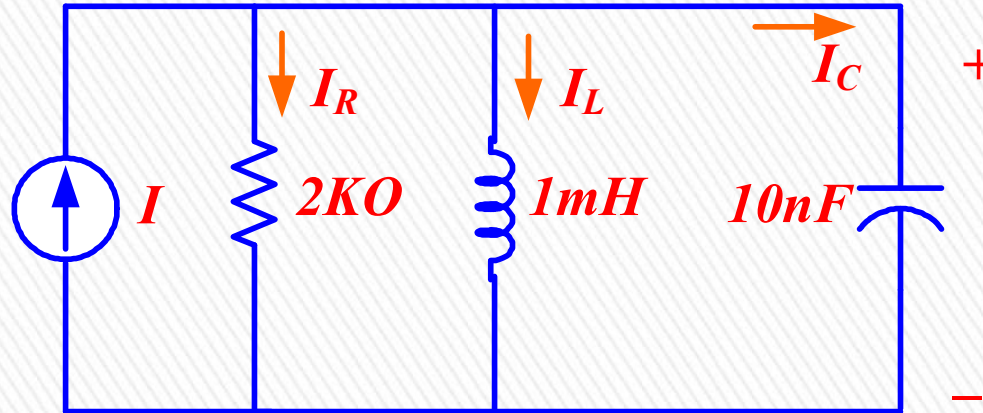Consider the parallel RLC resonant circuit with “ideal” elements given below.



2) The current through the resistance (I_R) at resonance is

- (a) 0 (b) 1 mA (c) 2 mA (d) 10 mA

Ans: (c)

3) 4) The inductor current I_L at resonance is

- a) Equal to I_R
b) Equal to I_C
c) Equal and opposite to I_C
d) Equal to I

Ans: (c)

Thank You

