

Benha University
Faculty Of Engineering at Shoubra



ECE 122
Electrical Circuits (2)(2017/2018)
Lecture (5)
Filters

Prepared By :

Dr. Moataz Elsherbini

motaz.ali@feng.bu.edu.eg

Filters

2

A **filter** is a circuit that is designed to pass signals with desired frequencies and reject or attenuate others.

- The filter can be treated as a networks designed to have frequency selective behavior
- A filter can be used to limit the frequency spectrum of a signal to some specified band of frequencies.
- Filters are the circuits used in radio and TV receivers to allow us to select one desired signal out of a multitude of broadcast signals in the environment

. **Filters** may be classified as either digital or analog.

. **Digital filters** are implemented using a digital computer or special purpose digital hardware.

. **Analog filters** may be classified as either passive or active and are usually implemented with R, L, and C components and operational amplifiers.

Filters

3

Background:

- An active filter is one that, along with R, L, and C components, also contains an energy source, such as that derived from an operational amplifier.
- A passive filter is one that contains only R, L, and C components. It is not necessary that all three be present. L is often omitted (on purpose) from passive filter design because of the size and cost of inductors – and they also carry along an R that must be included in the design.

Passive Analog Filters

4


Background:

Four types of filters - "Ideal"


lowpass




highpass

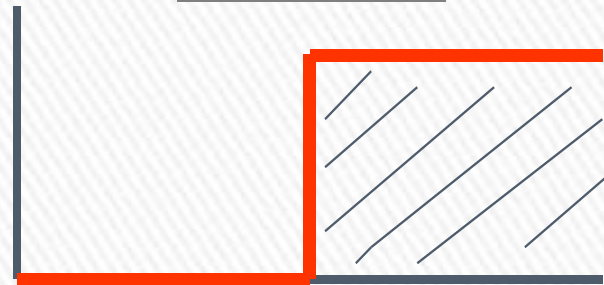

bandpass

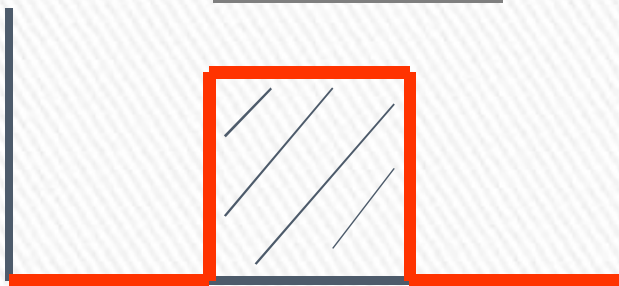

bandstop

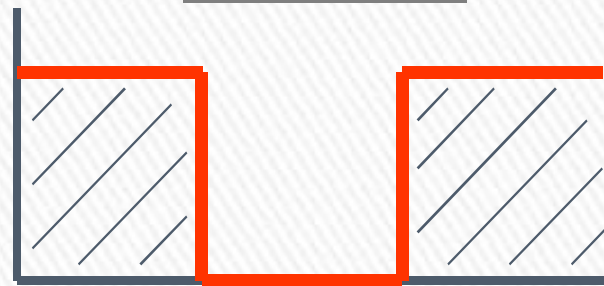


Passive Analog Filters

5


Background:

Realistic Filters:


lowpass

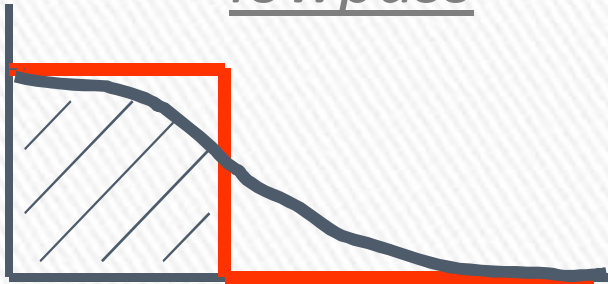


highpass

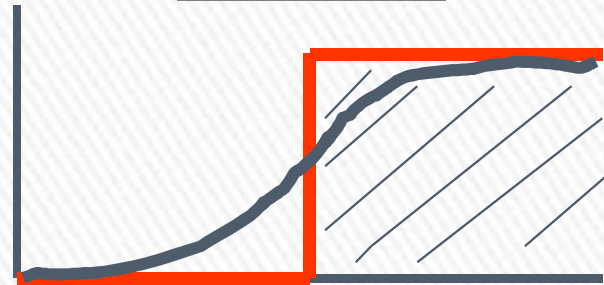

bandpass

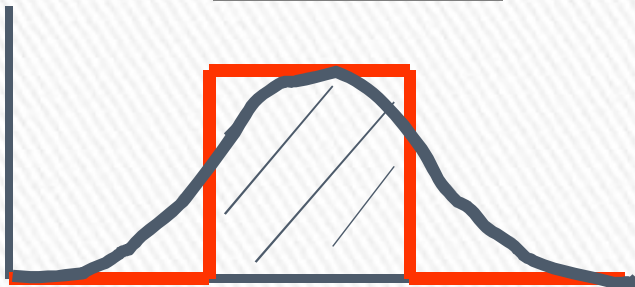

bandstop

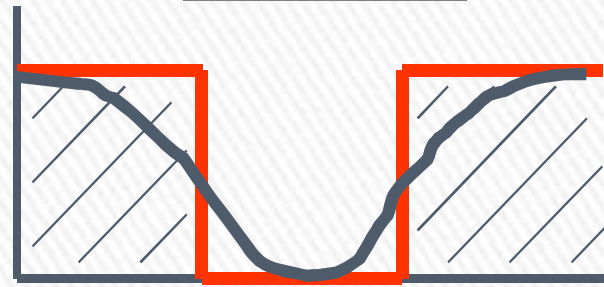

Filters

Important Table for determining the type of the filter from its Transfer function

Summary of the characteristics of ideal filters.

| Type of Filter | $H(0)$ | $H(\infty)$ | $H(\omega_c)$ or $H(\omega_0)$ |
|----------------|--------|-------------|--------------------------------|
| Lowpass | 1 | 0 | $1/\sqrt{2}$ |
| Highpass | 0 | 1 | $1/\sqrt{2}$ |
| Bandpass | 0 | 0 | 1 |
| Bandstop | 1 | 1 | 0 |


Low Pass Filter

Passive Analog Filters


8

Low Pass Filter

Consider the circuit below.

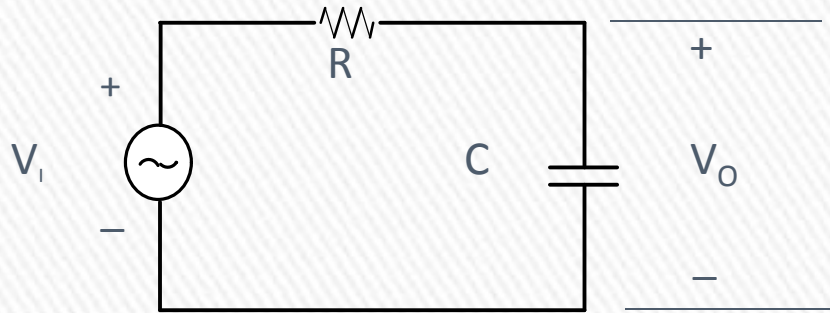

Low pass filter circuit

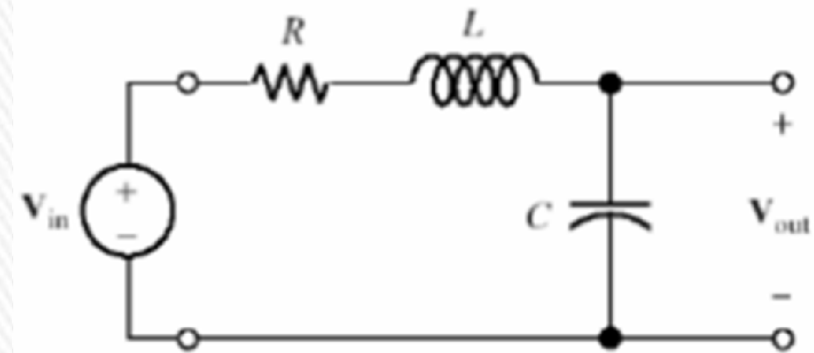


$$\frac{V_o(j\omega)}{V_i(j\omega)} = \frac{1}{R + \frac{1}{j\omega C}} = \frac{1}{1 + j\omega RC}$$

- At low frequency the capacitor is an open circuit ($V_o = V_{in}$)
- At high frequency the capacitor is a short and the inductor is open ($V_o = 0$)

Passive Analog Filters


9

Low Pass Filter

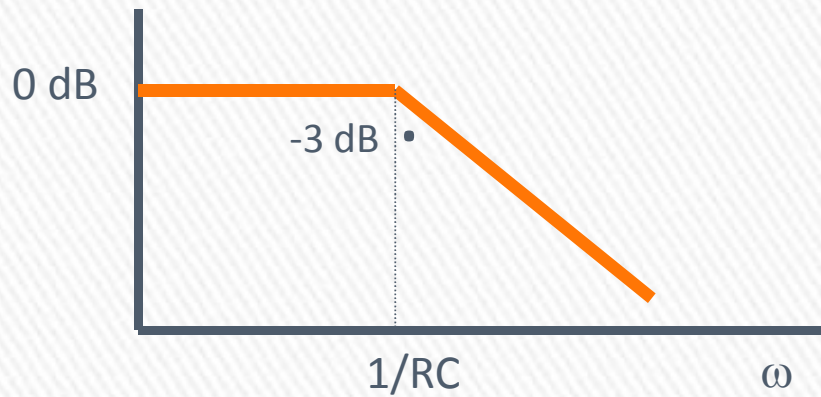

Bode

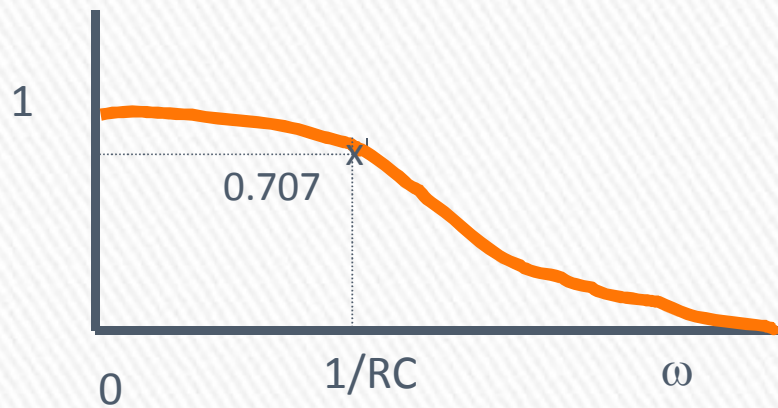Passes low frequencies
Attenuates high frequencies



Linear Plot

Example (1)


10

Show that a series LR circuit is a low-pass filter if the output is taken across the resistor. Calculate the corner frequency f_c if $L = 2 \text{ mH}$ and $R = 10 \text{ k}\Omega$.

$$V_o = V_i \frac{R}{R + j\omega L}$$

$$\frac{V_o}{V_i} = H(f) = \frac{R}{R + j\omega L}$$
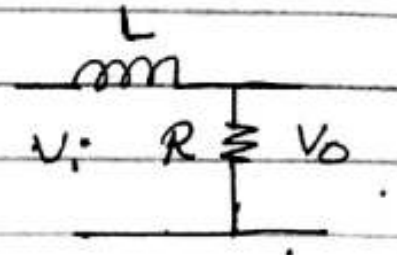
$$\begin{aligned} \text{at } \omega = 0 &\rightarrow H(f) = 1 \\ \omega = \infty &\rightarrow H(f) = 0 \end{aligned} \quad \square \text{ (LPF)}$$



Corner Freq. at $|H(f)| = \frac{1}{\sqrt{2}} H(0)$

$$H(f) = \frac{R}{R + j\omega L} = \frac{1}{1 + j\omega \frac{L}{R}} \quad f = \frac{\omega}{2\pi}$$

$$|H(f)| = \frac{1 \cdot L^0}{\sqrt{1 + \left(\frac{\omega L}{R}\right)^2} L^0} = \frac{1}{\sqrt{1 + \left(\frac{\omega L}{R}\right)^2}} = \frac{1}{\sqrt{2}}$$


$$\therefore 1 + \left(\frac{\omega L}{R}\right)^2 = 2 \quad \text{or } \frac{\omega L}{R} = 1 \quad \therefore \omega = \frac{R}{L}$$

$$\therefore 2\pi f = \frac{R}{L} \quad \text{so } f = \frac{1}{2\pi} \frac{R}{L} = 796 \text{ kHz}$$

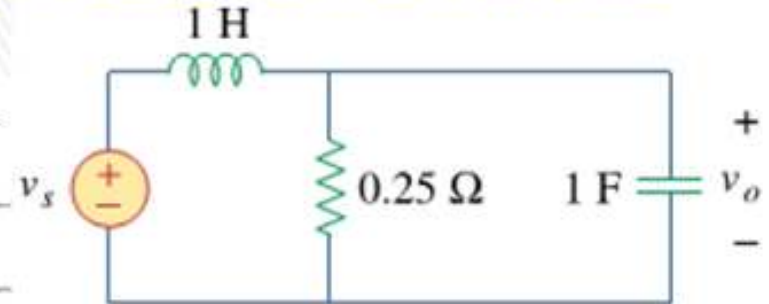Example (2)

11

Find the transfer function V_o/V_s of the circuit in Figure. Show that the circuit is a low-pass filter.



$$H(f) = \frac{R // X_c}{X_L + R // X_c}$$

$$= \frac{R \left(\frac{1}{j\omega C} \right) / \left(R + \frac{1}{j\omega C} \right)}{j\omega L + R \left(\frac{1}{j\omega C} \right)}$$

$$= \frac{R \left(\frac{1}{j\omega C} \right)}{\left(R + \frac{1}{j\omega C} \right) (j\omega L) + R \left(\frac{1}{j\omega C} \right)}$$

$$= \frac{R}{R + (j\omega C)(j\omega L)(R + \frac{1}{j\omega C})}$$

$$= \frac{R}{R + (j\omega C)(j\omega L)(R + \frac{1}{j\omega C})}$$

$$= \frac{R}{R + (j\omega C)(j\omega L)(R + \frac{1}{j\omega C})}$$

$$= \frac{R}{R + (j\omega C)(j\omega L)(R + \frac{1}{j\omega C})}$$

Example (2)

12

$$= \frac{R}{R - \omega^2 LC \left(R + \frac{1}{j\omega C} \right)}$$

$$= \frac{R}{R - \omega^2 LRC - \frac{1}{j}\omega L} = \frac{R}{R - \omega^2 LRC + j\omega L}$$

at $\omega = 0 \rightarrow H(f) = 1$

$\omega = \infty \rightarrow H(f) = 0$

\Rightarrow LPF

Example (3)

Determine the cutoff frequency of the low-pass filter described by

$$H(\omega) = \frac{4}{2 + j\omega 10}$$

Find the gain in dB and phase of $H(\omega)$ at $\omega = 2$ rad/s.

Sol. Cutoff freq calculated when
 $|H(\omega)| = \frac{1}{\sqrt{2}} |H(\omega)|_{\max}$

$$H(0) = \frac{4}{2} = 2 \rightarrow \text{is max}$$

$$H(\infty) = 0$$

~~∴~~ ∴ Cutoff freq calculated when $|H(\omega)| = \frac{1}{\sqrt{2}} (2)$.

$$\text{But } |H(\omega)| = \frac{4 \angle 0}{\sqrt{2^2 + (10\omega)^2} \angle \theta} = \frac{4^2}{\sqrt{4 + 100\omega^2}} = \frac{2}{\sqrt{2}}$$

Example (3)

14

$$\text{vi } \frac{4}{4+100\omega^2} = \frac{1}{2} \quad \text{or } \omega^2 = \frac{4}{100}$$
$$\text{vii } 100\omega^2 + 4 = 8 \quad \boxed{\omega = 0.2} \text{ rad/s}$$

$$H(2) = \frac{4}{2+j20} = \frac{2}{1+j10}$$

$$|H(2)| = \frac{2 \angle 0^\circ}{\sqrt{101} \angle \tan^{-1} 10} = \frac{2 \angle 0^\circ}{\sqrt{101} \angle 84.3^\circ}$$

$$\text{Phase } (0 - \tan^{-1} 10) = \underline{\underline{-84.3^\circ}}$$


$$\text{Mag} = \frac{2}{\sqrt{101}} = 0.199$$

$$\text{Mag dB} = 20 \log 0.199 = -14.023 \text{ dB}$$

High Pass Filter


Passive Analog Filters

High Pass Filter

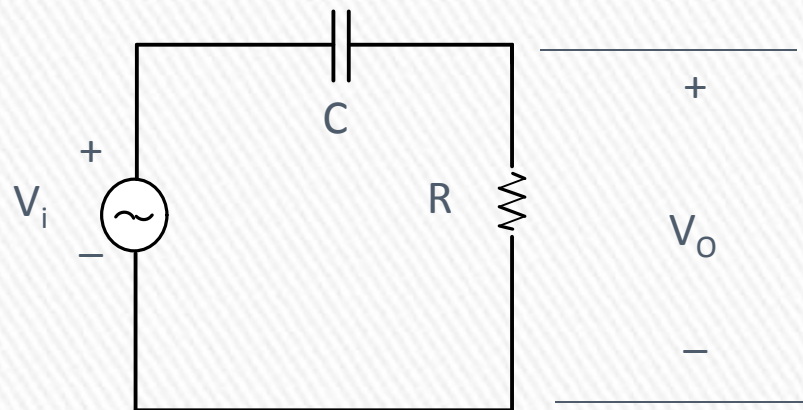

High Pass Filter
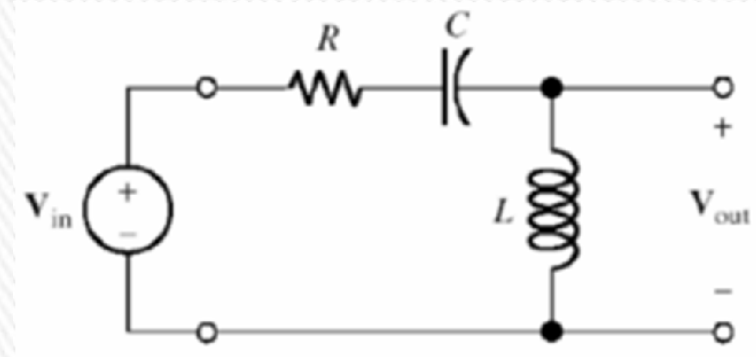
$$\frac{V_o(j\omega)}{V_i(j\omega)} = \frac{R}{R + \frac{1}{j\omega C}} = \frac{j\omega RC}{1 + j\omega RC}$$




- At low frequency the capacitor is an open circuit ($V_o = 0$)
- At high frequency the capacitor is a short and the inductor is open ($V_o = V_{in}$)

Passive Analog Filters

High Pass Filter


Bode

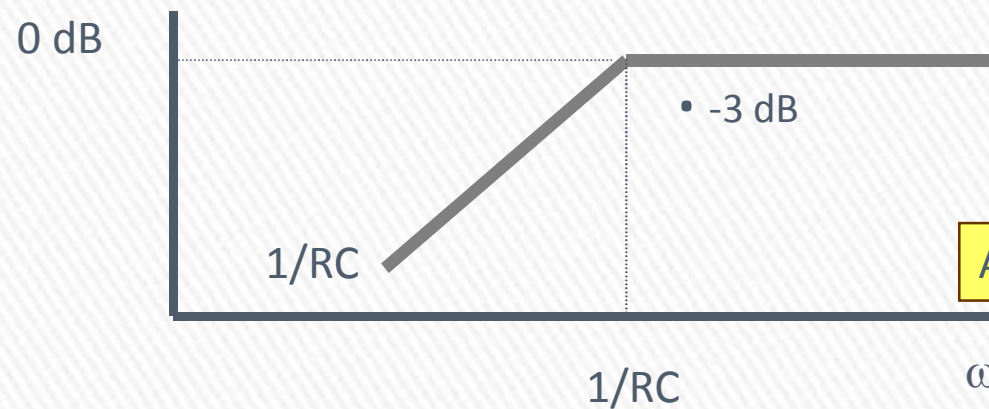

Passes high frequencies

Attenuates low frequencies


Linear

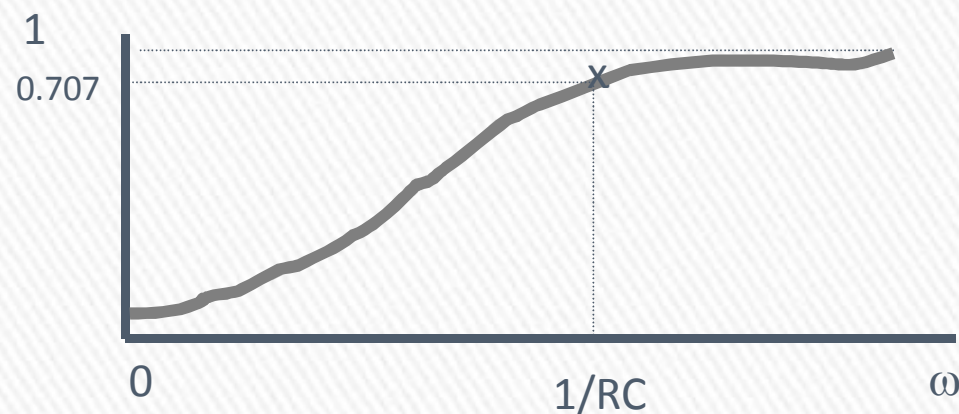

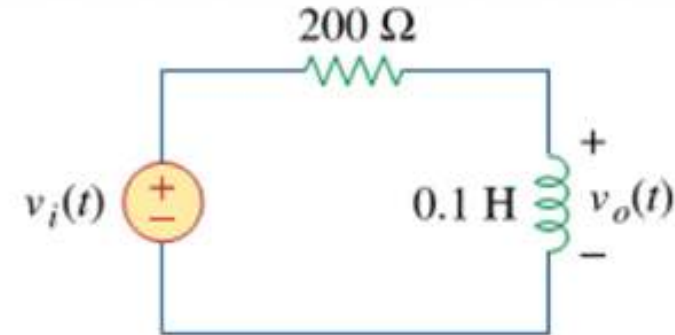Example (4)

18

Determine what type of filter in figure . Calculate the corner frequency f_c



$$V_o = V_i \left(\frac{j\omega L}{R + j\omega L} \right)$$

$$H(f) = \frac{j\omega L}{R + j\omega L} = \frac{1}{1 + \frac{R}{j\omega L}} \quad \text{at } \omega = 0 \rightarrow H(f) = 0$$

$$\omega = \infty \rightarrow H(f) = 1$$

\therefore HPF

$$\rightarrow |H(\omega)| = \frac{1}{\sqrt{2}} \text{ max} = \frac{1}{\sqrt{2}} H(\infty) = \frac{1}{\sqrt{2}}$$

$$= \left| \frac{1}{1 + \frac{R}{j\omega L}} \right| = \left| \frac{1}{1 - j\frac{R}{\omega L}} \right| = \frac{1}{\sqrt{1 + \left(\frac{R}{\omega L}\right)^2}} = \frac{1}{\sqrt{2}}$$

$$\text{or } 1 + \left(\frac{R}{\omega L}\right)^2 = 2 \quad \therefore \left(\frac{R}{\omega L}\right)^2 = 1$$

$$\therefore \omega = \frac{R}{L}, \quad 2\pi f = \frac{R}{L} \rightarrow f = 318.3 \text{ Hz}$$

Example (5)

19

In a high-pass RL filter with a cutoff frequency of 100 kHz, $L = 40$ mH. Find R .


Sol / So it is RL $\omega = \frac{R}{L} = 2\pi f_c$
 $\rightarrow 40\text{mH}$ $\rightarrow 100\text{K}$

$$R = 25.13 \text{ k}\Omega$$

Band Pass Filter

Simple Passive band-pass filter

21

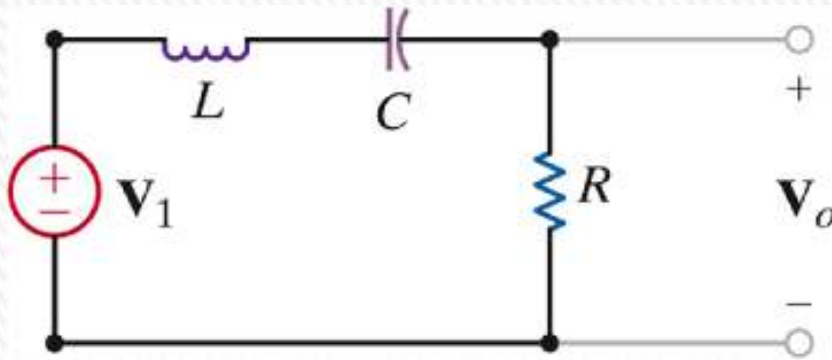

The RLC series resonant circuit provides a bandpass filter when the output is taken off the resistor as shown in Fig.


$$H = \frac{V_0}{V_1} = \frac{R}{R + j\left(\omega L - \frac{1}{\omega C}\right)}$$

Transfer Function

$$|H(\omega)| = \frac{\omega RC}{\sqrt{(\omega RC)^2 + (\omega^2 LC - 1)^2}}$$

$$H\left(\omega = \frac{1}{\sqrt{LC}}\right) = 1$$

$$H(\omega=0) = H(\omega=\infty) = 0$$

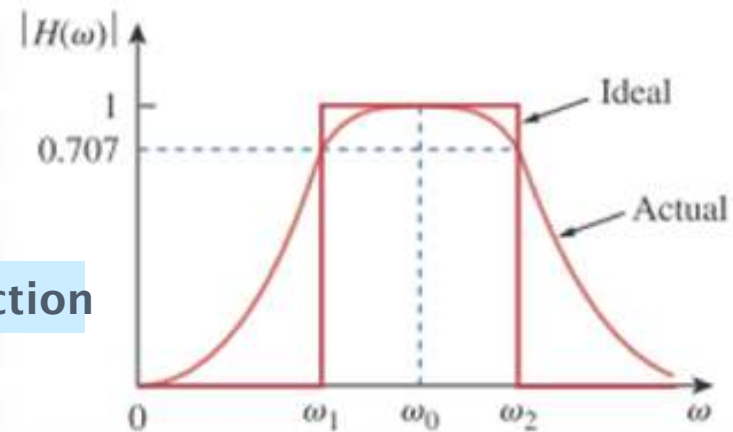

$$\omega_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\omega_2 = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$


$$H(\omega_{LO}) = \frac{1}{\sqrt{2}} = M(\omega_{HI})$$

$$BW = \omega_{HI} - \omega_{LO} = \frac{R}{L}$$


Band Stop Filter (reject) (notch)

Simple Passive band-stop filter

23

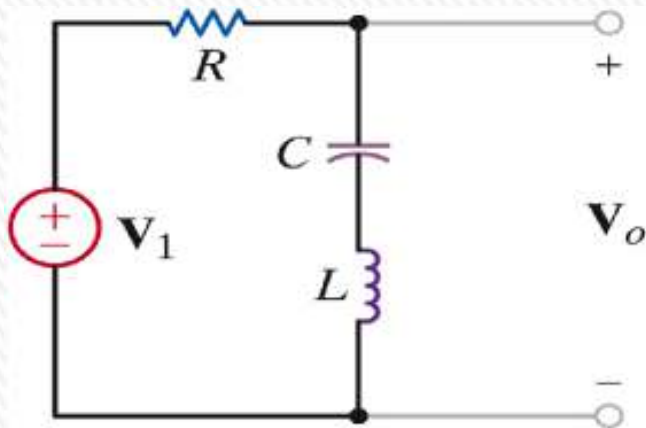

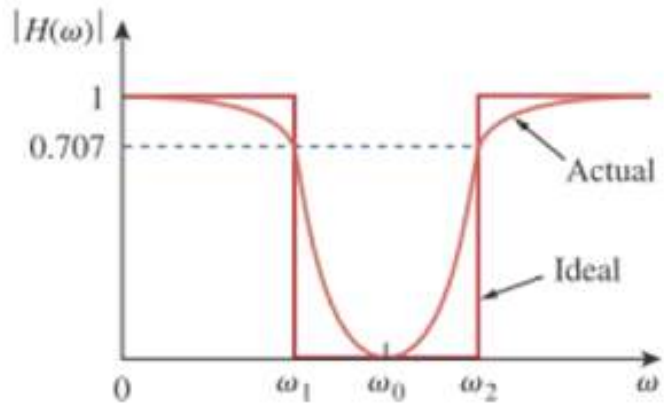- The RLC series resonant circuit provides a band-stop filter when the output is taken off the LC as shown in Fig.
- A filter that prevents a band of frequencies between two designated values
- It is also known as a band-stop, band-reject, or notch filter.



BW = Bandwidth of rejection

$$\mathbf{H(0) = 1, H(\infty) = 1.}$$

$$\mathbf{H(\omega) = \frac{V_o}{V_i} = \frac{j(\omega L - 1/\omega C)}{R + j(\omega L - 1/\omega C)}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \Rightarrow j\left(\omega_0 L - \frac{1}{\omega_0 C}\right) = 0$$

at $\omega = 0$ the capacitor acts as open circuit $\Rightarrow V_0 = V_1$

at $\omega = \infty$ the inductor acts as open circuit $\Rightarrow V_0 = V_1$

ω_1, ω_2 are determined as in the band - pass filter

Active Filters


Passive filters have several limitations:

1. Cannot generate gains greater than one
2. Loading effect makes them difficult to interconnect
3. Use of inductance makes them difficult to handle


➤ Using operational amplifiers one can design all basic filters, and more, with only resistors and capacitors

Remember


Filter types Remember

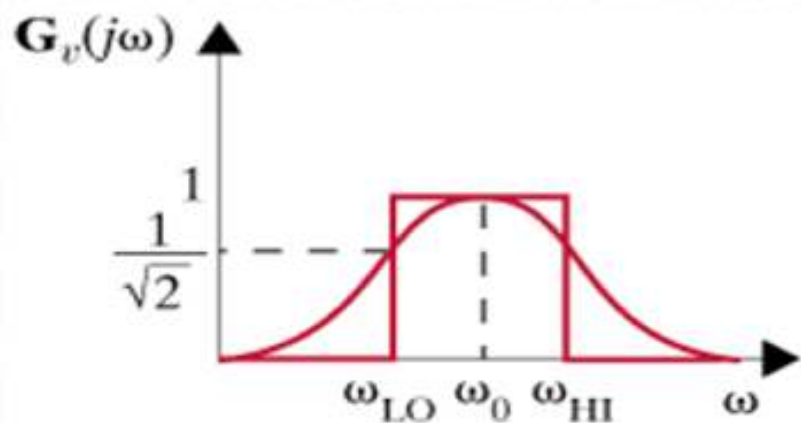


Band-pass filter

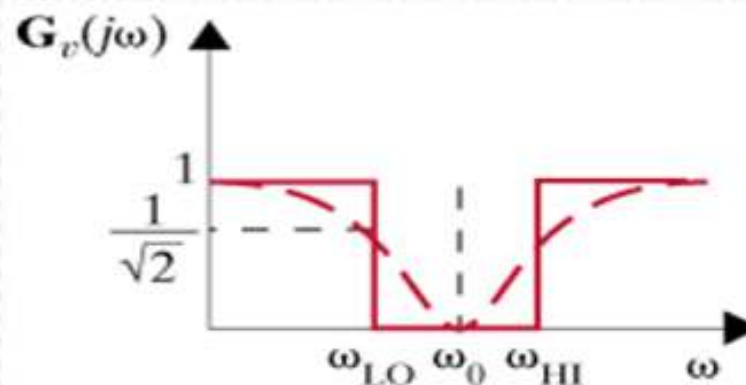

Band-reject filter

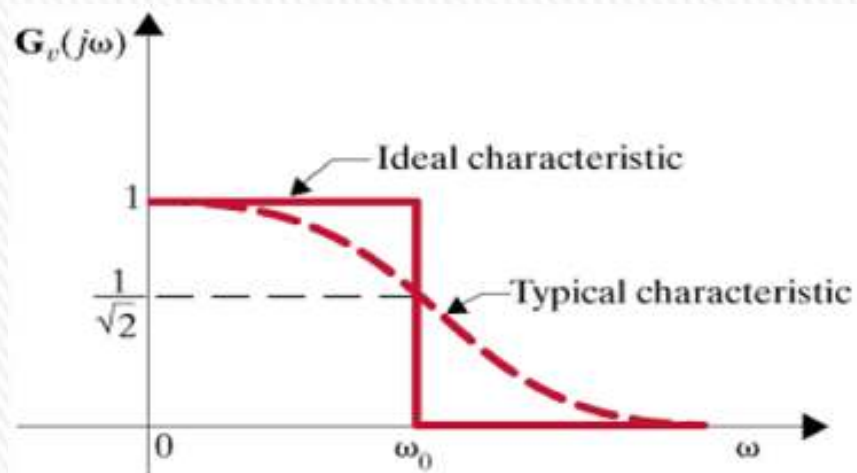

Low-pass filter

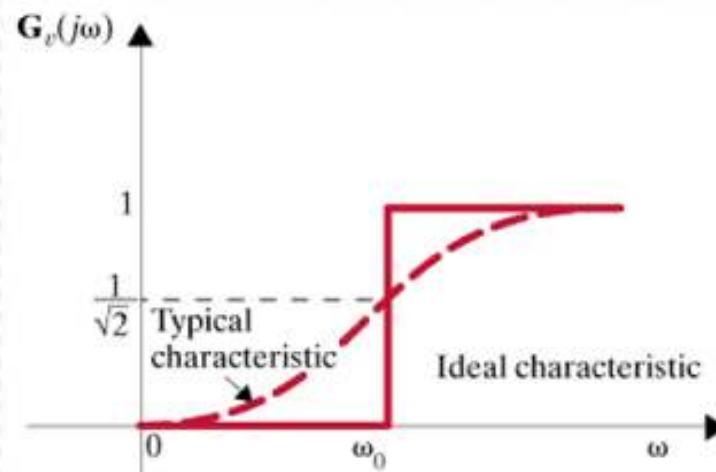

High-pass filter

Thank You

