

AC part (03)

1

AC Circuit Theory Techniques

Node
Mesh
Delta-Y
Source transformation
Superposition
Thevenin's & Norton's


حل دوائر التيار المتردد AC
Components Sources

1) Don't forget $Z = \frac{V}{I} = \text{magnitude} \angle \text{Phase}$

مقدار و زاویه

Power factor = $\cos[\text{phase}]$ \cos زاویه Z و \cos زاویه Z PF

EX(1)

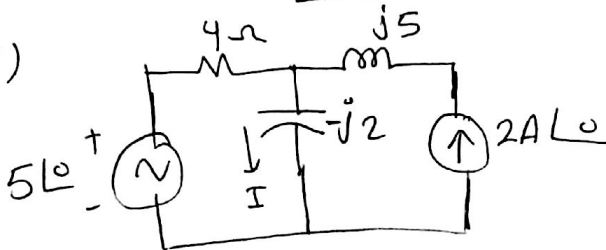

Determine I using

- * - Node
- * - Mesh
- * - Superposition
- * - Thevenin's
- * - Source transformation

1) Node method

حل دوائر التيار المتردد AC

$$\infty \frac{N_1 - 5\angle 0^\circ}{4} + \frac{N_1}{-j2} + 2A\angle 0^\circ = 0$$

$$\infty \frac{V_1}{4} - \frac{5}{4} - \left[\frac{V_1}{2j} \right] - 2 = 0$$

$$\frac{V_1}{4} - \frac{5}{4} - \left[\frac{V_1}{2j} \cdot \frac{j}{j} \right] - 2 = 0$$

$$\rightarrow \frac{V_1}{4} - \frac{5}{4} + \frac{jV_1}{2} - 2 = 0$$

$$N_1 \left[\frac{1}{4} + \frac{j}{2} \right] = \frac{5}{4} + 2 = \frac{13}{4}$$


$$V_1 = \frac{13/4}{\frac{1}{4} + j/2} = \frac{13}{1 + 2j} = \frac{13\angle 0^\circ}{\sqrt{1+4} \angle \tan^{-1} 2} = \frac{13\angle 0^\circ}{2.23 \angle 63.43^\circ}$$

$$V_1 = 5.81 \angle -63.43^\circ$$

$$\infty I = \frac{V_1}{-j2} = \frac{5.81 \angle -63.43^\circ}{2 \angle -90^\circ} = 2.9 \angle 26.56^\circ \text{ A}$$

(2)

2- Mesh Poop

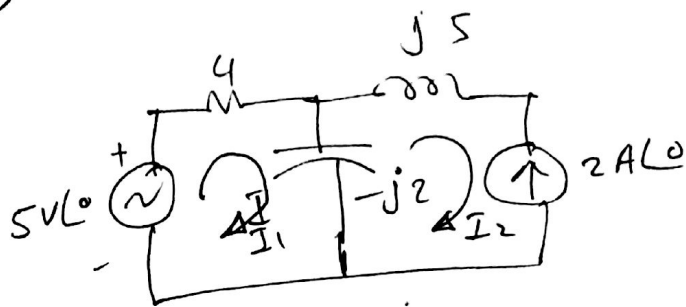

loop 1

$$5 \angle 0 = (4 - j2)I_1 - (-j2I_2)$$

$$\text{or } 5 \angle 0 = (4 - j2)\underline{I_1} + 2j\underline{I_2} \rightarrow (1)$$

loop 2

$$\underline{I_2} = -2 \angle 0$$

منس محتاج معادله

substitute in (1) or $5 = (4 - j2)I_1 + 2j \times (-2)$

$$5 = [4 - 2j]I_1 - 4j \rightarrow (5 + 4j) = (4 - 2j)I_1$$

$$\therefore I_1 = \frac{5 + 4j}{4 - 2j} = \frac{\sqrt{25+16} \angle \tan^{-1} \frac{4}{5}}{\sqrt{16+4} \angle \tan^{-1} \frac{-2}{4}} = \frac{6.4 \angle 38.66}{4.47 \angle -26.56}$$

$$I_1 = 1.43 \angle 65.22$$

∴ def $I = I_1 - I_2 = 1.43 \angle 65.22 - (-2)$



$$= (1.43 \cos 65.22) + j(1.43 \sin 65.22) + 2$$

$$I = 2.6 + 1.3j = 2.9 \angle 26.56^\circ$$

③ Superposition

[3]

① 1st step open circuit current source

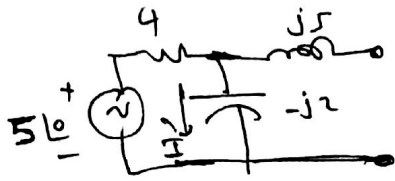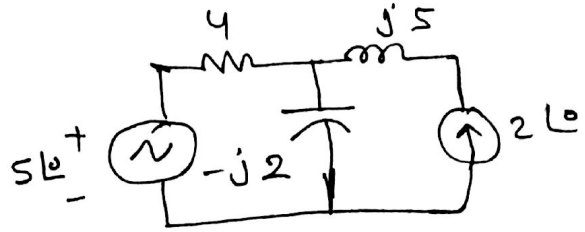

ثم نطبق اى نظرية قدرية لحساب التيار I ونصوب I'



∴ open circuit ∠ 2∠0°

الدائرة تكافئ دائرة مقصورة
تقريباً

$$\therefore I' = \frac{5\angle 0^\circ}{4 - 2j} = \frac{5\angle 0^\circ}{4.47 \angle -26.57^\circ} = 1.118 \angle 26.57^\circ$$

② 2nd step S.C voltage source

using current divider to calc. I''

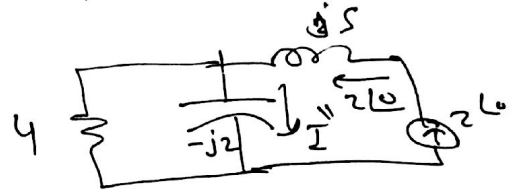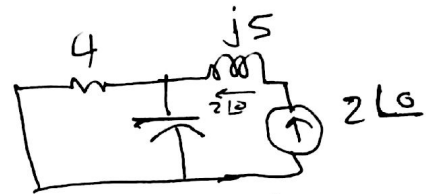

$$I'' = \frac{I_{total} \times 4}{4 - 2j} = \frac{2 \times 4\angle 0^\circ}{4 - 2j}$$


$$= \frac{8\angle 0^\circ}{4.47 \angle -26.57^\circ} = 1.789 \angle 26.57^\circ$$

$$\therefore I = I' + I'' = 1.118 \angle 26.57^\circ + 1.789 \angle 26.57^\circ$$


$$= 2.9 \angle 26.56^\circ$$

(4)


4) Source transformation

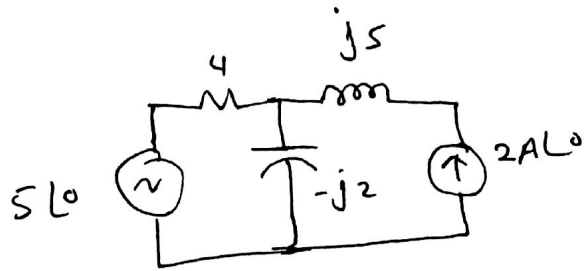

1st equivalent circuit

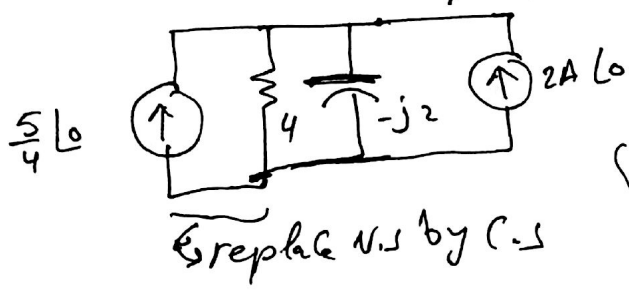

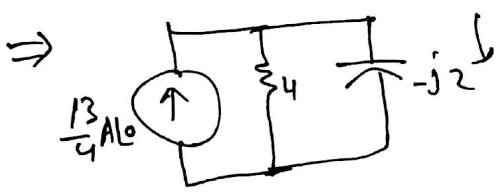
coil removed (has no effect with independent source)
 series element independent voltage source
 element independent voltage source
 independent voltage source



$$I = \frac{\frac{13}{4} L_0 \times 4}{4 - j2} = \frac{13 L_0}{4.47 \angle -26.56^\circ} = 2.9 \angle 26.56^\circ$$


5) Thevenin's || open circuit the capacitor

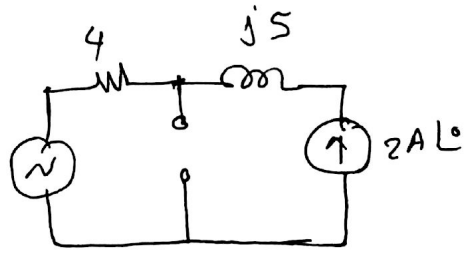(2) calc. V_{th} , Z_{th} across cap (المقاومة)




(a) to calc Z_{th} (o.c current source, s.c voltage source)

j5 cancelled open - C.C

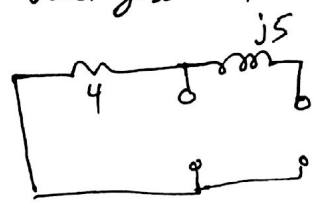


$Z_{th} = 4 \Omega$ only

(b) calc. V_{th} using KVL

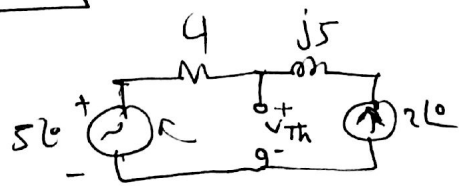

loop 1 $5 - V_{th} = 4I$
 loop 2 $V_{th} = 2A$ $I = -2L_0$
 $\therefore 5 - V_{th} = 4 \times -2$
 $V_{th} = 13 L_0$

(5)

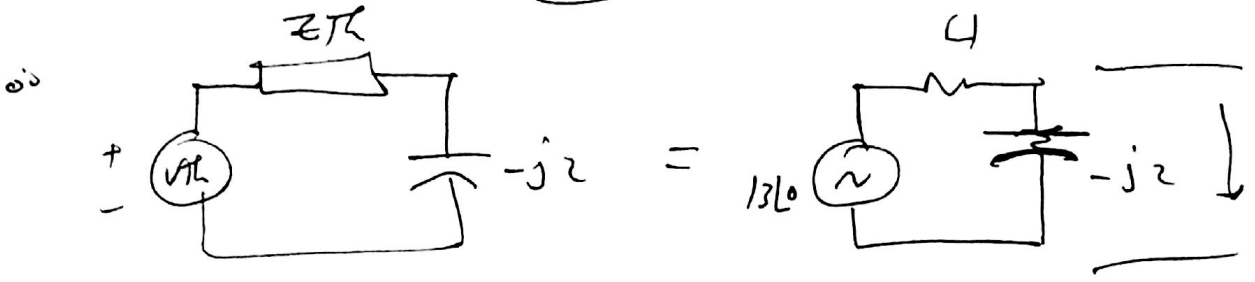

$$I = \frac{13\angle 0}{4 - j2} = 2.9 \angle 26.56$$

لا يمكن استخدام A-Y، بل يجب أن نأخذها من حيث هي صورة فلكل وقتية
المكافئ المراد حساب التيارية

فصل AC للرجوع * المحاضرة القادمة
DC & AC

Good Luck!

Quiz

$$2\angle 30 + j2\sin 30$$

لا حظ لو قابليت معادلتك (Meshloop) في

$$2\angle 30 = (2+j)I_1 + (3-2j)I_2$$

$$4\angle 60 + j4\sin 60$$

$$4\angle 60 = (5-2j)I_1 + (4)I_2$$

كلها انا !! الى قسم الهندسة الكهربائية، صورة الجواب
Complex source

$$\Delta = \begin{vmatrix} 2+j & 3-2j \\ 5-2j & 4 \end{vmatrix} = \text{نقلا} \quad \Delta_1 = \begin{vmatrix} 2\angle 30 + j2\sin 30 & 3-2j \\ 4\angle 60 + j4\sin 60 & 4 \end{vmatrix} = \text{نقلا}$$

$$\Delta_2 = \begin{vmatrix} 2+j & 2\angle 30 + j2\sin 30 \\ 5-2j & 4\angle 60 + j4\sin 60 \end{vmatrix} = \text{نقلا}$$

$$\therefore I_1 = \frac{\Delta_1}{\Delta} \quad I_2 = \frac{\Delta_2}{\Delta}$$