

Problems (AC)

11 A 200V, 50Hz supply is connected to coil of inductance (0.15H) connected in series with 32-Ω resistance

- Determine
- ① impedance of the circuit.
  - ② current & circuit phase angle.
  - ③ Pd (potential difference) ~~Power dissipated~~ across 32-Ω.
  - ④ " " " " coil.

← Solution →




①  $Z = R + j\omega L$   
 $= 32 + j(2\pi \times 50 \times 0.15)$   
 $= 32 + j\frac{47.1}{X_L} = 57 \angle 55.81^\circ$

②  $I = \frac{V}{Z} = \frac{200 \angle 0}{57 \angle 55.81} = 3.51 \angle -55.81^\circ$

③ Pd<sub>32Ω</sub> =  $V_R = IR = (3.51 \angle -55.81)(32 \angle 0)$   
 $= 112 \angle -55.81^\circ$

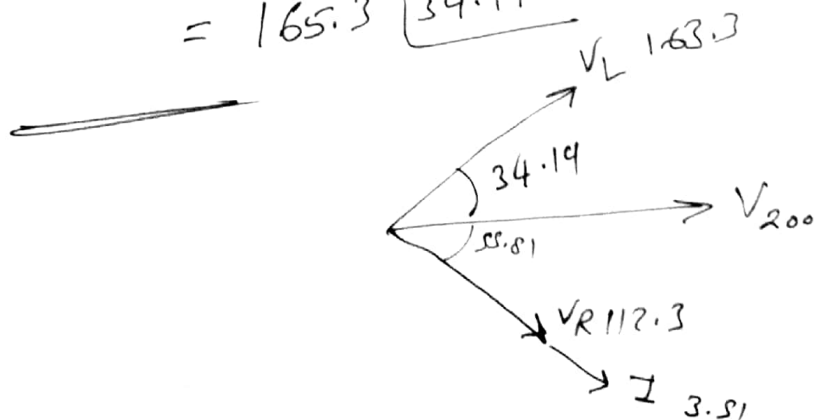④ Pd<sub>coil</sub> =  $V_L = I X_L = (3.51 \angle -55.81)(47.1 \angle 90)$   
 $= 165.3 \angle 34.19^\circ$




2 (جوابی) (4) (L, R, C)

if  $v = 2 \sin(100t + 245^\circ)$   
 $i = \cos(100t + 10^\circ)$

what type of impedance in box

sol

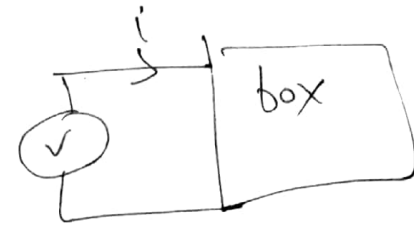


$$Z = \frac{v}{I} = \frac{2 \angle 45}{1 \angle 100} = 2 \angle -55$$

$$= 2 \cos 55 - j 2 \sin 55$$

capacitor  $\frac{1}{\omega C} = 2 \sin 55$   
 $C = \frac{1}{100 \times 2 \sin 55}$

7 find Z of  $N_a = 14 - j2$

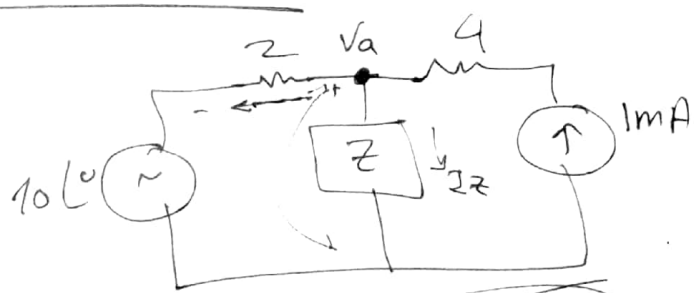

$$N_a - 10 \Omega = V_z$$

$$14 - j2 - 10 = V_z = 4 - j2$$

$$\therefore i_z = \frac{4 - j2}{2} = 2 - j1$$

$$i_z + i_2 = 1 \text{ mA}$$

$$i_z + 2 - j1 = 1 \times 10^{-3}$$

$$i_z = j1 + 2 + 1 \times 10^{-3}$$

$$\therefore \frac{N_a}{I_z} = \frac{14 - j2}{(2 + 0.001) + j}$$

فردی  
 $N_a$  و  $Z$  و  $i_z$   
 $i_z = 2 - j1$   
 $i_2 = 1 \text{ mA}$   
 $N_z = 2 + 0.001 + j$

$\frac{14 - j2}{(2 + 0.001) + j} = \frac{14 - j2}{2 + j} = 5 - 0j$   
C R  
Resistor

2

Q1 For the circuit shown determine  $Z_2$

← solution →

$$Z_{total} = \frac{V}{I} = \frac{70 \angle 30^\circ}{3.5 \angle -20^\circ}$$

$$= 20 \angle 50^\circ$$

$$= 12.86 + j15.32 \Omega$$


but

$$Z = Z_2 + \frac{4.36 - j2.1}{R - j\frac{1}{\omega C}}$$

$$\therefore 12.86 + j15.32 = Z_2 + 4.36 - j2.1$$

$$Z_2 = 8.5 + j17.42 \quad \text{or} \quad 19.38 \angle 63.99^\circ$$

$$I = 3.5 \angle -20^\circ$$

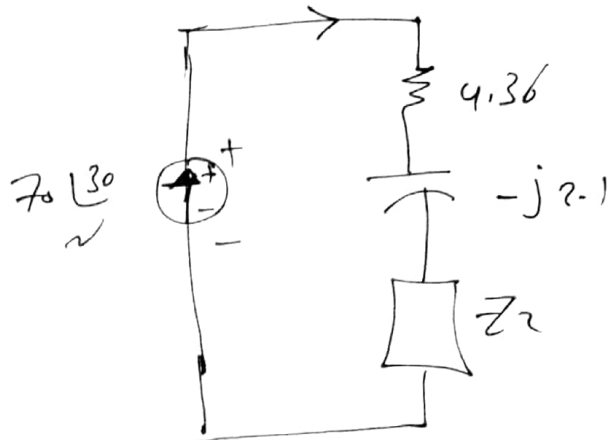

Q2 A series RL branch with  $R_1 = 10 \Omega$ ,  $X_L = 10 \Omega$  connected in parallel with series RC branch of  $R_2 = 40 \Omega$ ,  $X_C = 10 \Omega$ . The combination is connected to a 250V (rms) supply, 50Hz, find total impedance of circuit & total current (Magnitude & Phase)

$$Y_1 = \frac{1}{10 + j10} = \frac{10 - j10}{200}$$


$$= \frac{1}{20} - \frac{j}{20} = 0.05 - j0.05$$

$$Y_2 = \frac{1}{40 - j10} = \frac{40 + j10}{1600 + 100} = 0.0231 + j0.0058$$

$$Y_t = Y_1 + Y_2 = 0.0731 - j0.0442$$

$$= 0.0857 \angle -30.9^\circ$$
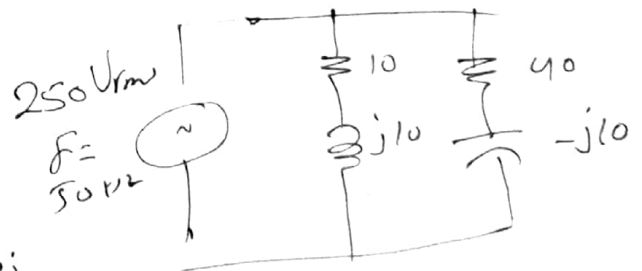
$$I = \frac{V}{Z_{eq}} = \frac{250\sqrt{2} \angle 0^\circ}{11.668 \angle 30.9^\circ} = 30.3 \angle -30.9^\circ$$



$$Z = \frac{1}{Y} = \frac{1}{0.0857 \angle -30.9^\circ} = 11.668 \angle 30.9^\circ$$

$$= 10.1 + j5.995$$

$$\text{or } 11.42 \angle 30.9^\circ \text{ rms}$$

③  
 [6] a series R-C circuit connected with AC supply with  $100\text{V}_{\text{rms}}$  & phase  $45^\circ$  at  $50\text{Hz}$ , the magnitude of capacitive element is ~~double~~ <sup>half</sup> of the pure element, find Power factor

← sol →

$$Z = R - j\left(\frac{1}{\omega C}\right)$$

$$\text{Pf} = \cos \angle \text{phase angle of } Z$$

$$\left|\frac{1}{\omega C}\right| = \frac{1}{2} |R| \quad \therefore \omega RC = \frac{1}{2}$$

$$\text{Pf} = \cos \left[ \tan^{-1} \frac{\text{Im}g}{\text{Real}} \right] = \cos \left[ \tan^{-1} \frac{-1}{\omega RC} \right]$$


$$= \cos \left[ \tan^{-1} \frac{-1}{\frac{1}{2}} \right] = 0.8944$$

[7] determine  $I, I_1, I_2$

$$Z_t = 5 + \frac{(8)(j6)}{8+j6} =$$

$$= 5 + \frac{48j[8-j6]}{(8)^2 + (6)^2}$$
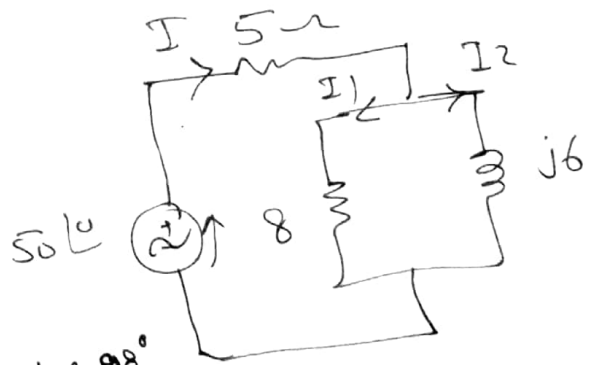
$$= 7.88 + j3.84 \Omega \text{ or } 8.77 \angle 25.98^\circ$$



$$I = \frac{V}{Z_t} = \frac{50 \angle 0^\circ}{8.77 \angle 25.98^\circ} = 5.7 \angle -25.98^\circ$$

$$I_1 = I \left( \frac{j6}{8+j6} \right) = 5.7 \angle -25.98^\circ \times \left[ \frac{6 \angle 90^\circ}{10 \angle 36.87^\circ} \right] = 3.42 \angle 77.15^\circ$$

$$I_2 = I \left( \frac{8}{8+j6} \right) = 5.7 \angle -25.98^\circ \times \left( \frac{8 \angle 0^\circ}{10 \angle 36.87^\circ} \right) = 4.56 \angle -62.85^\circ$$

8) For the Parallel network shown find I (5)

$$I = \frac{V}{Z} = VY = 40 \angle 0^\circ Y$$

$$Y = Y_1 + Y_2 + Y_3$$


$$= \frac{1}{5 + j12} + \frac{1}{3 - j4} + \frac{1}{8}$$

$$= \frac{5 - j12}{5^2 + 12^2} + \frac{3 + j4}{3^2 + 4^2} + \frac{1}{8}$$

$$= (0.0296 - j0.07) + (0.12 + j0.16) + 0.125$$


$$= 0.274 + j0.089 = 0.28 \angle 17.9^\circ$$
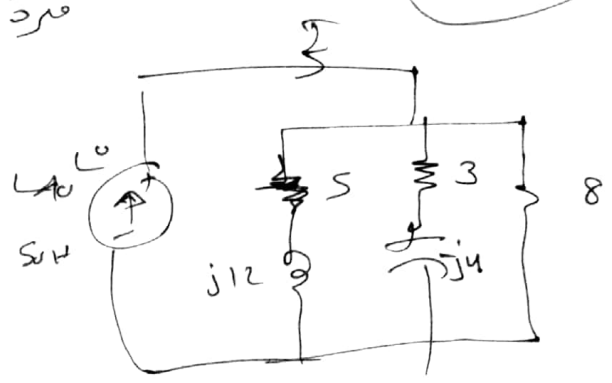
$$\therefore I = VY = 11.55 \angle 17.9^\circ$$



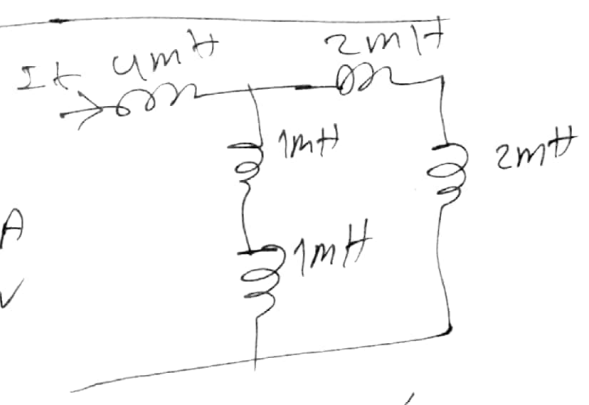9) (5)

what Freq. produce  $I_t = 500mA$  of  $V_t = 10V$



$$Z = \frac{V}{I} = \frac{10}{500mA} = 20$$

$$Z = j\omega L_{eq}$$

$$L_{eq} = \left[ (2m + 2m) \parallel (1m + 1m) \right] + 4m = Z_{eq}$$

$$= 5.33mH$$

$$5 \angle 0^\circ = 5 \angle \phi * 2 * \pi * f * 5.33mH = 20$$

$$\therefore f = \frac{20}{2\pi * 5.33 * 10^{-3}} = 596.8 Hz$$