

ECE 312


Electronic Circuits (A)

Lec. 2: BJT Review

Instructor


Dr. Maher Abdelrasoul

Outline

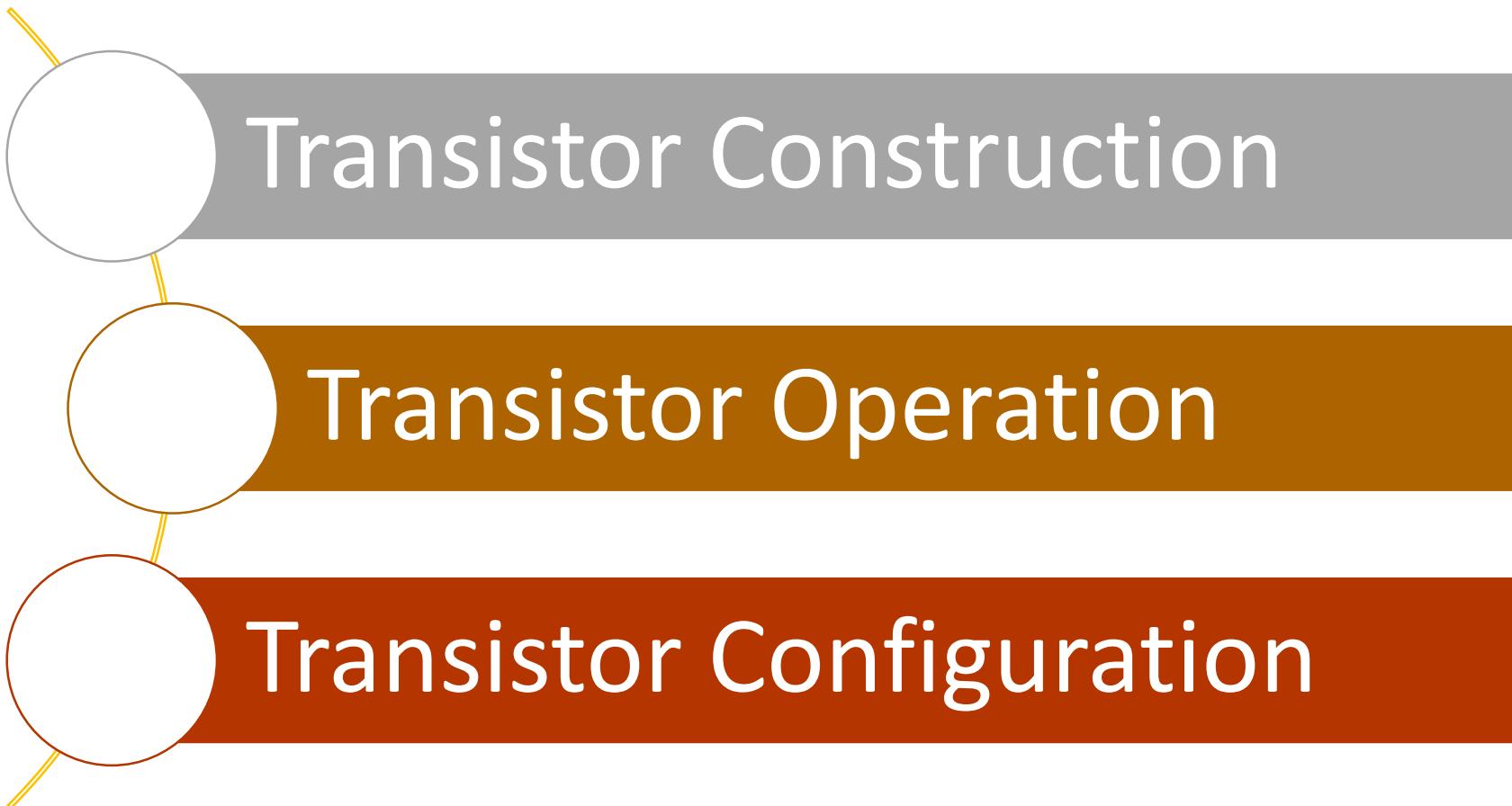

Transistor Construction

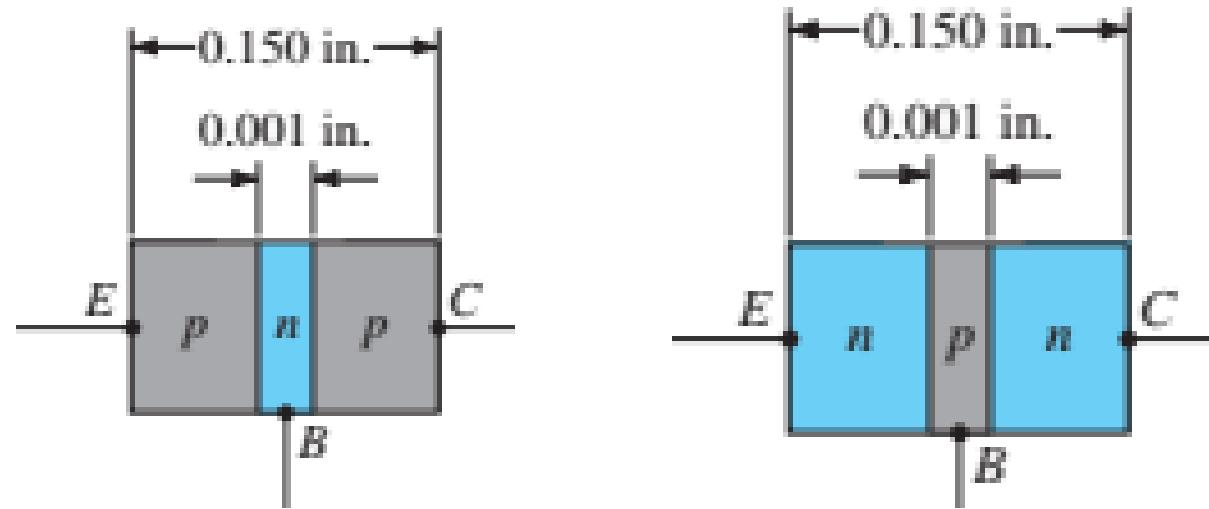
- The transistor is a three-layer semiconductor device consisting of either two *n*- and one *p*-type layers of material (npn transistor) or two *p*- and one *n*-type layers of material (pnp transistor).



Transistor Operation

- The operation discussed in pnp transistor

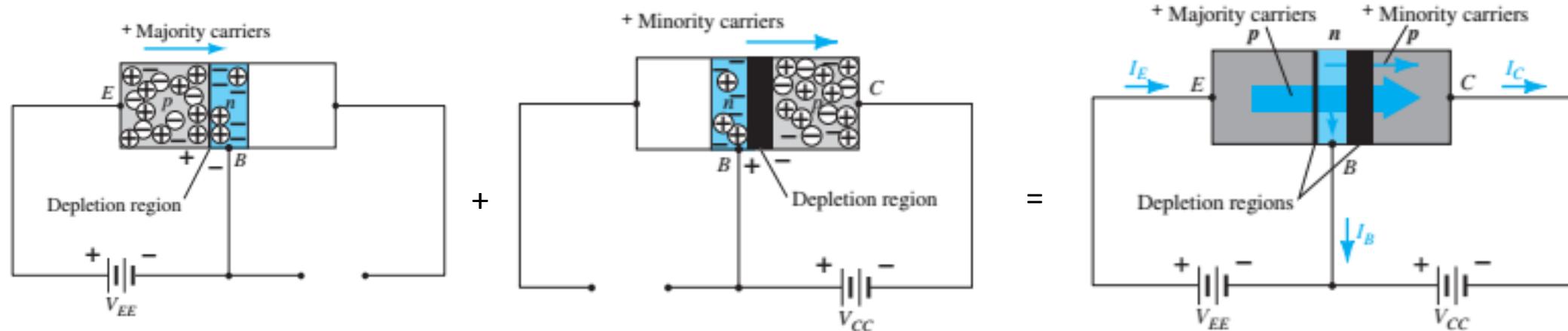***One p–n junction of a transistor is reverse-biased,
whereas the other is forward-biased***



- The collector current by Kirchhoff's law

$$I_E = I_C + I_B$$





$$I_C = I_{C\text{majority}} + I_{CO\text{minority}}$$

Transistor Configuration


1. Common-Base Configuration
2. Common-Emitter Configuration
3. Common-Collector Configuration

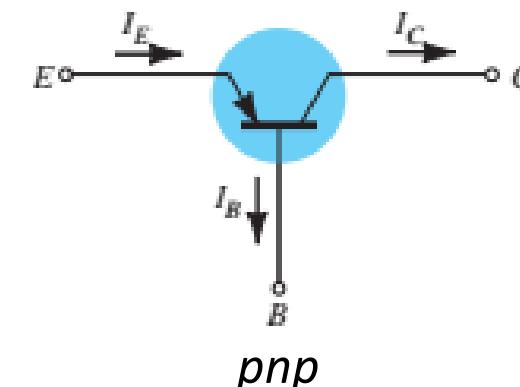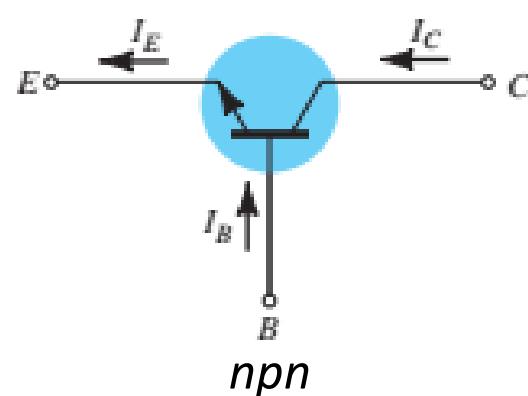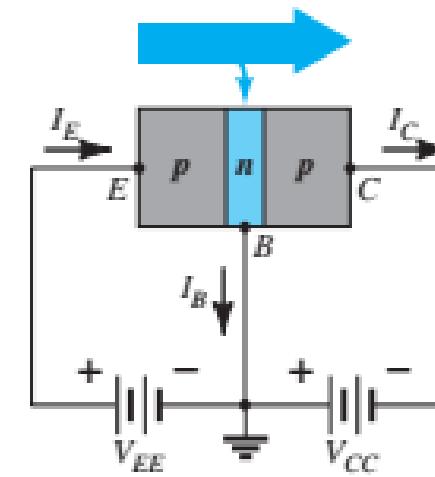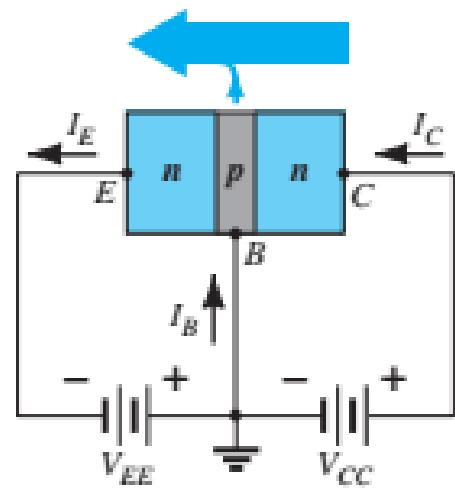1. Common-Base Configuration (1)


- The common-base terminology is derived from the fact that the base is common to both the input and output sides of the configuration.



1. Common-Base Configuration (2)

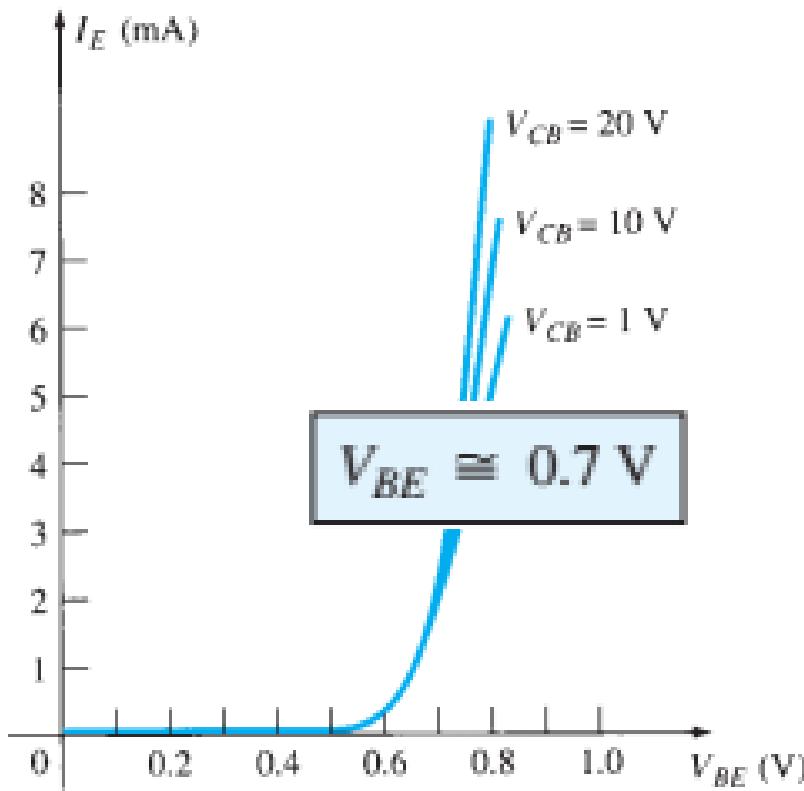

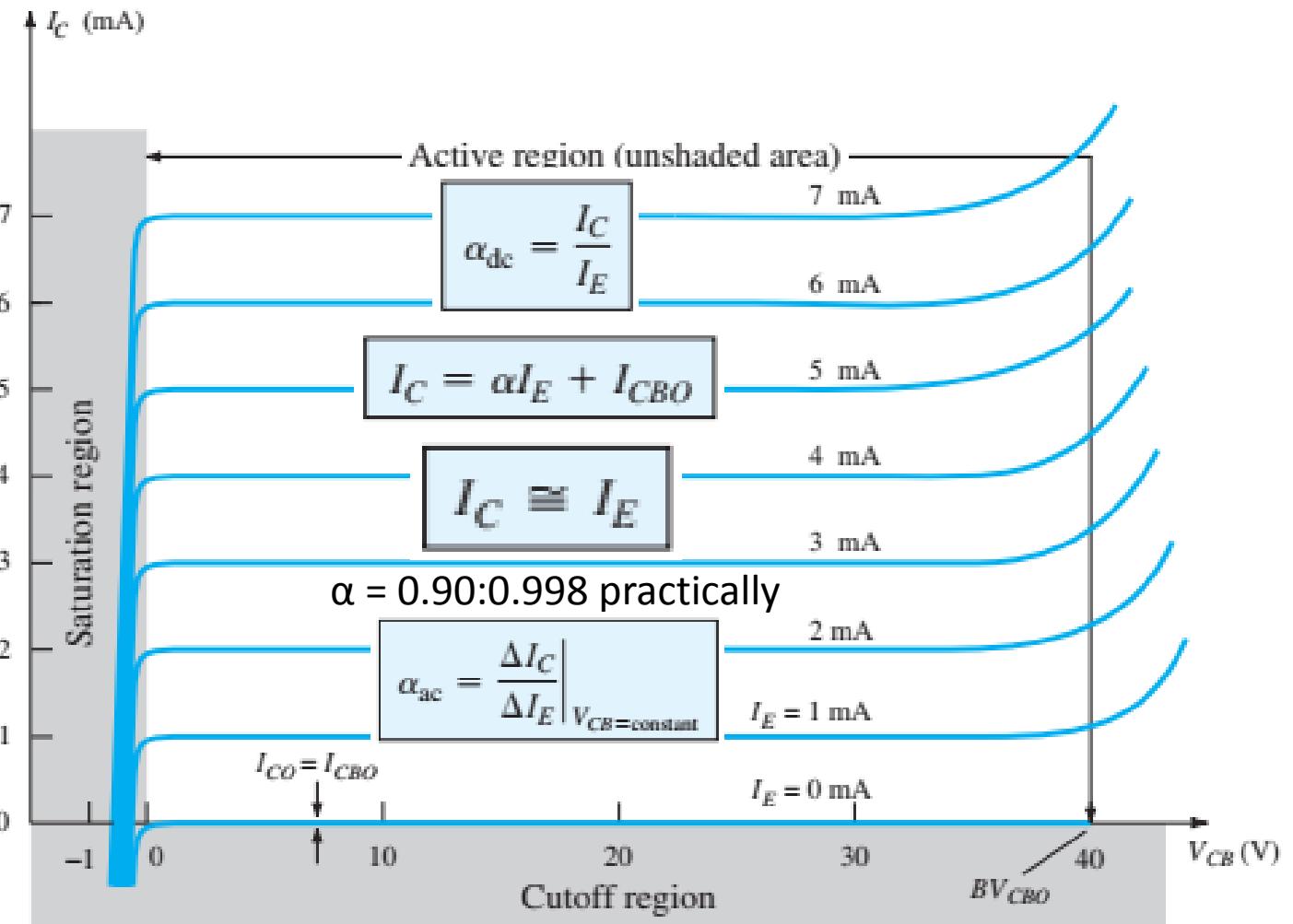Input or driving point characteristics for a common-base silicon transistor amplifier.




Output or collector characteristics for a common-base transistor amplifier.

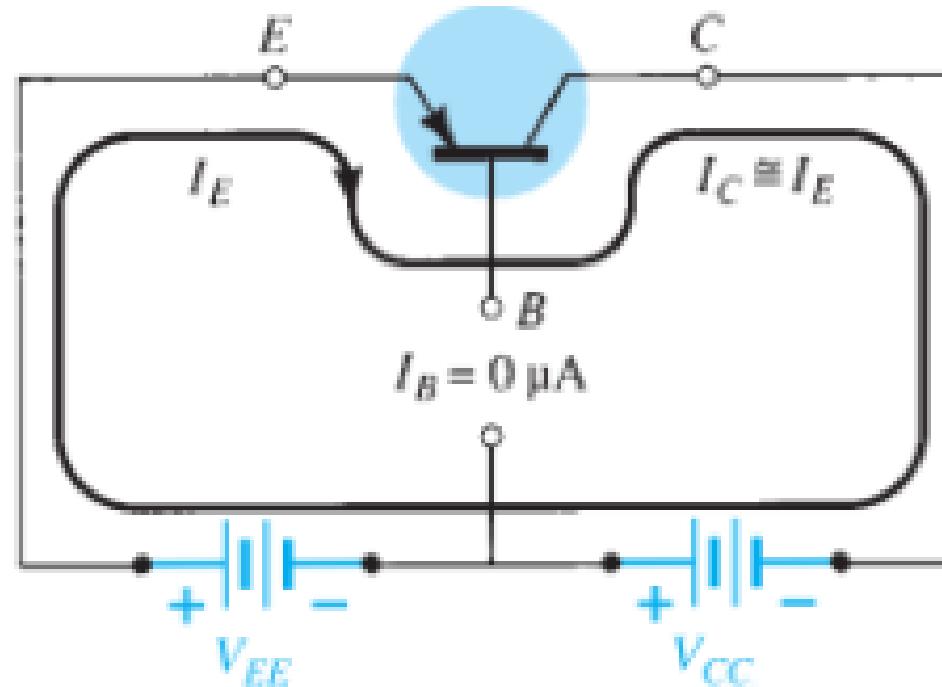1. Common-Base Configuration (3)





- Biasing of a CB pnp tr. in the active region:

In the active region the base-emitter junction is forward-biased, whereas the collector-base junction is reverse-biased.





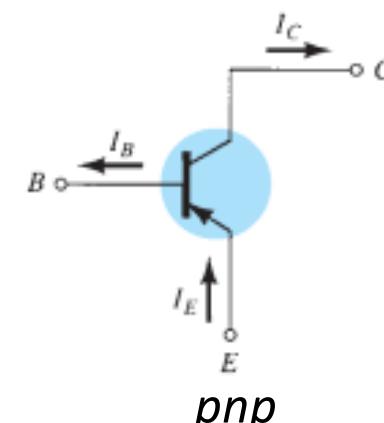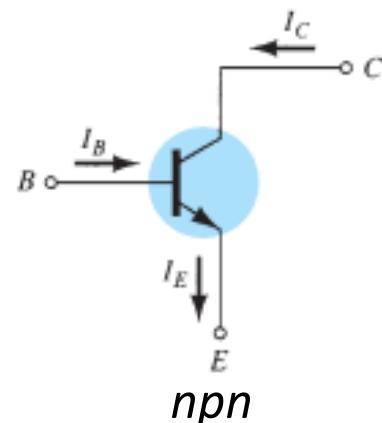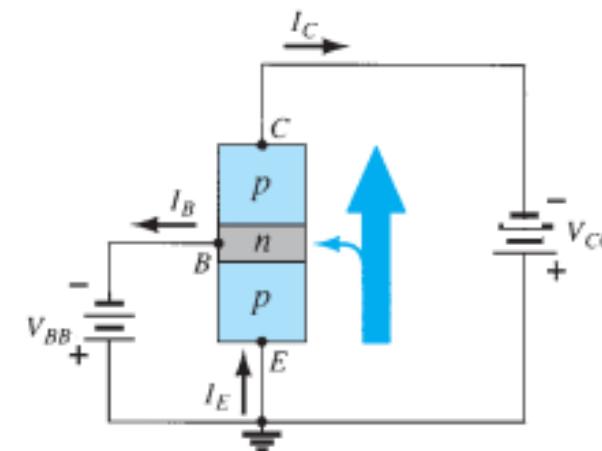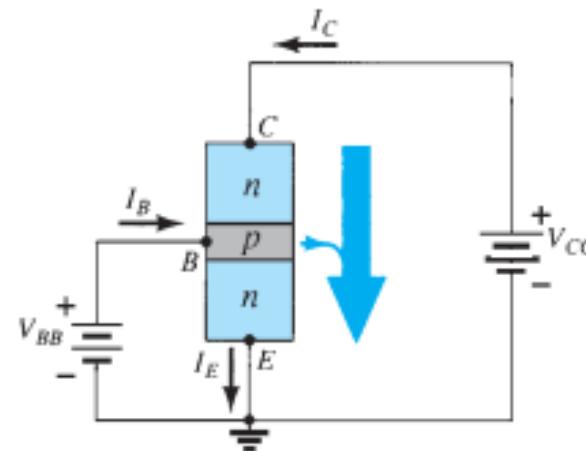2. Common-Emitter Configuration (1)

- It is called the *common-emitter configuration* because the emitter is common to both the input and output terminals (in this case common to both the base and collector terminals).



2. Common-Emitter Configuration (2)

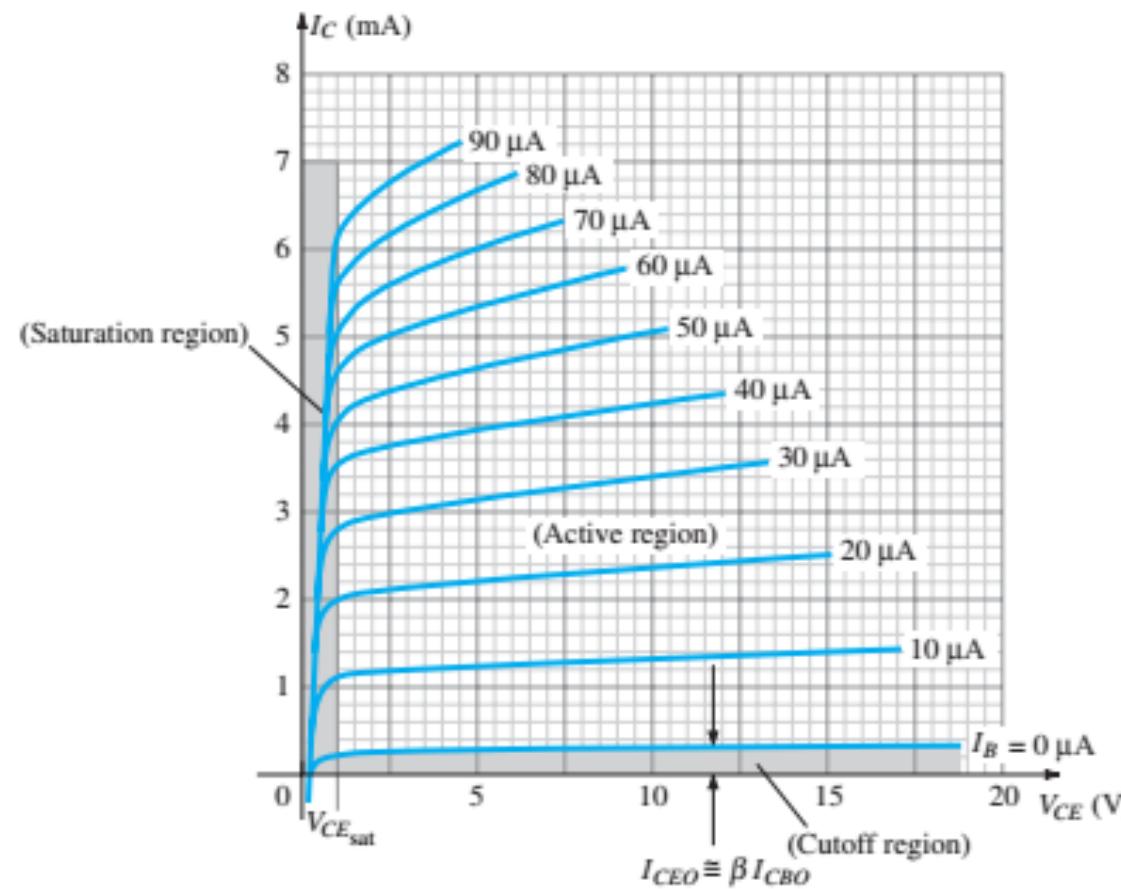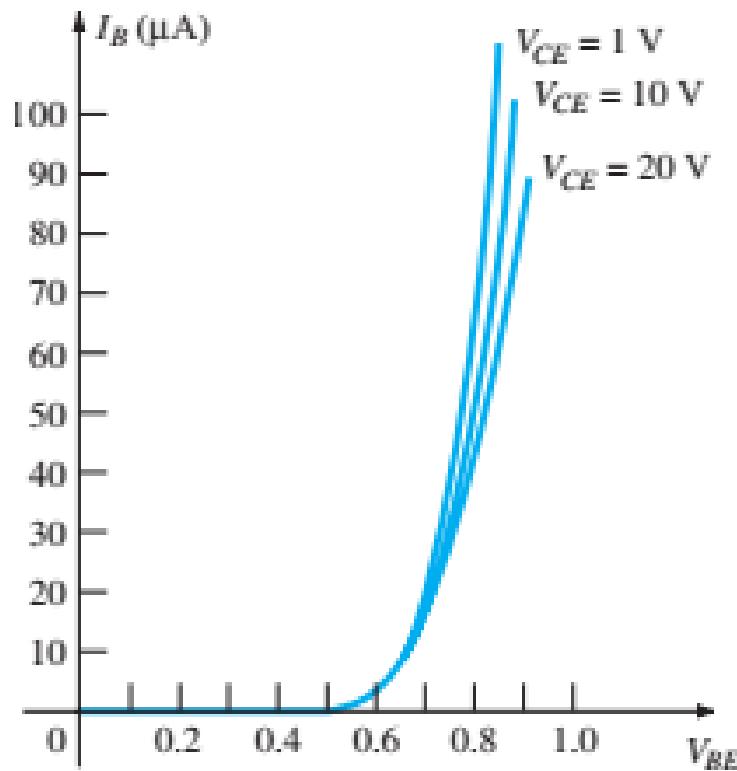

$$\beta_{dc} = \frac{I_C}{I_B}$$

$\beta=50:400$ practically

$$\beta_{ac} = \left. \frac{\Delta I_C}{\Delta I_B} \right|_{V_{CE}=\text{constant}}$$

$$\alpha = \frac{\beta}{\beta + 1}$$

$$\beta = \frac{\alpha}{1 - \alpha}$$


$$I_C = \beta I_B$$

$$I_E = (\beta + 1)I_B$$

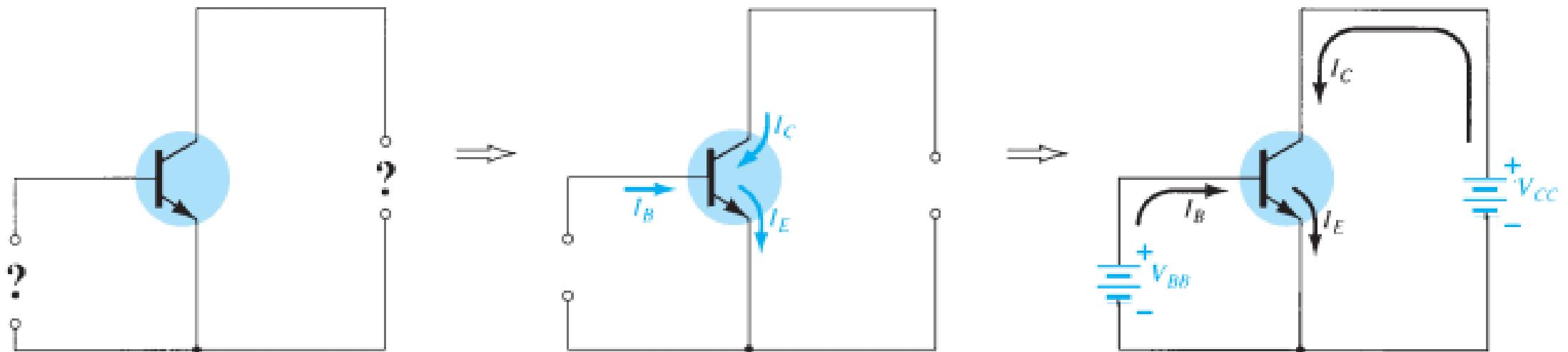2. Common-Emitter Configuration (3)


- Biasing of a CE npn tr. in the active region:

In the active region of a common-emitter amplifier, the base-emitter junction is forward-biased, whereas the collector-base junction is reverse-biased.



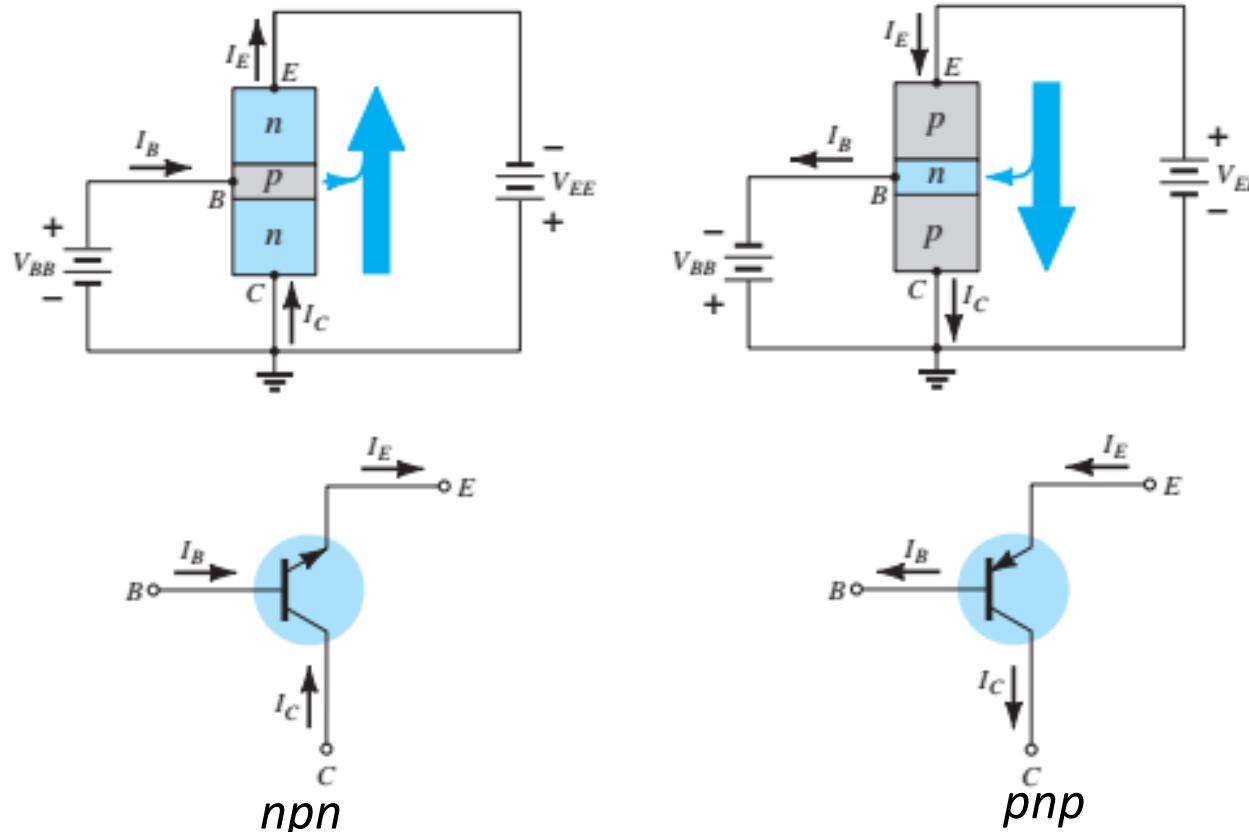3. Common-Collector Configuration (1)


- The common-collector configuration is used primarily for impedance-matching purposes since it has a high input impedance and low output impedance, opposite to that of the common-base and common emitter configurations.



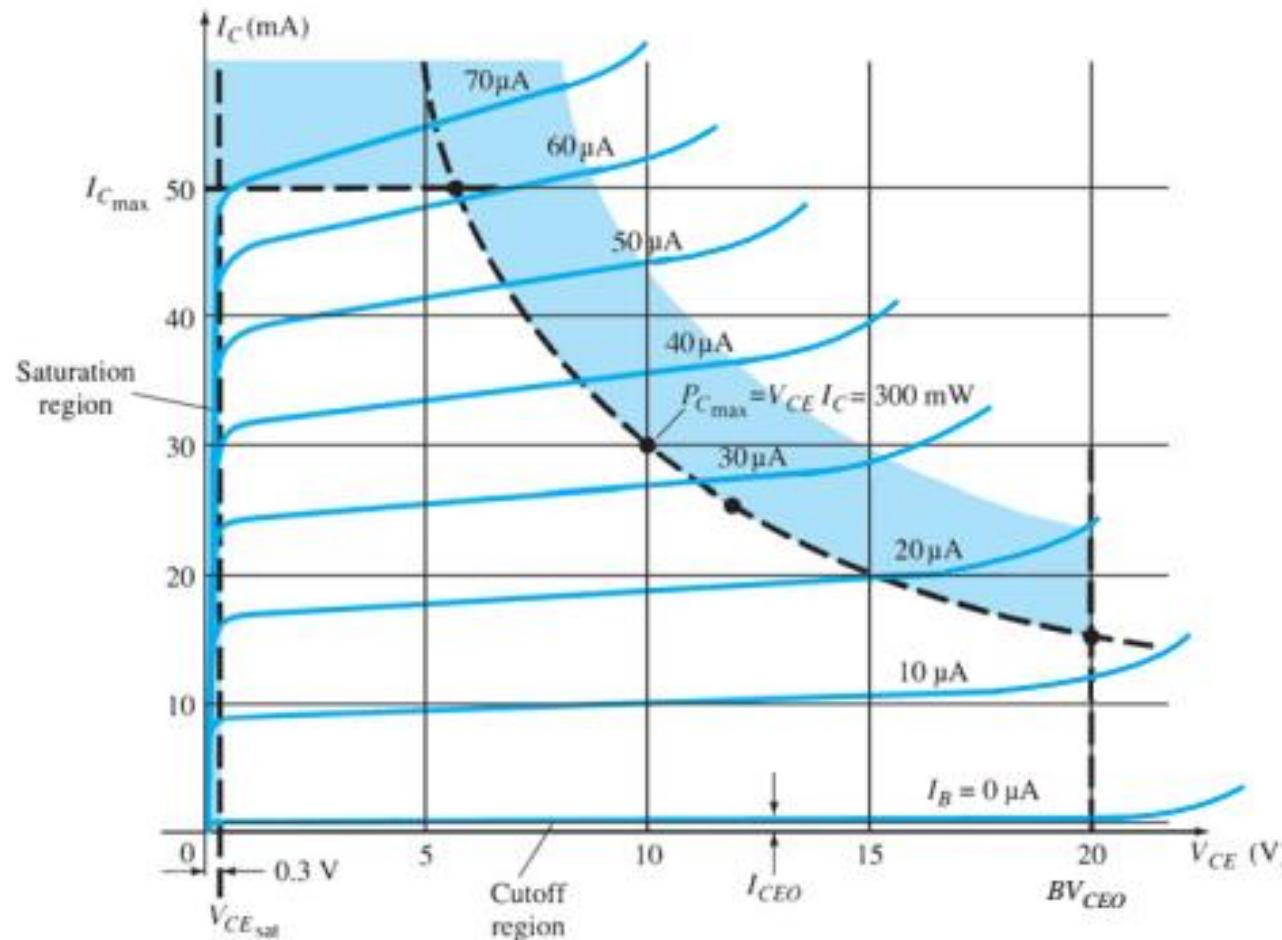3. Common-Collector Configuration (2)

- Limits of operation

Defining the linear (undistorted) region of operation for a transistor



The output characteristics of the common-collector configuration are the same as for the common-emitter configuration ($I_c \approx I_E$).

$$P_{C,max} = V_{CE} I_C$$

$$\begin{aligned}I_{CEO} &\leq I_C \leq I_{C,max} \\V_{CE_{sat}} &\leq V_{CE} \leq V_{CE_{max}} \\V_{CE} I_C &\leq P_{C,max}\end{aligned}$$

Transistor Configuration Summary

Configuration type	Current Gain	Voltage Gain	Power Gain	Input impedance	Output Impedance
Common Base	≈ 1	High	Average	Low	High
Common Emitter	High	High	High	Average	Average
Common Collector	High	≈ 1	Low	High	Low

Transistor Configuration Sheet

- Since the specification sheet is the communication link between the manufacturer and user, it is particularly important that the information provided be recognized and correctly understood.

OFF CHARACTERISTICS

Collector-Emitter Breakdown Voltage (1) ($I_C = 1.0 \text{ mA}_\text{dc}$, $I_E = 0$)	$V_{(\text{BR})\text{CEO}}$	30		V_dc
Collector-Base Breakdown Voltage ($I_C = 10 \mu\text{A}_\text{dc}$, $I_E = 0$)	$V_{(\text{BR})\text{CBO}}$	40		V_dc
Emitter-Base Breakdown Voltage ($I_E = 10 \mu\text{A}_\text{dc}$, $I_C = 0$)	$V_{(\text{BR})\text{EBO}}$	5.0	-	V_dc
Collector Cutoff Current ($V_{\text{CB}} = 20 \text{ V}_\text{dc}$, $I_E = 0$)	I_{CBO}	-	50	nA_dc
Emitter Cutoff Current ($V_{\text{BE}} = 3.0 \text{ V}_\text{dc}$, $I_C = 0$)	I_{EBO}	-	50	nA_dc

ON CHARACTERISTICS

DC Current Gain(1) ($I_C = 2.0 \text{ mA}_\text{dc}$, $V_{\text{CE}} = 1.0 \text{ V}_\text{dc}$) ($I_C = 50 \text{ mA}_\text{dc}$, $V_{\text{CE}} = 1.0 \text{ V}_\text{dc}$)	h_{FE}	50	150	-
Collector-Emitter Saturation Voltage(1) ($I_C = 50 \text{ mA}_\text{dc}$, $I_B = 5.0 \text{ mA}_\text{dc}$)	$V_{\text{CE}(\text{sat})}$	-	0.3	V_dc
Base-Emitter Saturation Voltage(1) ($I_C = 50 \text{ mA}_\text{dc}$, $I_B = 5.0 \text{ mA}_\text{dc}$)	$V_{\text{BE}(\text{sat})}$	-	0.95	V_dc

Small-Signal Current Gain
($I_C = 2.0 \text{ mA}_\text{dc}$, $V_{\text{CE}} = 10 \text{ V}_\text{dc}$, $f = 1.0 \text{ kHz}$)

h_{fe}	50	200	-
-----------------	----	-----	---



MAXIMUM RATINGS

Rating	Symbol	2N4123	Unit
Collector-Emitter Voltage	V_{CEO}	30	V_dc
Collector-Base Voltage	V_{CBO}	40	V_dc
Emitter-Base Voltage	V_{EBO}	5.0	V_dc
Collector Current - Continuous	I_C	200	mA_dc
Total Device Dissipation @ $T_A = 25^\circ\text{C}$ Derate above 25°C	P_D	625 5.0	mW mW°C
Operating and Storage Junction Temperature Range	T_J, T_{sg}	-55 to +150	$^\circ\text{C}$

Limits of Operation


$$7.5 \mu\text{A} \leq I_C \leq 200 \text{ mA}$$

$$0.3 \text{ V} \leq V_{\text{CE}} \leq 30 \text{ V}$$

$$V_{\text{CE}}I_C \leq 650 \text{ mW}$$

Transistor Testing

1. Curve Tracer

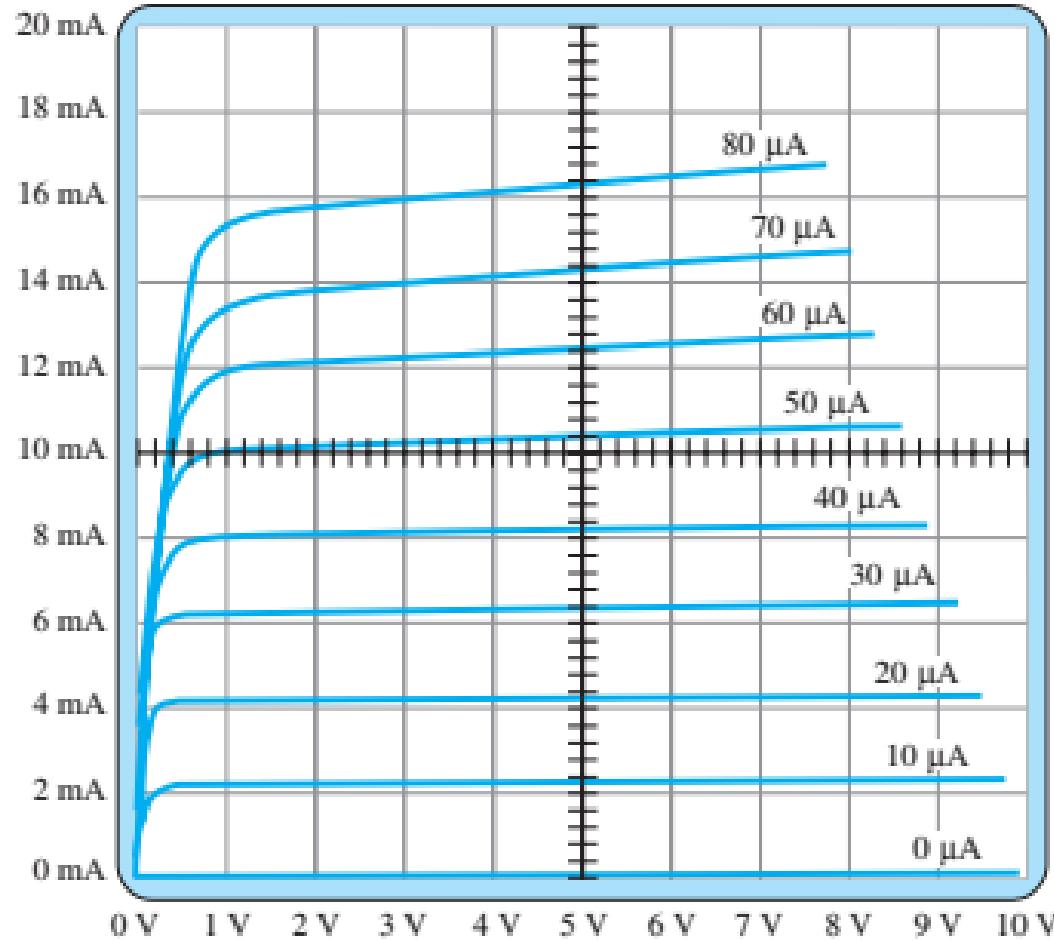

Vertical
per div
2 mA

Horizontal
per div
1 V



Per Step
10 μ A

β or gm
per div
200

2. Transistor Testers




3. Ohmmeter

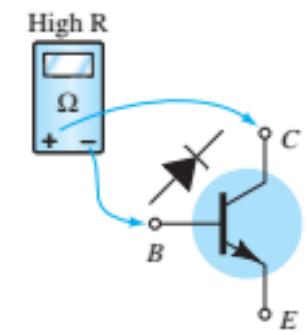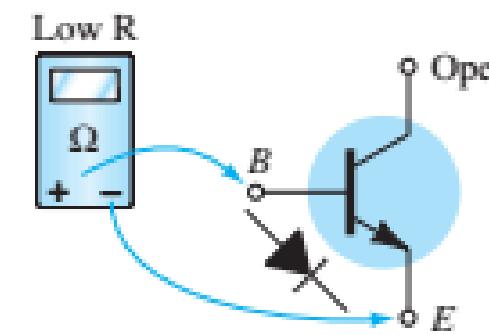



Transistor Casing and Terminal Identification

- Casing

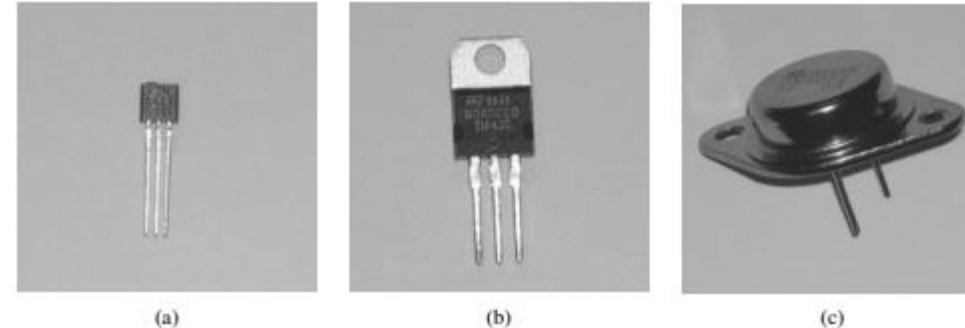

*Various types of general-purpose or switching transistors:
(a) low power; (b) medium power; (c) medium to high power.*


- Terminal Identification

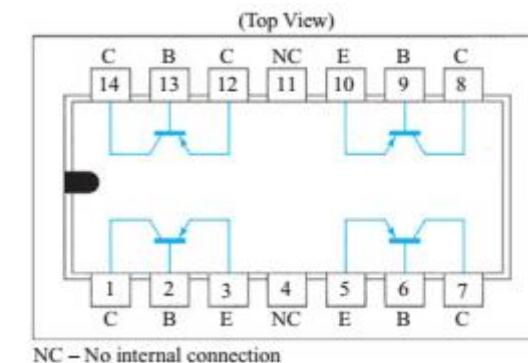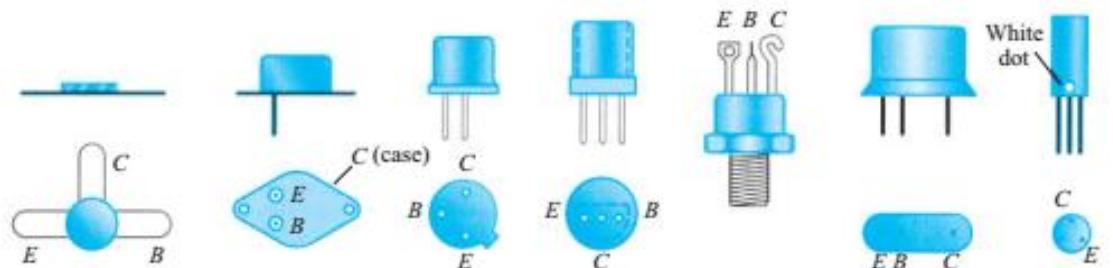

*Type Q2T2905 Texas Instruments quad
pnp silicon transistor*

Transistor Development

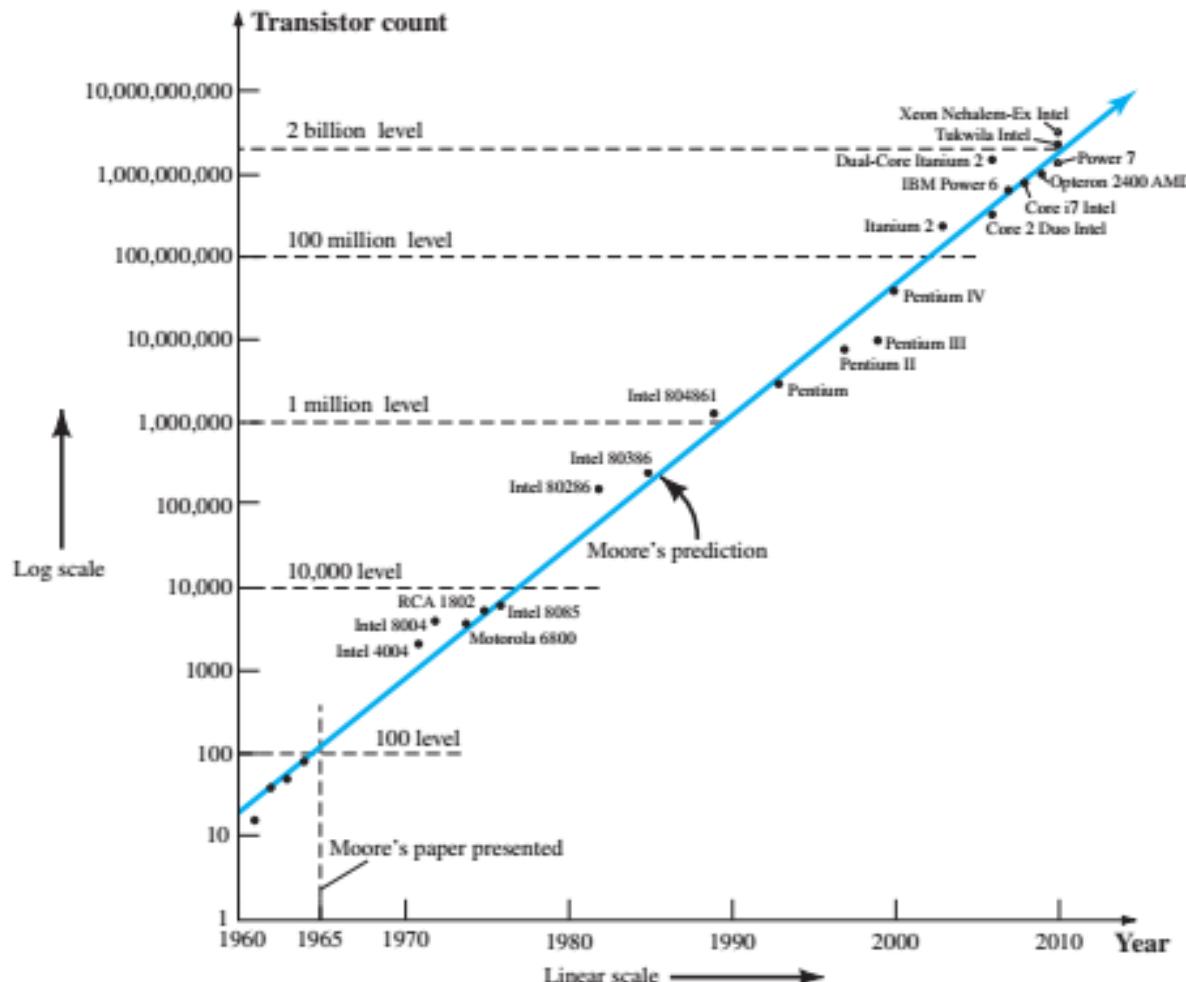- **Moore's law** predicts that the transistor count of an integrated circuit will double every 2 years.



Where can
the field go
from here?

Thank you!

