

# ECE 312

# Electronic Circuits (A)


Lec. 8: BJT Modeling and re Transistor Model (small signal analysis) (3)

Instructor

**Dr. Maher Abdelrasoul**


**<http://www.bu.edu.eg/staff/mahersalem3>**

# Agenda

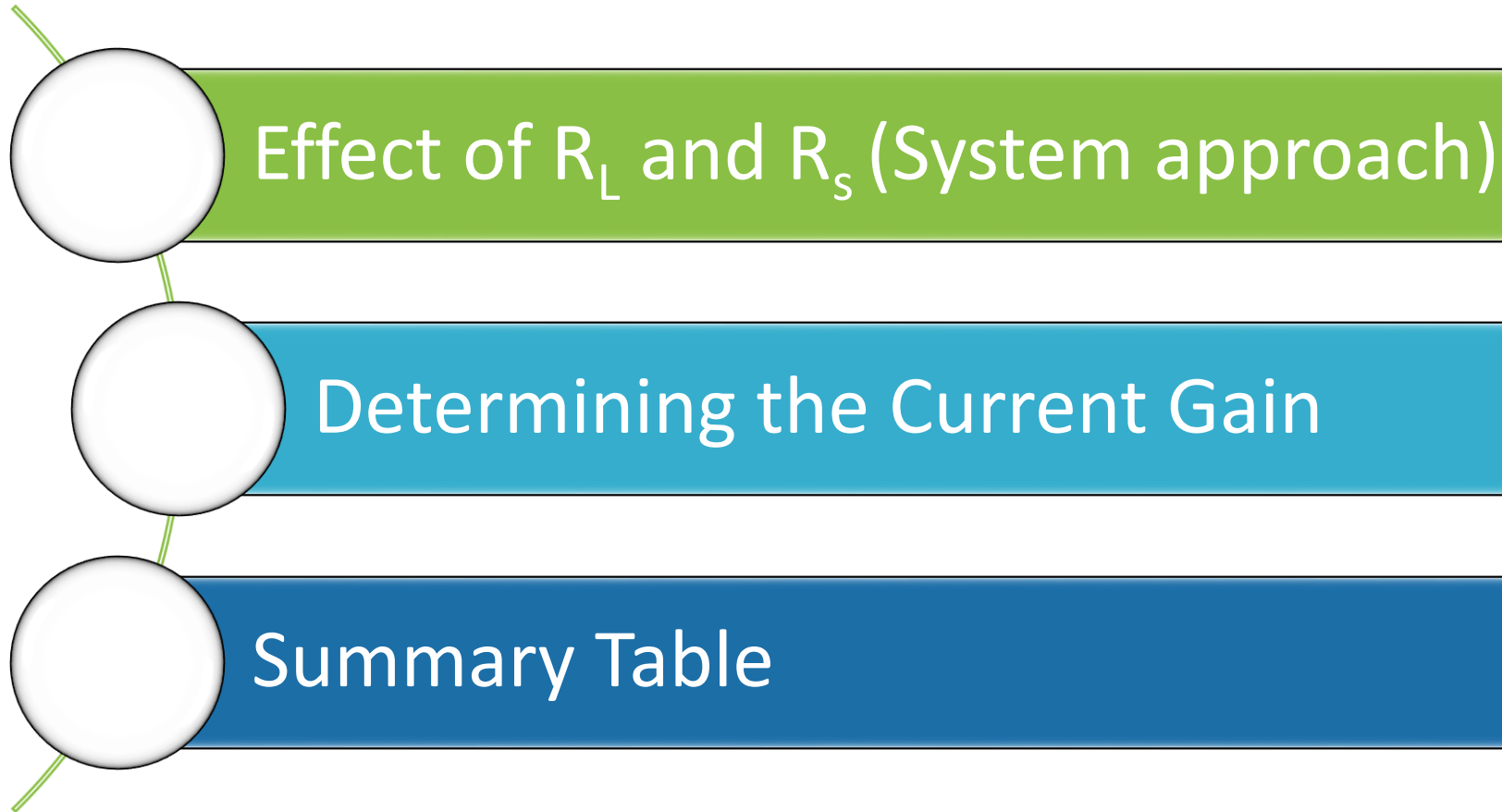- 
- Effect of  $R_L$  and  $R_s$  (System approach)
  - Determining the Current Gain
  - Summary Table

# Effect of $R_L$ and $R_S$ (System Approach)

# Effect of $R_L$ and $R_s$

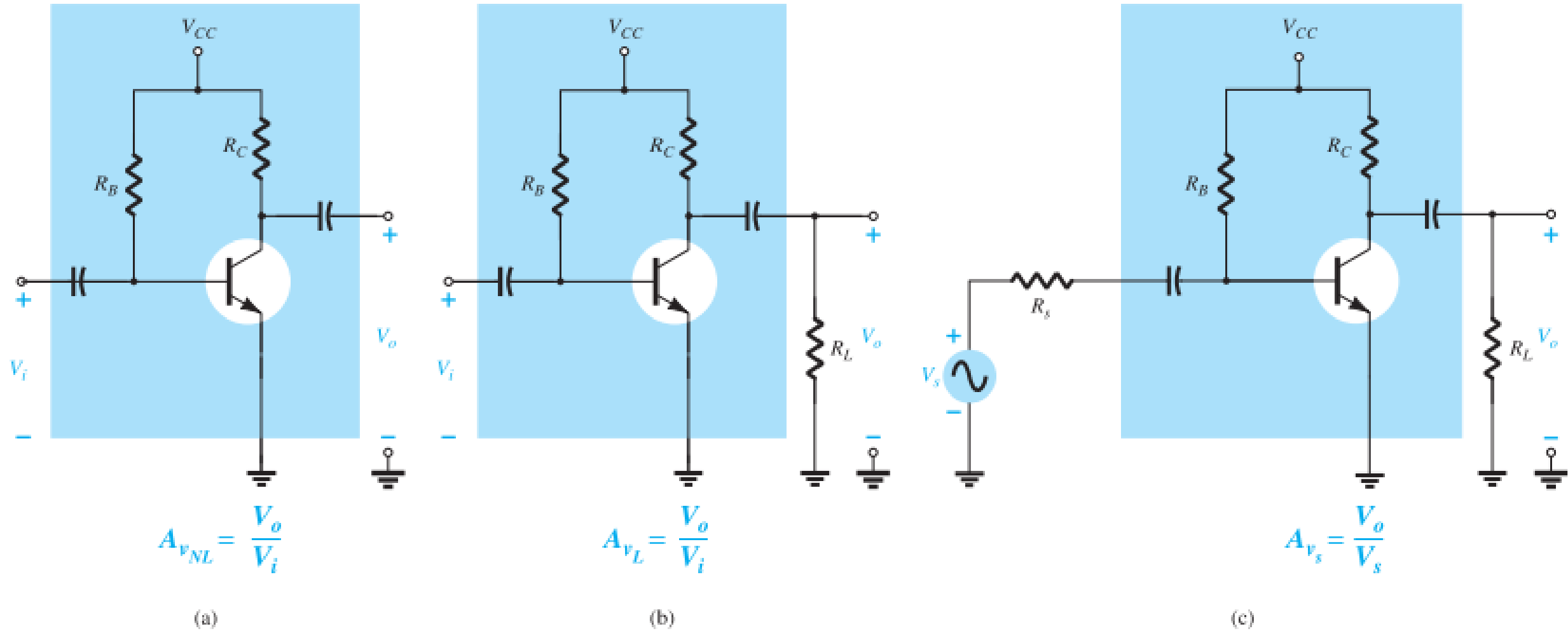


**FIG. 5.54**

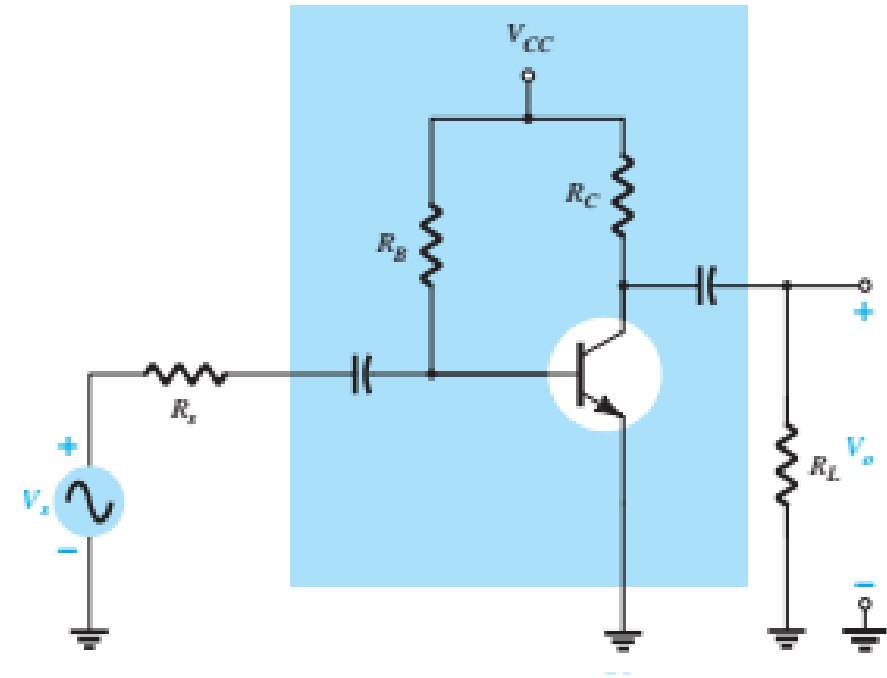
*Amplifier configurations: (a) unloaded; (b) loaded; (c) loaded with a source resistance.*

# Effect of $R_L$ and $R_S$

- The loaded voltage gain of an amplifier is always less than the no-load gain.
- The gain obtained with a source resistance in place will always be less than that obtained under loaded or unloaded conditions due to the drop in applied voltage across the source resistance.
- For the same configuration  $A_{vNL} > A_{vL} > A_{vS}$ .
- $R_L \uparrow \rightarrow A_{vS} \uparrow$
- $R_S \downarrow \rightarrow A_{vS} \uparrow$
- For any network that have coupling capacitors, the source and load resistance do not affect the dc biasing levels.



# Effect of $R_L$ and $R_S$ ..

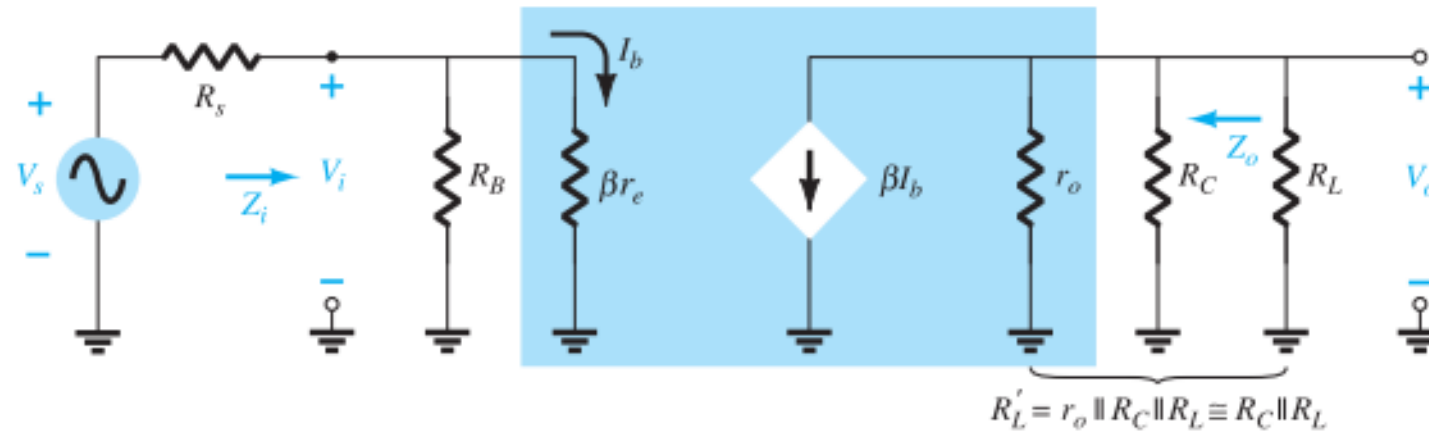

**FIG. 5.55**

The ac equivalent network for the network of Fig. 5.54c.

$$R'_L = r_o \parallel R_C \parallel R_L \cong R_C \parallel R_L$$

$$V_o = -\beta I_b R'_L = -\beta I_b (R_C \parallel R_L)$$

$$I_b = \frac{V_i}{\beta r_e}$$

$$V_o = -\beta \left( \frac{V_i}{\beta r_e} \right) (R_C \parallel R_L)$$

$$A_{vL} = \frac{V_o}{V_i} = -\frac{R_C \parallel R_L}{r_e}$$

$$Z_i = R_B \parallel \beta r_e$$

$$Z_o = R_C \parallel r_o$$

$$V_i = \frac{Z_i V_s}{Z_i + R_s}$$


$$\frac{V_i}{V_s} = \frac{Z_i}{Z_i + R_s}$$

$$A_{vS} = \frac{V_o}{V_s} = \frac{V_o}{V_i} \cdot \frac{V_i}{V_s} = A_{vL} \frac{Z_i}{Z_i + R_s}$$

$$A_{vS} = \frac{Z_i}{Z_i + R_s} A_{vL}$$

# Effect of $R_L$ and $R_S$ ..

Voltage-divider ct.

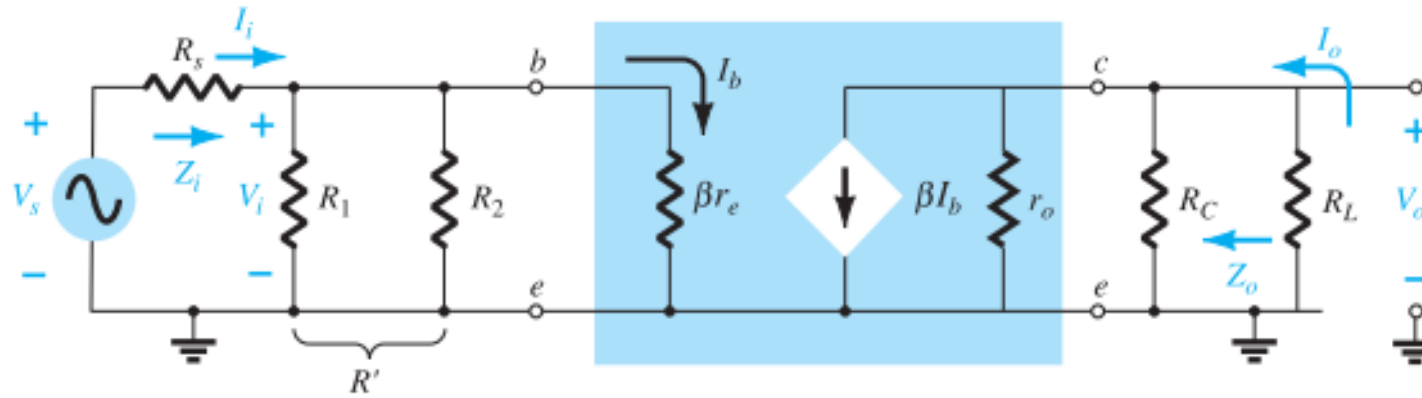


$$A_{vL} = \frac{V_o}{V_i} = -\frac{R_C \parallel R_L}{r_e}$$

$$Z_i = R_1 \parallel R_2 \parallel \beta r_e$$

$$Z_o = R_C \parallel r_o$$

Emitter-Follower Ct.

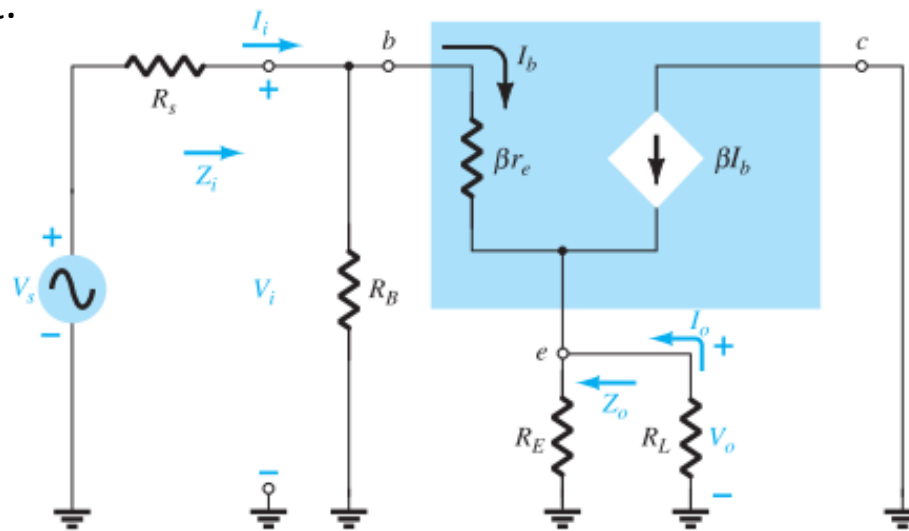

$$Z_i = R_B \parallel Z_b$$

$$Z_b \cong \beta(R_E \parallel R_L)$$


$$Z_o \cong r_e$$

$$A_{vL} = \frac{V_o}{V_i} = \frac{R_E \parallel R_L}{R_E \parallel R_L + r_e}$$

# Effect of $R_L$ and $R_s$ (Example)

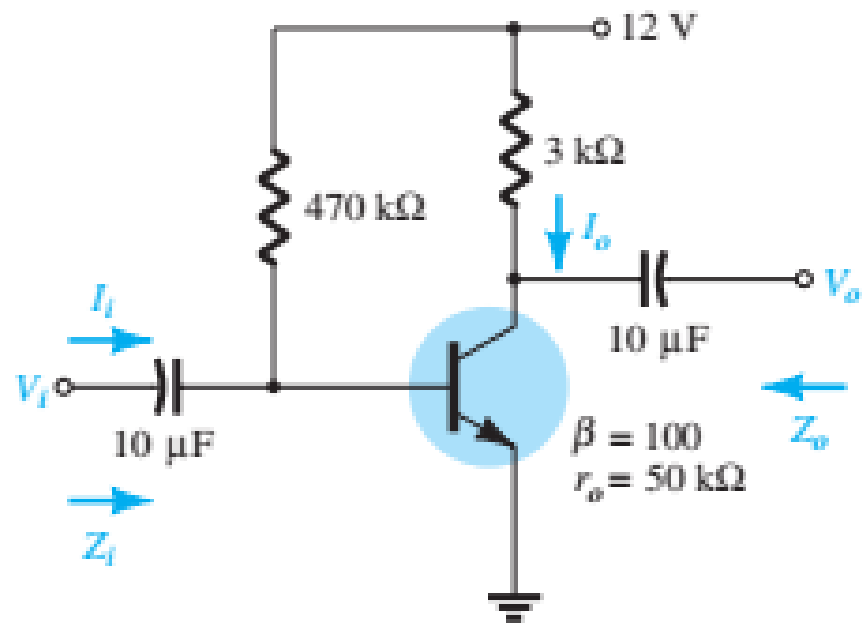**EXAMPLE 5.11** Using the parameter values for the fixed-bias configuration of Example 5.1 with an applied load of  $4.7 \text{ k}\Omega$  and a source resistance of  $0.3 \text{ k}\Omega$ , determine the following and compare to the no-load values:

- $A_{v_L}$ .
- $A_{v_s}$ .
- $Z_i$ .
- $Z_o$ .



**Solution:**

a. Eq. (5.73): 
$$A_{v_L} = -\frac{R_C \parallel R_L}{r_e} = -\frac{3 \text{ k}\Omega \parallel 4.7 \text{ k}\Omega}{10.71 \Omega} = -\frac{1.831 \text{ k}\Omega}{10.71 \Omega} = -170.98$$

which is significantly less than the no-load gain of  $-280.11$ .

b. Eq. (5.76): 
$$A_{v_s} = \frac{Z_i}{Z_i + R_s} A_{v_L}$$

With  $Z_i = 1.07 \text{ k}\Omega$  from Example 5.1, we have

$$A_{v_s} = \frac{1.07 \text{ k}\Omega}{1.07 \text{ k}\Omega + 0.3 \text{ k}\Omega} (-170.98) = -133.54$$

which again is significantly less than  $A_{v_{NL}}$  or  $A_{v_L}$ .

c.  $Z_i = 1.07 \text{ k}\Omega$  as obtained for the no-load situation.


d.  $Z_o = R_C = 3 \text{ k}\Omega$  as obtained for the no-load situation.

The example clearly demonstrates that  $A_{v_{NL}} > A_{v_L} > A_{v_s}$ .



# Determining the Current Gain

# Determining the Current gain

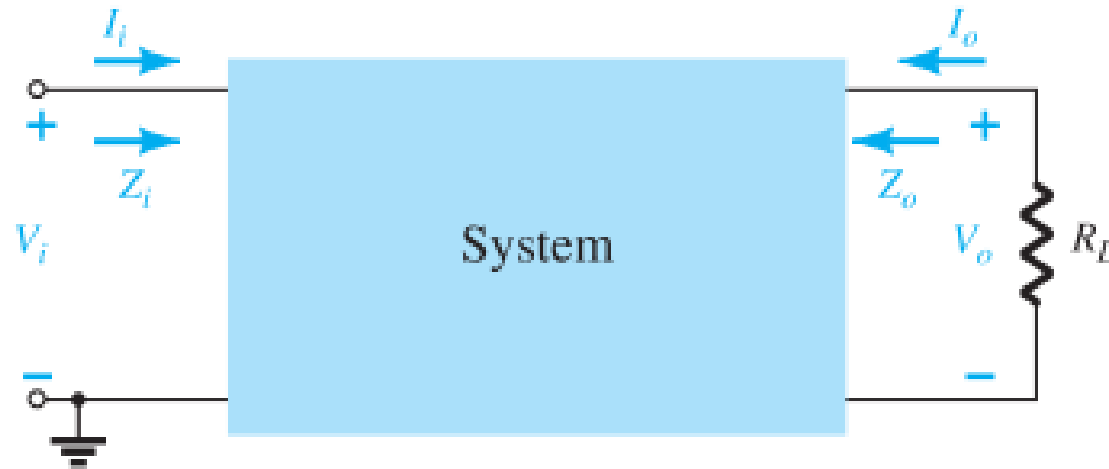

**FIG. 5.60**

*Determining the current gain using the voltage gain.*




- For each transistor configuration, the current gain can be determined directly from the voltage gain, the defined load, and the input impedance.




$$I_i = \frac{V_i}{Z_i} \quad \text{and} \quad I_o = -\frac{V_o}{R_L}$$
$$A_i = \frac{I_o}{I_i}$$



$$A_{iL} = \frac{I_o}{I_i} = \frac{-\frac{V_o}{R_L}}{\frac{V_i}{Z_i}} = -\frac{V_o}{V_i} \cdot \frac{Z_i}{R_L}$$

$$A_{iL} = -A_{vL} \frac{Z_i}{R_L}$$

# Summary Table
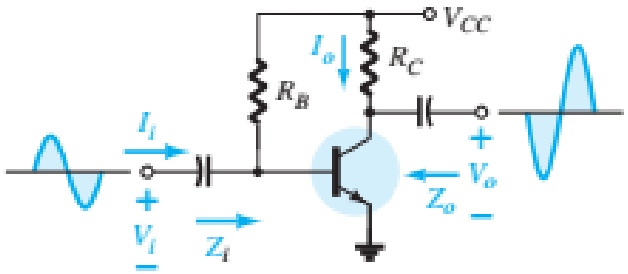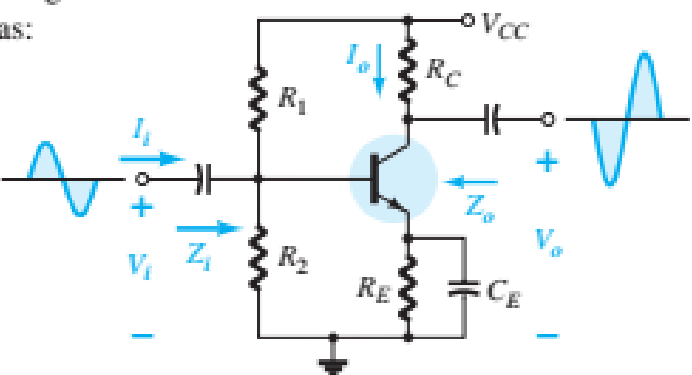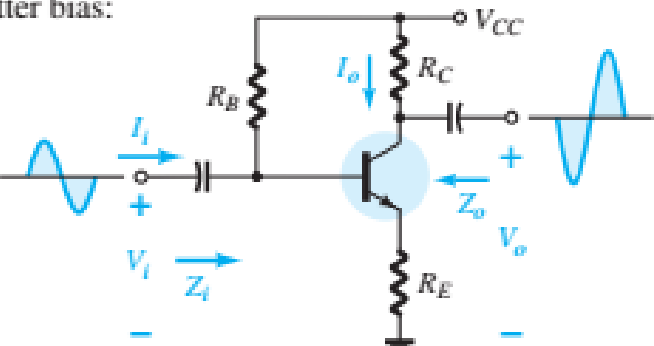
| Configuration  | $Z_i$   | $Z_o$   | $A_v$  | $A_i$  |
|--|---|---|--|--|
| Fixed-bias:                 | Medium (1 k $\Omega$ )<br>$= R_B \parallel \beta r_e$<br>$\equiv \beta r_e$<br>$(R_B \geq 10\beta r_e)$                                 | Medium (2 k $\Omega$ )<br>$= R_C \parallel r_o$<br>$\equiv R_C$<br>$(r_o \geq 10R_C)$ | High (-200)<br>$= -\frac{(R_C \parallel r_o)}{r_e}$<br>$\equiv -\frac{R_C}{r_e}$<br>$(r_o \geq 10R_C)$ | High (100)<br>$= \frac{\beta R_B r_o}{(r_o + R_C)(R_B + \beta r_e)}$<br>$\equiv \beta$<br>$(r_o \geq 10R_C, R_B \geq 10\beta r_e)$   |
| Voltage-divider bias:       | Medium (1 k $\Omega$ )<br>$= R_1 \parallel R_2 \parallel \beta r_e$   | Medium (2 k $\Omega$ )<br>$= R_C \parallel r_o$<br>$\equiv R_C$<br>$(r_o \geq 10R_C)$ | High (-200)<br>$= -\frac{R_C \parallel r_o}{r_e}$<br>$\equiv -\frac{R_C}{r_e}$<br>$(r_o \geq 10R_C)$   | High (50)<br>$= \frac{\beta(R_1 \parallel R_2)r_o}{(r_o + R_C)(R_1 \parallel R_2 + \beta r_e)}$<br>$\equiv \frac{\beta(R_1 \parallel R_2)}{R_1 \parallel R_2 + \beta r_e}$<br>$(r_o \geq 10R_C)$ |
| Unbypassed emitter bias:  | High (100 k $\Omega$ )<br>$= R_B \parallel Z_b$<br>$Z_b \equiv \beta(r_e + R_E)$<br>$\equiv R_B \parallel \beta R_E$<br>$(R_E \gg r_e)$ | Medium (2 k $\Omega$ )<br>$= R_C$<br>$(\text{any level of } r_o)$                     | Low (-5)<br>$= -\frac{R_C}{r_e + R_E}$<br>$\equiv -\frac{R_C}{R_E}$<br>$(R_E \gg r_e)$                 | High (50)<br>$\equiv \frac{\beta R_B}{R_B + Z_b}$  |
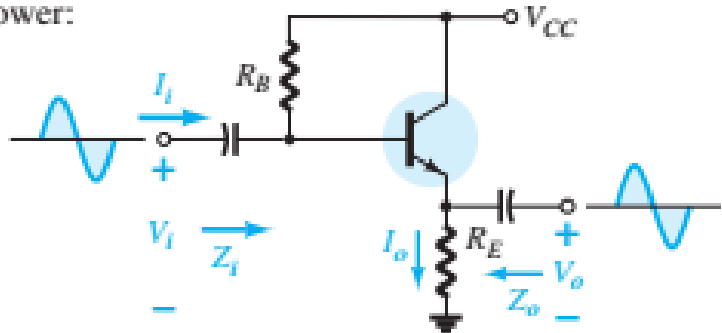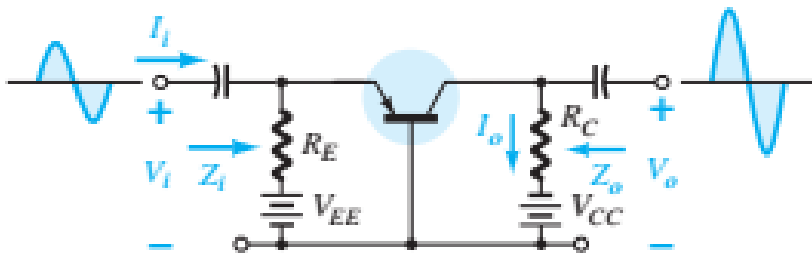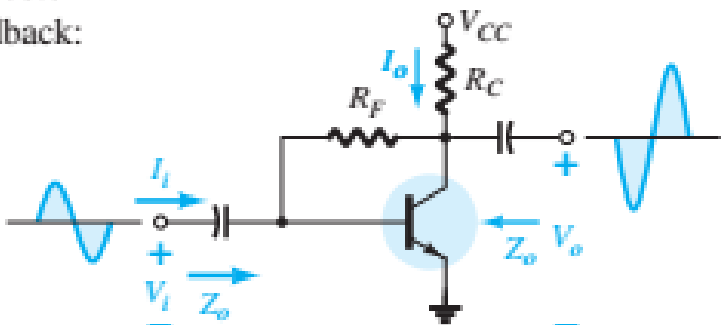
| Configuration   | $Z_i$   | $Z_o$  | $A_v$  | $A_i$  |
|---|---|--|--|--|
| Emitter-follower:<br>    | High (100 k $\Omega$ )<br>$= R_B \parallel Z_b$<br>$Z_b \equiv \beta(r_e + R_E)$<br>$\equiv R_B \parallel \beta R_E$<br>$(R_E \gg r_e)$ | Low (20 $\Omega$ )<br>$= R_E \parallel r_e$<br>$\equiv r_e$<br>$(R_E \gg r_e)$ | Low ( $\cong 1$ )<br>$= \frac{R_E}{R_E + r_e}$<br>$\equiv 1$                         | High ( $\approx 50$ )<br>$\equiv \frac{\beta R_B}{R_B + Z_b}$                  |
| Common-base:<br>         | Low (20 $\Omega$ )<br>$= R_E \parallel r_e$<br>$\equiv r_e$<br>$(R_E \gg r_e)$  | Medium (2 k $\Omega$ )<br>$= R_C$  | High (200)<br>$\equiv \frac{R_C}{r_e}$   | Low ( $-1$ )<br>$\equiv -1$  |
| Collector feedback:<br> | Medium (1 k $\Omega$ )<br>$= \frac{r_e}{\frac{1}{\beta} + \frac{R_C}{R_F}}$<br>$(r_o \geq 10R_C)$                                       | Medium (2 k $\Omega$ )<br>$\equiv R_C \parallel R_F$<br>$(r_o \geq 10R_C)$     | High ( $-200$ )<br>$\equiv \frac{R_C}{r_e}$<br>$(r_o \geq 10R_C)$<br>$(R_F \gg R_C)$ | High (50)<br>$= \frac{\beta R_F}{R_F + \beta R_C}$<br>$\equiv \frac{R_F}{R_C}$ |
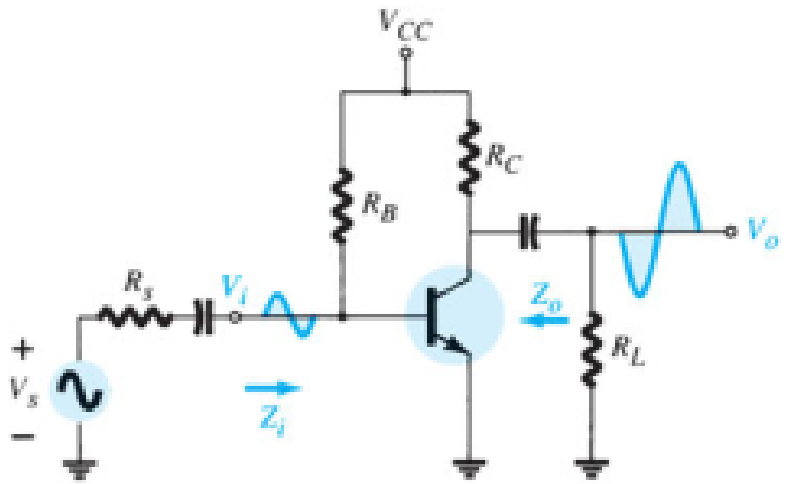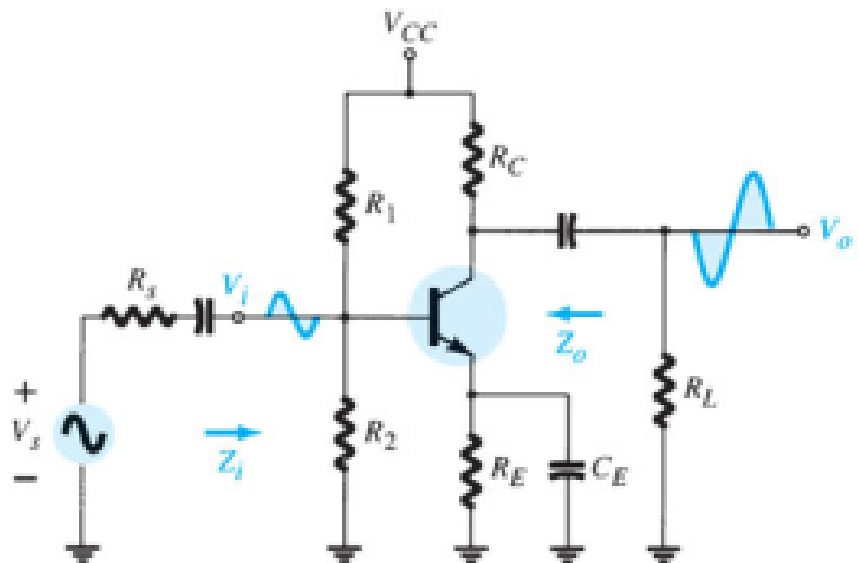
| Configuration   | $A_{v_L} = V_o/V_i$   | $Z_i$                                   | $Z_o$               |
|---|---|---|---------------------|
|   | $\frac{-(R_L \parallel R_C)}{r_e}$  | $R_B \parallel \beta r_e$               | $R_C$               |
|  | $\frac{-(R_L \parallel R_C)}{r_e}$  | $R_1 \parallel R_2 \parallel \beta r_e$ | $R_C$               |
|   | <p>Including <math>r_o</math>:</p> $\frac{-(R_L \parallel R_C \parallel r_o)}{r_e}$ | $R_B \parallel \beta r_e$               | $R_C \parallel r_o$ |
|   | <p>Including <math>r_o</math>:</p> $\frac{-(R_L \parallel R_C \parallel r_o)}{r_e}$ | $R_1 \parallel R_2 \parallel \beta r_e$ | $R_C \parallel r_o$ |

| Configuration | $A_{v_L} = V_o/V_i$   | $Z_i$   | $Z_o$   |
|---------------|---|---|---|
|               | $\cong 1$   | $R'_E = R_L \parallel R_E$<br>$R_1 \parallel R_2 \parallel \beta(r_e + R'_E)$ | $R'_s = R_s \parallel R_1 \parallel R_2$<br>$R_E \parallel \left( \frac{R'_s}{\beta} + r_e \right)$ |
|               | Including $r_o$ :<br>$\cong 1$  | $R_1 \parallel R_2 \parallel \beta(r_e + R'_E)$                               | $R_E \parallel \left( \frac{R'_s}{\beta} + r_e \right)$   |
|               | $\cong \frac{-(R_L \parallel R_C)}{r_e}$                                    | $R_E \parallel r_e$   | $R_C$   |
|               | Including $r_o$ :<br>$\cong \frac{-(R_L \parallel R_C \parallel r_o)}{r_e}$ | $R_E \parallel r_e$   | $R_C \parallel r_o$   |
|               | $\frac{-(R_L \parallel R_C)}{R_E}$  | $R_1 \parallel R_2 \parallel \beta(r_e + R_E)$                                | $R_C$   |
|               | Including $r_o$ :<br>$\frac{-(R_L \parallel R_C)}{R_E}$                     | $R_1 \parallel R_2 \parallel \beta(r_e + R_e)$                                | $\cong R_C$   |

| Configuration | $A_{v_L} = V_o/V_i$   | $Z_i$  | $Z_o$                             |
|---------------|---|--|-----------------------------------|
|               | $\frac{-(R_L \parallel R_C)}{R_{E1}}$                                 | $R_B \parallel \beta(r_e + R_{E1})$            | $R_C$                             |
|               | Including $r_o$ :<br>$\frac{-(R_L \parallel R_C)}{R_{E1}}$            | $R_B \parallel \beta(r_e + R_E)$               | $\equiv R_C$                      |
|               | $\frac{-(R_L \parallel R_C)}{r_e}$                                    | $\beta r_e \parallel \frac{R_F}{ A_v }$        | $R_C$                             |
|               | Including $r_o$ :<br>$\frac{-(R_L \parallel R_C \parallel r_o)}{r_e}$ | $\beta r_e \parallel \frac{R_F}{ A_v }$        | $R_C \parallel R_F \parallel r_o$ |
|               | $\frac{-(R_L \parallel R_C)}{R_E}$                                    | $\beta R_E \parallel \frac{R_F}{ A_v }$        | $\equiv R_C \parallel R_F$        |
|               | Including $r_o$ :<br>$\equiv \frac{-(R_L \parallel R_C)}{R_E}$        | $\equiv \beta R_E \parallel \frac{R_F}{ A_v }$ | $\equiv R_C \parallel R_F$        |



Thank You!

