

# Electronic Instrumentations and Measurements, Part 2

## Lecture 1: Digital Voltmeters

**Dr. Haitham El-Hussey**

Electronics and Communications Engineering  
**Faculty of Engineering (Shoubra)**  
**Benha University**



October 2016

## Part 2 Contents:

- Digital Voltmeters.
- Digital Frequency meters.
- Sensor and Transducers:
  - ▶ Displacement, position and proximity sensors.
  - ▶ Velocity and motion sensors.
  - ▶ Force sensors.
  - ▶ Fluid pressure, liquid flow and liquid level sensors.
  - ▶ Temperature sensors.
  - ▶ Light sensors.

### Part 2 Examination

Exam on Part 2 will be on: **Monday, 28/11/2016** Tuesday 21/11/2017

## Lecture Outline:


- 1 Introduction to Digital Voltmeters.
- 2 Ramp Type Digital Voltmeters.
- 3 Dual Slope Digital Voltmeters.
- 4 Range Changing.
- 5 Digital Voltmeter Accuracy.
- 6 Types of Digital Multi-meters.

# Table of Contents

- 1 Introduction to Digital Voltmeters.
- 2 Ramp Type Digital Voltmeters.
- 3 Dual Slope Digital Voltmeters.
- 4 Range Changing.
- 5 Digital Voltmeter Accuracy.
- 6 Types of Digital Multi-meters.
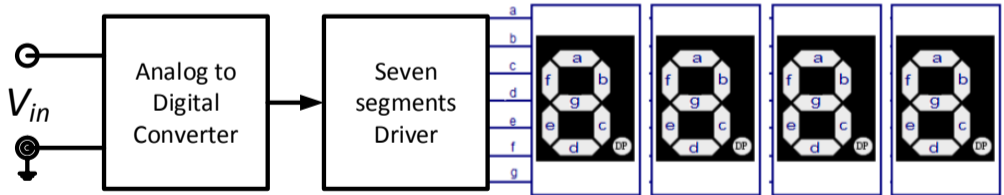
# Introduction to Digital Voltmeters:

- Digital voltmeters (DVM) are essentially **analog-to-digital** converters with **digital displays** to indicate the measured voltage.
- Two types will be covered: **Ramp-type** and **Dual slope Integrator** DVMs.




**Digital Voltmeter Basic Block Diagram**

# Table of Contents

- 1 Introduction to Digital Voltmeters.
- 2 Ramp Type Digital Voltmeters.**
- 3 Dual Slope Digital Voltmeters.
- 4 Range Changing.
- 5 Digital Voltmeter Accuracy.
- 6 Types of Digital Multi-meters.

## Ramp Type Digital Voltmeters:

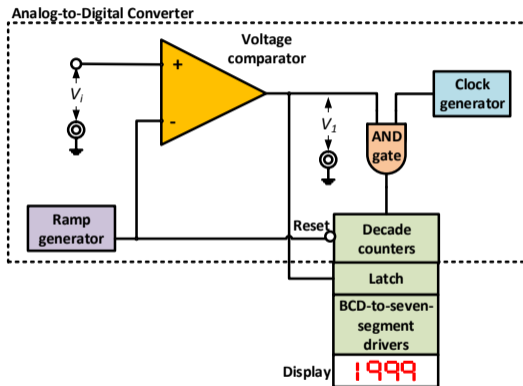


Ramp type DVM block

- A ramp signal is generated.
- the comparator compares the input  $V_i$  with the ramp  $V_r$ .


$$V_1 = \begin{cases} 1, & \text{if } V_i \geq V_r \\ 0, & \text{if } V_i < V_r \end{cases}$$

- If the comparator output is **high**, the counting circuit will count the pulses from clock generator.
- If the output  $V_1$  is **low**, the counting will stop.
- The value of  $V_i$  will be displayed by the end of the ramp signal.
- $N_{pulses} \propto V_i$

# Ramp Type Digital Voltmeters:

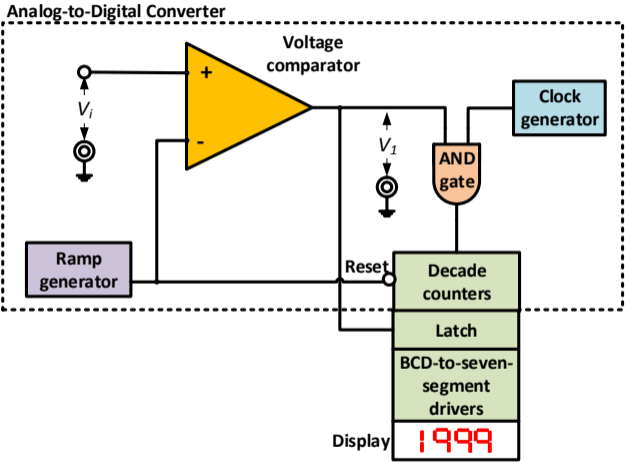

Ramp type DVM block

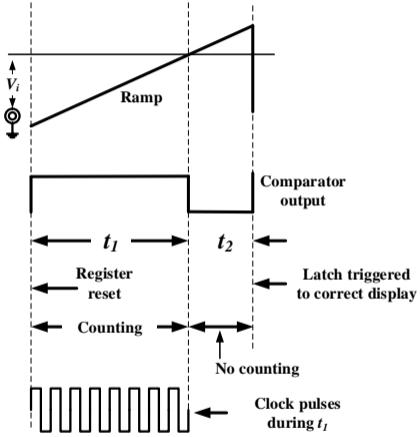



DVM waveform



# Ramp Type Digital Voltmeters:
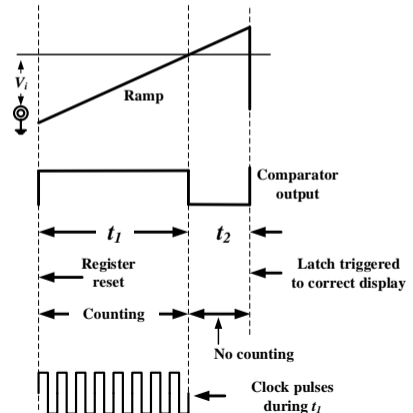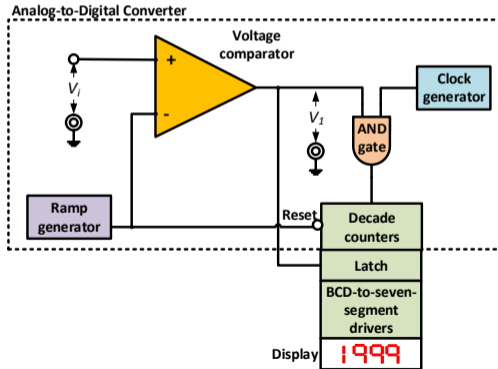
## The use of the Latch:


- The latch isolates the display from the counting circuit during the  $t_1$ .
- The latch will connect the display to the counting circuit at the rising edge of the comparator output.



# Table of Contents

- 1 Introduction to Digital Voltmeters.
- 2 Ramp Type Digital Voltmeters.
- 3 Dual Slope Digital Voltmeters.**
- 4 Range Changing.
- 5 Digital Voltmeter Accuracy.
- 6 Types of Digital Multi-meters.

# Dual Slope Digital Voltmeters:

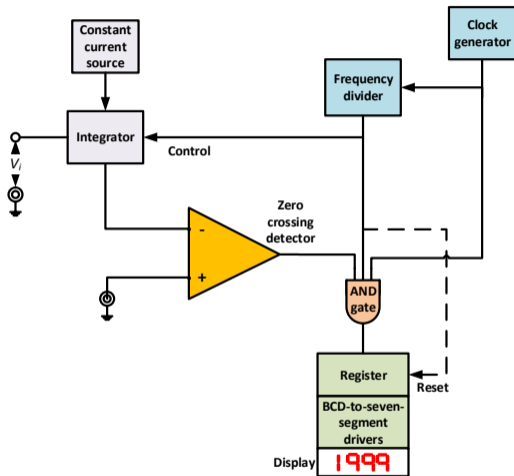


Dual Slope DVM block

## Limitations of Ramp type DVM


- The ramp type DVM requires precise ramp voltage and precise time periods. (Not accurate)
- The *Dual-slope-integrator DVM* eliminates this requirement.

# Dual Slope Digital Voltmeters:

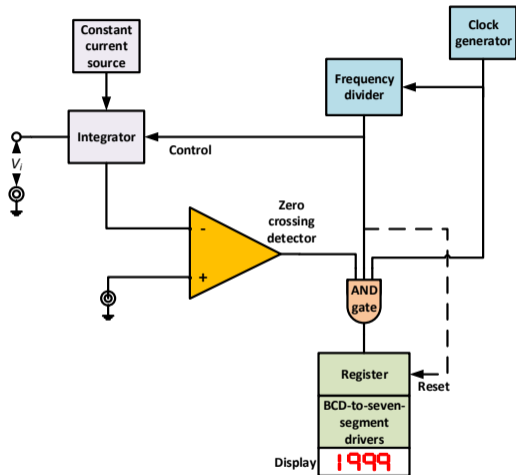


Dual Slope DVM block

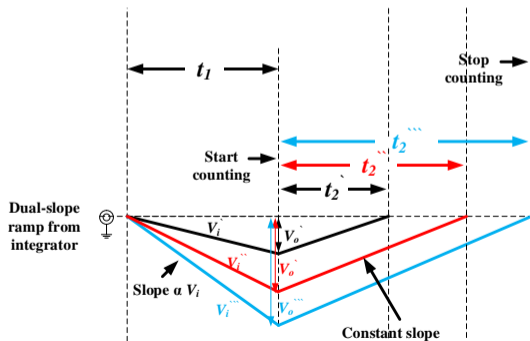- An integrator (e.g. capacitor) is either **charged negatively from  $V_i$**  or **discharged at a constant rate according to the control signal**.





# Dual Slope Digital Voltmeters:

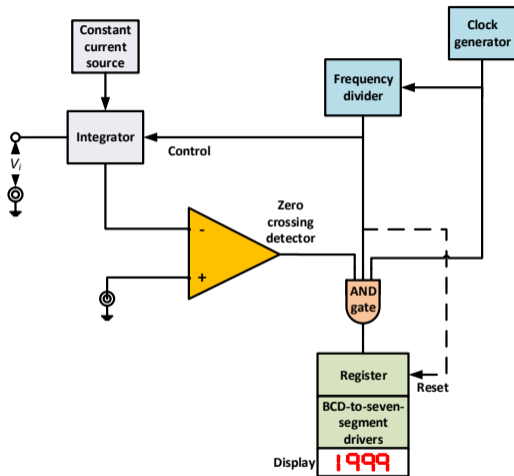

Dual Slope DVM block

- The **control** signal is derived from the clock generator and a frequency divider.
- During the charging, the integrator is charged to  $V_o$  that is depend on  $V_i$ .
- During the discharging, the integrator is discharged in constant rate in duration  $t_2$  that is depend on  $V_o$  and hence on  $V_i$ .
- A voltage comparator is used as **zero-crossing-detector** to output high if integrator voltage is lower than zero.

# Ramp Type Digital Voltmeters:

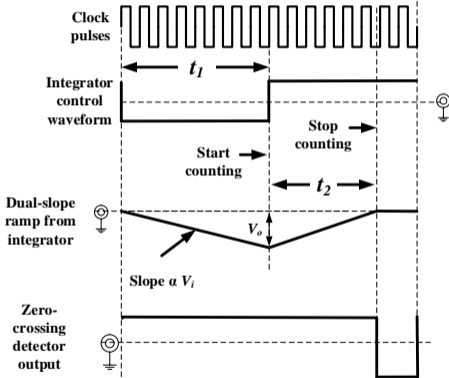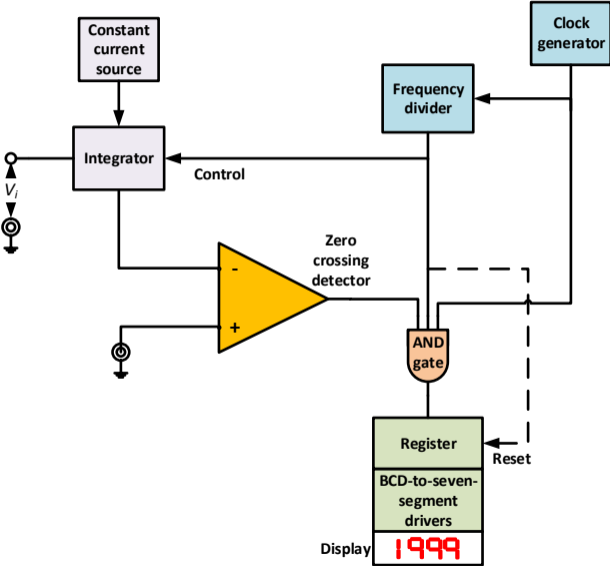

DVM waveform

# Ramp Type Digital Voltmeters:

How the Dual slope integrator DVM eliminates the need for accurate timing ?

(1) During charging:

$$V_o = -V_i t_1$$


(2) During discharging:

$$V_o = K t_2 \quad K \text{ is constant}$$

So,

$$V_i = -K \frac{t_2}{t_1}$$

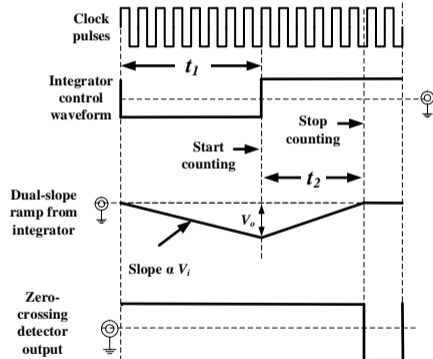Thus the input voltage measurement is not dependent on the clock frequency, but depends on the ratio  $\frac{t_1}{t_2}$ .



DVM waveform

# Table of Contents


- 1 Introduction to Digital Voltmeters.
- 2 Ramp Type Digital Voltmeters.
- 3 Dual Slope Digital Voltmeters.
- 4 Range Changing.**
- 5 Digital Voltmeter Accuracy.
- 6 Types of Digital Multi-meters.


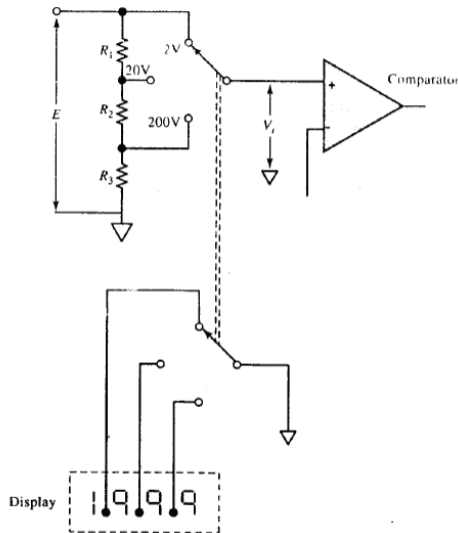
## Range Changing:

The attenuation circuit is used to select the range of input voltage:

- if  $V_{in} \leq 1.999V$ , the input is applied directly on the comparator.
- if  $1.999 \leq V_{in} \leq 19.99V$ , the input is attenuated and the decimal point is changed.
- and so on for  $19.99 \leq V_{in} \leq 199.9V$



DVM Range Changing

# Table of Contents

- 1 Introduction to Digital Voltmeters.
- 2 Ramp Type Digital Voltmeters.
- 3 Dual Slope Digital Voltmeters.
- 4 Range Changing.
- 5 Digital Voltmeter Accuracy.**
- 6 Types of Digital Multi-meters.

# Digital Voltmeter Accuracy:

## Accuracy in DVMs:

Digital voltmeter accuracy is usually stated as:

$$\pm(0.5\% \text{ rdg} + 1 \text{ digit})$$

where 1 *digit* refers to the extreme right (least significant digit).

### Example

If the accuracy is  $\pm(0.5\% \text{ rdg} + 1 \text{ digit})$  What is the maximum error of reading 1.800V on:

- (1) the 2V scale.
- (2) the 20V scale.

### Solution:

$$(1) \text{ error} = \pm[0.5\% \times 1.8V + 0.001] = 0.01V$$

$$(2) \text{ error} = \pm[0.5\% \times 1.8V + 0.01] = 0.019V$$

# Table of Contents

- 1 Introduction to Digital Voltmeters.
- 2 Ramp Type Digital Voltmeters.
- 3 Dual Slope Digital Voltmeters.
- 4 Range Changing.
- 5 Digital Voltmeter Accuracy.
- 6 Types of Digital Multi-meters.**

# Types of Digital Multi-meters:

## Hand-held Multimeter



## Bench-type Multimeter



# Types of Digital Multi-meters:

## Clamp Meters




### Clamp Meter

It is an electrical device having two jaws which open to allow **clamping around an electrical conductor**. This allows properties of the electric current in the conductor to be measured, **without having to make physical contact with it**, or to **disconnect it for insertion through the probe**.

# Types of Digital Multi-meters:

## Clamp Meters

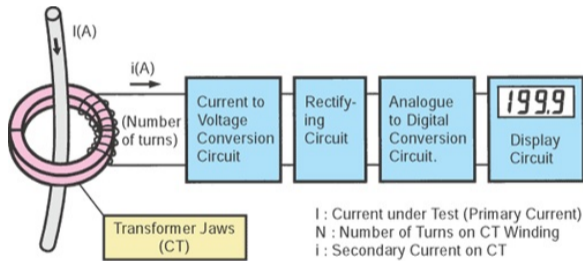

$I$  : Current under Test (Primary Current)  
 $N$  : Number of Turns on CT Winding  
 $i$  : Secondary Current on CT

$$i = \frac{I}{N} (A)$$

## How Do Clamp Meters Operate ?

AC clamp meters operate on the principle of current transformer(CT) used to pick up magnetic flux generated as a result of current flowing through a conductor. Assuming a current flowing through a conductor to be the primary current, you can obtain a current proportional to the primary current by electromagnetic induction from the secondary side(winding) of the transformer which is connected to a measuring circuit of the instrument. This permits you to take an AC current reading on the digital display.

# End of Lecture

Best Wishes