

ECE 321C

Electronic Circuits


Lec. 3: BJT Modeling and re Transistor Model (small signal analysis)

Instructor

Dr. Maher Abdelrasoul

<http://www.bu.edu.eg/staff/mahersalem3>

Agenda

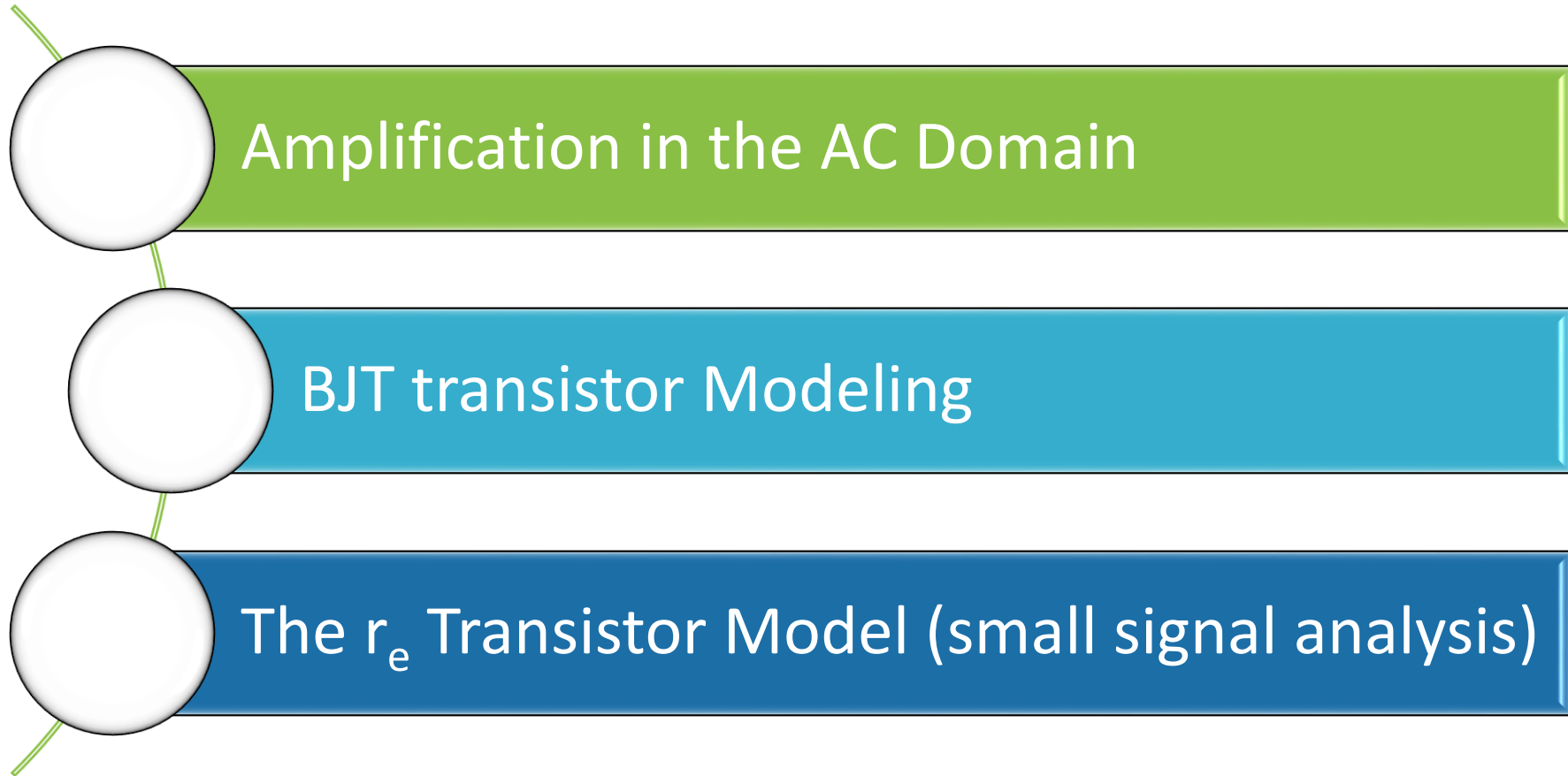

Amplification in the AC Domain

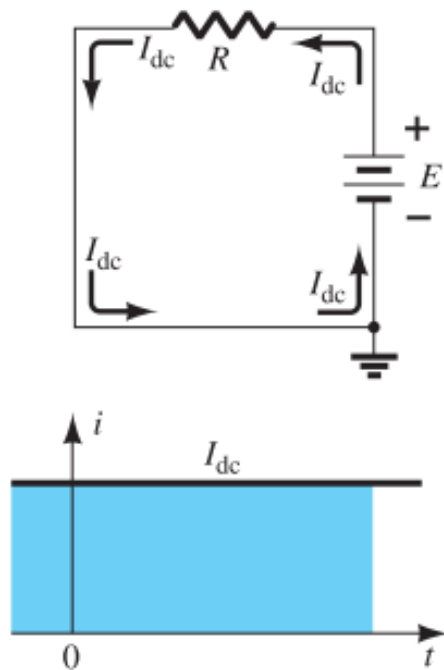


FIG. 5.1

Steady current established by a dc supply.

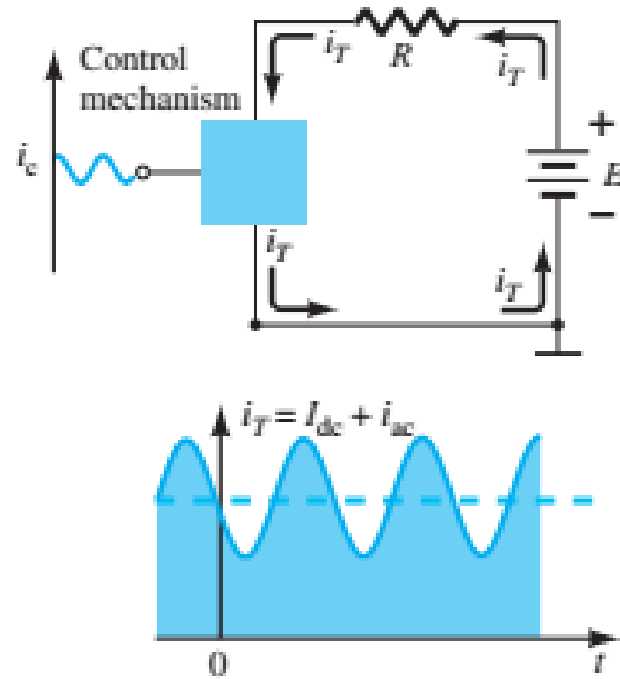




FIG. 5.2

Effect of a control element on the steady-state flow of the electrical system of Fig. 5.1.

The superposition theorem is applicable for the analysis and design of the DC and AC components of a BJT network, permitting the separation of the analysis of the dc and ac responses of the system.




BJT Transistor Modeling_{1/2}

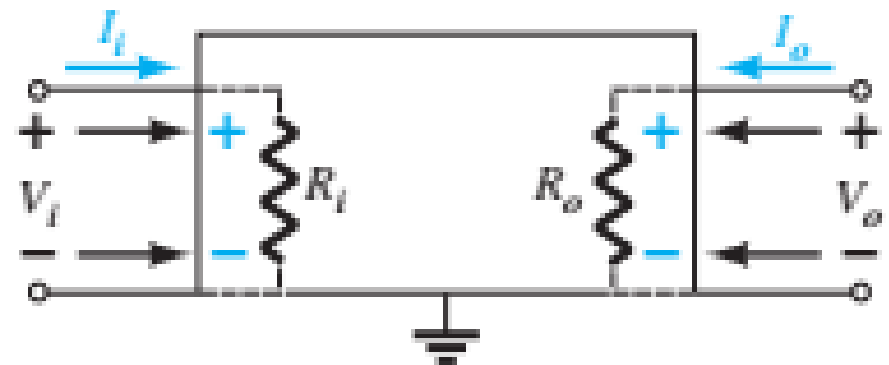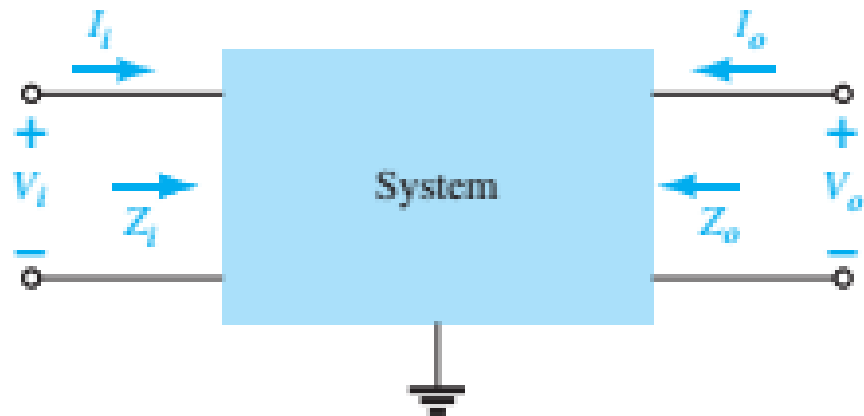- A **model** is a combination of circuit elements, properly chosen, that best approximates the actual behavior of a semiconductor device under specific operating conditions.
- Any electronic system has some important parameters have to be determined
 - Input and Output Voltage
 - Input and Output Impedance
 - Input and Output Current



BJT Transistor Modeling_{2/2}

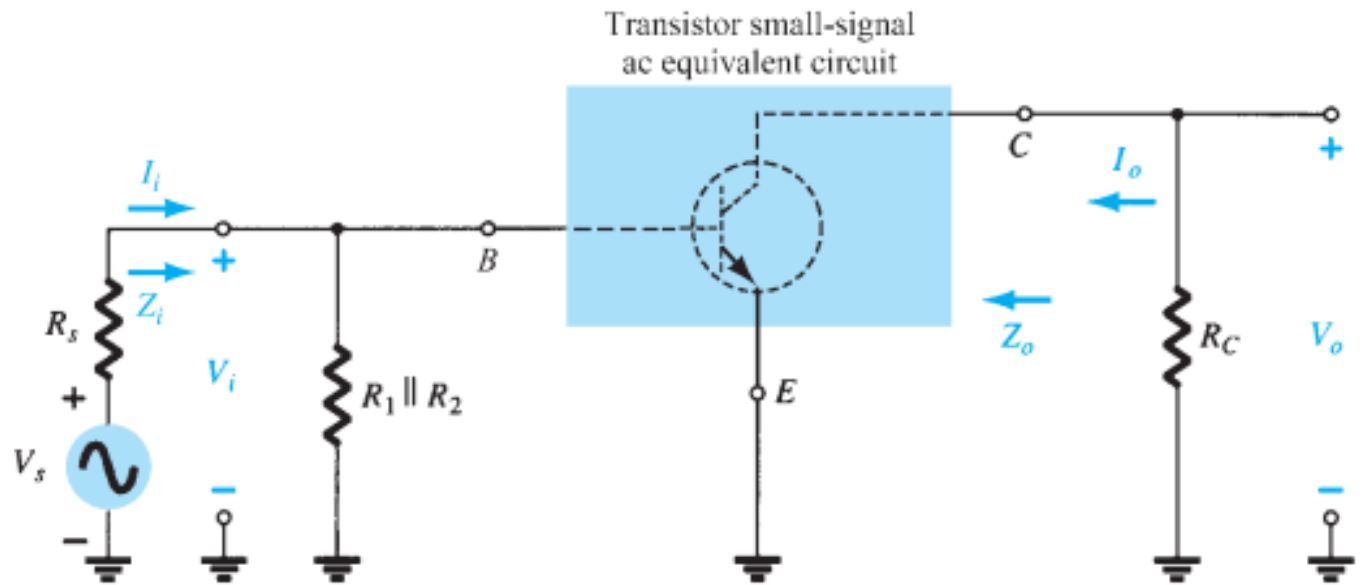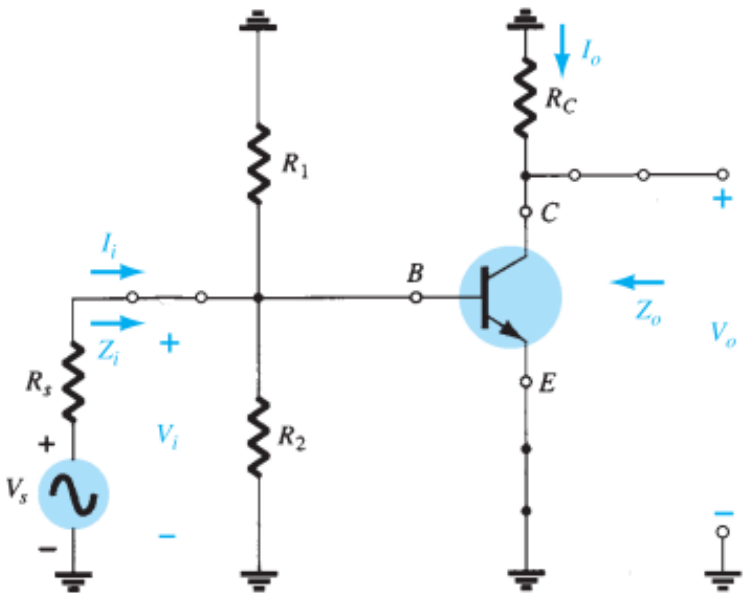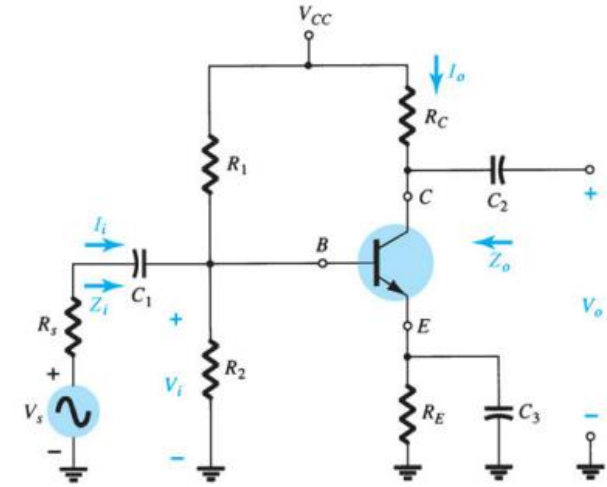- The **ac equivalent** of a transistor network is obtained by:
 - Setting all dc sources to zero and replacing them by a short-circuit equivalent
 - Replacing all capacitors by a short-circuit equivalent
 - Removing all elements bypassed by the short-circuit equivalents introduced by steps 1 and 2
 - Redrawing the network in a more convenient and logical form



The r_e Transistor Model (CE)_{1/4}

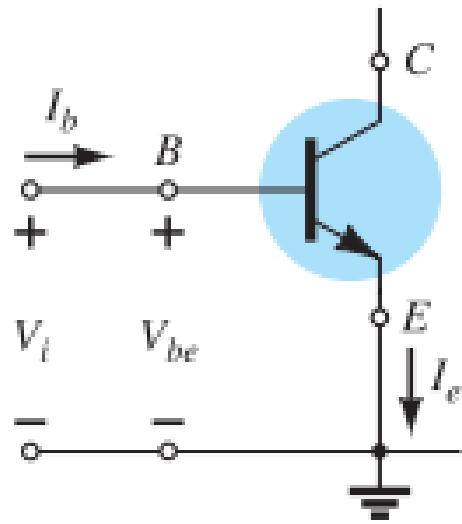


FIG. 5.8

Finding the input equivalent circuit for a BJT transistor.

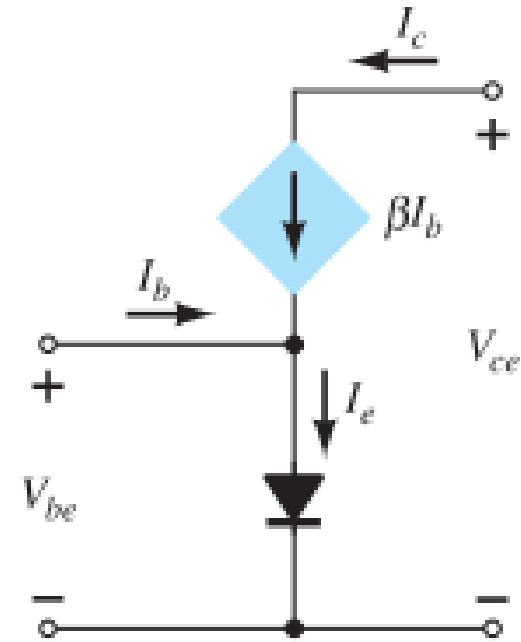


FIG. 5.12

BJT equivalent circuit.

The r_e Transistor Model (CE) _{2/4}


$$Z_i = \frac{V_i}{I_b} = \frac{V_{be}}{I_b}$$

$$V_{be} = I_e r_e = (I_c + I_b) r_e = (\beta I_b + I_b) r_e$$

$$= (\beta + 1) I_b r_e$$

$$Z_i = \frac{V_{be}}{I_b} = \frac{(\beta + 1) I_b r_e}{I_b}$$
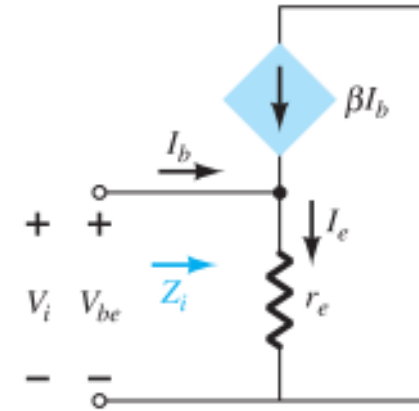
$$Z_i = (\beta + 1) r_e \cong \beta r_e$$



$$r_e = 26 \text{ mV} / I_E$$

FIG. 5.13

Defining the level of Z_i .

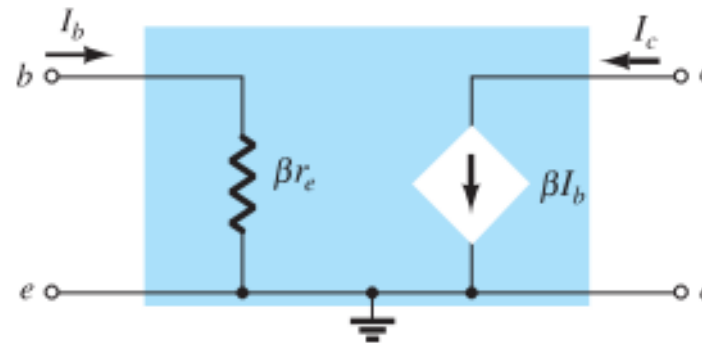


FIG. 5.14

Improved BJT equivalent circuit.

The r_e Transistor Model (CE) _{3/4}

$$r_o = \frac{\Delta V}{\Delta I} = \frac{V_A + V_{CEQ}}{I_{CQ}}$$

$$r_o \cong \frac{V_A}{I_{CQ}}$$

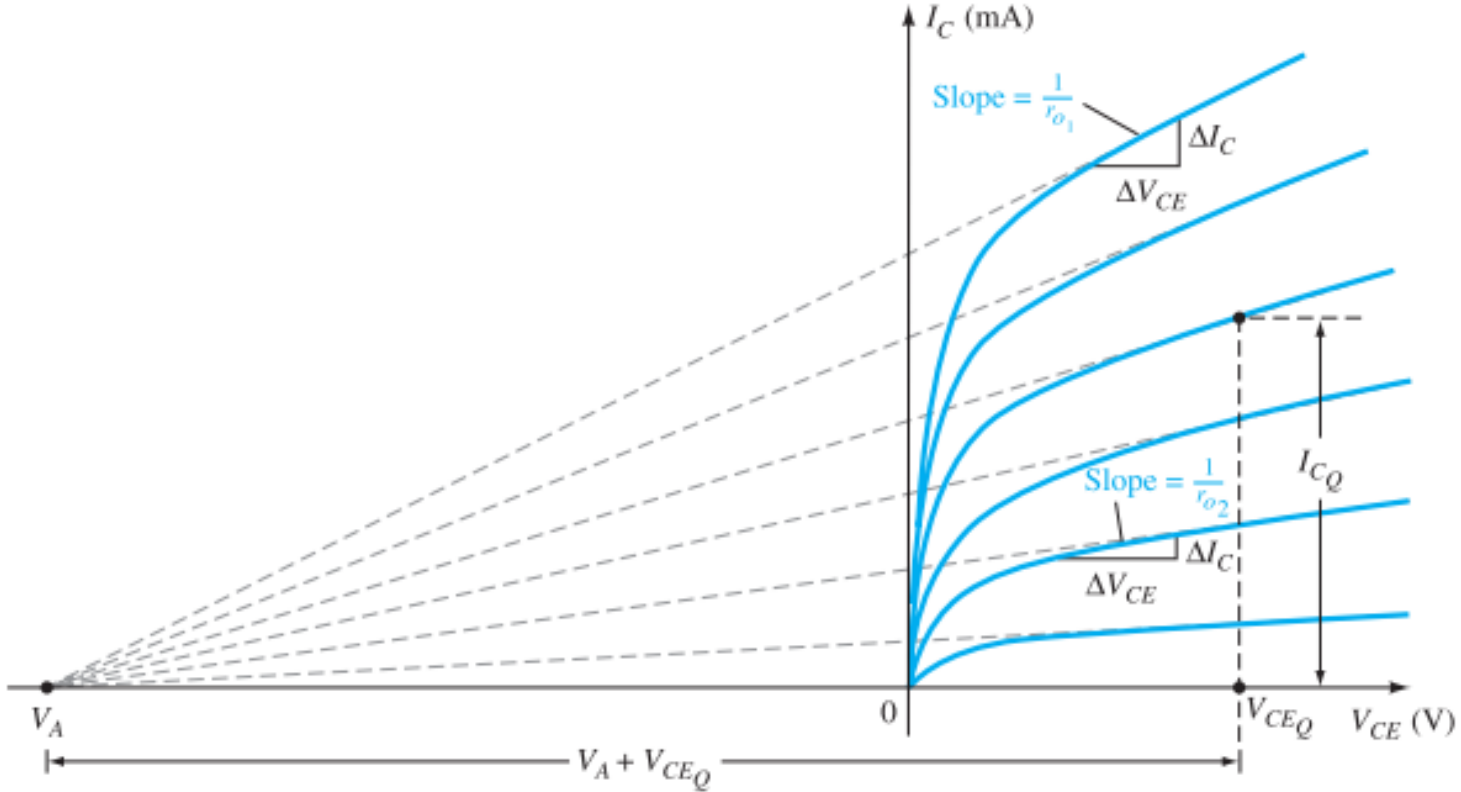


FIG. 5.15

Defining the Early voltage and the output impedance of a transistor.

The r_e Transistor Model (CE) 4/4

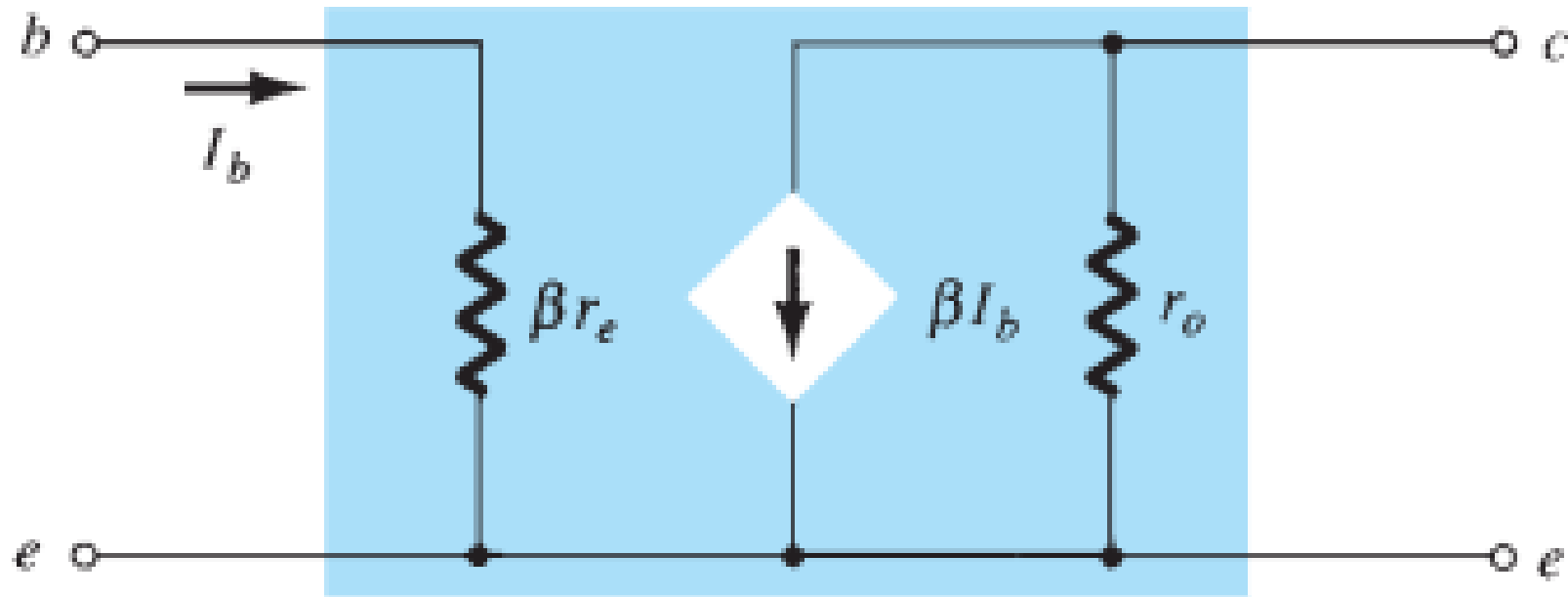


FIG. 5.16

r_e model for the common-emitter transistor configuration including effects of r_o

C.E. Voltage-Divider Bias_{1/2}

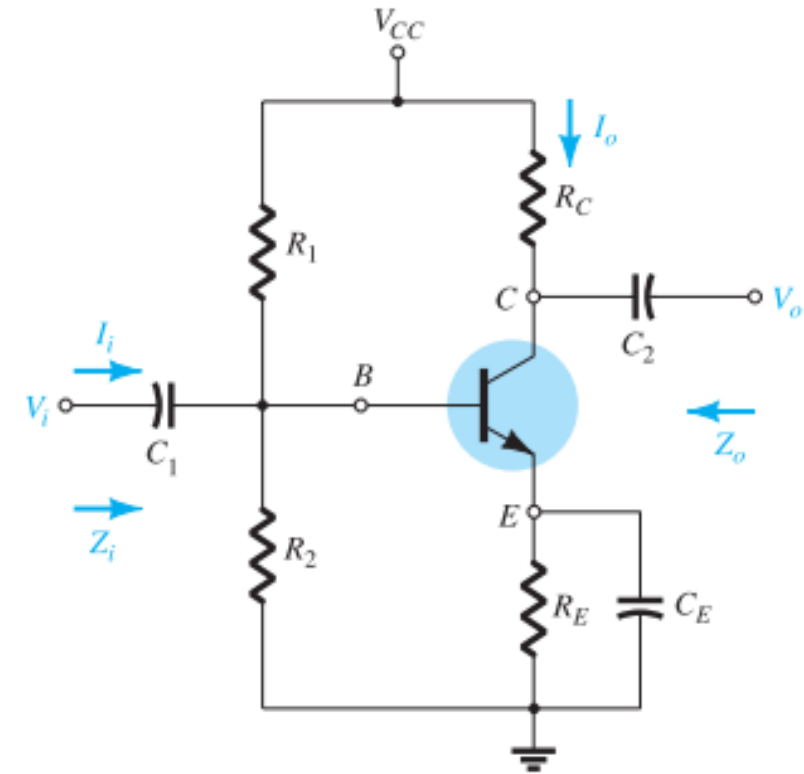


FIG. 5.26

Voltage-divider bias configuration.

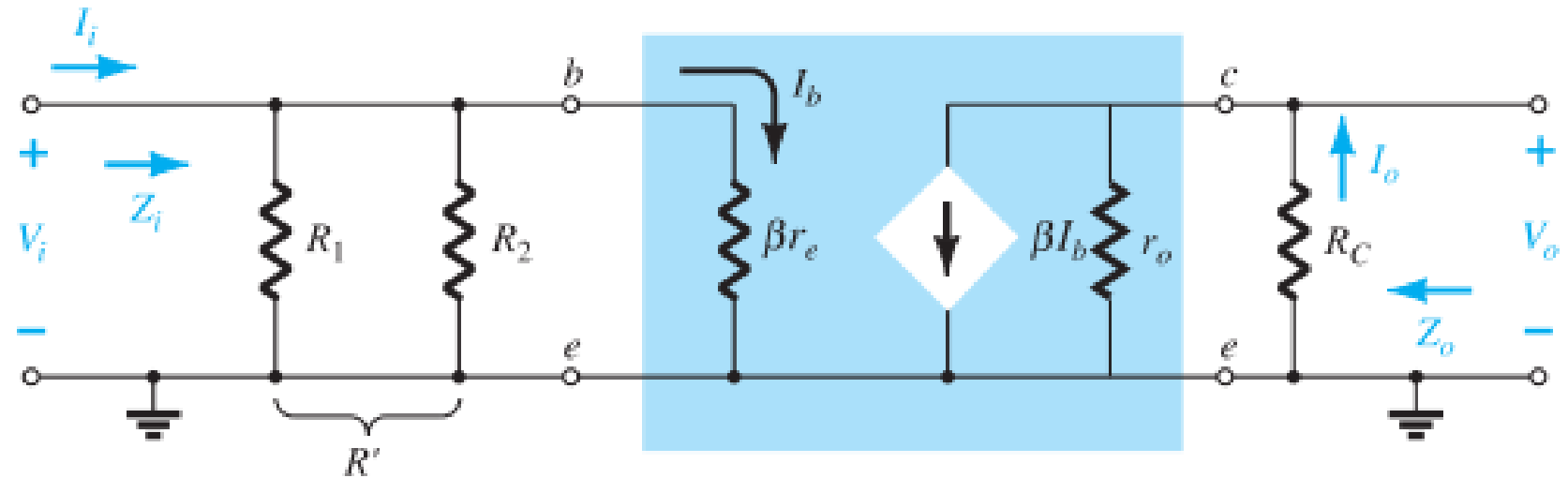


FIG. 5.27

Substituting the r_e equivalent circuit into the ac equivalent network of Fig. 5.26.

C.E. Voltage-Divider Bias_{2/2}

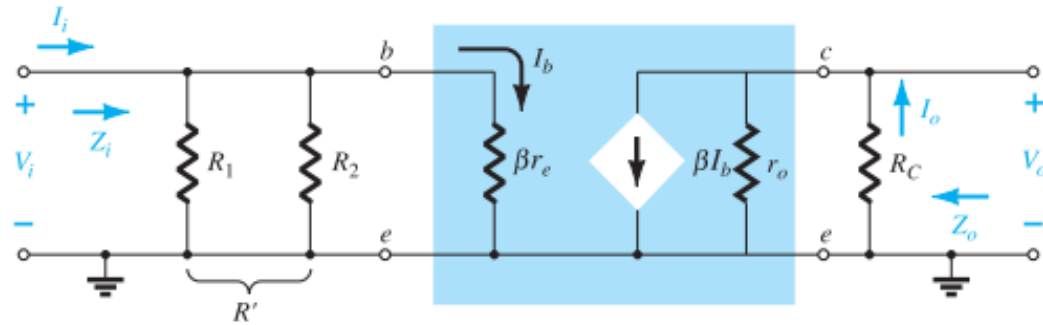


FIG. 5.27

Substituting the r_e equivalent circuit into the ac equivalent network of Fig. 5.26.

$$R' = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

$$Z_i = R' \parallel \beta r_e$$

$$Z_o = R_C \parallel r_o$$

$$Z_o \cong R_C$$

$$r_o \geq 10R_C$$

$$V_o = -(\beta I_b)(R_C \parallel r_o)$$

$$I_b = \frac{V_i}{\beta r_e}$$




$$V_o = -\beta \left(\frac{V_i}{\beta r_e} \right) (R_C \parallel r_o)$$




$$A_v = \frac{V_o}{V_i} = \frac{-R_C \parallel r_o}{r_e}$$



$$A_v = \frac{V_o}{V_i} \cong -\frac{R_C}{r_e}$$

$$r_o \geq 10R_C$$

180° phase shift

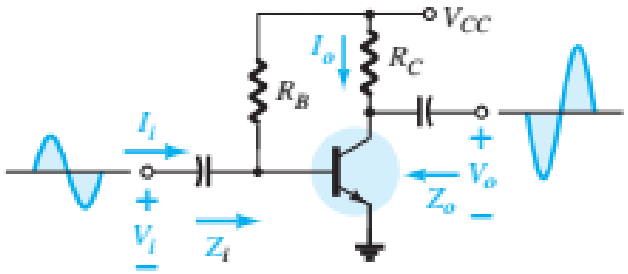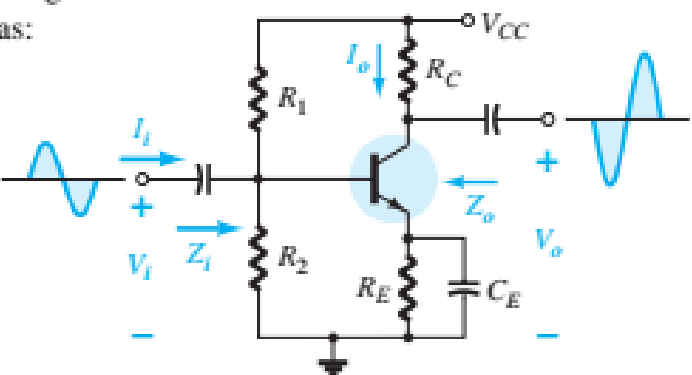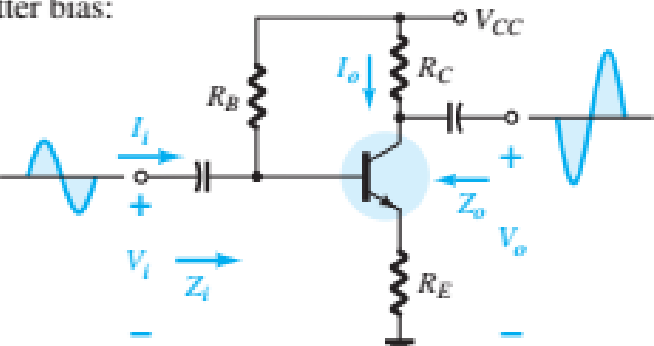Configuration	Z_i	Z_o	A_v	A_i
Fixed-bias: 	Medium (1 k Ω) $= R_B \parallel \beta r_e$ $\equiv \beta r_e$ ($R_B \geq 10\beta r_e$)	Medium (2 k Ω) $= R_C \parallel r_o$ $\equiv R_C$ ($r_o \geq 10R_C$)	High (-200) $= -\frac{(R_C \parallel r_o)}{r_e}$ $\equiv -\frac{R_C}{r_e}$ ($r_o \geq 10R_C$)	High (100) $= \frac{\beta R_B r_o}{(r_o + R_C)(R_B + \beta r_e)}$ $\equiv \beta$ ($r_o \geq 10R_C$, $R_B \geq 10\beta r_e$)
Voltage-divider bias: 	Medium (1 k Ω) $= R_1 \parallel R_2 \parallel \beta r_e$	Medium (2 k Ω) $= R_C \parallel r_o$ $\equiv R_C$ ($r_o \geq 10R_C$)	High (-200) $= -\frac{R_C \parallel r_o}{r_e}$ $\equiv -\frac{R_C}{r_e}$ ($r_o \geq 10R_C$)	High (50) $= \frac{\beta(R_1 \parallel R_2)r_o}{(r_o + R_C)(R_1 \parallel R_2 + \beta r_e)}$ $\equiv \frac{\beta(R_1 \parallel R_2)}{R_1 \parallel R_2 + \beta r_e}$ ($r_o \geq 10R_C$)
Unbypassed emitter bias: 	High (100 k Ω) $= R_B \parallel Z_b$ $Z_b \equiv \beta(r_e + R_E)$ $\equiv R_B \parallel \beta R_E$ ($R_E \gg r_e$)	Medium (2 k Ω) $= R_C$ (any level of r_o)	Low (-5) $= -\frac{R_C}{r_e + R_E}$ $\equiv -\frac{R_C}{R_E}$ ($R_E \gg r_e$)	High (50) $\equiv \frac{\beta R_B}{R_B + Z_b}$

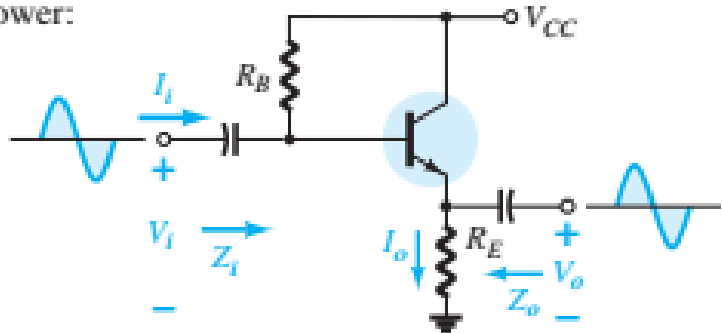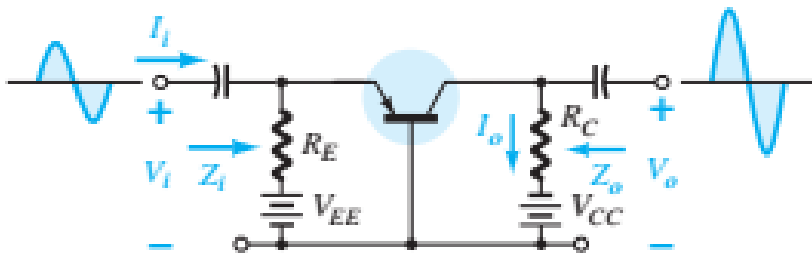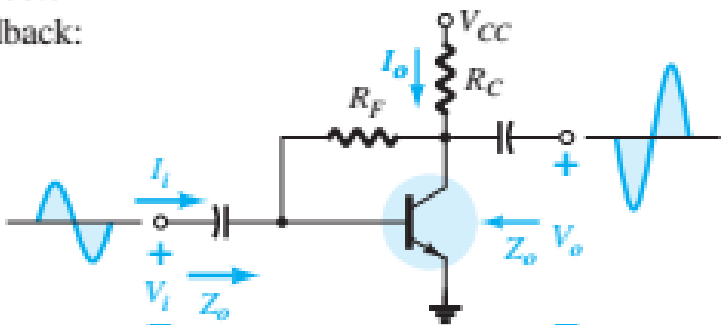Configuration	Z_i	Z_o	A_v	A_i
Emitter-follower: 	High (100 k Ω) $= R_B \parallel Z_b$ $Z_b \equiv \beta(r_e + R_E)$ $\equiv R_B \parallel \beta R_E$ $(R_E \gg r_e)$	Low (20 Ω) $= R_E \parallel r_e$ $\equiv r_e$ $(R_E \gg r_e)$	Low ($\cong 1$) $= \frac{R_E}{R_E + r_e}$ $\equiv 1$	High (≈ 50) $\equiv \frac{\beta R_B}{R_B + Z_b}$
Common-base: 	Low (20 Ω) $= R_E \parallel r_e$ $\equiv r_e$ $(R_E \gg r_e)$	Medium (2 k Ω) $= R_C$	High (200) $\equiv \frac{R_C}{r_e}$	Low (-1) $\equiv -1$
Collector feedback: 	Medium (1 k Ω) $= \frac{r_e}{\frac{1}{\beta} + \frac{R_C}{R_F}}$ $(r_o \geq 10R_C)$	Medium (2 k Ω) $\equiv R_C \parallel R_F$ $(r_o \geq 10R_C)$	High (≈ 200) $\equiv \frac{R_C}{r_e}$ $(r_o \geq 10R_C)$ $(R_F \gg R_C)$	High (50) $= \frac{\beta R_F}{R_F + \beta R_C}$ $\equiv \frac{R_F}{R_C}$

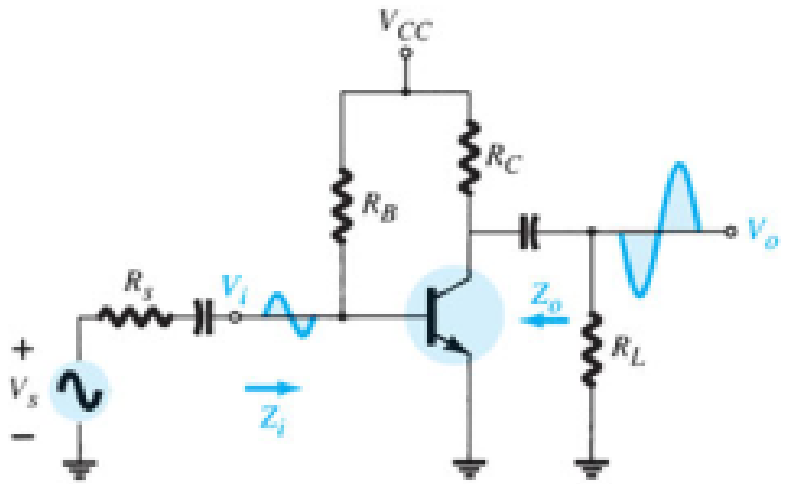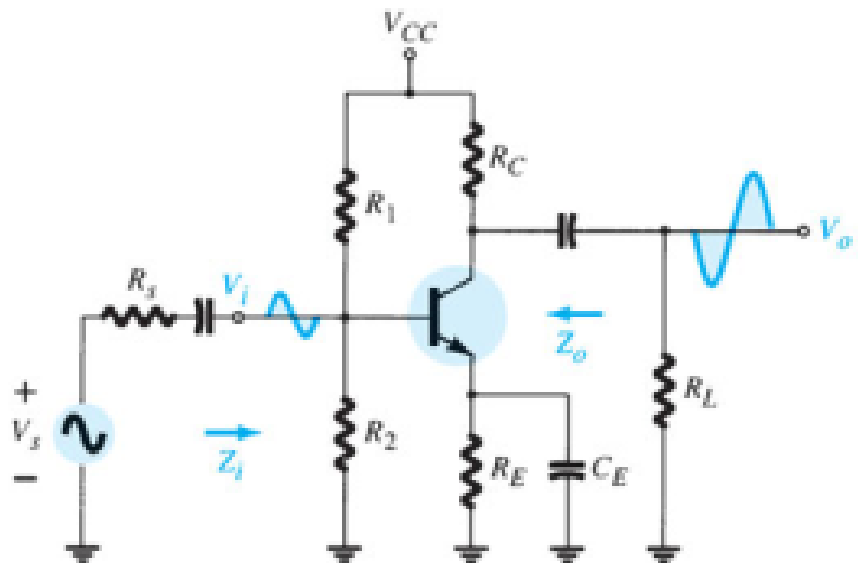Configuration	$A_{v_L} = V_o/V_i$	Z_i	Z_o
	$\frac{-(R_L \parallel R_C)}{r_e}$	$R_B \parallel \beta r_e$	R_C
	$\frac{-(R_L \parallel R_C)}{r_e}$	$R_1 \parallel R_2 \parallel \beta r_e$	R_C
<p>Including r_o:</p>	$\frac{-(R_L \parallel R_C \parallel r_o)}{r_e}$	$R_B \parallel \beta r_e$	$R_C \parallel r_o$

Configuration	$A_{v_L} = V_o/V_i$	Z_i	Z_o
	$\cong 1$	$R'_E = R_L \parallel R_E$ $R_1 \parallel R_2 \parallel \beta(r_e + R'_E)$	$R'_s = R_s \parallel R_1 \parallel R_2$ $R_E \parallel \left(\frac{R'_s}{\beta} + r_e \right)$
	Including r_o : $\cong 1$	$R_1 \parallel R_2 \parallel \beta(r_e + R'_E)$	$R_E \parallel \left(\frac{R'_s}{\beta} + r_e \right)$
	$\cong \frac{-(R_L \parallel R_C)}{r_e}$	$R_E \parallel r_e$	R_C
	Including r_o : $\cong \frac{-(R_L \parallel R_C \parallel r_o)}{r_e}$	$R_E \parallel r_e$	$R_C \parallel r_o$
	$\frac{-(R_L \parallel R_C)}{R_E}$	$R_1 \parallel R_2 \parallel \beta(r_e + R_E)$	R_C
	Including r_o : $\frac{-(R_L \parallel R_C)}{R_E}$	$R_1 \parallel R_2 \parallel \beta(r_e + R_e)$	$\cong R_C$

Configuration	$A_{v_L} = V_o/V_i$	Z_i	Z_o
	$\frac{-(R_L \parallel R_C)}{R_{E1}}$	$R_B \parallel \beta(r_e + R_{E1})$	R_C
	Including r_o : $\frac{-(R_L \parallel R_C)}{R_{E1}}$	$R_B \parallel \beta(r_e + R_E)$	$\equiv R_C$
	$\frac{-(R_L \parallel R_C)}{r_e}$	$\beta r_e \parallel \frac{R_F}{ A_v }$	R_C
	Including r_o : $\frac{-(R_L \parallel R_C \parallel r_o)}{r_e}$	$\beta r_e \parallel \frac{R_F}{ A_v }$	$R_C \parallel R_F \parallel r_o$
	$\frac{-(R_L \parallel R_C)}{R_E}$	$\beta R_E \parallel \frac{R_F}{ A_v }$	$\equiv R_C \parallel R_F$
	Including r_o : $\equiv \frac{-(R_L \parallel R_C)}{R_E}$	$\equiv \beta R_E \parallel \frac{R_F}{ A_v }$	$\equiv R_C \parallel R_F$

Thank You!

