

# ECE 321C

# Electronic Circuits


Lec. 5: BJT Modeling and re Transistor Model (Hybrid Equivalent Model) (2)

Instructor

**Dr. Maher Abdelrasoul**

**<http://www.bu.edu.eg/staff/mahersalem3>**

# Agenda

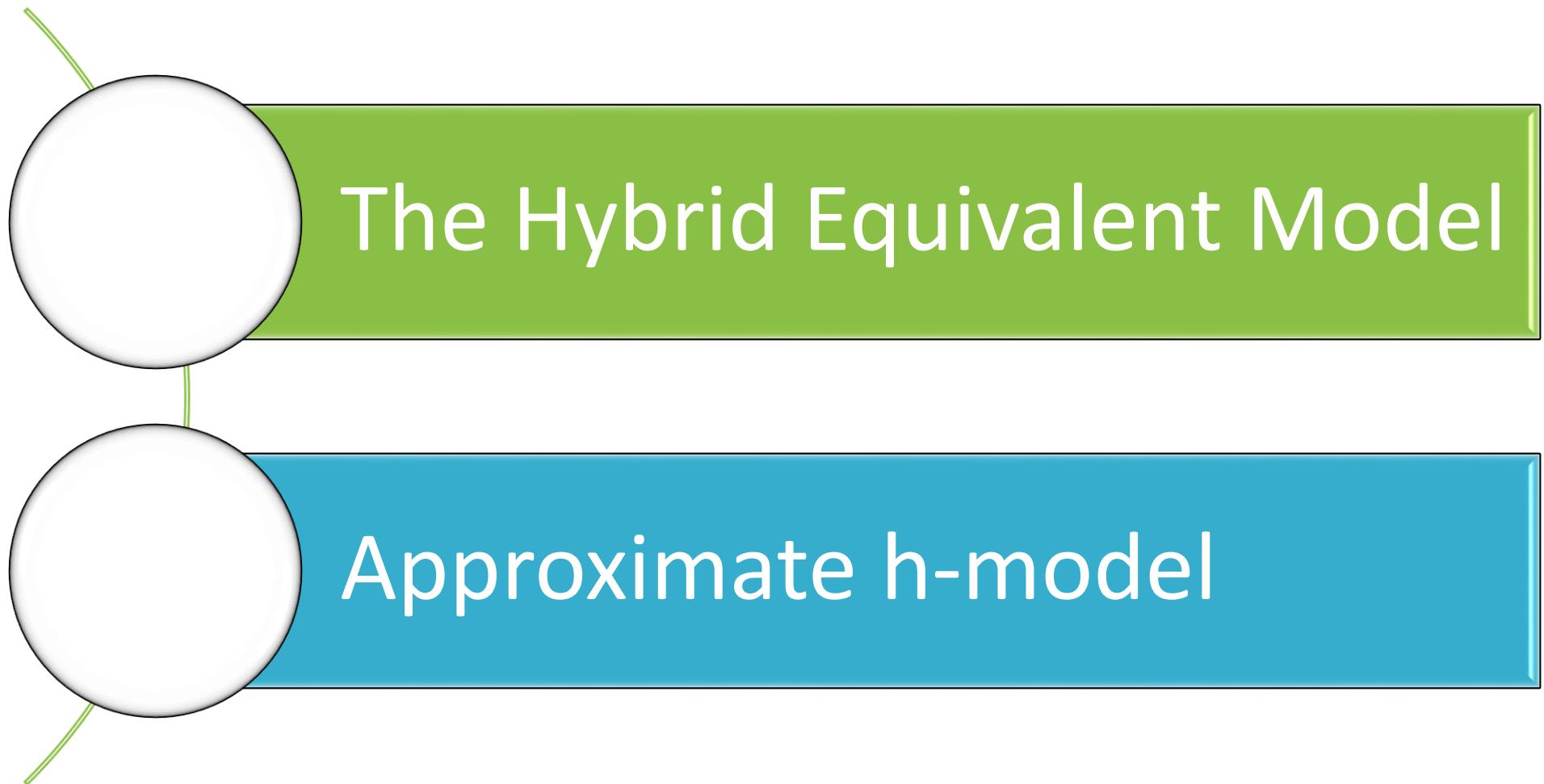

# The Hybrid Equivalent Model


# The Hybrid Equivalent Model

- Main Difference between  $r_e$  and H model is that:
  - The  $r_e$  model has the advantage that the parameters are defined by the actual operating conditions
  - The parameters of the hybrid equivalent circuit are defined in general terms for any operating conditions.

		Min.	Max.	
Input impedance ( $I_C = 1 \text{ mA dc}, V_{CE} = 10 \text{ V dc}, f = 1 \text{ kHz}$ )	$h_{ie}$	0.5	7.5	$\text{k}\Omega$
Voltage feedback ratio ( $I_C = 1 \text{ mA dc}, V_{CE} = 10 \text{ V dc}, f = 1 \text{ kHz}$ )	$h_{re}$	0.1	8.0	$\times 10^{-4}$
Small-signal current gain ( $I_C = 1 \text{ mA dc}, V_{CE} = 10 \text{ V dc}, f = 1 \text{ kHz}$ )	$h_{fe}$	20	250	—
Output admittance ( $I_C = 1 \text{ mA dc}, V_{CE} = 10 \text{ V dc}, f = 1 \text{ kHz}$ )	$h_{oe}$	1.0	30	$1 \mu\text{S}$

**FIG. 5.92**  
*Hybrid parameters for the 2N4400 transistor.*

# The Hybrid Equivalent Model

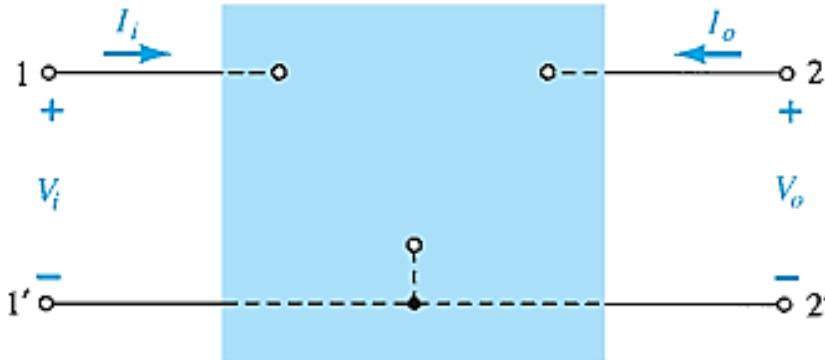

$$V_i = h_{11}I_i + h_{12}V_o$$

$$I_o = h_{21}I_i + h_{22}V_o$$

**FIG. 5.93**

Two-port system.

$$h_{11} = \frac{V_i}{I_i} \Big|_{V_o=0}$$

ohms → short-circuit input-impedance parameter

$$h_{21} = \frac{I_o}{I_i} \Big|_{V_o=0}$$

unitless → short-circuit forward transfer current ratio parameter

$$h_{12} = \frac{V_i}{V_o} \Big|_{I_i=0}$$

unitless → open-circuit reverse transfer voltage ratio parameter

$$h_{22} = \frac{I_o}{V_o} \Big|_{I_i=0}$$

siemens → open-circuit output admittance parameter

# Transistor Hybrid Equivalent Circuit

- Hybrid Equivalent Circuit:

$$V_i = h_{11}I_i + h_{12}V_o$$

$$I_o = h_{21}I_i + h_{22}V_o$$

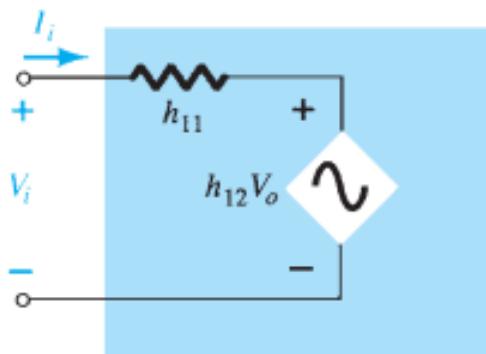


FIG. 5.94

Hybrid input equivalent circuit.

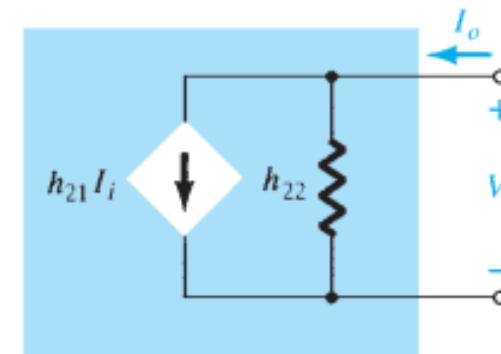


FIG. 5.95

Hybrid output equivalent circuit.

- For Transistor:

$h_{11} \rightarrow$  input resistance  $\rightarrow h_i$

$h_{12} \rightarrow$  reverse transfer voltage ratio  $\rightarrow h_r$

$h_{21} \rightarrow$  forward transfer current ratio  $\rightarrow h_f$

$h_{22} \rightarrow$  output conductance  $\rightarrow h_o$


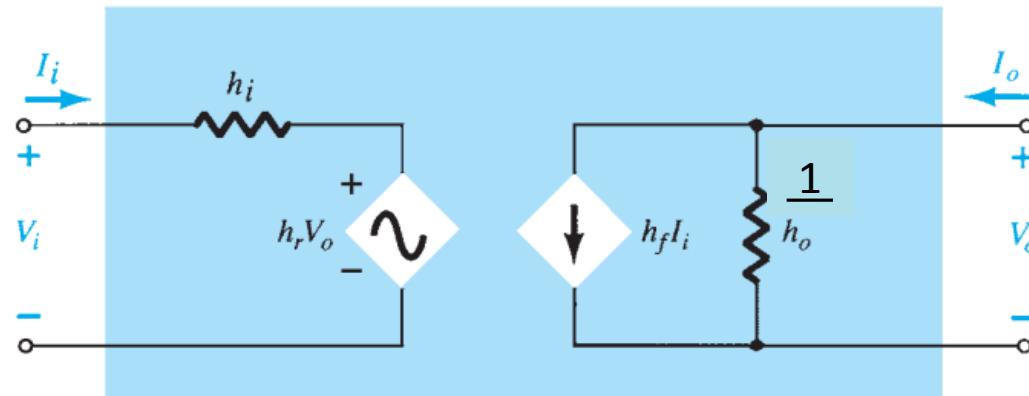


FIG. 5.96

Complete hybrid equivalent circuit.


# Transistor Hybrid Equivalent Circuit (CE)

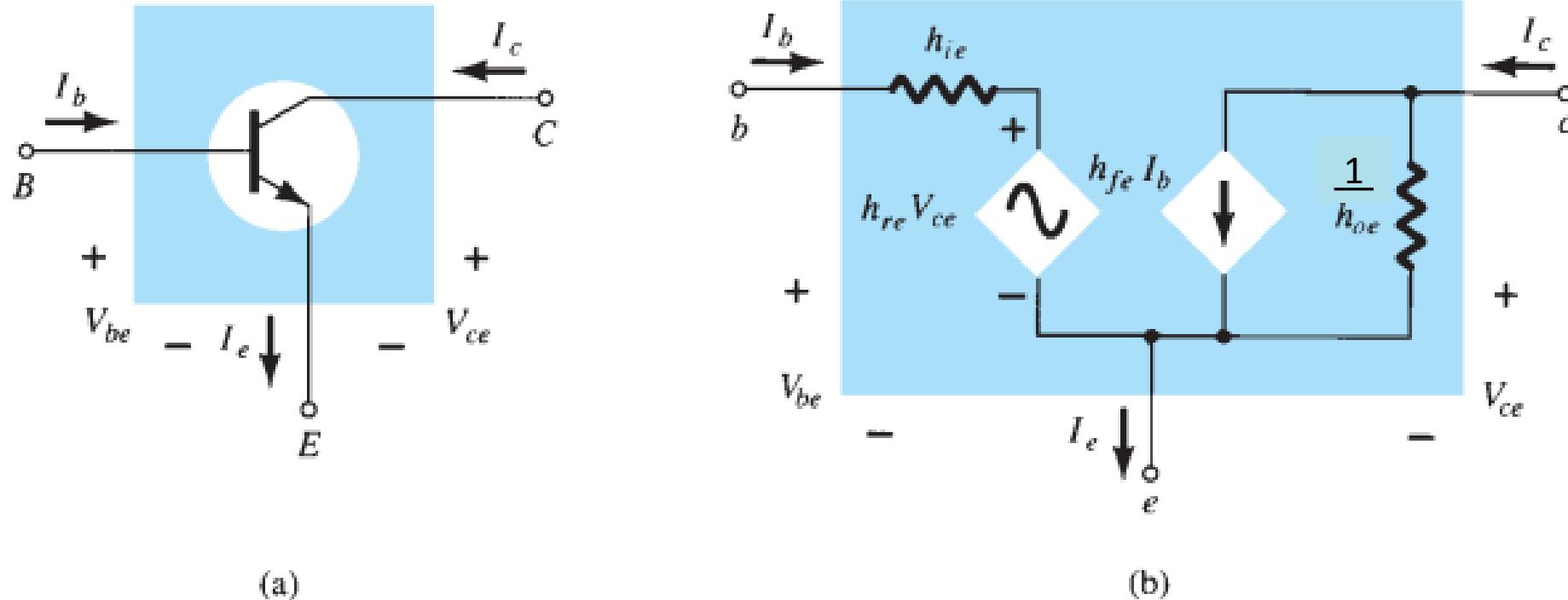

**FIG. 5.97**

Common-emitter configuration: (a) graphical symbol; (b) hybrid equivalent circuit.


# Transistor Hybrid Equivalent Circuit (CB)

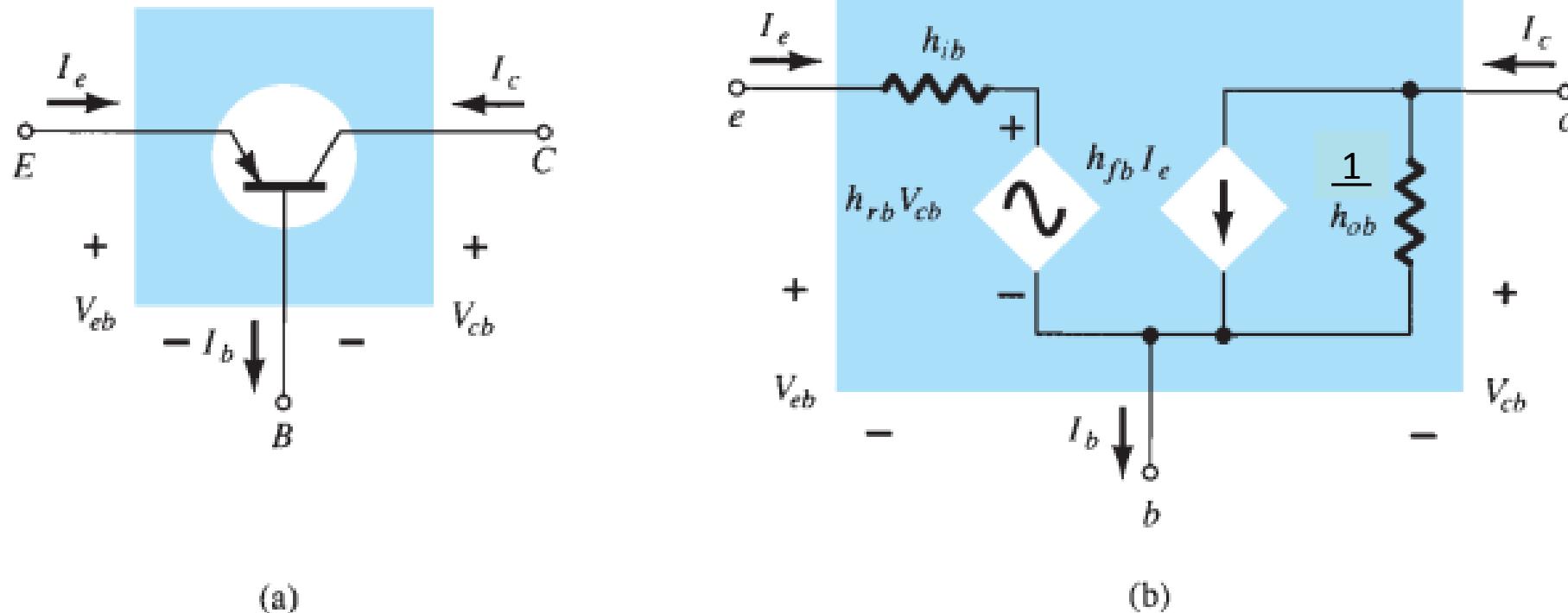

**FIG. 5.98**


Common-base configuration: (a) graphical symbol; (b) hybrid equivalent circuit.

# Hybrid Approximation

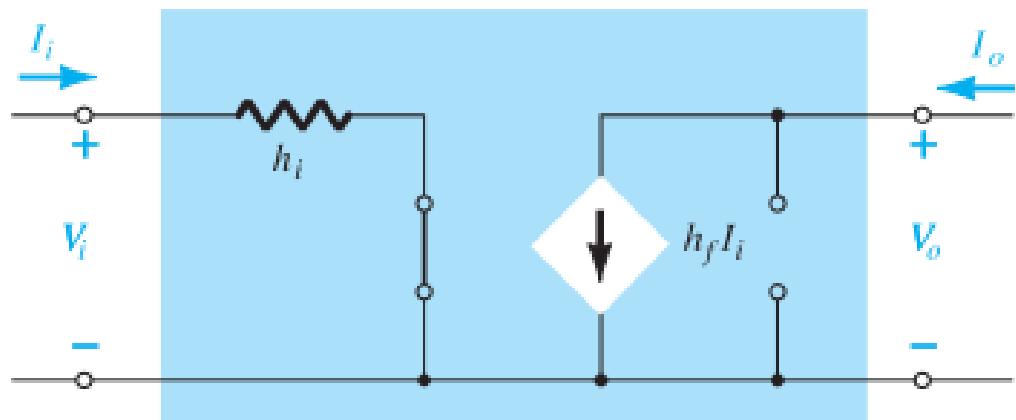

**FIG. 5.99**


*Effect of removing  $h_{re}$  and  $h_{oe}$  from the hybrid equivalent circuit.*

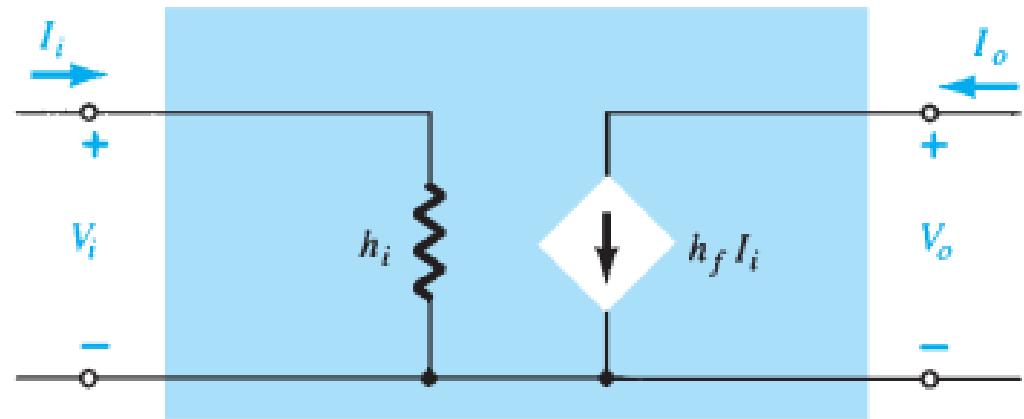

**FIG. 5.100**

*Approximate hybrid equivalent model.*

# Hybrid vs. $r_e$ model

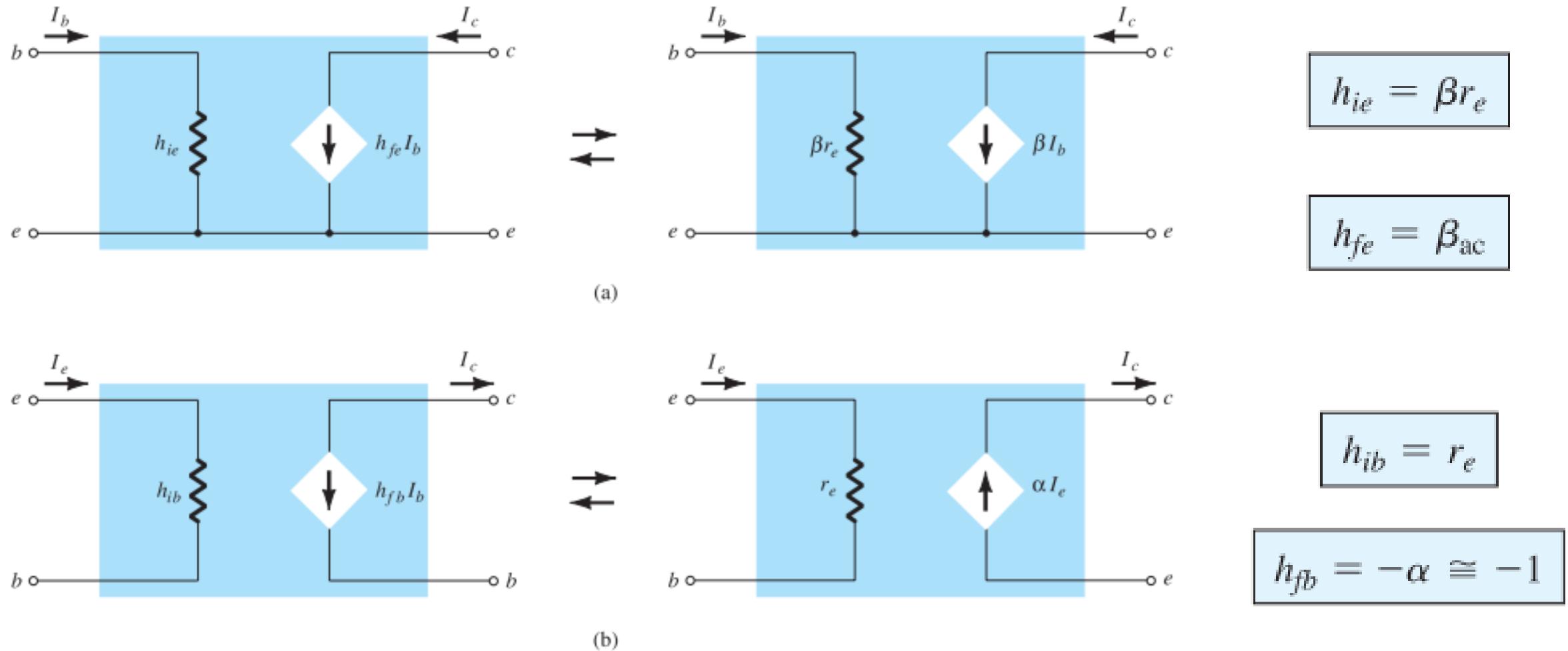

**FIG. 5.101**

Hybrid versus  $r_e$  model: (a) common-emitter configuration; (b) common-base configuration.

# Hybrid vs. $r_e$ model (Example)

**EXAMPLE 5.19** Given  $I_E = 2.5 \text{ mA}$ ,  $h_{fe} = 140$ ,  $h_{oe} = 20 \mu\text{S}$  ( $\mu\text{mho}$ ), and  $h_{ob} = 0.5 \mu\text{S}$ , determine:

- The common-emitter hybrid equivalent circuit.
- The common-base  $r_e$  model.

**Solution:**



$$\text{a. } r_e = \frac{26 \text{ mV}}{I_E} = \frac{26 \text{ mV}}{2.5 \text{ mA}} = 10.4 \Omega$$

$$h_{ie} = \beta r_e = (140)(10.4 \Omega) = 1.456 \text{ k}\Omega$$

$$r_o = \frac{1}{h_{oe}} = \frac{1}{20 \mu\text{S}} = 50 \text{ k}\Omega$$


$$\text{b. } r_e = 10.4 \Omega$$
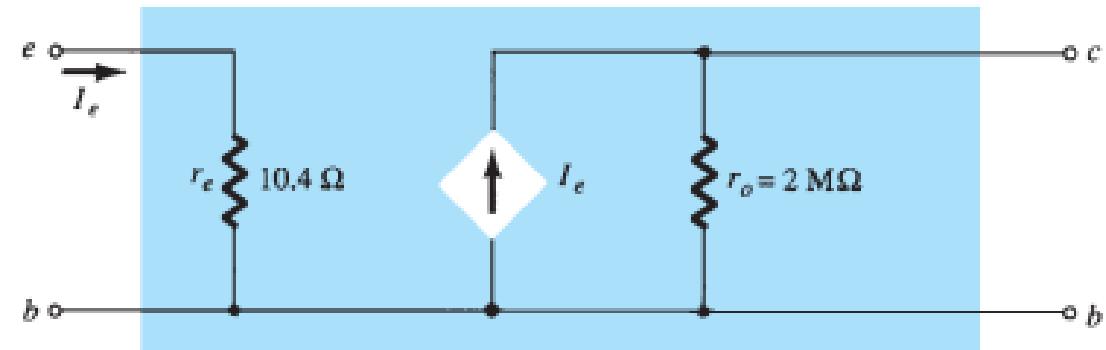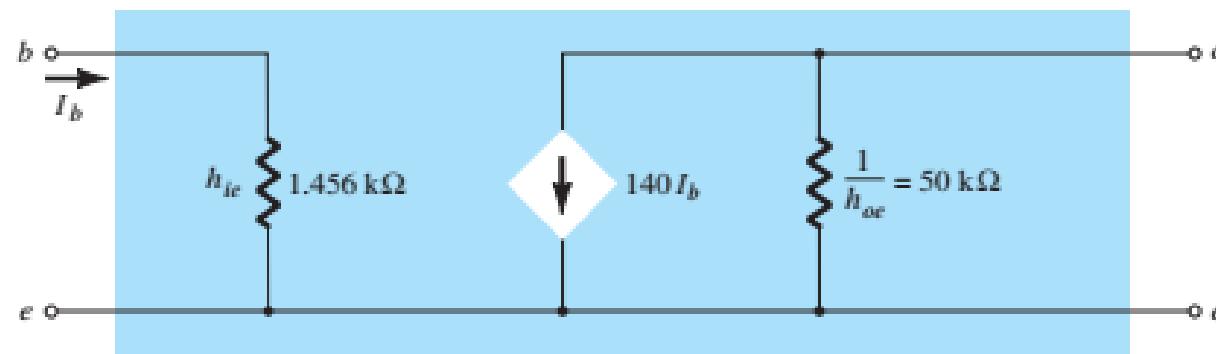
$$\alpha \approx 1, \quad r_o = \frac{1}{h_{ob}} = \frac{1}{0.5 \mu\text{S}} = 2 \text{ M}\Omega$$




# Approximate & Complete h-model

# Approximate h-model

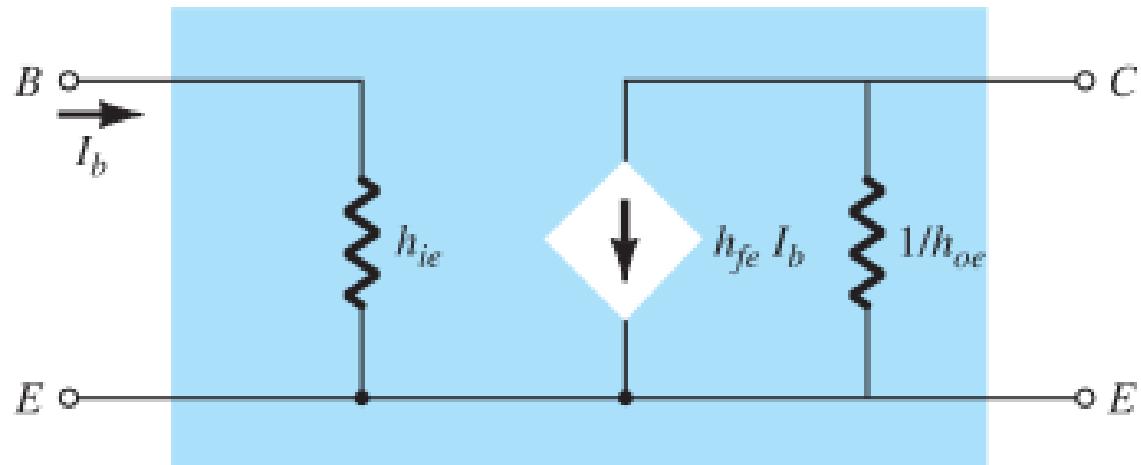

**FIG. 5.104**

Approximate common-emitter hybrid equivalent circuit.

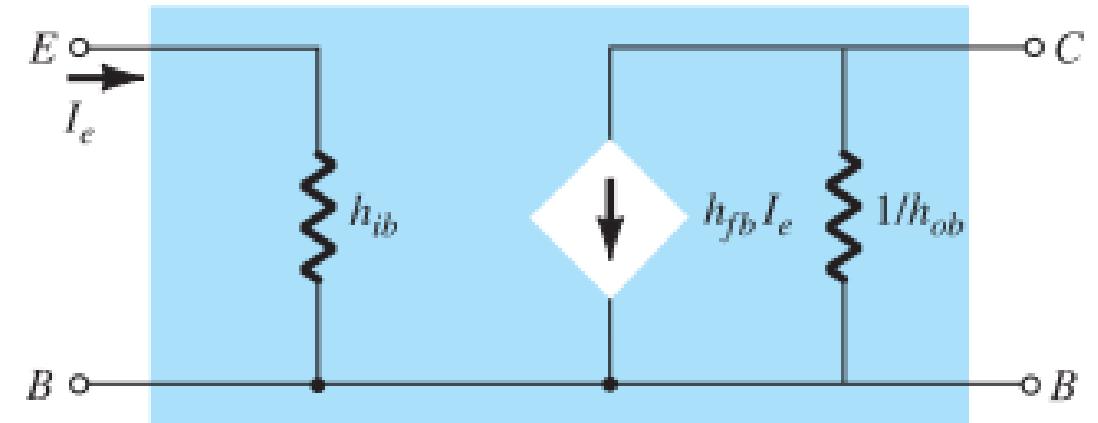


**FIG. 5.105**

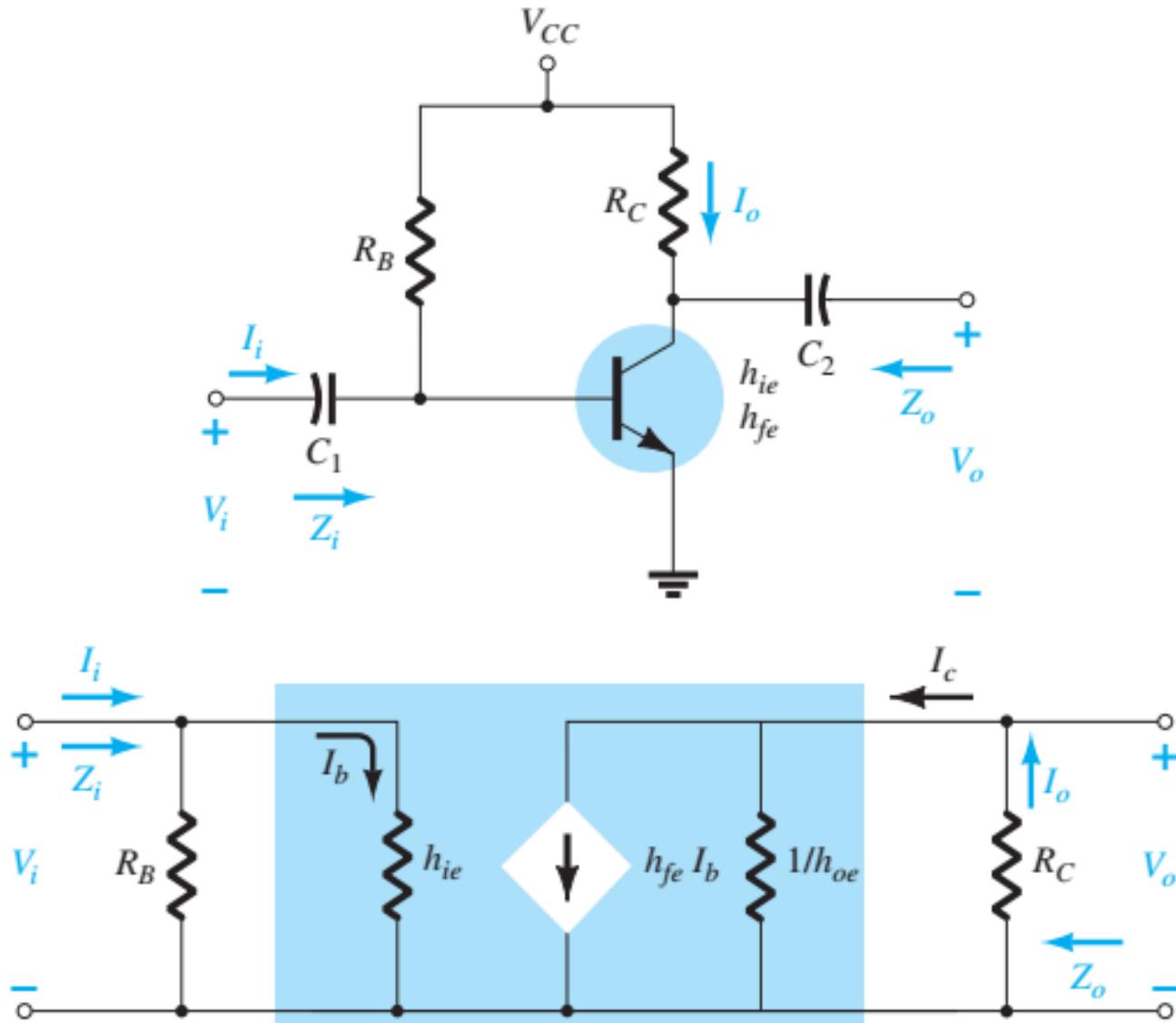Approximate common-base hybrid equivalent circuit.

# Approximate h-model

(Fixed Bias circuit)



$$Z_i = R_B \parallel h_{ie}$$

$$Z_o = R_C \parallel 1/h_{oe}$$

$$R' = 1/h_{oe} \parallel R_C$$

$$\begin{aligned} V_o &= -I_o R' = -I_C R' \\ &= -h_{fe} I_b R' \end{aligned}$$

$$I_b = \frac{V_i}{h_{ie}}$$

$$V_o = -h_{fe} \frac{V_i}{h_{ie}} R'$$


$$A_v = \frac{V_o}{V_i} = -\frac{h_{fe} (R_C \parallel 1/h_{oe})}{h_{ie}}$$

$$A_i = \frac{I_o}{I_i} \equiv h_{fe}$$

# Approximate h-model (Fixed Bias circuit, Example)

**EXAMPLE 5.20** For the network of Fig. 5.108, determine:

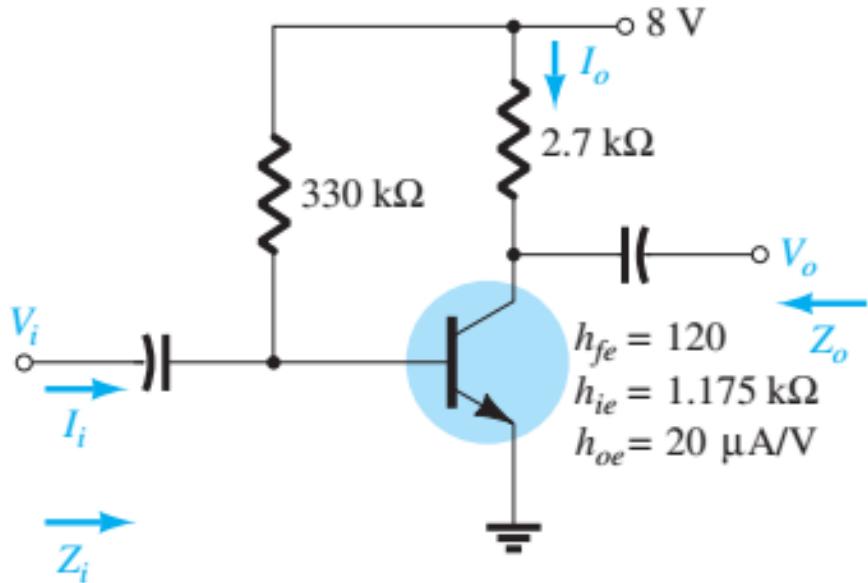- a.  $Z_i$ .
- b.  $Z_o$ .
- c.  $A_v$ .
- d.  $A_i$ .



**Solution:**

$$\begin{aligned} \text{a. } Z_i &= R_B \| h_{ie} = 330 \text{ k}\Omega \| 1.175 \text{ k}\Omega \\ &\cong h_{ie} = \mathbf{1.171 \text{ k}\Omega} \end{aligned}$$

$$\text{b. } r_o = \frac{1}{h_{oe}} = \frac{1}{20 \mu\text{A}/\text{V}} = 50 \text{ k}\Omega$$

$$Z_o = \frac{1}{h_{oe}} \| R_C = 50 \text{ k}\Omega \| 2.7 \text{ k}\Omega = \mathbf{2.56 \text{ k}\Omega} \cong R_C$$

$$\text{c. } A_v = -\frac{h_{fe}(R_C \| 1/h_{oe})}{h_{ie}} = -\frac{(120)(2.7 \text{ k}\Omega \| 50 \text{ k}\Omega)}{1.171 \text{ k}\Omega} = \mathbf{-262.34}$$

$$\text{d. } A_i \cong h_{fe} = \mathbf{120}$$

**Check Other Configurations**

Thank you!

