

ECE 321C

Electronic Circuits

Lec. 8: BJT Low Frequency Response

Instructor

Dr. Maher Abdelrasoul

<http://www.bu.edu.eg/staff/mahersalem3>

Agenda

- Low Frequency Analysis- Bode Plot
- Low Frequency Response – BJT Amplifier with R_L
- Impact of R_S on the BJT Low Frequency Response

Low Frequency Analysis- Bode Plot

Defining the Low Cutoff Frequency

- In the low-frequency region of the single-stage BJT amplifier, it is the RC combinations formed by the network capacitors C_C , C_E , and C_S and the network resistive parameters that determine the cutoff frequencies
- Voltage-Divider Bias Config.

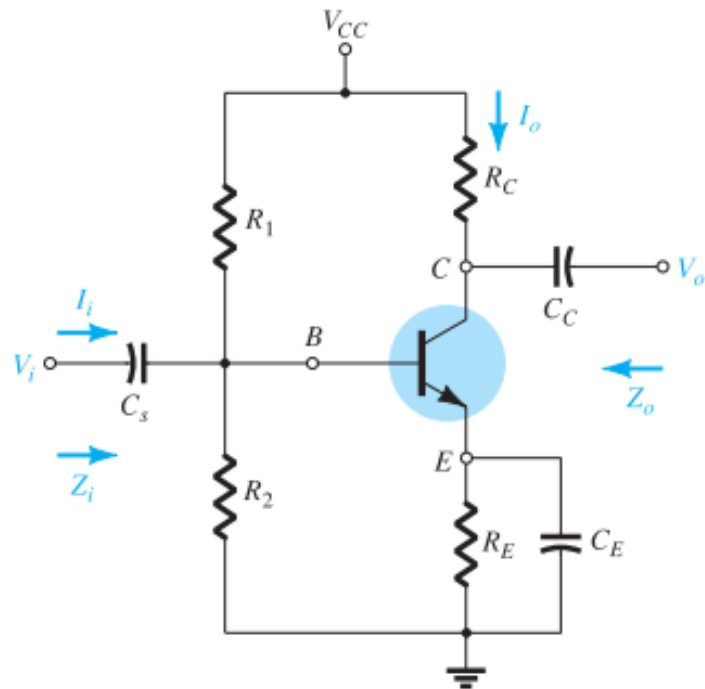


FIG. 9.15

Voltage-divider bias configuration.

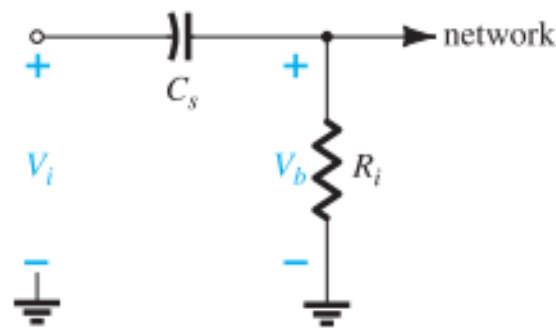


FIG. 9.16

Equivalent input circuit for the network of Fig. 9.15.

$$Z_i = R_i = R_1 \parallel R_2 \parallel \beta r_e$$

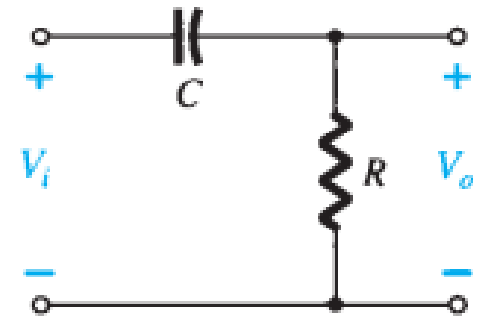


FIG. 9.14

RC combination that will define a low-cutoff frequency.


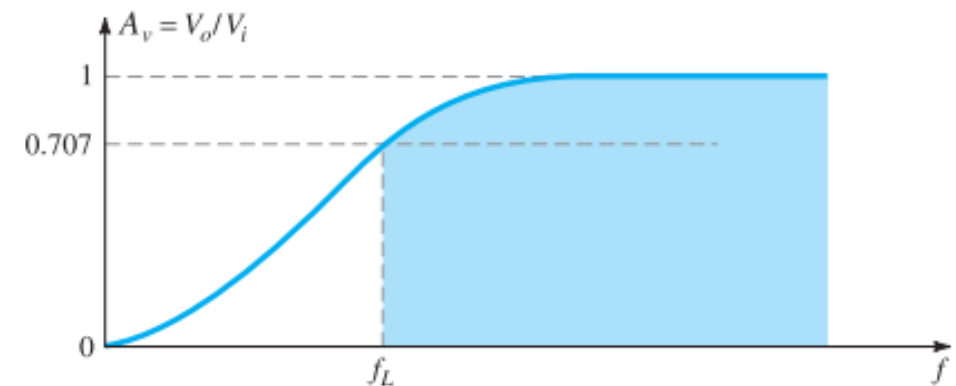


FIG. 9.19

Low-frequency response for the RC circuit of Fig. 9.14.

Defining The Low Cutoff Frequency ..

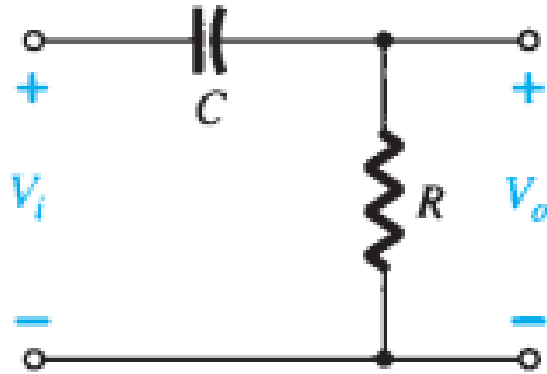

$$V_o = \frac{RV_i}{R + X_C}$$

The magnitude of V_o is

$$V_o = \frac{RV_i}{\sqrt{R^2 + X_C^2}}$$

For the special case where $X_C = R$,

$$V_o = \frac{RV_i}{\sqrt{R^2 + X_C^2}} = \frac{RV_i}{\sqrt{R^2 + R^2}} = \frac{RV_i}{\sqrt{2R^2}} = \frac{RV_i}{\sqrt{2}R} = \frac{1}{\sqrt{2}}V_i$$

$$|A_v| = \frac{V_o}{V_i} = \frac{1}{\sqrt{2}} = 0.707|_{X_C=R}$$

$$X_C = \frac{1}{2\pi f_L C} = R$$

$$f_L = \frac{1}{2\pi RC}$$

Defining The Low Cutoff Frequency ..

$$A_v = \frac{V_o}{V_i} = \frac{R}{R - jX_C} = \frac{1}{1 - j(X_C/R)} = \frac{1}{1 - j(1/\omega CR)} = \frac{1}{1 - j(1/2\pi fCR)}$$

$$A_v = \frac{1}{1 - j(f_L/f)}$$

In the magnitude and phase form,

$$A_v = \frac{V_o}{V_i} = \underbrace{\frac{1}{\sqrt{1 + (f_L/f)^2}}}_{\text{magnitude of } A_v} \underbrace{\angle \tan^{-1}(f_L/f)}_{\text{phase } \angle \text{ by which } V_o \text{ leads } V_i}$$

$$A_{v(\text{dB})} = 20 \log_{10} \frac{1}{\sqrt{1 + (f_L/f)^2}}$$

$$\theta = \tan^{-1} \frac{f_L}{f}$$

when $f = f_L$,

$$|A_v| = \frac{1}{\sqrt{1 + (1)^2}} = \frac{1}{\sqrt{2}} = 0.707 \Rightarrow -3 \text{ dB}$$

Bode Plot

$$A_{v(\text{dB})} = 20 \log_{10} \frac{1}{\sqrt{1 + (f_L/f)^2}}$$

$$\begin{aligned} A_{v(\text{dB})} &= -20 \log_{10} \left[1 + \left(\frac{f_L}{f} \right)^2 \right]^{1/2} \\ &= -\left(\frac{1}{2}\right)(20) \log_{10} \left[1 + \left(\frac{f_L}{f} \right)^2 \right] \\ &= -10 \log_{10} \left[1 + \left(\frac{f_L}{f} \right)^2 \right] \end{aligned}$$

For frequencies where $f \ll f_L$ or $(f_L/f)^2 \gg 1$,


$$A_{v(\text{dB})} = -10 \log_{10} \left(\frac{f_L}{f} \right)^2$$

$$A_{v(\text{dB})} = -20 \log_{10} \frac{f_L}{f} \quad f \ll f_L$$

Bode Plot

$$A_{v(\text{dB})} = -20 \log_{10} \frac{f_L}{f} \quad f \ll f_L$$

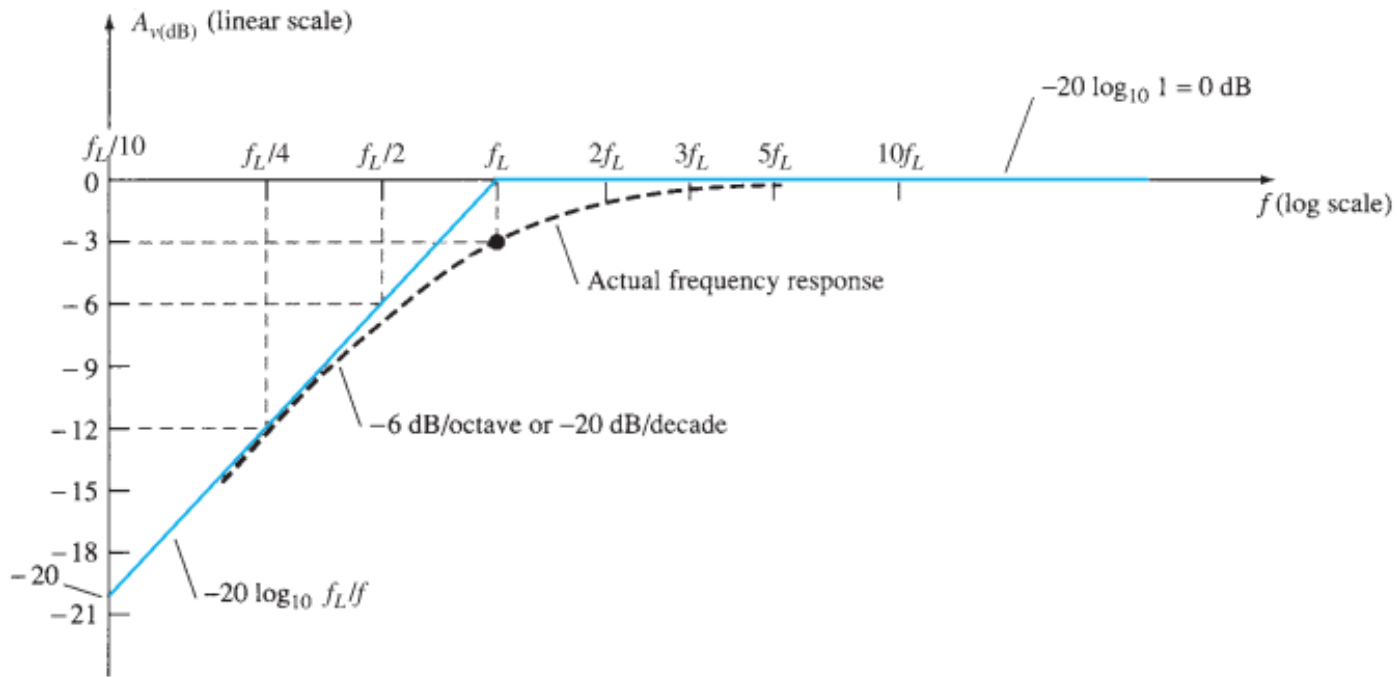- The piecewise linear plot of the asymptotes and associated breakpoints is called a **Bode plot** of the magnitude versus frequency.



- A change in frequency by a factor of two, equivalent to **one octave**, results in a 6-dB change in the ratio, as shown by the change in gain from $f_L/2$ to f_L .
- For a 10:1 change in frequency, equivalent to **one decade**, there is a 20-dB change in the ratio, as demonstrated between the frequencies of $f_L/10$ and f_L .

Bode Plot..

- Phase Angle:

$$\theta = \tan^{-1} \frac{f_L}{f}$$

For frequencies $f \ll f_L$,

$$\theta = \tan^{-1} \frac{f_L}{f} \rightarrow 90^\circ$$

For instance, if $f_L = 100f$,

$$\theta = \tan^{-1} \frac{f_L}{f} = \tan^{-1}(100) = 89.4^\circ$$

For $f = f_L$,

$$\theta = \tan^{-1} \frac{f_L}{f} = \tan^{-1} 1 = 45^\circ$$

For $f \gg f_L$,

$$\theta = \tan^{-1} \frac{f_L}{f} \rightarrow 0^\circ$$

For instance, if $f = 100f_L$,

$$\theta = \tan^{-1} \frac{f_L}{f} = \tan^{-1} 0.01 = 0.573^\circ$$

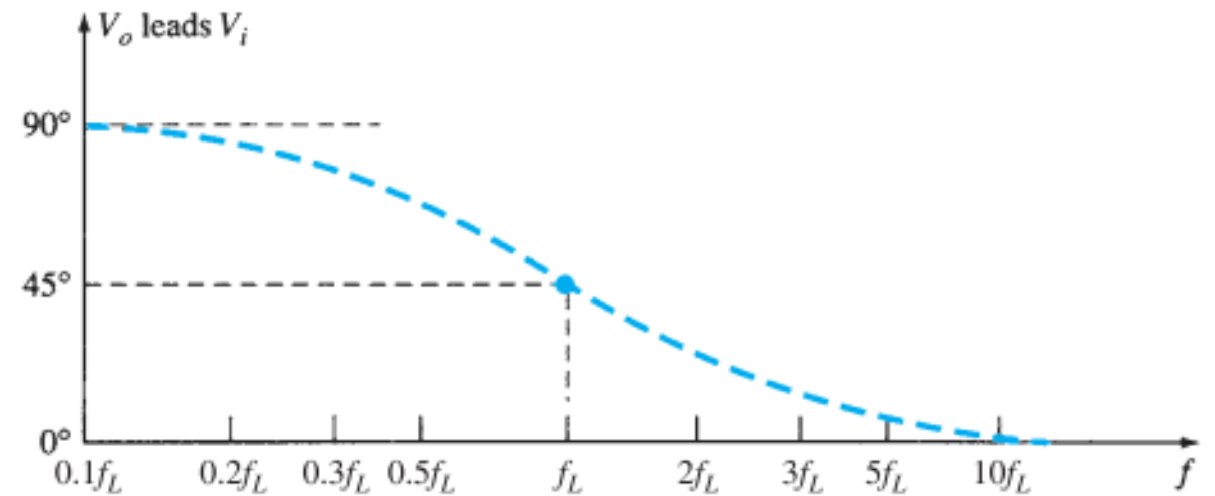


FIG. 9.22

Phase response for the RC circuit of Fig. 9.14.

Example

EXAMPLE 9.10 For the network of Fig. 9.23:

- Determine the break frequency.
- Sketch the asymptotes and locate the -3 -dB point.
- Sketch the frequency response curve.
- Find the gain at $A_{v(\text{dB})} = -6$ dB.

Solution:

$$\text{a. } f_L = \frac{1}{2\pi RC} = \frac{1}{(6.28)(5 \times 10^3 \Omega)(0.1 \times 10^{-6} \text{ F})} \\ \cong \mathbf{318.5 \text{ Hz}}$$

b. and c. See Fig. 9.24.

$$\text{d. Eq. (9.27): } A_v = \frac{V_o}{V_i} = 10^{A_{v(\text{dB})}/20} \\ = 10^{(-6/20)} = 10^{-0.3} = 0.501 \\ \text{and } V_o = 0.501 V_i \text{ or approximately } 50\% \text{ of } V_i.$$

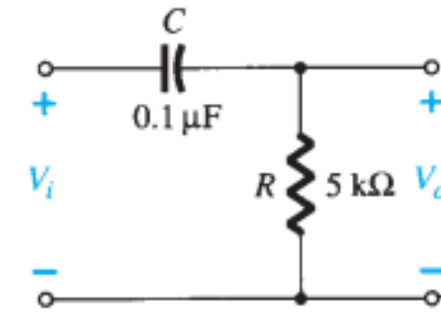


FIG. 9.23

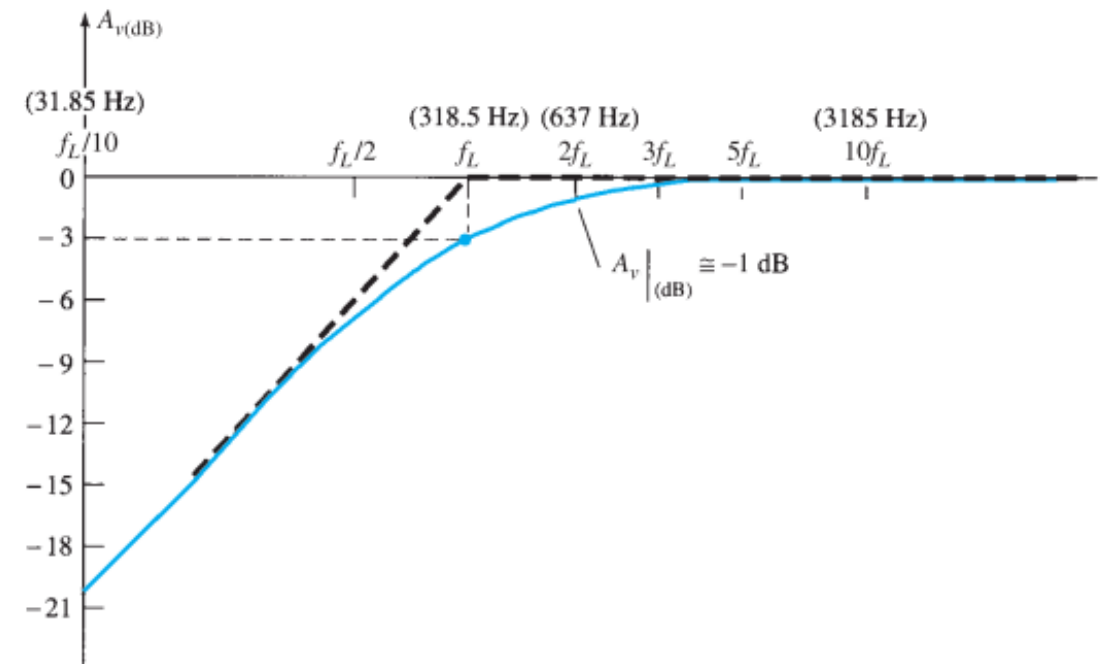


FIG. 9.24

Frequency response for the RC circuit of Fig. 9.23.

Low Frequency Response – BJT Amplifier with R_L

Loaded BJT Amplifier

In the voltage-divider ct.

→ the capacitors C_s , C_C , and C_E will determine the low-frequency response.

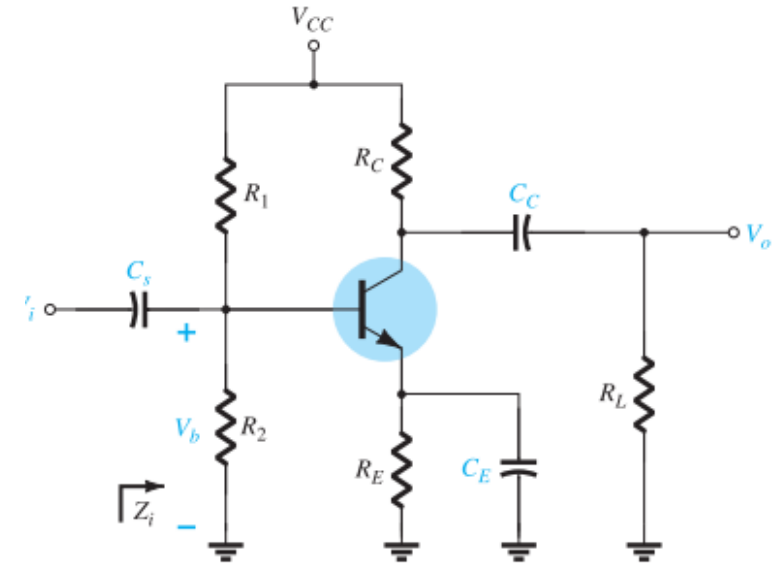


FIG. 9.25

Loaded BJT amplifier with capacitors that affect the low-frequency response.

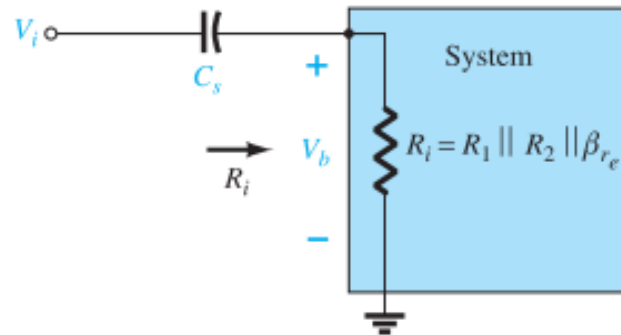


FIG. 9.26

Determining the effect of C_s on the low-frequency response.

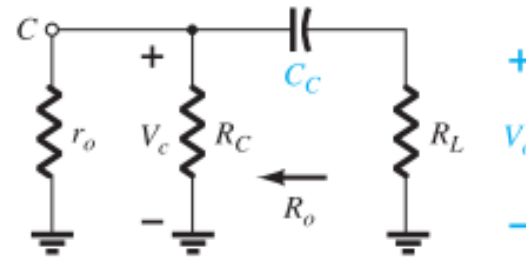


FIG. 9.28

Localized ac equivalent for C_C with $V_i = 0$ V.

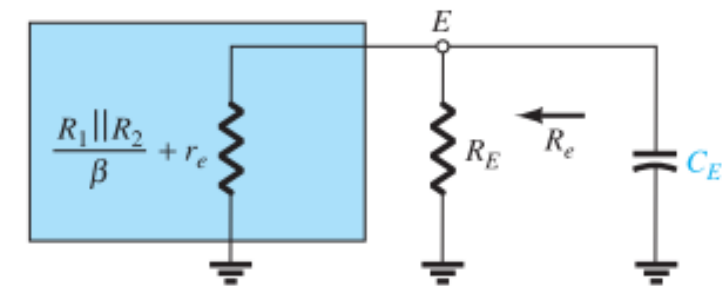


FIG. 9.30

Localized ac equivalent of C_E .

$$f_L = \max(f_{LS}, f_{LC}, f_{LE})$$

Loaded BJT Amplifier

→ C_s :

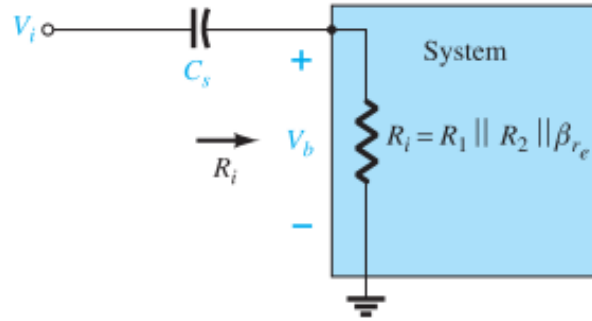


FIG. 9.26

Determining the effect of C_s on the low-frequency response.

$$R_i = R_1 \parallel R_2 \parallel \beta r_e$$

$$f_{L_s} = \frac{1}{2\pi R_i C_s}$$

→ C_c :

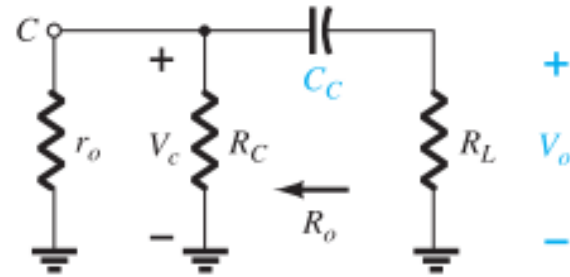


FIG. 9.28

Localized ac equivalent for C_c with $V_i = 0$ V.

$$R_o = R_c \parallel r_o$$

$$f_{L_c} = \frac{1}{2\pi (R_o + R_L) C_c}$$

→ C_E :

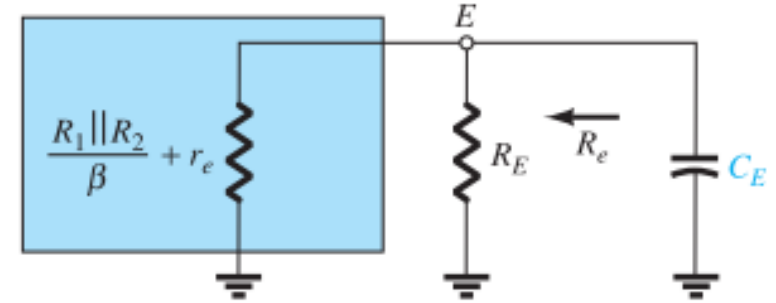


FIG. 9.30

Localized ac equivalent of C_E .

$$R_e = R_E \parallel \left(\frac{R_1 \parallel R_2}{\beta} + r_e \right)$$

$$f_{L_E} = \frac{1}{2\pi R_e C_E}$$

$$f_L = \max(f_{L_s}, f_{L_c}, f_{L_E})$$

Impact of R_S on the BJT Low Frequency Response

Impact of R_s

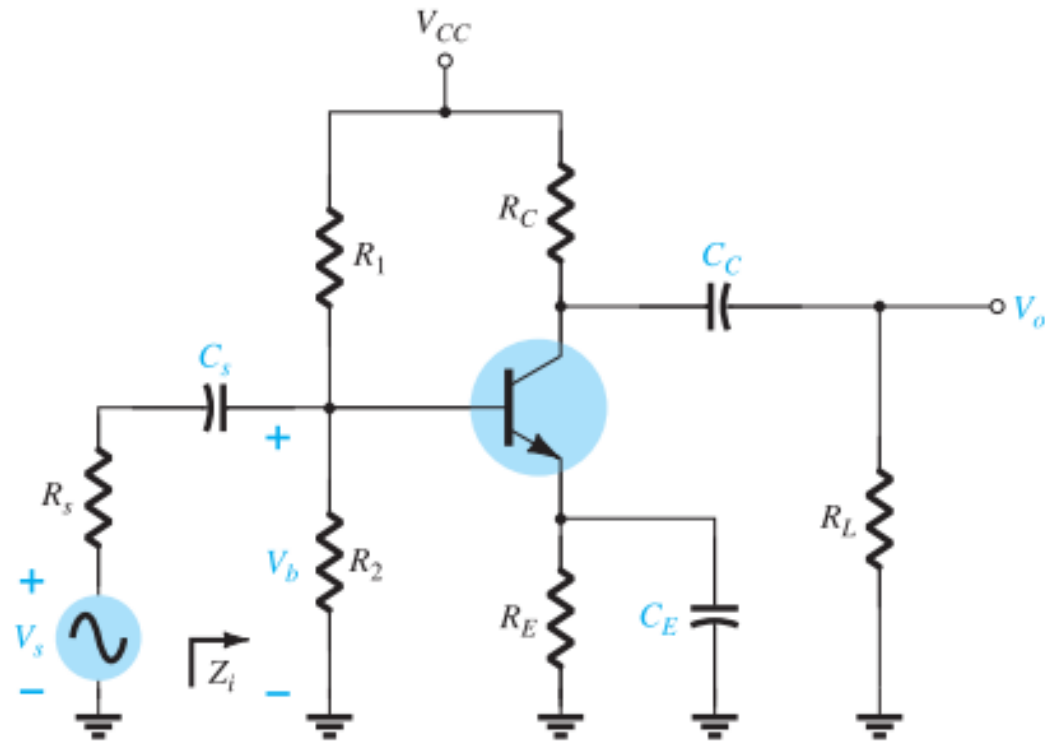


FIG. 9.32

Determining the effect of R_s on the low-frequency response of a BJT amplifier.

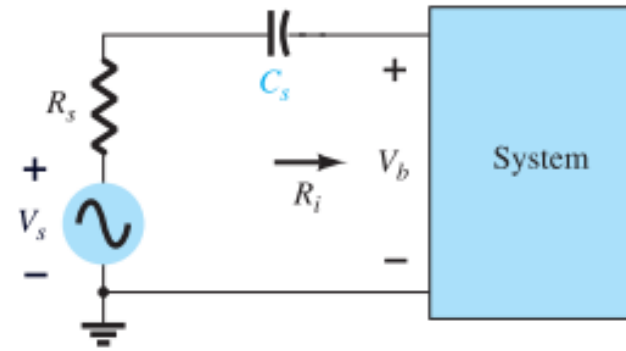


FIG. 9.33

Determining the effect of C_s on the low-frequency response.

$$f_{L_s} = \frac{1}{2\pi(R_i + R_s)C_s}$$

$$f_{L_C} = \frac{1}{2\pi(R_o + R_L)C_C}$$

$$f_{L_E} = \frac{1}{2\pi R_e C_E}$$

$$R_e = R_E \parallel \left(\frac{R'_s}{\beta} + r_e \right) \text{ and } R'_s = R_s \parallel R_1 \parallel R_2$$

Thank You!

