

# ECE 321C

# Electronic Circuits


Lec. 9: BJT High Frequency Response

Instructor

**Dr. Maher Abdelrasoul**

**<http://www.bu.edu.eg/staff/mahersalem3>**


# Agenda

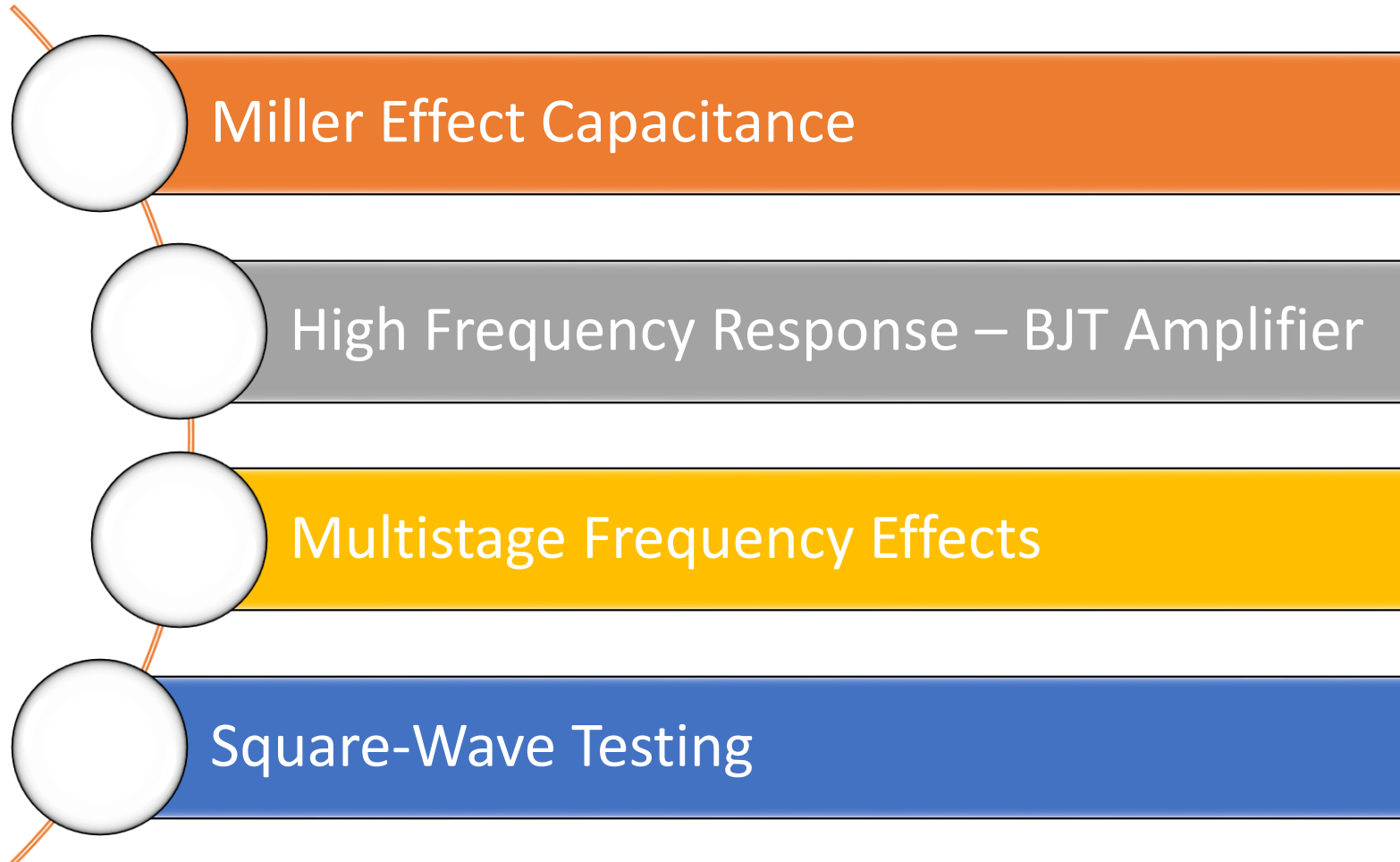- 
- Miller Effect Capacitance
  - High Frequency Response – BJT Amplifier
  - Multistage Frequency Effects
  - Square-Wave Testing

# Miller Effect Capacitance
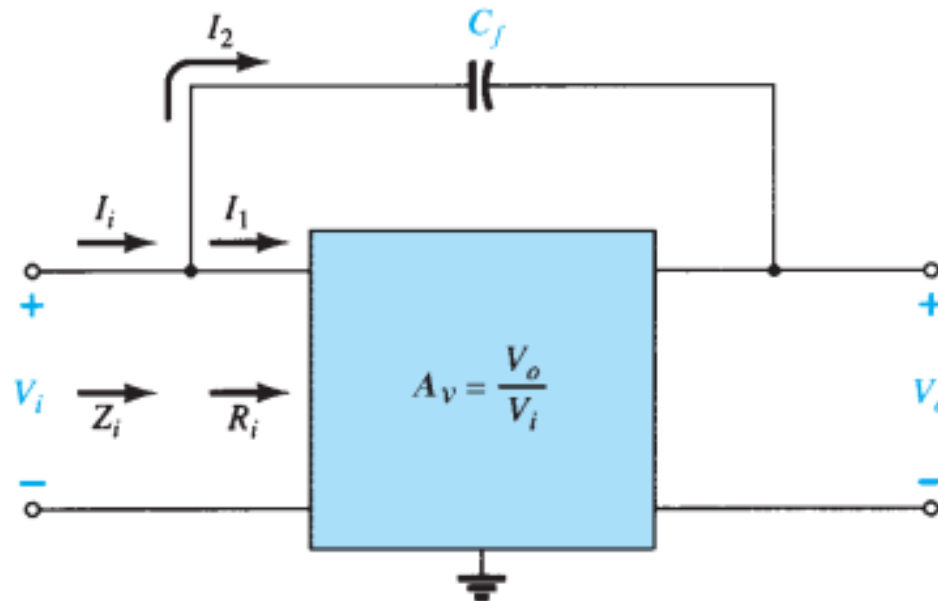
# Miller input capacitance

- In the high-frequency region, the capacitive elements of importance are the interelectrode (between-terminals) capacitances internal to the active device and the wiring capacitance between leads of the network.
- For any inverting amplifier, the input capacitance will be increased by a Miller effect capacitance sensitive to the gain of the amplifier and the interelectrode (parasitic) capacitance between the input and output terminals of the active device.



# Miller input capacitance

Applying Kirchhoff's current law gives

$$I_i = I_1 + I_2$$

Using Ohm's law yields

$$I_i = \frac{V_i}{Z_i}, \quad I_1 = \frac{V_i}{R_i}$$

and

$$I_2 = \frac{V_i - V_o}{X_{C_f}} = \frac{V_i - A_v V_i}{X_{C_f}} = \frac{(1 - A_v)V_i}{X_{C_f}}$$

Substituting, we obtain

$$\frac{V_i}{Z_i} = \frac{V_i}{R_i} + \frac{(1 - A_v)V_i}{X_{C_f}}$$

and



$$\frac{1}{Z_i} = \frac{1}{R_i} + \frac{1}{X_{C_f}/(1 - A_v)}$$

but

$$\frac{X_{C_f}}{1 - A_v} = \frac{1}{\omega(1 - A_v)C_f} = X_{C_M}$$

and
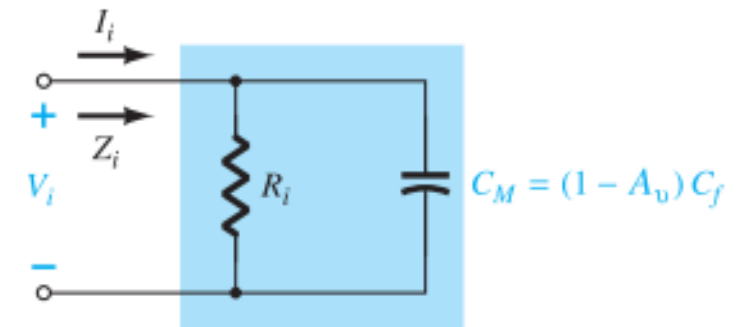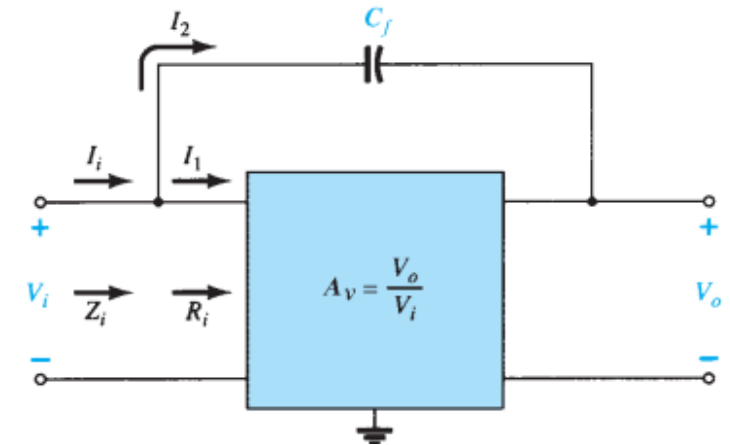
$$\frac{1}{Z_i} = \frac{1}{R_i} + \frac{1}{X_{C_M}}$$



$$C_{M_i} = (1 - A_v)C_f$$

- A positive value for  $A_v$  would result in a negative capacitance (for  $A_v > 1$ ).
- For noninverting amplifiers such as the common-base and emitter-follower configurations, the Miller effect capacitance is not a contributing concern for high-frequency applications.

# Miller output capacitance

- The Miller effect will also increase the level of output capacitance, which must also be considered when the high-frequency cutoff is determined.

$$I_o = I_1 + I_2$$

$$I_1 = \frac{V_o}{R_o} \quad \text{and} \quad I_2 = \frac{V_o - V_i}{X_{C_f}}$$

The resistance  $R_o$  is usually sufficiently large to permit ignoring the first term of the equation compared to the second term and assuming that

$$I_o \cong \frac{V_o - V_i}{X_{C_f}}$$

Substituting  $V_i = V_o/A_v$  from  $A_v = V_o/V_i$  results in


$$I_o = \frac{V_o - V_o/A_v}{X_{C_f}} = \frac{V_o(1 - 1/A_v)}{X_{C_f}}$$

and

$$\frac{I_o}{V_o} = \frac{1 - 1/A_v}{X_{C_f}}$$

or
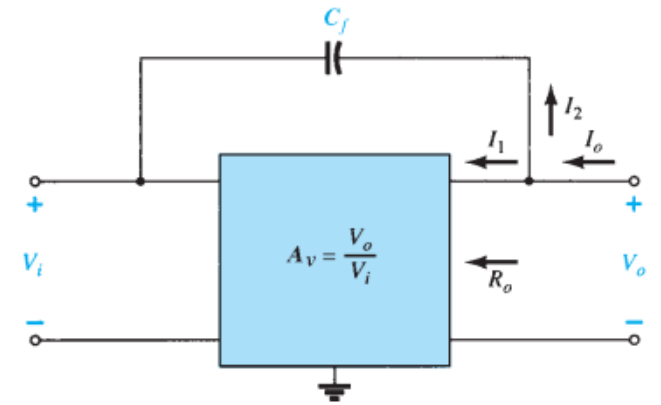
$$\frac{V_o}{I_o} = \frac{X_{C_f}}{1 - 1/A_v} = \frac{1}{\omega C_f(1 - 1/A_v)} = \frac{1}{\omega C_{M_o}}$$




$$C_{M_o} = \left(1 - \frac{1}{A_v}\right) C_f$$

$$C_{M_o} \cong C_f \quad |A_v| \gg 1$$

# High Frequency Response – BJT Amplifier


# High Frequency Response

- At the high-frequency end, there are two factors that define the 3-dB cutoff point:
  1. the network capacitance (parasitic and introduced)
  2. the frequency dependence of  $h_{fe}$  ( $\beta$ ).
- For RC circuit:

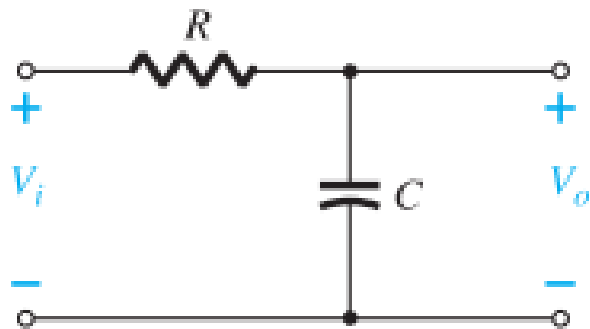

**FIG. 9.45**

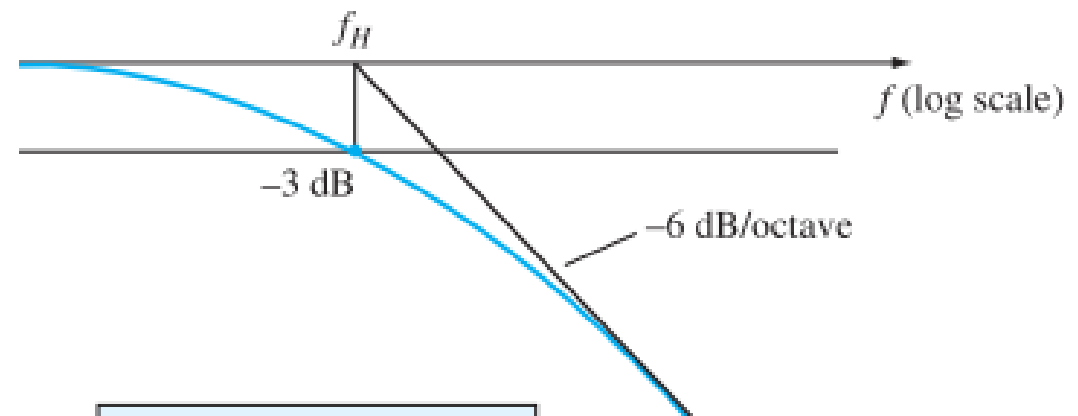*RC combination that will define a high-cutoff frequency.*




$$A_v = \frac{1}{1 + j(f/f_H)}$$



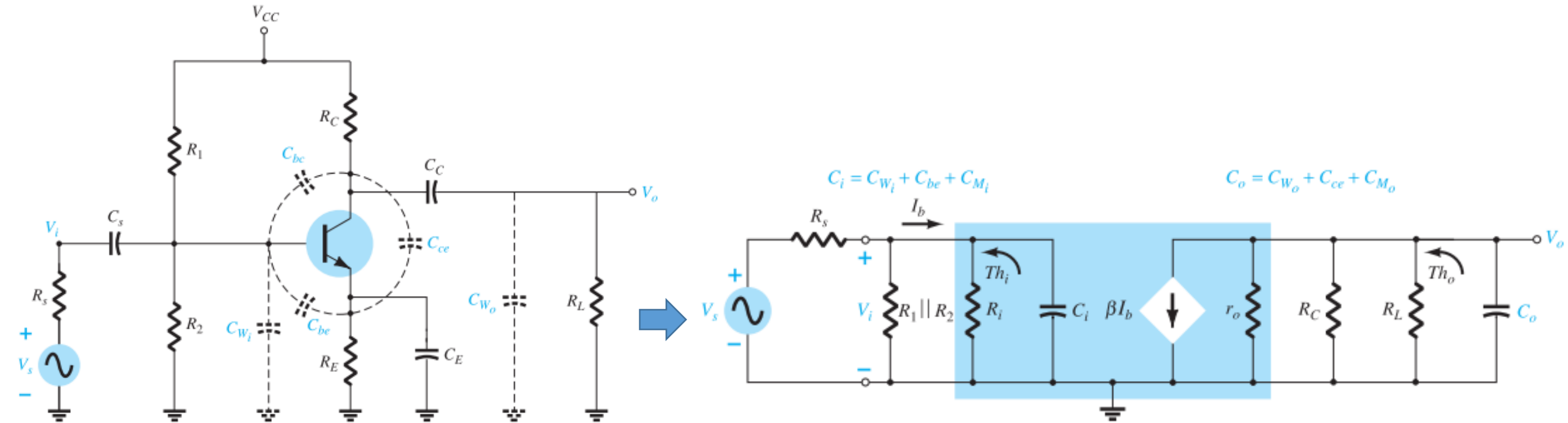
# 1. Network Parameters (1 of 2)

- At high frequencies, the various parasitic capacitances ( $C_{be}$ ,  $C_{bc}$ ,  $C_{ce}$ ) of the transistor are included with the wiring capacitances ( $C_{Wi}$ ,  $C_{Wo}$ ).



# 1. Network Parameters (2 of 2)

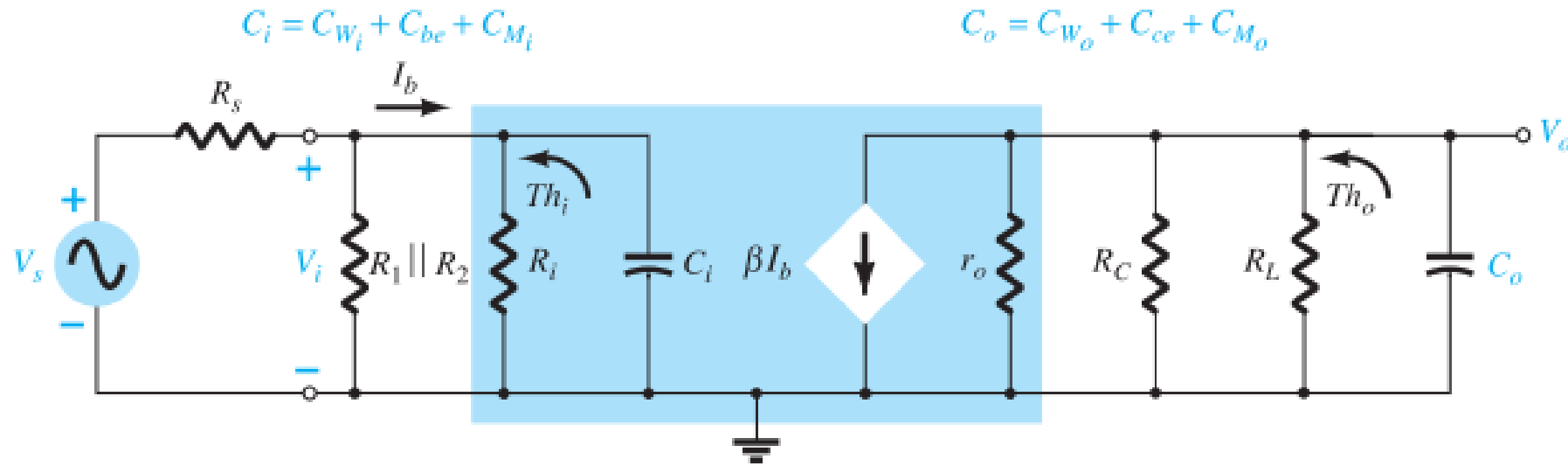

$$f_{H_i} = \frac{1}{2\pi R_{Th_i} C_i}$$

$$R_{Th_i} = R_s \parallel R_1 \parallel R_2 \parallel \beta r_e$$

$$C_i = C_{W_i} + C_{be} + C_{M_i} = C_{W_i} + C_{be} + (1 - A_v) C_{bc}$$

$$f_{H_o} = \frac{1}{2\pi R_{Th_o} C_o}$$

$$R_{Th_o} = R_C \parallel R_L \parallel r_o$$

$$C_o = C_{W_o} + C_{ce} + C_{M_o}$$

$$C_o = C_{W_o} + C_{ce} + (1 - 1/A_v) C_{bc}$$

$1 \gg 1/A_v$

$$C_o \cong C_{W_o} + C_{ce} + C_{bc}$$

## 2. $h_{fe}$ (or $\beta$ ) Variation

- The variation of  $h_{fe}$  (or  $\beta$ ) with frequency approaches the following relationship:

$$h_{fe} = \frac{h_{fe\text{mid}}}{1 + j(f/f_\beta)}$$

- The quantity,  $f_\beta$ , is determined by a set of parameters employed in the hybrid  $\pi$  model

$$f_\beta (\text{often appearing as } f_{h_{fe}}) = \frac{1}{2\pi r_\pi (C_\pi + C_u)}$$

$$f_\beta = \frac{1}{h_{fe\text{mid}}} \frac{1}{2\pi r_e (C_\pi + C_u)}$$

- $f_\beta$  is a function of the bias configuration.
- the small change in  $h_{fb}$  for the chosen frequency range, revealing that the common-base configuration displays improved high-frequency characteristics over the common-emitter configuration.

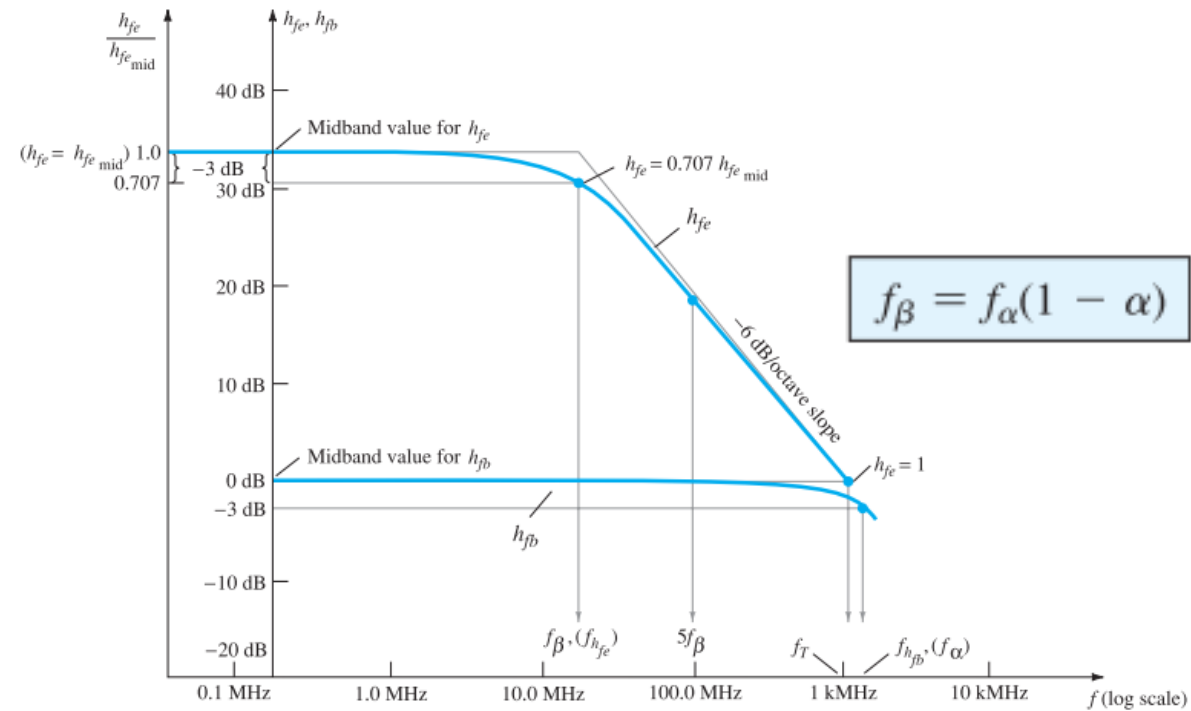
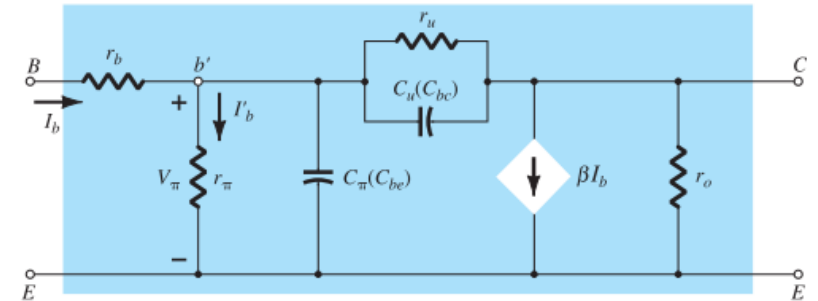


FIG. 9.51

$h_{fe}$  and  $h_{fb}$  versus frequency in the high-frequency region.

# Gain-Bandwidth Product

- There is a Figure of Merit applied to amplifiers called the Gain-Bandwidth Product (GBP) that is commonly used to initiate the design process of an amplifier.
- It provides important information about the relationship between the gain of the amplifier and the expected operating frequency range.

$$\text{GBP} = A_{v_{\text{mid}}} \text{BW}$$

$$\text{BW} = f_H - f_L \cong f_H$$

$$f_T = A_{v_{\text{mid}}} f_H \quad (\text{Hz})$$

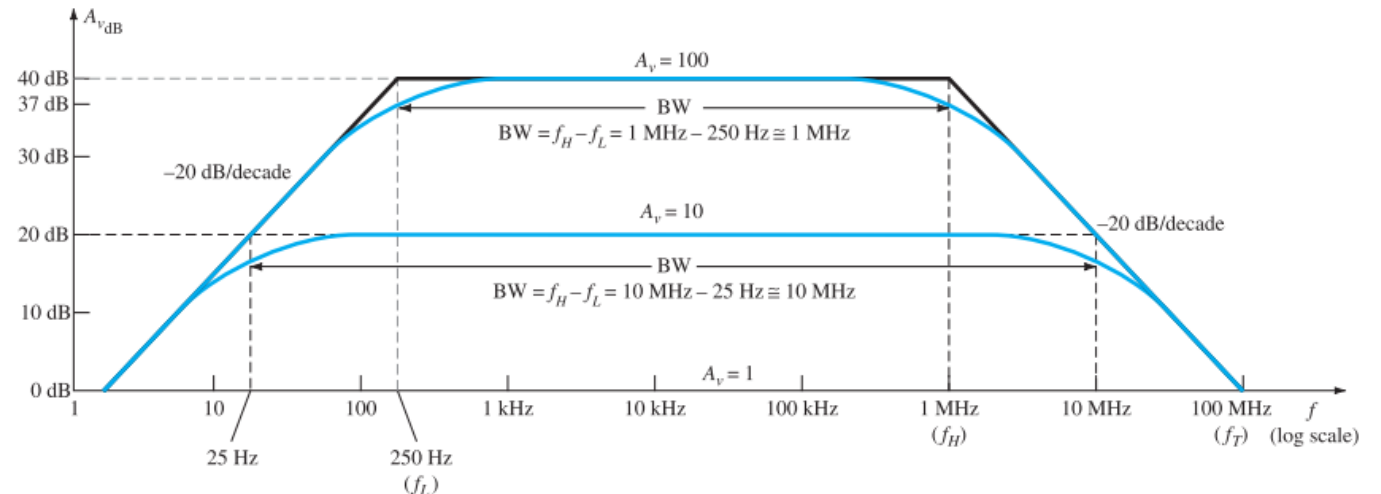


FIG. 9.53

Finding the bandwidth at two different gain levels.

- at any level of gain the product of the two remains a constant.
- the frequency  $f_T$  is called the unity-gain frequency and is always equal to the product of the midband gain of an amplifier and the bandwidth at any level of gain.

$$f_T = h_{fe_{\text{mid}}} \frac{1}{2\pi h_{fe_{\text{mid}}} r_e (C_\pi + C_u)}$$

$$f_T = h_{fe_{\text{mid}}} f_\beta \quad (\text{Hz})$$

$$f_T \cong \frac{1}{2\pi r_e (C_\pi + C_u)}$$

# Example

**EXAMPLE 9.14** Use the network of Fig. 9.47 with the same parameters as in Example 9.12, that is,

$$R_s = 1 \text{ k}\Omega, R_1 = 40 \text{ k}\Omega, R_2 = 10 \text{ k}\Omega, R_E = 2 \text{ k}\Omega, R_C = 4 \text{ k}\Omega, R_L = 2.2 \text{ k}\Omega$$


$$C_s = 10 \text{ }\mu\text{F}, C_C = 1 \text{ }\mu\text{F}, C_E = 20 \text{ }\mu\text{F}$$

$$h_{fe} = 100, r_o = \infty \text{ }\Omega, V_{CC} = 20 \text{ V}$$

with the addition of

$$C_{\pi}(C_{be}) = 36 \text{ pF}, C_u(C_{bc}) = 4 \text{ pF}, C_{ce} = 1 \text{ pF}, C_{W_i} = 6 \text{ pF}, C_{W_o} = 8 \text{ pF}$$

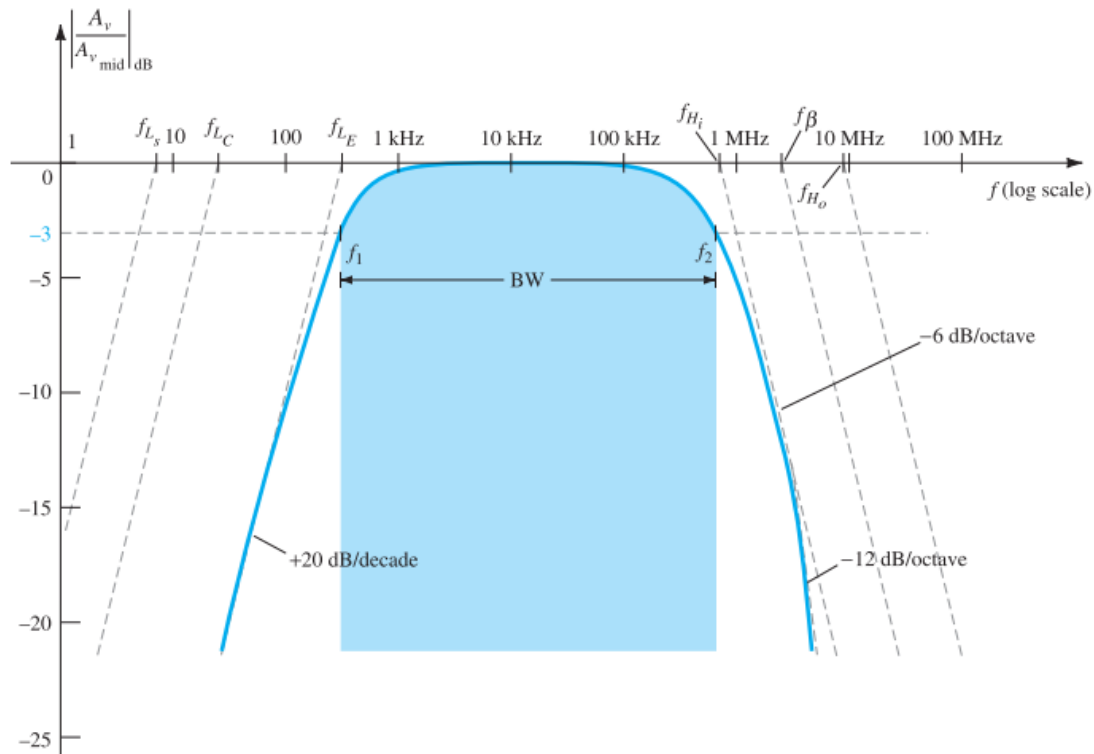- Determine  $f_{H_i}$  and  $f_{H_o}$ .
- Find  $f_{\beta}$  and  $f_T$ .
- Sketch the frequency response for the low- and high-frequency regions using the results of Example 9.12 and the results of parts (a) and (b).



## Solution:

a. From Example 9.12:

$$\beta r_e = 1.576 \text{ k}\Omega, \quad A_{v_{mid}}(\text{amplifier—not including effects of } R_s) = -90$$

$$\text{and} \quad R_{Th_i} = R_s \parallel R_1 \parallel R_2 \parallel \beta r_e = 1 \text{ k}\Omega \parallel 40 \text{ k}\Omega \parallel 10 \text{ k}\Omega \parallel 1.576 \text{ k}\Omega$$

$$\cong 0.57 \text{ k}\Omega$$

$$\text{with} \quad C_i = C_{W_i} + C_{be} + (1 - A_v)C_{bc}$$

$$= 6 \text{ pF} + 36 \text{ pF} + [1 - (-90)]4 \text{ pF}$$

$$= 406 \text{ pF}$$

$$f_{H_i} = \frac{1}{2\pi R_{Th_i} C_i} = \frac{1}{2\pi(0.57 \text{ k}\Omega)(406 \text{ pF})}$$

$$= \mathbf{687.73 \text{ kHz}}$$

$$R_{Th_o} = R_C \parallel R_L = 4 \text{ k}\Omega \parallel 2.2 \text{ k}\Omega = 1.419 \text{ k}\Omega$$

$$C_o = C_{W_o} + C_{ce} + C_{M_o} = 8 \text{ pF} + 1 \text{ pF} + \left(1 - \frac{1}{-90}\right)4 \text{ pF}$$

$$= 13.04 \text{ pF}$$

$$f_{H_o} = \frac{1}{2\pi R_{Th_o} C_o} = \frac{1}{2\pi(1.419 \text{ k}\Omega)(13.04 \text{ pF})}$$

$$= \mathbf{8.6 \text{ MHz}}$$

b. Applying Eq. (9.63) gives

$$f_{\beta} = \frac{1}{2\pi h_{fe_{mid}} r_e (C_{be} + C_{bc})}$$

$$= \frac{1}{2\pi(100)(15.76 \text{ }\Omega)(36 \text{ pF} + 4 \text{ pF})} = \frac{1}{2\pi(100)(15.76 \text{ }\Omega)(40 \text{ pF})}$$

$$= \mathbf{2.52 \text{ MHz}}$$

$$f_T = h_{fe_{mid}} f_{\beta} = (100)(2.52 \text{ MHz})$$

$$= \mathbf{252 \text{ MHz}}$$

c. See Fig. 9.54. The corner frequency  $f_{H_i}$  will determine the high cutoff frequency and the bandwidth of the amplifier. The upper cutoff frequency is very close to 600 kHz.

# Multistage Frequency Effects

# Multistage Frequency Effects

$$A_{v_{low, (overall)}} = A_{v_{1low}} A_{v_{2low}} A_{v_{3low}} \cdots A_{v_{nlow}}$$

but because all stages are identical,  $A_{v_{1low}} = A_{v_{2low}} = \text{etc.}$ , and

$$A_{v_{low, (overall)}} = (A_{v_{1low}})^n$$

or

$$\frac{A_{v_{low}}}{A_{v_{mid}}} (\text{overall}) = \left( \frac{A_{v_{low}}}{A_{v_{mid}}} \right)^n = \frac{1}{(1 - jf_L/f)^n}$$

Setting the magnitude of this result equal to  $1/\sqrt{2}$  (-3 dB level) results in

$$\frac{1}{\sqrt{[1 + (f_L/f_L')^2]^n}} = \frac{1}{\sqrt{2}}$$

or

$$\left\{ \left[ 1 + \left( \frac{f_L}{f_L'} \right)^2 \right]^{1/2} \right\}^n = \left\{ \left[ 1 + \left( \frac{f_L}{f_L'} \right)^2 \right]^n \right\}^{1/2} = (2)^{1/2}$$

so that

$$\left[ 1 + \left( \frac{f_L}{f_L'} \right)^2 \right]^n = 2$$

and

$$1 + \left( \frac{f_L}{f_L'} \right)^2 = 2^{1/n}$$

with the result that

$$f_L' = \frac{f_L}{\sqrt{2^{1/n} - 1}}$$

In a similar manner, it can be shown that for the high-frequency region,

$$f_H' = (\sqrt{2^{1/n} - 1}) f_H$$

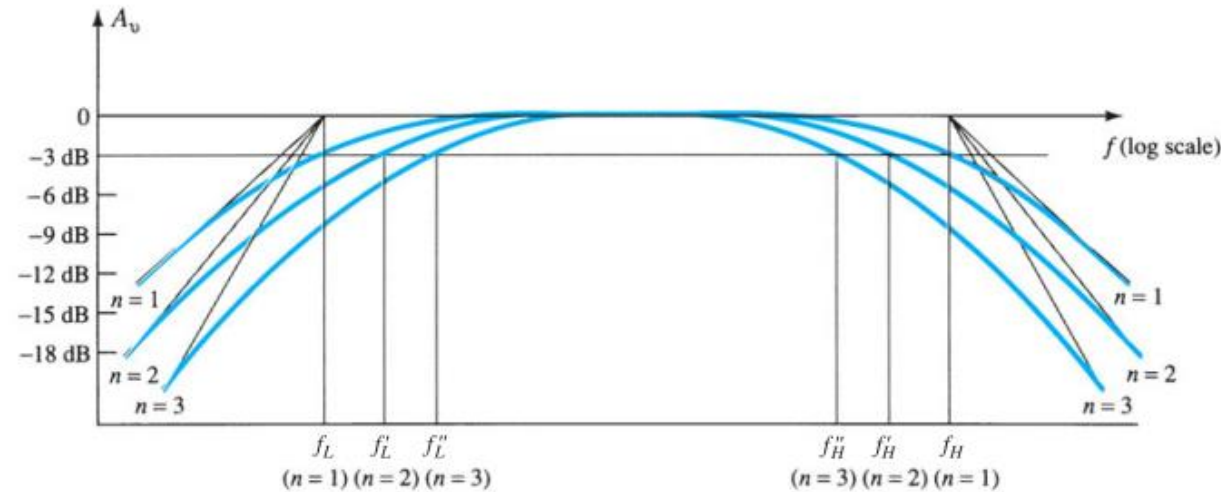


FIG. 9.58

Effect of an increased number of stages on the cutoff frequencies and the bandwidth.


$n$	$\sqrt{2^{1/n} - 1}$
2	0.64
3	0.51
4	0.43
5	0.39

# Square-Wave Testing



# Square-Wave Testing


- A sense for the frequency response of an amplifier can be determined experimentally by applying a square-wave signal to the amplifier and noting the output response.

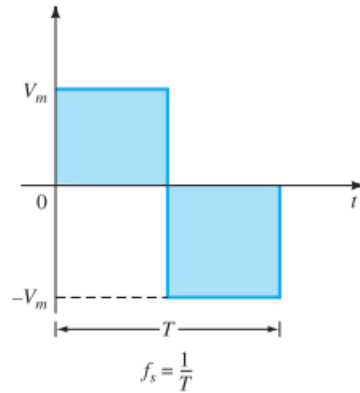


**FIG. 9.59**  
Square wave

The Fourier series expansion for the square wave of Fig. 9.59 is

$$v = \frac{4}{\pi} V_m \left( \underbrace{\sin 2\pi f_s t}_{\text{fundamental}} + \frac{1}{3} \underbrace{\sin 2\pi(3f_s)t}_{\text{third harmonic}} + \frac{1}{5} \underbrace{\sin 2\pi(5f_s)t}_{\text{fifth harmonic}} + \frac{1}{7} \underbrace{\sin 2\pi(7f_s)t}_{\text{seventh harmonic}} \right. \\ \left. + \frac{1}{9} \underbrace{\sin 2\pi(9f_s)t}_{\text{ninth harmonic}} + \cdots + \frac{1}{n} \underbrace{\sin 2\pi(nf_s)t}_{\text{nth harmonic}} \right)$$

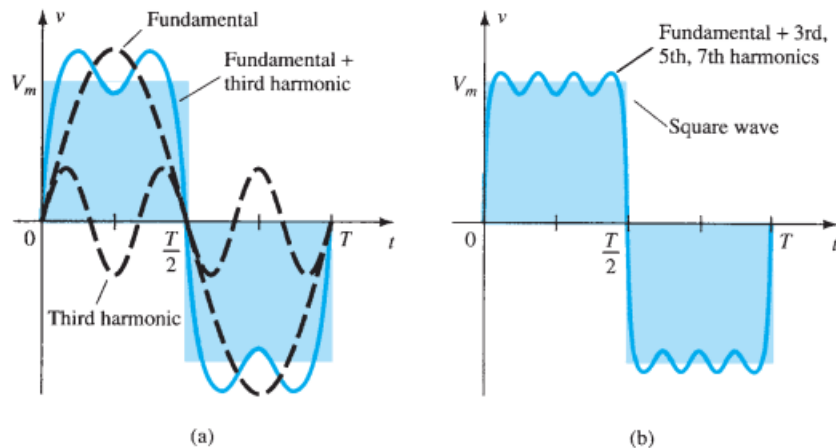

**FIG. 9.60**  
Harmonic content of a square wave.

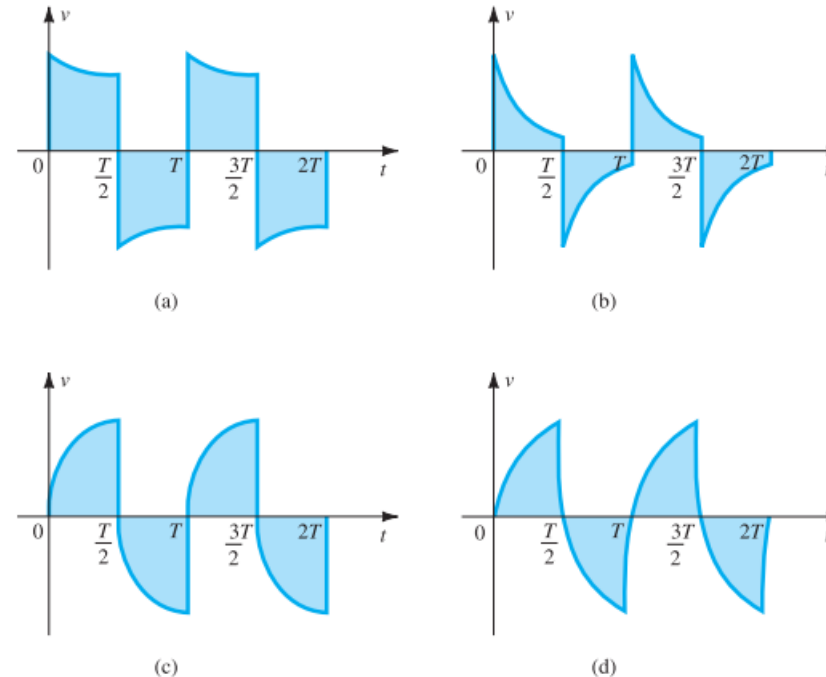

**FIG. 9.61**

(a) Poor low-frequency response; (b) very poor low-frequency response; (c) poor high-frequency response; (d) very poor high-frequency response.

Thank You!

