

ECE 121

Electronics (1)


Lec. 1: Introduction to BJT

Instructor

Dr. Maher Abdelrasoul

<http://www.bu.edu.eg/staff/mahersalem3>


Outline

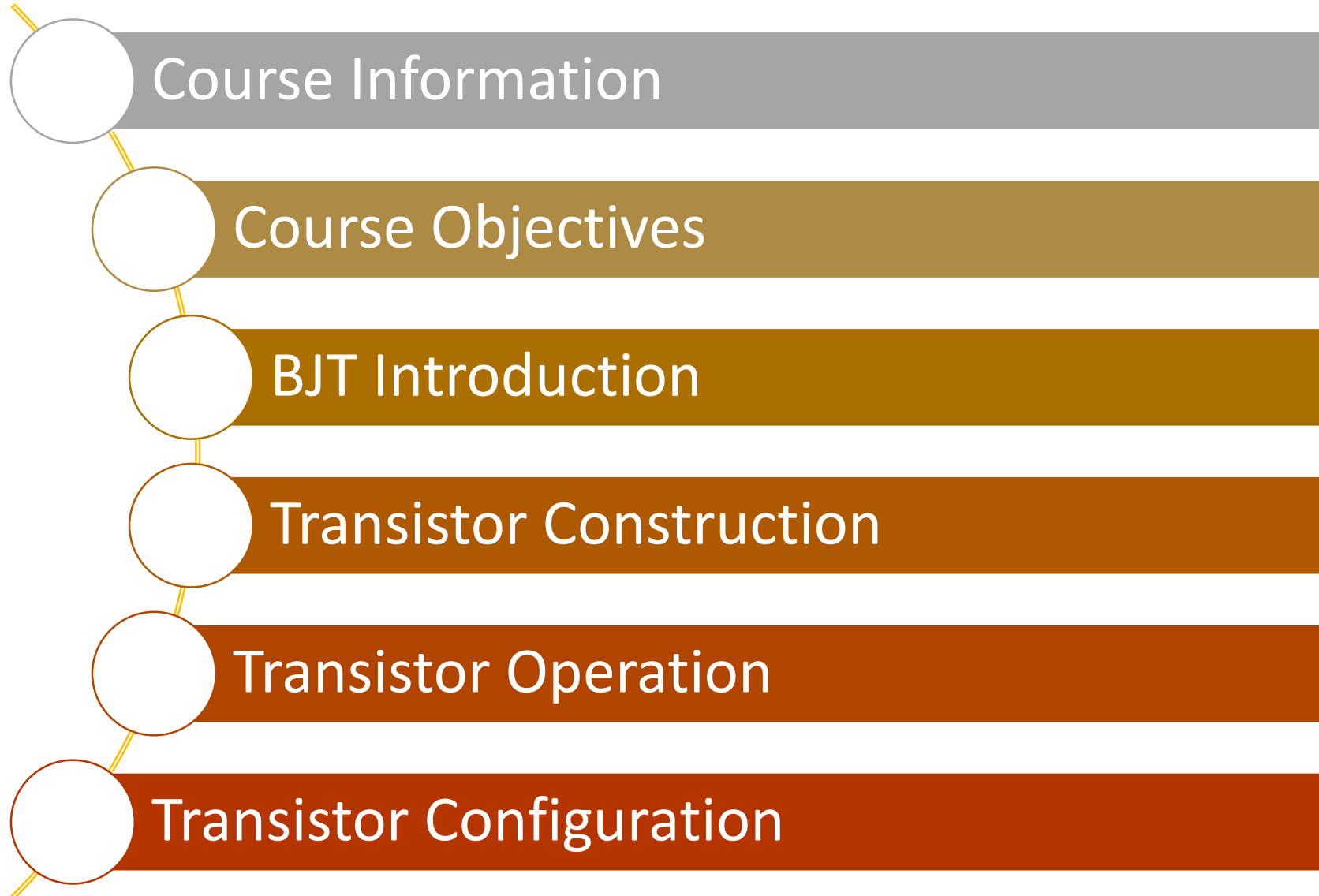

Course Information

Instructor:	Dr. Maher Abdelrasoul
Lectures:	Tuesday:10:40-12:10, Thursday: 9:00 -10:30
Office Hours:	Tuesday, Thursday
Teaching Assistant:	Eng. Ibrahim
Text Book:	R. Boylestad, Electronic Devices and Circuit Theory, 11th edition, Prentice Hall
Credit:	90 Marks
Grading:	<ul style="list-style-type: none">• Final Exam (50)• Mid Term Exam (25)• Oral exam, homework, and tutorials activities (15)

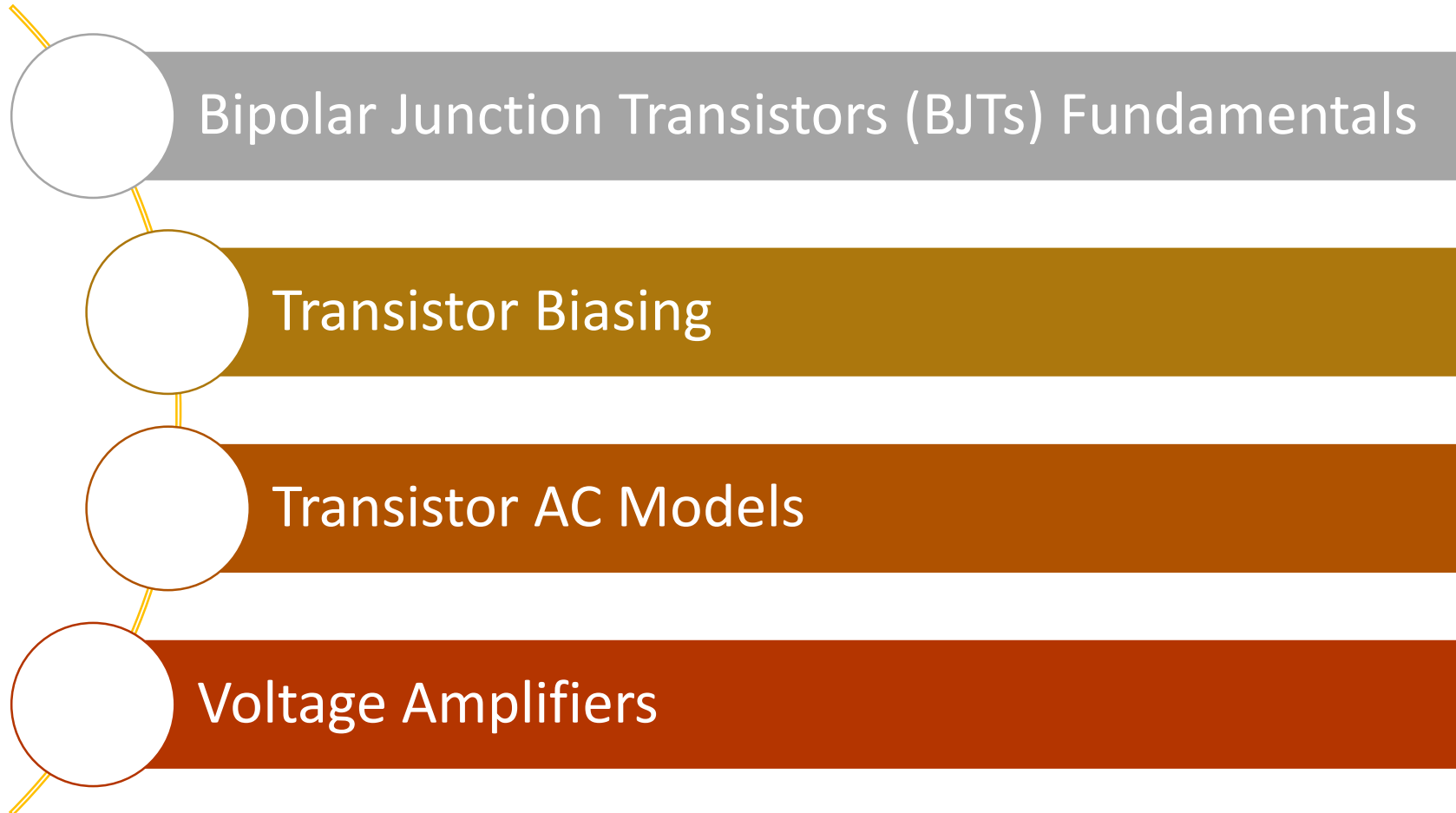Course Objective is to understand the following:




What is a Transistor?




Before BJT → Vacuum tubes

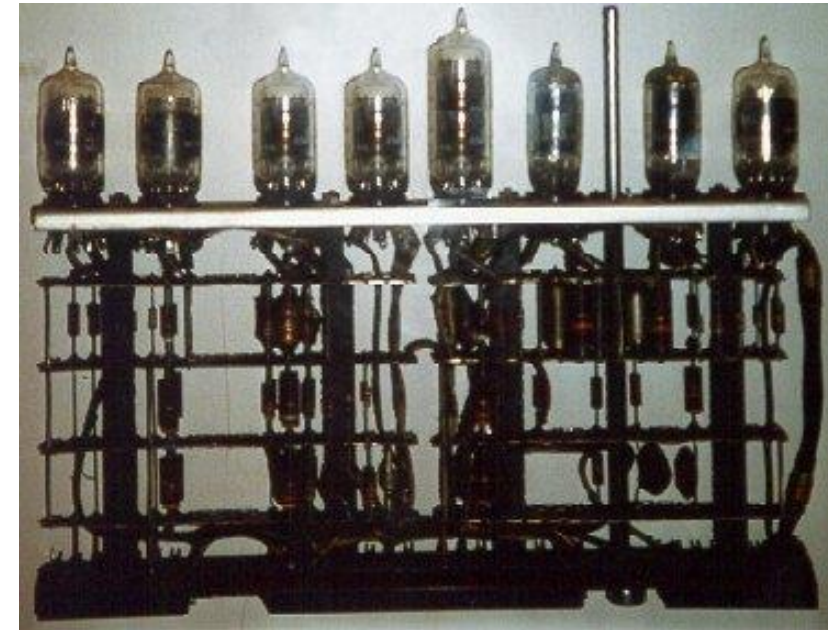- Purpose
 - Used as signal amplifiers and switches
- Advantages
 - High power and frequency operation
 - Operation at higher voltages
 - Less vulnerable to electromagnetic pulses
- Disadvantages
 - Very large and fragile
 - Energy inefficient
 - Expensive



Invention

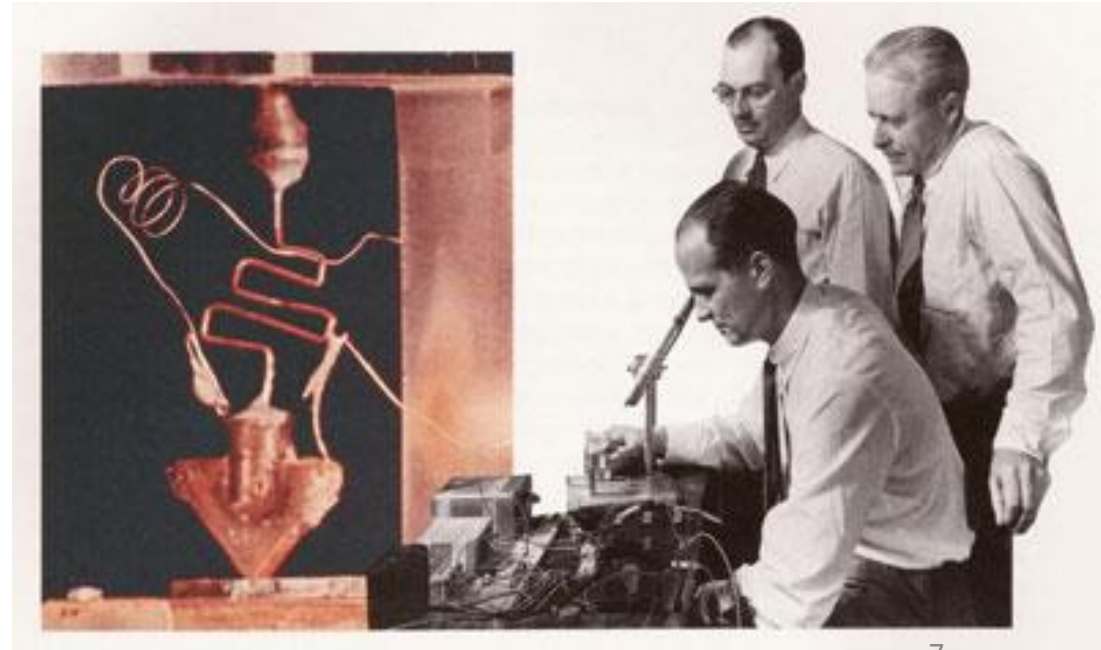- Evolution of electronics
 - In need of a device that was small, robust, reliable, energy efficient and cheap to manufacture
- 1947
 - John Bardeen, Walter Brattain and William Schockly invented transistor
- Transistor Effect
 - “when electrical contacts were applied to a crystal of germanium, the output power was larger than the input.”




General Applications



Transistor Development

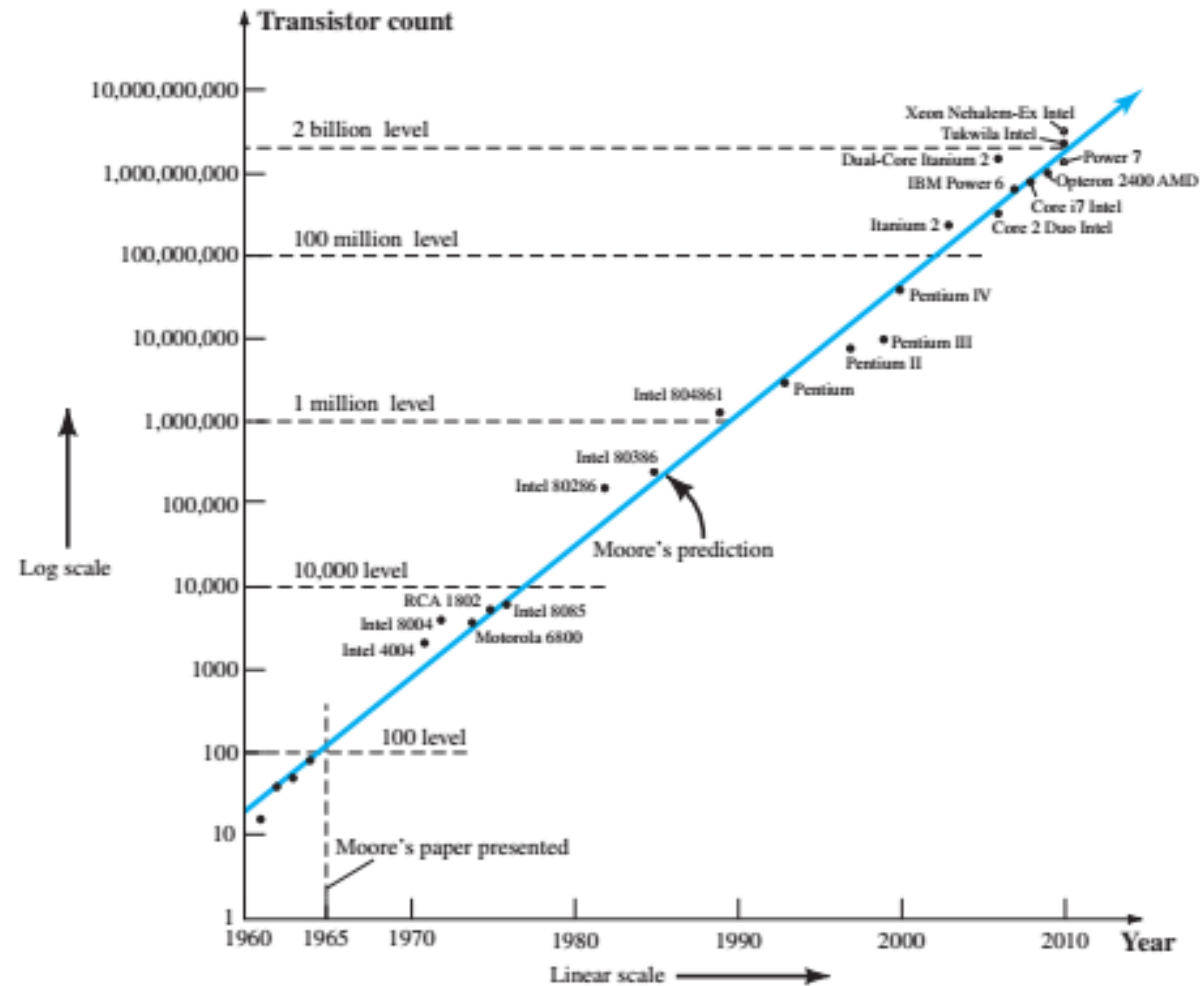
- **Moore's law** predicts that the transistor count of an integrated circuit will double every 2 years.



Where can the field go from here?


Transistor Construction₁

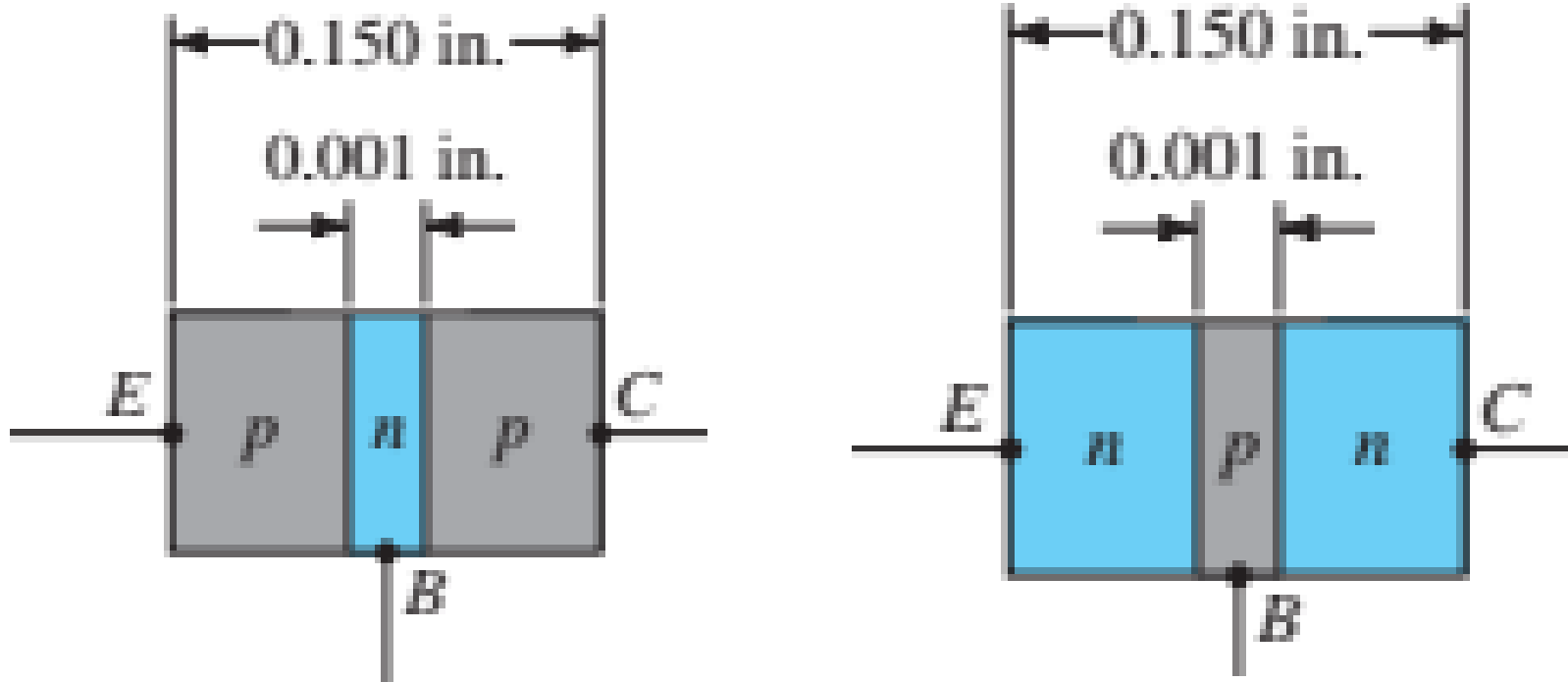- The transistor is a three-layer semiconductor device consisting of either two n - and one p -type layers of material (nnp transistor) or two p - and one n -type layers of material (pnp transistor).




Transistor Construction₂

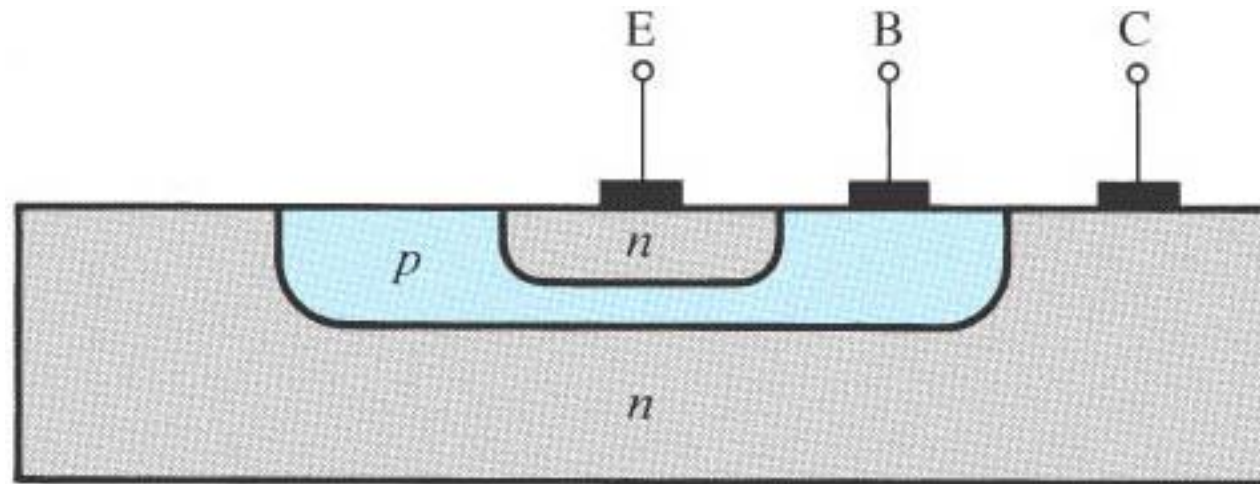- The three layers are Emitter, Base and Collector
 - **Base** region is much thinner as compared to the collector and emitter
 - **Emitter** is heavily doped, Base is lightly and collector is intermediate
 - **Collector** regions is physically largest




Transistor Operation₁

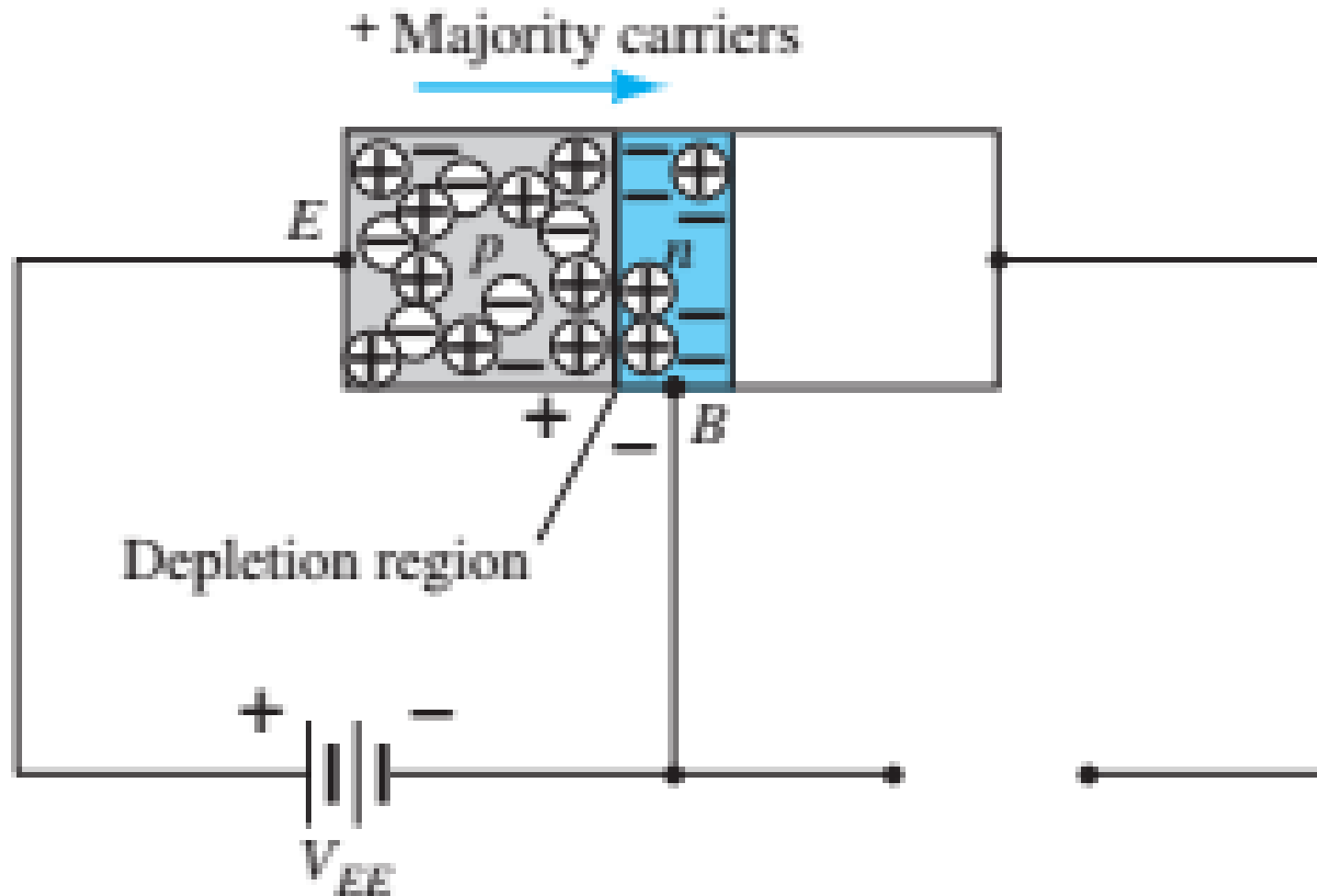- The operation discussed in pnp transistor





Transistor Operation₂

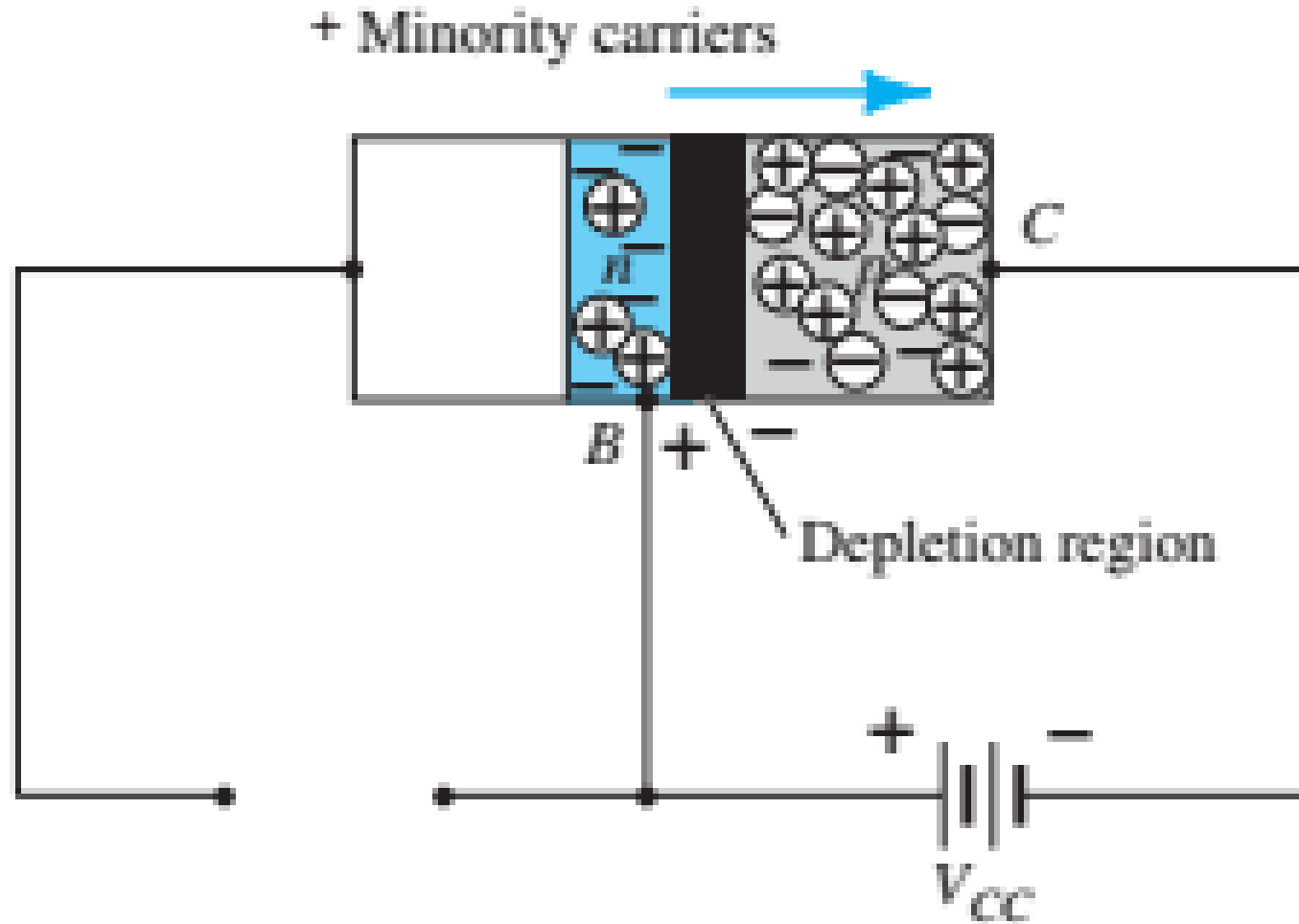- The operation discussed in pnp transistor



Transistor Operation

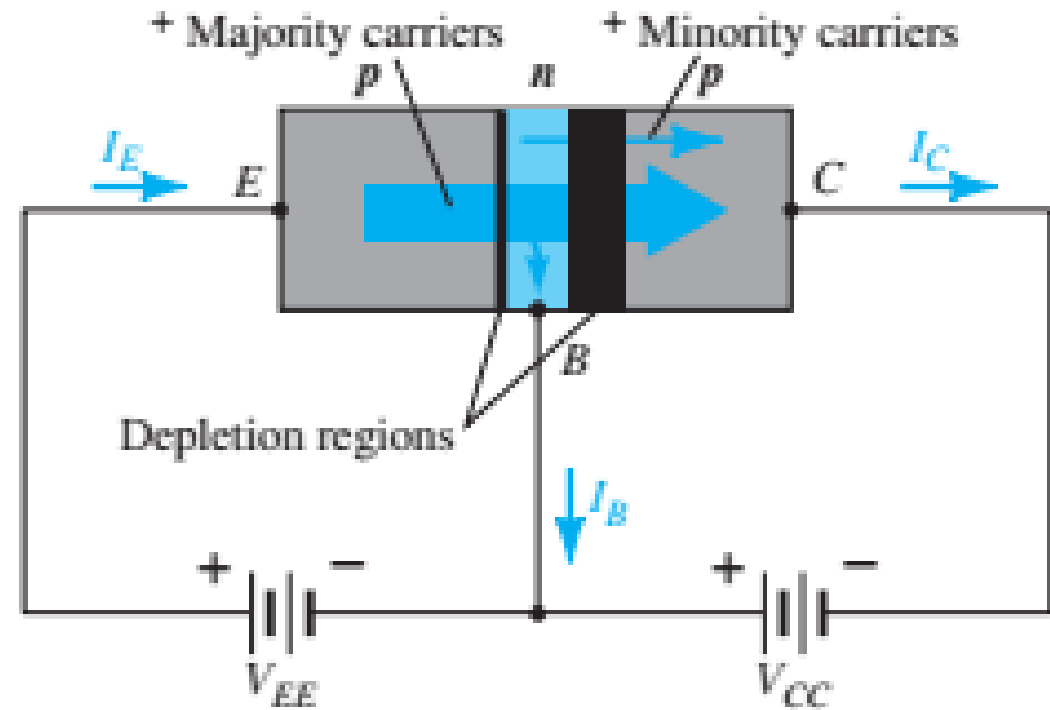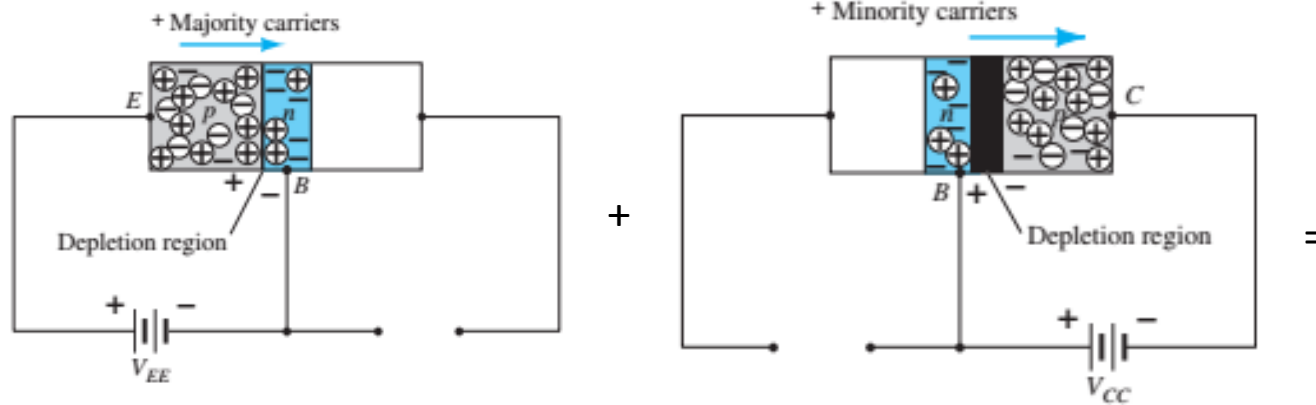- The operation discussed in pnp transistor




- The collector current by Kirchhoff's law

$$I_C = I_{C_{\text{majority}}} + I_{CO_{\text{minority}}}$$

- In Electronic analysis


$$I_E = I_C + I_B$$

Transistor Configuration

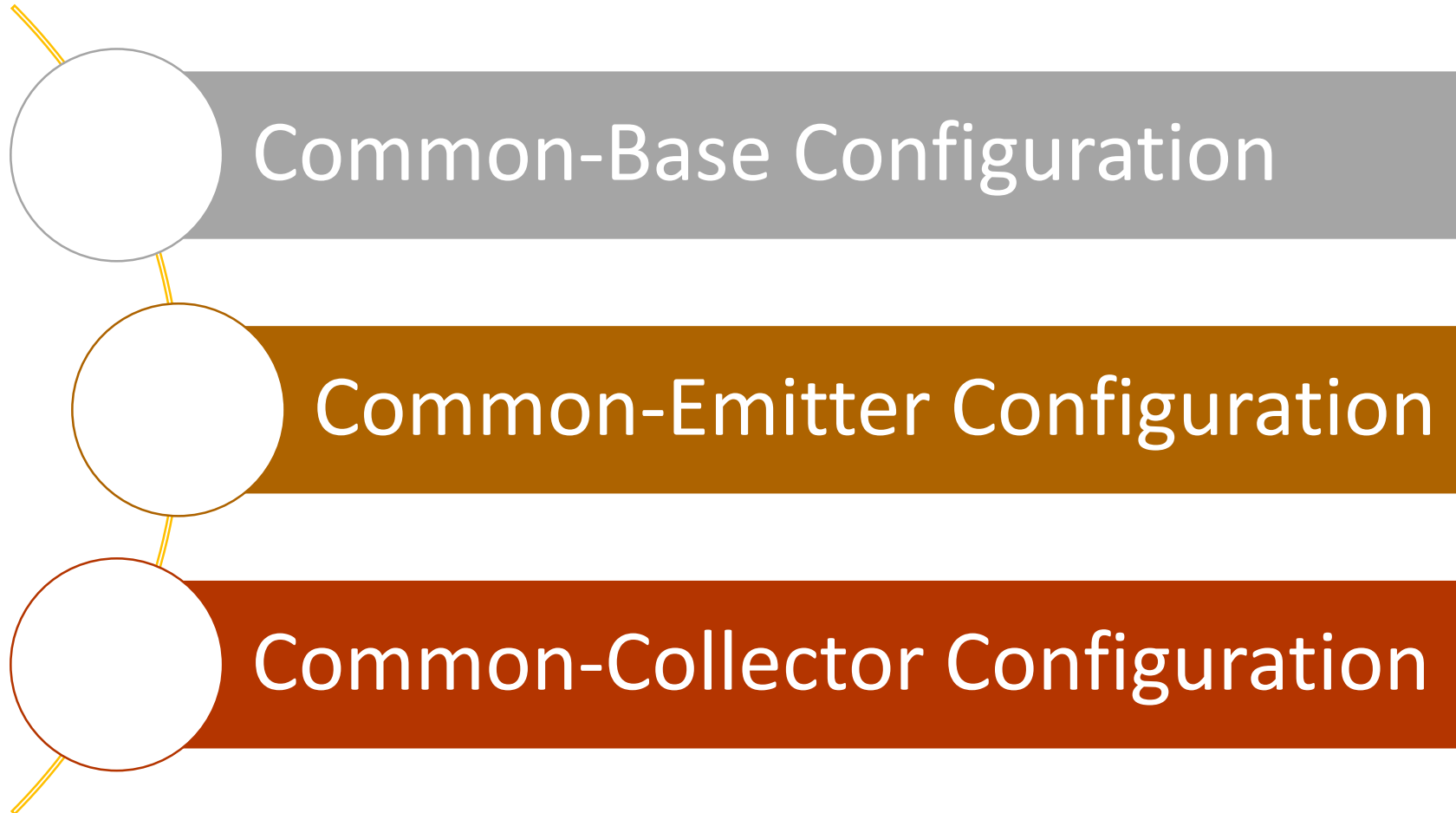


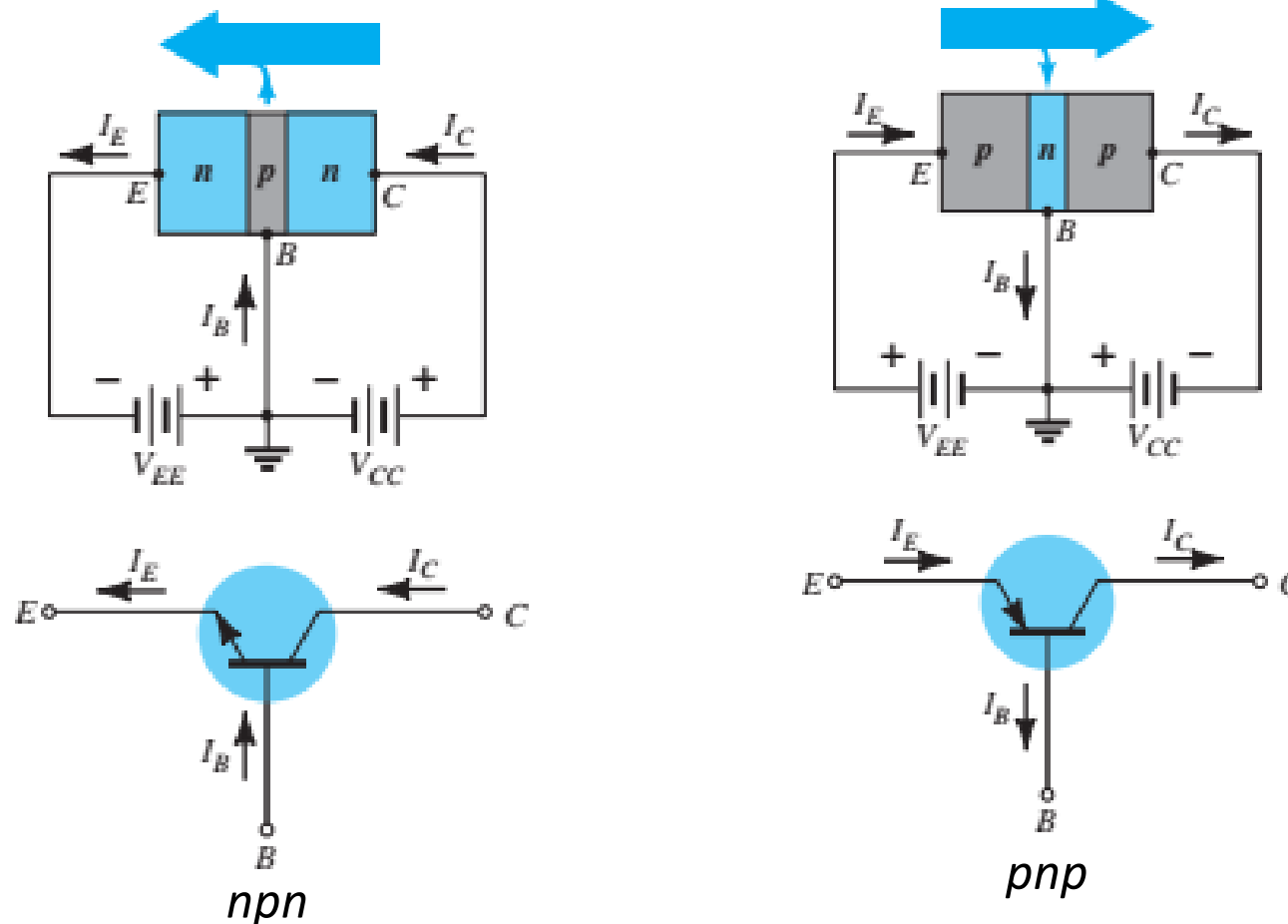1. Common-Base Configuration₁


- The common-base terminology is derived from the fact that the base is common to both the input and output sides of the configuration.



1. Common-Base Configuration₂

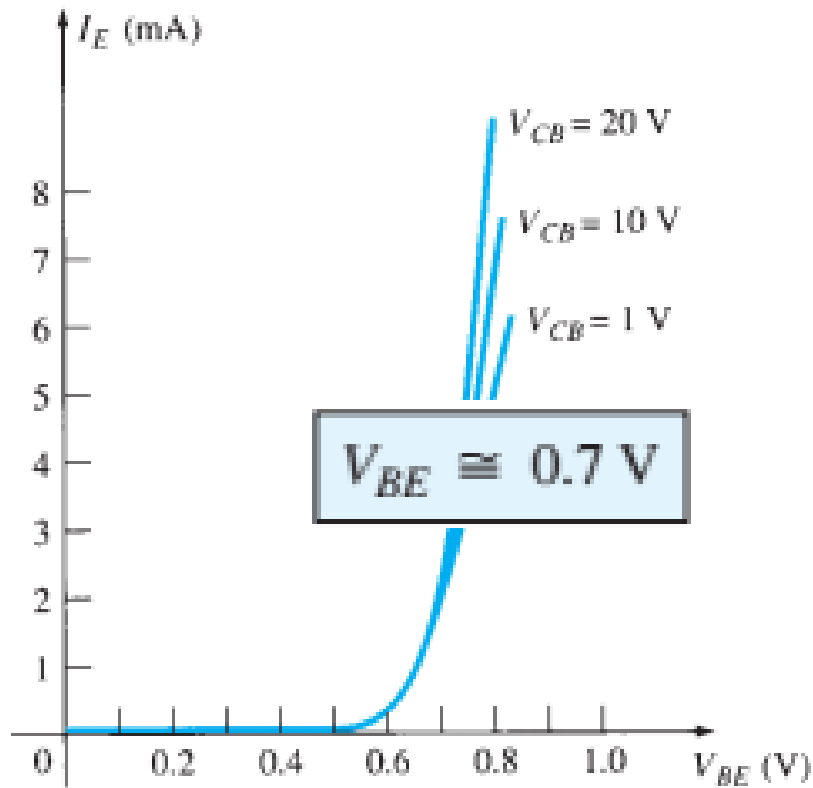




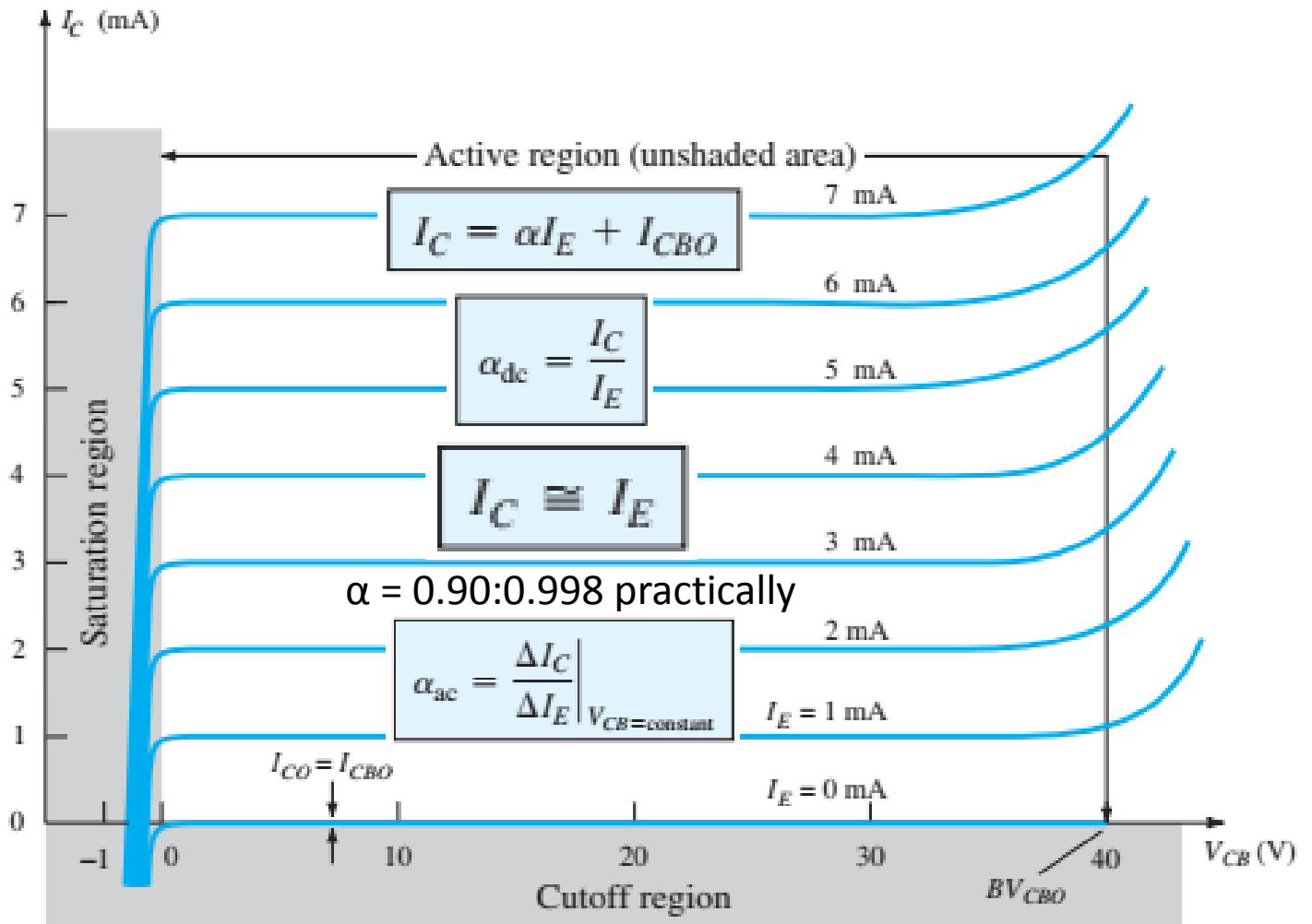
Input or driving point characteristics for a common-base silicon transistor amplifier.





Output or collector characteristics for a common-base transistor amplifier.

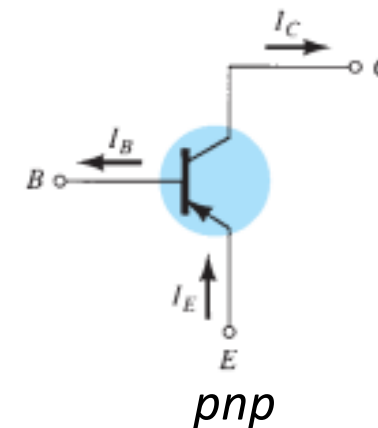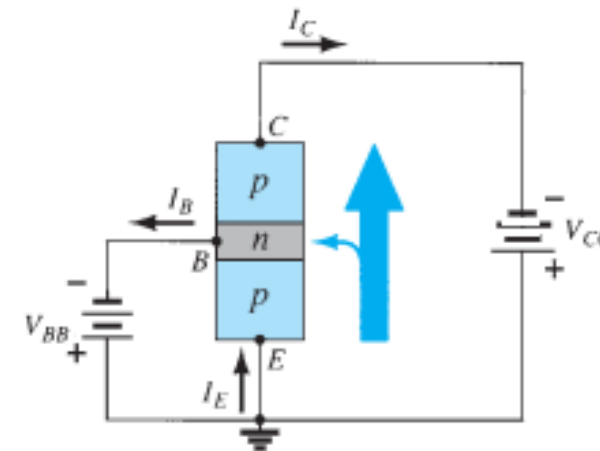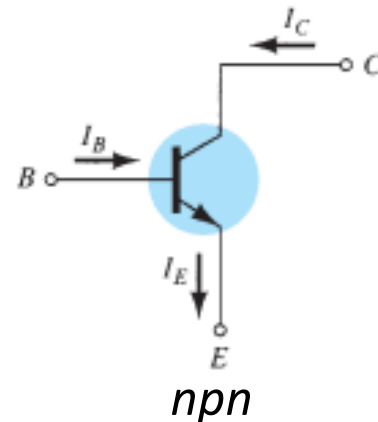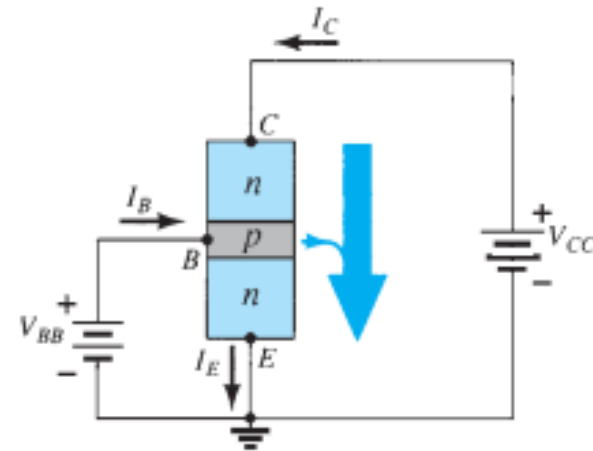2. Common-Emitter Configuration₁

- It is called the *common-emitter configuration* because the emitter is common to both the input and output terminals (in this case common to both the base and collector terminals).



2. Common-Emitter Configuration₂

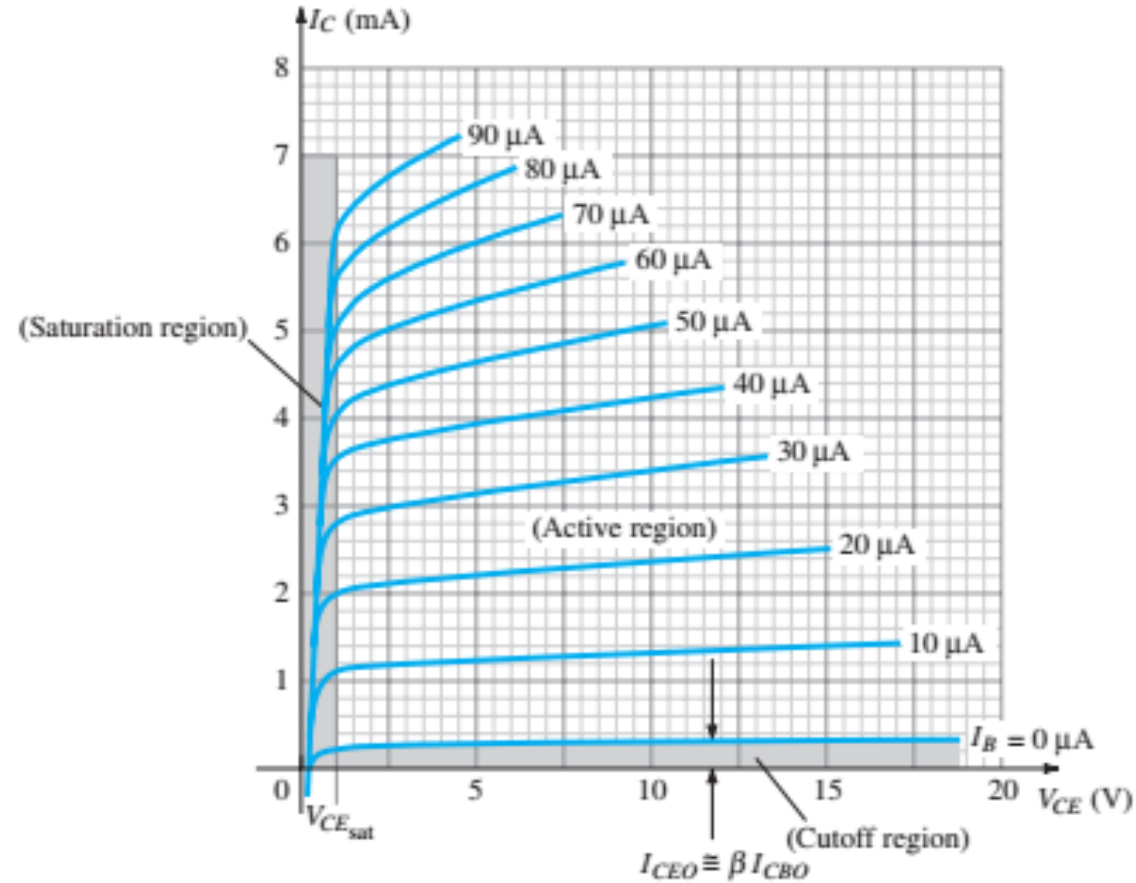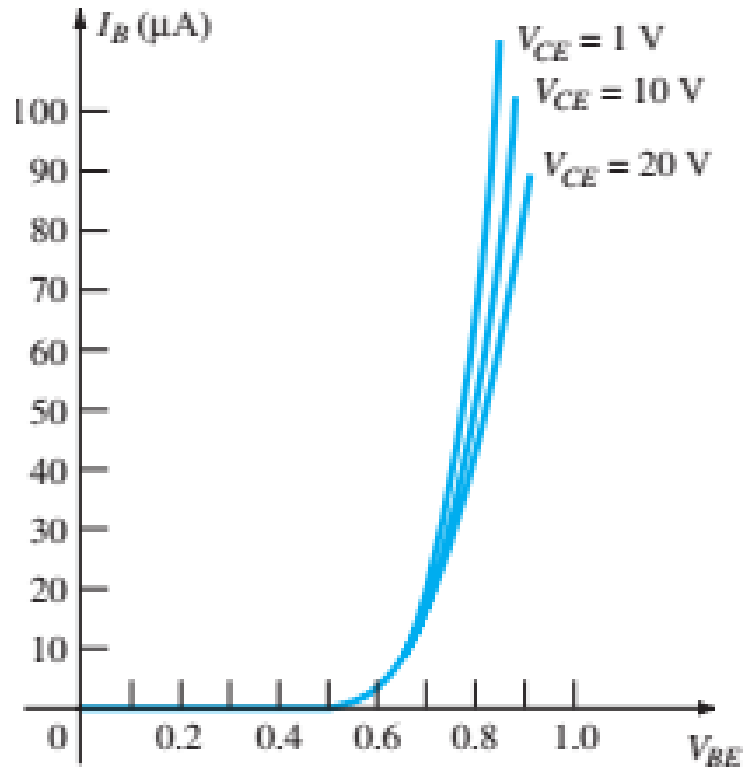

$$\beta_{dc} = \frac{I_C}{I_B}$$

$\beta=50:400$ practically

$$\beta_{ac} = \frac{\Delta I_C}{\Delta I_B} \Big|_{V_{CE}=\text{constant}}$$

$$\alpha = \frac{\beta}{\beta + 1}$$


$$\beta = \frac{\alpha}{1 - \alpha}$$

$$I_C = \beta I_B$$

$$I_E = (\beta + 1) I_B$$

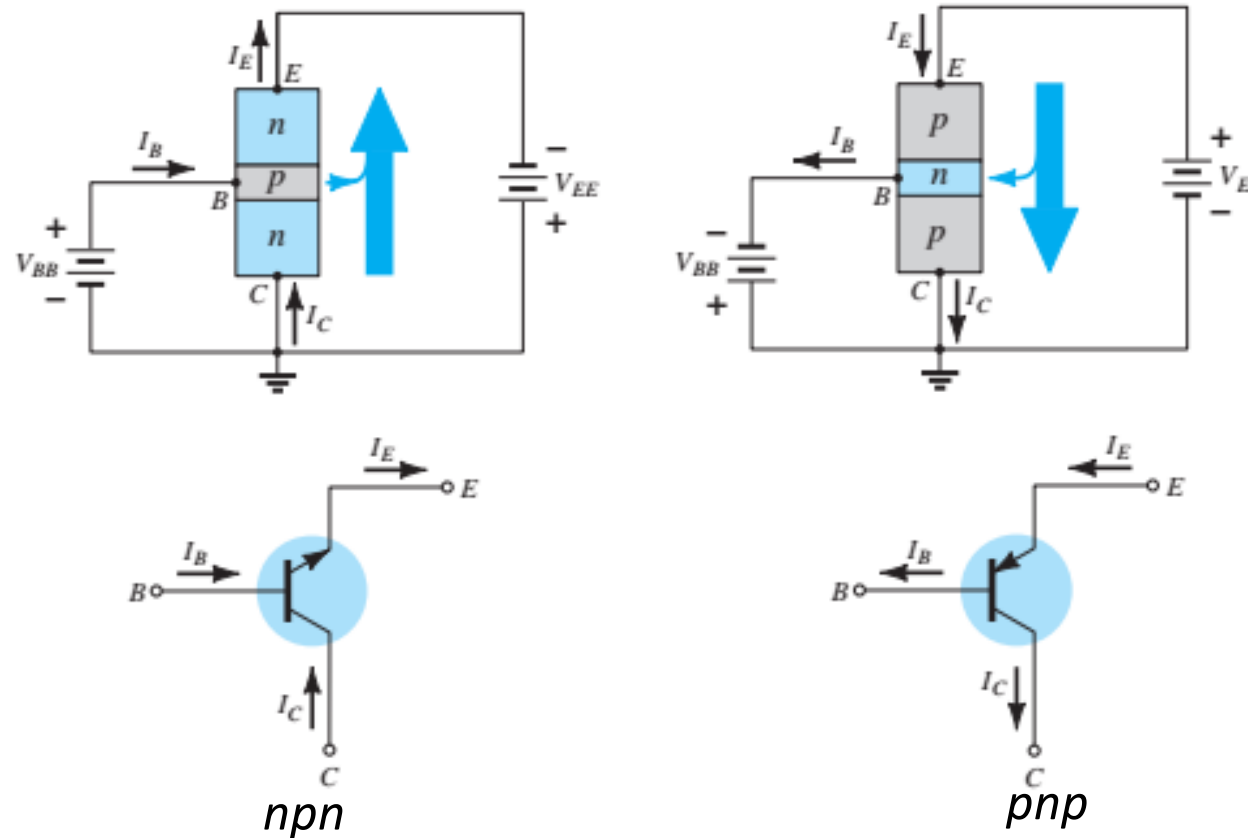3. Common-Collector Configuration₁


- The common-collector configuration is used primarily for impedance-matching purposes since it has a high input impedance and low output impedance, opposite to that of the common-base and common emitter configurations.



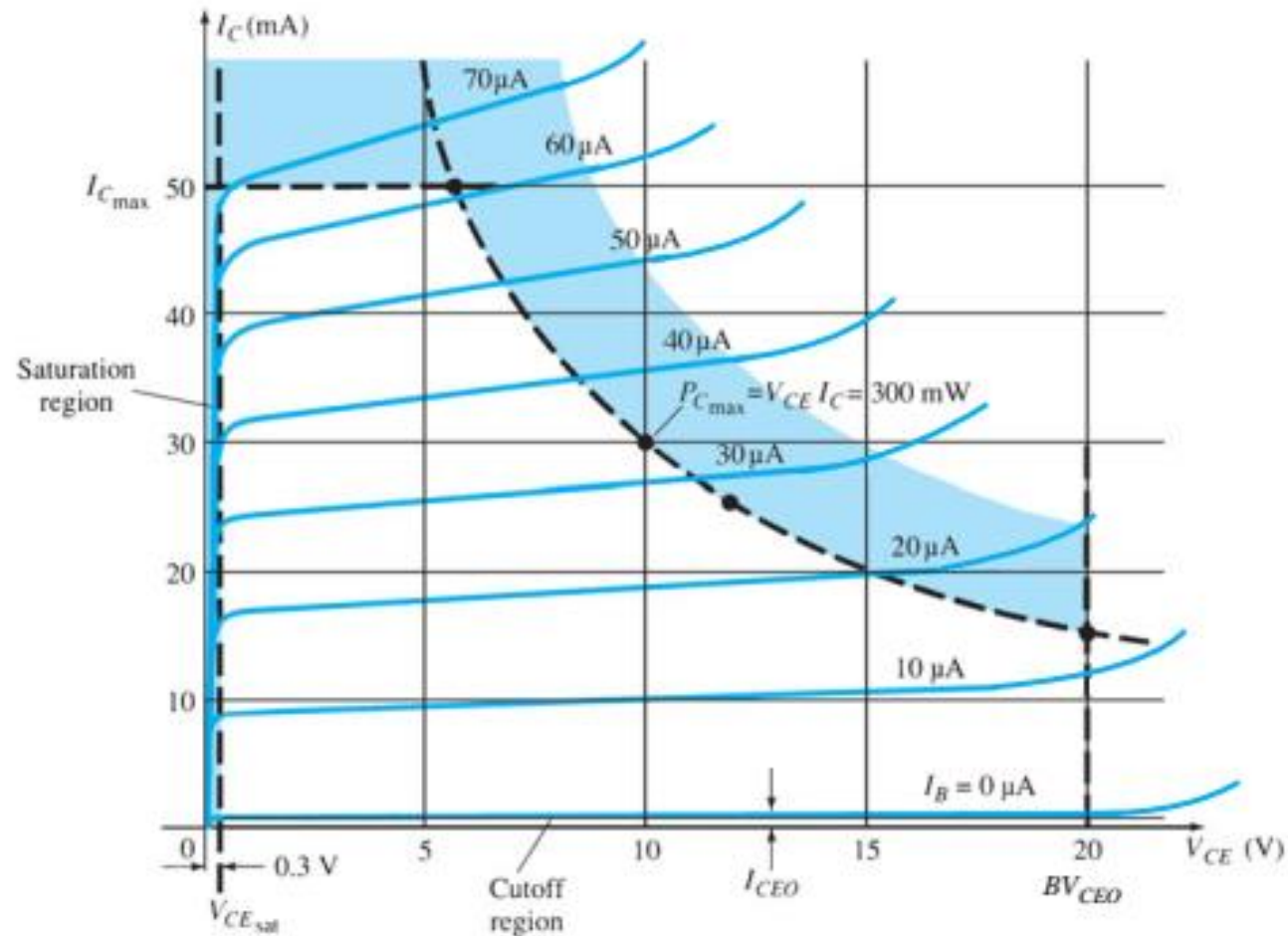3. Common-Collector Configuration₂

- Limits of operation

Defining the linear (undistorted) region of operation for a transistor



The output characteristics of the common-collector configuration are the same as for the common-emitter configuration ($I_C \approx I_E$).

$$P_{C_{max}} = V_{CE} I_C$$

$$\begin{aligned} I_{CE0} &\cong I_C \cong I_{C_{max}} \\ V_{CE_{sat}} &\cong V_{CE} \cong V_{CE_{max}} \\ V_{CE} I_C &\cong P_{C_{max}} \end{aligned}$$

Transistor Configuration Sheet

- Since the specification sheet is the communication link between the manufacturer and user, it is particularly important that the information provided be recognized and correctly understood.

OFF CHARACTERISTICS

Collector-Emitter Breakdown Voltage (1) ($I_C = 1.0 \text{ mA}$, $I_E = 0$)	$V_{(BR)CEO}$	30		Vdc
Collector-Base Breakdown Voltage ($I_C = 10 \mu\text{A}$, $I_E = 0$)	$V_{(BR)CBO}$	40		Vdc
Emitter-Base Breakdown Voltage ($I_E = 10 \mu\text{A}$, $I_C = 0$)	$V_{(BR)EBO}$	5.0	-	Vdc
Collector Cutoff Current ($V_{CB} = 20 \text{ Vdc}$, $I_B = 0$)	I_{CBO}	-	50	nA
Emitter Cutoff Current ($V_{BE} = 3.0 \text{ Vdc}$, $I_C = 0$)	I_{EBO}	-	50	nA

ON CHARACTERISTICS

DC Current Gain(1) ($I_C = 2.0 \text{ mA}$, $V_{CE} = 1.0 \text{ Vdc}$) ($I_C = 50 \text{ mA}$, $V_{CE} = 1.0 \text{ Vdc}$)	h_{FE}	50 25	150 -	-
Collector-Emitter Saturation Voltage(1) ($I_C = 50 \text{ mA}$, $I_B = 5.0 \text{ mA}$)	$V_{CE(sat)}$	-	0.3	Vdc
Base-Emitter Saturation Voltage(1) ($I_C = 50 \text{ mA}$, $I_B = 5.0 \text{ mA}$)	$V_{BE(sat)}$	-	0.95	Vdc
Small-Signal Current Gain ($I_C = 2.0 \text{ mA}$, $V_{CE} = 10 \text{ Vdc}$, $f = 1.0 \text{ kHz}$)	h_{fe}	50	200	-



MAXIMUM RATINGS

Rating	Symbol	2N4123	Unit
Collector-Emitter Voltage	V_{CEO}	30	Vdc
Collector-Base Voltage	V_{CBO}	40	Vdc
Emitter-Base Voltage	V_{EBO}	5.0	Vdc
Collector Current - Continuous	I_C	200	mA
Total Device Dissipation @ $T_A = 25^\circ\text{C}$ Derate above 25°C	P_D	625 5.0	mW mW/°C
Operating and Storage Junction Temperature Range	T_j, T_{stg}	-55 to +150	°C

Limits of Operation


$$7.5 \mu\text{A} \leq I_C \leq 200 \text{ mA}$$

$$0.3 \text{ V} \leq V_{CE} \leq 30 \text{ V}$$

$$V_{CE} I_C \leq 650 \text{ mW}$$

Transistor Testing

1. Curve Tracer

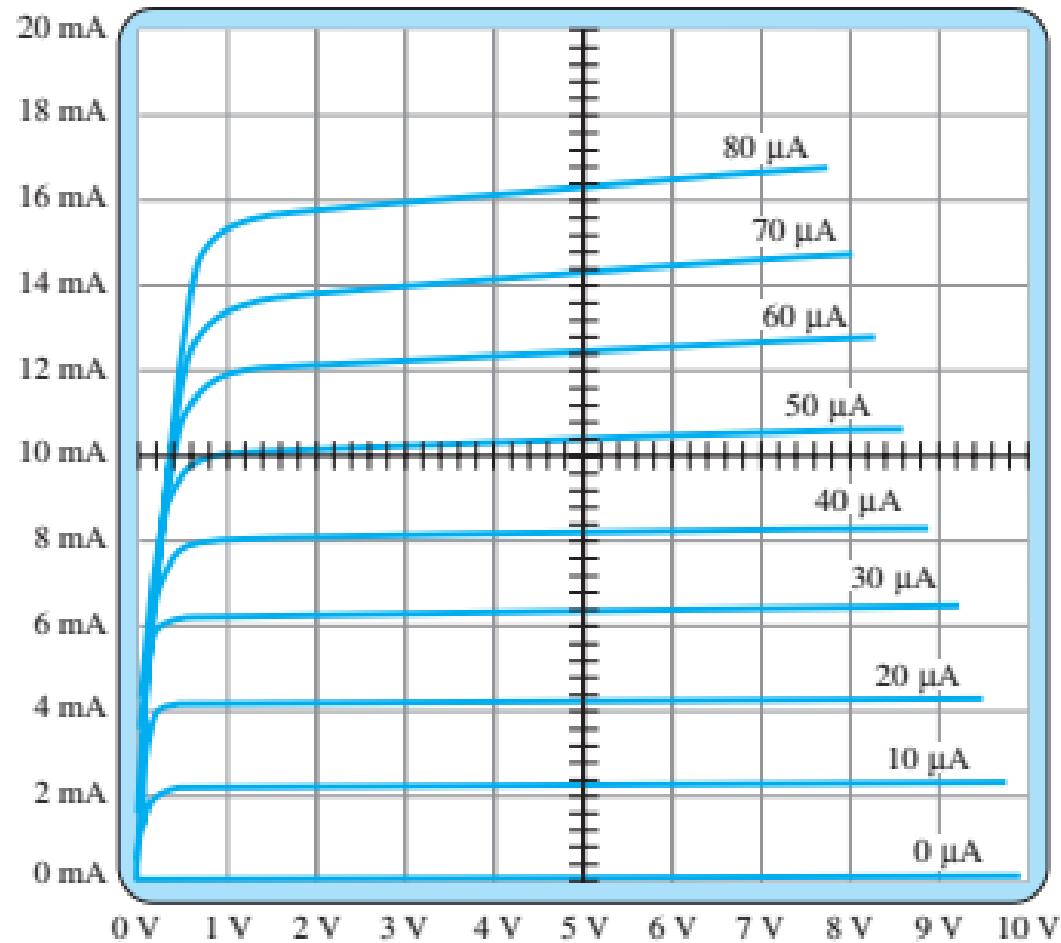


Curve tracer response to 2N3904 npn transistor.

- Vertical per div 2 mA
- Horizontal per div 1 V
- Per Step 10 μA
- β or gm per div 200



2. Transistor Testers



3. Ohmmeter

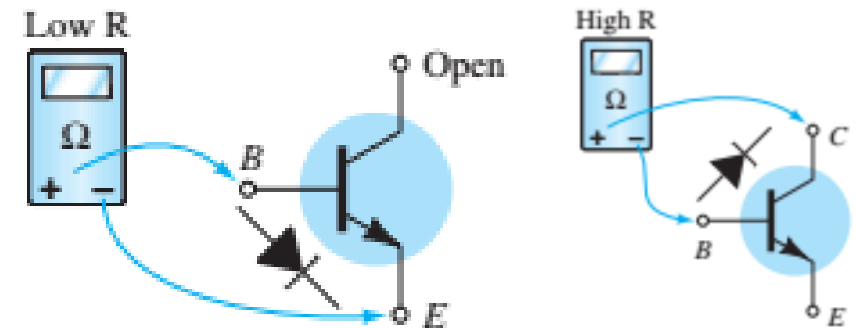


Modern Transistors

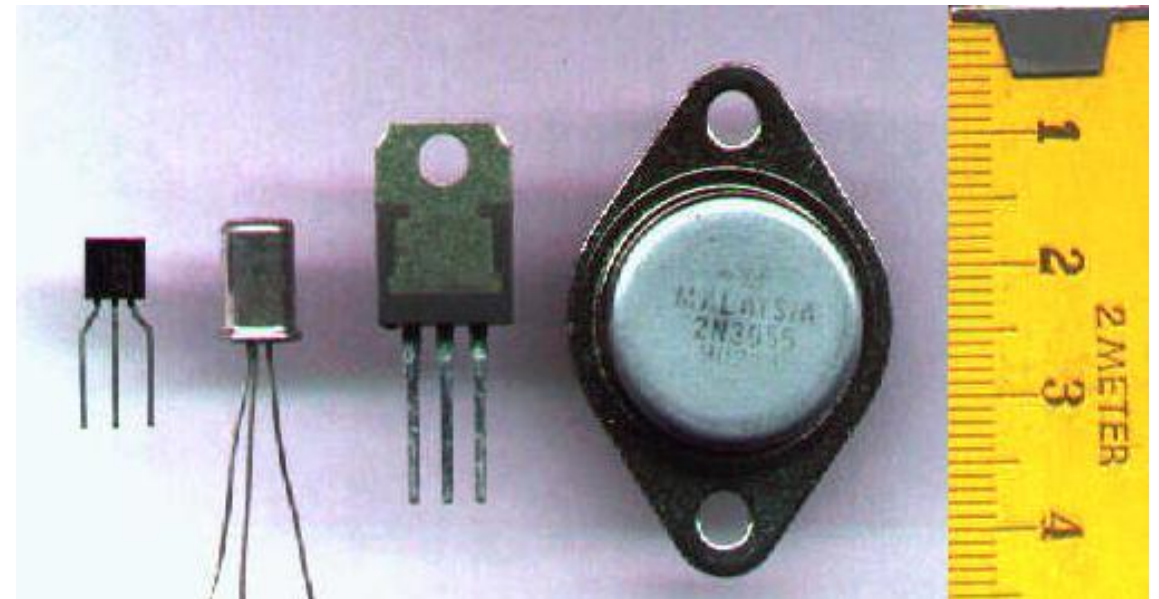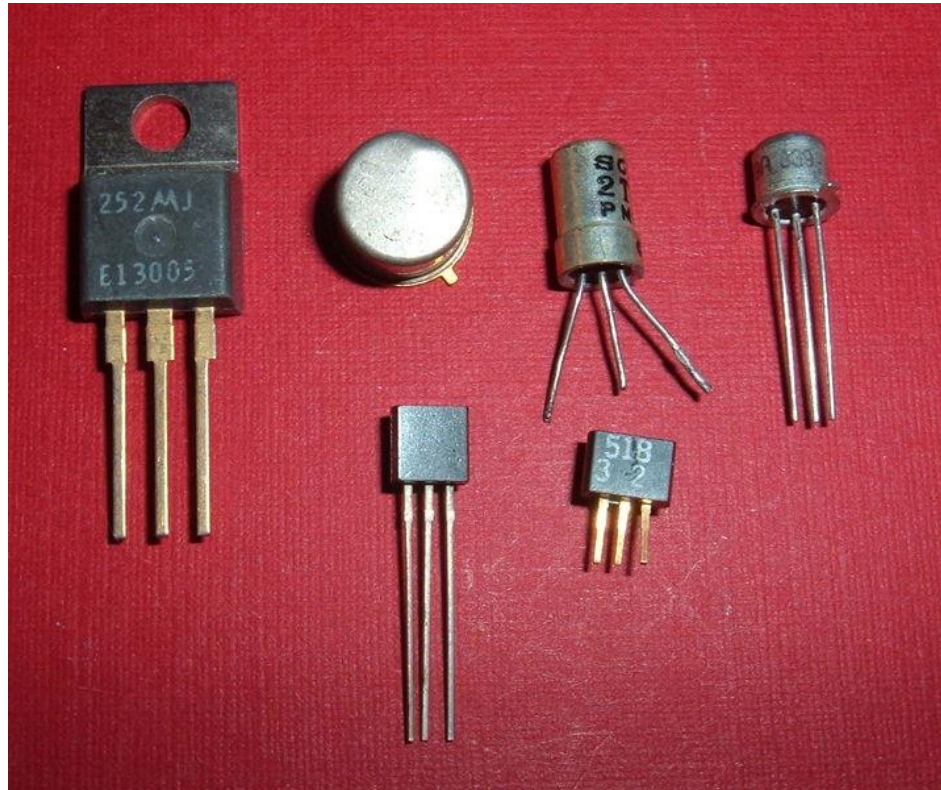



Transistor Casing and Terminal Identification

- Casing

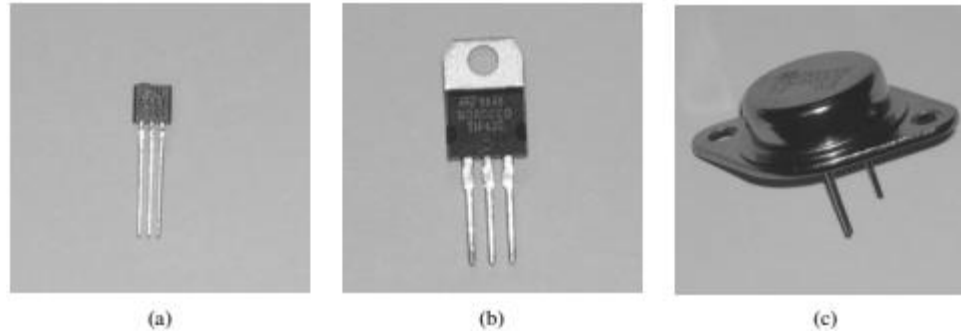

*Various types of general-purpose or switching transistors:
(a) low power; (b) medium power; (c) medium to high power.*

- Terminal Identification

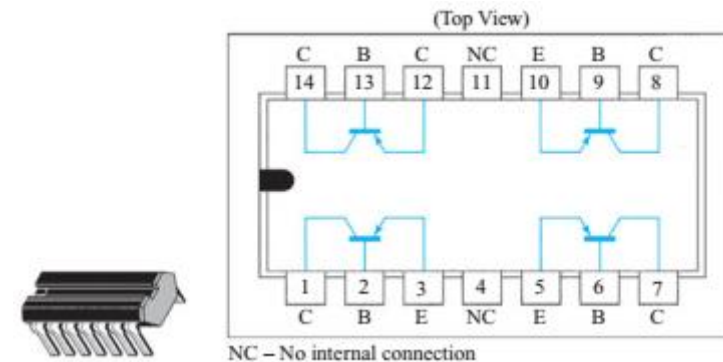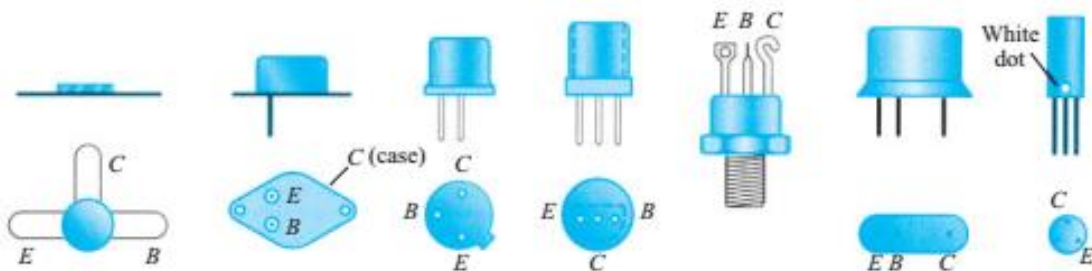

*Type Q2T2905 Texas Instruments quad
pnp silicon transistor*

Thank You!

