

ECE 121

Electronics (1)


Lec. 2: BJT Biasing Circuits

Instructor

**Dr. Maher Abdelrasoul**

<http://www.bu.edu.eg/staff/mahersalem3>

# Outline

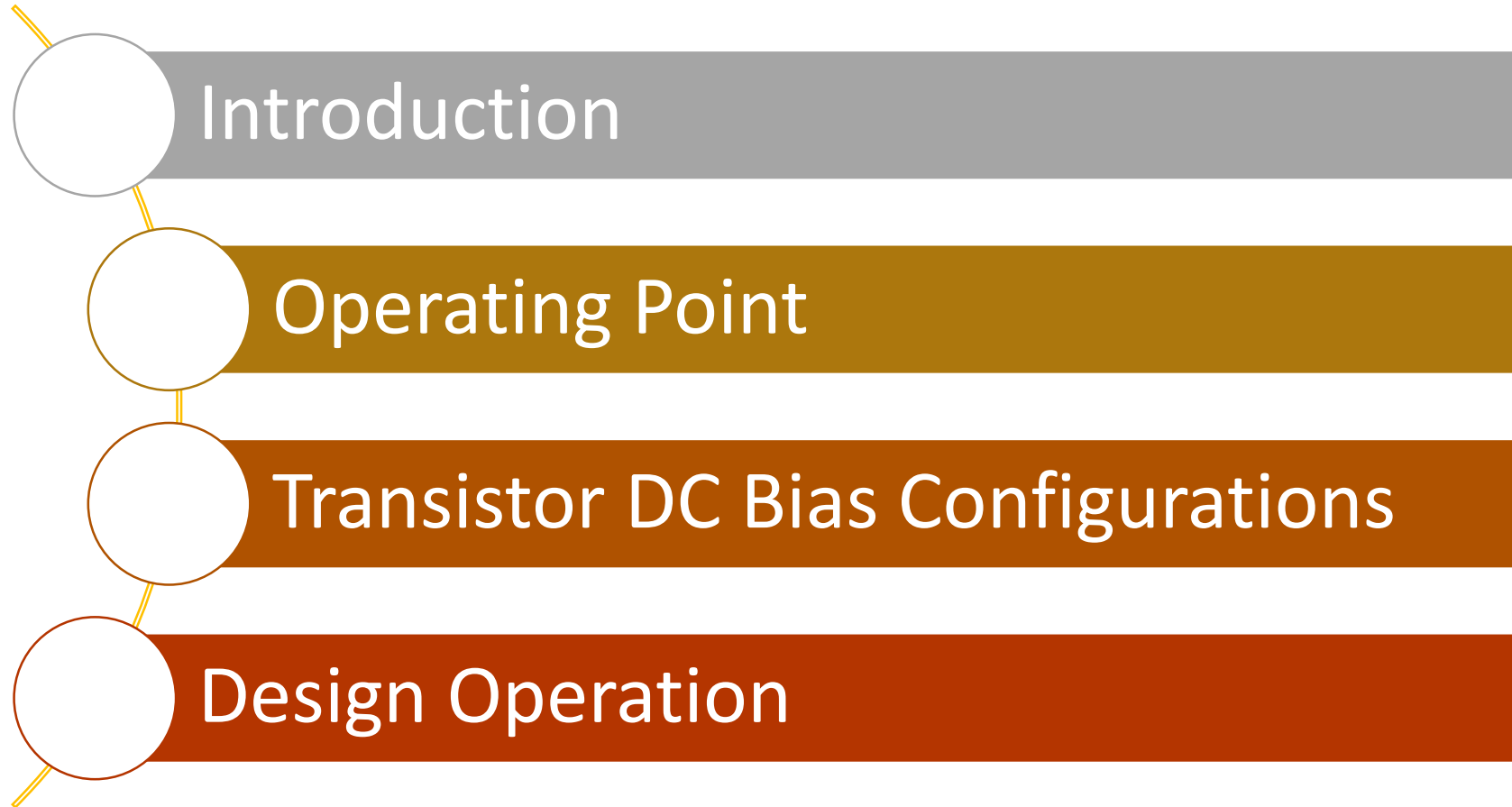

# Introduction

- Any increase in ac voltage, current, or power is the result of a transfer of energy from the applied dc supplies.
- The analysis or design of any electronic amplifier therefore has two components: a dc and an ac portion.
- Basic Relationships/formulas for a transistor:

$$V_{BE} \cong 0.7 \text{ V}$$

$$I_E = (\beta + 1)I_B \cong I_C$$

$$I_C = \beta I_B$$


- **Biassing** means applying of dc voltages to establish a fixed level of current and voltage. >>> Q-Point

# Operating Point

- For transistor amplifiers the resulting dc current and voltage establish an operating point on the characteristics that define the region that will be employed for amplification of the applied signal.
- Because the operating point is a fixed point on the characteristics, it is also called the quiescent point (abbreviated Q-point).

- Transistor Regions Operation:

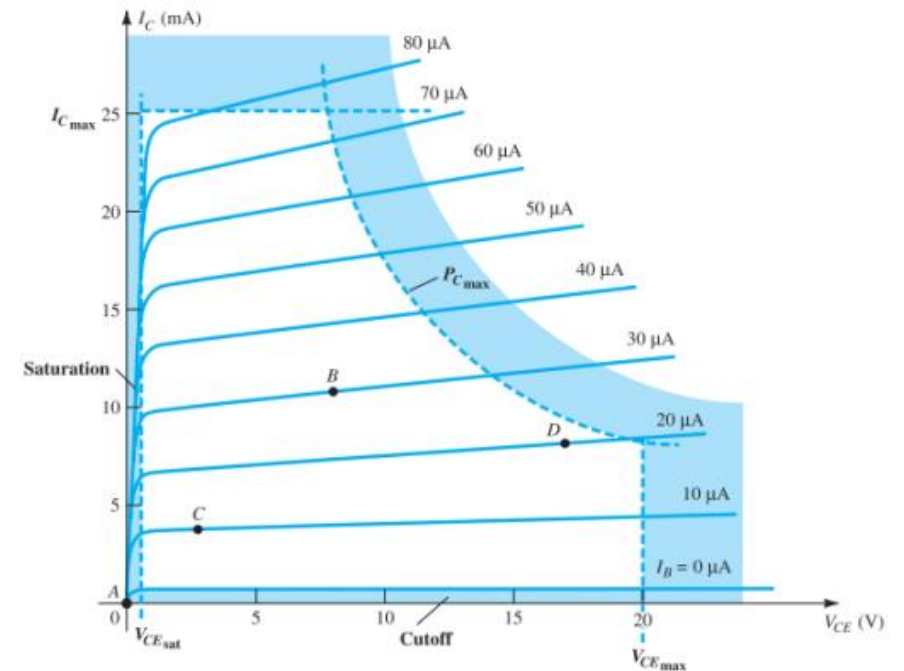
1. Linear-region operation:  
Base–emitter junction forward-biased  
Base–collector junction reverse-biased
2. Cutoff-region operation:  
Base–emitter junction reverse-biased  
Base–collector junction reverse-biased
3. Saturation-region operation:  
Base–emitter junction forward-biased  
Base–collector junction forward-biased



# Transistor DC Bias Configurations


- ✓ Fixed-Bias Configuration
- ✓ Emitter-Bias Configuration
- ✓ Voltage-Divider Bias Configuration
- ✓ Collector Feedback Configuration
- ✓ Emitter-Follower Configuration
- ✓ Common-Base Configuration
- ✓ Miscellaneous Bias Configurations

# Fixed-Bias Configuration (1 of 4)


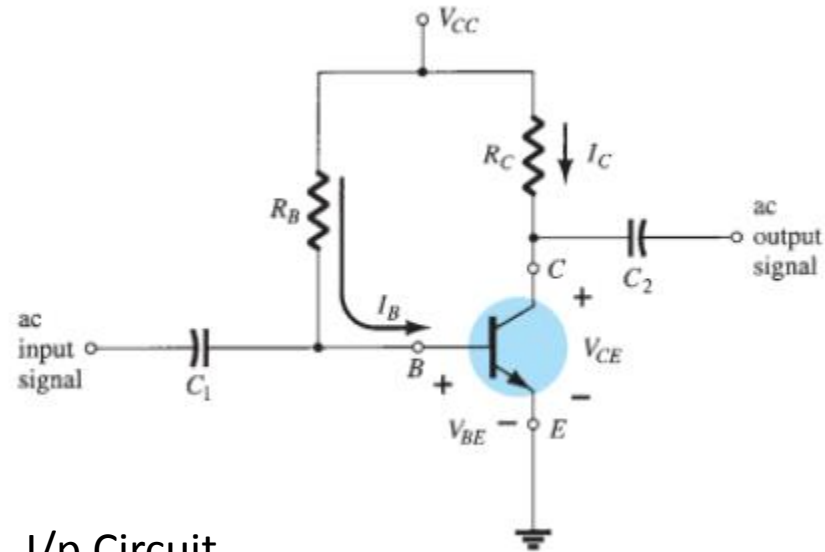


I/p Circuit

DC equivalent

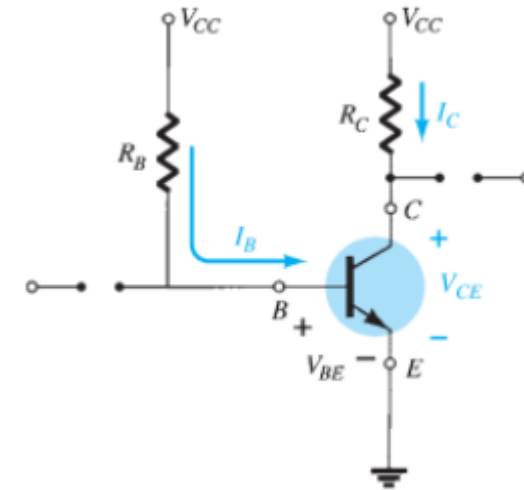

O/p Circuit

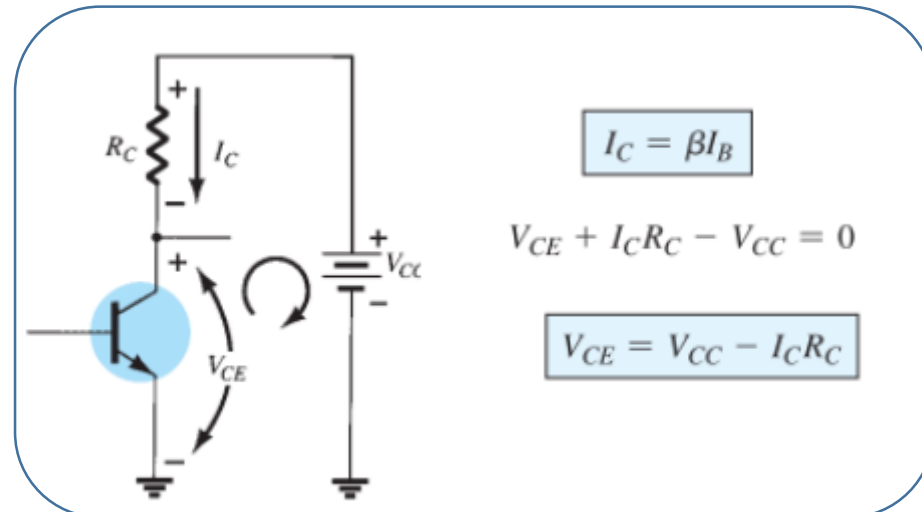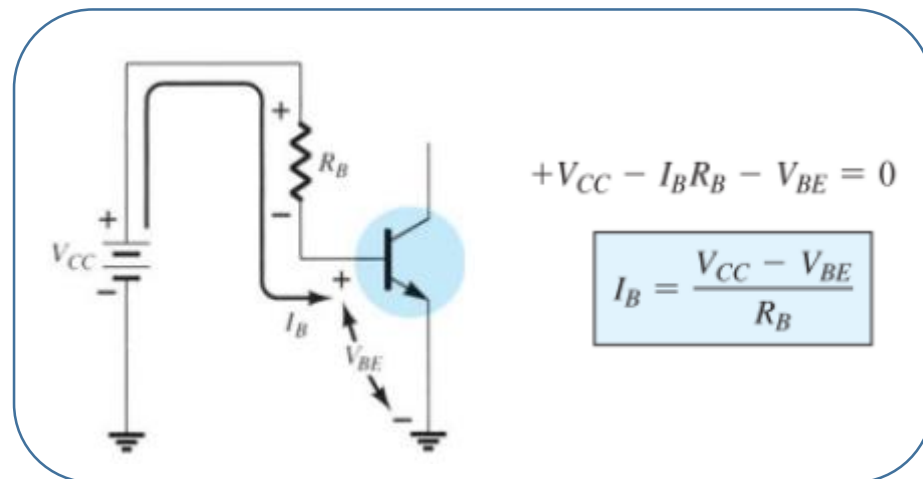

# Fixed-Bias Configuration (2 of 4)

**EXAMPLE 4.1** Determine the following for the fixed-bias configuration

- $I_{BQ}$  and  $I_{CQ}$ .
- $V_{CEQ}$ .
- $V_B$  and  $V_C$ .
- $V_{BC}$ .

**Solution:**

$$I_{BQ} = \frac{V_{CC} - V_{BE}}{R_B} = \frac{12 \text{ V} - 0.7 \text{ V}}{240 \text{ k}\Omega} = 47.08 \text{ }\mu\text{A}$$

$$I_{CQ} = \beta I_{BQ} = (50)(47.08 \text{ }\mu\text{A}) = 2.35 \text{ mA}$$


$$\begin{aligned} V_{CEQ} &= V_{CC} - I_C R_C \\ &= 12 \text{ V} - (2.35 \text{ mA})(2.2 \text{ k}\Omega) \\ &= 6.83 \text{ V} \end{aligned}$$

$$\begin{aligned} V_B &= V_{BE} = 0.7 \text{ V} \\ V_C &= V_{CE} = 6.83 \text{ V} \end{aligned}$$

Using double-subscript notation yields




$$\begin{aligned} V_{BC} &= V_B - V_C = 0.7 \text{ V} - 6.83 \text{ V} \\ &= -6.13 \text{ V} \end{aligned}$$

 with the negative sign revealing that the junction is reversed-biased, as it should be for linear amplification.



# Fixed-Bias Configuration (3 of 4)

- **Transistor Saturation**

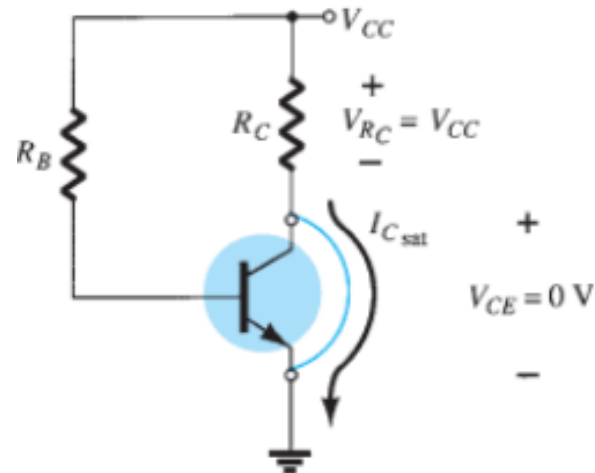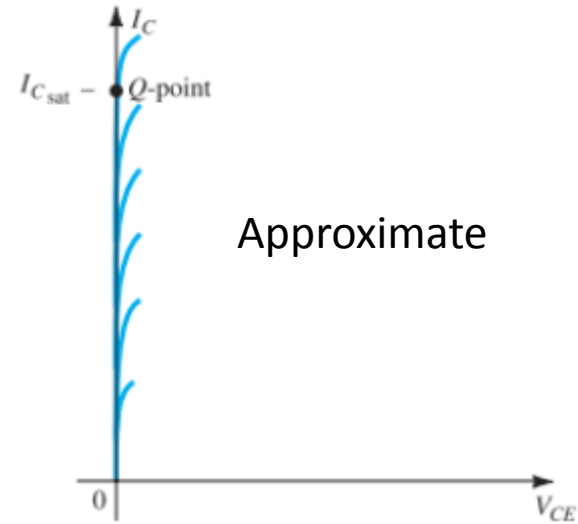
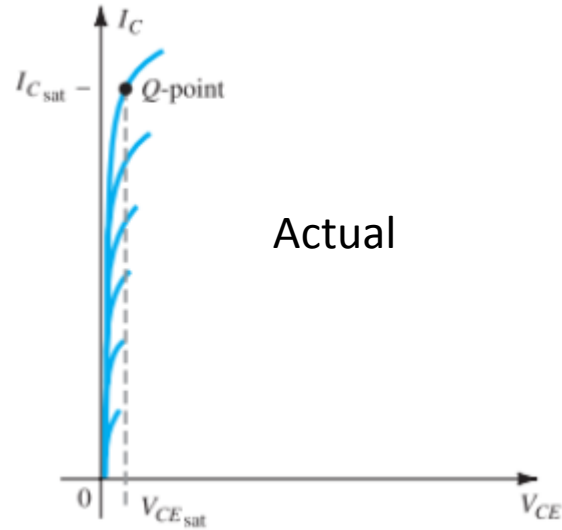


$$I_{C_{sat}} = \frac{V_{CC}}{R_C}$$



# Fixed-Bias Configuration (4 of 4)


- **Load Line Analysis**

 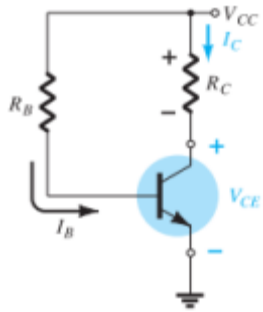


$$V_{CE} = V_{CC} - I_C R_C$$

$$V_{CE} = V_{CC} |_{I_C=0 \text{ mA}}$$


$$I_C = \frac{V_{CC}}{R_C} |_{V_{CE}=0 \text{ V}}$$

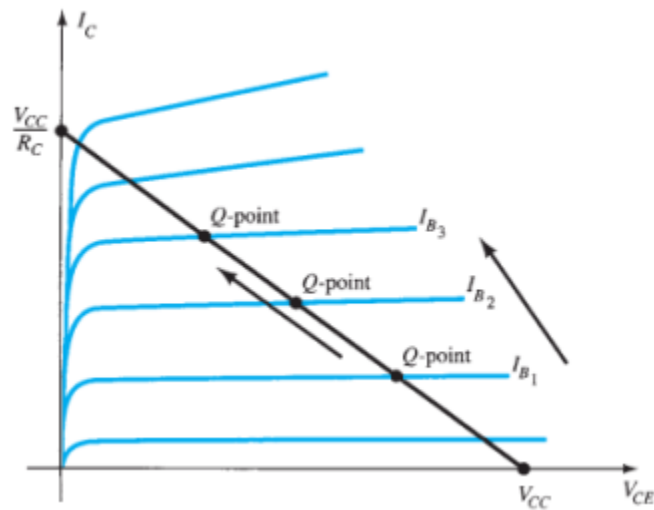

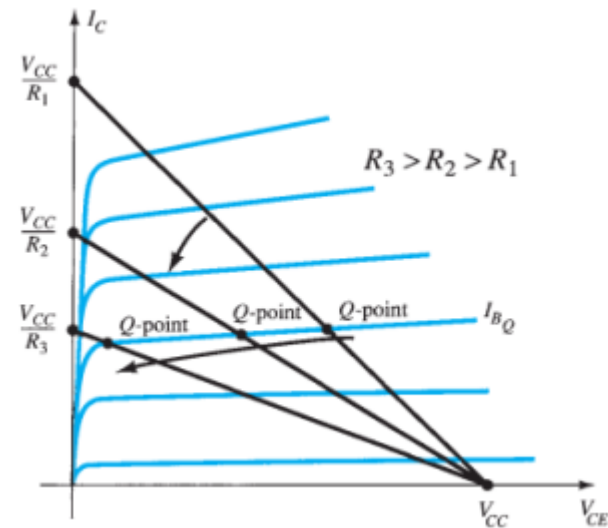Movement of the Q-point with increasing level of  $I_B$ .




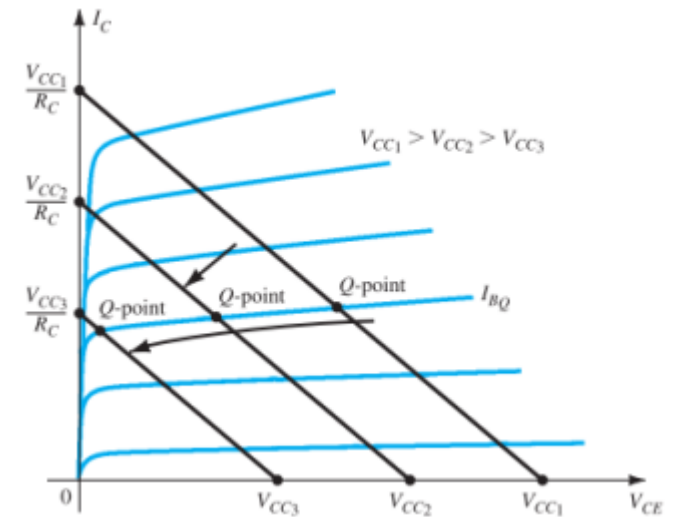Effect of an increasing level of  $R_C$  on the load line and the Q-point.




Effect of lower values of  $V_{CC}$  on the load line and the Q-point.


# Emitter-Bias Configuration (1 of 4)

 


DC equivalent →

 

I/p Circuit

 


O/p Circuit

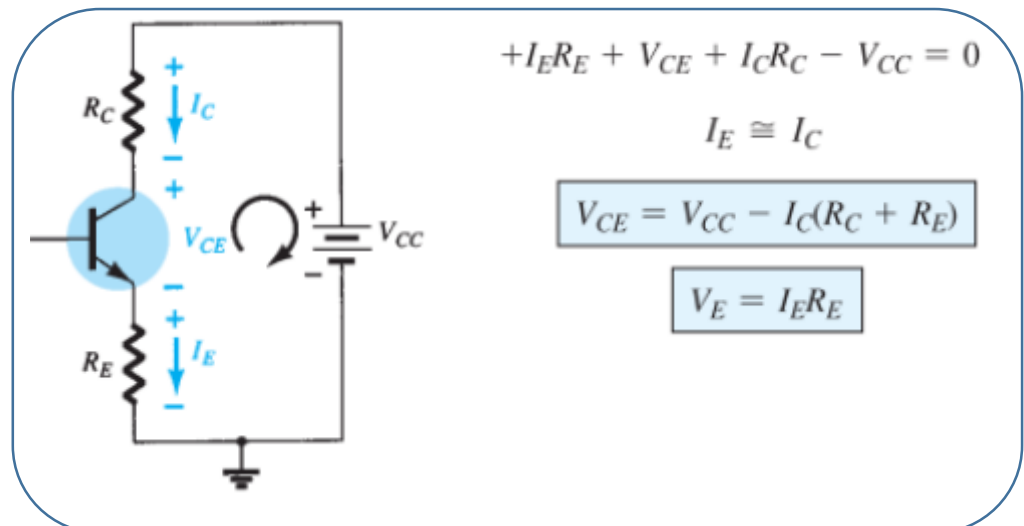

# Emitter-Bias Configuration (2 of 4)

**EXAMPLE 4.4** For the emitter-bias network of Fig. 4.23, determine:

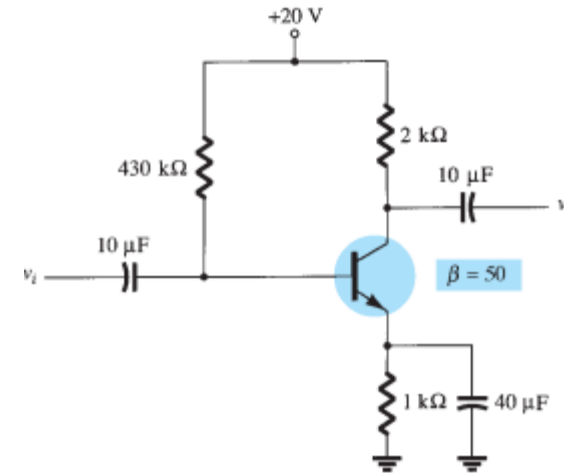- a.  $I_B$ .
- b.  $I_C$ .
- c.  $V_{CE}$ .
- d.  $V_C$ .
- e.  $V_E$ .
- f.  $V_B$ .
- g.  $V_{BC}$ .



**Solution:**

$$\begin{aligned} \text{a. Eq. (4.17): } I_B &= \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_E} = \frac{20 \text{ V} - 0.7 \text{ V}}{430 \text{ k}\Omega + (51)(1 \text{ k}\Omega)} \\ &= \frac{19.3 \text{ V}}{481 \text{ k}\Omega} = \mathbf{40.1 \mu\text{A}} \end{aligned}$$

$$\begin{aligned} \text{b. } I_C &= \beta I_B \\ &= (50)(40.1 \mu\text{A}) \\ &\cong \mathbf{2.01 \text{ mA}} \end{aligned}$$

$$\begin{aligned} \text{c. Eq. (4.19): } V_{CE} &= V_{CC} - I_C(R_C + R_E) \\ &= 20 \text{ V} - (2.01 \text{ mA})(2 \text{ k}\Omega + 1 \text{ k}\Omega) = 20 \text{ V} - 6.03 \text{ V} \\ &= \mathbf{13.97 \text{ V}} \end{aligned}$$

$$\begin{aligned} \text{d. } V_C &= V_{CC} - I_C R_C \\ &= 20 \text{ V} - (2.01 \text{ mA})(2 \text{ k}\Omega) = 20 \text{ V} - 4.02 \text{ V} \\ &= \mathbf{15.98 \text{ V}} \end{aligned}$$

$$\begin{aligned} \text{e. } V_E &= V_C - V_{CE} \\ &= 15.98 \text{ V} - 13.97 \text{ V} \\ &= \mathbf{2.01 \text{ V}} \end{aligned}$$

$$\begin{aligned} \text{or } V_E &= I_E R_E \cong I_C R_E \\ &= (2.01 \text{ mA})(1 \text{ k}\Omega) \\ &= \mathbf{2.01 \text{ V}} \end{aligned}$$


$$\begin{aligned} \text{f. } V_B &= V_{BE} + V_E \\ &= 0.7 \text{ V} + 2.01 \text{ V} \\ &= \mathbf{2.71 \text{ V}} \end{aligned}$$

$$\begin{aligned} \text{g. } V_{BC} &= V_B - V_C \\ &= 2.71 \text{ V} - 15.98 \text{ V} \\ &= \mathbf{-13.27 \text{ V}} \text{ (reverse-biased as required)} \end{aligned}$$
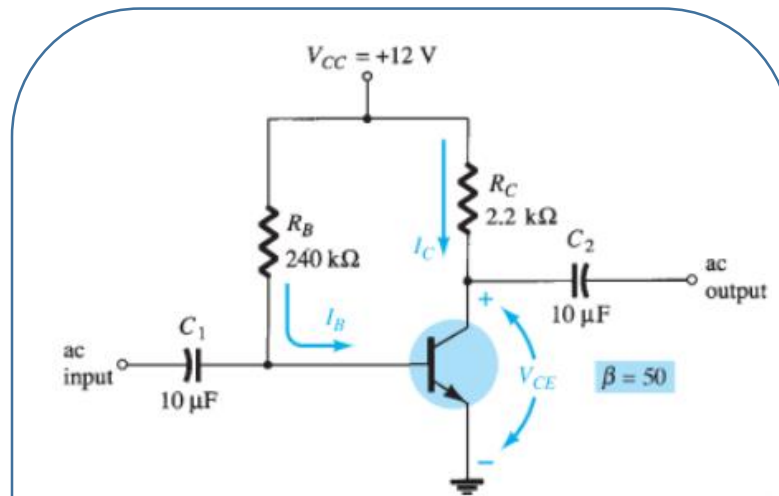
# Emitter-Bias Configuration (3 of 4)


- Improved Bias Stability

The addition of the emitter resistor to the dc bias of the BJT provides improved stability, that is, the dc bias currents and voltages remain closer to where they were set by the circuit when outside conditions, such as temperature and transistor beta, change.



Effect of  $\beta$  variation on the response of the fixed-bias configuration of Fig. 4.7.

$\beta$	$I_B$ ( $\mu\text{A}$ )	$I_C$ (mA)	$V_{CE}$ (V)
50	47.08	2.35	6.83
100	47.08	4.71	1.64

 


Effect of  $\beta$  variation on the response of the emitter-bias configuration of Fig. 4.23.

$\beta$	$I_B$ ( $\mu\text{A}$ )	$I_C$ (mA)	$V_{CE}$ (V)
50	40.1	2.01	13.97
100	36.3	3.63	9.11
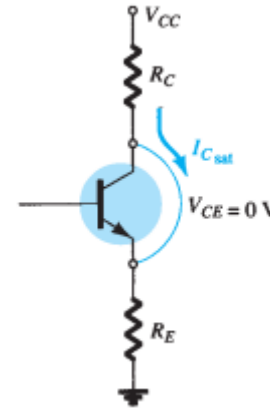
# Emitter-Bias Configuration (4 of 4)

- **Saturation Level**

$$I_{C_{sat}} = \frac{V_{CC}}{R_C + R_E}$$




- **Load-Line Analysis**


$$V_{CE} = V_{CC} - I_C(R_C + R_E)$$

$$V_{CE} = V_{CC} \Big|_{I_C = 0\text{ mA}}$$


$$I_C = \frac{V_{CC}}{R_C + R_E} \Big|_{V_{CE} = 0\text{ V}}$$

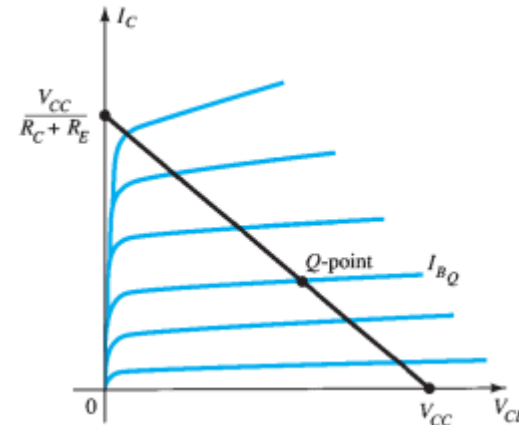

# Voltage-Divider Configuration (1 of 3)

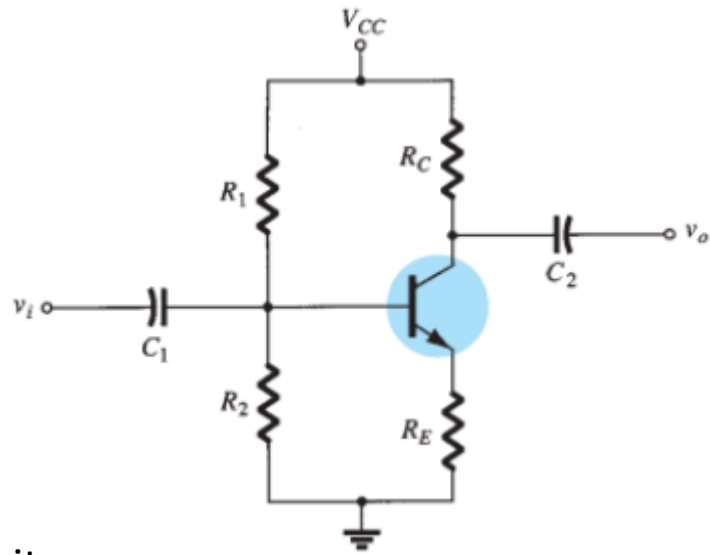

DC equivalent  $\rightarrow$

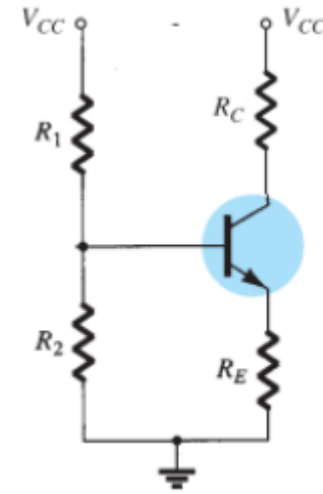


O/p Circuit


$$V_{CE} = V_{CC} - I_C(R_C + R_E)$$

I/p Circuit

Exact Analysis

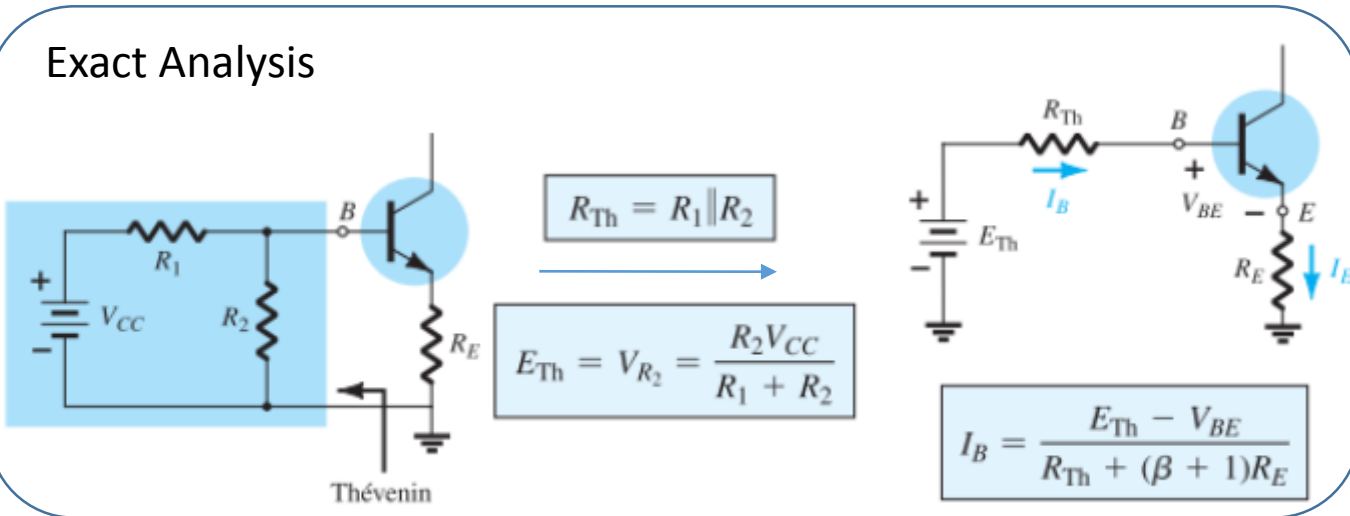

Approximate Analysis

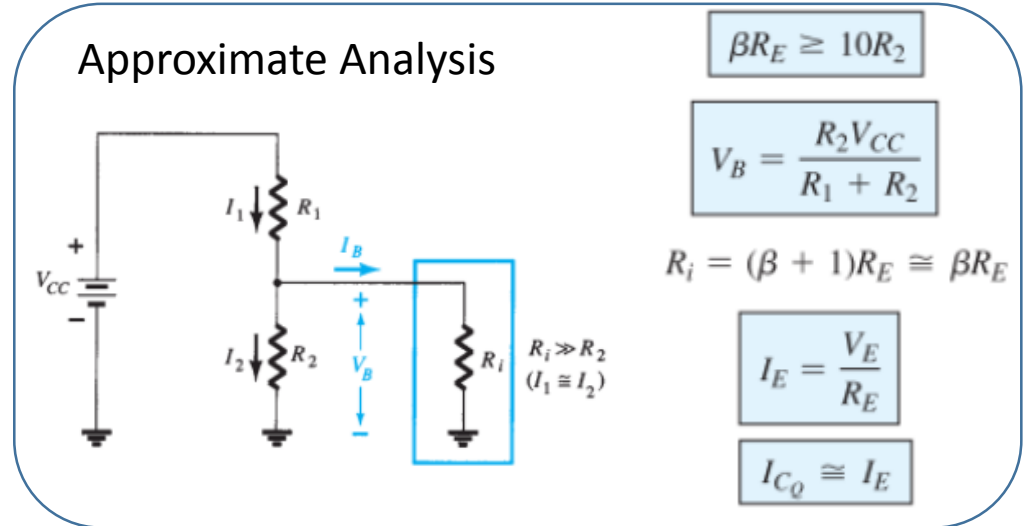

# Voltage-Divider Configuration (2 of 3)

**EXAMPLE 4.11** Determine the levels of  $I_{CQ}$  and  $V_{CEQ}$  for the voltage-divider configuration of Fig. 4.37 using the exact and approximate techniques and compare solutions. In this case, the conditions of Eq. (4.33) will not be satisfied and the results will reveal the difference in solution if the criterion of Eq. (4.33) is ignored.

**Solution:** Exact analysis:

Eq. (4.33):

$$\beta R_E \geq 10R_2$$

$$(50)(1.2 \text{ k}\Omega) \geq 10(22 \text{ k}\Omega)$$

$$60 \text{ k}\Omega \not\geq 220 \text{ k}\Omega \text{ (not satisfied)}$$


$$R_{Th} = R_1 \parallel R_2 = 82 \text{ k}\Omega \parallel 22 \text{ k}\Omega = 17.35 \text{ k}\Omega$$

$$E_{Th} = \frac{R_2 V_{CC}}{R_1 + R_2} = \frac{22 \text{ k}\Omega (18 \text{ V})}{82 \text{ k}\Omega + 22 \text{ k}\Omega} = 3.81 \text{ V}$$

$$I_B = \frac{E_{Th} - V_{BE}}{R_{Th} + (\beta + 1)R_E} = \frac{3.81 \text{ V} - 0.7 \text{ V}}{17.35 \text{ k}\Omega + (51)(1.2 \text{ k}\Omega)} = \frac{3.11 \text{ V}}{78.55 \text{ k}\Omega} = 39.6 \mu\text{A}$$

$$I_{CQ} = \beta I_B = (50)(39.6 \mu\text{A}) = \mathbf{1.98 \text{ mA}}$$
 
$$\begin{aligned} V_{CEQ} &= V_{CC} - I_C(R_C + R_E) \\ &= 18 \text{ V} - (1.98 \text{ mA})(5.6 \text{ k}\Omega + 1.2 \text{ k}\Omega) \\ &= \mathbf{4.54 \text{ V}} \end{aligned}$$



Approximate analysis:

$$V_B = E_{Th} = 3.81 \text{ V}$$

$$V_E = V_B - V_{BE} = 3.81 \text{ V} - 0.7 \text{ V} = 3.11 \text{ V}$$

$$I_{CQ} \cong I_E = \frac{V_E}{R_E} = \frac{3.11 \text{ V}}{1.2 \text{ k}\Omega} = \mathbf{2.59 \text{ mA}}$$

$$\begin{aligned} V_{CEQ} &= V_{CC} - I_C(R_C + R_E) \\ &= 18 \text{ V} - (2.59 \text{ mA})(5.6 \text{ k}\Omega + 1.2 \text{ k}\Omega) \\ &= \mathbf{3.88 \text{ V}} \end{aligned}$$

Comparing the exact and approximate approaches.

	$I_{CQ}$ (mA)	$V_{CEQ}$ (V)
Exact	1.98	4.54
Approximate	2.59	3.88


To ensure a close similarity between exact and approximate solutions.

$$\beta R_E \geq 10R_2$$
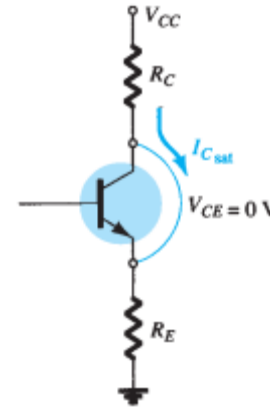
# Voltage-Divider Configuration (3 of 3)

- **Saturation Level**

$$I_{C_{sat}} = \frac{V_{CC}}{R_C + R_E}$$




- **Load-Line Analysis**

$$V_{CE} = V_{CC} - I_C(R_C + R_E)$$

$$V_{CE} = V_{CC} \Big|_{I_C=0\text{ mA}}$$


$$I_C = \frac{V_{CC}}{R_C + R_E} \Big|_{V_{CE}=0\text{ V}}$$

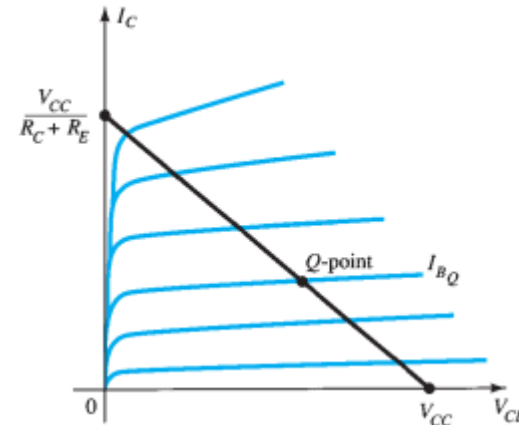




# Collector Feedback Configuration (1 of 3)


- DC bias circuit with voltage feedback.

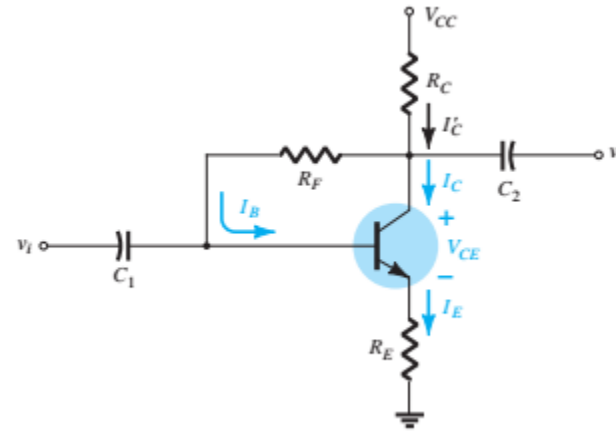

I/p Circuit

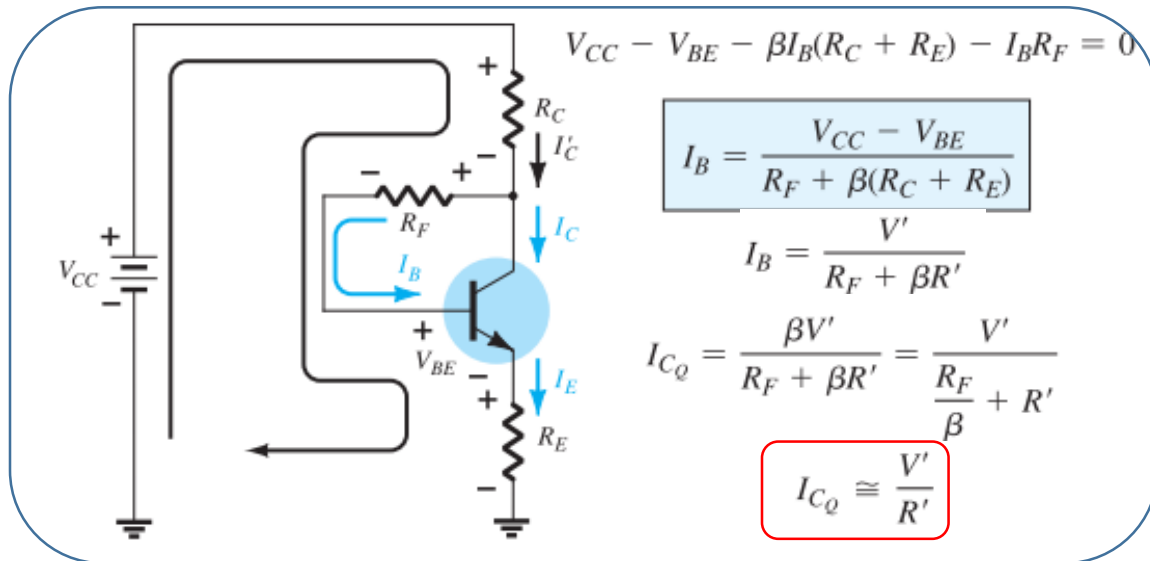


O/p Circuit

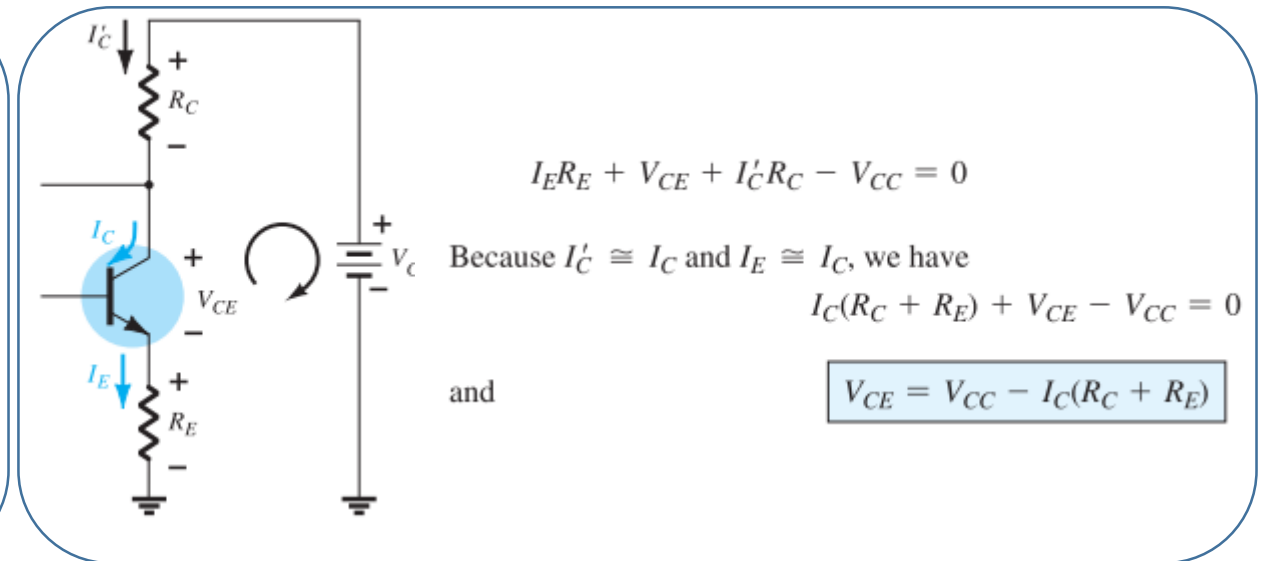

# Collector Feedback Configuration (2 of 3)

**EXAMPLE 4.14** Determine the dc level of  $I_B$  and  $V_C$  for the network of Fig. 4.42.

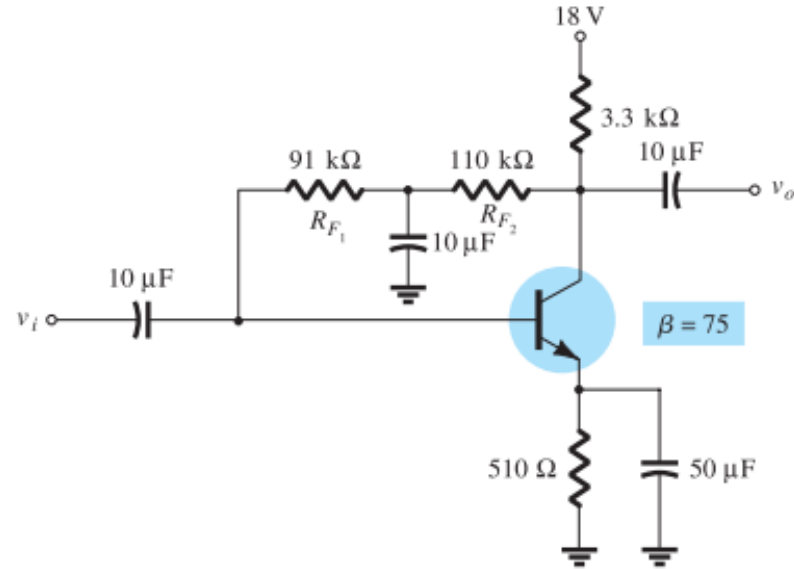

**FIG. 4.42**  
Network for Example 4.14.

**Solution:** In this case, the base resistance for the dc analysis is composed of two resistors with a capacitor connected from their junction to ground. For the dc mode, the capacitor assumes the open-circuit equivalence, and  $R_B = R_{F1} + R_{F2}$ .

Solving for  $I_B$  gives

$$\begin{aligned} I_B &= \frac{V_{CC} - V_{BE}}{R_B + \beta(R_C + R_E)} \\ &= \frac{18\ \text{V} - 0.7\ \text{V}}{(91\ \text{k}\Omega + 110\ \text{k}\Omega) + (75)(3.3\ \text{k}\Omega + 0.51\ \text{k}\Omega)} \\ &= \frac{17.3\ \text{V}}{201\ \text{k}\Omega + 285.75\ \text{k}\Omega} = \frac{17.3\ \text{V}}{486.75\ \text{k}\Omega} \\ &= \mathbf{35.5\ \mu\text{A}} \end{aligned}$$


$$\begin{aligned} I_C &= \beta I_B \\ &= (75)(35.5\ \mu\text{A}) \\ &= \mathbf{2.66\ \text{mA}} \end{aligned}$$

$$\begin{aligned} V_C &= V_{CC} - I_C' R_C \cong V_{CC} - I_C R_C \\ &= 18\ \text{V} - (2.66\ \text{mA})(3.3\ \text{k}\Omega) \\ &= 18\ \text{V} - 8.78\ \text{V} \\ &= \mathbf{9.22\ \text{V}} \end{aligned}$$
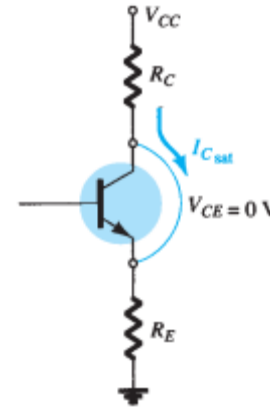
# Collector Feedback Configuration (3 of 3)

- **Saturation Level**

$$I_{C\text{sat}} = \frac{V_{CC}}{R_C + R_E}$$




- **Load-Line Analysis**

Continuing with the approximation  $I'_C = I_C$  results in the same load line defined for the voltage-divider and emitter-biased configurations.


$$V_{CE} = V_{CC} - I_C(R_C + R_E)$$

$$V_{CE} = V_{CC} |_{I_C=0\text{ mA}}$$

$$I_C = \frac{V_{CC}}{R_C + R_E} |_{V_{CE}=0\text{ V}}$$

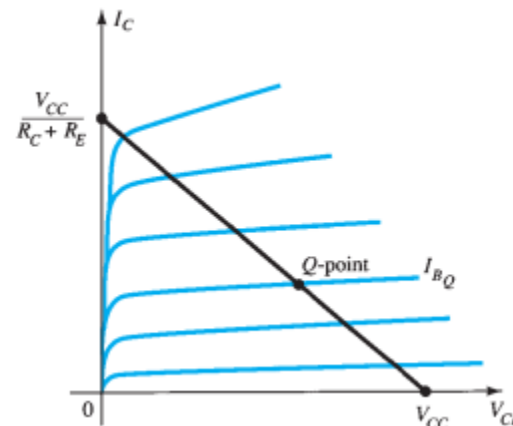
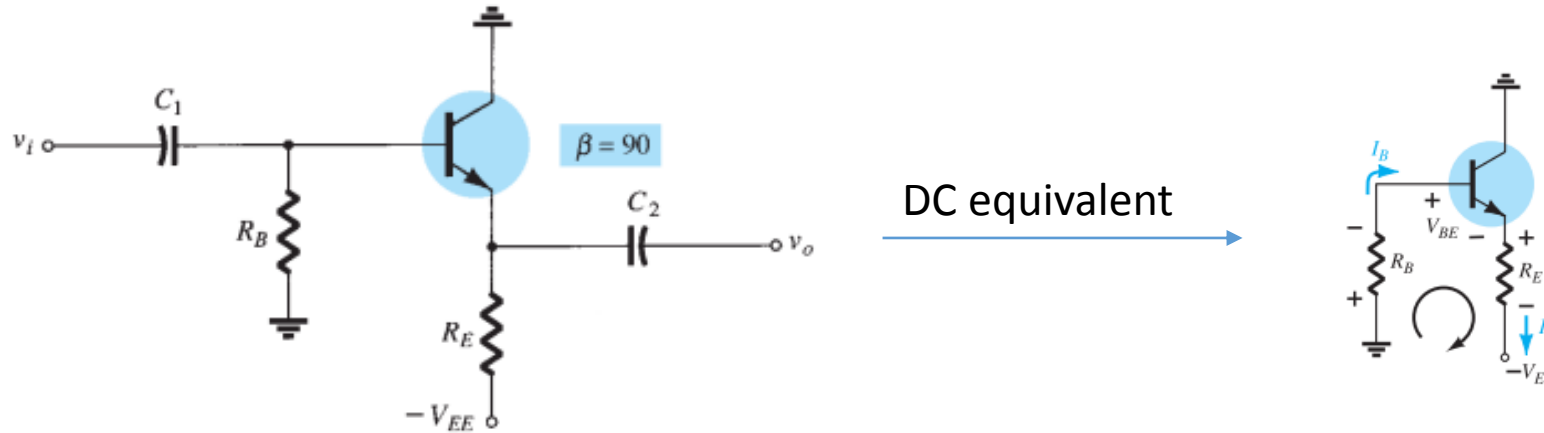
# Emitter-Follower Configuration (1 of 2)



I/p Circuit

$$-I_B R_B - V_{BE} - I_E R_E + V_{EE} = 0$$

$$I_B R_B + (\beta + 1) I_B R_E = V_{EE} - V_{BE}$$

$$I_B = \frac{V_{EE} - V_{BE}}{R_B + (\beta + 1) R_E}$$


O/p Circuit

$$-V_{CE} - I_E R_E + V_{EE} = 0$$

$$V_{CE} = V_{EE} - I_E R_E$$

# Emitter-Follower Configuration (2 of 2)

**EXAMPLE 4.16** Determine  $V_{CEQ}$  and  $I_{EQ}$  for the network of Fig. 4.48.

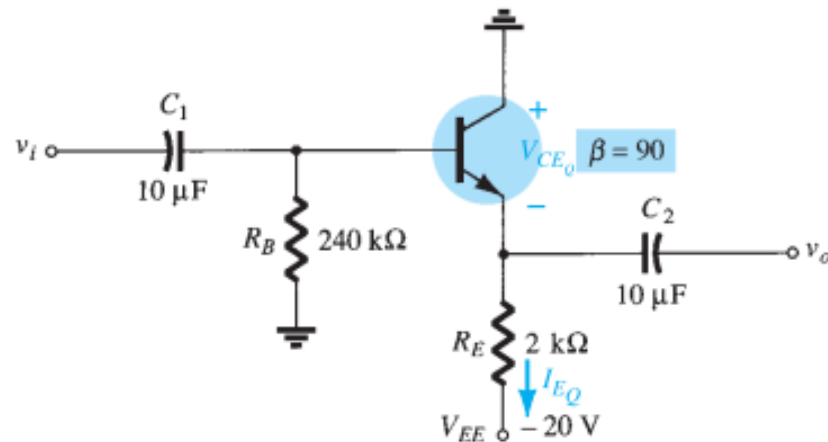

**FIG. 4.48**  
Example 4.16.

**Solution:**


Eq. 4.44:

$$\begin{aligned} I_B &= \frac{V_{EE} - V_{BE}}{R_B + (\beta + 1)R_E} \\ &= \frac{20 \text{ V} - 0.7 \text{ V}}{240 \text{ k}\Omega + (90 + 1)2 \text{ k}\Omega} = \frac{19.3 \text{ V}}{240 \text{ k}\Omega + 182 \text{ k}\Omega} \\ &= \frac{19.3 \text{ V}}{422 \text{ k}\Omega} = 45.73 \mu\text{A} \end{aligned}$$

and Eq. 4.45:



$$\begin{aligned} V_{CEQ} &= V_{EE} - I_E R_E \\ &= V_{EE} - (\beta + 1)I_B R_E \\ &= 20 \text{ V} - (90 + 1)(45.73 \mu\text{A})(2 \text{ k}\Omega) \\ &= 20 \text{ V} - 8.32 \text{ V} \\ &= \mathbf{11.68 \text{ V}} \\ I_{EQ} &= (\beta + 1)I_B = (91)(45.73 \mu\text{A}) \\ &= 4.16 \text{ mA} \end{aligned}$$

# Common-Base Configuration (1 of 2)

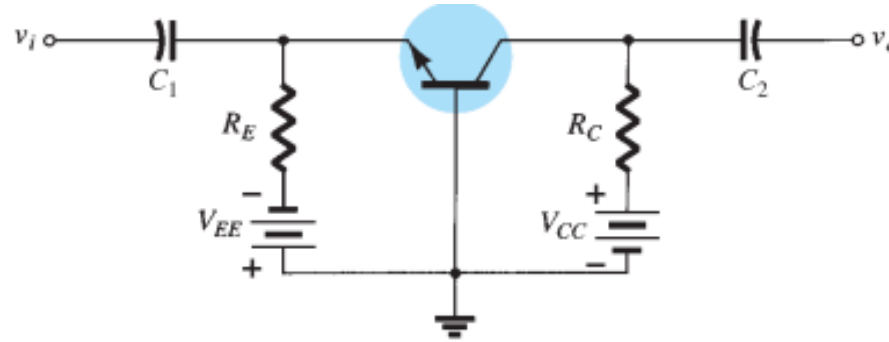


O/p Circuit

I/p Circuit

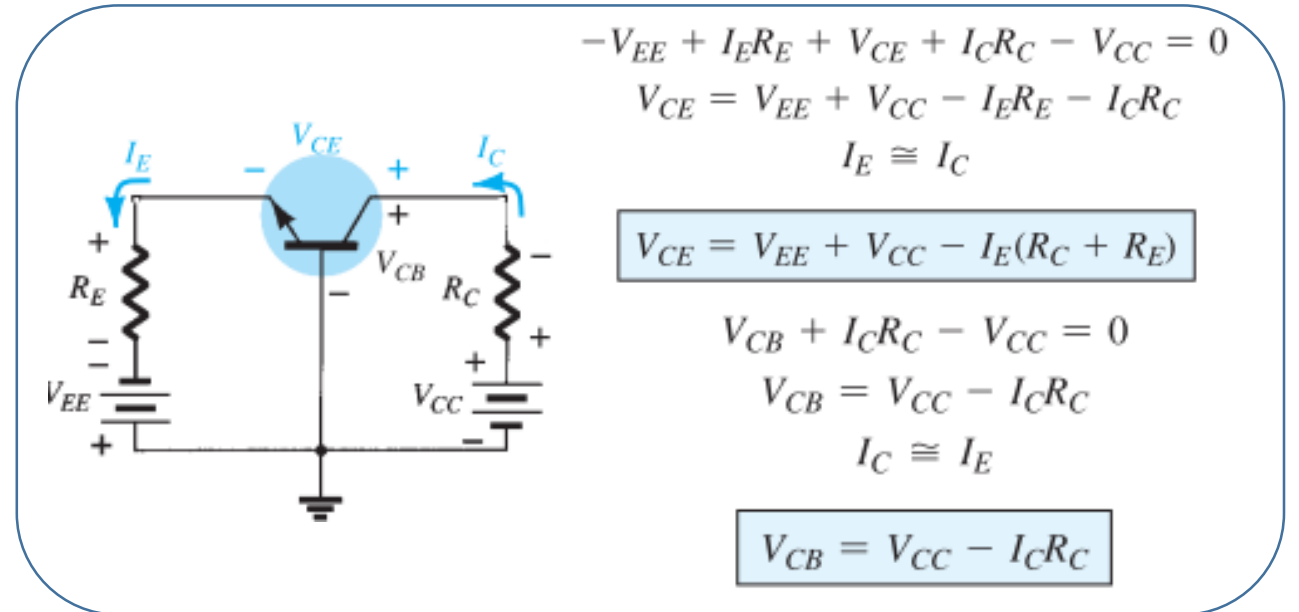 

# Common-Base Configuration (2 of 2)

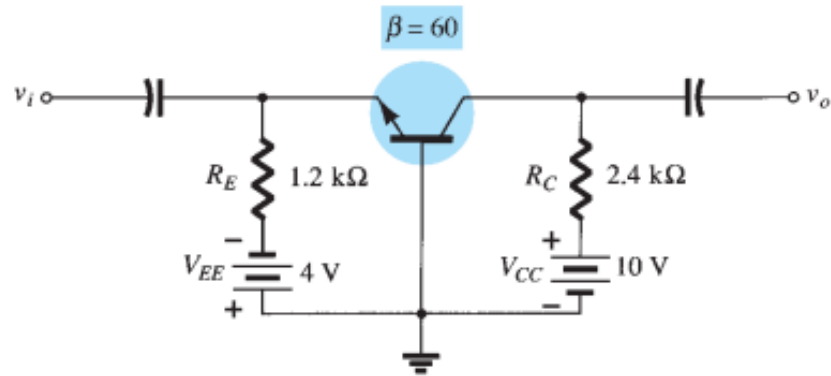**EXAMPLE 4.17** Determine the currents  $I_E$  and  $I_B$  and the voltages  $V_{CE}$  and  $V_{CB}$  for the common-base configuration of Fig. 4.52.



**Solution:** Eq. 4.46:

$$I_E = \frac{V_{EE} - V_{BE}}{R_E} \\ = \frac{4 \text{ V} - 0.7 \text{ V}}{1.2 \text{ k}\Omega} = \mathbf{2.75 \text{ mA}}$$

$$I_B = \frac{I_E}{\beta + 1} = \frac{2.75 \text{ mA}}{60 + 1} = \frac{2.75 \text{ mA}}{61} \\ = \mathbf{45.08 \mu\text{A}}$$

Eq. 4.47:

$$V_{CE} = V_{EE} + V_{CC} - I_E(R_C + R_E) \\ = 4 \text{ V} + 10 \text{ V} - (2.75 \text{ mA})(2.4 \text{ k}\Omega + 1.2 \text{ k}\Omega) \\ = 14 \text{ V} - (2.75 \text{ mA})(3.6 \text{ k}\Omega) \\ = 14 \text{ V} - 9.9 \text{ V} \\ = \mathbf{4.1 \text{ V}}$$


Eq. 4.48:

$$V_{CB} = V_{CC} - I_C R_C = V_{CC} - \beta I_B R_C \\ = 10 \text{ V} - (60)(45.08 \mu\text{A})(24 \text{ k}\Omega) \\ = 10 \text{ V} - 6.49 \text{ V} \\ = \mathbf{3.51 \text{ V}}$$

# Miscellaneous Bias Configurations (1 of 2)

 **EXAMPLE 4.18** For the network of Fig. 4.53:

- Determine  $I_{CQ}$  and  $V_{CEQ}$ .
- Find  $V_B$ ,  $V_C$ ,  $V_E$ , and  $V_{BC}$ .



**Solution:**

- The absence of  $R_E$  reduces the reflection of resistive levels to simply that of  $R_C$ , and the equation for  $I_B$  reduces to

$$\begin{aligned} I_B &= \frac{V_{CC} - V_{BE}}{R_B + \beta R_C} \\ &= \frac{20 \text{ V} - 0.7 \text{ V}}{680 \text{ k}\Omega + (120)(4.7 \text{ k}\Omega)} = \frac{19.3 \text{ V}}{1.244 \text{ M}\Omega} \\ &= \mathbf{15.51 \mu A} \end{aligned}$$

$$\begin{aligned} I_{CQ} &= \beta I_B = (120)(15.51 \mu A) \\ &= \mathbf{1.86 \text{ mA}} \end{aligned}$$

$$\begin{aligned} V_{CEQ} &= V_{CC} - I_C R_C \\ &= 20 \text{ V} - (1.86 \text{ mA})(4.7 \text{ k}\Omega) \\ &= \mathbf{11.26 \text{ V}} \end{aligned}$$

b.

$$V_B = V_{BE} = \mathbf{0.7 \text{ V}}$$

$$V_C = V_{CE} = \mathbf{11.26 \text{ V}}$$


$$V_E = \mathbf{0 \text{ V}}$$

$$\begin{aligned} V_{BC} &= V_B - V_C = 0.7 \text{ V} - 11.26 \text{ V} \\ &= \mathbf{-10.56 \text{ V}} \end{aligned}$$



# Miscellaneous Bias Configurations (2 of 2)

 **EXAMPLE 4.19** Determine  $V_C$  and  $V_B$  for the network of Fig. 4.54.



**Solution:** Applying Kirchhoff's voltage law in the clockwise direction for the base-emitter loop results in

$$-I_B R_B - V_{BE} + V_{EE} = 0$$

and

$$I_B = \frac{V_{EE} - V_{BE}}{R_B}$$

Substitution yields

$$\begin{aligned} I_B &= \frac{9 \text{ V} - 0.7 \text{ V}}{100 \text{ k}\Omega} \\ &= \frac{8.3 \text{ V}}{100 \text{ k}\Omega} \\ &= 83 \mu\text{A} \end{aligned}$$




$$\begin{aligned} I_C &= \beta I_B \\ &= (45)(83 \mu\text{A}) \\ &= 3.735 \text{ mA} \end{aligned}$$

$$\begin{aligned} V_C &= -I_C R_C \\ &= -(3.735 \text{ mA})(1.2 \text{ k}\Omega) \\ &= -4.48 \text{ V} \end{aligned}$$




$$\begin{aligned} V_B &= -I_B R_B \\ &= -(83 \mu\text{A})(100 \text{ k}\Omega) \\ &= -8.3 \text{ V} \end{aligned}$$

# Summary Table

BJT Bias Configurations

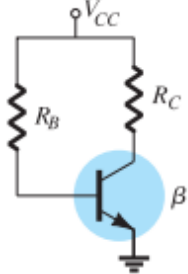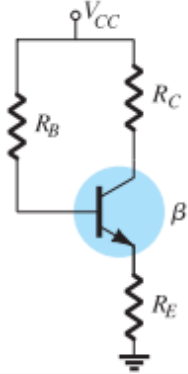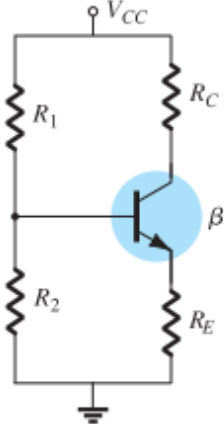Type	Configuration	Pertinent Equations
Fixed-bias		$I_B = \frac{V_{CC} - V_{BE}}{R_B}$ $I_C = \beta I_B, I_E = (\beta + 1)I_B$ $V_{CE} = V_{CC} - I_C R_C$
Emitter-bias		$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_E}$ $I_C = \beta I_B, I_E = (\beta + 1)I_B$ $R_i = (\beta + 1)R_E$ $V_{CE} = V_{CC} - I_C (R_C + R_E)$
Voltage-divider bias		<p>EXACT: <math>R_{Th} = R_1    R_2, E_{Th} = \frac{R_2 V_{CC}}{R_1 + R_2}</math></p> $I_B = \frac{E_{Th} - V_{BE}}{R_{Th} + (\beta + 1)R_E}$ $I_C = \beta I_B, I_E = (\beta + 1)I_B$ $V_{CE} = V_{CC} - I_C (R_C + R_E)$ <p>APPROXIMATE: <math>\beta R_E \geq 10R_2</math></p> $V_B = \frac{R_2 V_{CC}}{R_1 + R_2}, V_E = V_B - V_{BE}$ $I_E = \frac{V_E}{R_E}, I_B = \frac{I_E}{\beta + 1}$ $V_{CE} = V_{CC} - I_C (R_C + R_E)$

# Summary Table..

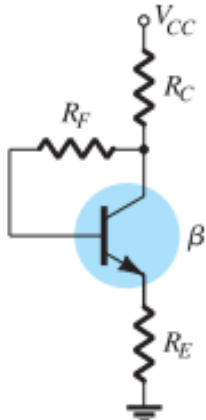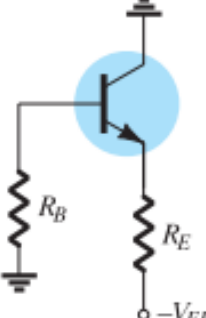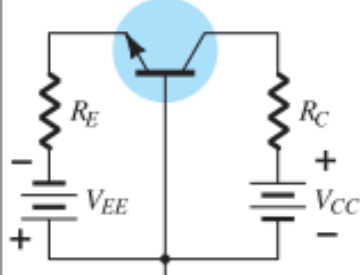Collector-feedback		$I_B = \frac{V_{CC} - V_{BE}}{R_F + \beta(R_C + R_E)}$ $I_C = \beta I_B, I_E = (\beta + 1)I_B$ $V_{CE} = V_{CC} - I_C(R_C + R_E)$
Emitter-follower		$I_B = \frac{V_{EE} - V_{BE}}{R_B + (\beta + 1)R_E}$ $I_C = \beta I_B, I_E = (\beta + 1)I_B$ $V_{CE} = V_{EE} - I_E R_E$
Common-base		$I_E = \frac{V_{EE} - V_{BE}}{R_E}$ $I_B = \frac{I_E}{\beta + 1}, I_C = \beta I_B$ $V_{CE} = V_{EE} + V_{CC} - I_E(R_C + R_E)$ $V_{CB} = V_{CC} - I_C R_C$



# Design Operation

# Design Operations

- Discussions thus far have focused on the analysis of existing networks. All the elements are in place, and it is simply a matter of solving for the current and voltage levels of the configuration.
- The design process is one where a current and/or voltage may be specified and the elements required to establish the designated levels must be determined.
- The design sequence is obviously sensitive to the components that are already specified and the elements to be determined. If the transistor and supplies are specified, the design process will simply determine the required resistors for a particular design.
- Once the theoretical values of the resistors are determined, the nearest standard commercial values are normally chosen and any variations due to not using the exact resistance values are accepted as part of the design.

# Design Operations Example 1

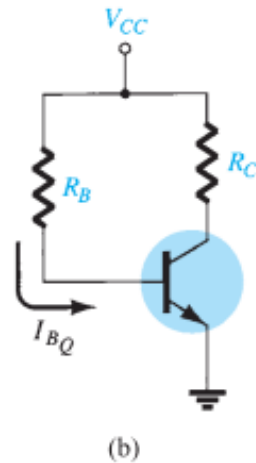 **EXAMPLE 4.21** Given the device characteristics of Fig. 4.59a, determine  $V_{CC}$ ,  $R_B$ , and  $R_C$  for the fixed-bias configuration of Fig. 4.59b.



**Solution:** From the load line

$$V_{CC} = 20 \text{ V}$$

$$I_C = \frac{V_{CC}}{R_C} \Big|_{V_{CE}=0 \text{ V}}$$

$$R_C = \frac{V_{CC}}{I_C} = \frac{20 \text{ V}}{8 \text{ mA}} = 2.5 \text{ k}\Omega$$

and

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

with

$$\begin{aligned} R_B &= \frac{V_{CC} - V_{BE}}{I_B} \\ &= \frac{20 \text{ V} - 0.7 \text{ V}}{40 \mu\text{A}} = \frac{19.3 \text{ V}}{40 \mu\text{A}} \\ &= 482.5 \text{ k}\Omega \end{aligned}$$

Standard resistor values are

$$R_C = 2.4 \text{ k}\Omega$$

$$R_B = 470 \text{ k}\Omega$$

Using standard resistor values gives

$$I_B = 41.1 \mu\text{A}$$


which is well within 5% of the value specified.

# Design Operations Example 2

- Design of a Current-Gain-Stabilized (Beta-Independent) Circuit

**EXAMPLE 4.25** Determine the levels of  $R_C$ ,  $R_E$ ,  $R_1$ , and  $R_2$  for the network of Fig. 4.63 for the operating point indicated.

**Solution:**

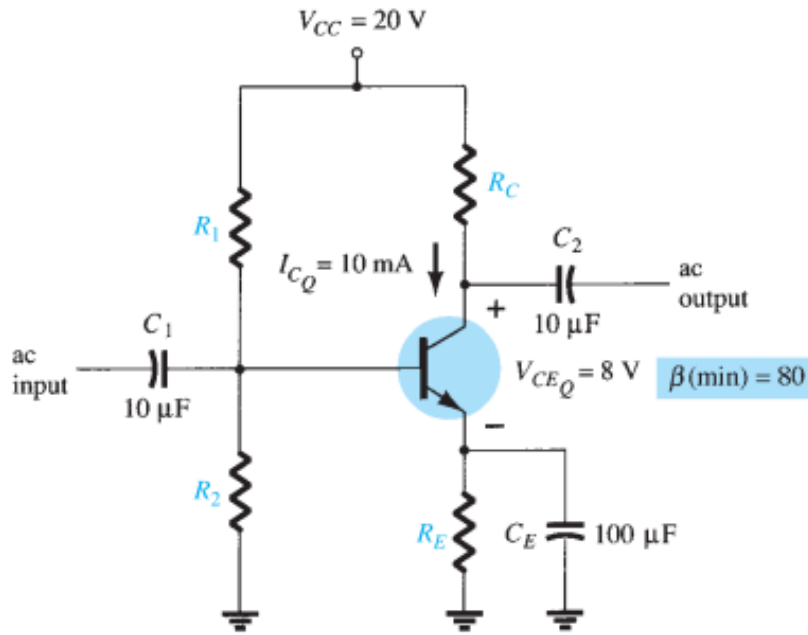

**FIG. 4.63**

*Current-gain-stabilized circuit for design considerations.*

$$V_E = \frac{1}{10}V_{CC} = \frac{1}{10}(20 \text{ V}) = 2 \text{ V}$$

$$R_E = \frac{V_E}{I_E} \cong \frac{V_E}{I_C} = \frac{2 \text{ V}}{10 \text{ mA}} = \mathbf{200 \Omega}$$

$$R_C = \frac{V_{R_C}}{I_C} = \frac{V_{CC} - V_{CE} - V_E}{I_C} = \frac{20 \text{ V} - 8 \text{ V} - 2 \text{ V}}{10 \text{ mA}} = \frac{10 \text{ V}}{10 \text{ mA}} = \mathbf{1 \text{ k}\Omega}$$

$$V_B = V_{BE} + V_E = 0.7 \text{ V} + 2 \text{ V} = 2.7 \text{ V}$$

$$R_2 \leq \frac{1}{10}\beta R_E$$

$$V_B = \frac{R_2}{R_1 + R_2}V_{CC}$$

and

Substitution yields

$$R_2 \leq \frac{1}{10}(80)(0.2 \text{ k}\Omega) = \mathbf{1.6 \text{ k}\Omega}$$

$$V_B = 2.7 \text{ V} = \frac{(1.6 \text{ k}\Omega)(20 \text{ V})}{R_1 + 1.6 \text{ k}\Omega}$$

$$2.7R_1 + 4.32 \text{ k}\Omega = 32 \text{ k}\Omega$$

$$2.7R_1 = 27.68 \text{ k}\Omega$$

$$R_1 = \mathbf{10.25 \text{ k}\Omega} \quad (\text{use } 10 \text{ k}\Omega)$$

Thank You!

