

ECE 121

Electronics (1)


Lec. 3: BJT Circuits & Troubleshooting

Instructor

Dr. Maher Abdelrasoul

<http://www.bu.edu.eg/staff/mahersalem3>

Outline

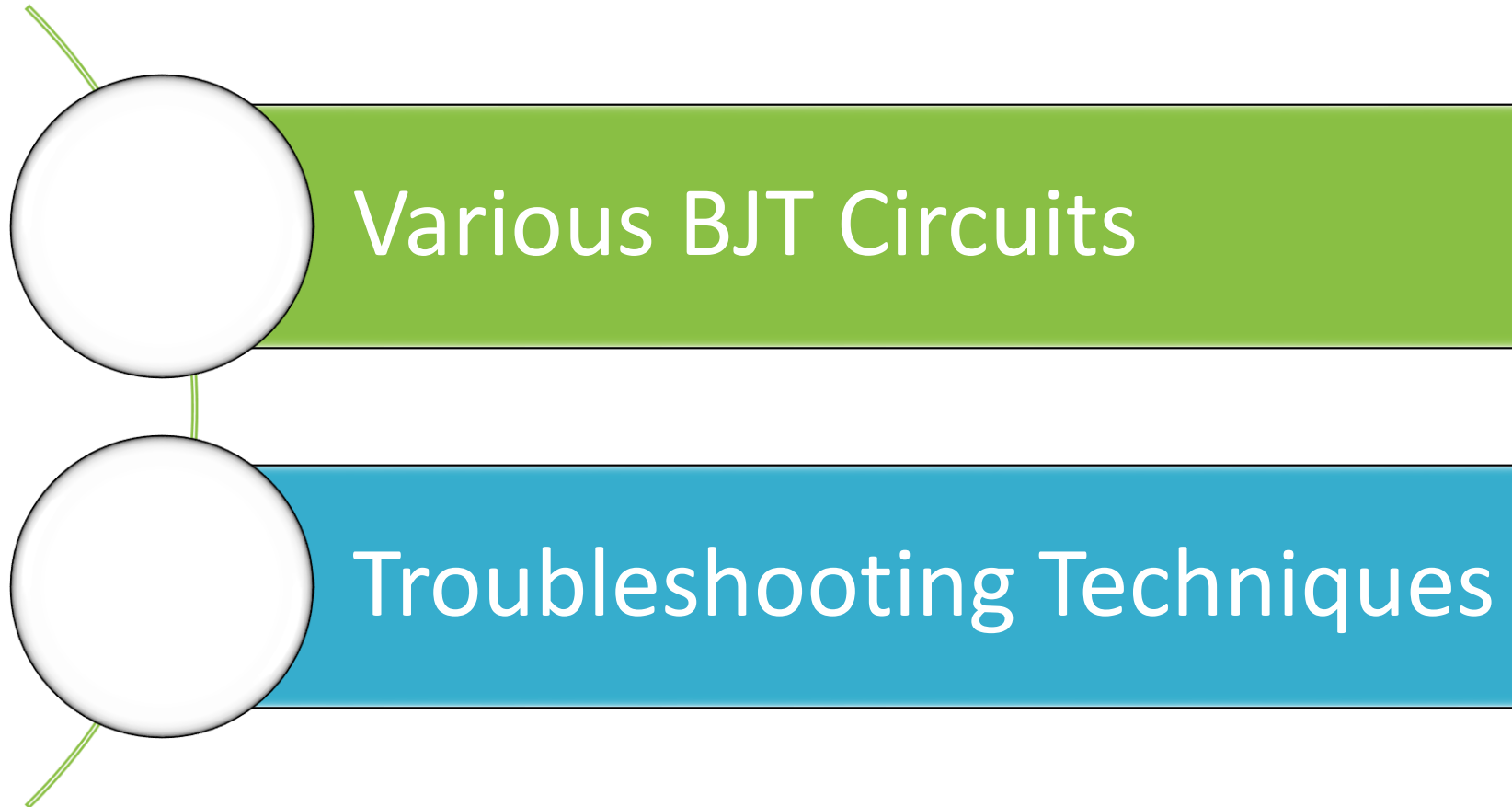

Various BJT Circuits

- MULTIPLE BJT NETWORKS
- CURRENT MIRRORS
- CURRENT SOURCE CIRCUITS
 - Bipolar Transistor Constant-Current Source
 - Transistor/Zener Constant-Current Source
- PNP TRANSISTORS
- TRANSISTOR SWITCHING NETWORKS

Multiple BJT Networks (1 of 6)

- R-C coupling

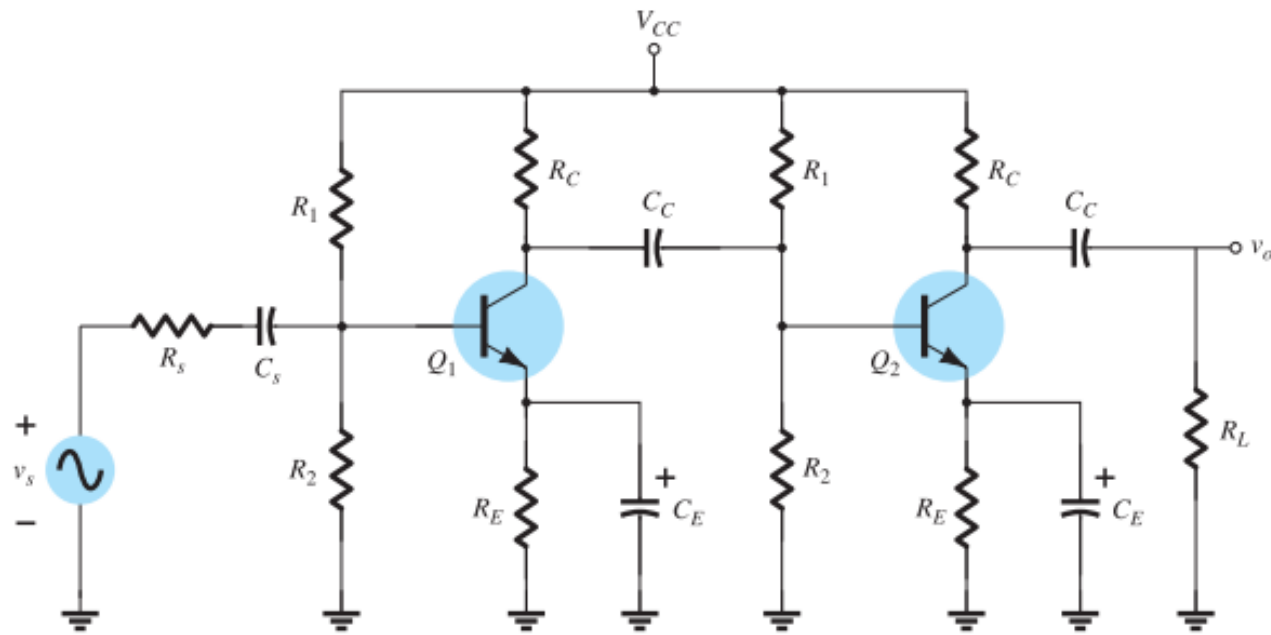


FIG. 4.64
R-C coupled BJT amplifiers.

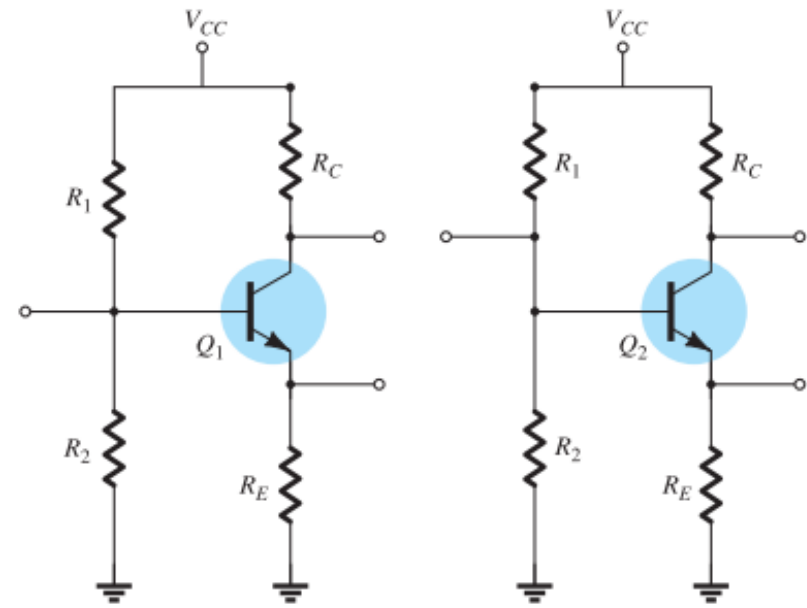


FIG. 4.65
DC equivalent of Fig. 4.64.

Multiple BJT Networks (2 of 6)

- Darlington configuration

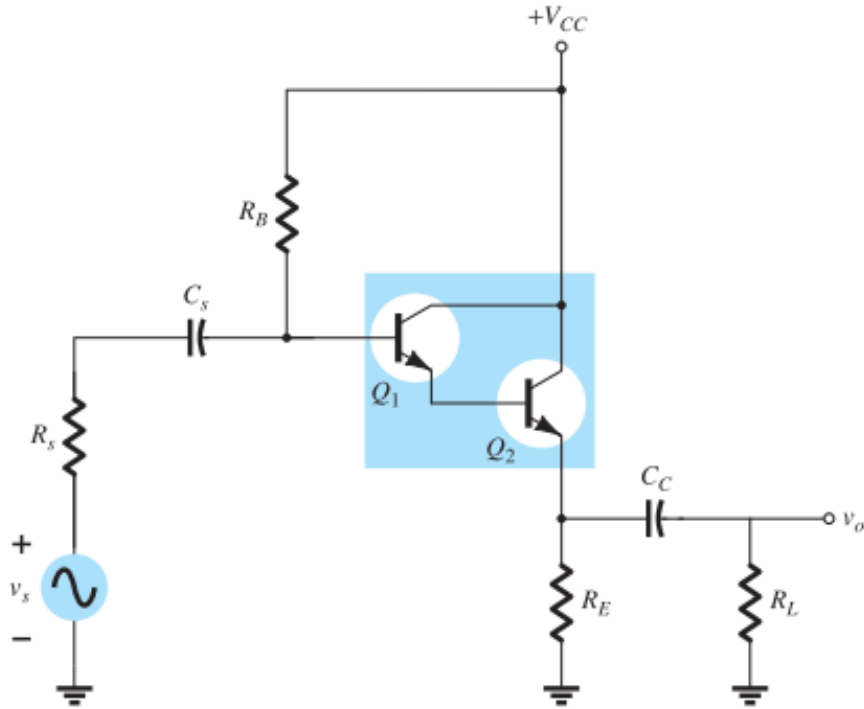


FIG. 4.66
Darlington amplifier.

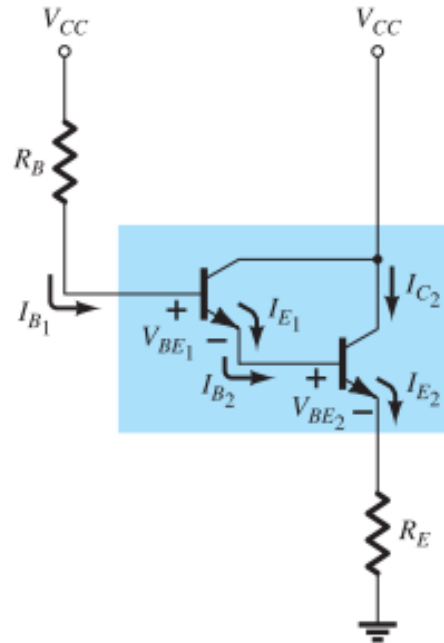


FIG. 4.67
DC equivalent of Fig. 4.66.

$$I_{B1} = \frac{V_{CC} - V_{BE1} - V_{BE2}}{R_B + (\beta_D + 1)R_E}$$

$$V_{BE_D} = V_{BE1} + V_{BE2}$$

$$I_{B1} = \frac{V_{CC} - V_{BE_D}}{R_B + (\beta_D + 1)R_E}$$

$$I_{C2} \cong I_{E2} = \beta_D I_{B1}$$

$$\beta_D = \beta_1 \beta_2$$

$$V_{E2} = I_{E2} R_E$$

$$V_{C2} = V_{CC}$$

$$V_{CE2} = V_{C2} - V_{E2}$$

$$V_{CE2} = V_{CC} - V_{E2}$$

Multiple BJT Networks (3 of 6)

- Cascode configuration

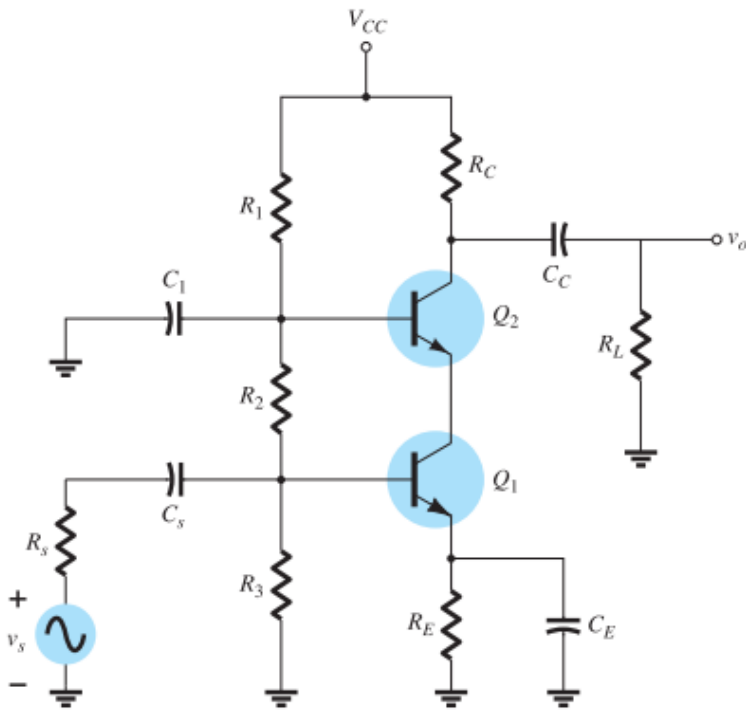


FIG. 4.68
Cascode amplifier.

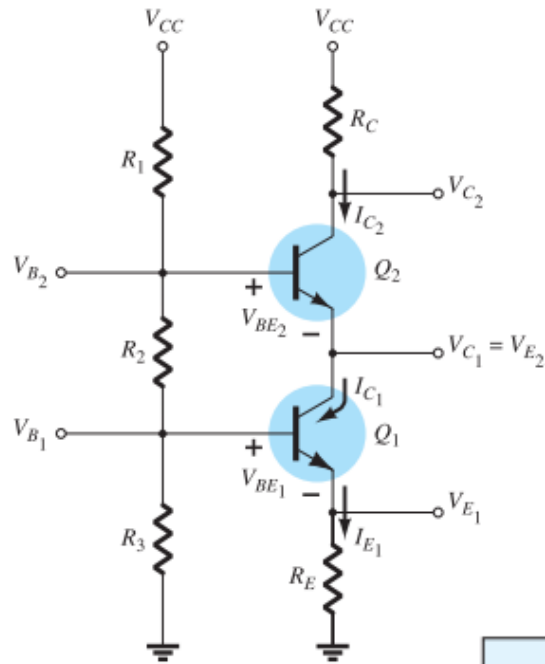


FIG. 4.69
DC equivalent of Fig. 4.68.

$$I_{R_1} \cong I_{R_2} \cong I_{R_3} \gg I_{B_1} \text{ or } I_{B_2}$$

$$V_{B_1} = \frac{R_3}{R_1 + R_2 + R_3} V_{CC}$$

$$V_{B_2} = \frac{(R_2 + R_3)}{R_1 + R_2 + R_3} V_{CC}$$

$$V_{E_1} = V_{B_1} - V_{BE_1}$$

$$V_{E_2} = V_{B_2} - V_{BE_2}$$

$$I_{C_2} \cong I_{E_2} \cong I_{C_1} \cong I_{E_1} = \frac{V_{B_1} - V_{BE_1}}{R_{E_1} + R_{E_2}}$$

$$V_{C_1} = V_{B_2} - V_{BE_2}$$

$$V_{C_2} = V_{CC} - I_{C_2} R_C$$

$$I_{R_1} \cong I_{R_2} \cong I_{R_3} = \frac{V_{CC}}{R_1 + R_2 + R_3}$$

$$I_{B_2} = \frac{I_{C_2}}{\beta_2}$$

$$I_{B_1} = \frac{I_{C_1}}{\beta_1}$$

R_E

Multiple BJT Networks (4 of 6)

- Feedback Pair

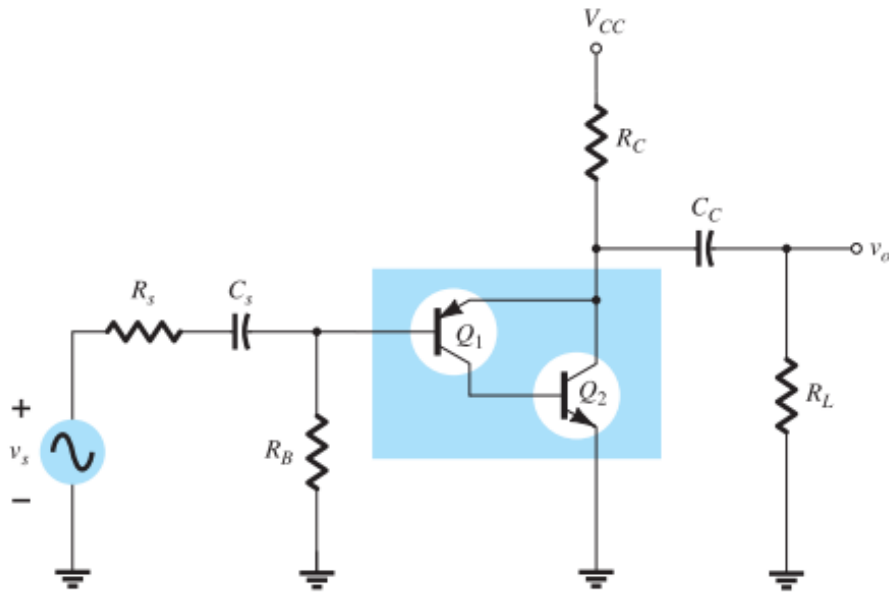


FIG. 4.70
Feedback Pair amplifier.

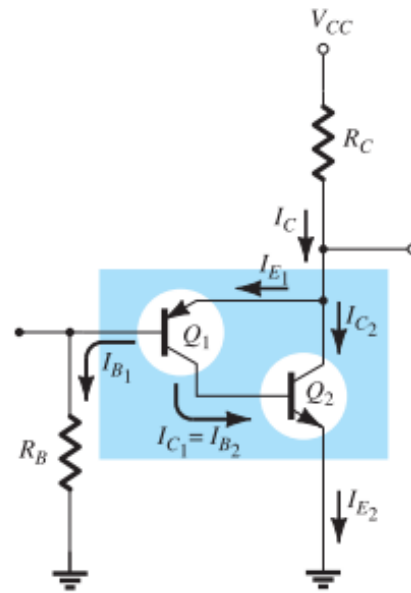


FIG. 4.71
DC equivalent of Fig. 4.70.

$$I_{B_2} = I_{C_1} = \beta_1 I_{B_1}$$

$$I_{C_2} = \beta_2 I_{B_2}$$

$$I_{C_2} \cong I_{E_2} = \beta_1 \beta_2 I_{B_1}$$

$$I_C = I_{E_1} + I_{E_2}$$

$$\cong \beta_1 I_{B_1} + \beta_1 \beta_2 I_{B_1}$$

$$= \beta_1 (1 + \beta_2) I_{B_1}$$

$$I_C \cong \beta_1 \beta_2 I_{B_1}$$

$$V_{CC} - I_C R_C - V_{EB_1} - I_{B_1} R_B = 0$$

$$V_{CC} - V_{EB_1} - \beta_1 \beta_2 I_{B_1} R_C - I_{B_1} R_B = 0$$

$$I_{B_1} = \frac{V_{CC} - V_{EB_1}}{R_B + \beta_1 \beta_2 R_C}$$

$$V_{B_1} = I_{B_1} R_B$$

$$V_{B_2} = V_{BE_2}$$

$$V_{C_2} = V_{CC} - I_C R_C$$

$$V_{C_1} = V_{BE_2}$$

$$V_{CE_2} = V_{C_2}$$

$$V_{EC_1} = V_{E_1} - V_{C_1}$$

$$V_{EC_1} = V_{C_2} - V_{BE_2}$$

Multiple BJT Networks (5 of 6)

- Direct Coupled

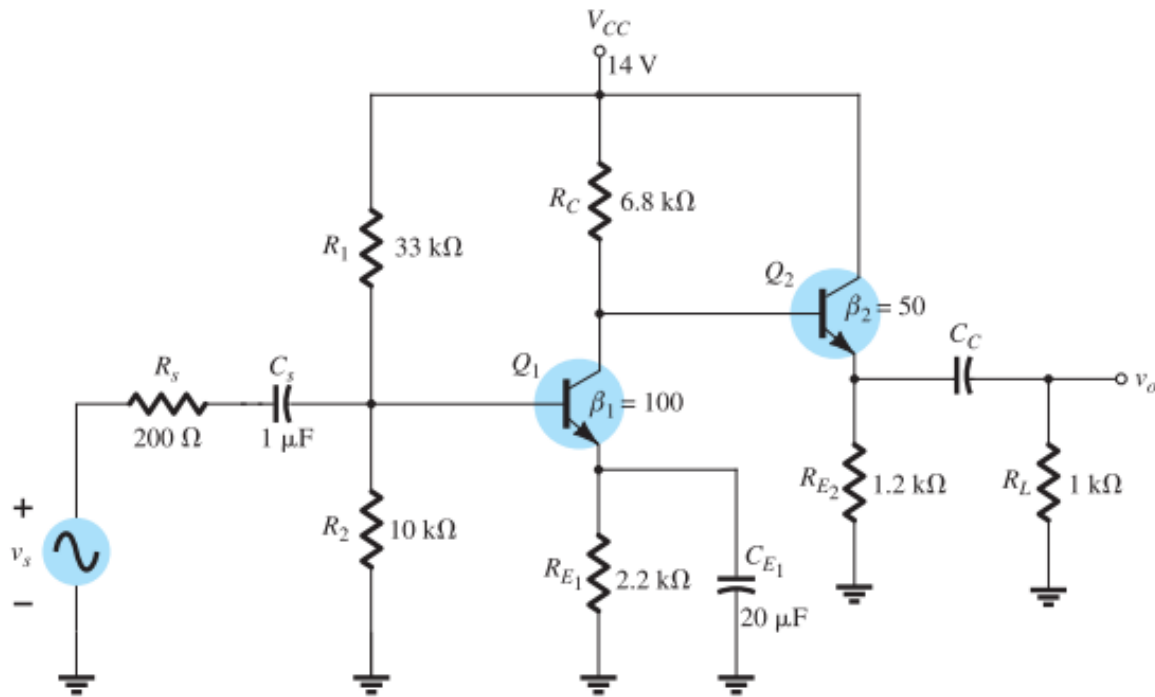


FIG. 4.72
Direct-coupled amplifier.

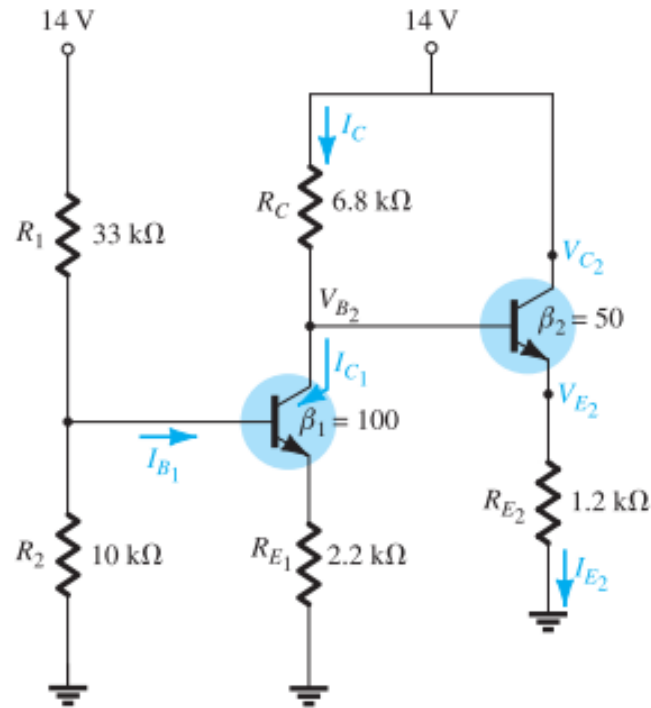


FIG. 4.73
DC equivalent of Fig. 4.72.

$$I_{B1} = \frac{E_{Th} - V_{BE}}{R_{Th} + (\beta + 1)R_{E1}}$$

$$R_{Th} = R_1 \parallel R_2$$

$$E_{Th} = \frac{R_2 V_{CC}}{R_1 + R_2}$$

$$V_{B2} = V_{CC} - I_C R_C$$

$$V_{E2} = V_{B2} - V_{BE2}$$

$$I_{E2} = \frac{V_{E2}}{R_{E2}}$$

$$V_{C2} = V_{CC}$$

$$V_{CE2} = V_{C2} - V_{E2}$$

$$V_{CE2} = V_{CC} - V_{E2}$$

Multiple BJT Networks (6 of 6)

In this case,

$$R_{Th} = 33 \text{ k}\Omega \parallel 10 \text{ k}\Omega = 7.67 \text{ k}\Omega$$

and

$$E_{Th} = \frac{10 \text{ k}\Omega(14 \text{ V})}{10 \text{ k}\Omega + 33 \text{ k}\Omega} = 3.26 \text{ V}$$

so that

$$\begin{aligned} I_{B_1} &= \frac{3.26 \text{ V} - 0.7 \text{ V}}{7.67 \text{ k}\Omega + (100 + 1) 2.2 \text{ k}\Omega} \\ &= \frac{2.56 \text{ V}}{229.2 \text{ k}\Omega} \\ &= \mathbf{11.17 \mu A} \end{aligned}$$

with

$$\begin{aligned} I_{C_1} &= \beta I_{B_1} \\ &= 100 (11.17 \mu A) \\ &= \mathbf{1.12 \text{ mA}} \end{aligned}$$

In Fig. 4.73 we find that

$$\begin{aligned} V_{B_2} &= V_{CC} - I_{C_1} R_C \\ &= 14 \text{ V} - (1.12 \text{ mA})(6.8 \text{ k}\Omega) \\ &= 14 \text{ V} - 7.62 \text{ V} \\ &= \mathbf{6.38 \text{ V}} \end{aligned}$$

and

$$\begin{aligned} V_{E_2} &= V_{B_2} - V_{BE_2} \\ &= 6.38 \text{ V} - 0.7 \text{ V} \\ &= \mathbf{5.68 \text{ V}} \end{aligned}$$

resulting in

$$\begin{aligned} I_{E_2} &= \frac{V_{E_2}}{R_{E_2}} \\ &= \frac{5.68 \text{ V}}{1.2 \text{ k}\Omega} \\ &= \mathbf{4.73 \text{ mA}} \end{aligned}$$

Obviously,

$$\begin{aligned} V_{C_2} &= V_{CC} \\ &= \mathbf{14 \text{ V}} \end{aligned}$$

and

$$\begin{aligned} V_{CE_2} &= V_{C_2} - V_{E_2} \\ V_{CE_2} &= V_{CC} - V_{E_2} \\ &= 14 \text{ V} - 5.68 \text{ V} \\ &= \mathbf{8.32 \text{ V}} \end{aligned}$$

Current Mirrors (1 of 2)

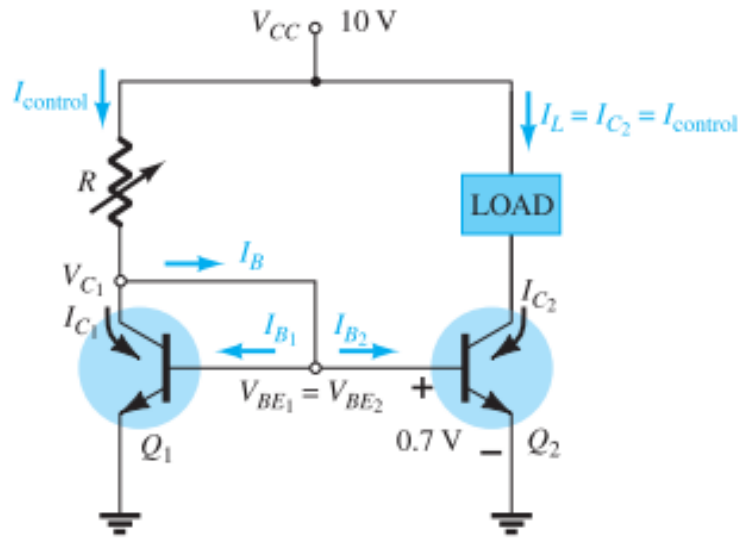


FIG. 4.74

Current mirror using back-to-back BJTs.

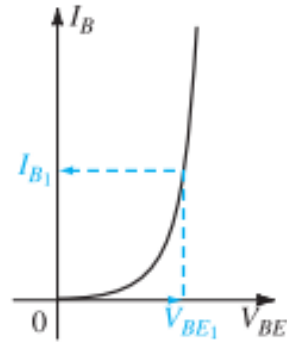


FIG. 4.75

Base characteristics for transistor Q_1 (and Q_2).

$$I_{\text{control}} = \frac{V_{CC} - V_{BE}}{R}$$

$$I_{\text{control}} = I_{C_1} + I_B = I_{C_1} + 2I_{B_1}$$

$$I_{C_1} = \beta_1 I_{B_1}$$

$$I_{\text{control}} = \beta_1 I_{B_1} + 2I_{B_1} = (\beta_1 + 2)I_{B_1}$$

β_1 is typically $\gg 2$, $I_{\text{control}} \cong \beta_1 I_{B_1}$

$$I_{B_1} = \frac{I_{\text{control}}}{\beta_1}$$

$$I_L = I_{C_2} = \beta I_{B_2}$$

$I_L \uparrow, I_{C_2} \uparrow, I_{B_2} \uparrow, V_{BE_2} \uparrow, V_{CE_1} \uparrow, I_R \downarrow, I_B \downarrow, I_{B_1} \downarrow, I_{C_1} \downarrow, I_L \downarrow$
 Note

Current Mirrors (2 of 2)

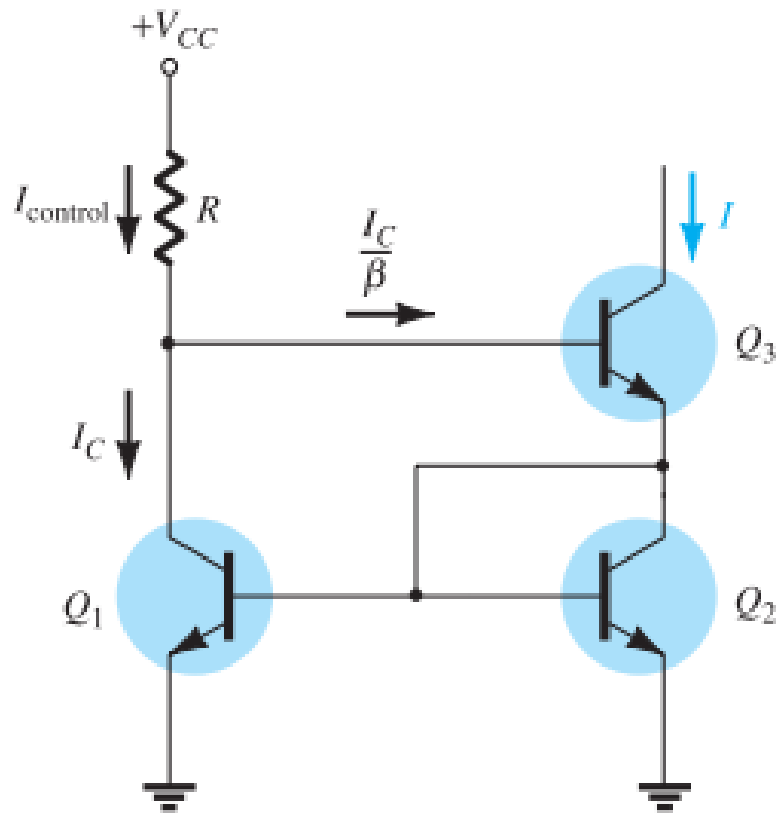



FIG. 4.78

Current mirror circuit with higher output impedance.

$$I_{\text{control}} = \frac{V_{CC} - 2V_{BE}}{R} \approx I_C + \frac{I_C}{\beta} = \frac{\beta + 1}{\beta} I_C \approx I_C$$

$$I \approx I_C = I_{\text{control}}$$

Current Source Circuits (1 of 2)

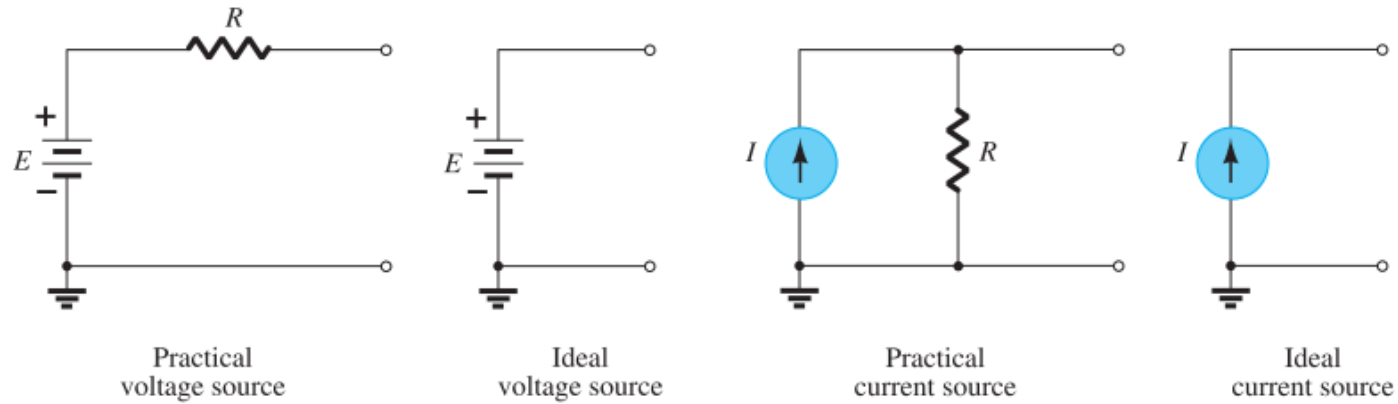

Bipolar Transistor Constant-Current Source

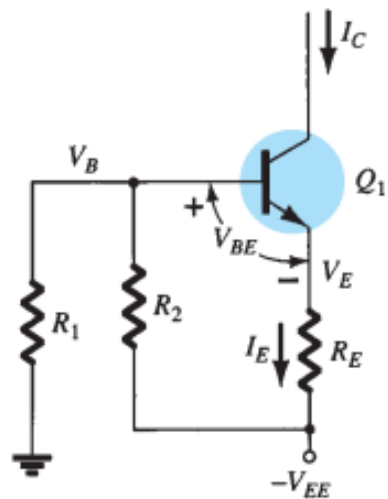


FIG. 4.81

Discrete constant-current source.

$$V_B = \frac{R_1}{R_1 + R_2} (-V_{EE})$$

$$V_E = V_B - 0.7 \text{ V}$$

$$I_E = \frac{V_E - (-V_{EE})}{R_E} \approx I_C$$

Transistor/Zener Constant-Current Source

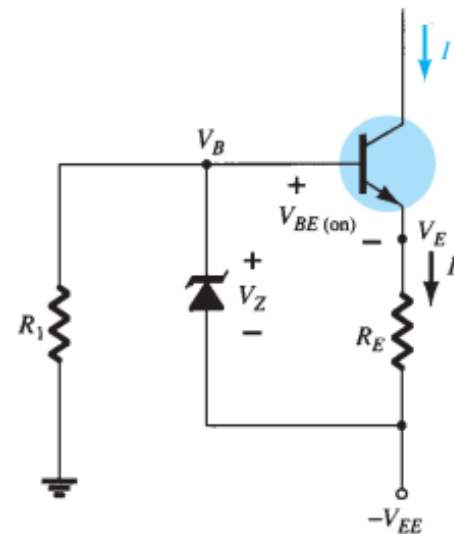


FIG. 4.83

Constant-current circuit using Zener diode.

$$I \approx I_E = \frac{V_Z - V_{BE}}{R_E}$$

Current Source Circuits (2 of 2)

EXAMPLE 4.30 Calculate the constant current I in the circuit of Fig. 4.84.

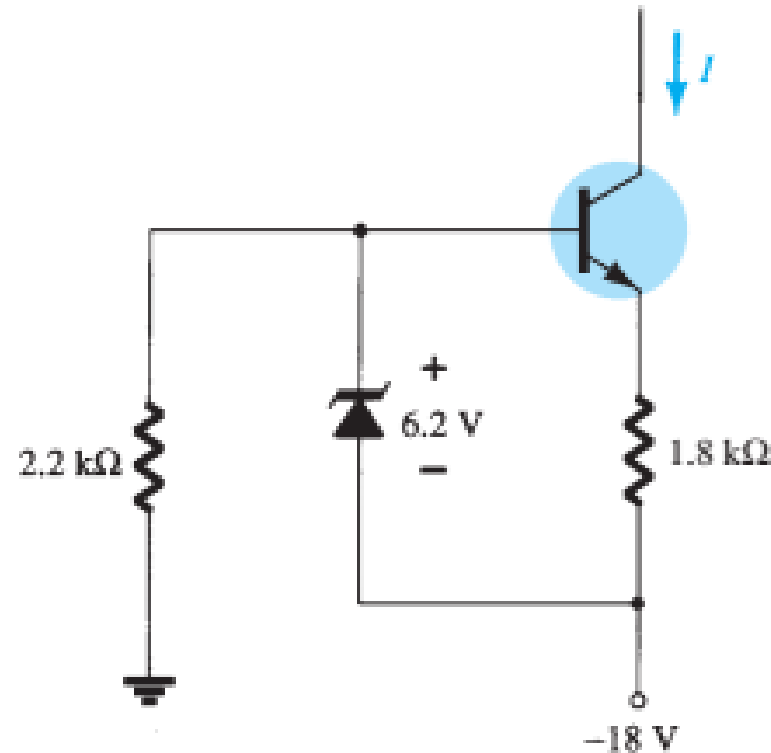


FIG. 4.84

Constant-current circuit for Example 4.30.

Solution:

$$\text{Eq. (4.83): } I = \frac{V_Z - V_{BE}}{R_E} = \frac{6.2 \text{ V} - 0.7 \text{ V}}{1.8 \text{ k}\Omega} = 3.06 \text{ mA} \approx \mathbf{3 \text{ mA}}$$

PNP Transistors (1 of 2)

- The analysis thus far has been limited totally to *npn* transistors.
- Fortunately, the analysis of *pnp* transistors follows the same pattern established for *npn* transistors.
- In fact, the only difference between the resulting equations for a network in which an *npn* transistor has been replaced by a *pnp* transistor is the sign associated with particular quantities.

$$-I_E R_E + V_{BE} - I_B R_B + V_{CC} = 0$$

$$I_B = \frac{V_{CC} + V_{BE}}{R_B + (\beta + 1)R_E}$$

$$-I_E R_E + V_{CE} - I_C R_C + V_{CC} = 0$$

$$V_{CE} = -V_{CC} + I_C(R_C + R_E)$$

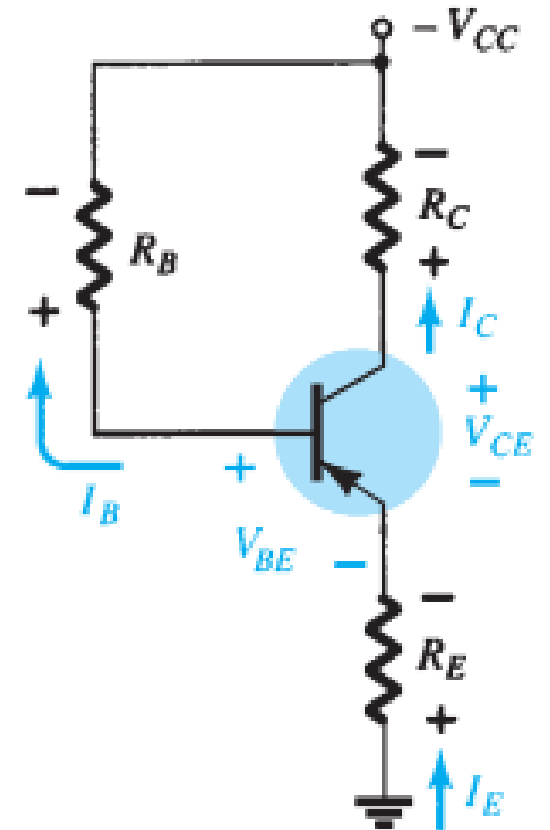


FIG. 4.85
pnp transistor in an emitter-stabilized configuration.

PNP Transistors (2 of 2)

EXAMPLE 4.31 Determine V_{CE} for the voltage-divider bias configuration of Fig. 4.86.


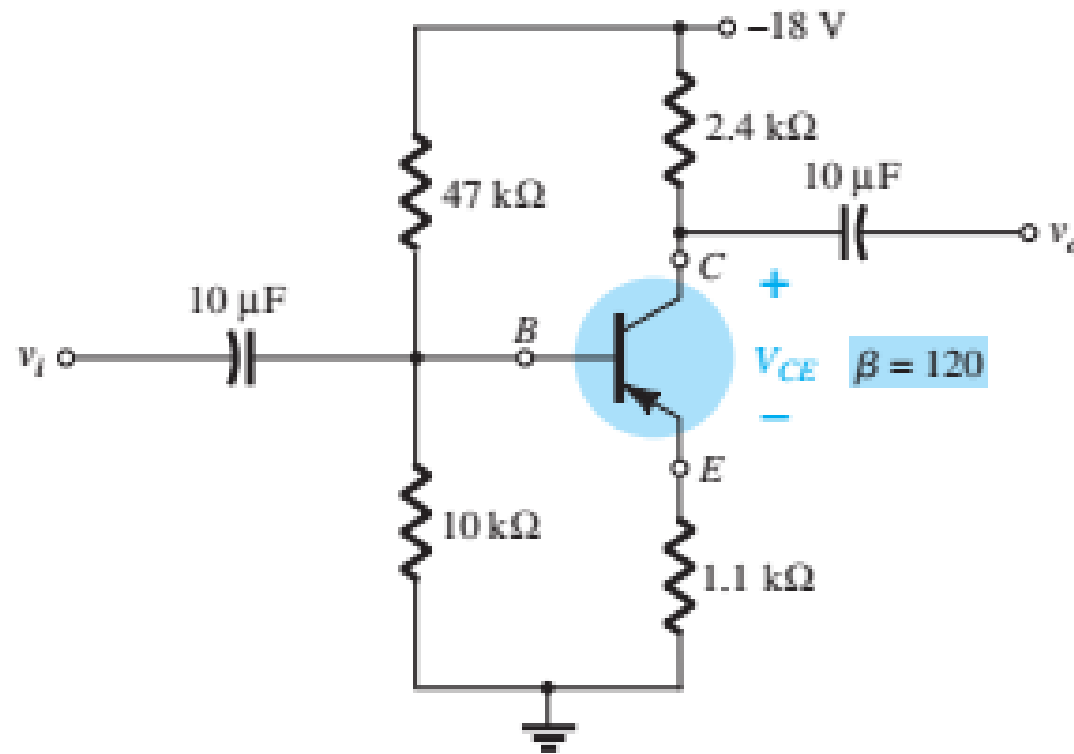


FIG. 4.86

pnp transistor in a voltage-divider bias configuration.

Write the
equations
of solution


Transistor Switching Networks (1 of 3)

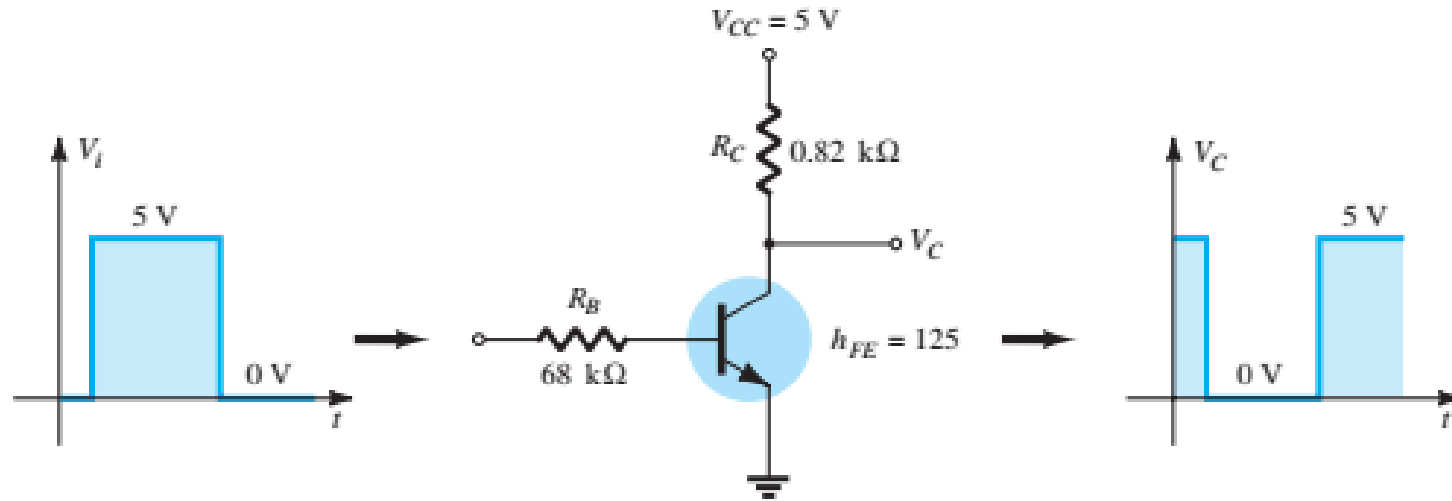

$$I_{C_{\text{sat}}} = \frac{V_{CC}}{R_C}$$


$$I_{B_{\text{max}}} \cong \frac{I_{C_{\text{sat}}}}{\beta_{\text{dc}}}$$
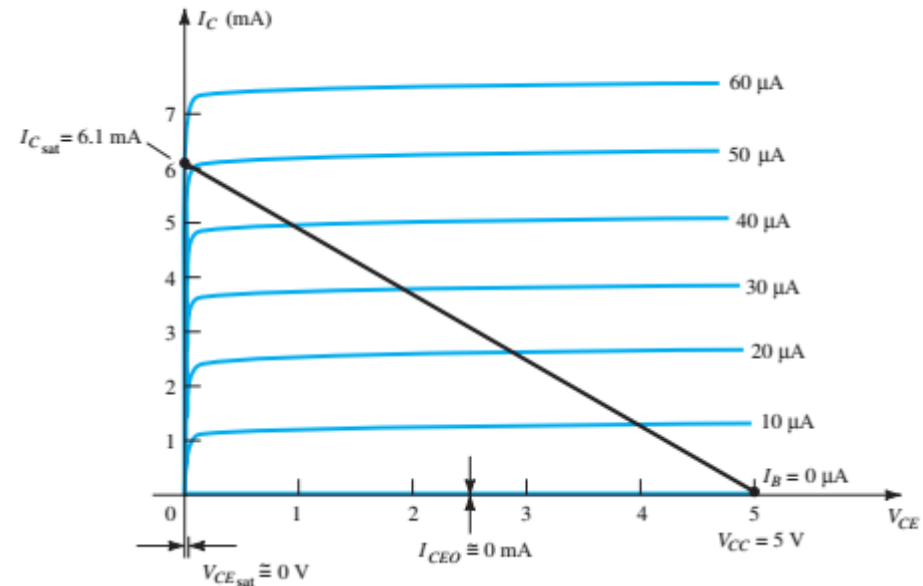
$$I_B > \frac{I_{C_{\text{sat}}}}{\beta_{\text{dc}}}$$



Transistor Switching Networks (2 of 3)

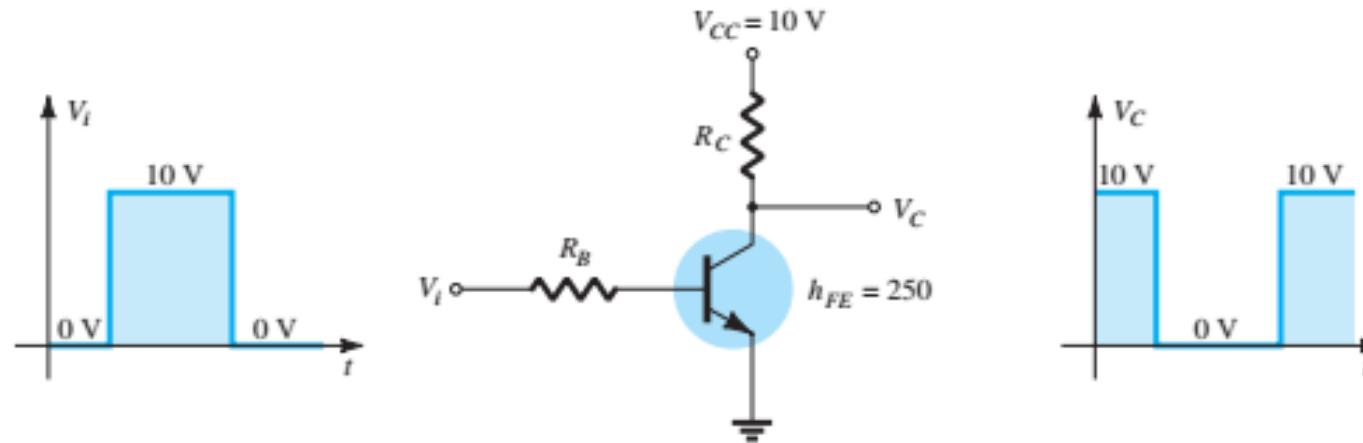EXAMPLE 4.32 Determine R_B and R_C for the transistor inverter of Fig. 4.90 if $I_{C_{sat}} = 10 \text{ mA}$.



Solution: At saturation,

$$I_{C_{sat}} = \frac{V_{CC}}{R_C}$$

and

$$10 \text{ mA} = \frac{10 \text{ V}}{R_C}$$

so that

$$R_C = \frac{10 \text{ V}}{10 \text{ mA}} = 1 \text{ k}\Omega$$

At saturation,

$$I_B \cong \frac{I_{C_{sat}}}{\beta_{dc}} = \frac{10 \text{ mA}}{250} = 40 \mu\text{A}$$

Choosing $I_B = 60 \mu\text{A}$ to ensure saturation and using

$$I_B = \frac{V_i - 0.7 \text{ V}}{R_B}$$

we obtain

$$R_B = \frac{V_i - 0.7 \text{ V}}{I_B} = \frac{10 \text{ V} - 0.7 \text{ V}}{60 \mu\text{A}} = 155 \text{ k}\Omega$$

Choose $R_B = 150 \text{ k}\Omega$, which is a standard value. Then

$$I_B = \frac{V_i - 0.7 \text{ V}}{R_B} = \frac{10 \text{ V} - 0.7 \text{ V}}{150 \text{ k}\Omega} = 62 \mu\text{A}$$

and

$$I_B = 62 \mu\text{A} > \frac{I_{C_{sat}}}{\beta_{dc}} = 40 \mu\text{A}$$

Therefore, use $R_B = 150 \text{ k}\Omega$ and $R_C = 1 \text{ k}\Omega$.

Transistor Switching Networks (3 of 3)

$$R_{\text{sat}} = \frac{V_{CE_{\text{sat}}}}{I_{C_{\text{sat}}}}$$

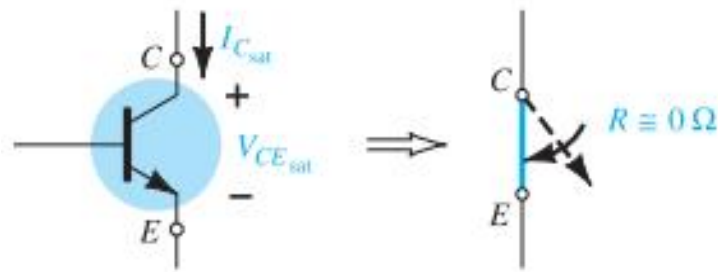


FIG. 4.88

Saturation conditions and the resulting terminal resistance.

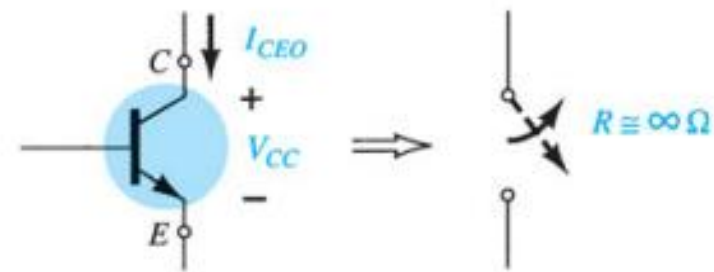


FIG. 4.89

Cutoff conditions and the resulting terminal resistance.

Using a typical average value of $V_{CE_{\text{sat}}}$ such as 0.15 V gives

$$R_{\text{sat}} = \frac{V_{CE_{\text{sat}}}}{I_{C_{\text{sat}}}} = \frac{0.15 \text{ V}}{6.1 \text{ mA}} = 24.6 \Omega$$

$$R_{\text{cutoff}} = \frac{V_{CC}}{I_{CEO}} = \frac{5 \text{ V}}{0 \text{ mA}} = \infty \Omega$$

$$R_{\text{cutoff}} = \frac{V_{CC}}{I_{CEO}} = \frac{5 \text{ V}}{10 \mu\text{A}} = 500 \text{ k}\Omega$$

Troubleshooting Techniques

- For an “on” transistor, the voltage V_{BE} should be in the neighborhood of 0.7 V.
- For the typical transistor amplifier in the active region, V_{CE} is usually about 25% to 75% of V_{CC} .

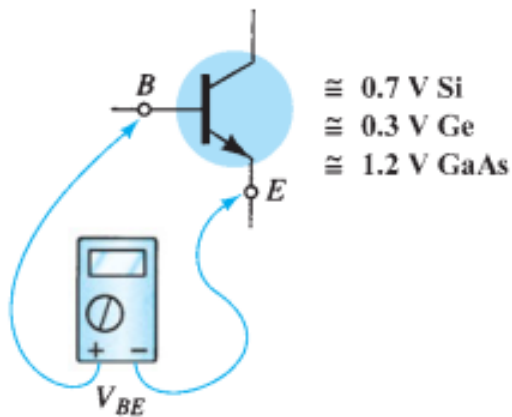


FIG. 4.92

Checking the dc level of V_{BE} .

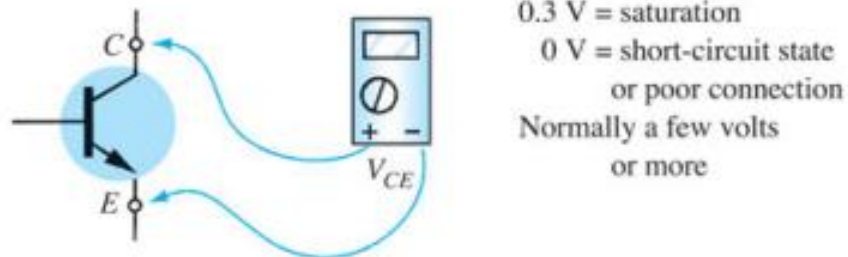


FIG. 4.93

Checking the dc level of V_{CE} .

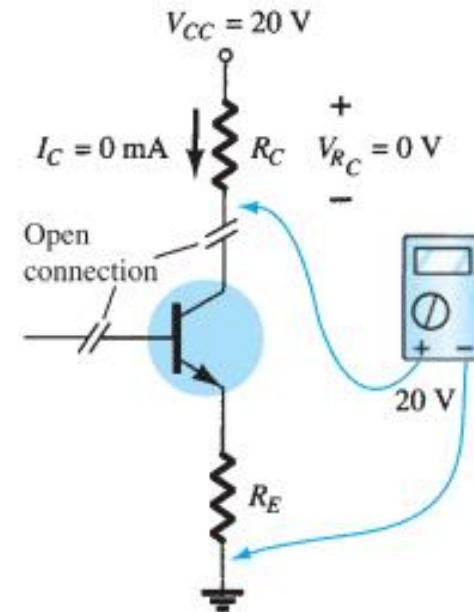


FIG. 4.94

Effect of a poor connection or damaged device.

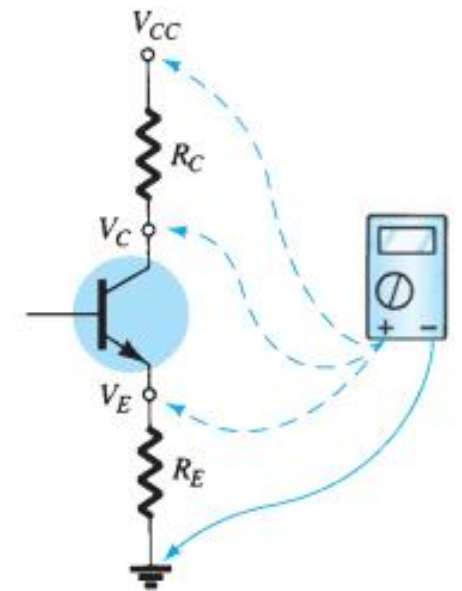


FIG. 4.95

Checking voltage levels with respect to ground.

Thank You!

