

ECE 121

Electronics (1)


Lec. 5: BJT Modeling and re Transistor Model (small signal analysis)

Instructor

Dr. Maher Abdelrasoul

<http://www.bu.edu.eg/staff/mahersalem3>

Agenda

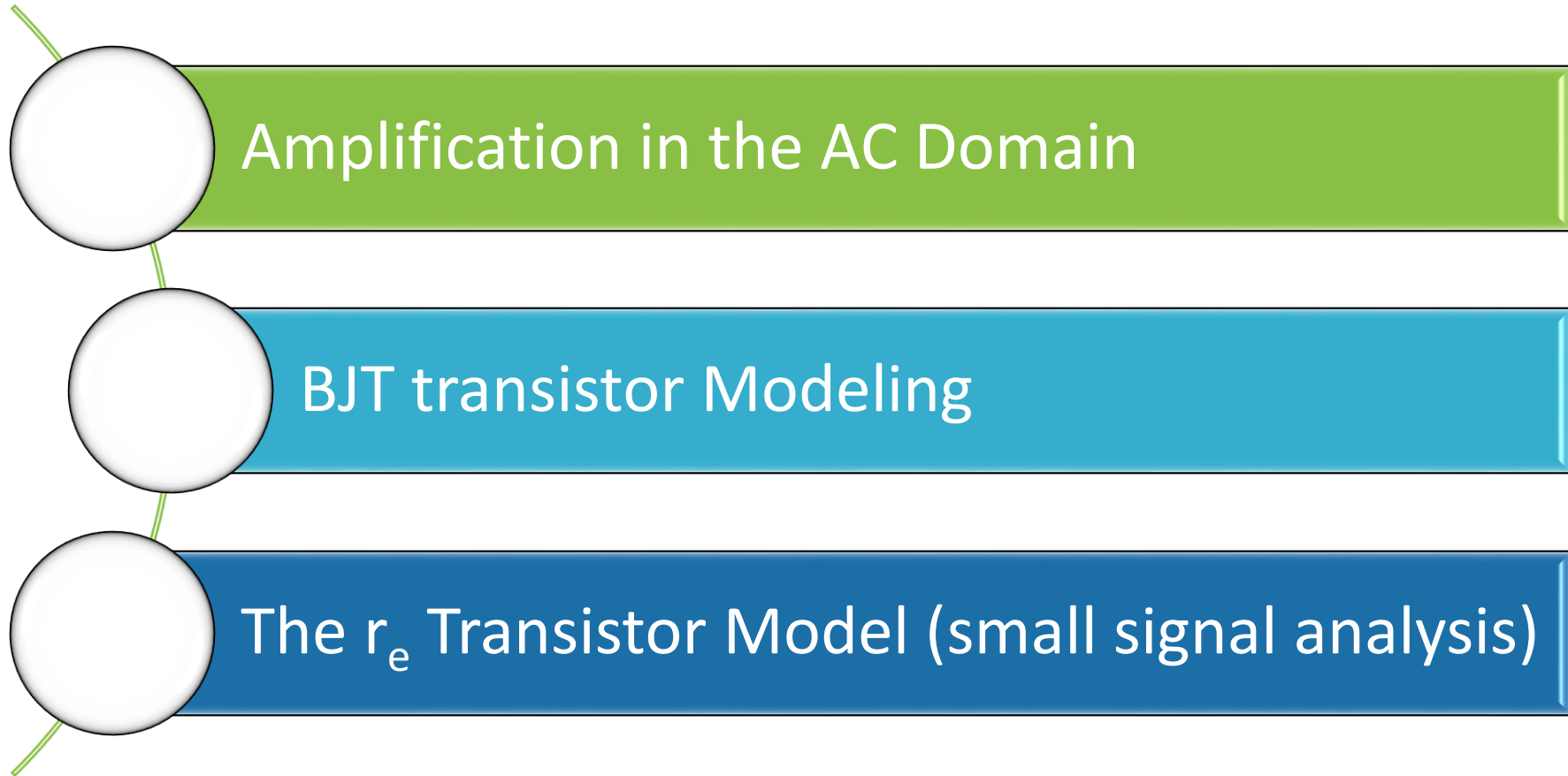

Amplification in the AC Domain

Amplification in the AC Domain

$\eta = P_o/P_i$ cannot be greater than 1.

In fact, a *conversion efficiency* is defined by $\eta = P_{o(ac)}/P_{i(dc)}$, where $P_{o(ac)}$ is the ac power to the load and $P_{i(dc)}$ is the dc power supplied.

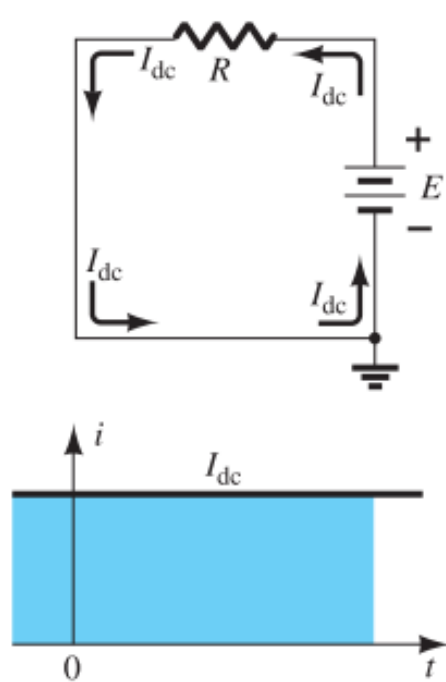


FIG. 5.1

Steady current established by a dc supply.

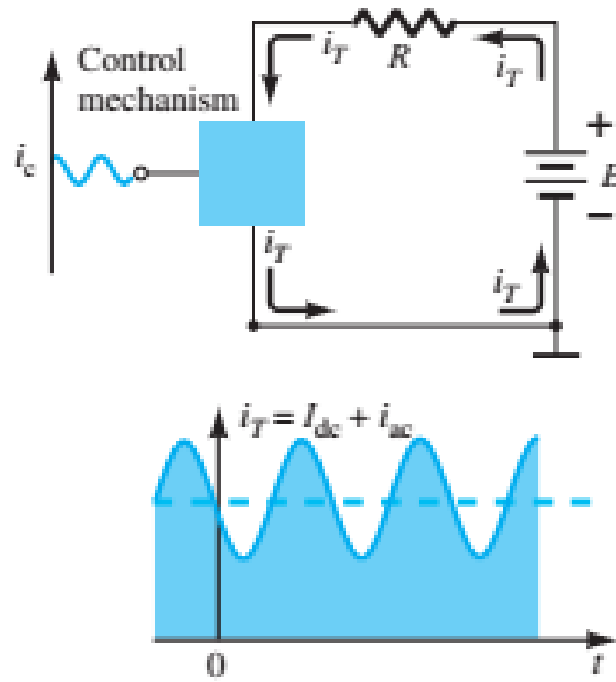



FIG. 5.2

Effect of a control element on the steady-state flow of the electrical system of Fig. 5.1.

The superposition theorem is applicable for the analysis and design of the DC and AC components of a BJT network, permitting the separation of the analysis of the dc and ac responses of the system.



BJT Transistor Modeling

BJT Transistor Modeling

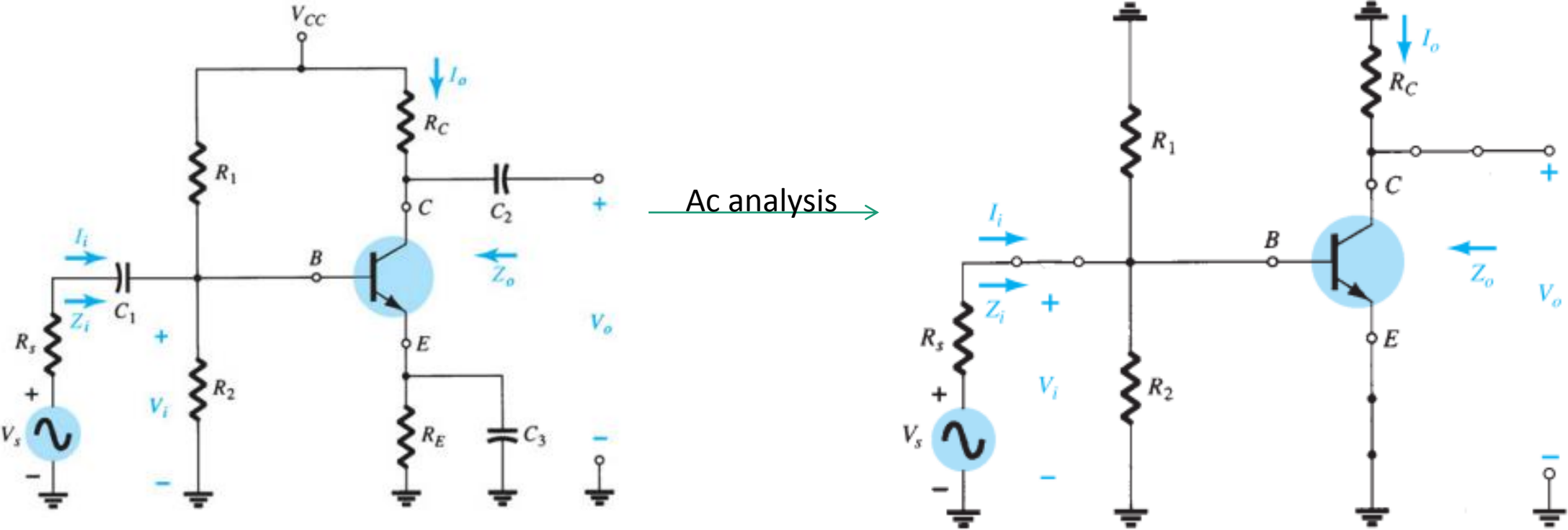




BJT Transistor Modeling (1 of 2)

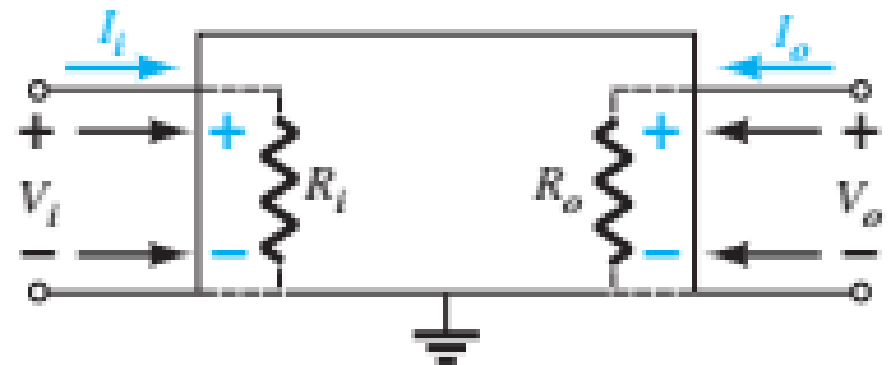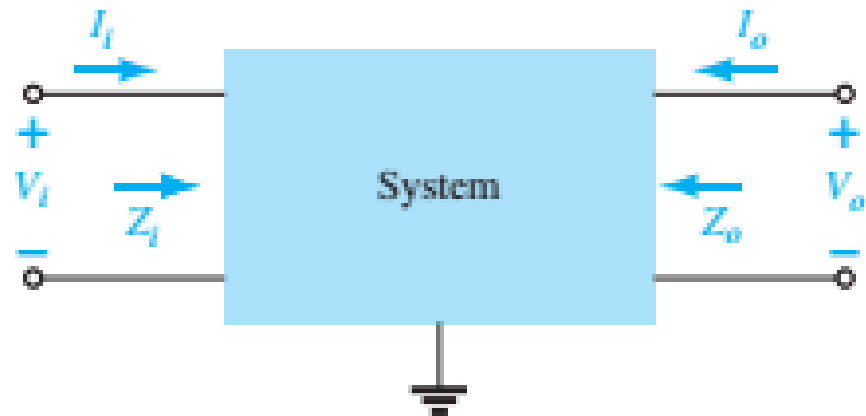- A **model** is a combination of circuit elements, properly chosen, that best approximates the actual behavior of a semiconductor device under specific operating conditions.
- Any electronic system has some important parameters have to be determined
 - Input and Output Voltage
 - Input and Output Impedance
 - Input and Output Current



BJT Transistor Modeling (2 of 2)

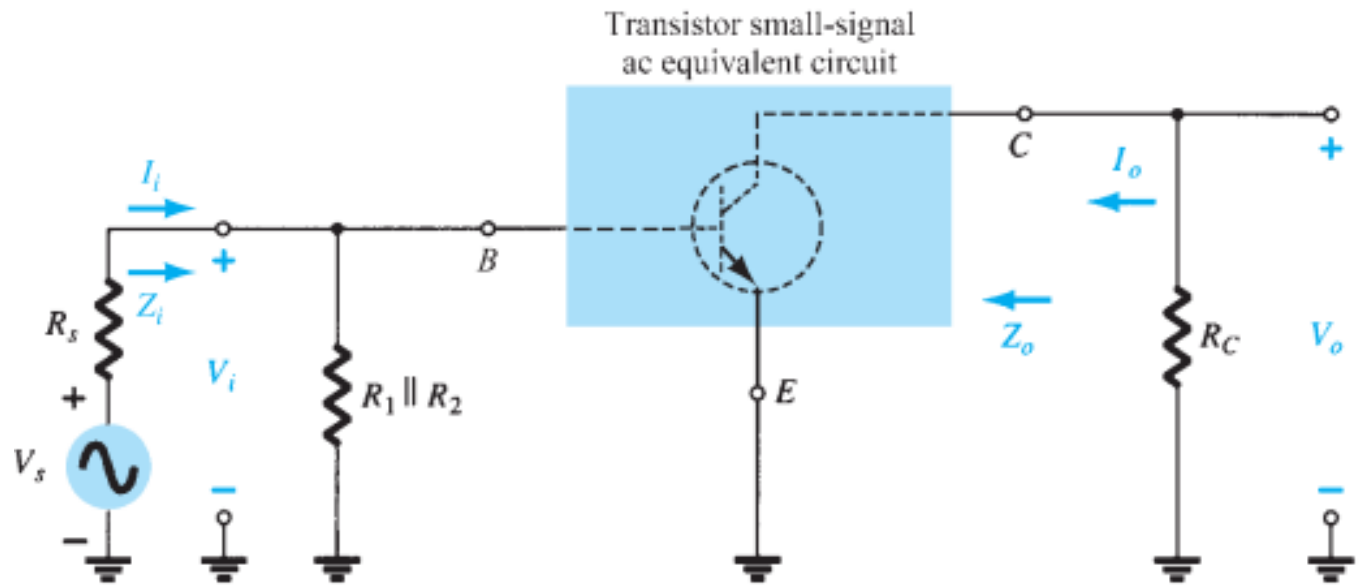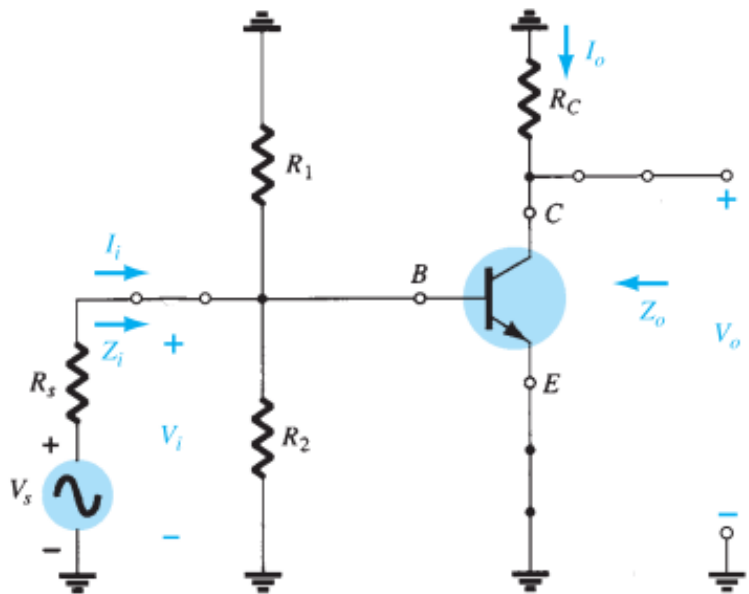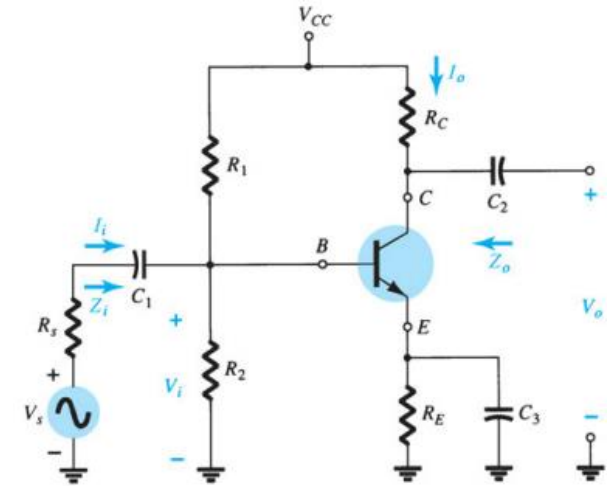- The **ac equivalent** of a transistor network is obtained by:
 - Setting all dc sources to zero and replacing them by a short-circuit equivalent
 - Replacing all capacitors by a short-circuit equivalent
 - Removing all elements bypassed by the short-circuit equivalents introduced by steps 1 and 2
 - Redrawing the network in a more convenient and logical form



The r_e Transistor Model

- Common Emitter Configuration
- Common Base Configuration
- Common Collector Configuration
- r_e Model in Different Bias Circuits

The r_e Transistor Model (CE)

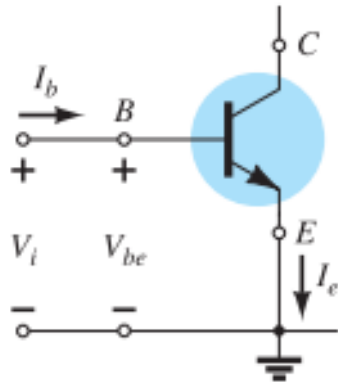


FIG. 5.8

Finding the input equivalent circuit for a BJT transistor.

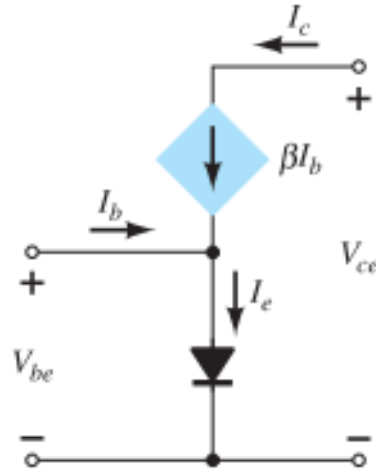


FIG. 5.12

BJT equivalent circuit.

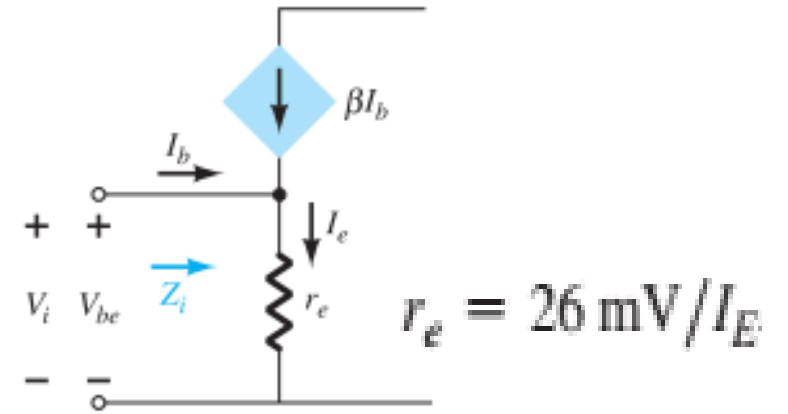


FIG. 5.13

Defining the level of Z_i .

$$Z_i = \frac{V_i}{I_b} = \frac{V_{be}}{I_b}$$

$$V_{be} = I_e r_e = (I_c + I_b) r_e = (\beta I_b + I_b) r_e$$

$$= (\beta + 1) I_b r_e$$

$$Z_i = \frac{V_{be}}{I_b} = \frac{(\beta + 1) I_b r_e}{I_b}$$

$$Z_i = (\beta + 1) r_e \cong \beta r_e$$

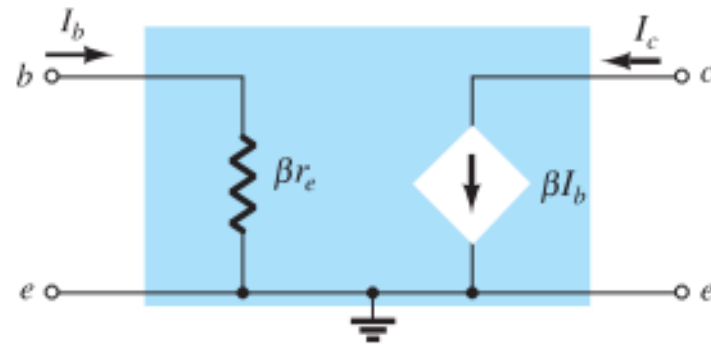


FIG. 5.14

Improved BJT equivalent circuit.

The r_e Transistor Model (CE)

Early Voltage

$$\text{Slope} = \frac{\Delta y}{\Delta x} = \frac{\Delta I_C}{\Delta V_{CE}} = \frac{1}{r_o}$$

$$r_o = \frac{\Delta V_{CE}}{\Delta I_C}$$

$$r_o = \frac{\Delta V}{\Delta I} = \frac{V_A + V_{CEQ}}{I_{CQ}}$$

$$r_o \cong \frac{V_A}{I_{CQ}}$$

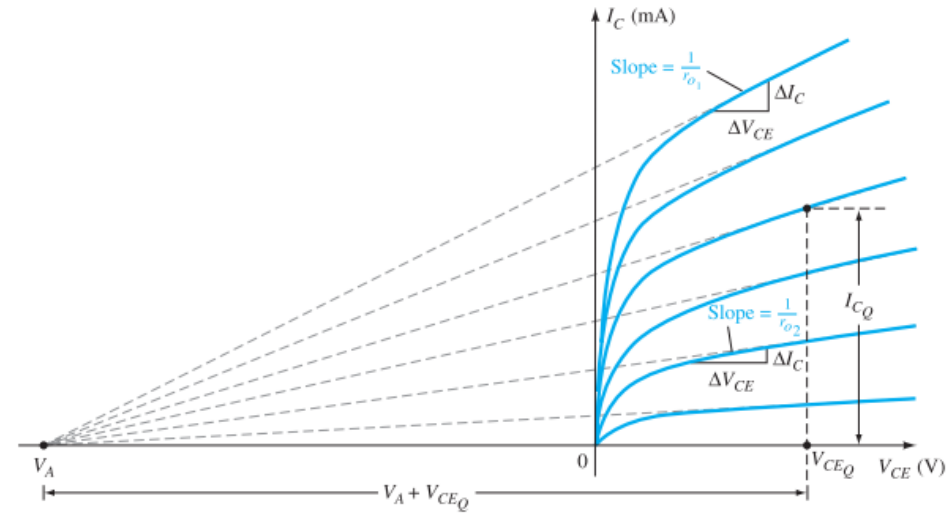


FIG. 5.15

Defining the Early voltage and the output impedance of a transistor.

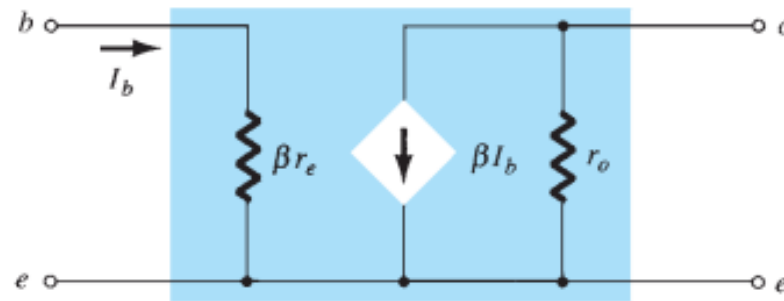


FIG. 5.16

r_e model for the common-emitter transistor configuration including effects of r_o .

The r_e Transistor Model (CB)

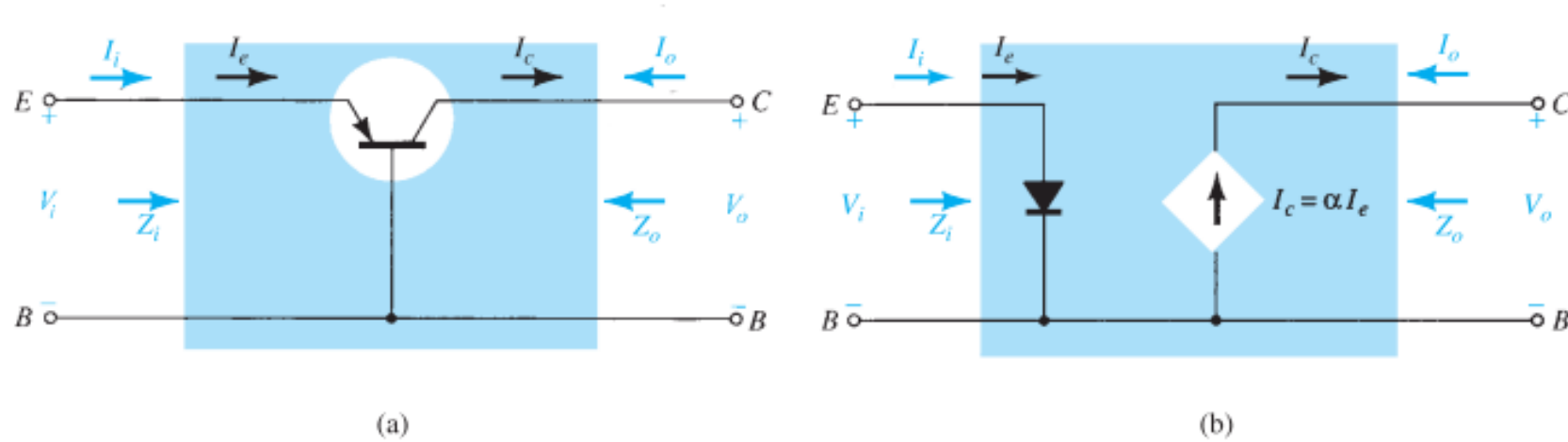


FIG. 5.17

(a) Common-base BJT transistor; (b) equivalent circuit for configuration of (a).

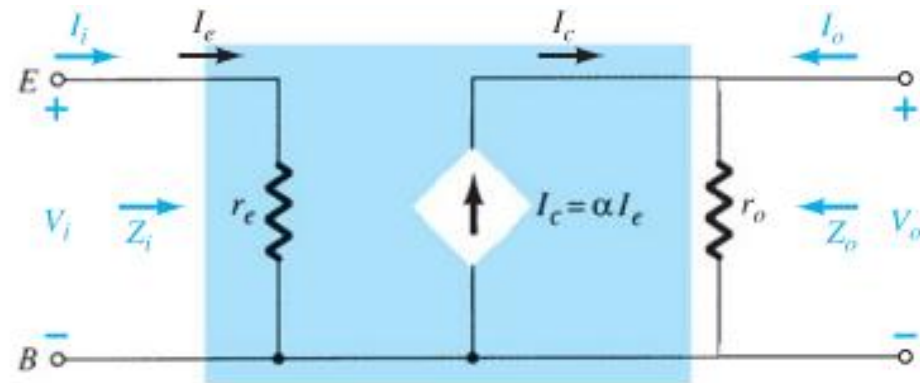


FIG. 5.18

Common base r_e equivalent circuit.

The r_e Transistor Model (CC)

- For the common-collector configuration, the model defined for the common-emitter configuration is normally applied rather than defining a model for the common-collector configuration.

npn versus pnp

- The dc analysis of *npn* and *pnp* configurations is quite different in the sense that the currents will have opposite directions and the voltages opposite polarities.
- However, for an ac analysis where the signal will progress between positive and negative values, the ac equivalent circuit will be the same.

C.E. Fixed Bias Configuration

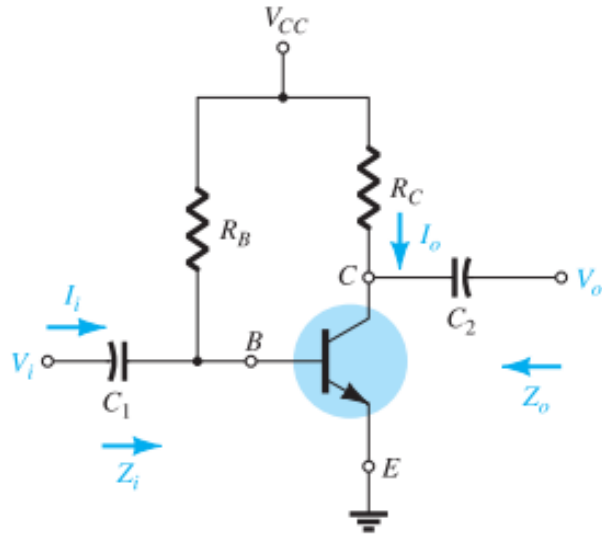


FIG. 5.20

Common-emitter fixed-bias configuration.

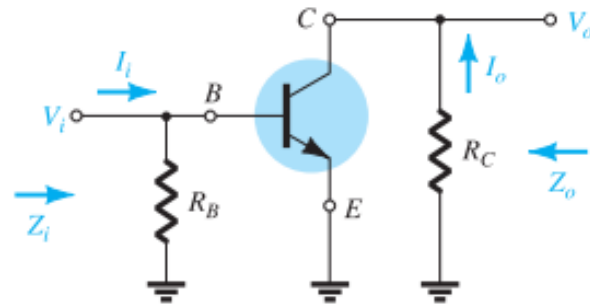


FIG. 5.21

Network of Fig. 5.20 following the removal of the effects of V_{CC} , C_1 , and C_2 .

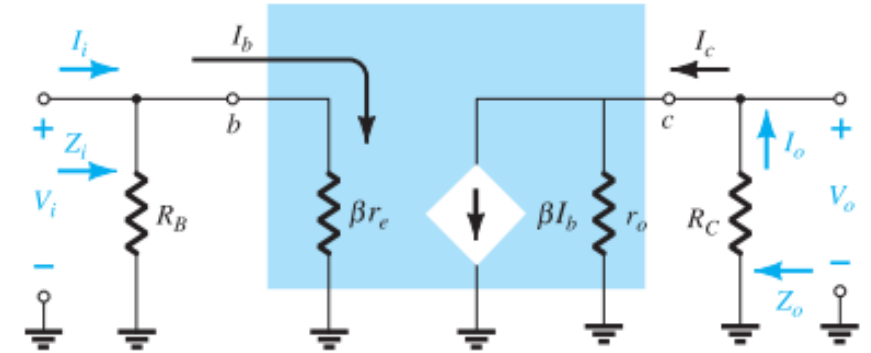


FIG. 5.22

Substituting the r_e model into the network of Fig. 5.21.

$$Z_i = R_B \parallel \beta r_e \quad \text{ohms}$$

$$Z_i \cong \beta r_e \quad \text{ohms} \quad R_B \geq 10\beta r_e$$

$$Z_o = R_C \parallel r_o \quad \text{ohms}$$

$$Z_o \cong R_C \quad \text{ohms} \quad r_o \geq 10R_C$$

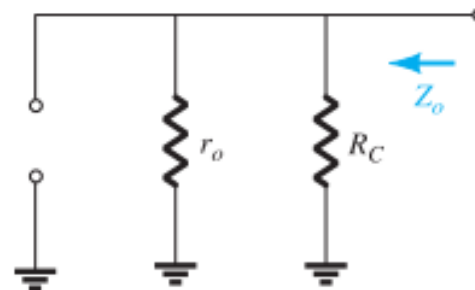


FIG. 5.23

Determining Z_o for the network of Fig. 5.22.

$$V_o = -\beta I_b (R_C \parallel r_o)$$

$$I_b = \frac{V_i}{\beta r_e}$$

$$V_o = -\beta \left(\frac{V_i}{\beta r_e} \right) (R_C \parallel r_o)$$

$$A_v = -\frac{R_C}{r_e} \quad r_o \geq 10R_C$$

$$A_v = \frac{V_o}{V_i} = -\frac{(R_C \parallel r_o)}{r_e}$$

C.E. Fixed Bias Configuration (Phase relationship)

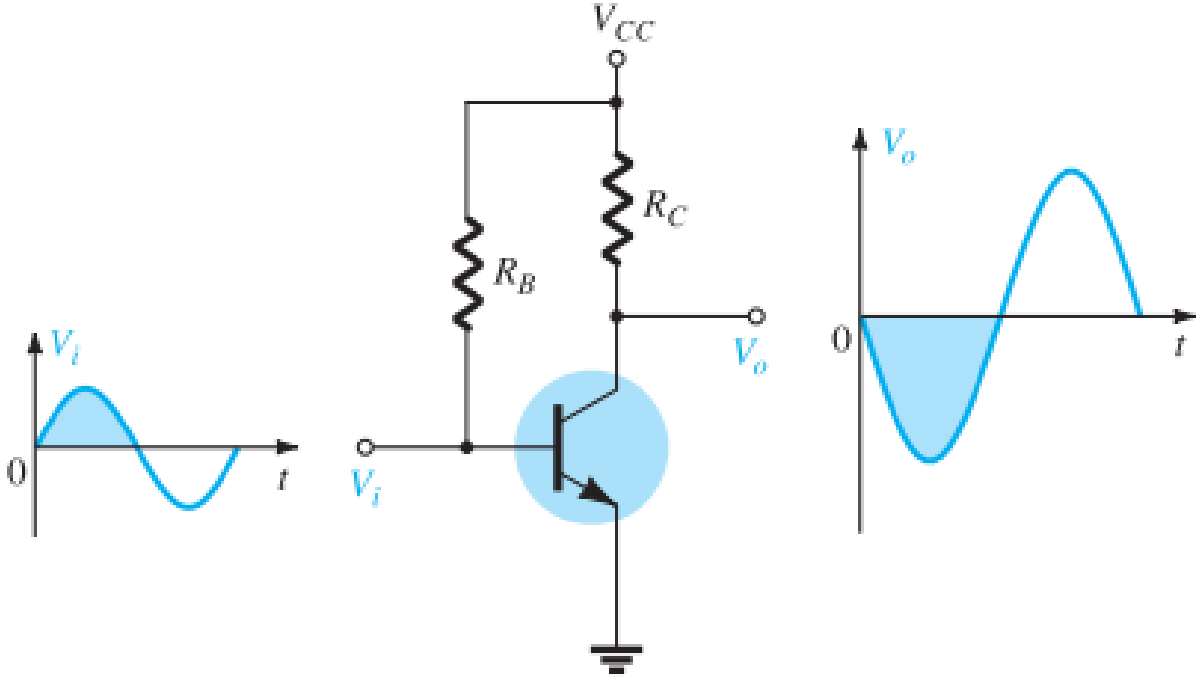


FIG. 5.24

Demonstrating the 180° phase shift between input and output waveforms.

C.E. Fixed Bias Configuration (Example)

EXAMPLE 5.1 For the network of Fig. 5.25:

- Determine r_e .
- Find Z_i (with $r_o = \infty \Omega$).
- Calculate Z_o (with $r_o = \infty \Omega$).
- Determine A_v (with $r_o = \infty \Omega$).
- Repeat parts (c) and (d) including $r_o = 50 \text{ k}\Omega$ in all calculations and compare results.

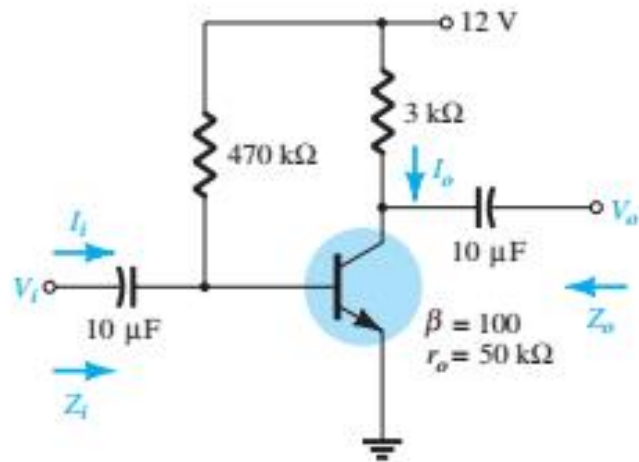


FIG. 5.25
Example 5.1.

Solution:

a. DC analysis:

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{12 \text{ V} - 0.7 \text{ V}}{470 \text{ k}\Omega} = 24.04 \mu\text{A}$$

$$I_E = (\beta + 1)I_B = (101)(24.04 \mu\text{A}) = 2.428 \text{ mA}$$

$$r_e = \frac{26 \text{ mV}}{I_E} = \frac{26 \text{ mV}}{2.428 \text{ mA}} = \mathbf{10.71 \Omega}$$

b. $\beta r_e = (100)(10.71 \Omega) = 1.071 \text{ k}\Omega$

$$Z_i = R_B \parallel \beta r_e = 470 \text{ k}\Omega \parallel 1.071 \text{ k}\Omega = \mathbf{1.07 \text{ k}\Omega}$$

c. $Z_o = R_C = \mathbf{3 \text{ k}\Omega}$

$$d. A_v = -\frac{R_C}{r_e} = -\frac{3 \text{ k}\Omega}{10.71 \Omega} = \mathbf{-280.11}$$

e. $Z_o = r_o \parallel R_C = 50 \text{ k}\Omega \parallel 3 \text{ k}\Omega = \mathbf{2.83 \text{ k}\Omega}$ vs. $3 \text{ k}\Omega$

$$A_v = -\frac{r_o \parallel R_C}{r_e} = \frac{2.83 \text{ k}\Omega}{10.71 \Omega} = \mathbf{-264.24}$$
 vs. -280.11

C.E. Voltage-Divider Bias

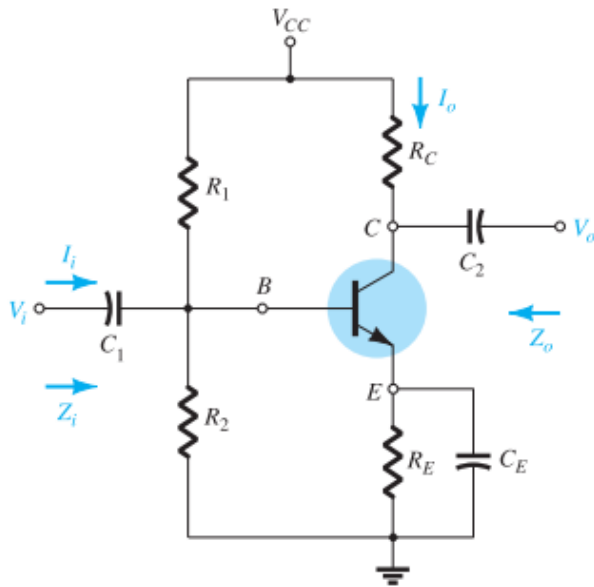


FIG. 5.26
Voltage-divider bias configuration.

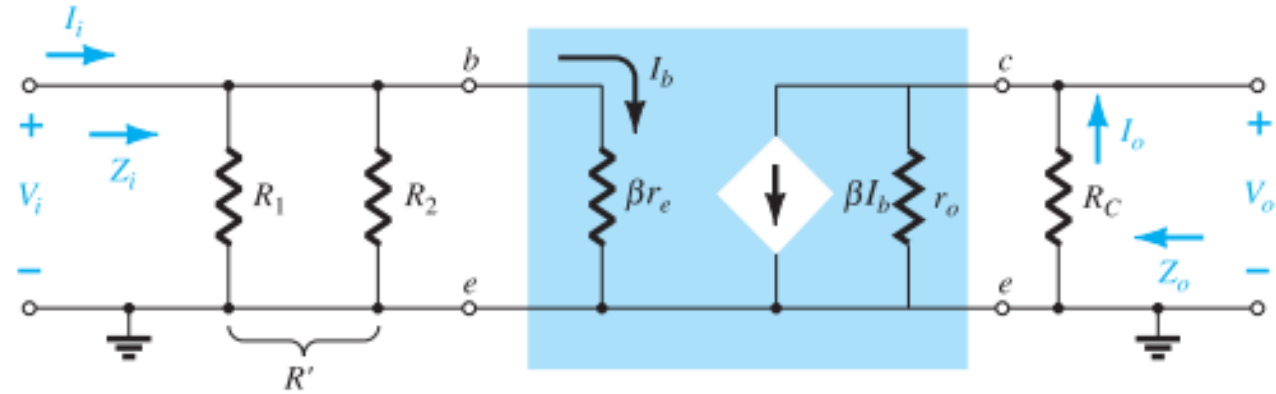


FIG. 5.27

Substituting the r_e equivalent circuit into the ac equivalent network of Fig. 5.26.

$$R' = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

$$Z_i = R' \parallel \beta r_e$$

$$Z_o = R_C \parallel r_o$$

$$Z_o \cong R_C \quad r_o \geq 10R_C$$

$$V_o = -(\beta I_b)(R_C \parallel r_o)$$

$$I_b = \frac{V_i}{\beta r_e}$$

$$V_o = -\beta \left(\frac{V_i}{\beta r_e} \right) (R_C \parallel r_o)$$

$$A_v = \frac{V_o}{V_i} = \frac{-R_C \parallel r_o}{r_e}$$

$$A_v = \frac{V_o}{V_i} \cong -\frac{R_C}{r_e} \quad r_o \geq 10R_C$$

180° phase shift

C.E. Emitter Bias Configuration (Un-bypassed without r_o)

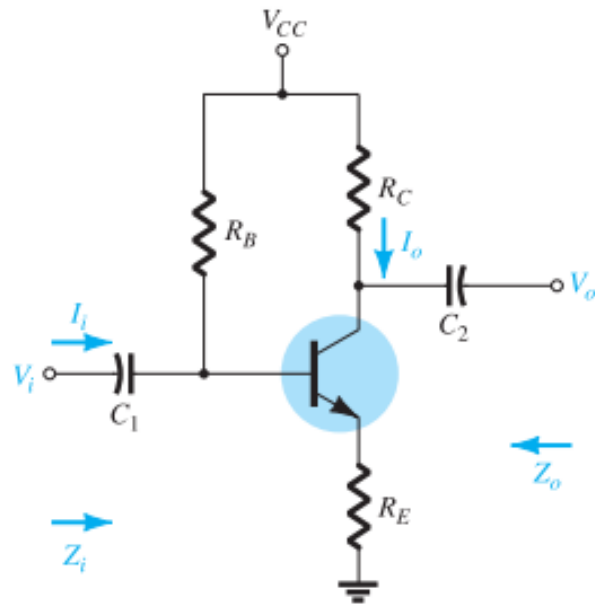


FIG. 5.29

CE emitter-bias configuration.

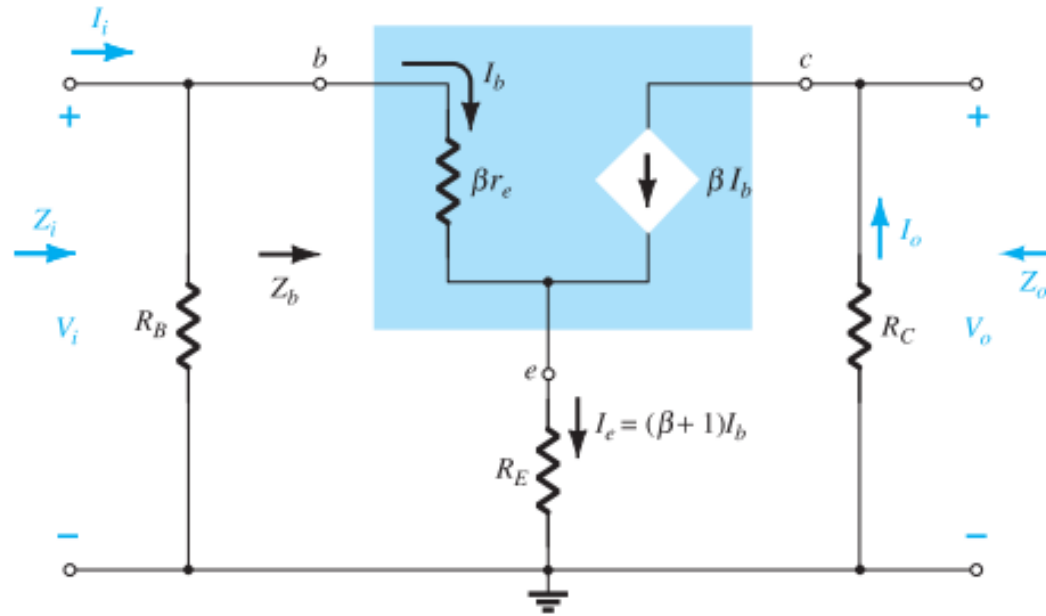


FIG. 5.30

Substituting the r_e equivalent circuit into the ac equivalent network of Fig. 5.29.

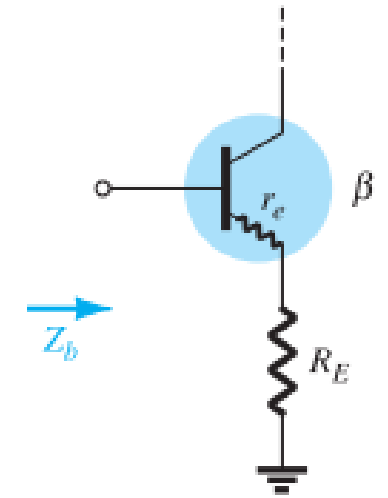


FIG. 5.31

Defining the input impedance of a transistor with an unbypassed emitter resistor.

$$V_i = I_b \beta r_e + I_e R_E$$

$$V_i = I_b \beta r_e + (\beta + 1) I_b R_E$$

$$Z_b = \frac{V_i}{I_b} = \beta r_e + (\beta + 1) R_E$$

$$Z_b = \beta r_e + (\beta + 1) R_E$$

$$Z_b \cong \beta r_e + \beta R_E$$

$$Z_b \cong \beta (r_e + R_E)$$

$$Z_b \cong \beta R_E$$

$$Z_i = R_B \parallel Z_b$$

$$Z_o = R_C$$

C.E. Emitter Bias Configuration (Un-bypassed without r_o)

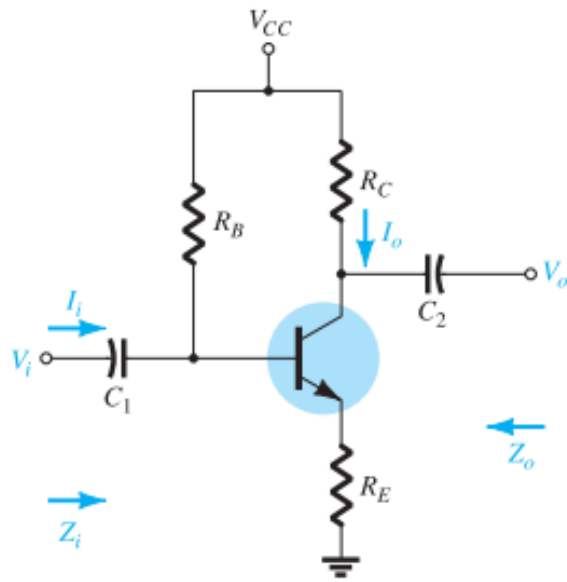


FIG. 5.29
CE emitter-bias configuration.

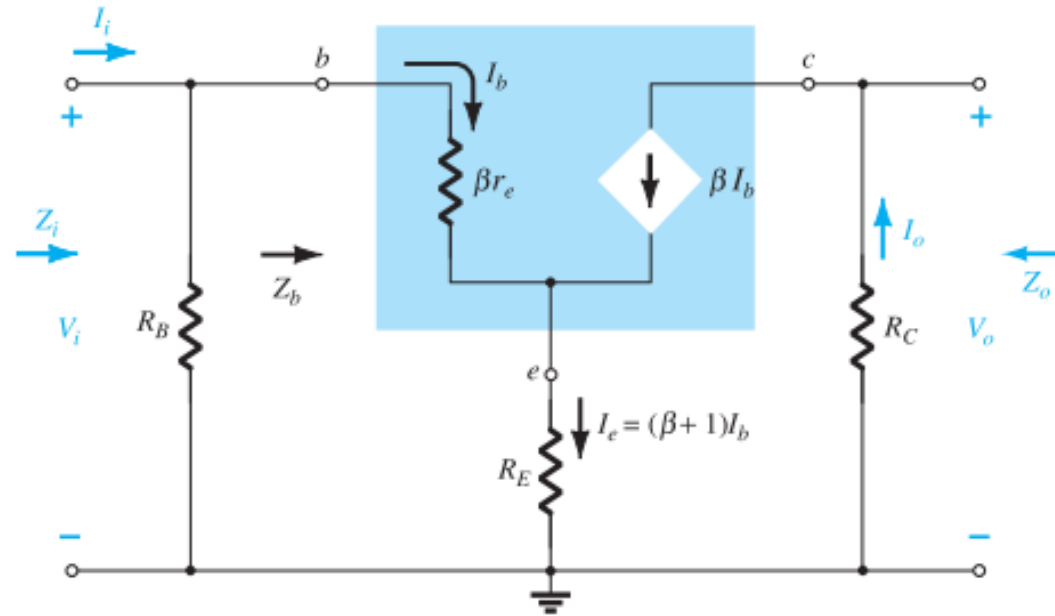


FIG. 5.30
Substituting the r_e equivalent circuit into the ac equivalent network of Fig. 5.29.

$$I_b = \frac{V_i}{Z_b}$$

$$V_o = -I_o R_C = -\beta I_b R_C$$

$$= -\beta \left(\frac{V_i}{Z_b} \right) R_C$$

$$A_v = \frac{V_o}{V_i} = -\frac{\beta R_C}{Z_b}$$

$$Z_b \cong \beta(r_e + R_E)$$

$$Z_b \cong \beta R_E$$

$$A_v = \frac{V_o}{V_i} \cong -\frac{R_C}{r_e + R_E}$$

$$A_v = \frac{V_o}{V_i} \cong -\frac{R_C}{R_E}$$

180° phase shift

C.E. Emitter Bias Configuration (Un-bypassed with r_o)

$$Z_i = R_B \parallel Z_b$$

$$Z_b = \beta r_e + \left[\frac{(\beta + 1) + R_C/r_o}{1 + (R_C + R_E)/r_o} \right] R_E$$

R_C/r_o is always much less than $(\beta + 1)$,

$$Z_b \cong \beta r_e + \frac{(\beta + 1)R_E}{1 + (R_C + R_E)/r_o}$$

For $r_o \geq 10(R_C + R_E)$,

$$Z_b \cong \beta r_e + (\beta + 1)R_E$$

$$Z_b \cong \beta(r_e + R_E) \quad r_o \geq 10(R_C + R_E)$$

$$Z_o = R_C \parallel \left[r_o + \frac{\beta(r_o + r_e)}{1 + \frac{\beta r_e}{R_E}} \right]$$

$r_o \gg r_e$

$$Z_o \cong R_C \parallel r_o \left[1 + \frac{\beta}{1 + \frac{\beta r_e}{R_E}} \right]$$

$$Z_o \cong R_C \parallel r_o \left[1 + \frac{1}{\frac{1}{\beta} + \frac{r_e}{R_E}} \right]$$

Typically $1/\beta$ and r_e/R_E are less than one with a sum usually less than one.

$$Z_o \cong R_C \quad \text{Any level of } r_o$$

$$A_v = \frac{V_o}{V_i} = \frac{-\frac{\beta R_C}{Z_b} \left[1 + \frac{r_e}{r_o} \right] + \frac{R_C}{r_o}}{1 + \frac{R_C}{r_o}}$$

$\frac{r_e}{r_o} \ll 1$,


$$A_v = \frac{V_o}{V_i} \cong \frac{-\frac{\beta R_C}{Z_b} + \frac{R_C}{r_o}}{1 + \frac{R_C}{r_o}}$$

$r_o \geq 10R_C$,

$$A_v = \frac{V_o}{V_i} \cong -\frac{\beta R_C}{Z_b} \quad r_o \geq 10R_C$$

C.E. Emitter Bias Configuration (bypassed)

Same as CE fixed bias config.

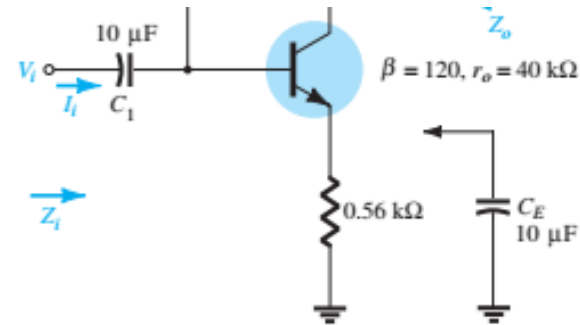

Portion bypassed

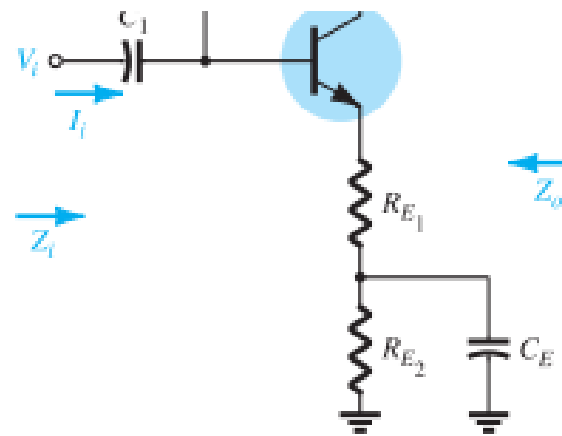


FIG. 5.35

An emitter-bias configuration with a portion of the emitter-bias resistance bypassed in the ac domain.

C.E. Emitter Bias Configuration (Example)

EXAMPLE 5.3 For the network of Fig. 5.32, without C_E (unbypassed), determine:

- r_e .
- Z_i .
- Z_o .
- A_v .

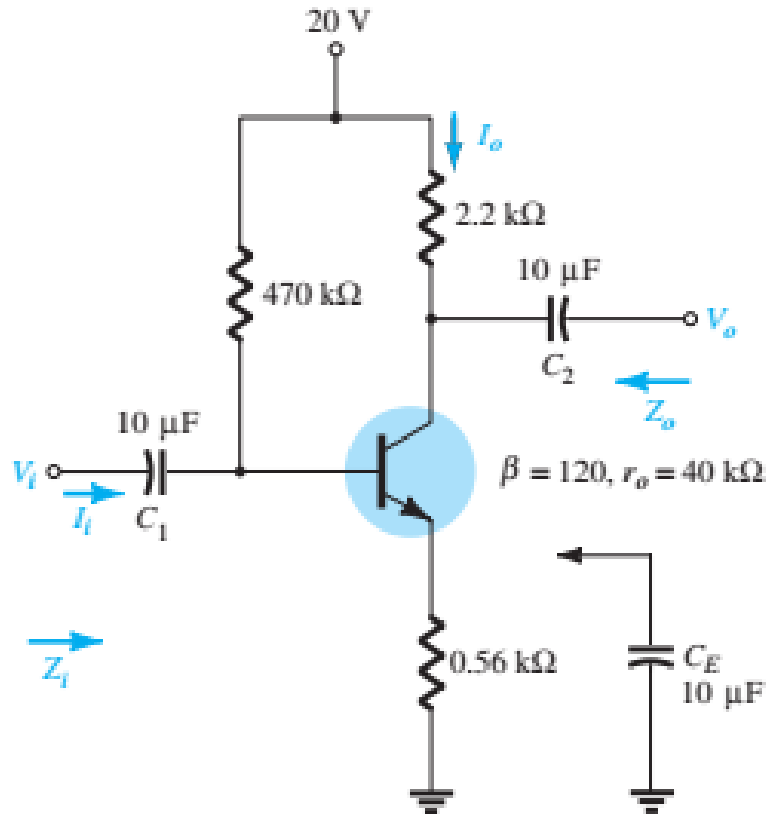


FIG. 5.32
Example 5.3.

Solution:

a. DC:

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_E} = \frac{20\text{ V} - 0.7\text{ V}}{470\text{ k}\Omega + (121)0.56\text{ k}\Omega} = 35.89\ \mu\text{A}$$

$$I_E = (\beta + 1)I_B = (121)(35.89\ \mu\text{A}) = 4.34\ \text{mA}$$

$$\text{and } r_e = \frac{26\text{ mV}}{I_E} = \frac{26\text{ mV}}{4.34\ \text{mA}} = 5.99\ \Omega$$

b. Testing the condition $r_o \geq 10(R_C + R_E)$, we obtain

$$40\text{ k}\Omega \geq 10(2.2\text{ k}\Omega + 0.56\text{ k}\Omega)$$

$$40\text{ k}\Omega \geq 10(2.76\text{ k}\Omega) = 27.6\text{ k}\Omega \text{ (satisfied)}$$

Therefore,

$$Z_b \cong \beta(r_e + R_E) = 120(5.99\ \Omega + 560\ \Omega) = 67.92\text{ k}\Omega$$

and

$$Z_i = R_B \parallel Z_b = 470\text{ k}\Omega \parallel 67.92\text{ k}\Omega = 59.34\text{ k}\Omega$$

c. $Z_o = R_C = 2.2\text{ k}\Omega$

d. $r_o \geq 10R_C$ is satisfied. Therefore,

$$A_v = \frac{V_o}{V_i} \cong -\frac{\beta R_C}{Z_b} = -\frac{(120)(2.2\text{ k}\Omega)}{67.92\text{ k}\Omega} = -3.89$$

compared to -3.93 using Eq. (5.20): $A_v \cong -R_C/R_E$.

C.E. Emitter Bias Configuration (Example)

EXAMPLE 5.3 For the network of Fig. 5.32, without C_E (unbypassed), determine:

- r_e .
- Z_i .
- Z_o .
- A_v .

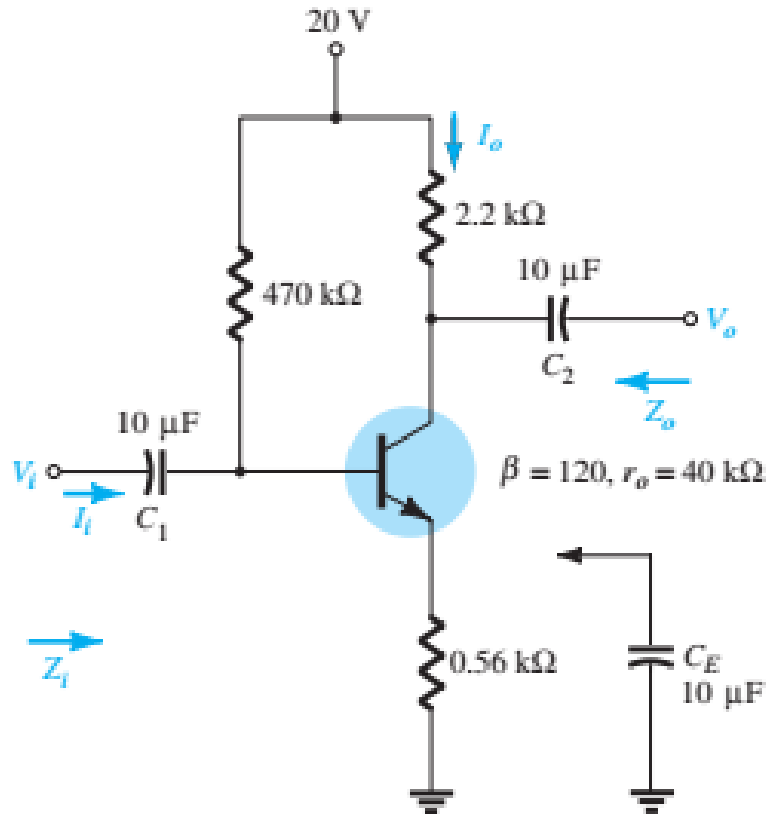


FIG. 5.32
Example 5.3.

EXAMPLE 5.4 Repeat the analysis of Example 5.3 with C_E in place.

Solution:

- The dc analysis is the same, and $r_e = 5.99 \Omega$.
- R_E is “shorted out” by C_E for the ac analysis. Therefore,

$$Z_i = R_B \parallel Z_b = R_B \parallel \beta r_e = 470 \text{ k}\Omega \parallel (120)(5.99 \Omega)$$

$$= 470 \text{ k}\Omega \parallel 718.8 \Omega \cong 717.70 \Omega$$
- $Z_o = R_C = 2.2 \text{ k}\Omega$
- $A_v = -\frac{R_C}{r_e}$

$$= -\frac{2.2 \text{ k}\Omega}{5.99 \Omega} = -367.28 \text{ (a significant increase)}$$

Emitter Follower (Common Collector) Configuration

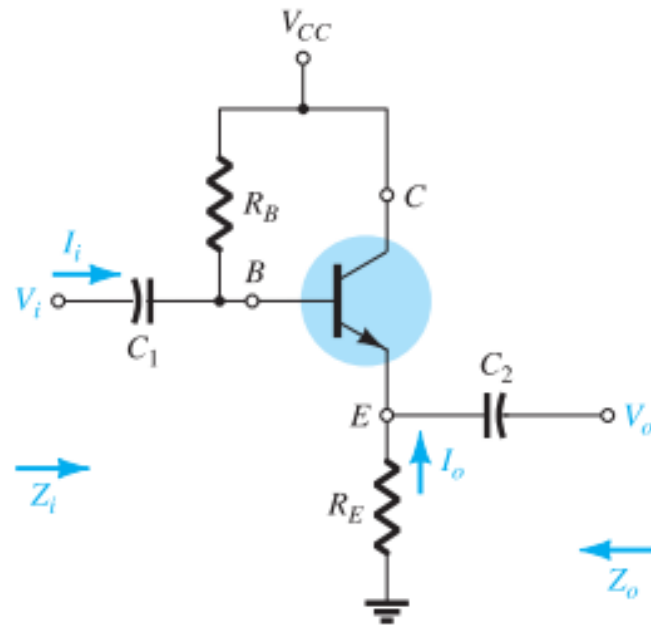


FIG. 5.36

Emitter-follower configuration.

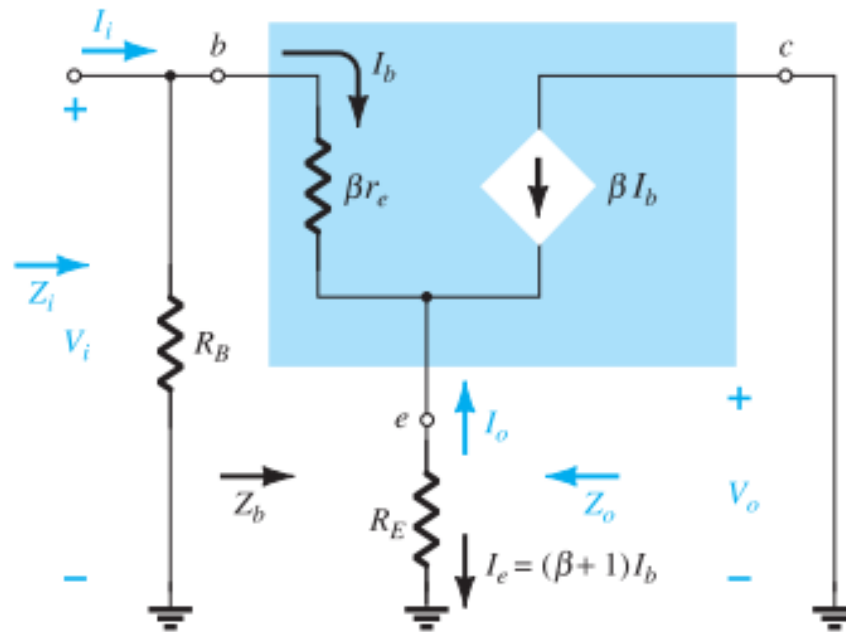


FIG. 5.37

Substituting the r_e equivalent circuit into the ac equivalent network of Fig. 5.36.

$$Z_i = R_B \parallel Z_b$$

$$Z_b = \beta r_e + (\beta + 1)R_E$$

$$Z_b \cong \beta(r_e + R_E)$$

$$Z_b \cong \beta R_E \quad R_E \gg r_e$$

Emitter Follower Configuration (o/p impedance and Gain)

$$I_e = (\beta + 1)I_b = (\beta + 1)\frac{V_i}{Z_b}$$

$$I_e = \frac{(\beta + 1)V_i}{\beta r_e + (\beta + 1)R_E}$$

$$I_e = \frac{V_i}{[\beta r_e / (\beta + 1)] + R_E}$$

$$(\beta + 1) \cong \beta$$

$$\frac{\beta r_e}{\beta + 1} \cong \frac{\beta r_e}{\beta} = r_e$$

$$I_e \cong \frac{V_i}{r_e + R_E}$$

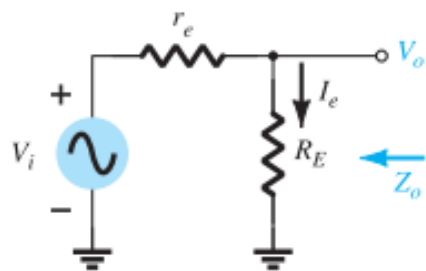


FIG. 5.38

Defining the output impedance for the emitter-follower configuration.

$$Z_o = R_E \parallel r_e$$

$$Z_o \cong r_e$$

$$V_o = \frac{R_E V_i}{R_E + r_e}$$

$$A_v = \frac{V_o}{V_i} = \frac{R_E}{R_E + r_e}$$

Because R_E is usually much greater than r_e ,

$$R_E + r_e \cong R_E;$$

$$A_v = \frac{V_o}{V_i} \cong 1$$

in phase

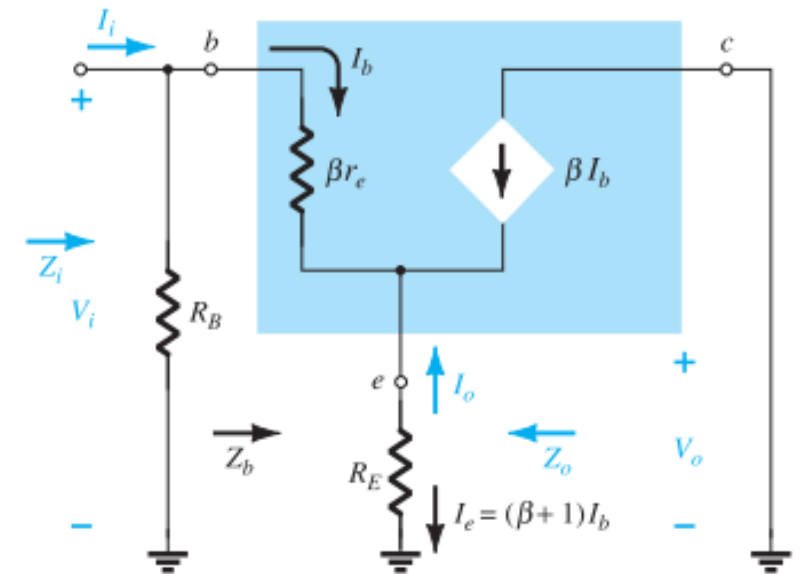


FIG. 5.37

Substituting the r_e equivalent circuit into the ac equivalent network of Fig. 5.36.

Emitter Follower Configuration..

Effect of r_o

$$Z_b = \beta r_e + \frac{(\beta + 1)R_E}{1 + \frac{R_E}{r_o}}$$

$$Z_o = r_o \parallel R_E \parallel \frac{\beta r_e}{(\beta + 1)}$$

$$A_v = \frac{(\beta + 1)R_E/Z_b}{1 + \frac{R_E}{r_o}}$$

$$r_o \geq 10R_E$$

$$Z_b = \beta r_e + (\beta + 1)R_E$$

$$Z_o = r_o \parallel R_E \parallel r_e$$

$$A_v \cong \frac{\beta R_E}{Z_b}$$

$$Z_b \cong \beta(r_e + R_E)$$

$r_o \geq 10R_E$

$$Z_o \cong R_E \parallel r_e$$

Any r_o

$$Z_b \cong \beta(r_e + R_E)$$

$$A_v \cong \frac{\beta R_E}{\beta(r_e + R_E)}$$

$$Z_o \cong r_e$$

$$A_v \cong \frac{R_E}{r_e + R_E}$$

$r_o \geq 10R_E$

Emitter Follower Configuration (Example (wo/ro))

EXAMPLE 5.7 For the emitter-follower network of Fig. 5.39, determine:

- r_e .
- Z_i .
- Z_o .
- A_v .
- Repeat parts (b) through (d) with $r_o = 25 \text{ k}\Omega$ and compare results.

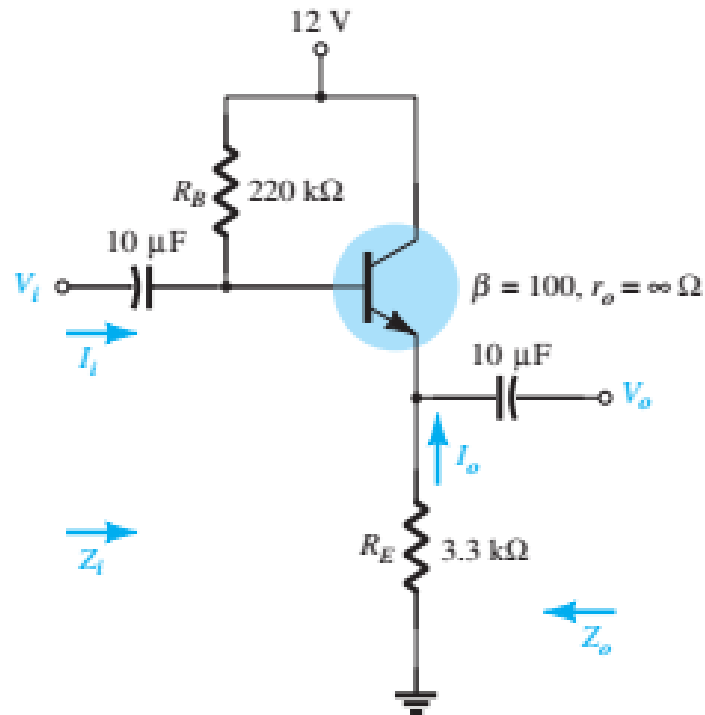


FIG. 5.39

Solution:

$$\begin{aligned} \text{a. } I_B &= \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_E} \\ &= \frac{12 \text{ V} - 0.7 \text{ V}}{220 \text{ k}\Omega + (101)3.3 \text{ k}\Omega} = 20.42 \mu\text{A} \end{aligned}$$

$$\begin{aligned} I_E &= (\beta + 1)I_B \\ &= (101)(20.42 \mu\text{A}) = 2.062 \text{ mA} \end{aligned}$$

$$r_e = \frac{26 \text{ mV}}{I_E} = \frac{26 \text{ mV}}{2.062 \text{ mA}} = 12.61 \Omega$$

$$\begin{aligned} \text{b. } Z_b &= \beta r_e + (\beta + 1)R_E \\ &= (100)(12.61 \Omega) + (101)(3.3 \text{ k}\Omega) \\ &= 1.261 \text{ k}\Omega + 333.3 \text{ k}\Omega \\ &= 334.56 \text{ k}\Omega \cong \beta R_E \end{aligned}$$

$$\begin{aligned} Z_i &= R_B \parallel Z_b = 220 \text{ k}\Omega \parallel 334.56 \text{ k}\Omega \\ &= 132.72 \text{ k}\Omega \end{aligned}$$

$$\begin{aligned} \text{c. } Z_o &= R_E \parallel r_e = 3.3 \text{ k}\Omega \parallel 12.61 \Omega \\ &= 12.56 \Omega \cong r_e \end{aligned}$$

$$\begin{aligned} \text{d. } A_v &= \frac{V_o}{V_i} = \frac{R_E}{R_E + r_e} = \frac{3.3 \text{ k}\Omega}{3.3 \text{ k}\Omega + 12.61 \Omega} \\ &= 0.996 \cong 1 \end{aligned}$$

Emitter Follower Configuration (Example w/ro)

e. Checking the condition $r_o \geq 10R_E$, we have

$$25 \text{ k}\Omega \geq 10(3.3 \text{ k}\Omega) = 33 \text{ k}\Omega$$

which is *not* satisfied. Therefore,

$$\begin{aligned} Z_b &= \beta r_e + \frac{(\beta + 1)R_E}{1 + \frac{R_E}{r_o}} = (100)(12.61 \text{ }\Omega) + \frac{(100 + 1)3.3 \text{ k}\Omega}{1 + \frac{3.3 \text{ k}\Omega}{25 \text{ k}\Omega}} \\ &= 1.261 \text{ k}\Omega + 294.43 \text{ k}\Omega \\ &= 295.7 \text{ k}\Omega \end{aligned}$$

with $Z_i = R_B \parallel Z_b = 220 \text{ k}\Omega \parallel 295.7 \text{ k}\Omega$
 $= \mathbf{126.15 \text{ k}\Omega}$ vs. $132.72 \text{ k}\Omega$ obtained earlier

$$Z_o = R_E \parallel r_e = \mathbf{12.56 \text{ }\Omega}$$
 as obtained earlier

$$\begin{aligned} A_v &= \frac{(\beta + 1)R_E/Z_b}{\left[1 + \frac{R_E}{r_o}\right]} = \frac{(100 + 1)(3.3 \text{ k}\Omega)/295.7 \text{ k}\Omega}{\left[1 + \frac{3.3 \text{ k}\Omega}{25 \text{ k}\Omega}\right]} \\ &= \mathbf{0.996 \cong 1} \end{aligned}$$

matching the earlier result.

Emitter Follower Configuration (Diff. Biasing)

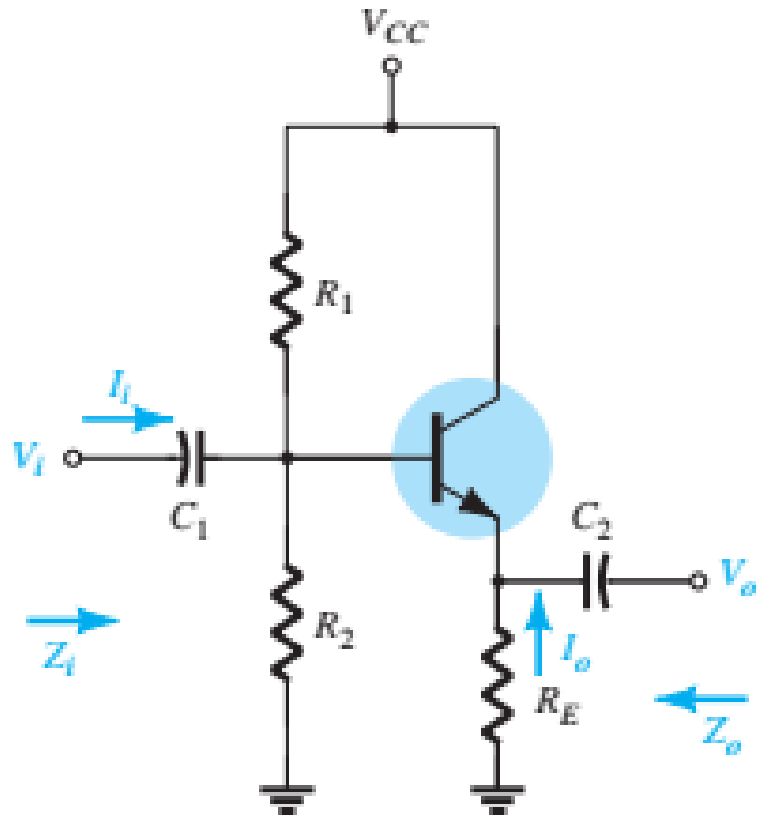


FIG. 5.40

Emitter-follower configuration with a voltage-divider biasing arrangement.

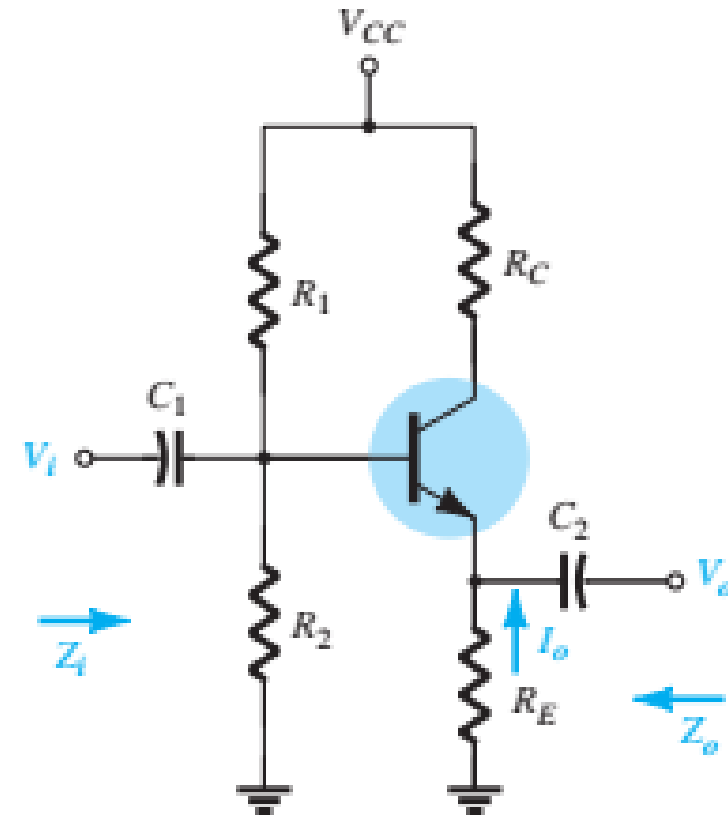


FIG. 5.41

Emitter-follower configuration with a collector resistor R_C .

Thank You!

