

# ECE 312


# Electronic Circuits (A)

Lec. 3: BJT Circuits & Troubleshooting

Instructor

**Dr. Maher Abdelrasoul**

# Outline

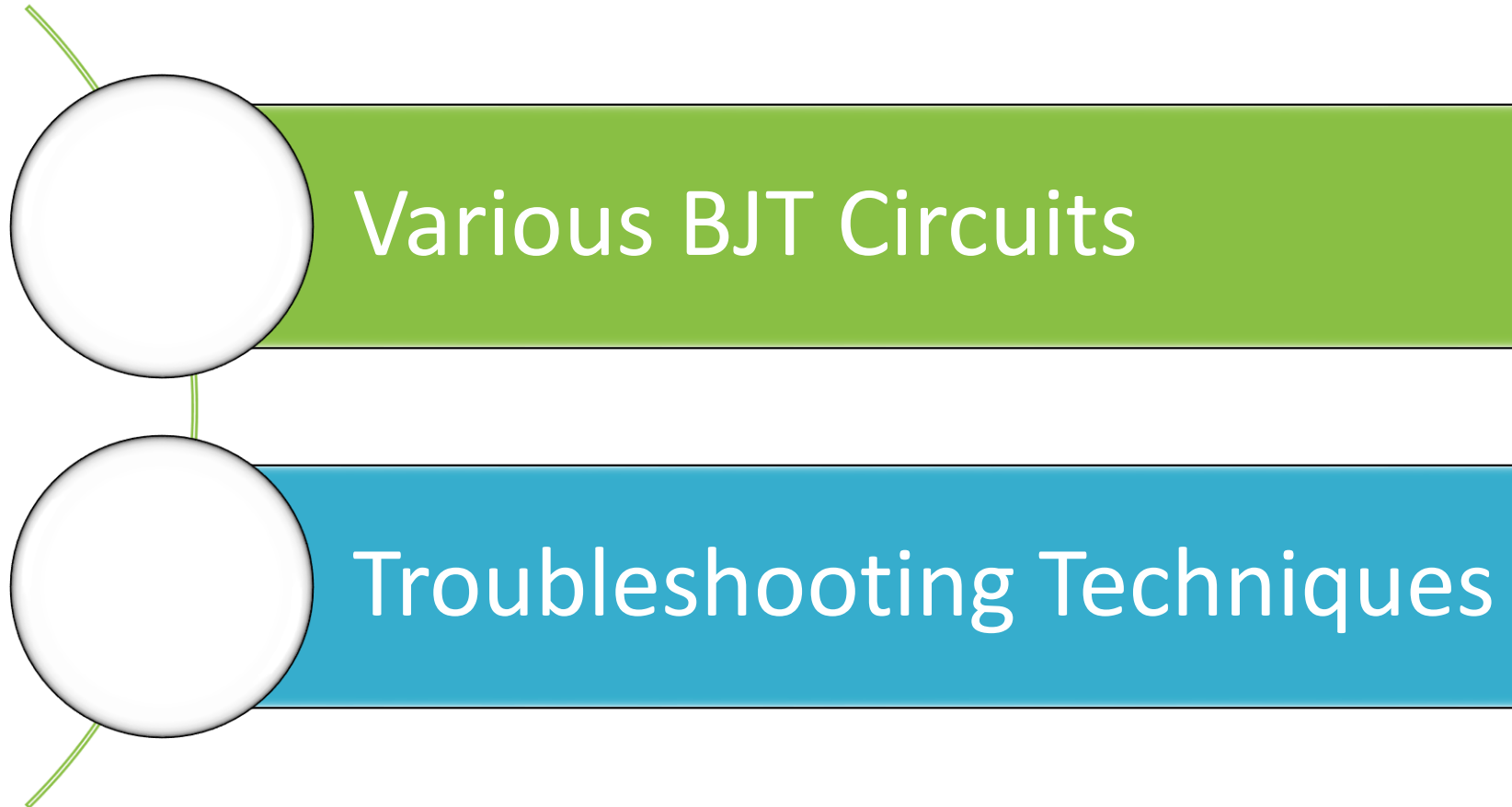


# Various BJT Circuits

- MULTIPLE BJT NETWORKS
- CURRENT MIRRORS
- CURRENT SOURCE CIRCUITS
  - Bipolar Transistor Constant-Current Source
  - Transistor/Zener Constant-Current Source
- PNP TRANSISTORS
- TRANSISTOR SWITCHING NETWORKS


# Multiple BJT Networks (1 of 5)

- R-C coupling

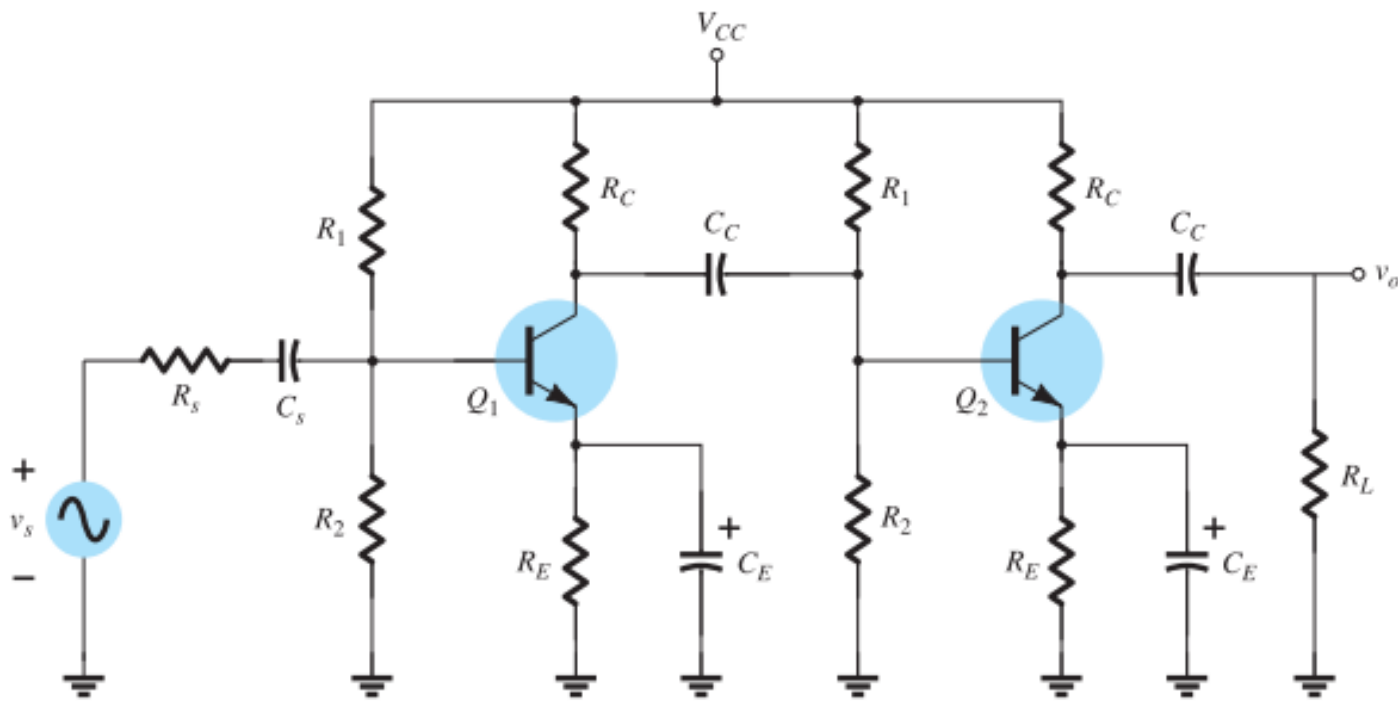

**FIG. 4.64**

*R-C coupled BJT amplifiers.*

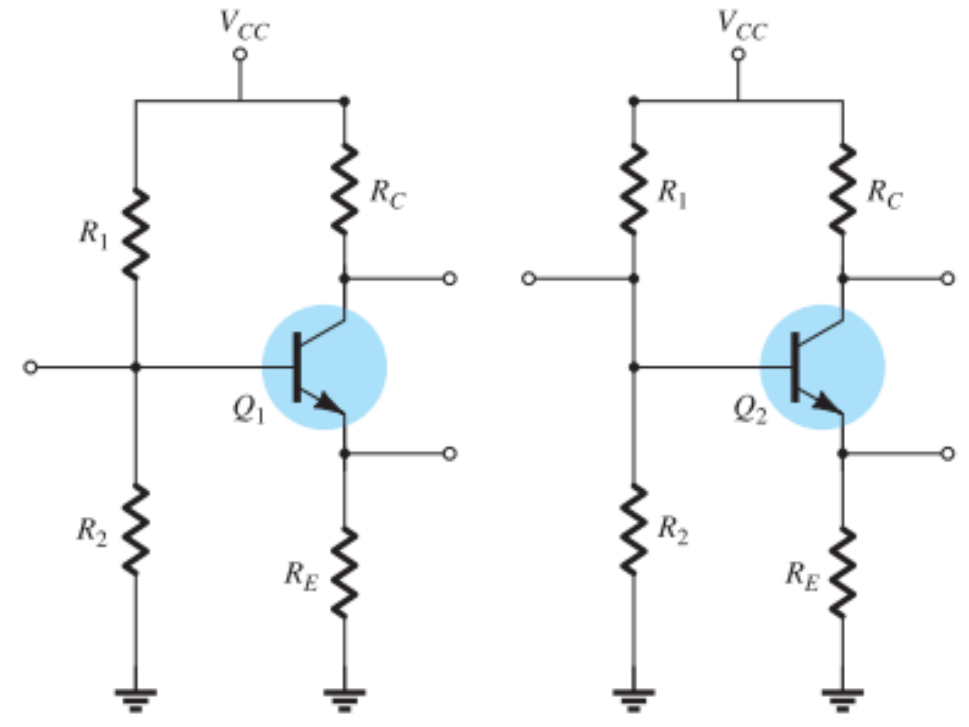


**FIG. 4.65**


*DC equivalent of Fig. 4.64.*

# Multiple BJT Networks (2 of 5)<sub>1</sub>

- Direct Coupled

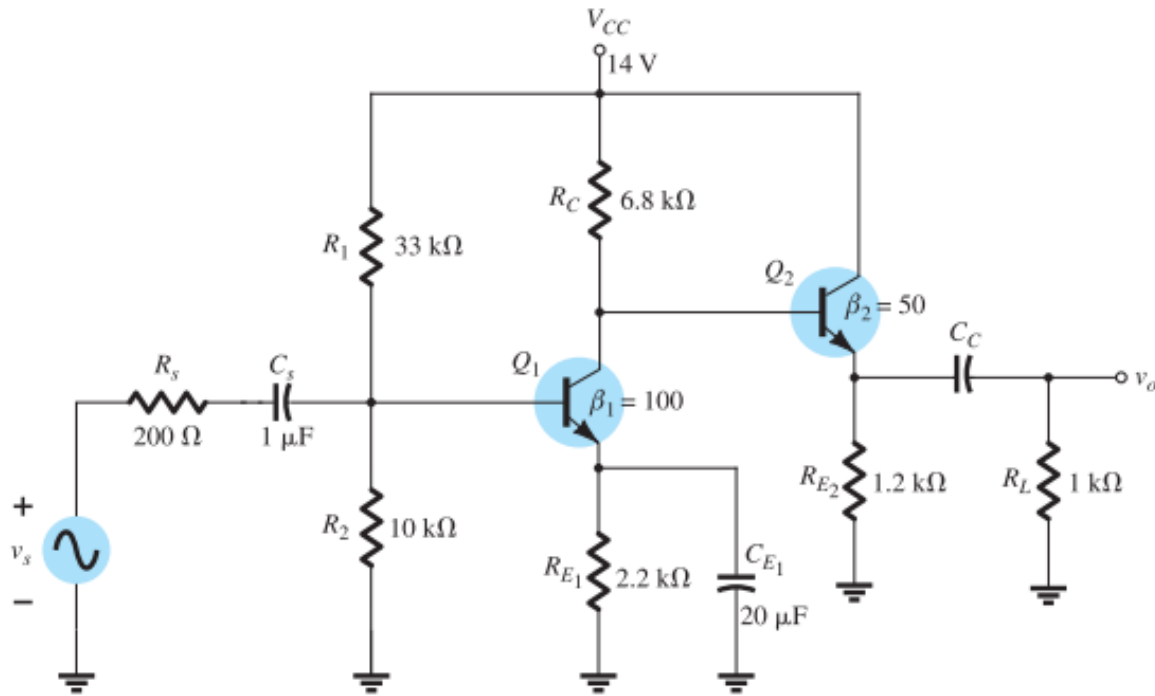

**FIG. 4.72**  
Direct-coupled amplifier.

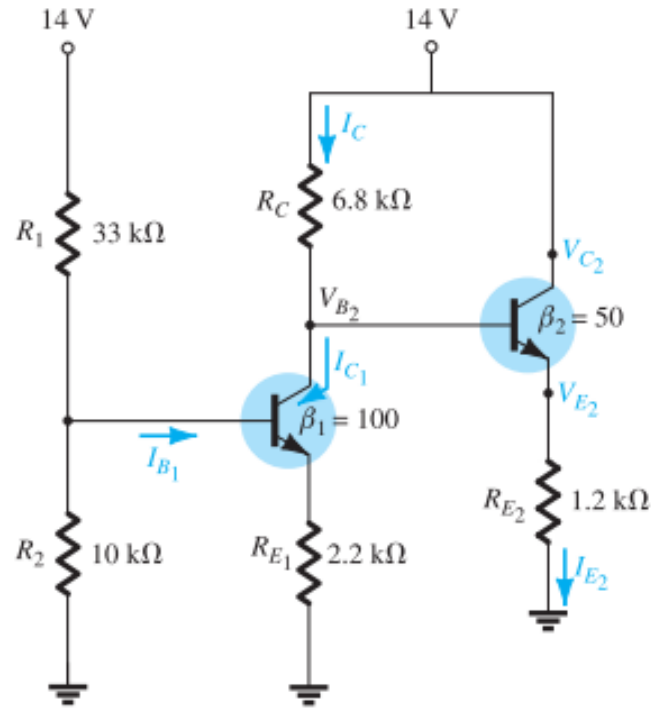

**FIG. 4.73**  
DC equivalent of Fig. 4.72.

$$I_{B1} = \frac{E_{Th} - V_{BE}}{R_{Th} + (\beta + 1)R_{E1}}$$

$$R_{Th} = R_1 \parallel R_2$$

$$E_{Th} = \frac{R_2 V_{CC}}{R_1 + R_2}$$

$$V_{B2} = V_{CC} - I_C R_C$$

$$V_{E2} = V_{B2} - V_{BE2}$$

$$I_{E2} = \frac{V_{E2}}{R_{E2}}$$

$$V_{C2} = V_{CC}$$

$$V_{CE2} = V_{C2} - V_{E2}$$

$$V_{CE2} = V_{CC} - V_{E2}$$

# Multiple BJT Networks (2 of 5)<sub>2</sub>

In this case,

$$R_{Th} = 33 \text{ k}\Omega \parallel 10 \text{ k}\Omega = 7.67 \text{ k}\Omega$$

and

$$E_{Th} = \frac{10 \text{ k}\Omega(14 \text{ V})}{10 \text{ k}\Omega + 33 \text{ k}\Omega} = 3.26 \text{ V}$$

so that

$$I_{B_1} = \frac{3.26 \text{ V} - 0.7 \text{ V}}{7.67 \text{ k}\Omega + (100 + 1) 2.2 \text{ k}\Omega}$$

$$= \frac{2.56 \text{ V}}{229.2 \text{ k}\Omega}$$

$$= \mathbf{11.17 \mu A}$$

with

$$I_{C_1} = \beta I_{B_1}$$
$$= 100 (11.17 \mu A)$$

$$= \mathbf{1.12 \text{ mA}}$$

In Fig. 4.73 we find that

$$V_{B_2} = V_{CC} - I_{C_1} R_C$$

$$= 14 \text{ V} - (1.12 \text{ mA})(6.8 \text{ k}\Omega)$$

$$= 14 \text{ V} - 7.62 \text{ V}$$

$$= \mathbf{6.38 \text{ V}}$$

and

$$V_{E_2} = V_{B_2} - V_{BE_2}$$
$$= 6.38 \text{ V} - 0.7 \text{ V}$$
$$= \mathbf{5.68 \text{ V}}$$

resulting in

$$I_{E_2} = \frac{V_{E_2}}{R_{E_2}}$$

$$= \frac{5.68 \text{ V}}{1.2 \text{ k}\Omega}$$

$$= \mathbf{4.73 \text{ mA}}$$

Obviously,

$$V_{C_2} = V_{CC}$$

$$= 14 \text{ V}$$

and

$$V_{CE_2} = V_{C_2} - V_{E_2}$$

$$V_{CE_2} = V_{CC} - V_{E_2}$$

$$= 14 \text{ V} - 5.68 \text{ V}$$

$$= \mathbf{8.32 \text{ V}}$$

# Multiple BJT Networks (3 of 5)

- Cascode configuration

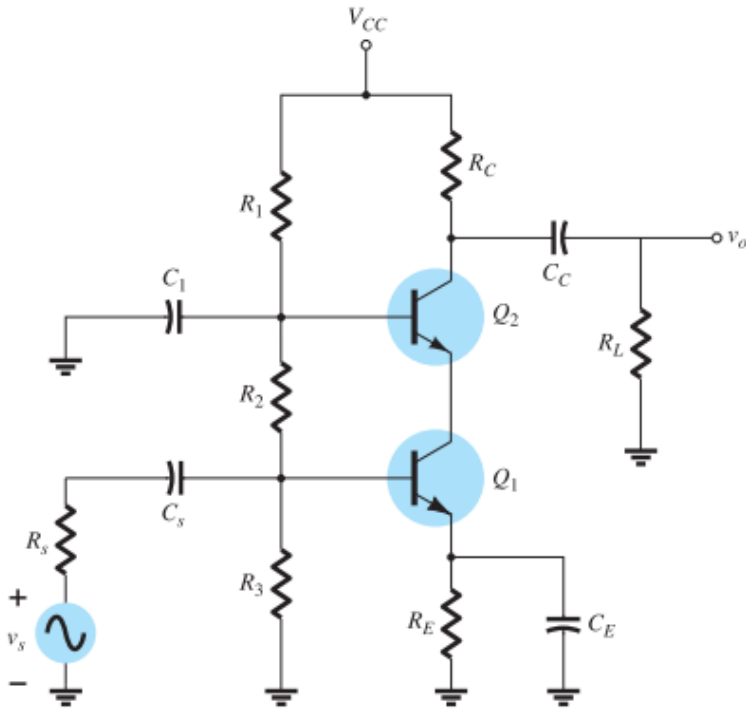


FIG. 4.68  
Cascode amplifier.

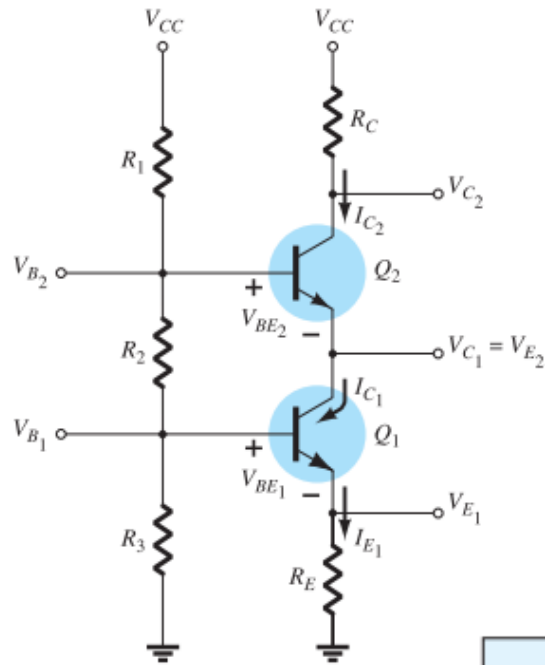


FIG. 4.69  
DC equivalent of Fig. 4.68.

$$I_{R_1} \cong I_{R_2} \cong I_{R_3} \gg I_{B_1} \text{ or } I_{B_2}$$

$$V_{B_1} = \frac{R_3}{R_1 + R_2 + R_3} V_{CC}$$

$$V_{B_2} = \frac{(R_2 + R_3)}{R_1 + R_2 + R_3} V_{CC}$$

$$V_{E_1} = V_{B_1} - V_{BE_1}$$

$$V_{E_2} = V_{B_2} - V_{BE_2}$$

$$I_{C_2} \cong I_{E_2} \cong I_{C_1} \cong I_{E_1} = \frac{V_{B_1} - V_{BE_1}}{R_{E_1} + R_{E_2}}$$

$$V_{C_1} = V_{B_2} - V_{BE_2}$$

$$V_{C_2} = V_{CC} - I_{C_2} R_C$$

$$I_{R_1} \cong I_{R_2} \cong I_{R_3} = \frac{V_{CC}}{R_1 + R_2 + R_3}$$


$$I_{B_2} = \frac{I_{C_2}}{\beta_2}$$

$$I_{B_1} = \frac{I_{C_1}}{\beta_1}$$


$R_E$

# Multiple BJT Networks (4 of 5)

- Darlington configuration

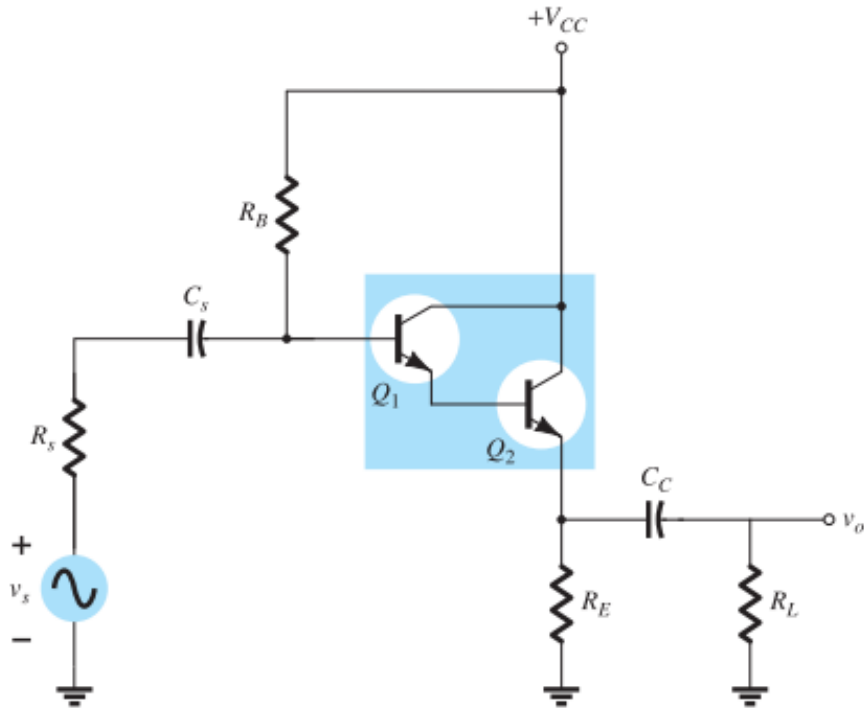

**FIG. 4.66**  
Darlington amplifier.

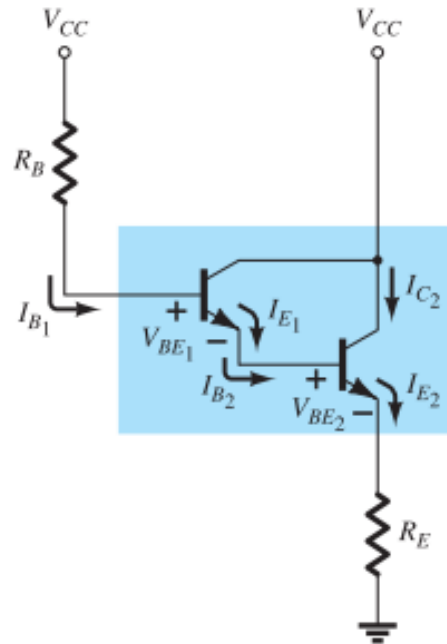

**FIG. 4.67**  
DC equivalent of Fig. 4.66.

$$I_{B1} = \frac{V_{CC} - V_{BE1} - V_{BE2}}{R_B + (\beta_D + 1)R_E}$$

$$V_{BE_D} = V_{BE1} + V_{BE2}$$

$$I_{B1} = \frac{V_{CC} - V_{BE_D}}{R_B + (\beta_D + 1)R_E}$$

$$I_{C2} \cong I_{E2} = \beta_D I_{B1}$$

$$\beta_D = \beta_1 \beta_2$$

$$V_{E2} = I_{E2} R_E$$

$$V_{C2} = V_{CC}$$


$$V_{CE2} = V_{C2} - V_{E2}$$

$$V_{CE2} = V_{CC} - V_{E2}$$




# Multiple BJT Networks (5 of 5)

- Feedback Pair

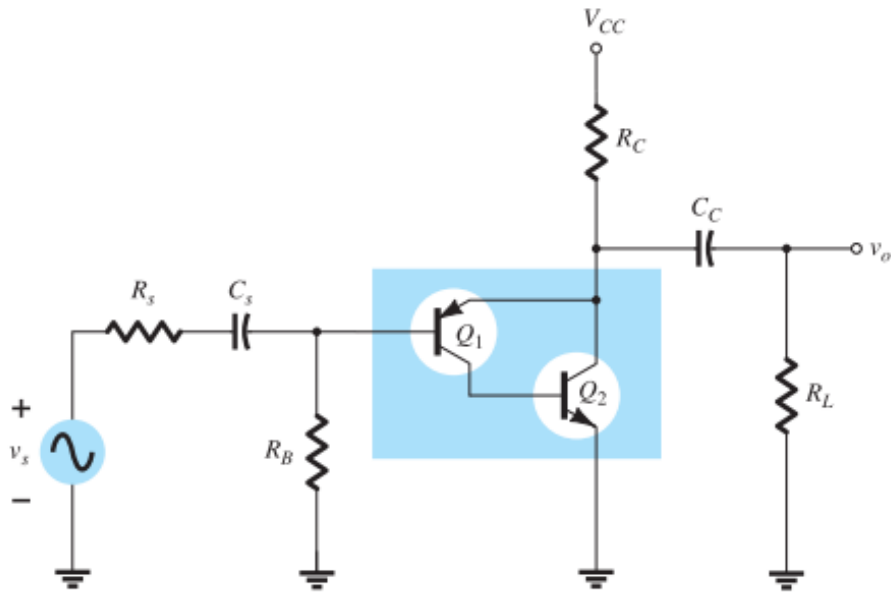

**FIG. 4.70**  
Feedback Pair amplifier.

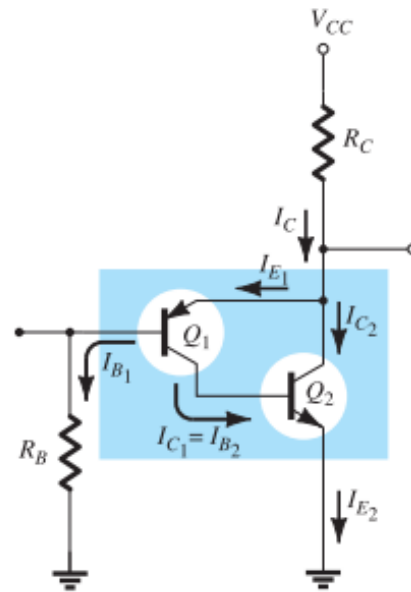

**FIG. 4.71**  
DC equivalent of Fig. 4.70.

$$I_{B_2} = I_{C_1} = \beta_1 I_{B_1}$$

$$I_{C_2} = \beta_2 I_{B_2}$$

$$I_{C_2} \cong I_{E_2} = \beta_1 \beta_2 I_{B_1}$$

$$I_C = I_{E_1} + I_{E_2}$$

$$\cong \beta_1 I_{B_1} + \beta_1 \beta_2 I_{B_1}$$

$$= \beta_1 (1 + \beta_2) I_{B_1}$$

$$I_C \cong \beta_1 \beta_2 I_{B_1}$$

$$V_{CC} - I_C R_C - V_{EB_1} - I_{B_1} R_B = 0$$

$$V_{CC} - V_{EB_1} - \beta_1 \beta_2 I_{B_1} R_C - I_{B_1} R_B = 0$$

$$I_{B_1} = \frac{V_{CC} - V_{EB_1}}{R_B + \beta_1 \beta_2 R_C}$$

$$V_{B_1} = I_{B_1} R_B$$

$$V_{B_2} = V_{BE_2}$$

$$V_{C_2} = V_{CC} - I_C R_C$$


$$V_{C_1} = V_{BE_2}$$

$$V_{CE_2} = V_{C_2}$$

$$V_{EC_1} = V_{E_1} - V_{C_1}$$


$$V_{EC_1} = V_{C_2} - V_{BE_2}$$

# Current Mirrors (1 of 2)

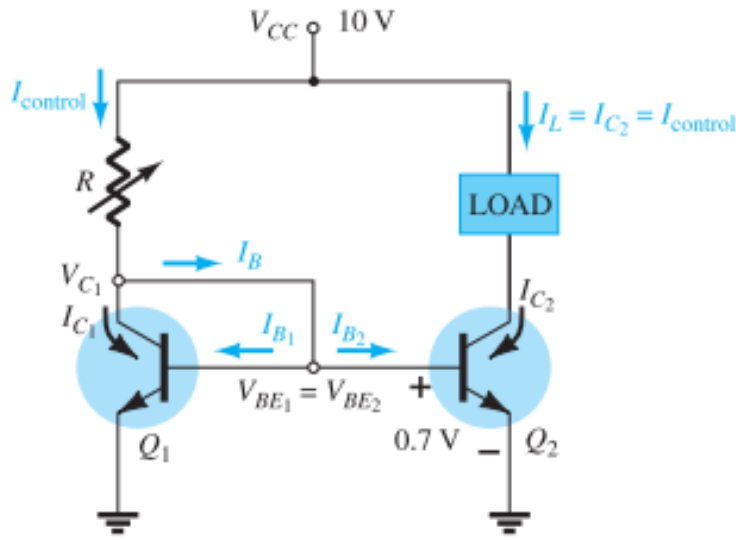

**FIG. 4.74**

Current mirror using back-to-back BJTs.

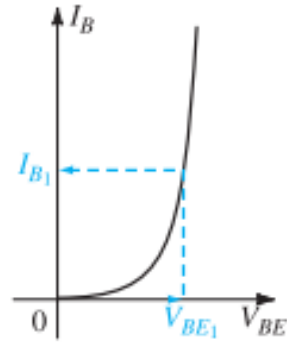

**FIG. 4.75**

Base characteristics for transistor  $Q_1$  (and  $Q_2$ ).

$$I_{\text{control}} = \frac{V_{CC} - V_{BE}}{R}$$

$$I_{\text{control}} = I_{C_1} + I_B = I_{C_1} + 2I_{B_1}$$

$$I_{C_1} = \beta_1 I_{B_1}$$

$$I_{\text{control}} = \beta_1 I_{B_1} + 2I_{B_1} = (\beta_1 + 2)I_{B_1}$$


$\beta_1$  is typically  $\gg 2$ ,  $I_{\text{control}} \cong \beta_1 I_{B_1}$

$$I_{B_1} = \frac{I_{\text{control}}}{\beta_1}$$

$$I_L = I_{C_2} = \beta I_{B_2}$$

$I_L \uparrow, I_{C_2} \uparrow, I_{B_2} \uparrow, V_{BE_2} \uparrow, V_{CE_1} \uparrow, I_R \downarrow, I_B \downarrow, I_{B_1} \downarrow, I_{C_1} \downarrow, I_L \downarrow$   
 Note

# Current Mirrors (2 of 2)

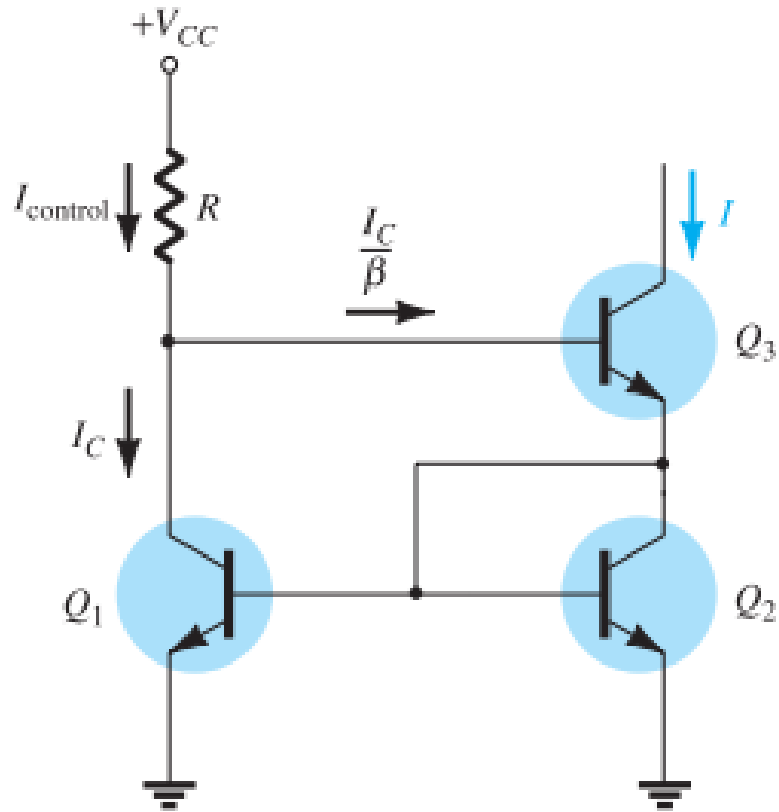


**FIG. 4.78**

*Current mirror circuit with higher output impedance.*


$$I_{\text{control}} = \frac{V_{CC} - 2V_{BE}}{R} \approx I_C + \frac{I_C}{\beta} = \frac{\beta + 1}{\beta} I_C \approx I_C$$

$$I \approx I_C = I_{\text{control}}$$

# Current Source Circuits (1 of 2)

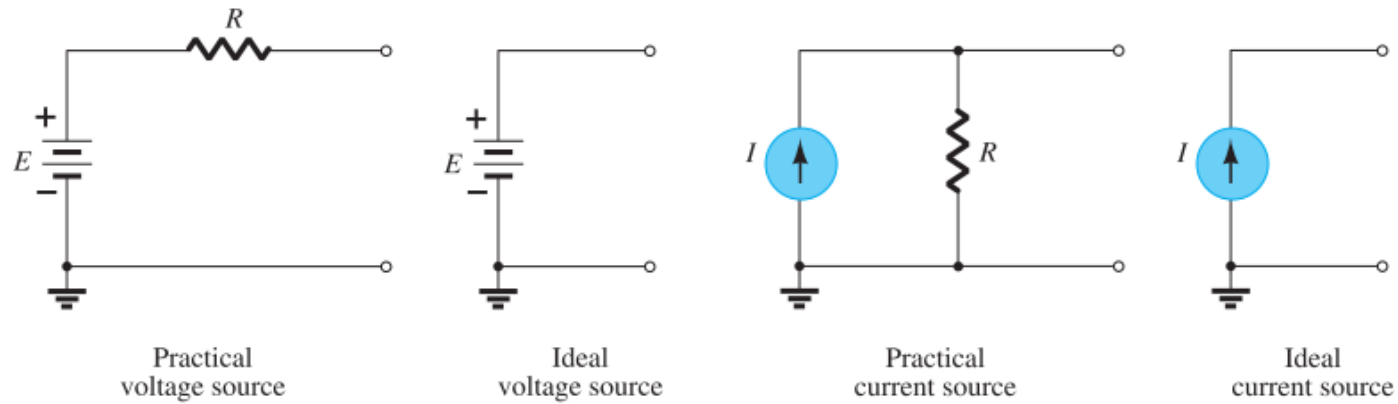
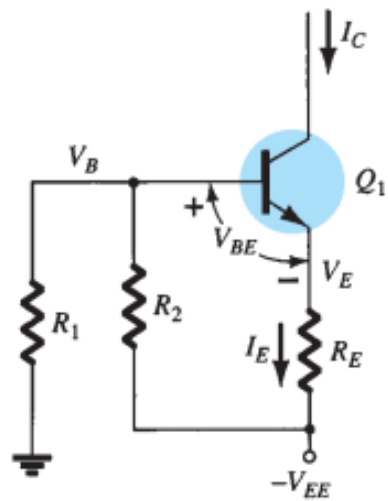
## Bipolar Transistor Constant-Current Source



$$V_B = \frac{R_1}{R_1 + R_2} (-V_{EE})$$


$$V_E = V_B - 0.7 \text{ V}$$

$$I_E = \frac{V_E - (-V_{EE})}{R_E} \approx I_C$$

**FIG. 4.81**

Discrete constant-current source.
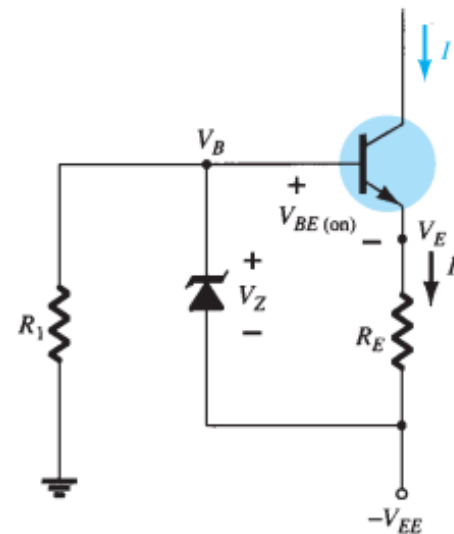
## Transistor/Zener Constant-Current Source




$$I \approx I_E = \frac{V_Z - V_{BE}}{R_E}$$

**FIG. 4.83**

Constant-current circuit using Zener diode.

# Current Source Circuits (2 of 2)

**EXAMPLE 4.30** Calculate the constant current  $I$  in the circuit of Fig. 4.84.

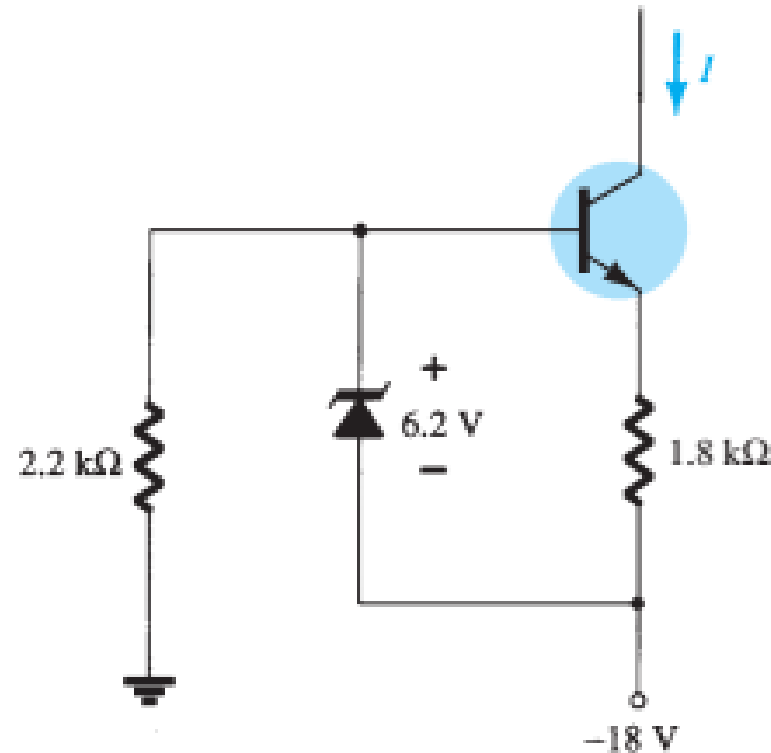

**FIG. 4.84**

*Constant-current circuit for Example 4.30.*

**Solution:**

$$\text{Eq. (4.83): } I = \frac{V_Z - V_{BE}}{R_E} = \frac{6.2 \text{ V} - 0.7 \text{ V}}{1.8 \text{ k}\Omega} = 3.06 \text{ mA} \approx \mathbf{3 \text{ mA}}$$

# PNP Transistors (1 of 2)


- The analysis thus far has been limited totally to *npn* transistors.
- Fortunately, the analysis of *pnp* transistors follows the same pattern established for *npn* transistors.
- In fact, the only difference between the resulting equations for a network in which an *npn* transistor has been replaced by a *pnp* transistor is the sign associated with particular quantities.

$$-I_E R_E + V_{BE} - I_B R_B + V_{CC} = 0$$

$$I_B = \frac{V_{CC} + V_{BE}}{R_B + (\beta + 1)R_E}$$

$$-I_E R_E + V_{CE} - I_C R_C + V_{CC} = 0$$


$$V_{CE} = -V_{CC} + I_C(R_C + R_E)$$

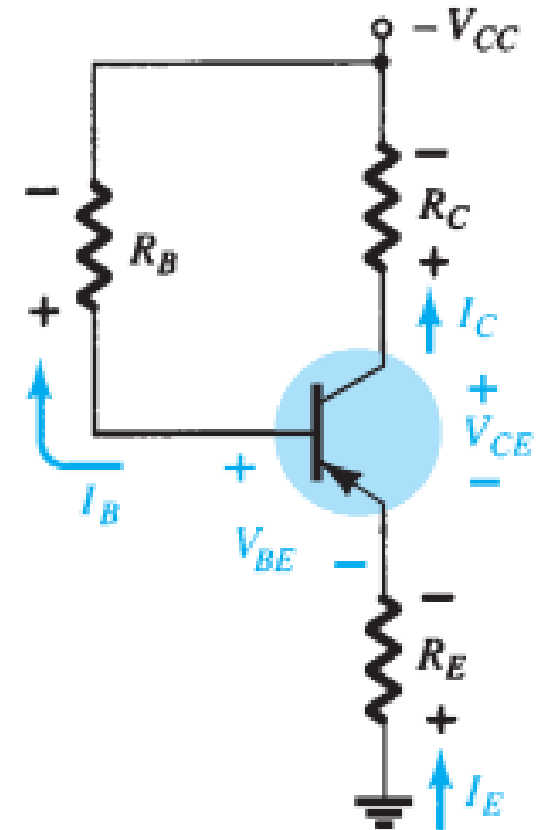

**FIG. 4.85**  
*pnp* transistor in an emitter-stabilized configuration.

# PNP Transistors (2 of 2)

**EXAMPLE 4.31** Determine  $V_{CE}$  for the voltage-divider bias configuration of Fig. 4.86.

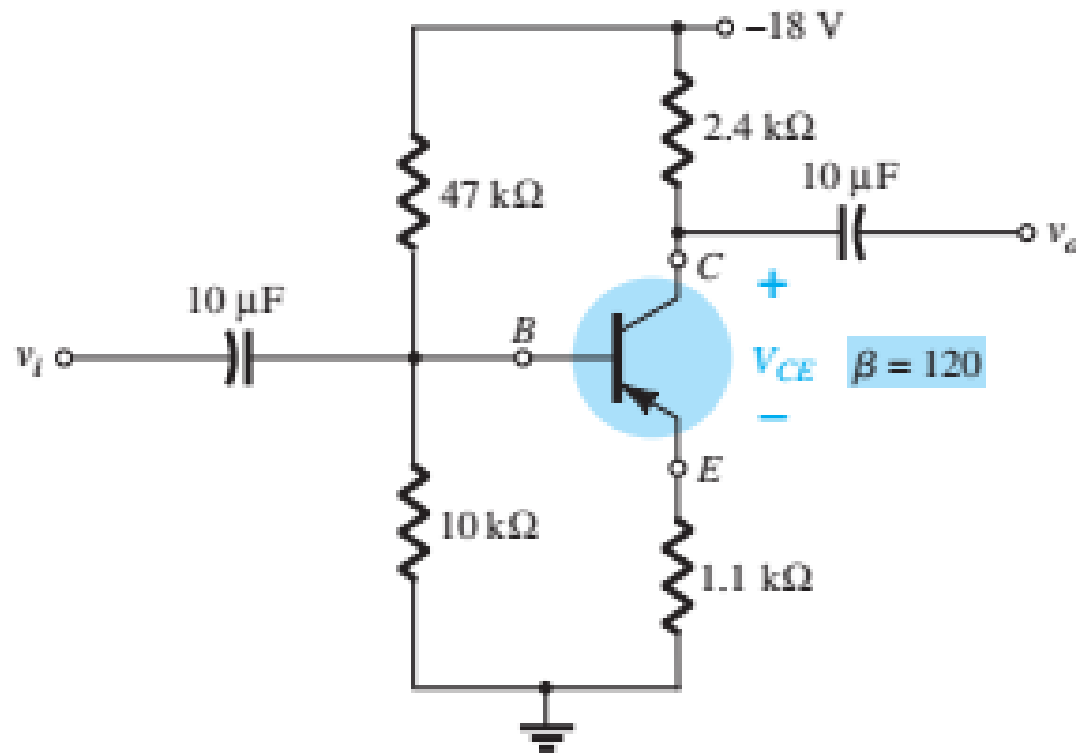


**FIG. 4.86**

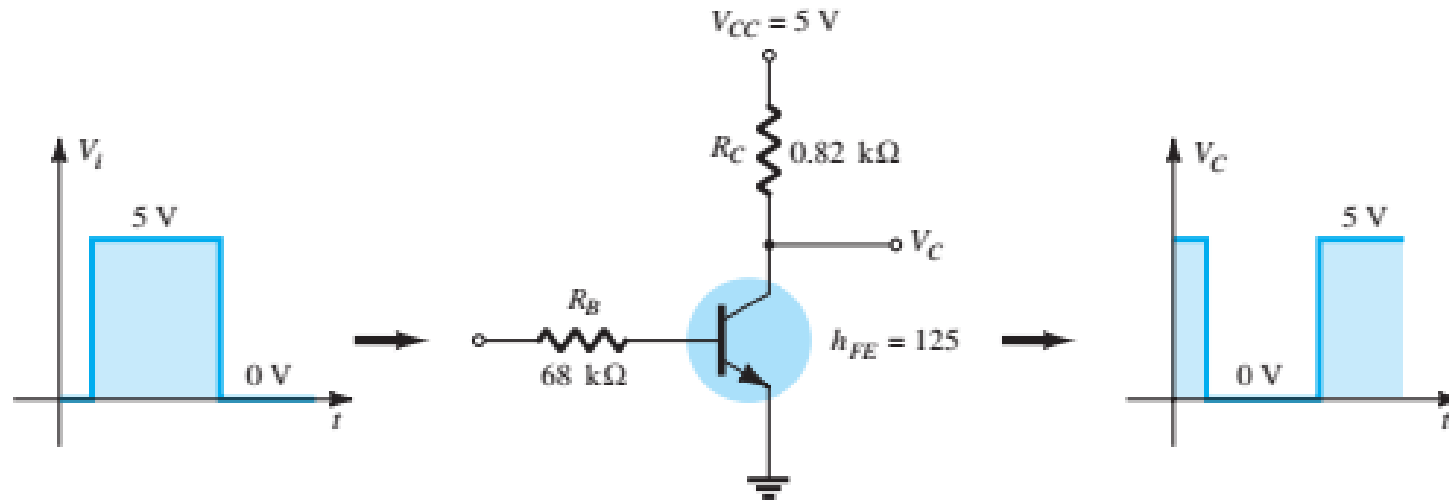*pnp transistor in a voltage-divider bias configuration.*

Write the  
equations  
of solution


# Transistor Switching Networks (1 of 3)



$$I_{C_{\text{sat}}} = \frac{V_{CC}}{R_C}$$

$$I_{B_{\text{max}}} \cong \frac{I_{C_{\text{sat}}}}{\beta_{\text{dc}}}$$

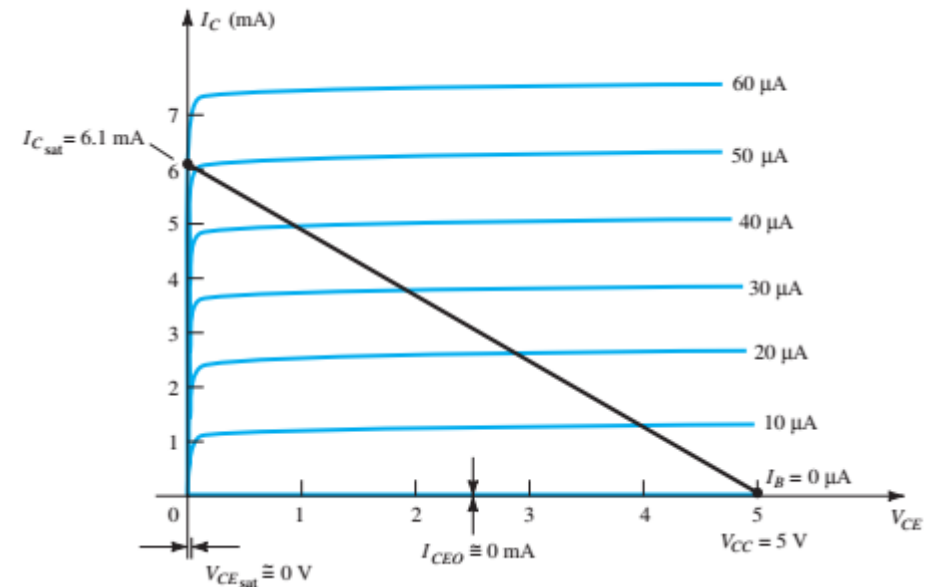
$$I_B > \frac{I_{C_{\text{sat}}}}{\beta_{\text{dc}}}$$





# Transistor Switching Networks (2 of 3)

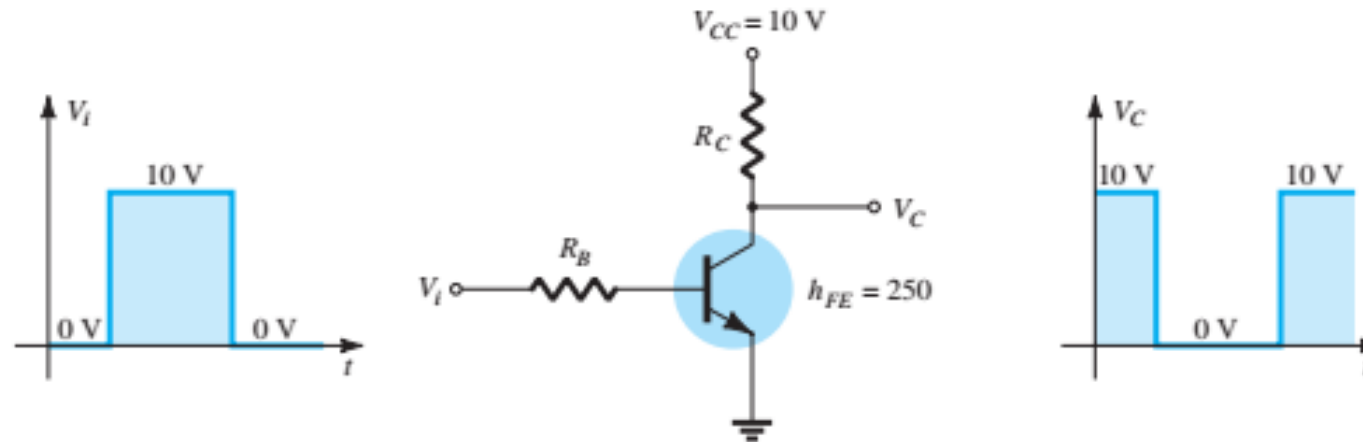**EXAMPLE 4.32** Determine  $R_B$  and  $R_C$  for the transistor inverter of Fig. 4.90 if  $I_{C_{sat}} = 10 \text{ mA}$ .



**Solution:** At saturation,

$$I_{C_{sat}} = \frac{V_{CC}}{R_C}$$

and

$$10 \text{ mA} = \frac{10 \text{ V}}{R_C}$$

so that

$$R_C = \frac{10 \text{ V}}{10 \text{ mA}} = 1 \text{ k}\Omega$$

At saturation,

$$I_B \cong \frac{I_{C_{sat}}}{\beta_{dc}} = \frac{10 \text{ mA}}{250} = 40 \mu\text{A}$$

Choosing  $I_B = 60 \mu\text{A}$  to ensure saturation and using

$$I_B = \frac{V_i - 0.7 \text{ V}}{R_B}$$

we obtain

$$R_B = \frac{V_i - 0.7 \text{ V}}{I_B} = \frac{10 \text{ V} - 0.7 \text{ V}}{60 \mu\text{A}} = 155 \text{ k}\Omega$$

Choose  $R_B = 150 \text{ k}\Omega$ , which is a standard value. Then

$$I_B = \frac{V_i - 0.7 \text{ V}}{R_B} = \frac{10 \text{ V} - 0.7 \text{ V}}{150 \text{ k}\Omega} = 62 \mu\text{A}$$


and

$$I_B = 62 \mu\text{A} > \frac{I_{C_{sat}}}{\beta_{dc}} = 40 \mu\text{A}$$

Therefore, use  $R_B = 150 \text{ k}\Omega$  and  $R_C = 1 \text{ k}\Omega$ .


# Transistor Switching Networks (3 of 3)

$$R_{\text{sat}} = \frac{V_{CE_{\text{sat}}}}{I_{C_{\text{sat}}}}$$

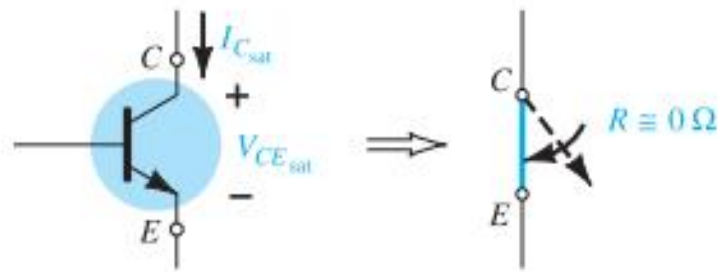

**FIG. 4.88**

*Saturation conditions and the resulting terminal resistance.*

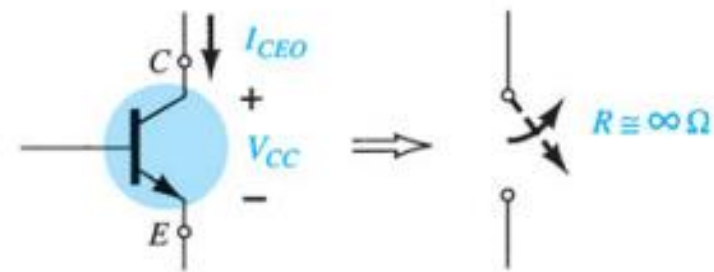

**FIG. 4.89**

*Cutoff conditions and the resulting terminal resistance.*

Using a typical average value of  $V_{CE_{\text{sat}}}$  such as 0.15 V gives


$$R_{\text{sat}} = \frac{V_{CE_{\text{sat}}}}{I_{C_{\text{sat}}}} = \frac{0.15 \text{ V}}{6.1 \text{ mA}} = 24.6 \Omega$$

$$R_{\text{cutoff}} = \frac{V_{CC}}{I_{CEO}} = \frac{5 \text{ V}}{0 \text{ mA}} = \infty \Omega$$

$$R_{\text{cutoff}} = \frac{V_{CC}}{I_{CEO}} = \frac{5 \text{ V}}{10 \mu\text{A}} = 500 \text{ k}\Omega$$


# Troubleshooting Techniques

- For an “on” transistor, the voltage  $V_{BE}$  should be in the neighborhood of 0.7 V.
- For the typical transistor amplifier in the active region,  $V_{CE}$  is usually about 25% to 75% of  $V_{CC}$ .

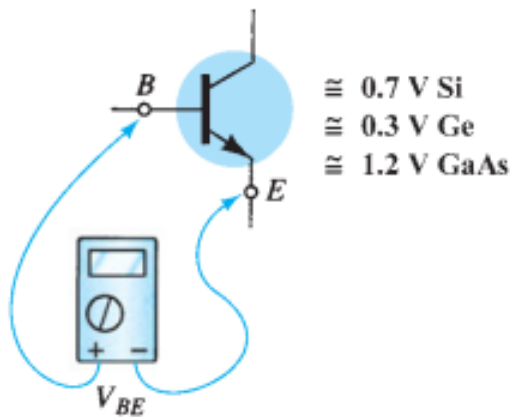


**FIG. 4.92**

Checking the dc level of  $V_{BE}$ .

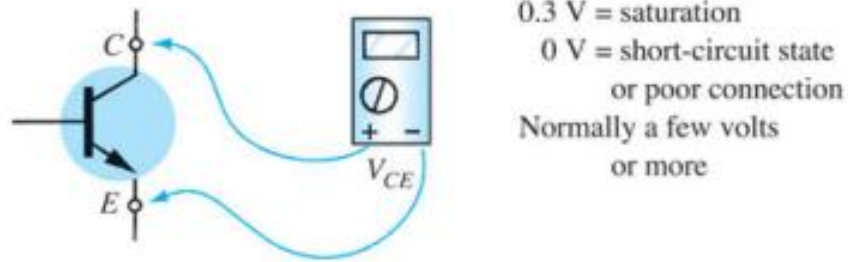


**FIG. 4.93**

Checking the dc level of  $V_{CE}$ .

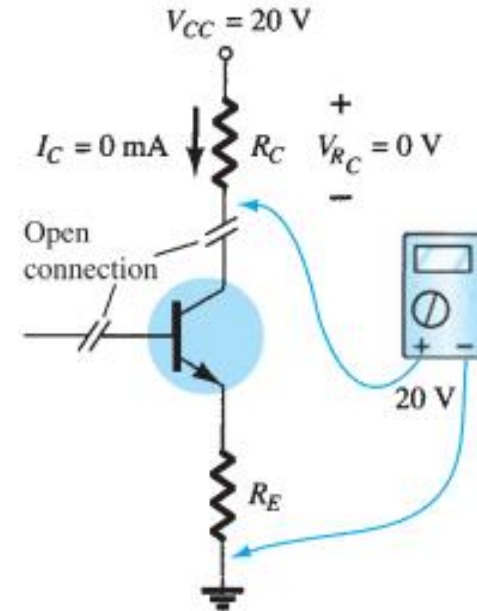

**FIG. 4.94**

Effect of a poor connection or damaged device.

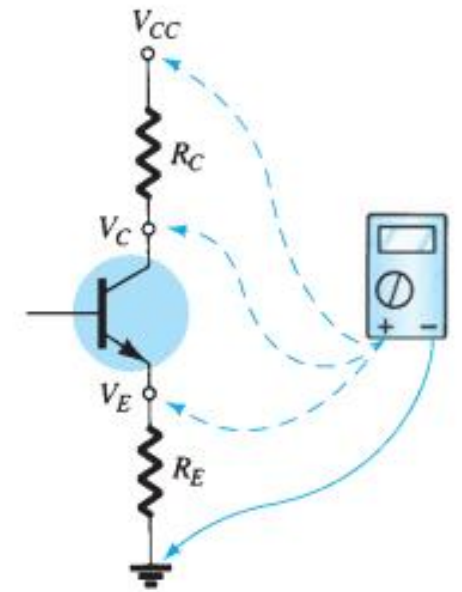

**FIG. 4.95**

Checking voltage levels with respect to ground.

Thank You!

