

ECE 312

Electronic Circuits (A)


Lec. 7: BJT Modeling and re Transistor Model (small signal analysis) (3)

Instructor

Dr. Maher Abdelrasoul

<http://www.bu.edu.eg/staff/mahersalem3>

Agenda

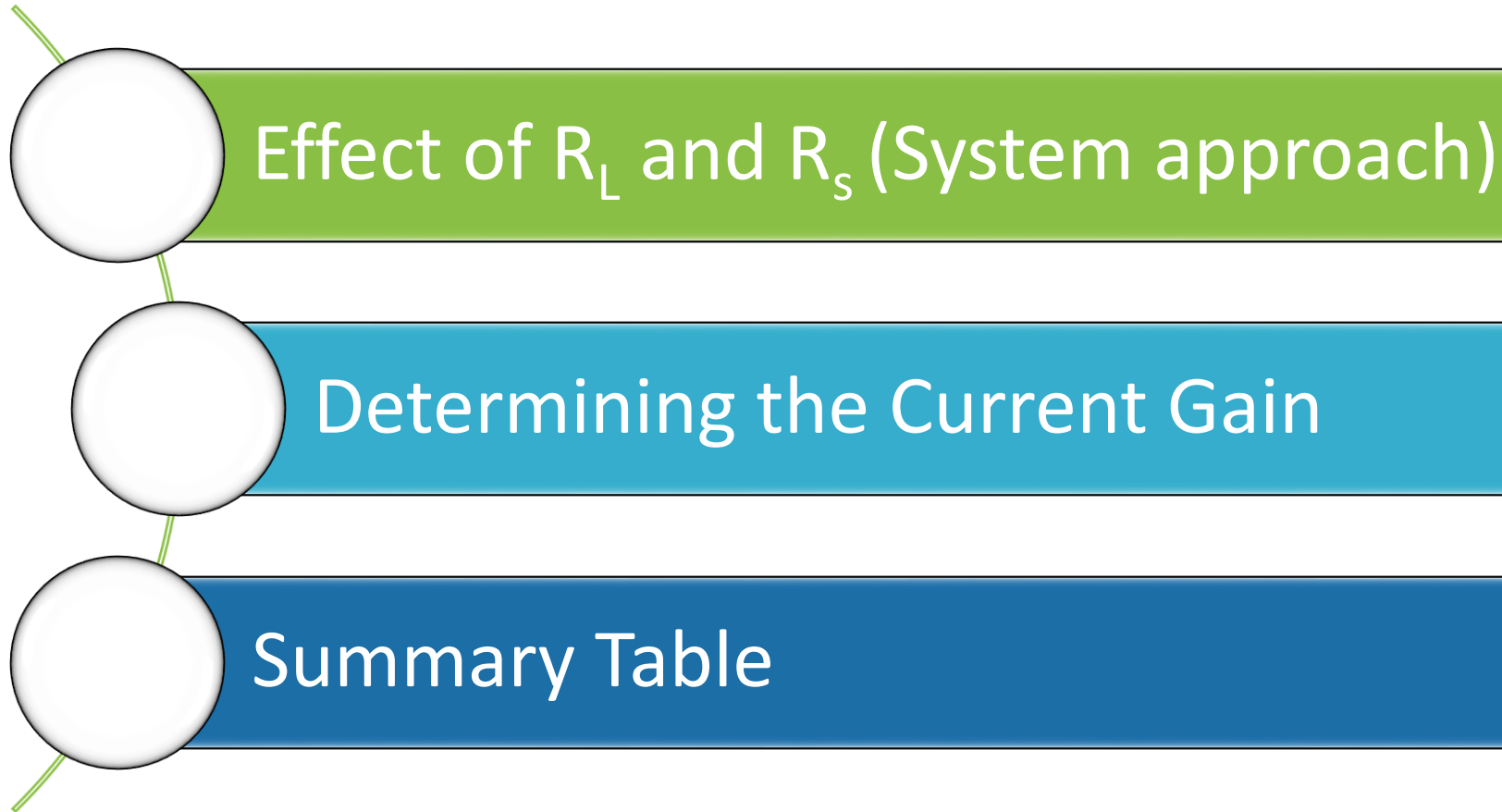- 
- Effect of R_L and R_s (System approach)
 - Determining the Current Gain
 - Summary Table

Effect of R_L and R_S (System Approach)

Effect of R_L and R_S


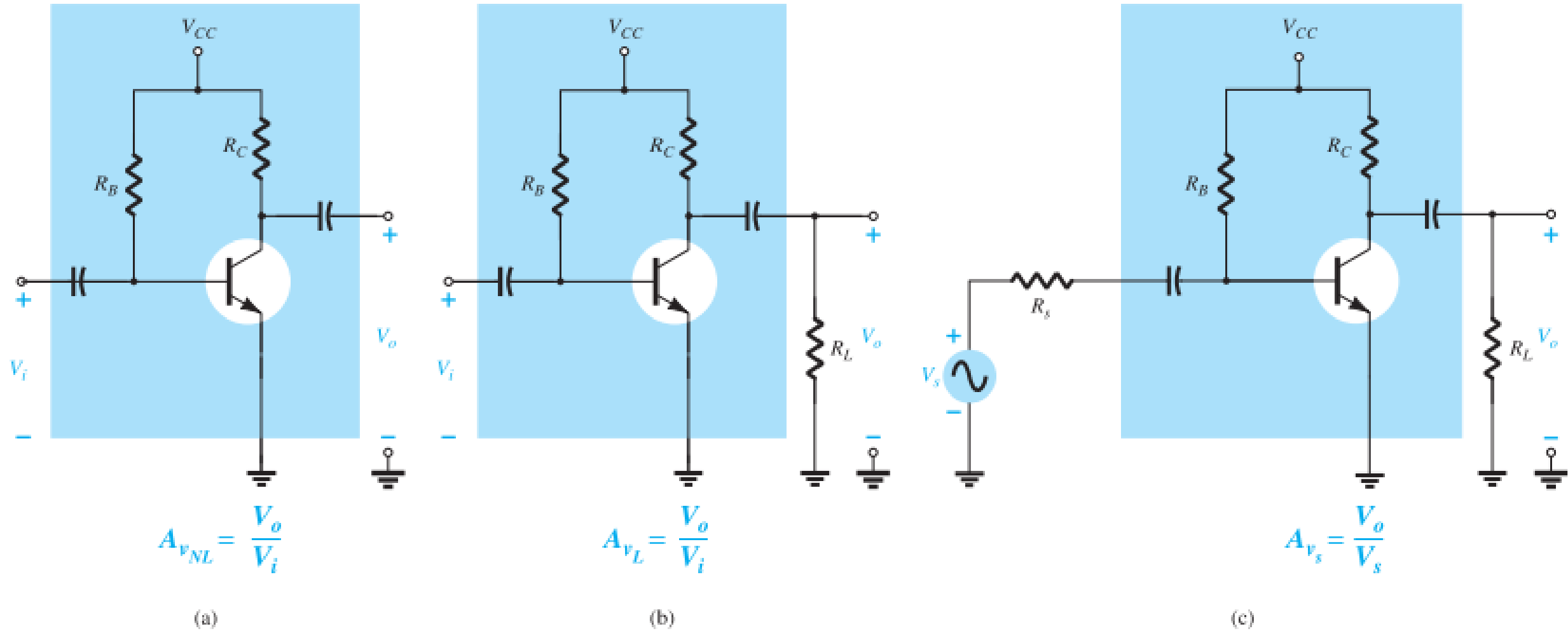


FIG. 5.54

Amplifier configurations: (a) unloaded; (b) loaded; (c) loaded with a source resistance.


Effect of R_L and R_S

- The loaded voltage gain of an amplifier is always less than the no-load gain.
- The gain obtained with a source resistance in place will always be less than that obtained under loaded or unloaded conditions due to the drop in applied voltage across the source resistance.
- For the same configuration $A_{vNL} > A_{vL} > A_{vS}$.
- $R_L \uparrow \rightarrow A_{vS} \uparrow$
- $R_S \downarrow \rightarrow A_{vS} \uparrow$
- For any network that have coupling capacitors, the source and load resistance do not affect the dc biasing levels.

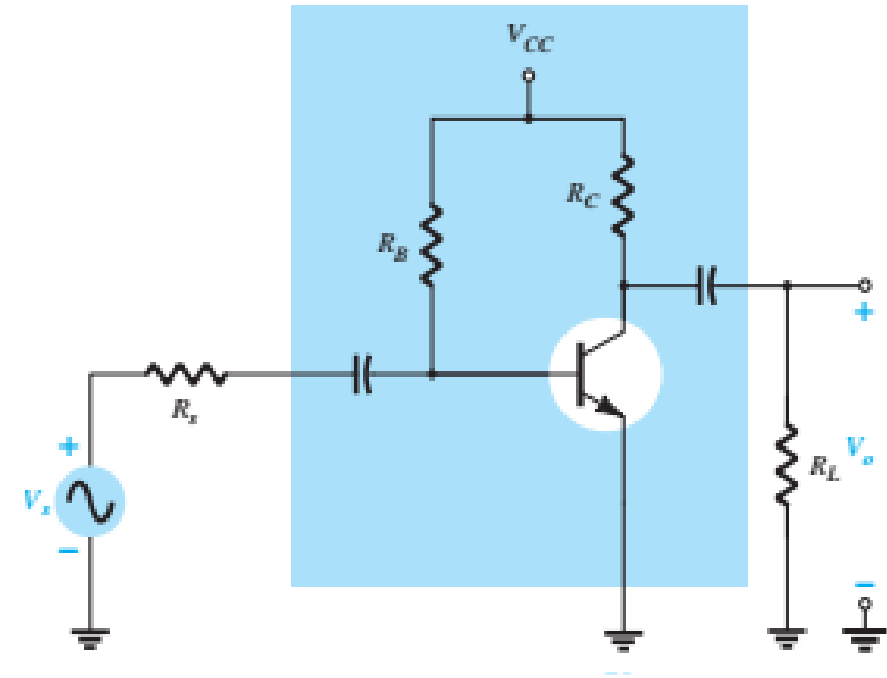

Effect of R_L and R_S on different biasing Circuits (1)

Fixed bias ct.

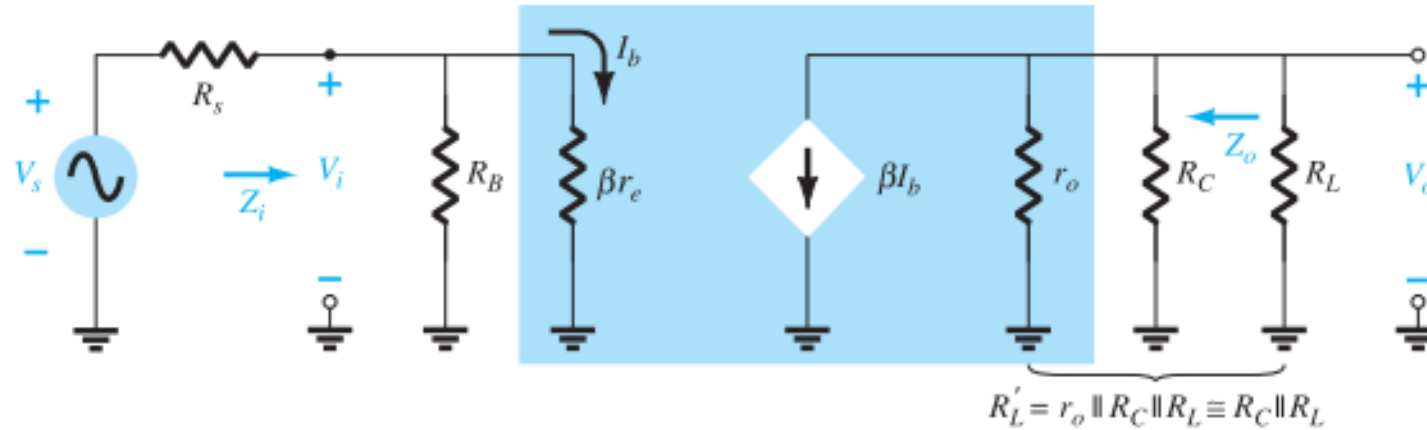

$$R'_L = r_o \parallel R_C \parallel R_L \cong R_C \parallel R_L$$

$$V_o = -\beta I_b R'_L = -\beta I_b (R_C \parallel R_L)$$

$$I_b = \frac{V_i}{\beta r_e}$$

$$V_o = -\beta \left(\frac{V_i}{\beta r_e} \right) (R_C \parallel R_L)$$

$$A_{vL} = \frac{V_o}{V_i} = -\frac{R_C \parallel R_L}{r_e}$$

$$Z_i = R_B \parallel \beta r_e$$

$$Z_o = R_C \parallel r_o$$

$$V_i = \frac{Z_i V_s}{Z_i + R_s}$$


$$\frac{V_i}{V_s} = \frac{Z_i}{Z_i + R_s}$$

$$A_{vS} = \frac{V_o}{V_s} = \frac{V_o}{V_i} \cdot \frac{V_i}{V_s} = A_{vL} \frac{Z_i}{Z_i + R_s}$$

$$A_{vS} = \frac{Z_i}{Z_i + R_s} A_{vL}$$

Effect of R_L and R_S on different biasing Circuits (2)

Voltage-divider ct.

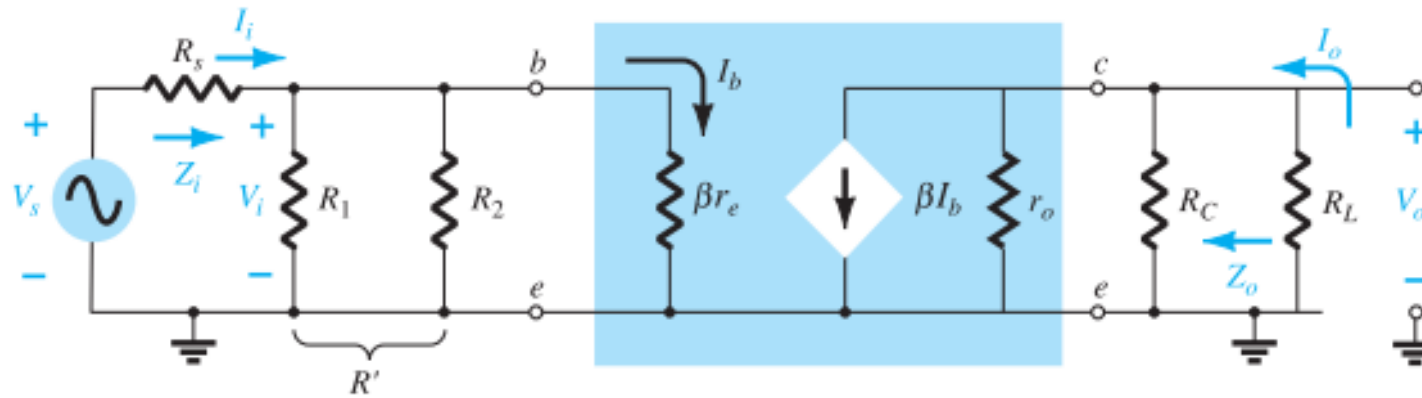


$$A_{vL} = \frac{V_o}{V_i} = -\frac{R_C \parallel R_L}{r_e}$$

$$Z_i = R_1 \parallel R_2 \parallel \beta r_e$$

$$Z_o = R_C \parallel r_o$$

Emitter-Follower Ct.

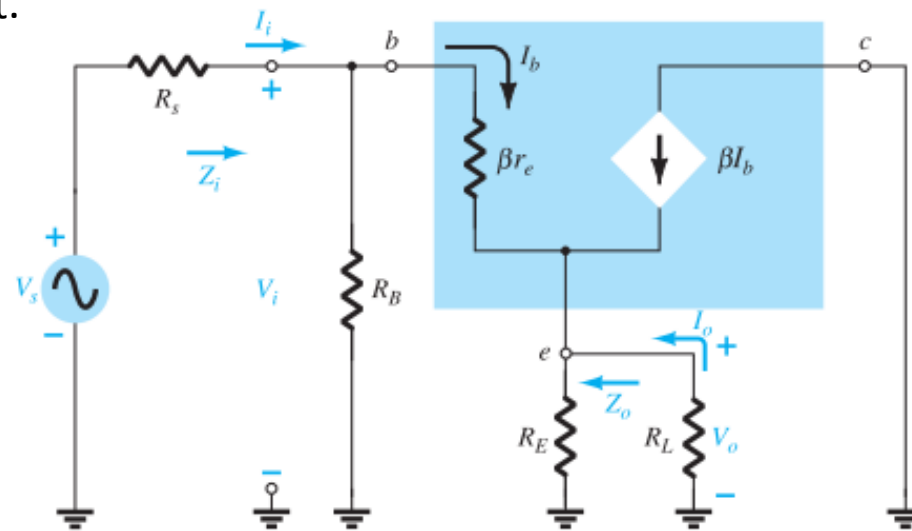

$$Z_i = R_B \parallel Z_b$$

$$Z_b \cong \beta(R_E \parallel R_L)$$


$$Z_o \cong r_e$$

$$A_{vL} = \frac{V_o}{V_i} = \frac{R_E \parallel R_L}{R_E \parallel R_L + r_e}$$

Effect of R_L and R_S (Example)

EXAMPLE 5.11 Using the parameter values for the fixed-bias configuration of Example 5.1 with an applied load of $4.7\text{ k}\Omega$ and a source resistance of $0.3\text{ k}\Omega$, determine the following and compare to the no-load values:

- A_{v_L}
- A_{v_s}
- Z_i
- Z_o

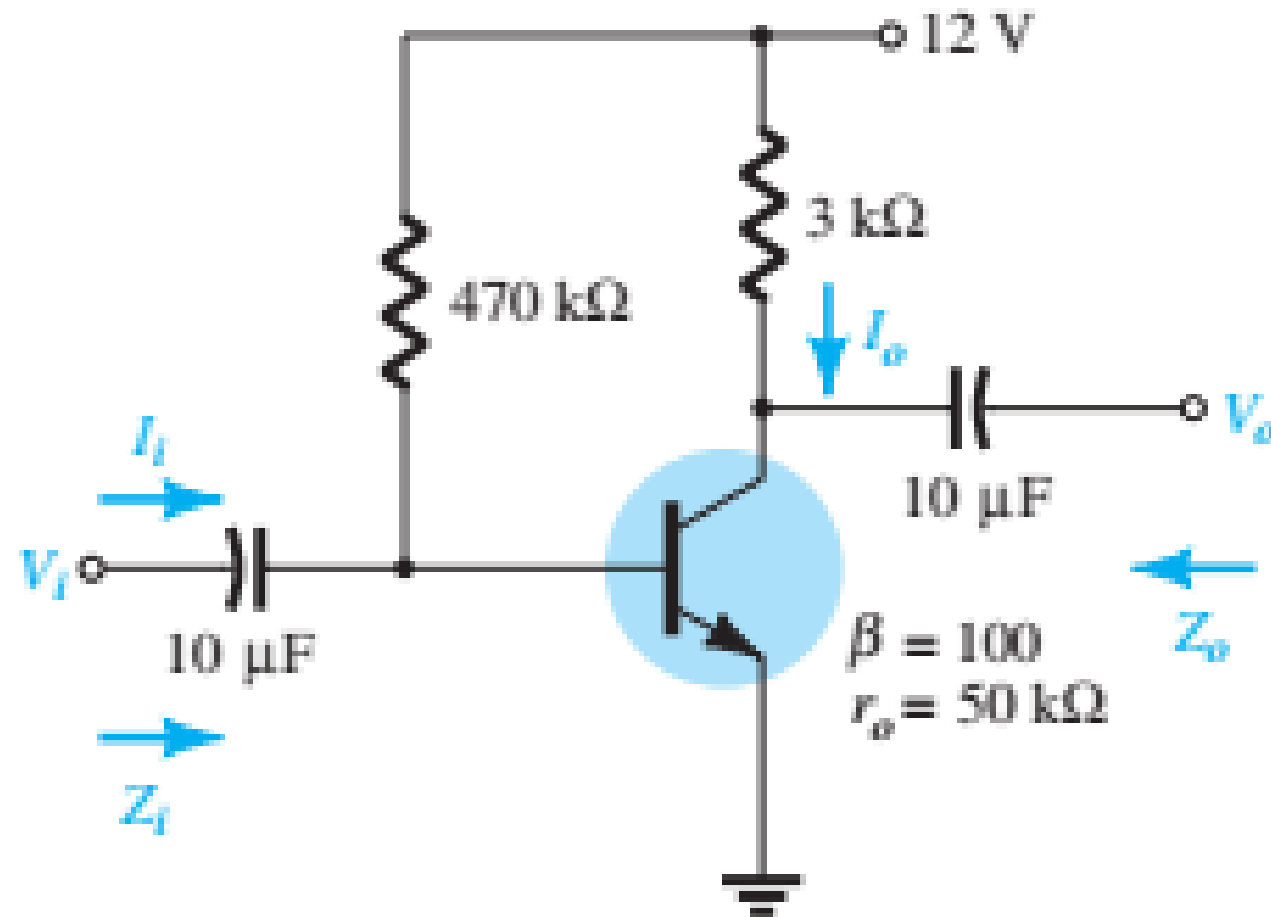

Effect of R_L and R_s (Example)

EXAMPLE 5.11 Using the parameter values for the fixed-bias configuration of Example 5.1 with an applied load of $4.7 \text{ k}\Omega$ and a source resistance of $0.3 \text{ k}\Omega$, determine the following and compare to the no-load values:

- A_{v_L} .
- A_{v_s} .
- Z_i .
- Z_o .

Solution:

a. Eq. (5.73):
$$A_{v_L} = -\frac{R_C \parallel R_L}{r_e} = -\frac{3 \text{ k}\Omega \parallel 4.7 \text{ k}\Omega}{10.71 \Omega} = -\frac{1.831 \text{ k}\Omega}{10.71 \Omega} = -170.98$$

which is significantly less than the no-load gain of -280.11 .

b. Eq. (5.76):
$$A_{v_s} = \frac{Z_i}{Z_i + R_s} A_{v_L}$$

With $Z_i = 1.07 \text{ k}\Omega$ from Example 5.1, we have


$$A_{v_s} = \frac{1.07 \text{ k}\Omega}{1.07 \text{ k}\Omega + 0.3 \text{ k}\Omega} (-170.98) = -133.54$$

which again is significantly less than $A_{v_{NL}}$ or A_{v_L} .

c. $Z_i = 1.07 \text{ k}\Omega$ as obtained for the no-load situation.

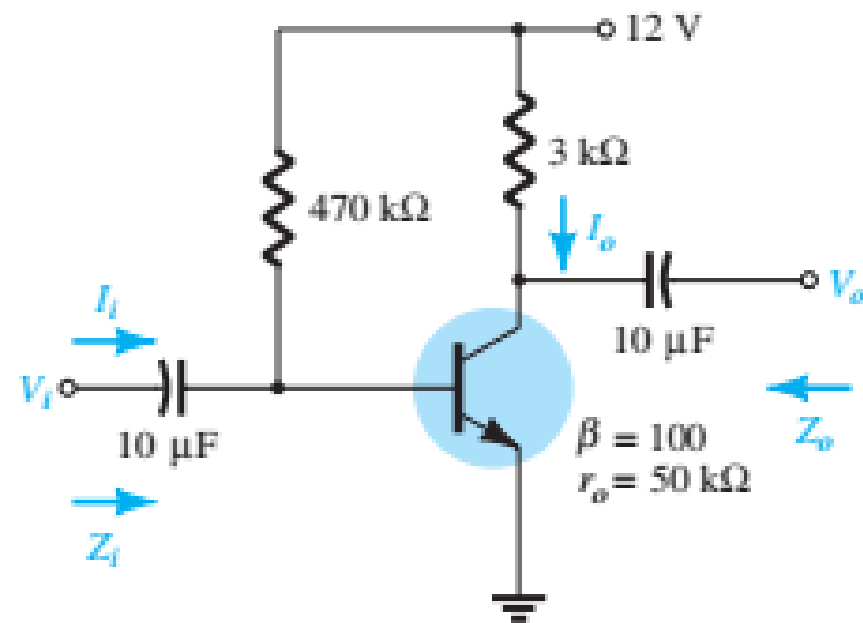d. $Z_o = R_C = 3 \text{ k}\Omega$ as obtained for the no-load situation.

The example clearly demonstrates that $A_{v_{NL}} > A_{v_L} > A_{v_s}$.



Determining the Current Gain

Determining the Current gain

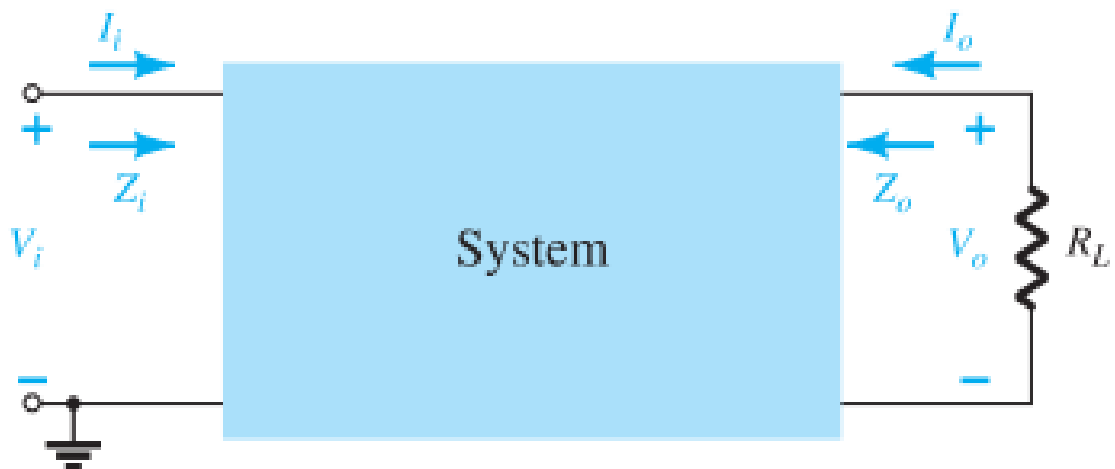


FIG. 5.60

Determining the current gain using the voltage gain.

- For each transistor configuration, the current gain can be determined directly from the voltage gain, the defined load, and the input impedance.




$$I_i = \frac{V_i}{Z_i} \quad \text{and} \quad I_o = -\frac{V_o}{R_L}$$

$$A_i = \frac{I_o}{I_i}$$



$$A_{iL} = \frac{I_o}{I_i} = \frac{-\frac{V_o}{R_L}}{\frac{V_i}{Z_i}} = -\frac{V_o}{V_i} \cdot \frac{Z_i}{R_L}$$

$$A_{iL} = -A_{vL} \frac{Z_i}{R_L}$$

Summary Table

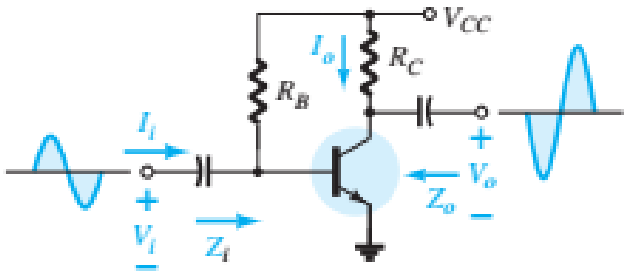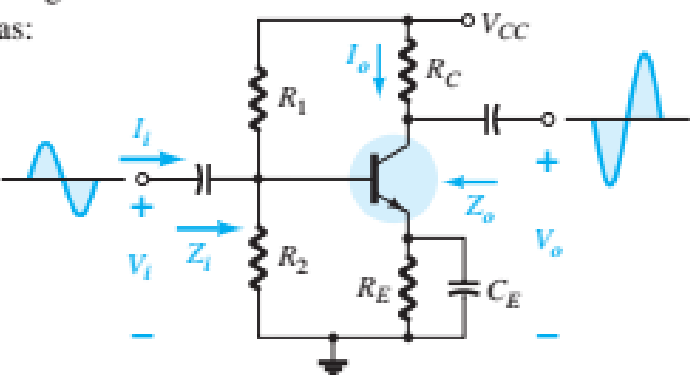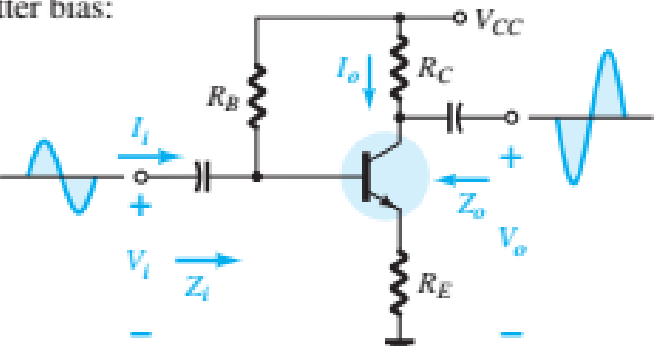Configuration	Z_i	Z_o	A_v	A_i
Fixed-bias: 	Medium (1 k Ω) $= R_B \parallel \beta r_e$ $\equiv \beta r_e$ ($R_B \geq 10\beta r_e$)	Medium (2 k Ω) $= R_C \parallel r_o$ $\equiv R_C$ ($r_o \geq 10R_C$)	High (-200) $= -\frac{(R_C \parallel r_o)}{r_e}$ $\equiv -\frac{R_C}{r_e}$ ($r_o \geq 10R_C$)	High (100) $= \frac{\beta R_B r_o}{(r_o + R_C)(R_B + \beta r_e)}$ $\equiv \beta$ ($r_o \geq 10R_C$, $R_B \geq 10\beta r_e$)
Voltage-divider bias: 	Medium (1 k Ω) $= R_1 \parallel R_2 \parallel \beta r_e$	Medium (2 k Ω) $= R_C \parallel r_o$ $\equiv R_C$ ($r_o \geq 10R_C$)	High (-200) $= -\frac{R_C \parallel r_o}{r_e}$ $\equiv -\frac{R_C}{r_e}$ ($r_o \geq 10R_C$)	High (50) $= \frac{\beta(R_1 \parallel R_2)r_o}{(r_o + R_C)(R_1 \parallel R_2 + \beta r_e)}$ $\equiv \frac{\beta(R_1 \parallel R_2)}{R_1 \parallel R_2 + \beta r_e}$ ($r_o \geq 10R_C$)
Unbypassed emitter bias: 	High (100 k Ω) $= R_B \parallel Z_b$ $Z_b \equiv \beta(r_e + R_E)$ $\equiv R_B \parallel \beta R_E$ ($R_E \gg r_e$)	Medium (2 k Ω) $= R_C$ (any level of r_o)	Low (-5) $= -\frac{R_C}{r_e + R_E}$ $\equiv -\frac{R_C}{R_E}$ ($R_E \gg r_e$)	High (50) $\equiv \frac{\beta R_B}{R_B + Z_b}$

Configuration	Z_i	Z_o	A_v	A_i
Emitter-follower: 	High (100 k Ω) $= R_B \parallel Z_b$ $Z_b \equiv \beta(r_e + R_E)$ $\equiv R_B \parallel \beta R_E$ $(R_E \gg r_e)$	Low (20 Ω) $= R_E \parallel r_e$ $\equiv r_e$ $(R_E \gg r_e)$	Low ($\cong 1$) $= \frac{R_E}{R_E + r_e}$ $\equiv 1$	High (≈ 50) $\equiv \frac{\beta R_B}{R_B + Z_b}$
Common-base: 	Low (20 Ω) $= R_E \parallel r_e$ $\equiv r_e$ $(R_E \gg r_e)$	Medium (2 k Ω) $= R_C$	High (200) $\equiv \frac{R_C}{r_e}$	Low (-1) $\equiv -1$
Collector feedback: 	Medium (1 k Ω) $= \frac{r_e}{\frac{1}{\beta} + \frac{R_C}{R_F}}$ $(r_o \geq 10R_C)$	Medium (2 k Ω) $\equiv R_C \parallel R_F$ $(r_o \geq 10R_C)$	High (≈ 200) $\equiv \frac{R_C}{r_e}$ $(r_o \geq 10R_C)$ $(R_F \gg R_C)$	High (50) $= \frac{\beta R_F}{R_F + \beta R_C}$ $\equiv \frac{R_F}{R_C}$

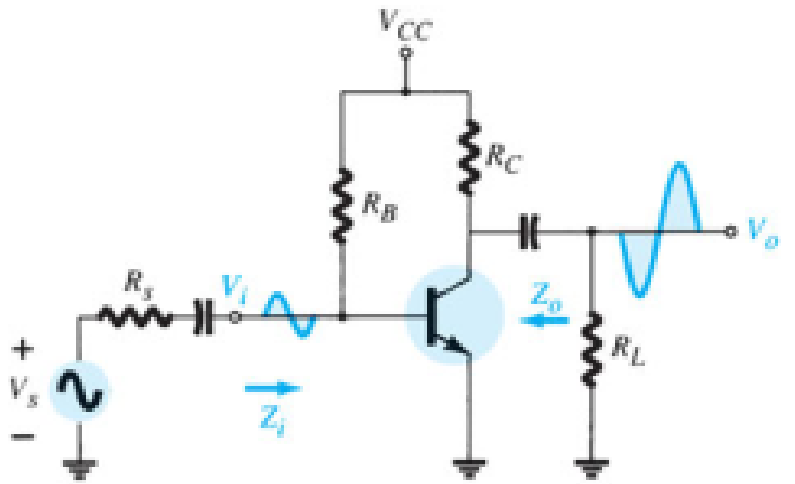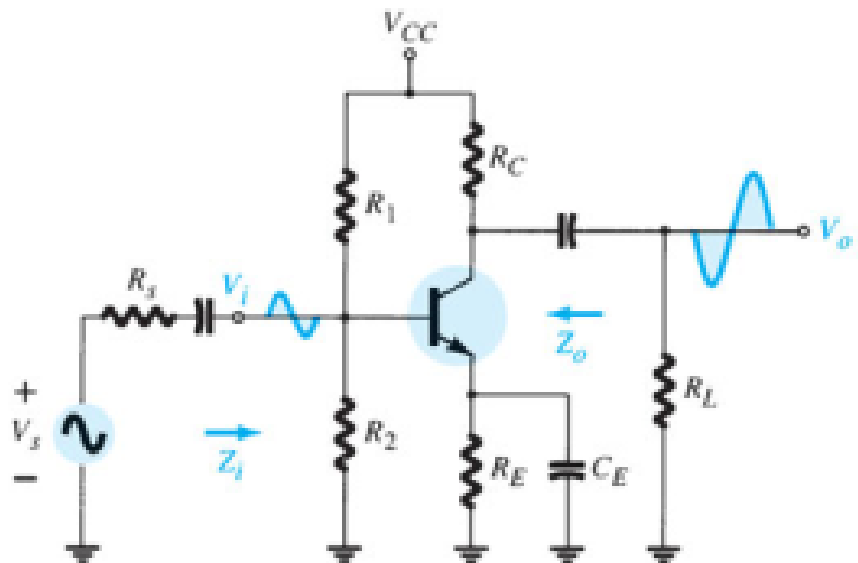Configuration	$A_{v_L} = V_o/V_i$	Z_i	Z_o
	$\frac{-(R_L \parallel R_C)}{r_e}$	$R_B \parallel \beta r_e$	R_C
	Including r_o : $\frac{(R_L \parallel R_C \parallel r_o)}{r_e}$	$R_B \parallel \beta r_e$	$R_C \parallel r_o$
	$\frac{-(R_L \parallel R_C)}{r_e}$	$R_1 \parallel R_2 \parallel \beta r_e$	R_C
	Including r_o : $\frac{-(R_L \parallel R_C \parallel r_o)}{r_e}$	$R_1 \parallel R_2 \parallel \beta r_e$	$R_C \parallel r_o$

Configuration	$A_{v_L} = V_o/V_i$	Z_i	Z_o
	$\cong 1$	$R'_E = R_L \parallel R_E$ $R_1 \parallel R_2 \parallel \beta(r_e + R'_E)$	$R'_s = R_s \parallel R_1 \parallel R_2$ $R_E \parallel \left(\frac{R'_s}{\beta} + r_e \right)$
	Including r_o : $\cong 1$	$R_1 \parallel R_2 \parallel \beta(r_e + R'_E)$	$R_E \parallel \left(\frac{R'_s}{\beta} + r_e \right)$
	$\cong \frac{-(R_L \parallel R_C)}{r_e}$	$R_E \parallel r_e$	R_C
	Including r_o : $\cong \frac{-(R_L \parallel R_C \parallel r_o)}{r_e}$	$R_E \parallel r_e$	$R_C \parallel r_o$
	$\frac{-(R_L \parallel R_C)}{R_E}$	$R_1 \parallel R_2 \parallel \beta(r_e + R_E)$	R_C
	Including r_o : $\frac{-(R_L \parallel R_C)}{R_E}$	$R_1 \parallel R_2 \parallel \beta(r_e + R_e)$	$\cong R_C$

Configuration	$A_{v_L} = V_o/V_i$	Z_i	Z_o
	$\frac{-(R_L \parallel R_C)}{R_{E1}}$	$R_B \parallel \beta(r_e + R_{E1})$	R_C
	Including r_o : $\frac{-(R_L \parallel R_C)}{R_{E1}}$	$R_B \parallel \beta(r_e + R_E)$	$\equiv R_C$
	$\frac{-(R_L \parallel R_C)}{r_e}$	$\beta r_e \parallel \frac{R_F}{ A_v }$	R_C
	Including r_o : $\frac{-(R_L \parallel R_C \parallel r_o)}{r_e}$	$\beta r_e \parallel \frac{R_F}{ A_v }$	$R_C \parallel R_F \parallel r_o$
	$\frac{-(R_L \parallel R_C)}{R_E}$	$\beta R_E \parallel \frac{R_F}{ A_v }$	$\equiv R_C \parallel R_F$
	Including r_o : $\equiv \frac{-(R_L \parallel R_C)}{R_E}$	$\equiv \beta R_E \parallel \frac{R_F}{ A_v }$	$\equiv R_C \parallel R_F$

Thank You!

