
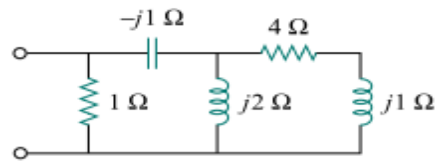


Name:	Sec:	B.N.:
-------	------	-------

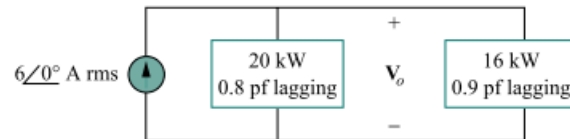1. Obtain the power factor for the circuits in Figure, Specify power factor as leading or lagging.



2. For the circuit in Figure, find V_o and the input power factor.



3. Find the rms value of the periodic signal in figure

