 


Digital Fundamentals


Tenth Edition

Floyd



Elementary Logic Gates

The Inverter

 


The inverter performs the Boolean **NOT** operation. When the input is LOW, the output is HIGH; when the input is HIGH, the output is LOW.

Input	Output
A	X
LOW (0)	HIGH (1)
HIGH (1)	LOW(0)


The **NOT** operation (complement) is shown with an overbar. Thus, the Boolean expression for an inverter is $X = \overline{A}$.

Summary


The Inverter

 

Example waveforms:


 


 A group of inverters can be used to form the 1's complement of a binary number:



Summary

The AND Gate

  



The **AND** gate produces a HIGH output when all inputs are HIGH; otherwise, the output is LOW. For a 2-input gate, the truth table is

Inputs		Output
<i>A</i>	<i>B</i>	<i>X</i>
0	0	0
0	1	0
1	0	0
1	1	1


The **AND** operation is usually shown with a dot between the variables but it may be implied (no dot). Thus, the AND operation is written as $X = A \cdot B$ or $X = AB$.

Summary

The AND Gate

  

Example waveforms:


 


The AND operation is used in computer programming as a selective mask. If you want to retain certain bits of a binary number but reset the other bits to 0, you could set a mask with 1's in the position of the retained bits.

Example If the binary number 10100011 is ANDed with the mask 00001111, what is the result? **00000011**

Summary

The OR Gate

  



The **OR** gate produces a HIGH output if any input is HIGH; if all inputs are LOW, the output is LOW. For a 2-input gate, the truth table is

Inputs		Output
<i>A</i>	<i>B</i>	<i>X</i>
0	0	0
0	1	1
1	0	1
1	1	1


The **OR** operation is shown with a plus sign (+) between the variables. Thus, the OR operation is written as $X = A + B$.

Summary

The OR Gate

  

Example waveforms:

 



The OR operation can be used in computer programming to set certain bits of a binary number to 1.

Example ASCII letters have a 1 in the bit 5 position for lower case letters and a 0 in this position for capitals. (Bit positions are numbered from right to left starting with 0.) What will be the result if you OR an ASCII letter with the 8-bit mask 00100000?

Solution The resulting letter will be lower case.

Summary

The NAND Gate

  



The **NAND** gate produces a LOW output when all inputs are HIGH; otherwise, the output is HIGH. For a 2-input gate, the truth table is

Inputs		Output
<i>A</i>	<i>B</i>	<i>X</i>
0	0	1
0	1	1
1	0	1
1	1	0


The **NAND** operation is shown with a dot between the variables and an overbar covering them. Thus, the **NAND** operation is written as $X = \overline{A \cdot B}$ (Alternatively, $X = \overline{AB}$.)

Summary

The NAND Gate

  


Example waveforms:

 



The NAND gate is particularly useful because it is a “universal” gate – all other basic gates can be constructed from NAND gates.

 Question How would you connect a 2-input NAND gate to form a basic inverter?



Summary

The NOR Gate

  



The **NOR** gate produces a LOW output if any input is HIGH; if all inputs are HIGH, the output is LOW. For a 2-input gate, the truth table is

Inputs		Output
<i>A</i>	<i>B</i>	<i>X</i>
0	0	1
0	1	0
1	0	0
1	1	0


The **NOR** operation is shown with a plus sign (+) between the variables and an overbar covering them. Thus, the NOR operation is written as $X = \overline{A + B}$.

Summary

The NOR Gate

  


Example waveforms:

 

The NOR operation will produce a LOW if any input is HIGH.


 
Example When is the LED is ON for the circuit shown?

Solution The LED will be on when any of the four inputs are HIGH.



Summary

The XOR Gate

  

The **XOR** gate produces a HIGH output only when both inputs are at opposite logic levels. The truth table is



Inputs		Output
A	B	X
0	0	0
0	1	1
1	0	1
1	1	0

The **XOR** operation is written as $X = \bar{A}B + A\bar{B}$.


Alternatively, it can be written with a circled plus sign between the variables as $X = A \oplus B$.

Summary

The XOR Gate

  

Example waveforms:

 



Notice that the XOR gate will produce a HIGH only when exactly one input is HIGH.

Question If the A and B waveforms are both inverted for the above waveforms, how is the output affected?

There is no change in the output.

Summary

The XNOR Gate

  



The **XNOR** gate produces a HIGH output only when both inputs are at the same logic level. The truth table is

Inputs		Output
<i>A</i>	<i>B</i>	<i>X</i>
0	0	1
0	1	0
1	0	0
1	1	1


The **XNOR** operation shown as $X = \overline{A}\overline{B} + AB$. Alternatively, the XNOR operation can be shown with a circled dot between the variables. Thus, it can be shown as $X = A \odot B$.

Summary

The XNOR Gate

  

Example waveforms:

 

Notice that the XNOR gate will produce a HIGH when both inputs are the same. This makes it useful for comparison functions.


Question If the *A* waveform is inverted but *B* remains the same, how is the output affected?

The output will be inverted.

Digital Fundamentals

Tenth Edition

Floyd

 

Boolean Algebra

Boolean Addition

In Boolean algebra, a **variable** is a symbol used to represent an action, a condition, or data. A single variable can only have a value of 1 or 0.

The **complement** represents the inverse of a variable and is indicated with an overbar. Thus, the complement of A is \bar{A} .

A **literal** is a variable or its complement.

Addition is equivalent to the OR operation. The sum term is 1 if one or more of the literals are 1. The sum term is zero only if each literal is 0.

Example Determine the values of A , B , and C that make the sum term of the expression $\bar{A} + B + \bar{C} = 0$?

Solution Each literal must = 0; therefore $A = 1$, $B = 0$ and $C = 1$.

Summary

Boolean Multiplication

In Boolean algebra, multiplication is equivalent to the AND operation. The product of literals forms a product term. The product term will be 1 only if all of the literals are 1.

Example What are the values of the A , B and C if the product term of $A \cdot \overline{B} \cdot \overline{C} = 1$?

Solution Each literal must = 1; therefore $A = 1$, $B = 0$ and $C = 0$.

Summary

Commutative Laws

The **commutative laws** are applied to addition and multiplication. For addition, the commutative law states
In terms of the result, the order in which variables are ORed makes no difference.

$$A + B = B + A$$

For multiplication, the commutative law states
In terms of the result, the order in which variables are ANDed makes no difference.

$$AB = BA$$


Summary

Distributive Law

The **distributive law** is the factoring law. A common variable can be factored from an expression just as in ordinary algebra. That is

$$AB + AC = A(B + C)$$

 The distributive law can be illustrated with equivalent circuits:



Summary

Rules of Boolean Algebra

1. $A + 0 = A$

2. $A + 1 = 1$

3. $A \cdot 0 = 0$

4. $A \cdot 1 = A$

5. $A + A = A$

6. $A + \bar{A} = 1$

7. $A \cdot A = A$

8. $A \cdot \bar{A} = 0$

9. $\bar{\bar{A}} = A$

10. $A + AB = A$

11. $A + \bar{A}B = A + B$

12. $(A + B)(A + C) = A + BC$


Summary

Rules of Boolean Algebra

Rules of Boolean algebra can be illustrated with *Venn* diagrams. The variable A is shown as an area.

The rule $A + AB = A$ can be illustrated easily with a diagram. Add an overlapping area to represent the variable B .

 The overlap region between A and B represents AB .



The diagram visually shows that $A + AB = A$. Other rules can be illustrated with the diagrams as well.

Summary

Rules of Boolean Algebra

Rule 12, which states that $(A + B)(A + C) = A + BC$, can be proven by applying earlier rules as follows:

$$\begin{aligned}(A + B)(A + C) &= AA + AC + AB + BC \\ &= A + AC + AB + BC \\ &= A(1 + C + B) + BC \\ &= A \cdot 1 + BC \\ &= A + BC\end{aligned}$$

This rule is a little more complicated, but it can also be shown with a Venn diagram, as given on the following slide...

Summary


DeMorgan's Theorem

DeMorgan's 1st Theorem

The complement of a product of variables is equal to the sum of the complemented variables.

$$\overline{AB} = \overline{A} + \overline{B}$$

 Applying DeMorgan's first theorem to gates:



Inputs		Output	
A	B	\overline{AB}	$\overline{A} + \overline{B}$
0	0	1	1
0	1	1	1
1	0	1	1
1	1	0	0

Summary


DeMorgan's Theorem

DeMorgan's 2nd Theorem

The complement of a sum of variables is equal to the product of the complemented variables.

$$\overline{A + B} = \overline{A} \cdot \overline{B}$$

 Applying DeMorgan's second theorem to gates:



Inputs		Output	
A	B	$\overline{A + B}$	$\overline{A} \cdot \overline{B}$
0	0	1	1
0	1	0	0
1	0	0	0
1	1	0	0

Summary

DeMorgan's Theorem

Example

Apply DeMorgan's theorem to remove the overbar covering both terms from the expression $X = \overline{C + D}$.

Solution

To apply DeMorgan's theorem to the expression, you can break the overbar covering both terms and change the sign between the terms. This results in $X = \overline{\overline{C}} \cdot \overline{\overline{D}}$. Deleting the double bar gives $X = C \cdot \overline{D}$.

Summary


Boolean Analysis of Logic Circuits

Combinational logic circuits can be analyzed by writing the expression for each gate and combining the expressions according to the rules for Boolean algebra.

Example Solution

Apply Boolean algebra to derive the expression for X .

Write the expression for each gate:

 

Applying DeMorgan's theorem and the distribution law:

$$X = C(\overline{A} \overline{B}) + D = \overline{A} \overline{B} C + D$$

Summary

SOP and POS forms

Boolean expressions can be written in the **sum-of-products** form (**SOP**) or in the **product-of-sums** form (**POS**). These forms can simplify the implementation of combinational logic, particularly with PLDs. In both forms, an overbar cannot extend over more than one variable.

An expression is in SOP form when two or more product terms are summed as in the following examples:

$$\bar{A}\bar{B}\bar{C} + AB$$

$$ABC + \bar{C}\bar{D}$$

$$CD + \bar{E}$$

An expression is in POS form when two or more sum terms are multiplied as in the following examples:

$$(A + B)(\bar{A} + C)$$

$$(A + B + \bar{C})(B + D)$$

$$(\bar{A} + B)C$$

Summary

SOP Standard form

In **SOP standard form**, every variable in the domain must appear in each term. This form is useful for constructing truth tables or for implementing logic in PLDs.

You can expand a nonstandard term to standard form by multiplying the term by a term consisting of the sum of the missing variable and its complement.

Example Solution

Convert $X = \bar{A}\bar{B} + ABC$ to standard form.

The first term does not include the variable C . Therefore, multiply it by the $(C + \bar{C})$, which = 1:

$$\begin{aligned} X &= \bar{A}\bar{B}(C + \bar{C}) + ABC \\ &= \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C} + ABC \end{aligned}$$

Summary

POS Standard form

In **POS standard form**, every variable in the domain must appear in each sum term of the expression.

You can expand a nonstandard POS expression to standard form by adding the product of the missing variable and its complement and applying rule 12, which states that $(A + B)(A + C) = A + BC$.

Example Convert $X = (\bar{A} + \bar{B})(A + B + C)$ to standard form.

Solution The first sum term does not include the variable C . Therefore, add $C\bar{C}$ and expand the result by rule 12.

$$\begin{aligned} X &= (\bar{A} + \bar{B} + C\bar{C})(A + B + C) \\ &= (\bar{A} + \bar{B} + C)(\bar{A} + \bar{B} + \bar{C})(A + B + C) \end{aligned}$$