

Electrical Circuits (2)

Lecture 3 Resonance

Dr.Eng. Basem ElHalawany

References

- A. Fundamentals of Electric Circuits (Alexander and Sadiku)
- B. Principles of Electric Circuits (Floyd)
- C. Circuit Analysis – Theories and Practice (Robinson & Miller)
- D. Introductory Circuit Analysis (Boylestad)**

Series Resonance Circuit (Cont.)

Quality Factor (Different Formulas)

$$Q_s = \frac{\omega_s L}{R}$$

$$\begin{aligned} Q_s &= \frac{\omega_s L}{R} = \frac{2\pi f_s L}{R} = \frac{2\pi}{R} \left(\frac{1}{2\pi\sqrt{LC}} \right) L \\ &= \frac{L}{R} \left(\frac{1}{\sqrt{LC}} \right) = \left(\frac{\sqrt{L}}{\sqrt{L}} \right) \frac{L}{R\sqrt{LC}} \end{aligned}$$

$$Q_s = \frac{1}{R} \sqrt{\frac{L}{C}}$$

Series Resonance Circuit (Cont.)

EXAMPLE 20.5 A series R - L - C circuit is designed to resonant at $\omega_s = 10^5$ rad/s, have a bandwidth of $0.15\omega_s$, and draw 16 W from a 120-V source at resonance.

- Determine the value of R .
- Find the bandwidth in hertz.
- Find the nameplate values of L and C .
- Determine the Q_s of the circuit.

$$BW = f_2 - f_1 = \frac{R}{2\pi L}$$

a. $P = \frac{E^2}{R}$ and $R = \frac{E^2}{P} = \frac{(120 \text{ V})^2}{16 \text{ W}} = \mathbf{900 \ \Omega}$

b. $BW = 0.15f_s$ $f_s = \frac{\omega_s}{2\pi} = \frac{10^5 \text{ rad/s}}{2\pi} = 15,915.49 \text{ Hz}$

$$BW = 0.15f_s = 0.15(15,915.49 \text{ Hz}) = \mathbf{2387.32 \text{ Hz}}$$

c. $BW = \frac{R}{2\pi L}$ and $L = \frac{R}{2\pi BW} = \frac{900 \ \Omega}{2\pi(2387.32 \text{ Hz})} = \mathbf{60 \text{ mH}}$

$$f_s = \frac{1}{2\pi\sqrt{LC}} \text{ and } C = \frac{1}{4\pi^2 f_s^2 L} = \frac{1}{4\pi^2 (15,915.49 \text{ Hz})^2 (60 \times 10^{-3} \text{ H})} = \mathbf{1.67 \text{ nF}}$$

d. $Q_s = \frac{X_L}{R} = \frac{2\pi f_s L}{R} = \frac{2\pi(15,915.49 \text{ Hz})(60 \text{ mH})}{900 \ \Omega} = \mathbf{6.67}$

Note that at resonance:

1. The impedance is purely resistive, thus, $\mathbf{Z} = R$. In other words, the LC series combination acts like a short circuit, and the entire voltage is across R .
2. The voltage \mathbf{V}_s and the current \mathbf{I} are in phase, so that the power factor is unity.
3. The inductor voltage and capacitor voltage can be much more than the source voltage.


➤ Point (3) can be verified by applying the voltage divider rule to the circuit of Fig. 20.2, we obtain

$$V_L = \frac{X_L E}{Z_T} = \frac{X_L E}{R} \quad (\text{at resonance})$$

$$V_{L_s} = Q_s E$$

$$V_C = \frac{X_C E}{Z_T} = \frac{X_C E}{R}$$

$$V_{C_s} = Q_s E$$

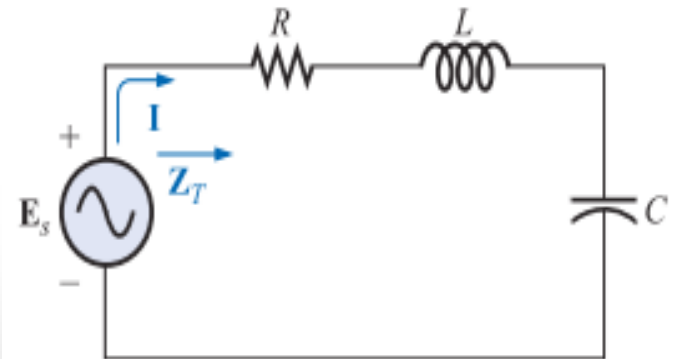

Ch.20D
P.892

Series Resonance Circuit (Cont.)

6

$$V_{L_s} = Q_s E$$


$$V_{C_s} = Q_s E$$

➤ Since Q_s is usually greater than 1, the voltage across the capacitor or inductor of a series resonant circuit can be significantly greater than the input voltage.

➤ Analyze the circuit, and verify your results by simulation?

- $L = 10 \text{ mH}$
- $C = 4.05 \text{ nF}$
- $R = 25 \text{ Ohms}$
- $E_s = 625 \text{ mV}$

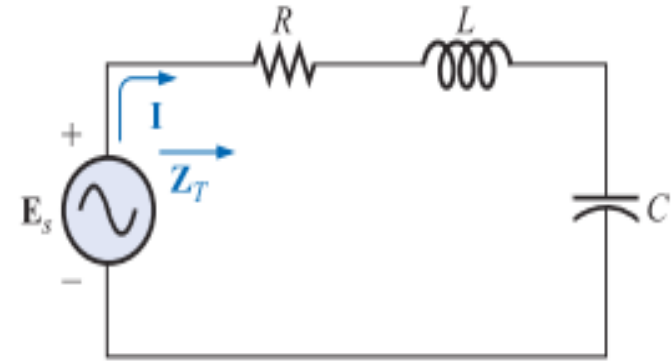- $F = 1/(2 \text{ Pi Sqrt}(L*C)) = 25008.75 \text{xxxxx Hz}$
- $Q = X_L/R = \omega L/R = 62.854$
- $V_L = Q E_s = 62.854 * 635 \text{ mV} = 39.9 \text{ Volts}$



Check Proteus Simulation Tutorials at the following link

<http://www.bu.edu.eg/staff/basem.mamdoh-courses/12142/URLs>

Next Lecture

Parallel Resonance