

# Electrical Circuits (2)

## Lecture 4

### Parallel Resonance and its Filters

Dr.Eng. Basem ElHalawany

# Parallel Resonance Circuit

It is usually called tank circuit

## Ideal Circuits

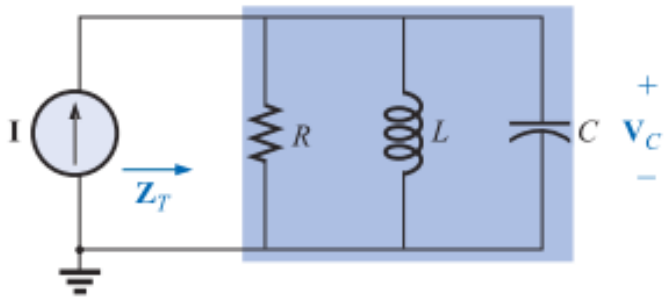


FIG. 20.21

*Ideal parallel resonant network.*

## Practical Circuits


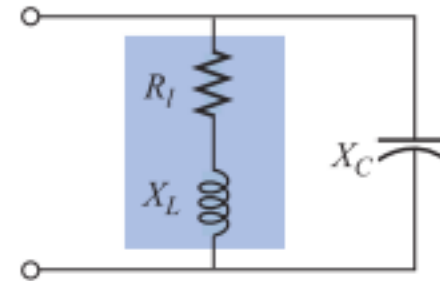


FIG. 20.22

*Practical parallel L-C network.*

## Complex Configuration

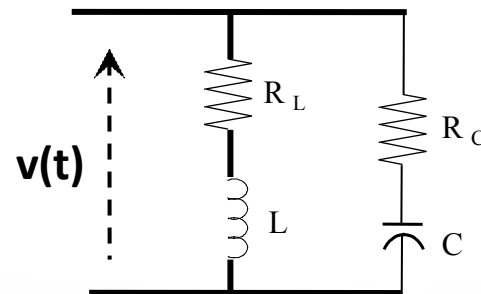

# Ideal Parallel Resonance Circuit


The total admittance

$$Y = Y_1 + Y_2 + Y_3$$

$$Y = \frac{1}{R} + \frac{1}{(j\omega L)} + \frac{1}{(-j/\omega C)}$$

$$Y = \frac{1}{R} + \frac{-j}{\omega L} + j\omega C$$
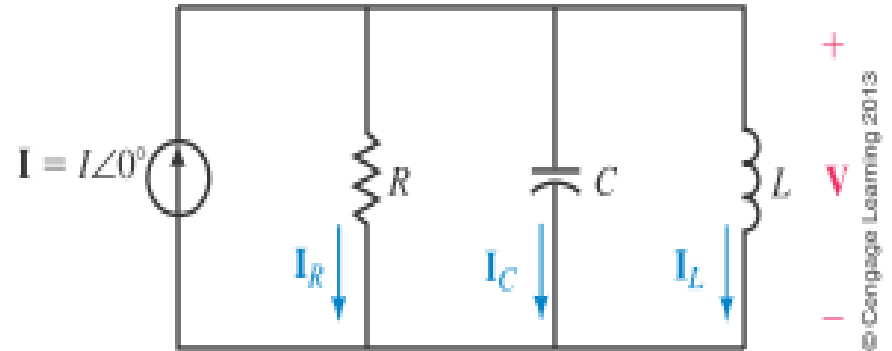
$$Y = \frac{1}{R} + j(\omega C - 1/\omega L)$$



## Condition for Ideal Parallel Resonance

Resonance occurs when the imaginary part of  $Y$  is zero

$$\omega C - \frac{1}{\omega L} = 0$$

$$X_C = X_L$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \text{ rad/s}$$

# Ideal Parallel Resonance Circuit


4

At parallel resonance:


- ✓ At resonance, the admittance consists only conductance  $G = 1/R$ .
- ✓ The value of current will be minimum since the total admittance is minimum.
- ✓ The voltage and current are in phase (Power factor is unity).
- ✓ The inductor and capacitor reactances cancel, resulting in a circuit voltage simply determined by Ohm's law as:

$$V = IR = IR \angle 0^\circ$$

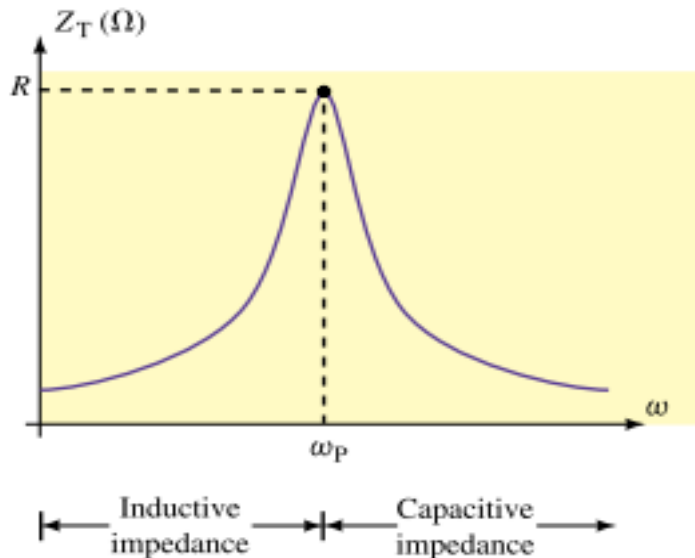- ✓ The frequency response of the impedance of the parallel circuit is shown



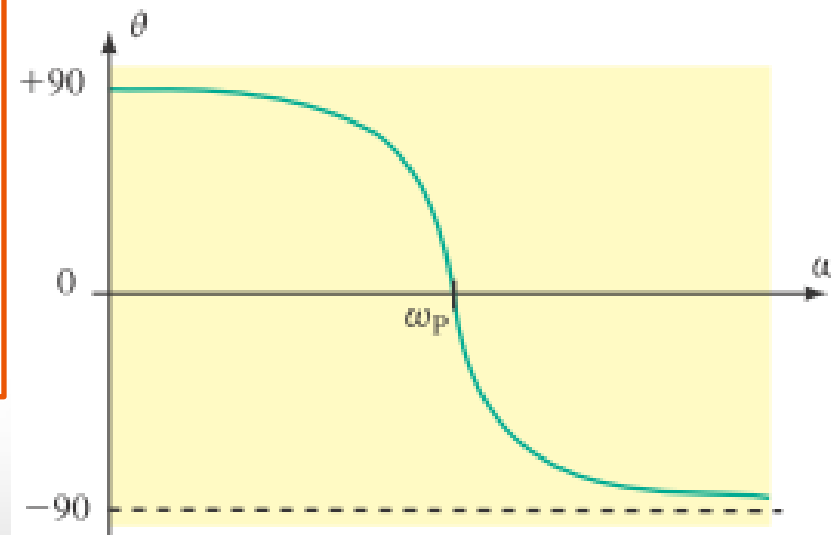exactly opposite to that in series resonant circuits,



# Ideal Parallel Resonance Circuit

5

The Q of the parallel circuit is determined from the definition as

$$Q_P = \frac{\text{reactive power}}{\text{average power}} \\ = \frac{V^2/X_L}{V^2/R}$$

$$Q_P = \frac{R}{X_{LP}} = \frac{R}{X_C}$$

Reciprocal of series

The current

$$I_R = \frac{V}{R} = I$$

$$I_L = \frac{V}{X_L \angle 90^\circ} \\ = \frac{V}{R/Q_P} \angle -90^\circ \\ = Q_P I \angle -90^\circ$$

$$I_C = \frac{V}{X_C \angle -90^\circ} \\ = \frac{V}{R/Q_P} \angle 90^\circ \\ = Q_P I \angle 90^\circ$$

- ✓ The currents through the inductor and the capacitor have the same magnitudes but are 180 out of phase.
- ✓ Notice that the magnitude of current in the reactive elements at resonance is Q times greater than the applied source current.

# Ideal Parallel Resonance Circuit

6

➤ Parallel resonant circuit has same parameters as the series resonant circuit.

Resonance frequency:

$$\omega_p = \frac{1}{\sqrt{LC}} \text{ rad/s}$$

Half-power frequencies:

$$\omega_1 = -\frac{1}{2RC} + \sqrt{\frac{1}{4R^2C^2} + \frac{1}{LC}} \text{ (rad/s)}$$

$$\omega_2 = \frac{1}{2RC} + \sqrt{\frac{1}{4R^2C^2} + \frac{1}{LC}} \text{ (rad/s)}$$

Bandwidth and Q-factor:

$$BW = \omega_2 - \omega_1 = \frac{1}{RC} \text{ (rad/s)}$$

$$BW = \frac{\omega_p}{R(\omega_p C)} = \frac{X_C}{R} \omega_p$$

$$BW = \frac{\omega_p}{Q_P} \text{ (rad/s)}$$


$$Q = \frac{\omega_0}{B} = \omega_0 RC = \frac{R}{\omega_0 L}$$

$$\omega_1 = \omega_0 \sqrt{1 + \left(\frac{1}{2Q}\right)^2} - \frac{\omega_0}{2Q}$$

$$\omega_2 = \omega_0 \sqrt{1 + \left(\frac{1}{2Q}\right)^2} + \frac{\omega_0}{2Q}$$

## Effect of Winding Resistance on the Parallel Resonant Frequency


- The internal resistance of the coil must be taken into consideration because it is no longer be included in a simple series or parallel combination with the source resistance and any other resistance added for design purposes.
- Even though  $R_L$  is usually relatively small in magnitude compared with other resistance and reactance levels of the network, it does have an important impact on the parallel resonant condition,

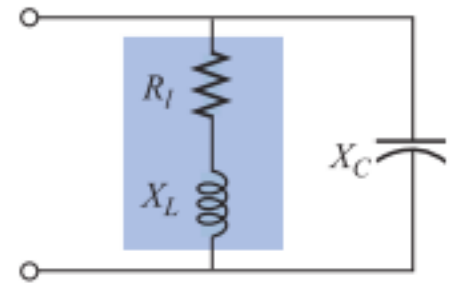

**FIG. 20.22**

*Practical parallel L-C network.*

1. Find a parallel network equivalent to the series R-L branch

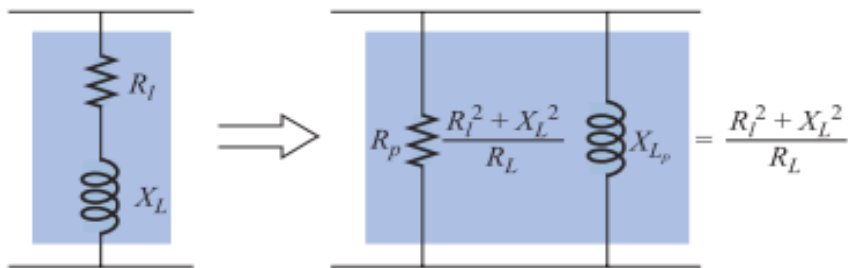

**FIG. 20.23**

*Equivalent parallel network for a series R-L combination.*

$$\mathbf{Z}_{R-L} = R_i + j X_L$$

$$\mathbf{Y}_{R-L} = \frac{1}{\mathbf{Z}_{R-L}} = \frac{1}{R_i + j X_L} = \frac{R_i}{R_i^2 + X_L^2} - j \frac{X_L}{R_i^2 + X_L^2}$$


# Practical Parallel Resonance Circuit

$$Y_{R-L} = \frac{1}{\frac{R_l^2 + X_L^2}{R_l}} + \frac{1}{j\left(\frac{R_l^2 + X_L^2}{X_L}\right)} = \frac{1}{R_p} + \frac{1}{jX_{Lp}}$$

$$R_p = \frac{R_l^2 + X_L^2}{R_l}$$


$$X_{Lp} = \frac{R_l^2 + X_L^2}{X_L}$$

Redrawing the network

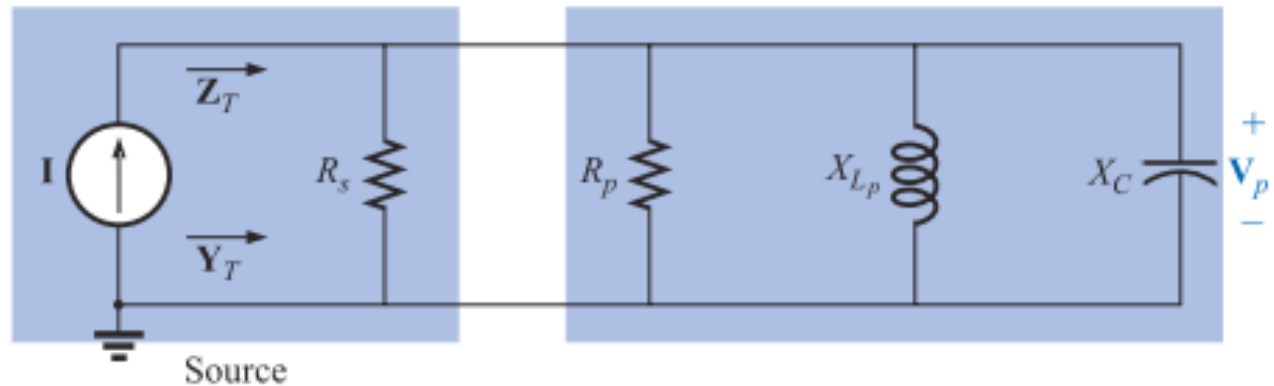

If we define the parallel combination of  $R_s$  and  $R_p$  by the notation

$$R = R_s \parallel R_p$$

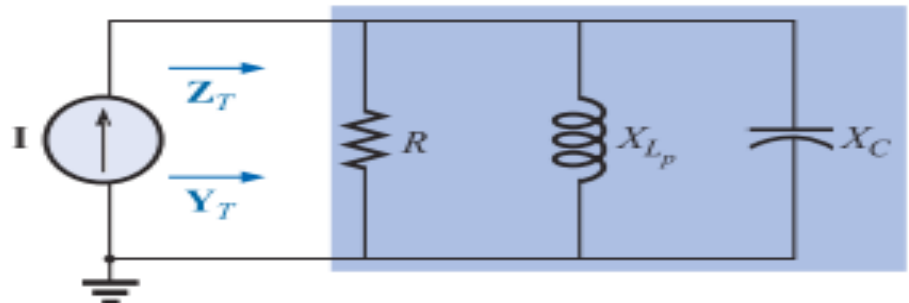



# Practical Parallel Resonance Circuit

9

$$Y_T = \frac{1}{R} + j \left( \frac{1}{X_C} - \frac{1}{X_{L_p}} \right)$$

$$\frac{1}{X_C} - \frac{1}{X_{L_p}} = 0$$

$$\frac{1}{X_C} = \frac{1}{X_{L_p}}$$

$$X_{L_p} = X_C$$

$$\frac{R_i^2 + X_L^2}{X_L} = X_C$$

The resonant frequency,  $f_p$ , can now be determined as follows:

$$R_i^2 + X_L^2 = X_C X_L = \left( \frac{1}{\omega C} \right) \omega L = \frac{L}{C}$$

$$X_L^2 = \frac{L}{C} - R_i^2$$

$$2\pi f_p L = \sqrt{\frac{L}{C} - R_i^2}$$

$$f_p = \frac{1}{2\pi L} \sqrt{\frac{L}{C} - R_i^2}$$

Multiplying within the square-root sign by C/L and rearranging produces :

$$f_p = \frac{1}{2\pi\sqrt{LC}} \sqrt{1 - \frac{R_i^2 C}{L}}$$

$$f_p = f_s \sqrt{1 - \frac{R_i^2 C}{L}}$$

## 1. Maximum impedance

➤ At  $f = f_p$  the input impedance of a parallel resonant circuit will be near its maximum value but not quite its maximum value due to the frequency dependence of  $R_p$ .

➤ The frequency at which maximum impedance will occur is:

$$f_m = f_s \sqrt{1 - \frac{1}{4} \left( \frac{R_s^2 C}{L} \right)}$$

$f_m$  is determined by differentiating the general equation for  $Z_T$  with respect to frequency

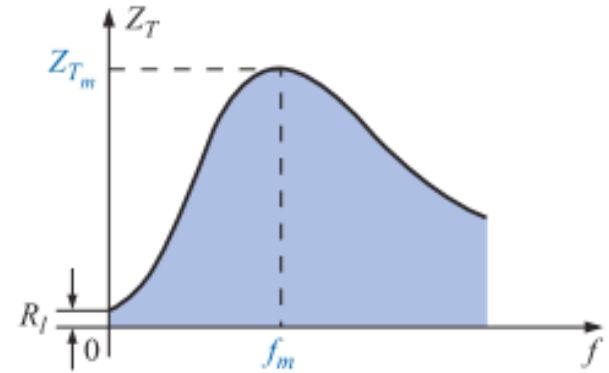


FIG. 20.26

$Z_T$  versus frequency for the parallel resonant circuit.

## 2. Minimum impedance

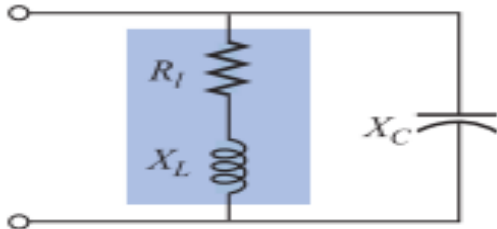


FIG. 20.22

Practical parallel L-C network.

At  $f = 0$  Hz,

$X_C$  is O.C,  $X_L = \text{zero}$

$$Z_T = R_s \parallel R_l \cong R_l.$$

As  $R_s$  is sufficiently large for the current source (ideally infinity)


➤ The quality factor of the practical parallel resonant circuit

determined by the ratio of the reactive power to the real power at resonance

$$Q_p = \frac{V_p^2 / X_{L_p}}{V_p^2 / R}$$

$$R = R_s \parallel R_p$$

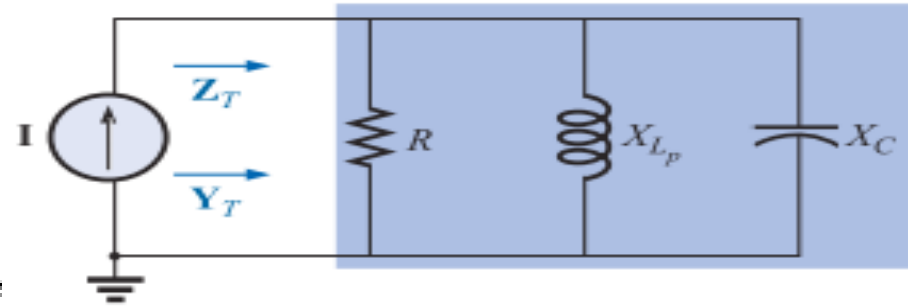$V_p$  is the voltage across the parallel branches.



$$Q_p = \frac{R}{X_{L_p}} = \frac{R_s \parallel R_p}{X_{L_p}}$$

$$Q_p = \frac{R_s \parallel R_p}{X_C}$$

For the ideal current source ( $R_s = \infty \Omega$ )

$$R = R_s \parallel R_p \cong R_p$$

$$Q_p = \frac{R_s \parallel R_p}{X_{L_p}} = \frac{R_p}{X_{L_p}} = \frac{(R_l^2 + X_L^2) / R_l}{(R_l^2 + X_L^2) / X_L}$$


$$Q_p = \frac{X_L}{R_l} = Q_l$$

$$R_s \gg R_p$$

which is simply the quality factor  $Q_l$  of the coil.

## ➤ Bandwidth and Half-Power point

$$BW = f_2 - f_1 = \frac{f_r}{Q_p}$$

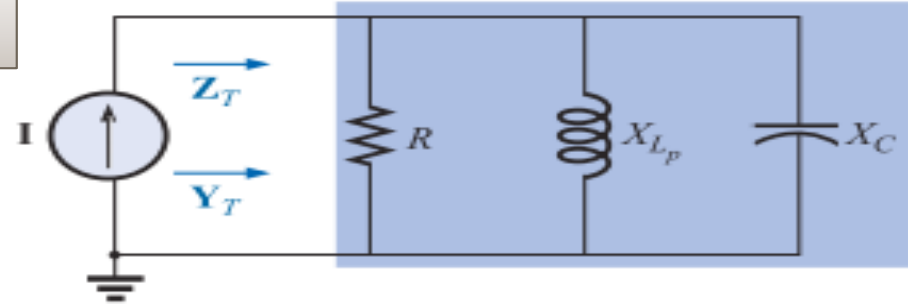



➤ The cutoff frequencies  $f_1$  and  $f_2$  can be determined using the equivalent network shown in the figure:

$$Z = \frac{1}{\frac{1}{R} + j\left(\omega C - \frac{1}{\omega L}\right)} = 0.707R$$

$$f_1 = \frac{1}{4\pi C} \left[ \frac{1}{R} - \sqrt{\frac{1}{R^2} + \frac{4C}{L}} \right]$$

$$f_2 = \frac{1}{4\pi C} \left[ \frac{1}{R} + \sqrt{\frac{1}{R^2} + \frac{4C}{L}} \right]$$

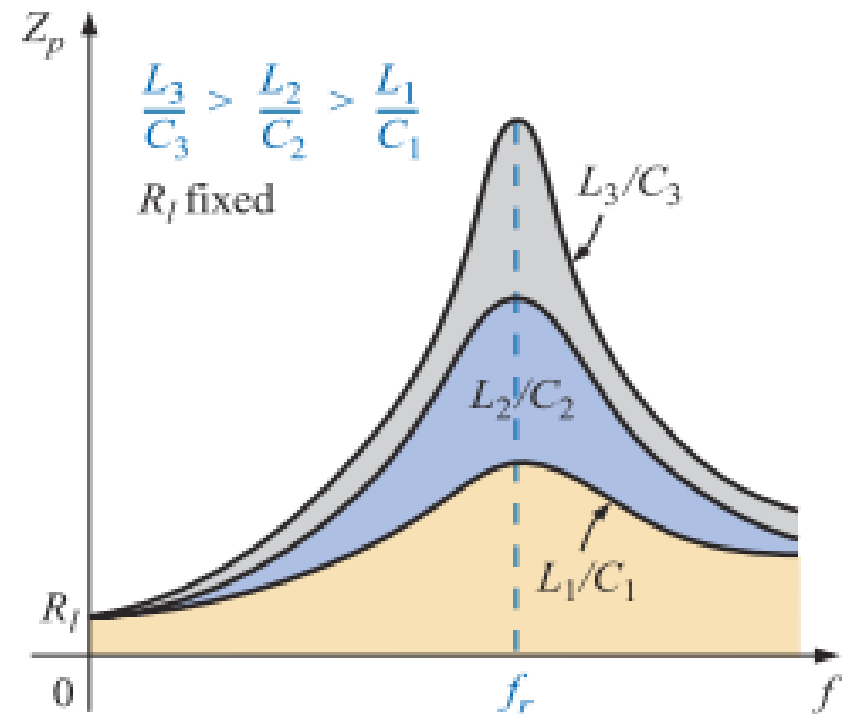
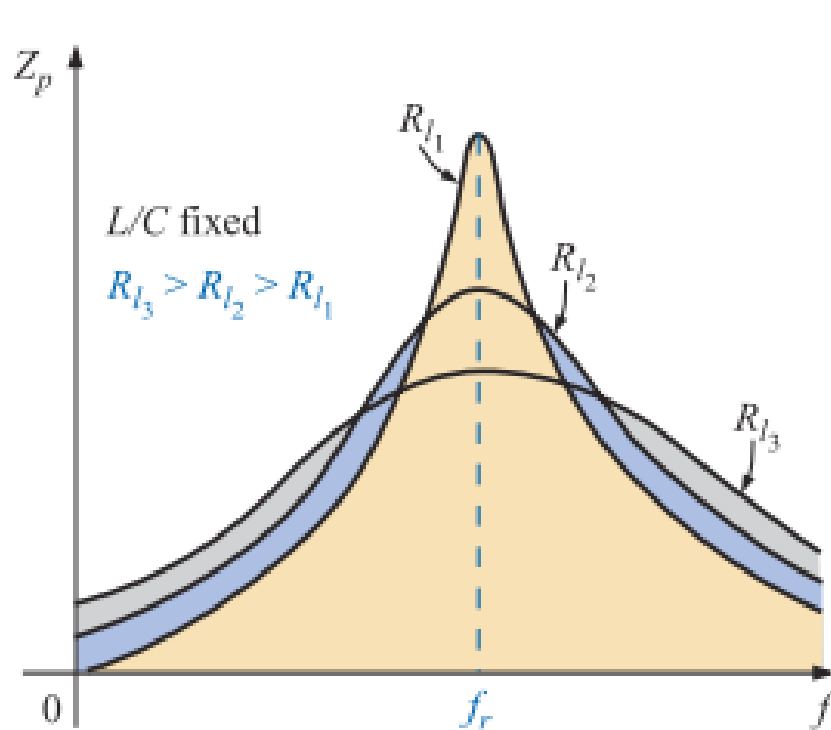
The effect of  $R$ ,  $L$ , and  $C$  on the shape



➤ The same effect as in series resonance
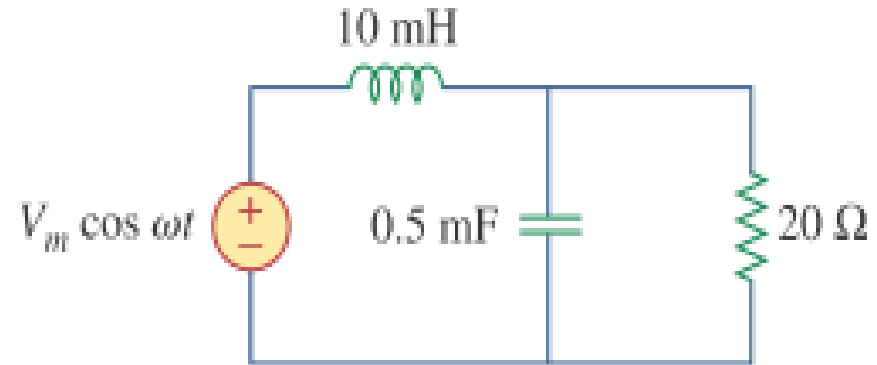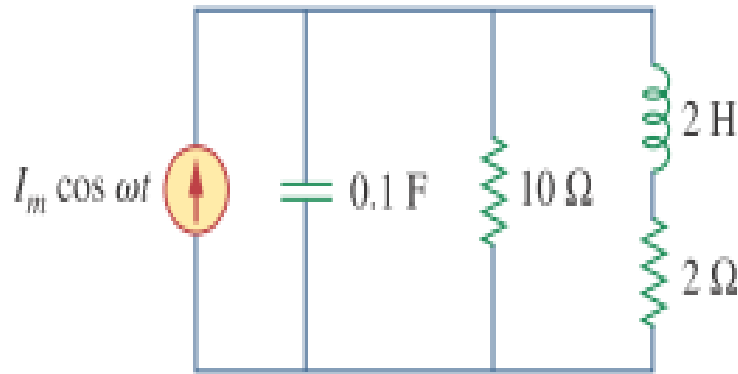
# Assignment No(1)

Determine the resonant frequency of the circuit in Fig.



➤ **Validate your analysis using simulation (Proteus or Multisim)**

- **Hint (1): review properties of resonant case to know how to validate the analysis using simulation**
- **Hint (2): you may use “current probe” + Oscilloscope in Multisim**
- **Hint (3): you may use “current probe” + Mixed Graph in Proteus**

- 1. Group solution is not permitted**
- 2. Cheating or copying other students work will not be tolerated)**

## FILTER NETWORKS


A **filter** is a circuit that is designed to pass signals with desired frequencies and reject or attenuate others.

- The filter can be treated as a networks designed to have frequency selective behavior
- A filter can be used to limit the frequency spectrum of a signal to some specified band of frequencies.
- Filters are the circuits used in radio and TV receivers to allow us to select one desired signal out of a multitude of broadcast signals in the environment


1. **Passive filter:** it consists of only passive elements R, L, and C.
2. **Active filter:** it consists of active elements (such as transistors and op amps) in addition to passive elements

# Filter Networks


## COMMON types of FILTERS

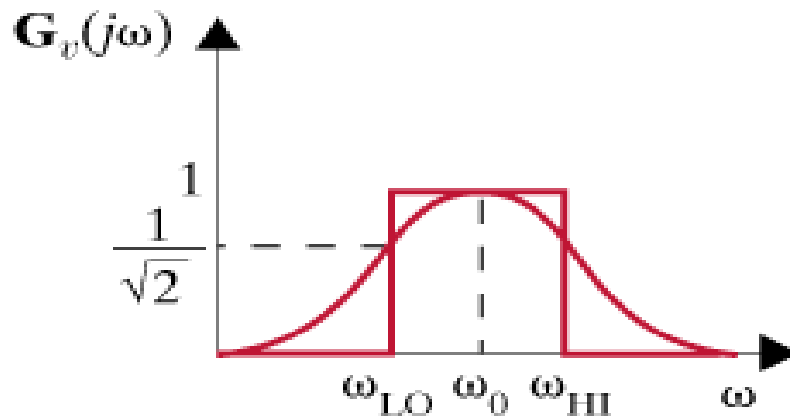


**Band-pass filter**

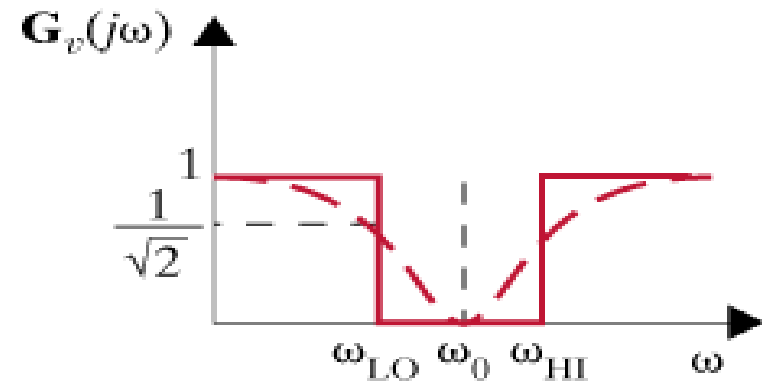

**Band-reject filter**

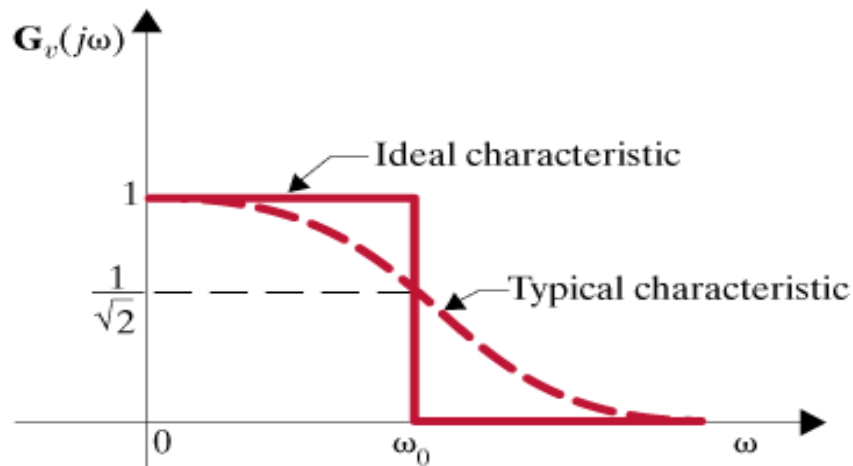

**Low-pass filter**

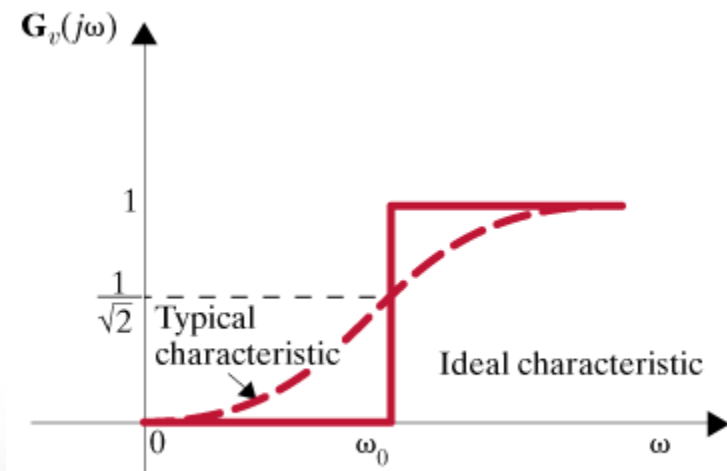

**High-pass filter**




Important Table for determining the type of the filter from its Transfer function

Summary of the characteristics of ideal filters.

Type of Filter	$H(0)$	$H(\infty)$	$H(\omega_c)$ or $H(\omega_0)$
Lowpass	1	0	$1/\sqrt{2}$
Highpass	0	1	$1/\sqrt{2}$
Bandpass	0	0	1
Bandstop	1	1	0
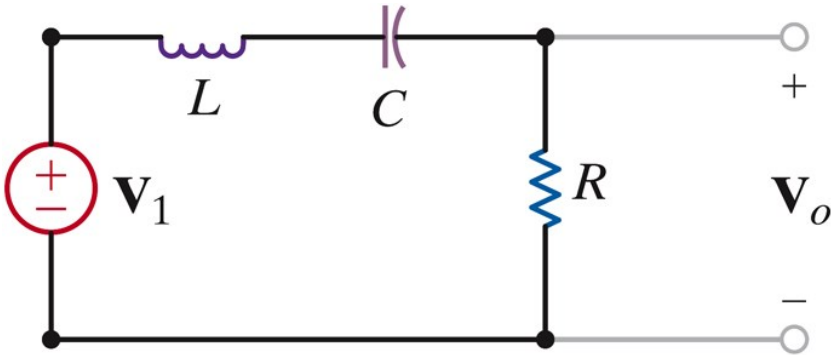
## Simple Passive band-pass filter

The RLC series resonant circuit provides a bandpass filter when the output is taken off the resistor as shown in Fig.



$$H = \frac{V_0}{V_1} = \frac{R}{R + j\left(\omega L - \frac{1}{\omega C}\right)}$$

Transfer Function


$$|H(\omega)| = \frac{\omega RC}{\sqrt{(\omega RC)^2 + (\omega^2 LC - 1)^2}}$$

$$H\left(\omega = \frac{1}{\sqrt{LC}}\right) = 1$$

$$H(\omega = 0) = H(\omega = \infty) = 0$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$
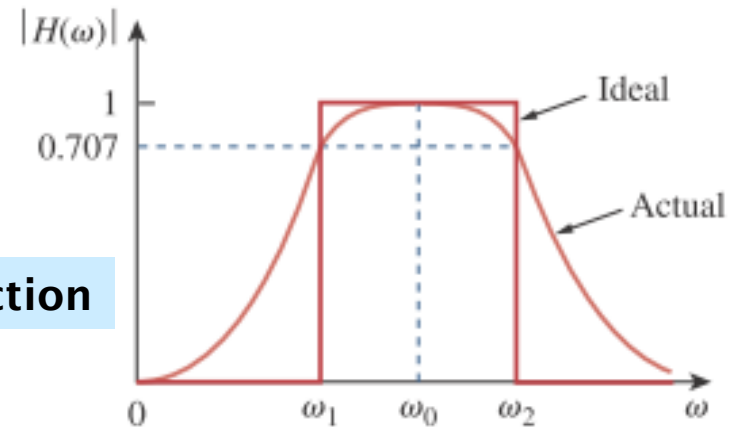
$$H(\omega_{LO}) = \frac{1}{\sqrt{2}} = M(\omega_{HI})$$




$$\omega_{LO} = \frac{-(R/L) + \sqrt{(R/L)^2 + 4\omega_0^2}}{2}$$


$$\omega_{HI} = \frac{(R/L) + \sqrt{(R/L)^2 + 4\omega_0^2}}{2}$$

$$BW = \omega_{HI} - \omega_{LO} = \frac{R}{L}$$

## Simple Passive band-stop filter

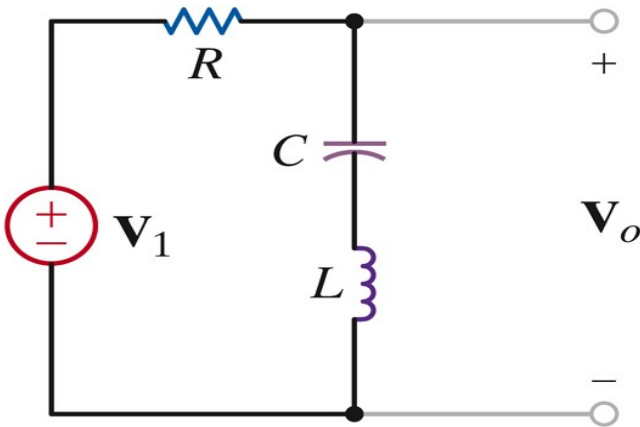

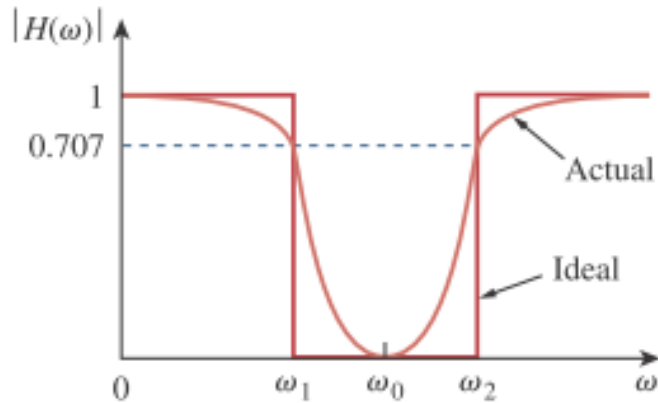- The RLC series resonant circuit provides a band-stop filter when the output is taken off the LC as shown in Fig.
- A filter that prevents a band of frequencies between two designated values
- It is also known as a band-stop, band-reject, or notch filter.



BW = Bandwidth of rejection

$$\mathbf{H(0) = 1, H(\infty) = 1.}$$

$$\mathbf{H(\omega) = \frac{V_o}{V_i} = \frac{j(\omega L - 1/\omega C)}{R + j(\omega L - 1/\omega C)}$$


$$\omega_0 = \frac{1}{\sqrt{LC}} \Rightarrow j\left(\omega_0 L - \frac{1}{\omega_0 C}\right) = 0$$

at  $\omega = 0$  the capacitor acts as open circuit  $\Rightarrow V_0 = V_1$

at  $\omega = \infty$  the inductor acts as open circuit  $\Rightarrow V_0 = V_1$


$\omega_1, \omega_2$  are determined as in the band - pass filter

## High-Pass Filter

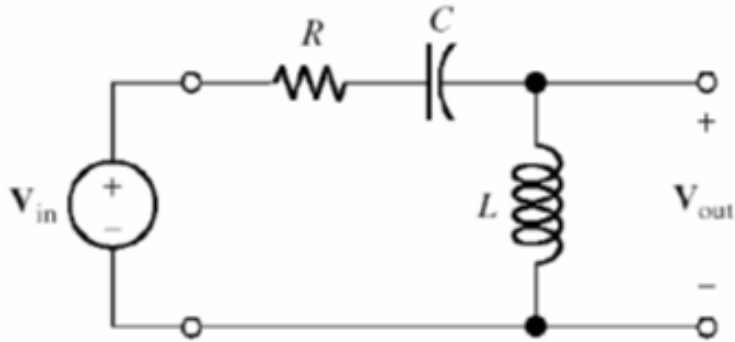


- At low frequency the capacitor is an open circuit ( $V_o = 0$ )
- At high frequency the capacitor is a short and the inductor is open ( $V_o = V_{in}$ )

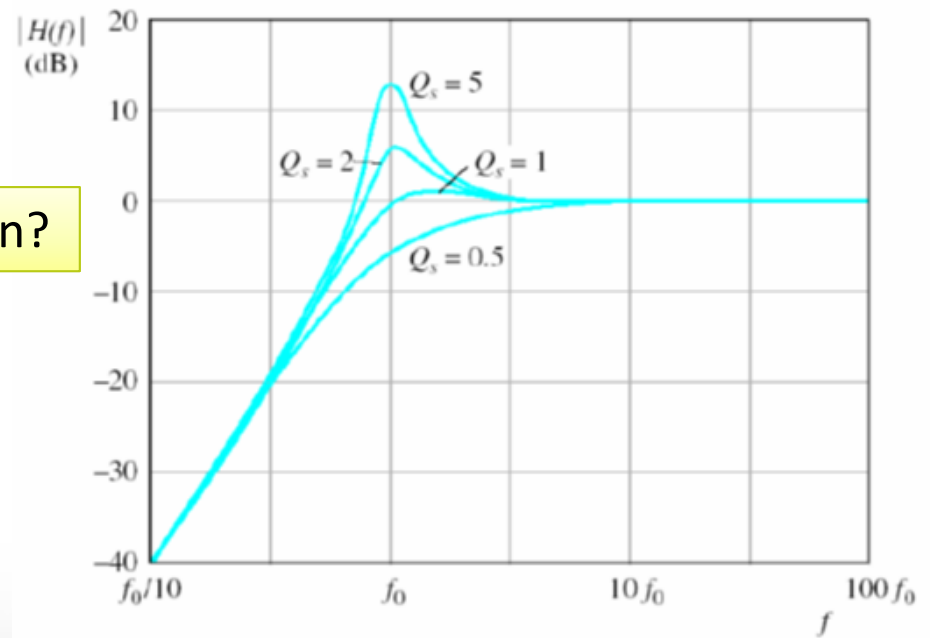Calculate/ Search for the transfer function?




## Low-Pass Filter

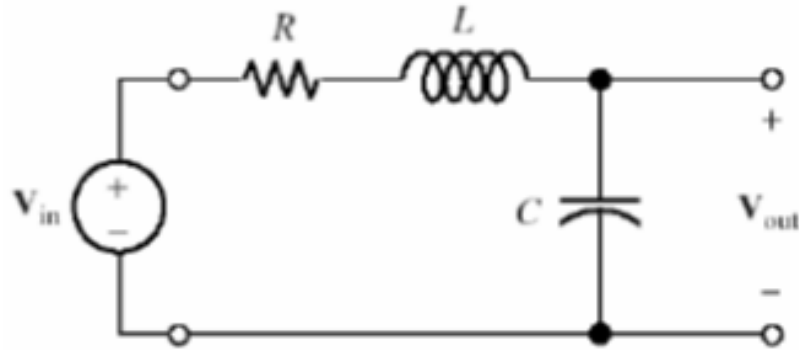


- At low frequency the capacitor is an open circuit ( $V_o = V_{in}$ )
- At high frequency the capacitor is a short and the inductor is open ( $V_o = 0$ )

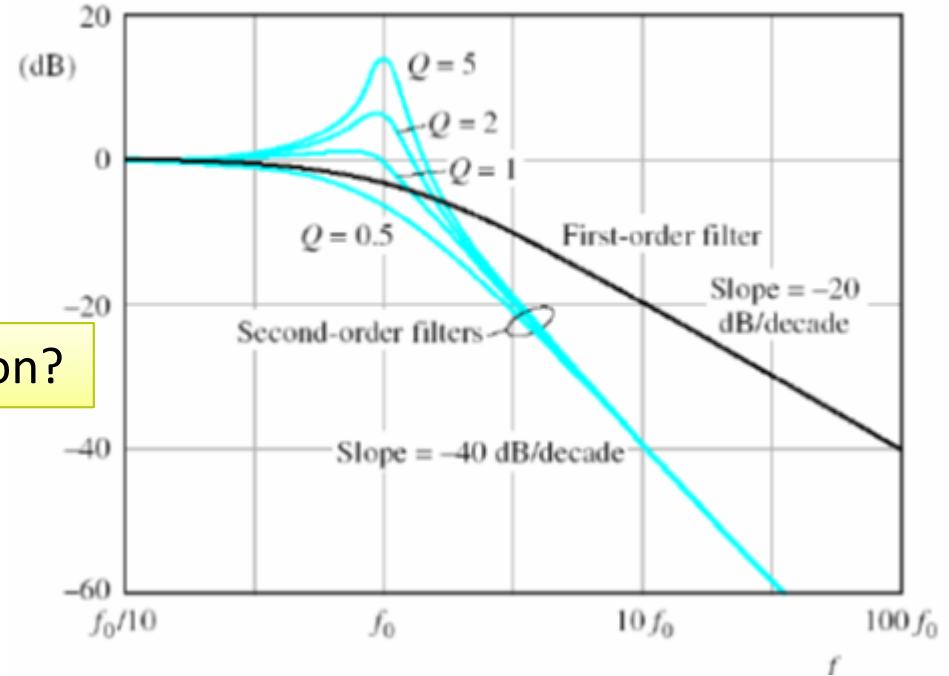
Calculate/ Search for the transfer function?



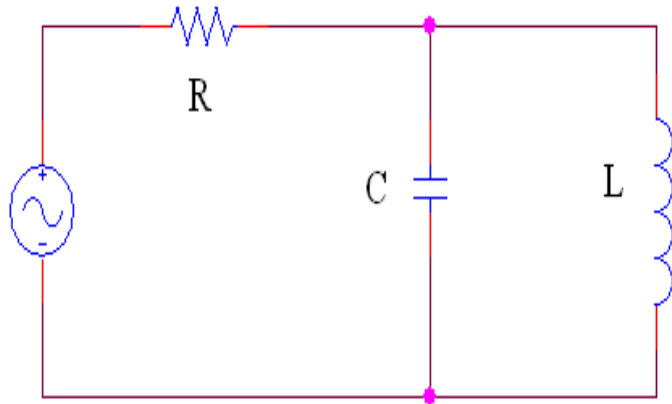Band-Pass Filter  
(Using Parallel Resonance Circuits)



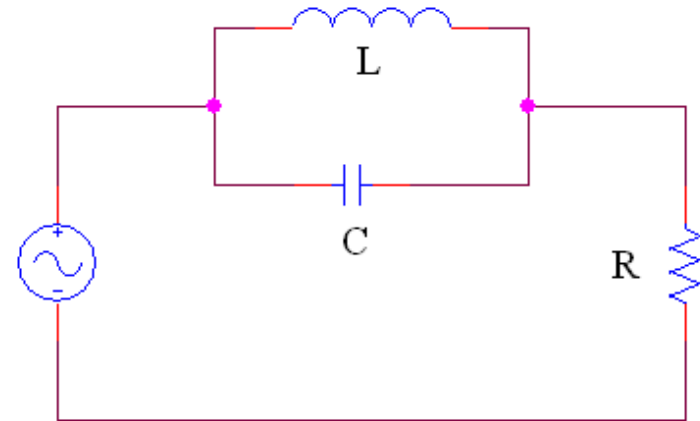Band-stop Filter  
(Using Parallel Resonance Circuits)



Calculate/ Search for the transfer function?

- All the previously described filters are **Second Order Filters** because they contain two reactive elements (L and C)
- It is possible to create another type of filters using RC or RL only (**First-order Filters**) >>> **not a complete series/parallel resonant circuit**

## Active Filters

**Passive filters have several limitations:**


- 1. Cannot generate gains greater than one**
- 2. Loading effect makes them difficult to interconnect**
- 3. Use of inductance makes them difficult to handle**

- **Using operational amplifiers one can design all basic filters, and more, with only resistors and capacitors**

**Thank you**



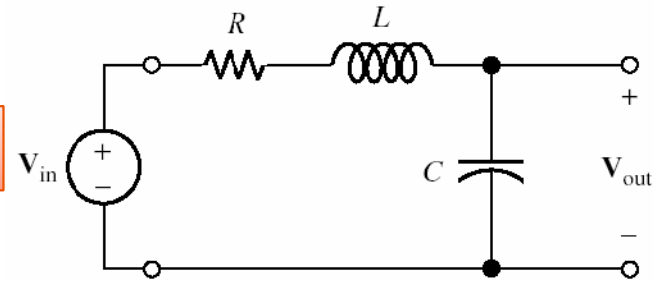
## Second Order Low-Pass Filter Transfer Function (1/2)



$$\mathbf{V}_{out} = \frac{Z_C}{Z_R + Z_L + Z_C} \mathbf{V}_{in} = \frac{\frac{-j}{2\pi f C}}{R + j2\pi f L - \frac{j}{2\pi f C}} \mathbf{V}_{in} = \frac{\frac{-j}{2\pi f RC}}{1 + j \frac{2\pi f_0 L}{R} \left( \frac{f}{f_0} - \frac{1}{2\pi f f_0 LC} \right)} \mathbf{V}_{in}$$

$$\frac{\mathbf{V}_{out}}{\mathbf{V}_{in}} = H(f) = \frac{\frac{-j}{2\pi f RC}}{1 + j \frac{2\pi f_0 L}{R} \left( \frac{f}{f_0} - \frac{1}{2\pi f f_0 LC} \right)} = \frac{-jQ_S(f/f_0)}{1 + jQ_S \left( \frac{f}{f_0} - \frac{f_0}{f} \right)}$$

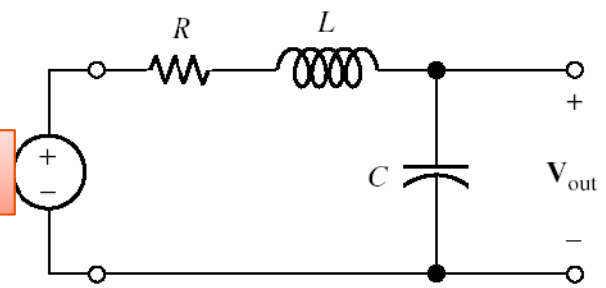Second Order Low-Pass Filter Transfer Function (2/2)



$$\begin{aligned}
 H(f) &= \frac{V_{\text{out}}}{V_{\text{in}}} = \frac{-jQ_s(f_0/f)}{1 + jQ_s(f/f_0 - f_0/f)} \\
 &= \frac{Q_s(f_0/f) \angle -90^\circ}{\sqrt{1 + Q_s^2(f/f_0 - f_0/f)^2} \angle \tan^{-1} Q_s(f/f_0 - f_0/f)} \\
 |H(f)| &= \frac{Q_s(f_0/f)}{\sqrt{1 + Q_s^2(f/f_0 - f_0/f)^2}}
 \end{aligned}$$