

# Electrical Circuits (2)

## Lecture 8


### Transient Analysis Part(2)

Dr.Eng. Basem ElHalawany
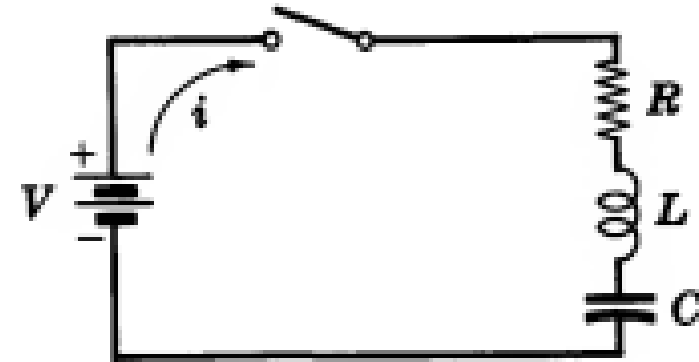
## Second-Order RLC Transient (Step Response)

- The Switch “S” is closed at  $t=0$
- Applying KVL will produce the following Integro-Differential equation:

$$Ri + L \frac{di}{dt} + \frac{1}{C} \int i dt = V$$



- Differentiating, we obtain

$$L \frac{d^2i}{dt^2} + R \frac{di}{dt} + \frac{i}{C} = 0 \quad \text{or} \quad \left( D^2 + \frac{R}{L}D + \frac{1}{LC} \right) i = 0$$

This **second order**, linear differential equation is of the **homogeneous** type with a **particular solution of zero**.

- ✓ The complementary function can be one of **three different types** according to **the roots of the auxiliary equation** which depends upon the relative magnitudes of R, L and C.

$$m^2 + \frac{R}{L}m + \frac{1}{LC} = 0$$

## Second-Order RLC Transient (Step Response)

We can Rewrite the auxiliary equation as:

$$m^2 + \frac{R}{L}m + \frac{1}{LC} = 0$$

$$m^2 + 2\zeta\omega_0 m + \omega_0^2 = 0$$

$\zeta$  : exponential damping ratio

$\omega_0$  : undamped natural frequency

$$\begin{cases} \frac{R}{L} = 2\zeta\omega_0 \\ \frac{1}{\sqrt{LC}} = \omega_0 \end{cases}$$

➤ The roots of the equation (or natural frequencies):

$$\begin{cases} m_1 = -\zeta\omega_0 + \omega_0\sqrt{\zeta^2 - 1} \\ m_2 = -\zeta\omega_0 - \omega_0\sqrt{\zeta^2 - 1} \end{cases}$$

$$\begin{cases} m_1 = -\frac{R}{2L} + \sqrt{\frac{R^2}{4L^2} - \frac{1}{LC}} \\ m_2 = -\frac{R}{2L} - \sqrt{\frac{R^2}{4L^2} - \frac{1}{LC}} \end{cases}$$

$$\begin{cases} m_1 = -\sigma + \sqrt{\sigma^2 - \omega_0^2} \\ m_2 = -\sigma - \sqrt{\sigma^2 - \omega_0^2} \end{cases}$$

# Second-Order RLC Transient (Step Response)

**Case 1: Overdamped,**

$$\zeta > 1$$

$\Rightarrow m_1, m_2$  are real and unequal

$$\frac{R}{2L} > \frac{1}{\sqrt{LC}}$$

$$\sigma^2 > \omega_0^2$$

$$\begin{cases} m_1 = -\zeta\omega_0 + \omega_0\sqrt{\zeta^2 - 1} \\ m_2 = -\zeta\omega_0 - \omega_0\sqrt{\zeta^2 - 1} \end{cases}$$

Natural response is the sum of two decaying exponentials:

$$i_{tr} = K_1 e^{m_1 t} + K_2 e^{m_2 t}$$

**Case 2: Critically damped,**

$$\zeta = 1$$

$\Rightarrow m_1, m_2$  are real and equal.

$$\frac{R}{2L} = \frac{1}{\sqrt{LC}}$$

$$\sigma^2 = \omega_0^2$$

$$m_1 = m_2 = -\omega_0$$

$$x_c(t) = e^{m_1 t} (B_1 + B_2 t)$$

**Use the initial conditions to get the constants**

**Usually it is reduced to:**

$$x_c(t) = B.t.e^{m_1 t}$$

## Case 3: Underdamped,

$$\zeta < 1$$

$$\frac{R}{2L} < \frac{1}{\sqrt{LC}}$$


$$\sigma^2 < \omega_o^2$$

$\Rightarrow m_1, m_2$  are complex and conjugate.

$$\begin{cases} m_1 = -\sigma + j\omega_d = (-\zeta\omega_0) + j(\omega_0\sqrt{1-\zeta^2}) \\ m_2 = -\sigma - j\omega_d = (-\zeta\omega_0) - j(\omega_0\sqrt{1-\zeta^2}) \end{cases}$$

Natural response is an exponentially damped oscillatory response:
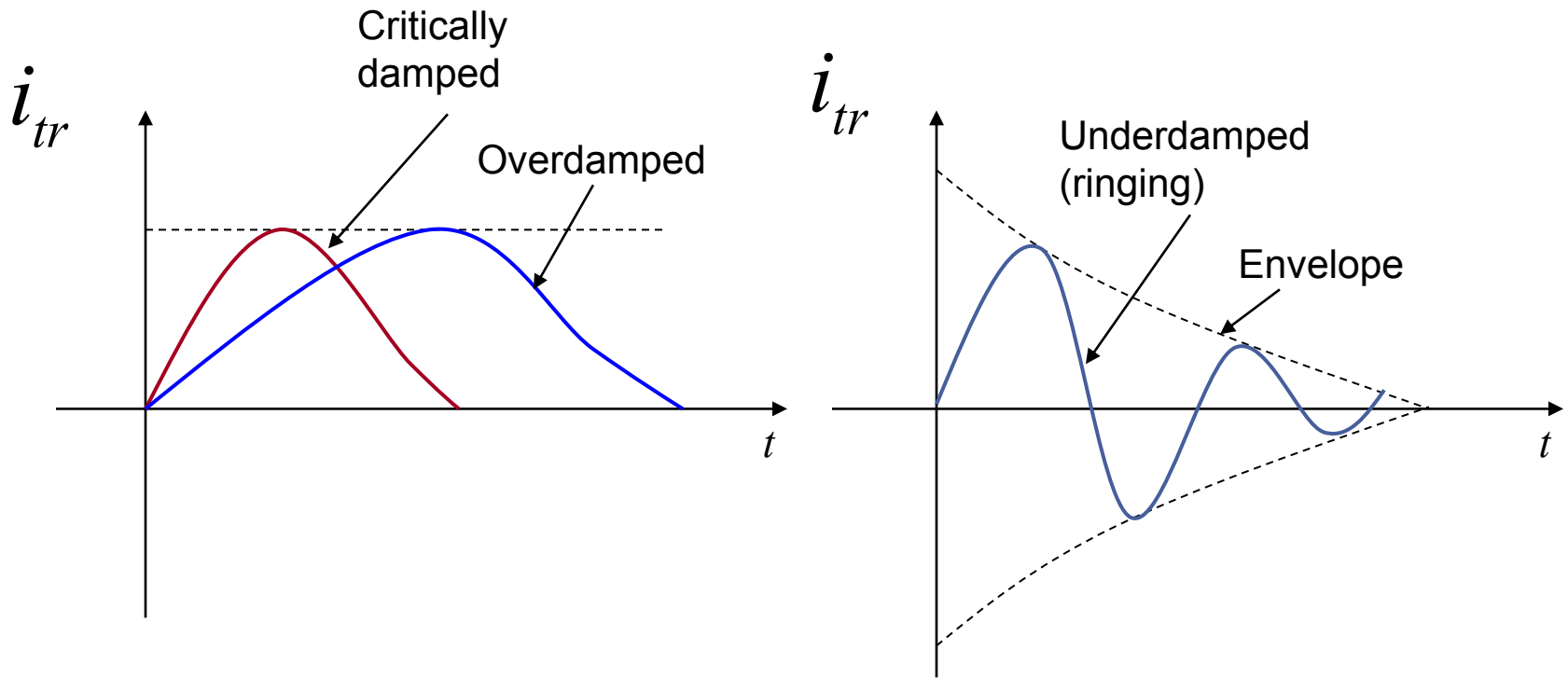
$$i_{tr} = e^{-\sigma t} \{A_1 \cos(\omega_d t) + A_2 \sin(\omega_d t)\}$$




- ✓ The current in all cases contains the exponential decaying factor (damping factor) assuring that the final value is zero
- ✓ In other words, assuring that the complementary function decays in a relatively short time.

# Alternating Current Transients
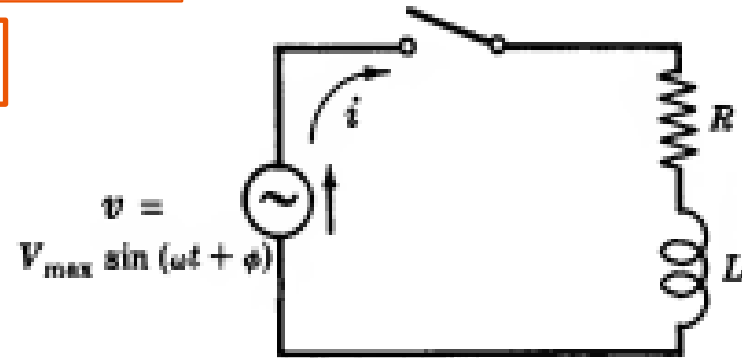
## RL Sinusoidal Transient

$$Ri + L \frac{di}{dt} = V_{\max} \sin(\omega t + \phi)$$

$$\left(D + \frac{R}{L}\right)i = \frac{V_{\max}}{L} \sin(\omega t + \phi)$$



1. Complementary (Transient) Solution is the solution of the homogeneous 1<sup>st</sup> order DE

The same as before, The auxiliary equation is :

$$m + \frac{R}{L} = 0$$

**The complementary function is  $i_c = ce^{-(R/L)t}$**

2. Particular (Steady-State) Solution

The steady-state value of the current for ac source is :

$$I_{ss} = \frac{V_{\max}}{\sqrt{X_L^2 + R^2}} \sin(\omega t + \phi - \tan^{-1}(\omega L / R))$$

# Alternating Current Transients

## RL Sinusoidal Transient

The complete solution is

$$i = i_c + i_p = ce^{-(R/L)t} + \frac{V_{\max}}{\sqrt{R^2 + \omega^2 L^2}} \sin(\omega t + \phi - \tan^{-1} \omega L/R)$$

Use the initial condition to find the value of c

$$i_0 = 0 = c(1) + \frac{V_{\max}}{\sqrt{R^2 + \omega^2 L^2}} \sin(\phi - \tan^{-1} \omega L/R)$$

$$c = \frac{-V_{\max}}{\sqrt{R^2 + \omega^2 L^2}} \sin(\phi - \tan^{-1} \omega L/R)$$


Substituting by the constant values, we get:

$$i = e^{-(R/L)t} \left[ \frac{-V_{\max}}{\sqrt{R^2 + \omega^2 L^2}} \sin(\phi - \tan^{-1} \omega L/R) \right] + \frac{V_{\max}}{\sqrt{R^2 + \omega^2 L^2}} \sin(\omega t + \phi - \tan^{-1} \omega L/R) \quad (5)$$



# Alternating Current Transients

## RC Sinusoidal Transient

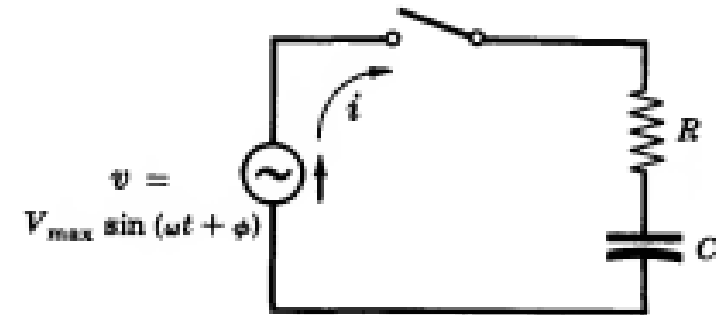

$$i = e^{-t/RC} \left[ \frac{V_{\max}}{R} \sin \phi - \frac{V_{\max}}{\sqrt{R^2 + (1/\omega C)^2}} \sin(\phi + \tan^{-1} 1/\omega CR) \right] + \frac{V_{\max}}{\sqrt{R^2 + (1/\omega C)^2}} \sin(\omega t + \phi + \tan^{-1} 1/\omega CR)$$

# Alternating Current Transients


## RLC Sinusoidal Transient

### ➤ Particular (Steady-State) Solution

$$i_p = \frac{V_{\max}}{\sqrt{R^2 + (1/\omega C - \omega L)^2}} \sin\left(\omega t + \phi + \tan^{-1} \frac{(1/\omega C - \omega L)}{R}\right)$$
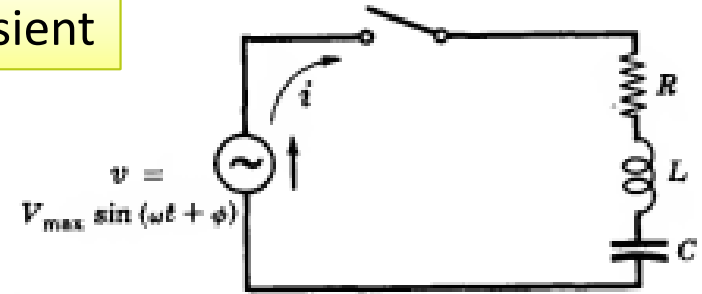
### ➤ Complementary(Transient) Solution

The complementary function is identical to that of the DC series RLC circuit examined previously where the result was overdamped, critically damped or oscillatory, depending upon R, L and C.




For the complete analysis  
Check Chapter 16 Schaum Series (Old version)

# Transient Analysis using Laplace Transform

- Laplace transform is considered one of the most important tools in Electrical Engineering
- It can be used for:
  - ✓ Solving differential equations
  - ✓ Circuit analysis (Transient and general circuit analysis)
  - ✓ Digital Signal processing in Communications and
  - ✓ Digital Control

# Transient Analysis using Laplace Transform

## Circuit Elements in the “S” Domain

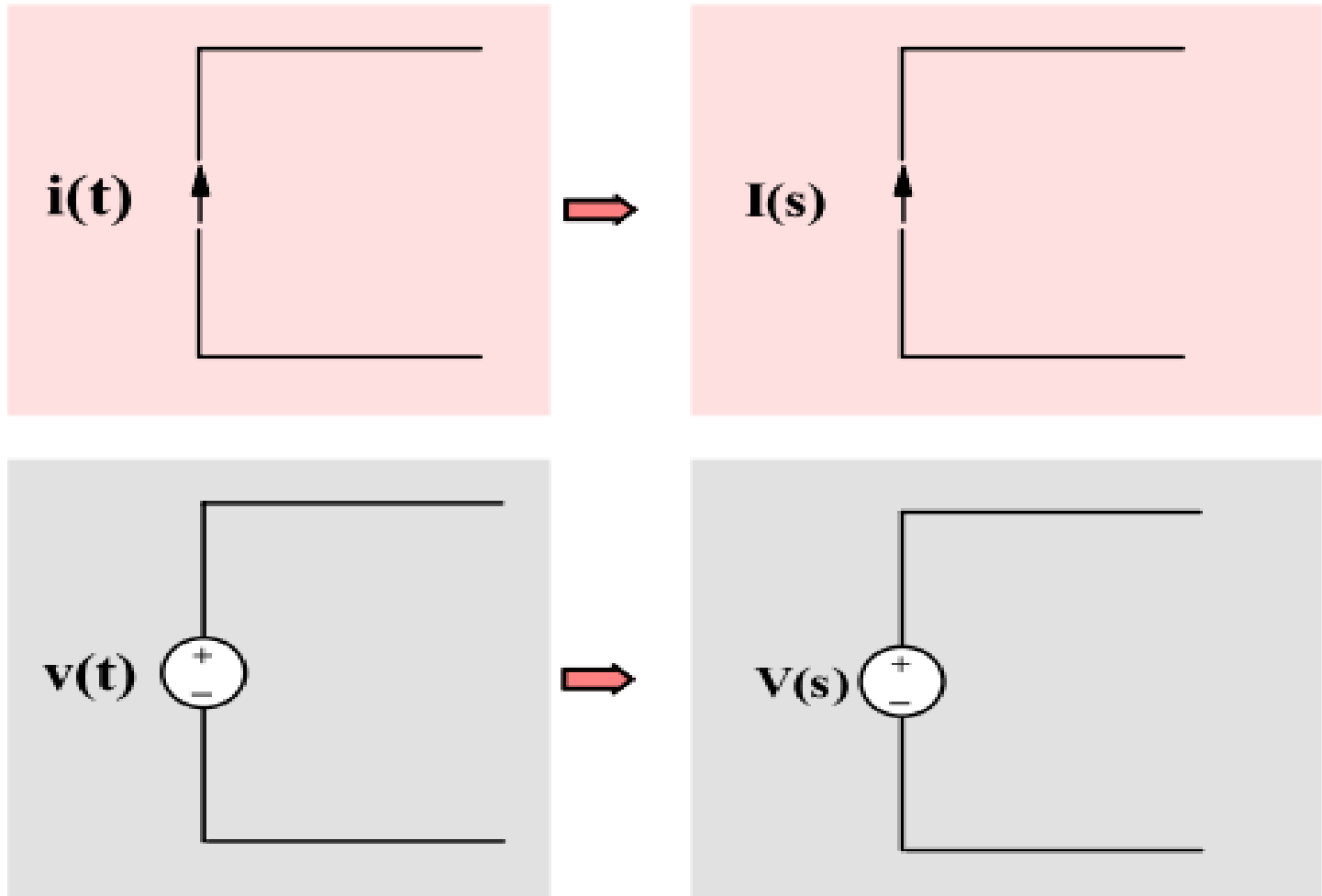

# Circuit Elements in the “S” Domain



## Circuit Element Modeling

The method used so far follows the steps:

1. Write the differential equation model
2. Use Laplace transform to convert the model to an algebraic form

### 1.0 Resistance


#### Resistor

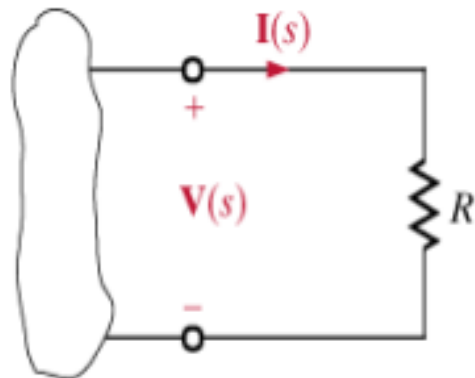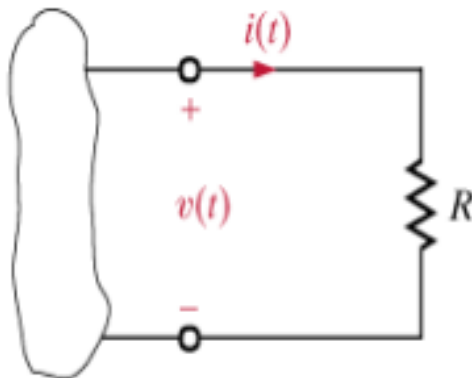

$$v(t) = Ri(t) \Rightarrow V(s) = RI(s)$$


# Circuit Elements in the “S” Domain

## 2.0 Inductor

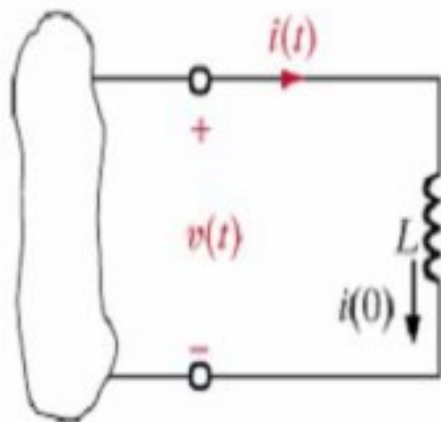


$$v(t) = L \frac{di}{dt}(t)$$

$\Rightarrow$

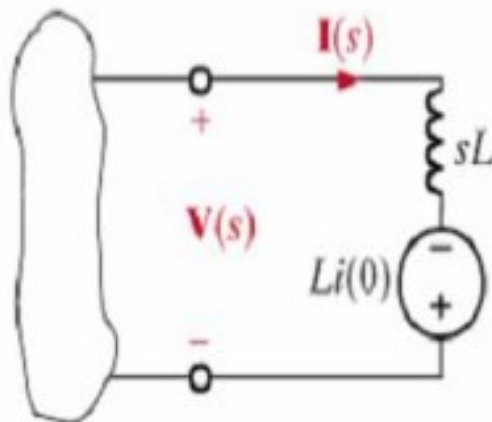

$$V(s) = LsI(s) - Li(0)$$


$\Rightarrow$

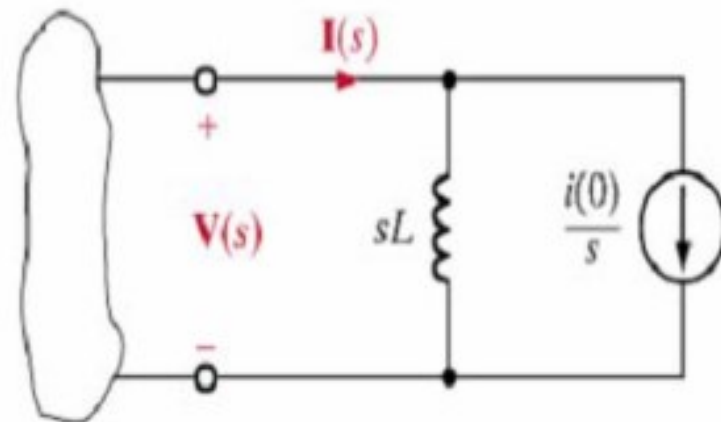


$$I(s) = \frac{V(s)}{Ls} + \frac{i(0)}{s}$$

# Circuit Elements in the “S” Domain


## 3.0 Capacitor

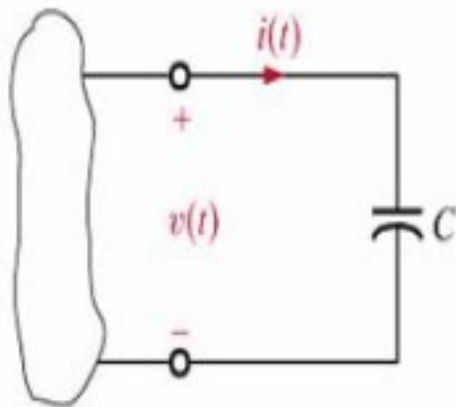
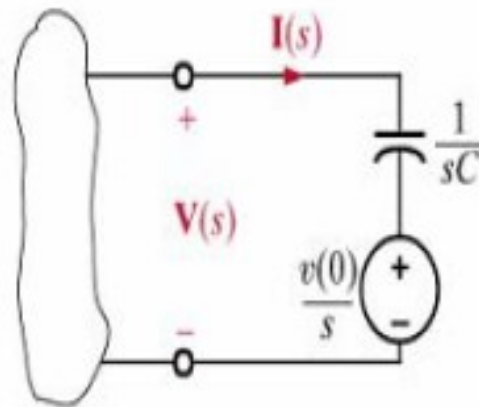
$$v_c(t) = \frac{1}{C} \int_0^t i(t) dt + v_c(0)$$


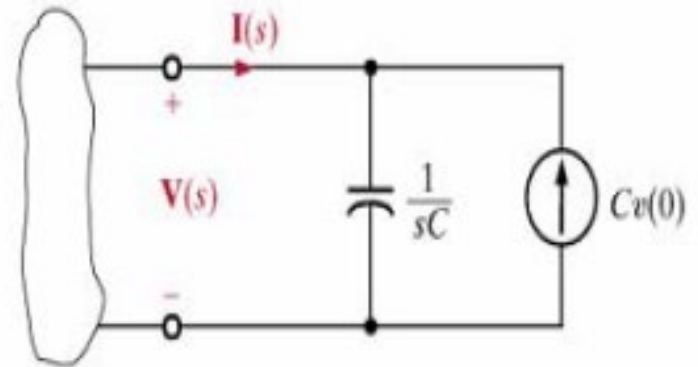
$$V(s) = \frac{1}{Cs} I(s) + \frac{v(0)}{s}$$



$$I(s) = CsV(s) - Cv(0)$$

# First-Order RL Transient (Step-Response)

- The switch “S” is closed at  $t = 0$  to allow the step voltage to excite the circuit
- Apply KVL to the circuit in figure:

$$Ri + L \frac{di}{dt} = V$$

- Apply Laplace Transform on both sides


$$R.I(s) + L[s.I(s) - i(0)] = \frac{V}{s}$$

$i(0) = 0$  >> initial value of the current at  $t = 0$

$$I(s).[R + sL] = \frac{V}{s}$$

$$I(s) = \frac{V}{s[R + sL]} = \frac{V/L}{s[s + R/L]}$$

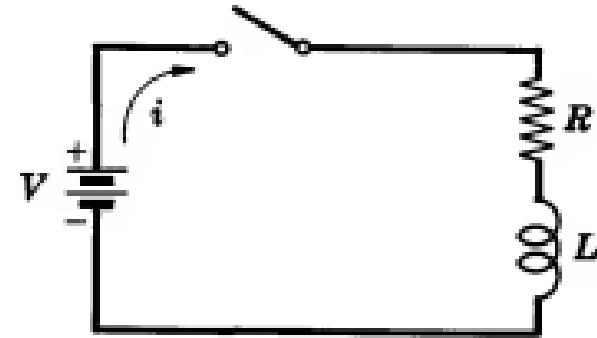- Apply the inverse Laplace Transform technique to get the expression of the current  $i(t)$





# First-Order RL Transient (Step-Response)

- Use the partial fraction technique

$$I(s) = \frac{V/L}{s[s + R/L]} = \frac{A_1}{s} + \frac{A_2}{s + R/L}$$

- Multiply both sides by  $s.(s + R/L)$

$$V/L = A_1.(s + R/L) + A_2.s$$

$$\dots\dots = (A_1 + A_2).s + A_1 \cdot \frac{R}{L}$$

$$A_1 = V/R \quad A_2 = -V/R$$

- So, the current in s-domain is given by:

- Apply the inverse Laplace transform :

The same as last lecture

OR

$$A_1 = sI(s) \Big|_{s=0} = \frac{V}{R}$$

$$A_2 = (s + R/L)I(s) \Big|_{s=-R/L} = -\frac{V}{R}$$

both sides Compare the coefficients

$$I(s) = \frac{V}{R} \left( \frac{1}{s} - \frac{1}{s + R/L} \right)$$

$$i(t) = \frac{V}{R} \left( 1 - e^{-\frac{R}{L}t} \right); t > 0$$

# First-Order RL Transient (Discharge)

- The RL circuit shown in Figure contains an initial current of  $(V/R)$
- The Switch "S" is moved to position "2" at  $t=0$

$$L \frac{di}{dt} + Ri = 0$$

- Apply Laplace Transform on both sides

$$R.I(s) + L[s.I(s) - i(0)] = 0$$

$i(0) = V/R$  >> initial value of the current at  $t = 0$

$$R.I(s) + L[s.I(s) - \frac{V}{R}] = 0$$




$$I(s) = \frac{V/R}{[s + R/L]}$$

- Apply the inverse Laplace transform :

$$i(t) = \frac{V}{R} \cdot e^{-\frac{R}{L}t} = I_o \cdot e^{-\frac{R}{L}t} ; t > 0$$

- The same as before

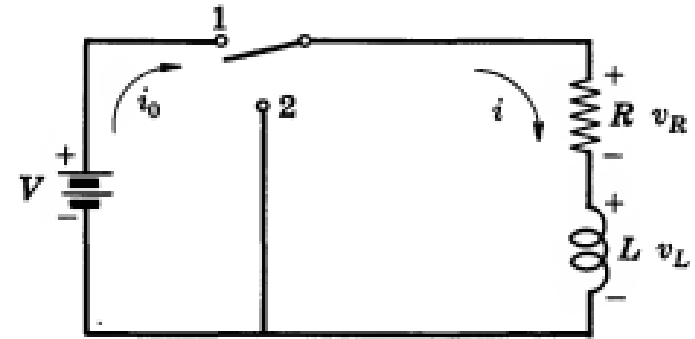

# First-Order RC Transient (Step-Response)

- Assume the switch S is closed at  $t = 0$
- Apply KVL to the series RC circuit shown:

$$\left[ \frac{1}{C} \int i(t) \cdot dt + v_c(0) \right] + R \cdot i(t) = V$$

- Apply Laplace Transform on both sides

$$\left[ \frac{I(s)}{Cs} + \frac{v_c(0)}{s} \right] + R \cdot I(s) = \frac{V}{s}$$

$V_c(0) = 0$  >> initial value of the voltage at  $t = 0$


$$I(s) \cdot \left[ R + \frac{1}{Cs} \right] = \frac{V}{s}$$

$$I(s) = \frac{V/s}{\left[ R + \frac{1}{Cs} \right]} = \frac{V/R}{\left[ s + \frac{1}{CR} \right]}$$

- Apply the inverse Laplace Transform technique to get the expression of the current  $i(t)$

$$i(t) = \frac{V}{R} e^{-\frac{1}{RC}t}; t > 0$$

The same as last lecture

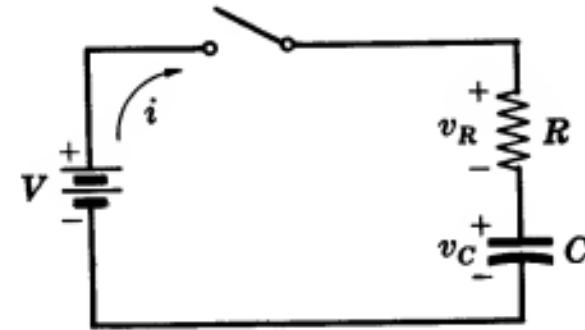

# Second-Order RLC Transient (Step Response)

- The Switch "S" is closed at  $t=0$
- Applying KVL will produce the following Integro-Differential equation:

$$\left[ \frac{1}{C} \int i(t) \cdot dt + v_c(0) \right] + L \frac{di(t)}{dt} + R \cdot i(t) = V$$

- Apply Laplace Transform on both sides

$$\left[ \frac{I(s)}{Cs} + \frac{v_c(0)}{s} \right] + L \cdot [s \cdot I(s) - i(0)] + R \cdot I(s) = \frac{V}{s}$$

$$I(s) = \frac{V/s}{[R + sL + 1/Cs]} = \frac{V/L}{[s^2 + s \cdot (R/L) + 1/LC]}$$


Assume:

$$v_c(0) = 0 \text{ \& } i(0) = 0$$

- To convert this to time-domain, it will depend on the roots of the denominator which could be expressed as:

$(s-S1) \cdot (s-S2) \ggggg$  similar to last lecture  $(m-m1) \cdot (m-m2)$
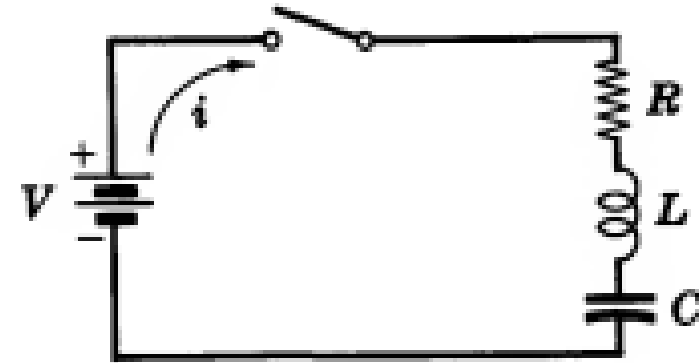
$$m^2 + \frac{R}{L}m + \frac{1}{LC} = 0$$



## Second-Order RLC Transient (Step Response)

$$S_{1,2} = \frac{-R}{2L} \mp \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$\zeta$  : exponential damping ratio

$\omega_0$  : undamped natural frequency

$$S_{1,2} = -\zeta\omega_0 \mp \omega_0\sqrt{\zeta^2 - 1}$$

$$S_{1,2} = -\sigma \mp \sqrt{\sigma^2 - \omega_0^2}$$

➤ Apply Partial Fraction:

$$I(s) = \frac{V/L}{[s^2 + s.(R/L) + 1/LC]} = \frac{A}{s - S_1} + \frac{B}{s - S_2}$$

$$A = (s - S_1).I(s) \Big|_{s=S_1} = \frac{V}{2L.\omega_0\sqrt{\zeta^2 - 1}}$$

$$B = (s - S_2).I(s) \Big|_{s=S_2} = \frac{-V}{2L.\omega_0\sqrt{\zeta^2 - 1}} = -A$$

$$I(s) = \frac{V}{2L.\omega_0\sqrt{\zeta^2 - 1}} \cdot \left[ \frac{1}{s - S_1} - \frac{1}{s - S_2} \right]$$

# Second-Order RLC Transient (Step Response)

➤ Apply Partial According to the values of the roots , we have 3 scenarios:

1. Over-damped Case

i.e. Two real distinct roots

$$i(t) = \frac{V}{2L\omega_o \sqrt{\zeta^2 - 1}} \cdot [e^{S_1 t} - e^{S_2 t}]$$

1. Critically-damped Case

i.e. Two real equal roots  $\sigma = \omega_o$

$$S_1 = S_2 = -\sigma = \frac{-R}{2L}$$

$$I(s) = \frac{V/L}{[s^2 + s \cdot (R/L) + 1/LC]} = \frac{V/L}{(S - S_1)^2} = \frac{V/L}{(S + \sigma)^2} = \frac{V/L}{(S + \omega_o)^2}$$

Convert by inverse L.T:

$$\frac{1}{(S + a)^n} \Leftrightarrow \frac{t^{n-1}}{(n-1)!} \cdot e^{-at}$$

$$i(t) = \frac{V}{L} \cdot t \cdot e^{S_1 t} = \frac{V}{L} \cdot t \cdot e^{-\omega_o t}$$

## Second-Order RLC Transient (Step Response)

### 3. Under-damped Case

i.e. Two Complex-conjugate roots


$$S_{1,2} = -\sigma \mp \sqrt{\sigma^2 - \omega_0^2} = -\sigma \mp j\omega_d$$

$$i(t) = e^{\sigma \cdot t} [A_1 \cos(\omega_d t) + A_2 \sin(\omega_d t)]$$

$$\dots = Ae^{\sigma \cdot t} \left[ \frac{A_1}{A} \cos(\omega_d t) + \frac{A_2}{A} \sin(\omega_d t) \right]$$

$$\dots = Ae^{\sigma \cdot t} [\sin \psi \cdot \cos(\omega_d t) + \cos \psi \cdot \sin(\omega_d t)]$$
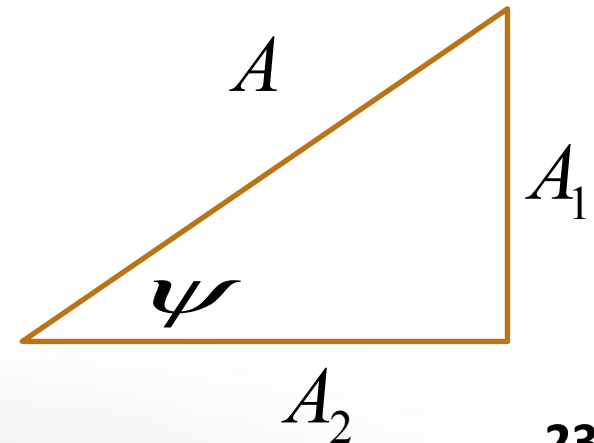
$$\dots = Ae^{\sigma \cdot t} \sin(\omega_d t + \psi)$$



## RL Sinusoidal Transient

$R = 5 \text{ ohms}$ ,  $L = 0.01 \text{ H}$ ,  $V_m = 100 \text{ volts}$ ,  $\phi = 0$ ,  $\omega = 500$

$$Ri + L \frac{di}{dt} = V_{\max} \sin(\omega t + \phi)$$

➤ Apply Laplace Transform on both sides

$$R.I(s) + L[s.I(s) - i(0)] = 100 \frac{\omega}{s^2 + \omega^2}$$

$i(0) = 0$  >> initial value of the current at  $t = 0$


$$I(s) \cdot [L(s + \frac{R}{L})] = 100 \frac{\omega}{s^2 + \omega^2}$$

$$I(s) = \frac{100 \cdot \omega}{L \cdot (s^2 + \omega^2) \cdot (s + \frac{R}{L})} = \frac{5 \times 10^6}{(s^2 + \omega^2) \cdot (s + 500)}$$

$$S_1 = -500$$

$$S_2 = -j\omega$$

$$S_3 = j\omega$$

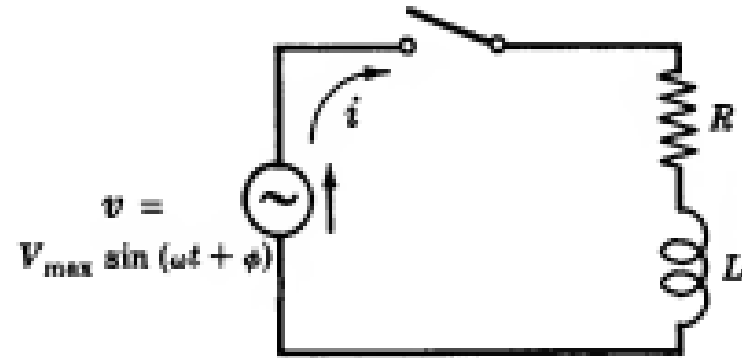



## RL Sinusoidal Transient

➤ Use Partial Fraction:

$$I(s) = \frac{5 \times 10^6}{(s^2 + \omega^2) \cdot (s + 500)} = \frac{A_1}{s - j\omega} + \frac{A_2}{s + j\omega} + \frac{A_3}{s + 500}$$

OR

$$= \frac{B_1 s + B_2}{s^2 + \omega^2} + \frac{A_3}{s + 500}$$

Compare to find the constants:


$$I(s) = \frac{10[-s + 500]}{s^2 + \omega^2} + \frac{10}{s + 500} = 10 \cdot \frac{500}{s^2 + 500^2} - 10 \cdot \frac{s}{s^2 + 500^2} + \frac{10}{s + 500}$$

➤ Use Inverse L.T.  $i(t) = 10 \cdot \sin(500t) - 10 \cdot \cos(500t) + 10 \cdot e^{-500t}$

$$i(t) = 10 \cdot [\sin(500t) - \cos(500t)] + 10 \cdot e^{-500t}$$

$$A = \sqrt{1^2 + (-1)^2} = \sqrt{2}$$


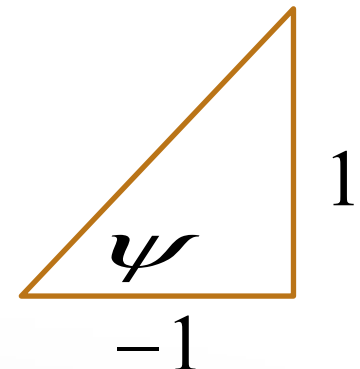
$$\psi = \tan^{-1} \left( \frac{1}{-1} \right) = 45^\circ$$



$$i(t) = 10 \cdot \sqrt{2} \cdot \sin(500t - 45^\circ) + 10 \cdot e^{-500t} = I_{s.s} + I_{tr}$$
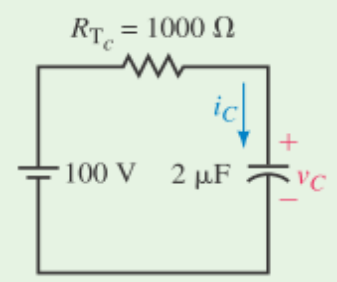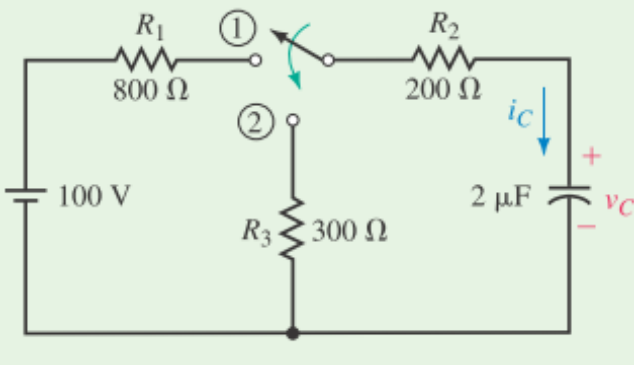
# Examples


The capacitor of Figure 11–24(a) is uncharged. The switch is moved to position 1 for 10 ms, then to position 2, where it remains.



$$\tau_C = (R_1 + R_2)C = (1 \text{ k}\Omega)(2 \mu\text{F}) = 2.0 \text{ ms.}$$

a.  $v_C = E(1 - e^{-t/\tau_C}) = 100(1 - e^{-500t}) \text{ V}$   
 b.  $i_C = \frac{E}{R_{Tc}} e^{-t/\tau_C} = \frac{100}{1000} e^{-500t} = 100e^{-500t} \text{ mA}$

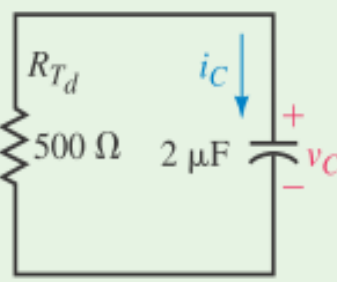(b) Charging circuit  
 $R_{Tc} = R_1 + R_2$





$$\tau_d = (500 \Omega)(2 \mu\text{F}) = 1.0 \text{ ms}$$

$$v_C = V_0 e^{-t/\tau_d} = 100 e^{-1000t} \text{ V}$$

$$i_C = -\frac{V_0}{R_2 + R_3} e^{-t/\tau_d} = -\frac{100}{500} e^{-1000t} = -200 e^{-1000t} \text{ mA}$$

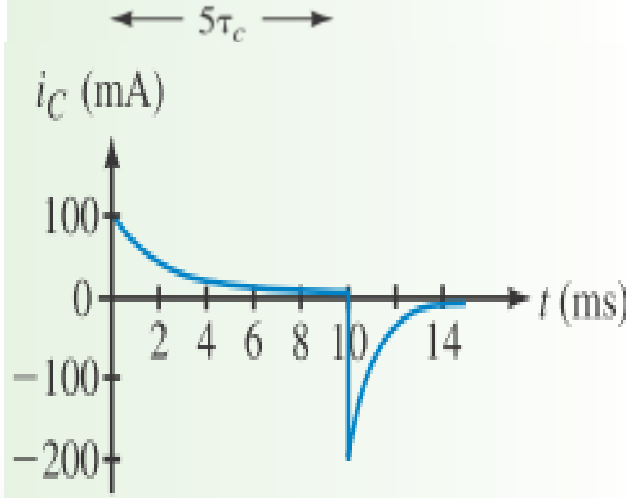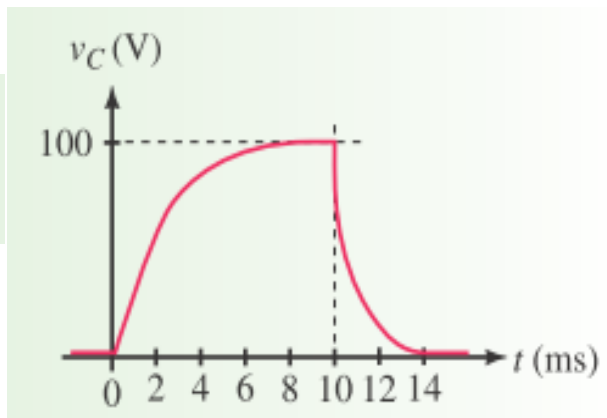(c) Discharging circuit  
 $V_0 = 100 \text{ V at } t = 0 \text{ s}$



Note that discharge is more rapid than charge since  $\tau_d < \tau_C$ .