

Electrical, Electronic and Digital Principles (EEDP)



Lecture 2 BJT Biasing

د. باسم ممدوح الحلوانى

Course Info

Title Electrical, Electronic and Digital Principles (EEDP)

Code T/601/1395

Lecturer: Dr. Basem ElHalawany

Lecturer Email: Basem.mamdoh@feng.bu.edu.eg /
Eng_basem2@yahoo.com

Lecturer Webpage: <http://www.bu.edu.eg/staff/basem.mamdoh>

Course Webpage <http://www.bu.edu.eg/staff/basem.mamdoh-courses/12138>

References Multiple references will be used

Software Packages Proteus Design Suite

Course Aims

This unit aims to develop learners' understanding of :

- **The electrical,**
- **Electronic and**
- **Digital principles**

needed for further study of electro-mechanical systems.



Course Contents

1. Apply complex notation in the analysis of single phase circuits

➤ Series and parallel LCR circuits:

- Voltage, current and power with sine wave signals;
- Conditions for resonance

➤ Circuit performance

- Tolerancing (effect of changes in component values)

2. Apply circuit theory to the solution of circuit problems

➤ Circuit theorems:

- Norton - Kirchhoff - Thevenin's
- Superposition - maximum power

➤ Circuit analysis:

- Mesh - nodal
- Impedance matching



Course Contents

3. Understand the operation of electronic amplifier circuits

➤ Single- and two-stage transistor amplifiers:

- Class of operation (A, B, AB and C) - analysis of bias - DC conditions
- AC conditions – coupling- input impedance - output impedance

➤ Design, test and evaluate a single-stage amplifier to a given specification

- compare measured (Implemented or simulated) and theoretical results

4. Be able to design and test digital electronic circuits

➤ Digital electronic devices

➤ Combinational circuits

➤ Design and test: circuit designed should be bread-boarded or simulated using an appropriate computer software package

Part 3

3. Understand the operation of electronic amplifier circuits

- ✓ A transistor must be **properly biased** in order to operate as an **amplifier**.
 - ✓ **DC biasing** is used to establish fixed dc values for the transistor currents and voltages - called the **dc operating point** or **quiescent point** (Q-point).
-
- ✓ In this lecture, several types of bias circuits are discussed.
 - ✓ This part lays the groundwork for the study of amplifiers, and other circuits that require proper biasing.



ELECTRONIC DEVICES
9th Edition
Thomas L. Floyd

5


TRANSISTOR BIAS CIRCUITS

- 5-1 The DC Operating Point
- 5-2 Voltage-Divider Bias
- 5-3 Other Bias Methods



 5-1 THE DC OPERATING POINT

- A transistor must be **properly biased** with a dc voltage in order to operate as a **linear amplifier**.
- A dc operating point **must be set** so **that signal variations** at the input terminal are amplified and accurately reproduced at the output terminal.



(a) Linear operation: larger output has same shape as input except that it is inverted




5-1 THE DC OPERATING POINT


If an amplifier is not biased with correct dc voltages, it can go into **saturation** or **cutoff** when an input signal is applied.

➤ Improper biasing can cause distortion in the output signal by:

 - ✓ limiting of the **positive portion** of the **output voltage** as a result of a Q-point (dc operating point) being too close to **cutoff**.
- ✓ limiting of the **negative portion** of the **output voltage** as a result of a dc operating point being too close to **saturation**.



 (b) Nonlinear operation: output voltage limited (clipped) by cutoff




(c) Nonlinear operation: output voltage limited (clipped) by saturation



Graphical Analysis & DC Load Line

❖ Explain graphically the effects of dc bias

 - The transistor in Fig. is biased with V_{CC} and V_{BB} to obtain certain values of I_B , I_C , I_E , and V_{CE} .
- V_{BB} is adjusted to obtain different values of I_B




(a) DC biased circuit

First, V_{BB} is adjusted to produce an I_B of $200 \mu A$,


$$I_C = \beta_{DC} I_B = 20 \text{ mA}$$

$$V_{CE} = V_{CC} - I_C R_C = 10 \text{ V} - (20 \text{ mA})(220 \Omega) = 10 \text{ V} - 4.4 \text{ V} = 5.6 \text{ V}$$



 
- Changing V_{BB} will cause changes in all voltages and current (See Next Slide)



(a) $I_B = 200 \mu A$


 


Graphical Analysis & DC Load Line

   

DC Load Line

 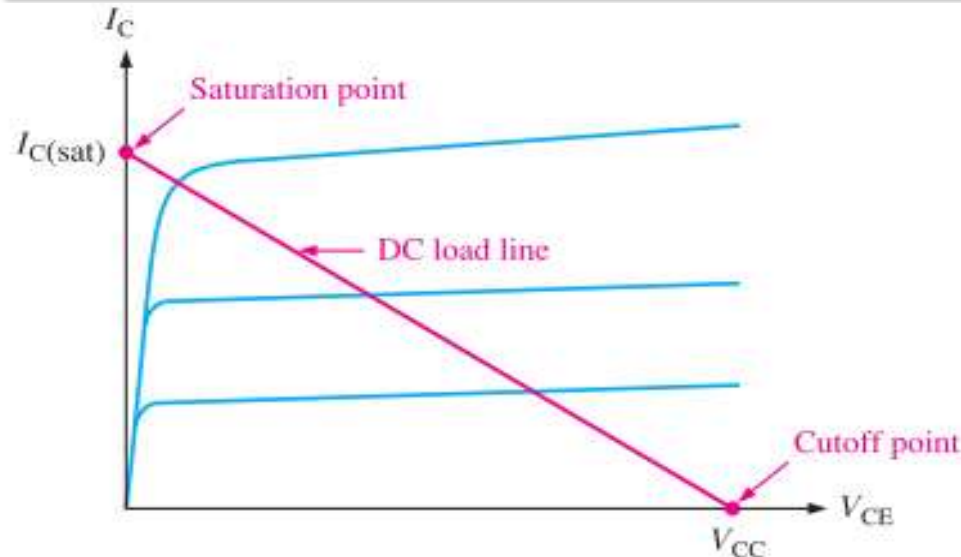This is a straight line drawn on the characteristic curves from the saturation value of I_C on the y-axis to the cutoff value of V_{CE} on the x-axis,




Graphical Analysis & DC Load Line

$$V_{CE} = V_{CC} - I_C R_C$$

When VCE saturates ($V_{CE(sat)}$ near 0):

$$I_{C(sat)} = \frac{V_{CC} - V_{CE(sat)}}{R_C}$$

For Ideal Case , let $V_{CE(sat)} = 0$

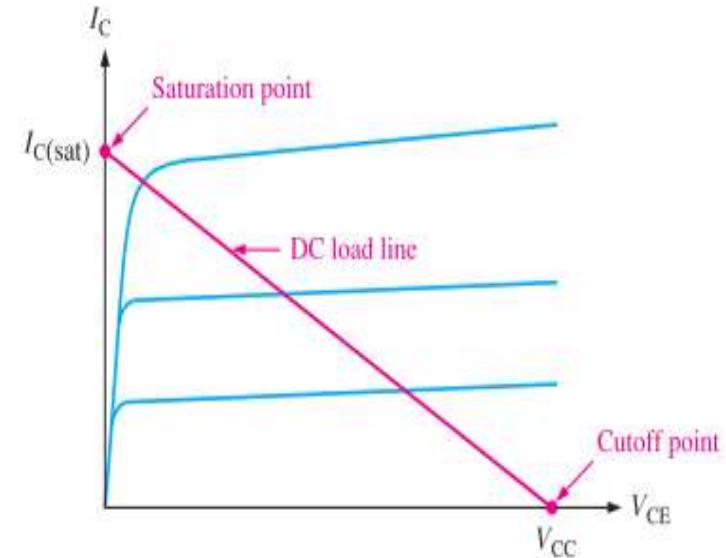


➤ DC Load Line Equation

$$I_C = \frac{V_{CC} - V_{CE}}{R_C} = \frac{V_{CC}}{R_C} - \frac{V_{CE}}{R_C} = -\frac{V_{CE}}{R_C} + \frac{V_{CC}}{R_C} = -\left(\frac{1}{R_C}\right)V_{CE} + \frac{V_{CC}}{R_C}$$




Linear Operation

 - The region along the load line including all points between saturation and cutoff is generally known as the linear region of the transistor's operation.
- As long as the transistor is operated in this region, the output voltage is ideally a linear reproduction of the input.



Ac quantities I_b & V_{ce}

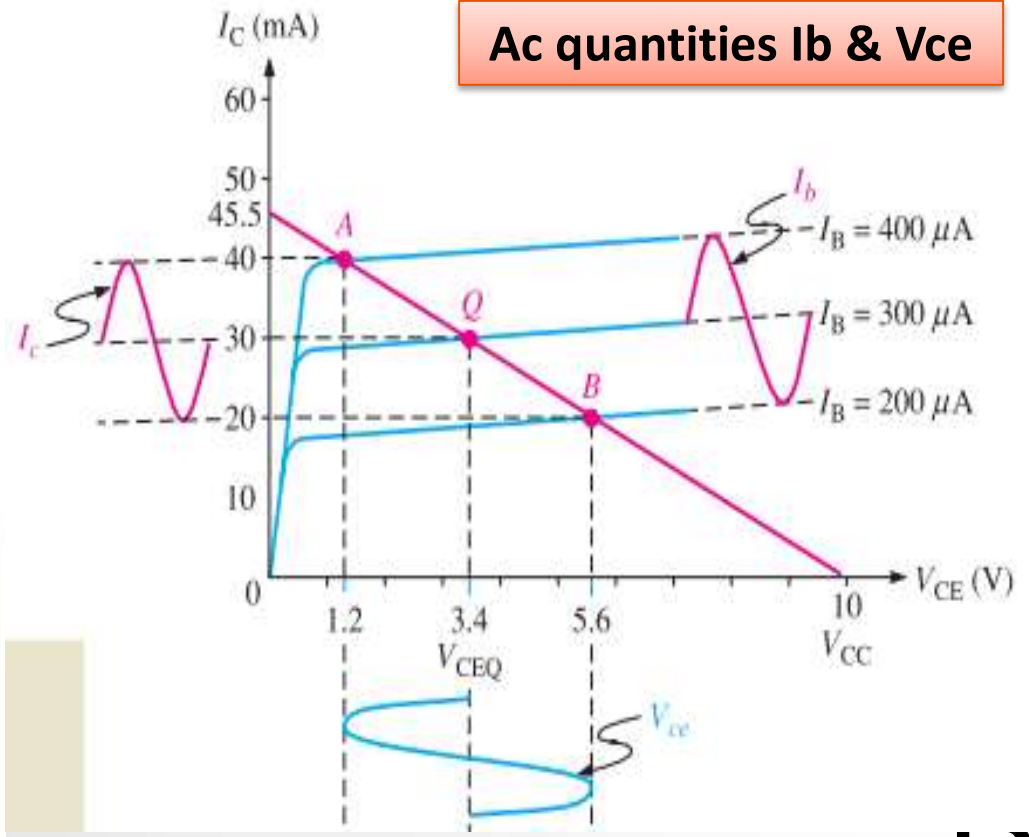

$$I_{BQ} = \frac{V_{BB} - 0.7V}{R_B} = \frac{3.7V - 0.7V}{10k\Omega} = 300\mu A$$


$$I_{CQ} = \beta_{DC} I_{BQ} = (100)(300\mu A) = 30mA$$

$$V_{CEQ} = V_{CC} - I_{CQ} R_C = 10V - (30mA)(220\Omega) = 3.4V$$


Waveform Distortion

- Under certain input signal conditions the location of the Q-point on the load line can cause one peak of the Vce waveform to be limited or clipped

 In each case the **input signal** is **too large** for the Q-point location and is driving the transistor into cutoff or saturation during a portion of the input cycle.




 (a) Transistor is driven into saturation because the Q-point is too close to saturation for the given input signal.



(b) Transistor is driven into cutoff because the Q-point is too close to cutoff for the given input signal.

Waveform Distortion

 

(c) Transistor is driven into both saturation and cutoff because the input signal is too large.



Determine the Q-point for the circuit in Figure 5–7 and draw the dc load line. Find the maximum peak value of base current for linear operation. Assume $\beta_{DC} = 200$.

Solution

The Q-point is defined by the values of I_C and V_{CE} .

$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{10\text{ V} - 0.7\text{ V}}{47\text{ k}\Omega} = 198\ \mu\text{A}$$

$$I_C = \beta_{DC} I_B = (200)(198\ \mu\text{A}) = 39.6\text{ mA}$$



$$V_{CE} = V_{CC} - I_C R_C = 20\text{ V} - 13.07\text{ V} = 6.93\text{ V}$$

$$I_{C(\text{sat})} = \frac{V_{CC}}{R_C} = \frac{20\text{ V}}{330\ \Omega} = 60.6\text{ mA}$$

The dc load line is graphically illustrated in Figure



Before saturation is reached, I_C can increase an amount ideally equal to:
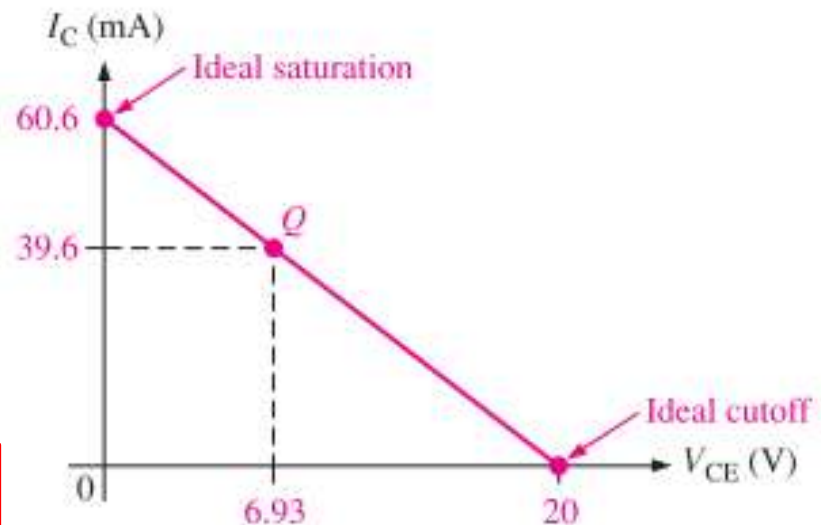 
$$I_{C(\text{sat})} - I_{CQ} = 60.6\text{ mA} - 39.6\text{ mA} = 21.0\text{ mA}$$



However, I_C can decrease by 39.6 mA before cutoff ($I_C = 0$) is reached.

  - Therefore, the limiting excursion is 21 mA because the Q-point is closer to saturation than to cutoff
- The 21 mA is the maximum peak variation of the collector current.
- Actually, it would be slightly less in practice because $V_{CE(sat)}$ is not quite zero



Determine the maximum peak variation of the base current as follows:

$$I_{b(peak)} = \frac{I_{c(peak)}}{\beta_{DC}} = \frac{21 \text{ mA}}{200} = 105 \mu\text{A}$$




5-2 VOLTAGE-DIVIDER BIAS

- This is the most widely used biasing method.
- It uses a single-source resistive voltage divider.

- To simplify the schematic, the battery symbol is omitted and replaced by a line termination circle with a voltage indicator (V_{CC}) as shown.

 - Generally, voltage-divider bias circuits are designed so that **the base current is much smaller** than the current (I_2) through R_2
- In this case, the voltage-divider circuit is very straightforward to analyze because **the loading effect** of the base current **can be ignored**.



- ✓ It is called a ((stiff voltage divider)) because the base voltage is relatively **independent** of **different transistors** and **temperature** effects.
- ✓ In other words: **“That the transistor does not appear as a significant load”**

5-2 VOLTAGE-DIVIDER BIAS

Stiff voltage divider circuit analysis

✓ The voltage on the base using the unloaded voltage-divider rule:

$$V_B \cong \left(\frac{R_2}{R_1 + R_2} \right) V_{CC}$$


➤ you can find the voltages and currents in the circuit, as

$$V_E = V_B - V_{BE}$$

$$I_C \cong I_E = \frac{V_E}{R_E}$$

$$V_C = V_{CC} - I_C R_C$$

$$V_{CE} = V_C - V_E$$

 

Not Completely accurate




Thevenin's Theorem Applied to Voltage-Divider Bias

To analyze a voltage-divider biased transistor circuit for base current loading effects


1. let's get an equivalent base-emitter circuit for the circuit in Figure 5-13(a)

 2. Apply Thevenin's theorem to the circuit left of point A,




$$V_{TH} = \left(\frac{R_2}{R_1 + R_2} \right) V_{CC}$$

$$R_{TH} = \frac{R_1 R_2}{R_1 + R_2}$$

 

(b)

 

(c)

The Thevenin equivalent of the bias circuit, connected to the transistor base

Thevenin's Theorem Applied to Voltage-Divider Bias

3. Applying Kirchhoff's voltage law around the equivalent base-emitter loop gives

$$V_{TH} - V_{R_{TH}} - V_{BE} - V_{R_E} = 0$$

$$V_{TH} = I_B R_{TH} + V_{BE} + I_E R_E$$

Substituting I_E/β_{DC} for I_B ,

$$V_{TH} = I_E(R_E + R_{TH}/\beta_{DC}) + V_{BE}$$


Then solving for I_E ,

$$I_E = \frac{V_{TH} - V_{BE}}{R_E + R_{TH}/\beta_{DC}}$$

If R_{TH}/β_{DC} is small compared to R_E , the result is the same as for an unloaded voltage divider.

- If we do not use the current approximation ($I_E = I_C$)
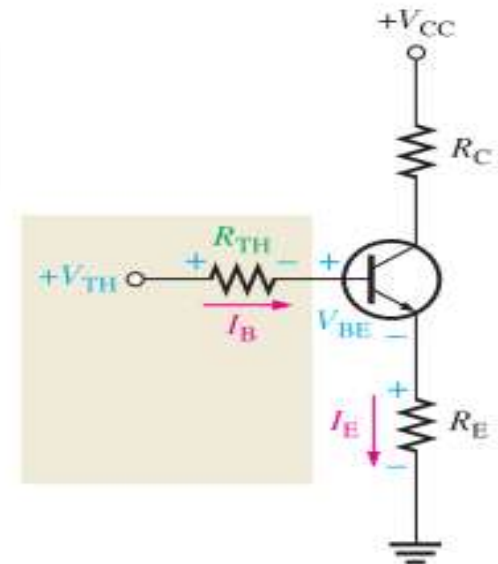
$$I_B = \frac{E_{Th} - V_{BE}}{R_{Th} + (\beta + 1)R_E}$$



(c)



Voltage-Divider Biased PNP Transistor


1. Negative collector supply voltage, V_{CC}

$$V_{TH} = \left(\frac{R_2}{R_1 + R_2} \right) V_{CC}$$
$$R_{TH} = \frac{R_1 R_2}{R_1 + R_2}$$
$$I_B = \frac{I_E}{\beta_{DC}}$$

applying Kirchhoff's voltage law

$$V_{TH} + I_B R_{TH} - V_{BE} + I_E R_E = 0$$
 
$$I_E = \frac{-V_{TH} + V_{BE}}{R_E + R_{TH}/\beta_{DC}}$$



(a) Negative collector supply voltage, V_{CC}

Check EXAMPLE 5-5



Voltage-Divider Biased PNP Transistor

2. Positive emitter supply voltage, V_{EE}

$$V_{TH} = \left(\frac{R_1}{R_1 + R_2} \right) V_{EE}$$

$$R_{TH} = \frac{R_1 R_2}{R_1 + R_2}$$


$$I_B = \frac{I_E}{\beta_{DC}}$$

applying Kirchhoff's voltage law


$$-V_{TH} + I_B R_{TH} - V_{BE} + I_E R_E - V_{EE} = 0$$

$$I_E = \frac{V_{TH} + V_{BE} - V_{EE}}{R_E + R_{TH}/\beta_{DC}}$$

Check EXAMPLE 5-4

 

 (b) Positive emitter supply voltage, V_{EE}



(c) The circuit in (b) redrawn

