

Electrical, Electronic and Digital Principles (EEDP)



Lecture 4 BJT Amplifiers

د. باسم ممدوح الحلوانى



BJT AMPLIFIERS

- 6-1 Amplifier Operation
- 6-2 Transistor AC Models
- 6-3 The Common-Emitter Amplifier
- 6-4 The Common-Collector Amplifier
- 6-5 The Common-Base Amplifier
- 6-6 Multistage Amplifiers




- ❖ The purpose of biasing is to establish a Q-point about which variations in current and voltage can occur in response to an ac input signal.
- ❖ In applications where small signal voltages must be amplified such as from an antenna or a microphone—variations about the Q-point are relatively small.
- ❖ Amplifiers designed to handle these small ac signals are often referred to as **small-signal amplifiers**.

The Linear Amplifier

A linear amplifier provides amplification of a signal without any distortion so that the output signal is an exact amplified replica of the input signal.

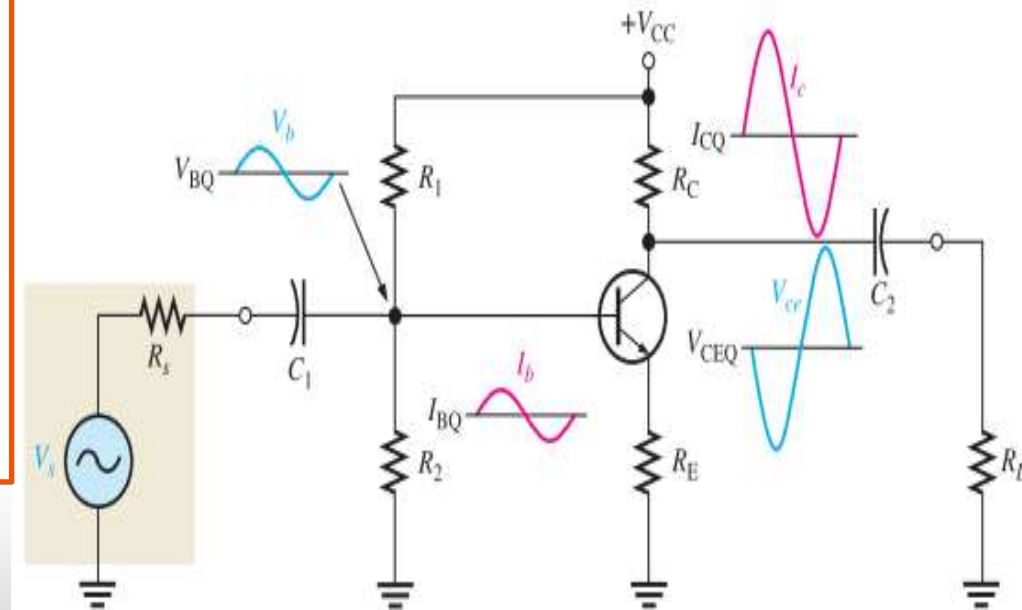- ✓ The coupling capacitors block dc and thus prevent the internal source resistance, R_s , and the load resistance, R_L , from changing the dc bias voltages at the base and collector.
- ✓ The capacitors ideally appear as shorts to the signal voltage.



- ✓ For an amplifying device, the output sinusoidal signal is greater than the input sinusoidal signal, or, stated another way, **the output ac power is greater than the input ac power.**

$$\eta = P_o/P_i \text{ cannot be greater than 1.}$$

In fact, a *conversion efficiency* is defined by $\eta = P_{o(ac)}/P_{i(dc)}$, where $P_{o(ac)}$ is the ac power to the load and $P_{i(dc)}$ is the dc power supplied.

- ✓ In other words, there is an “exchange” of dc power to the ac domain that permits establishing a higher output ac power.

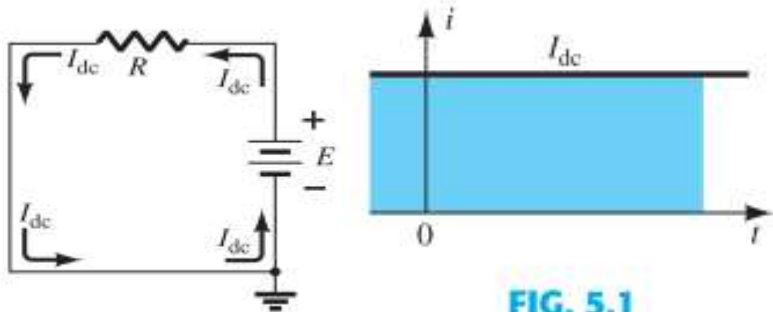


FIG. 5.1

Steady current established by a dc supply.

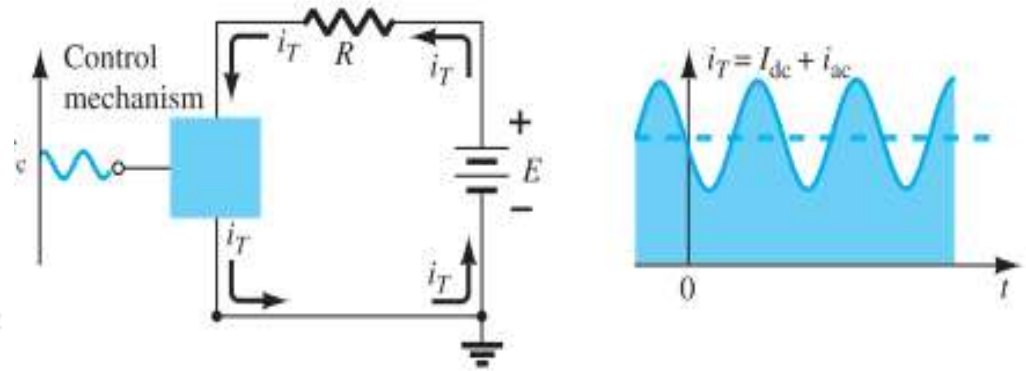


FIG. 5.2

Effect of a control element on the steady-state flow of the electrical system of Fig. 5.1.



$$i_{ac(p-p)} \gg i_{c(p-p)}$$

- ✓ The peak value of the oscillation in the output circuit is controlled by the established dc level.
- ✓ Any attempt to exceed the limit set by the dc level will result in a “clipping” (flattening)

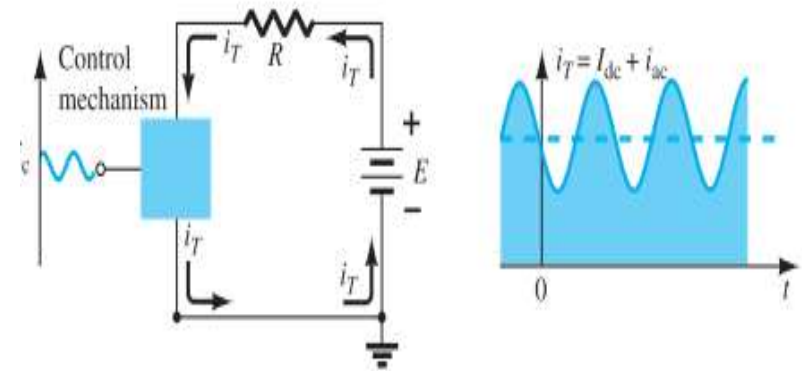


FIG. 5.2

Effect of a control element on the steady-state flow of the electrical system of Fig. 5.1.

The superposition theorem is applicable for the analysis and design of the dc and ac components of a BJT network, permitting the separation of the analysis of the dc and ac responses of the system.

- Once the dc analysis is complete, the ac response can be determined using a completely ac analysis.
- However, one of the components appearing in the ac analysis of BJT networks will be determined by the dc conditions (link between the two types of analysis).



- ✓ To visualize the operation of a transistor in an amplifier circuit, it is often useful to represent the device by a model circuit.

A model is a combination of circuit elements, properly chosen, that best approximates the actual behavior of a semiconductor device under specific operating conditions.


There are three models commonly used in the small-signal ac analysis of transistor

r_e model, the hybrid π model, and the hybrid equivalent model.




r-Parameter Transistor Model

r parameters.

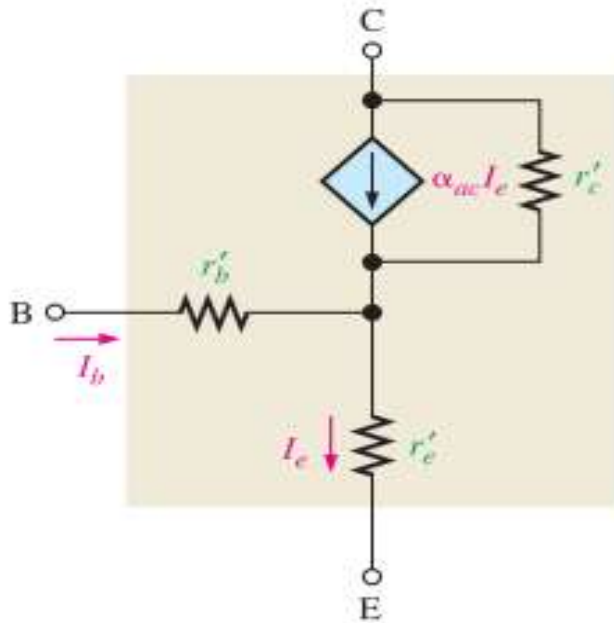

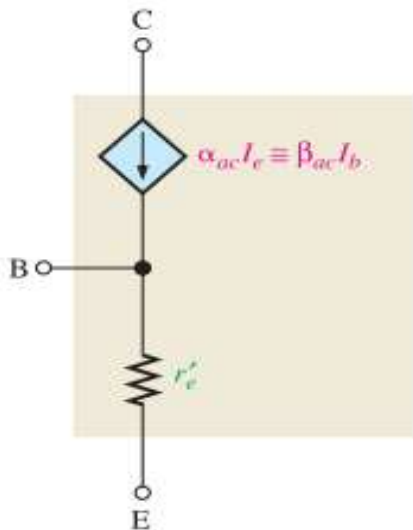
(a) Generalized r -parameter model for a BJT



(b) Simplified r -parameter model for a BJT

r PARAMETER	DESCRIPTION
α_{ac}	ac alpha (I_c/I_e)
β_{ac}	ac beta (I_c/I_b)
r'_e	ac emitter resistance
r'_b	ac base resistance
r'_c	ac collector resistance

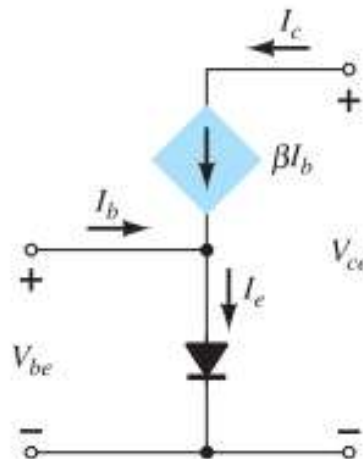- ✓ The effect of the ac base resistance small enough to neglect
- ✓ (R_c or r_o) The ac collector resistance is usually hundreds of kilohms and can be replaced by an open.



Determining r'_e by a Formula

$$r'_e \cong \frac{25 \text{ mV}}{I_E}$$


BE Forward diode resistance

Comparison of the AC Beta (β_{ac}) to the DC Beta (β_{DC})


For a typical transistor, a graph of I_C versus I_B is nonlinear, as shown in Figure 6–7(a).

$$\beta_{DC} = I_C/I_B \text{ and } \beta_{ac} = \Delta I_C/\Delta I_B,$$

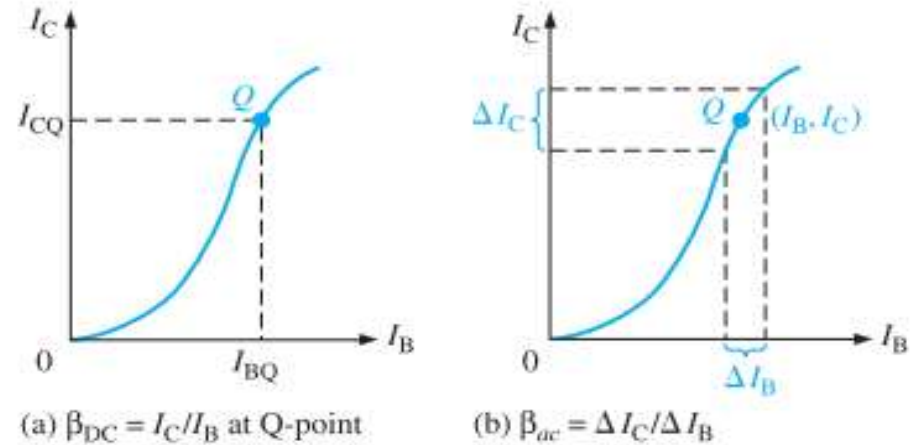The values of these two quantities can differ slightly.



Input and output resistance of the BJT

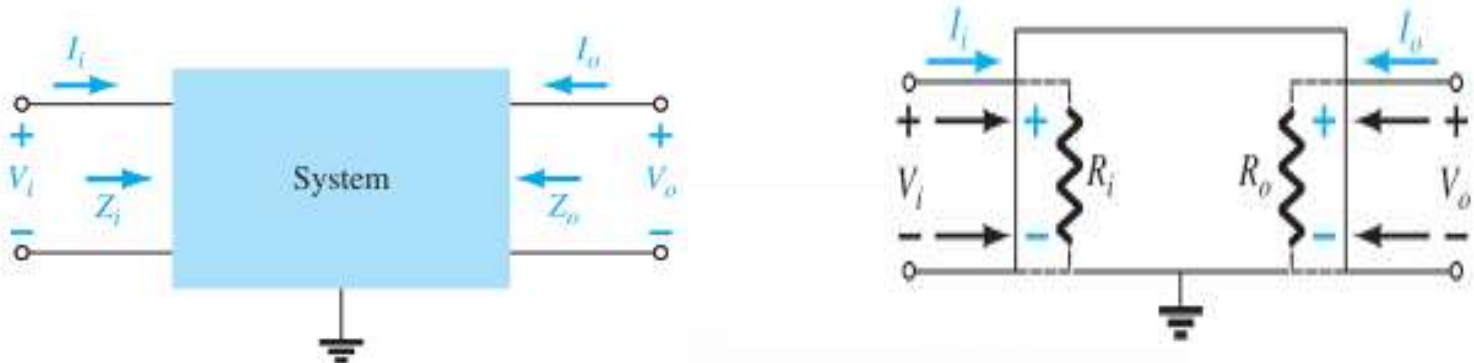

Input Resistance at the Base $R_{in(base)}$

➤ use the simplified r-parameter model of the transistor.

➤ $Z_i = R_{in(base)}$

$$R_{in(base)} = \frac{V_{in}}{I_{in}} = \frac{V_b}{I_b}$$



$$Z_i = \frac{V_i}{I_b} = \frac{V_{be}}{I_b}$$

$$V_{be} = I_e r_e = (I_c + I_b) r_e = (\beta I_b + I_b) r_e$$


$$= (\beta + 1) I_b r_e$$

$$Z_i = \frac{V_{be}}{I_b} = \frac{(\beta + 1) I_b r_e}{I_b}$$
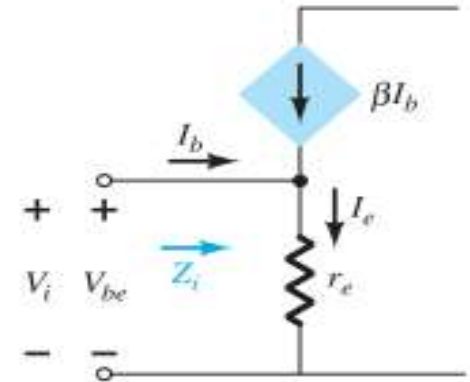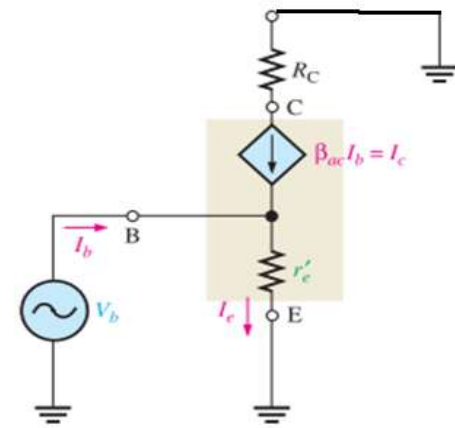
$$Z_i = (\beta + 1) r_e \cong \beta r_e$$



Improved BJT equivalent circuit.

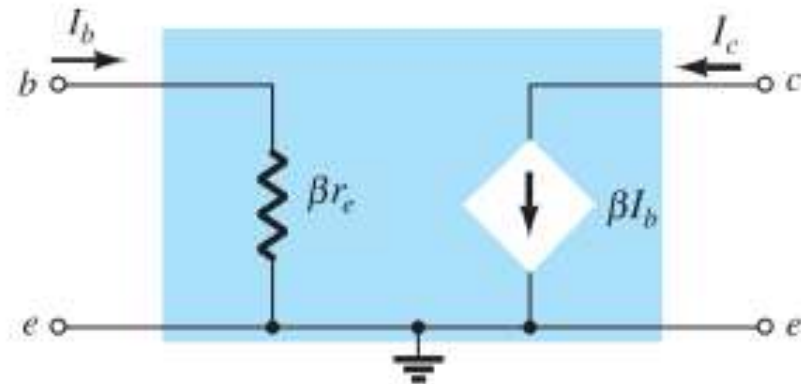

- ✓ now the input and output circuits are isolated and only linked by the controlled source
- ✓ This form is much easier to work with when analyzing networks.

Output Characteristic

The output characteristic is not practically the same as assumed in the model with constant β curves

- ✓ Rather, they have a slope as shown in Fig. 5.15 that defines the output impedance of the device.
- ✓ The steeper the slope, the less the output impedance and the less ideal the transistor.
- ✓ In general, it is desirable to have large output impedances to avoid loading down the next stage of a design.

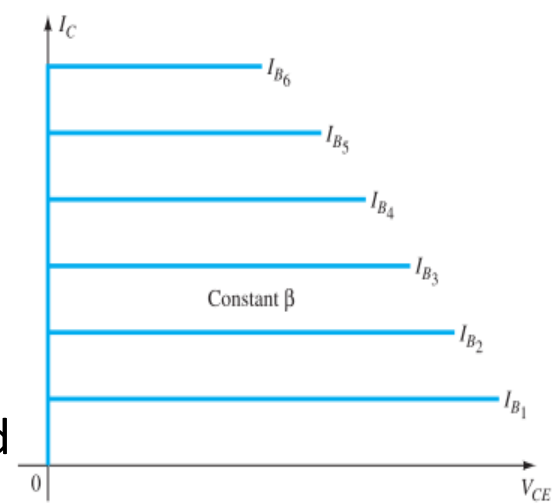


FIG. 5.11
Constant β characteristics.

$$r_o = \frac{\Delta V}{\Delta I} = \frac{V_A + V_{CEQ}}{I_{CQ}}$$


V_A = Early voltage.

$$r_o \cong \frac{V_A}{I_{CQ}}$$

$V_A \gg V_{CEQ}$

$$r_o = \frac{\Delta V_{CE}}{\Delta I_C}$$

If V_A value not available

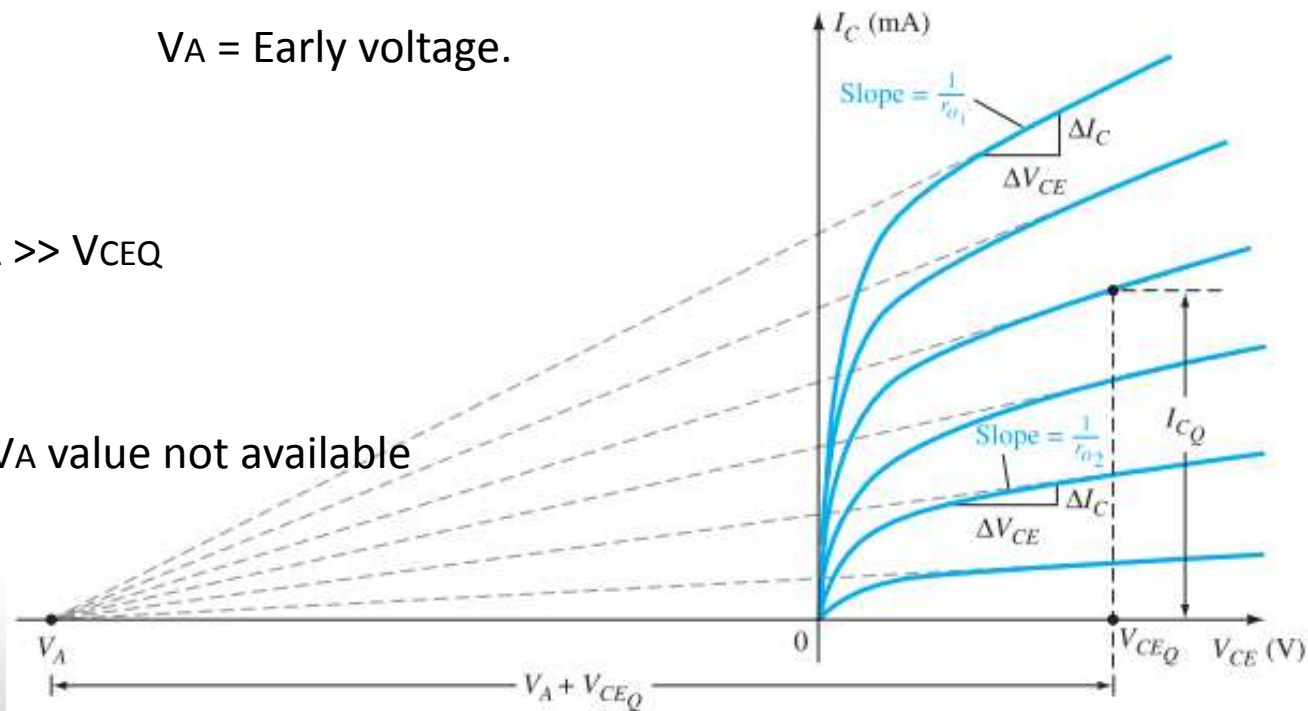

Output Resistance

The output impedance will appear as a resistor in parallel with the output as shown in Fig. 5.16 .

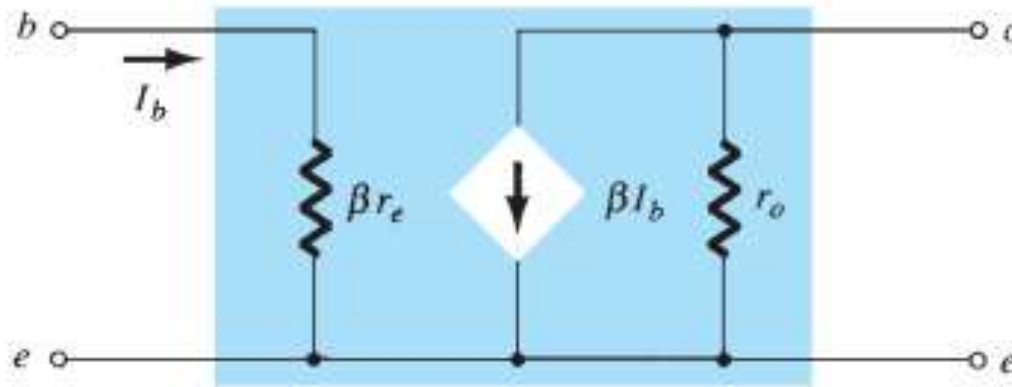


FIG. 5.16

r_e model for the common-emitter transistor configuration including effects of r_o




6-3

THE COMMON-EMITTER AMPLIFIER

Three amplifier configurations are:

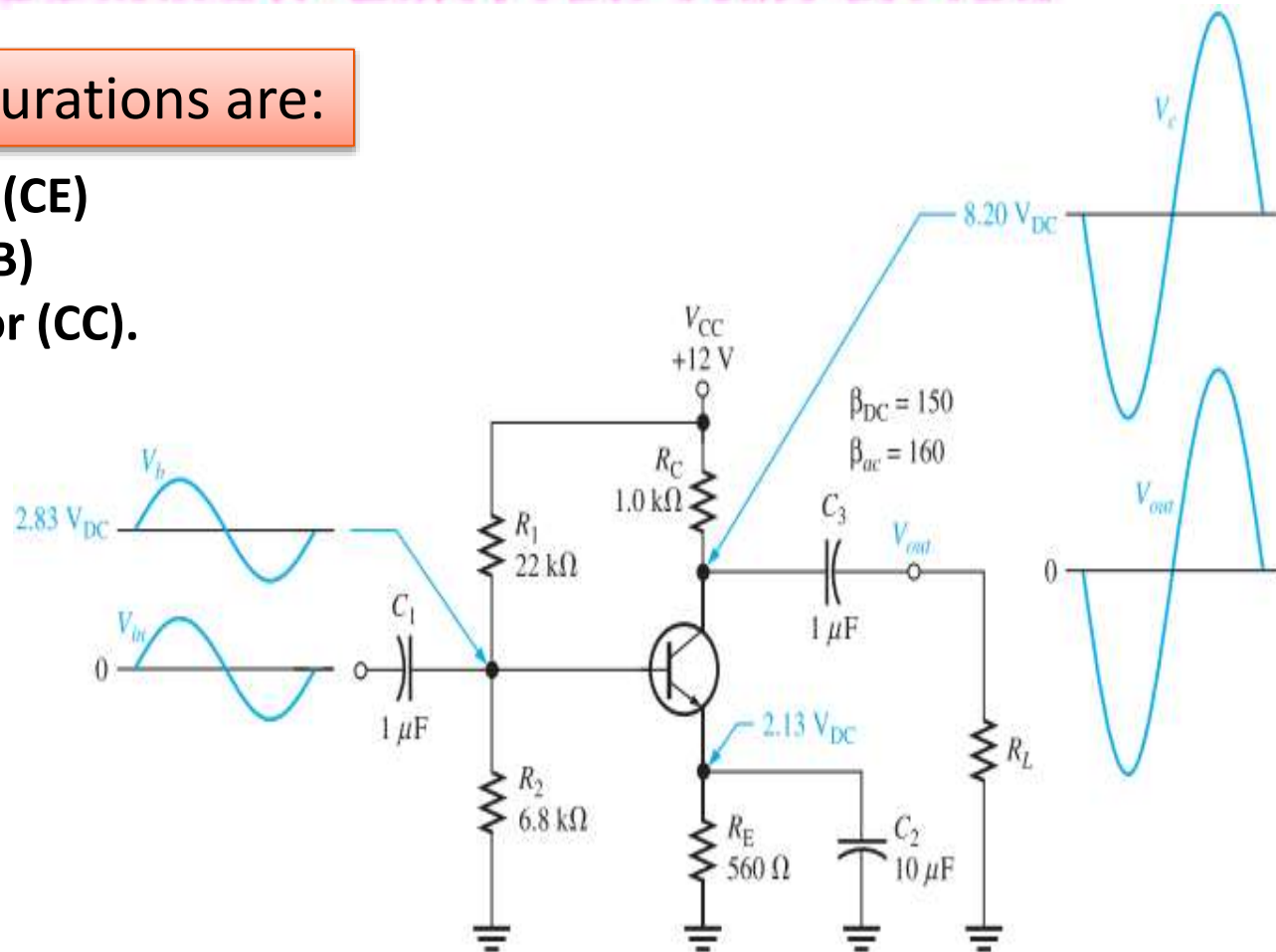1. The Common-Emitter (CE)
2. The Common-Base (CB)
3. The Common-Collector (CC).



- ✓ The common-emitter (CE) configuration has the emitter as the common terminal, or ground, to an ac signal.
- ✓ CE amplifiers exhibit high voltage gain and high current gain.

- The figure shows a CE amplifier with voltage-divider bias and coupling capacitors C1 and C3 on the input and output and a **bypass capacitor**, C2, from emitter to ground.
- The input signal, V_{in} , is capacitively coupled to the base terminal,
- The output signal, V_{out} , is capacitively coupled from the collector to the load.

- ✓ The amplified output is 180° out of phase with the input
- ✓ There is no signal at the emitter because the bypass capacitor effectively shorts the emitter to ground at the signal frequency.



DC Analysis

- a dc equivalent circuit is developed by removing the coupling and bypass capacitors because they appear open as far as the dc bias is concerned.

$$R_{TH} = \frac{R_1 R_2}{R_1 + R_2} = \frac{(6.8 \text{ k}\Omega)(22 \text{ k}\Omega)}{6.8 \text{ k}\Omega + 22 \text{ k}\Omega} = 5.19 \text{ k}\Omega$$

$$V_{TH} = \left(\frac{R_2}{R_1 + R_2} \right) V_{CC} = \left(\frac{6.8 \text{ k}\Omega}{6.8 \text{ k}\Omega + 22 \text{ k}\Omega} \right) 12 \text{ V} = 2.83 \text{ V}$$

$$I_E = \frac{V_{TH} - V_{BE}}{R_E + R_{TH}/\beta_{DC}} = \frac{2.83 \text{ V} - 0.7 \text{ V}}{560 \Omega + 34.6 \Omega} = 3.58 \text{ mA}$$


$$I_C \cong I_E = 3.58 \text{ mA}$$

$$V_E = I_E R_E = (3.58 \text{ mA})(560 \Omega) = 2 \text{ V}$$


$$V_B = V_E + 0.7 \text{ V} = 2.7 \text{ V}$$

$$V_C = V_{CC} - I_C R_C = 12 \text{ V} - (3.58 \text{ mA})(1.0 \text{ k}\Omega) = 8.42 \text{ V}$$

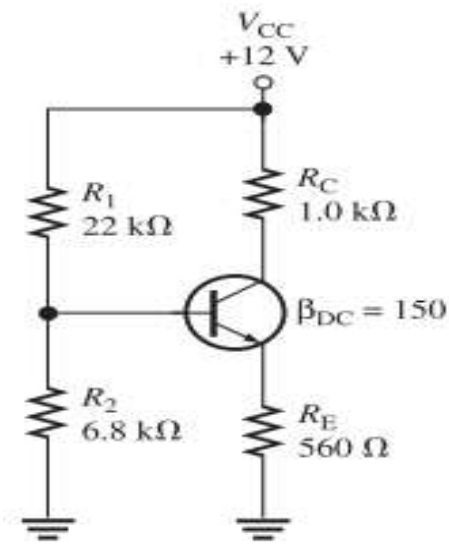
$$V_{CE} = V_C - V_E = 8.42 \text{ V} - 2 \text{ V} = 6.42 \text{ V}$$



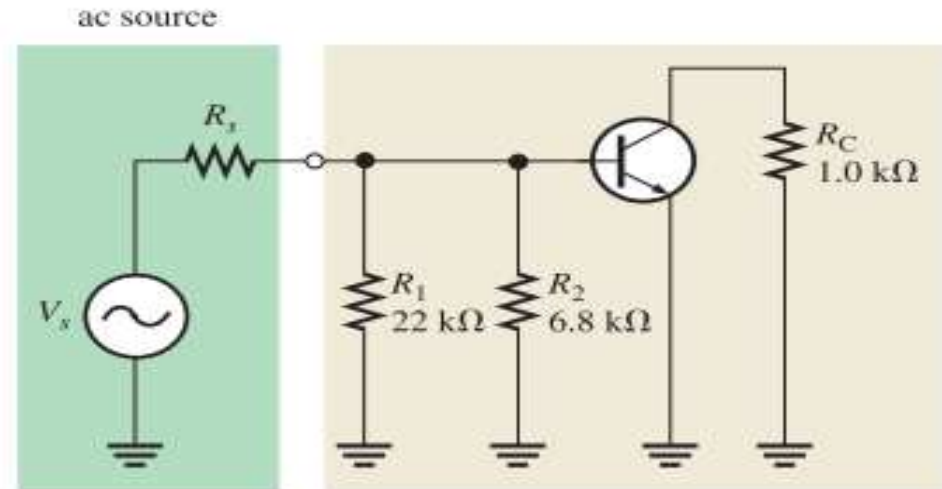1. The capacitors C_1 , C_2 , and C_3 are replaced by effective shorts because their values are selected so that X_C is negligible at the signal frequency and can be considered to be 0Ω .
2. The dc source is replaced by ground.



(b) With an input signal voltage

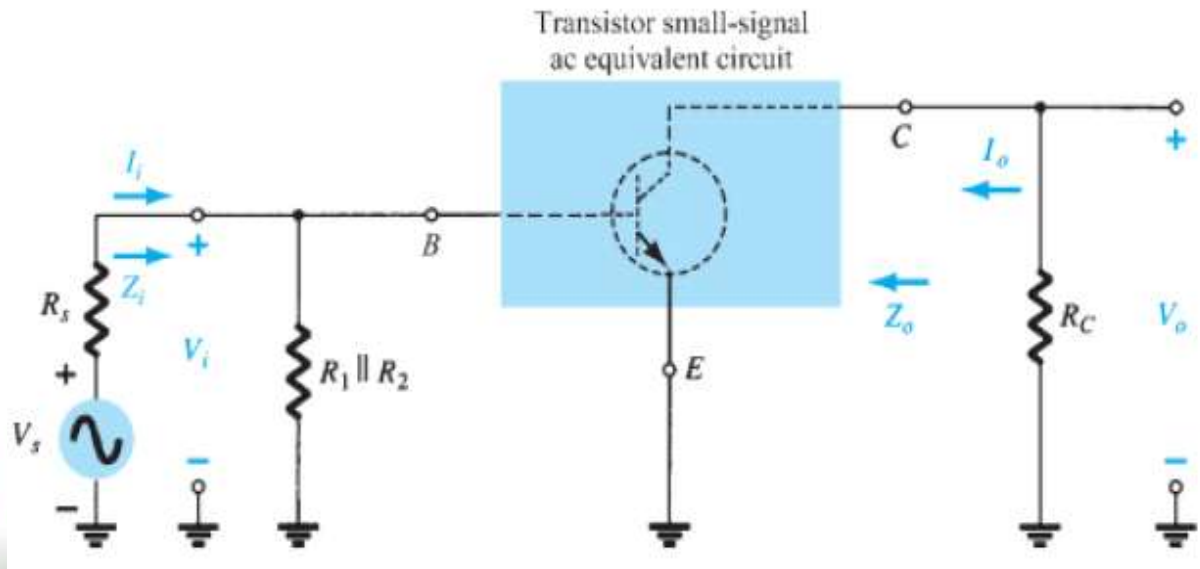


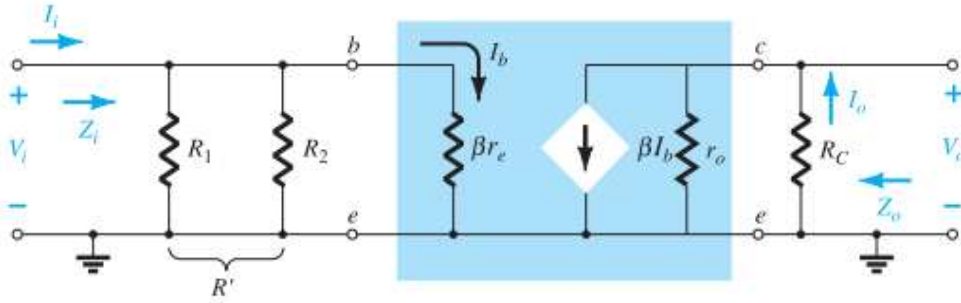


FIG. 5.27


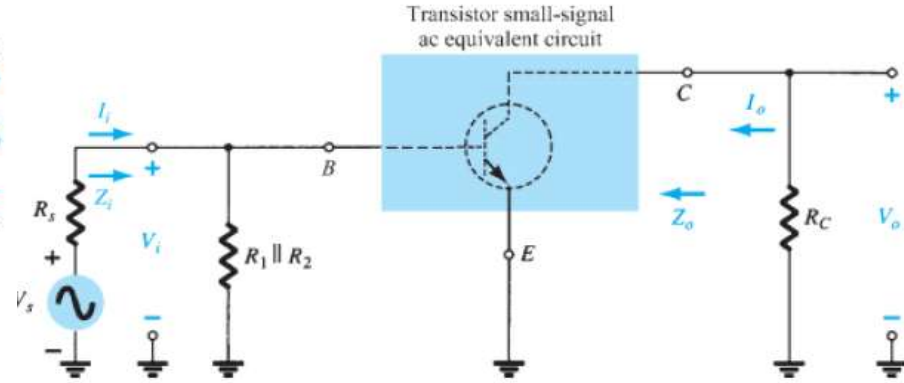
Substituting the r_e equivalent circuit into the ac equivalent network of Fig. 5.26.



Total Input Resistance

is the resistance "seen" by an ac source connected to the input

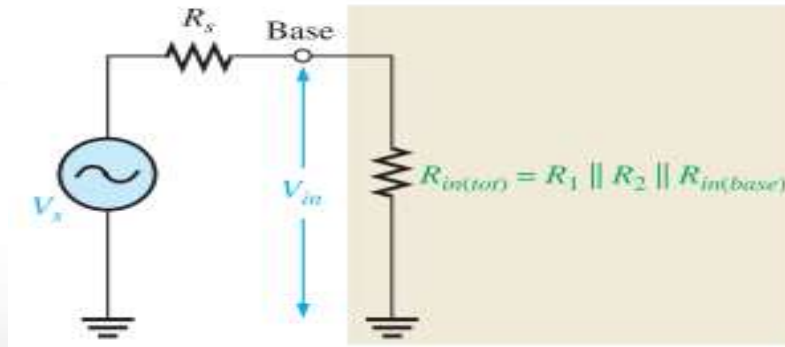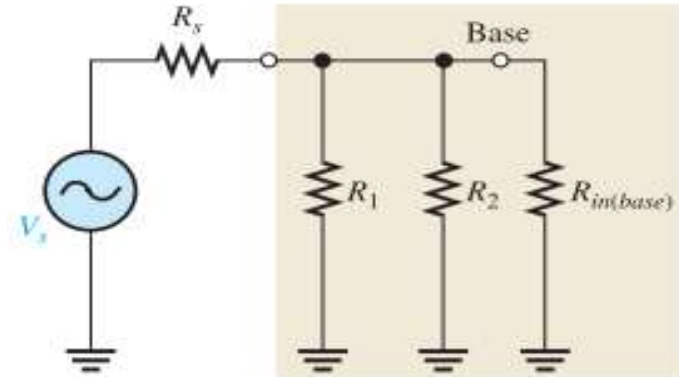
$$R_{in(tot)} = R_1 \parallel R_2 \parallel R_{in(base)}$$



Signal (AC) Voltage at the Base

Two factors for determining the actual signal voltage at the base:

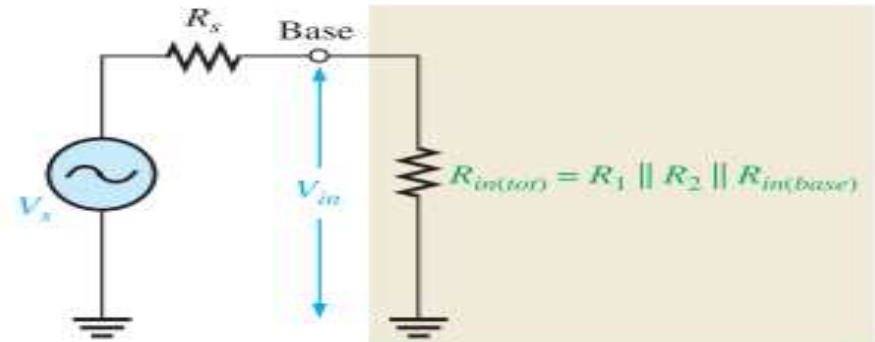1. The source resistance (R_s),
2. The ac input resistance at the base of the transistor $R_{in(base)}$



✓ The signal voltage at the base of the transistor is found by the voltage-divider:

$$V_b = \left(\frac{R_{in(tot)}}{R_s + R_{in(tot)}} \right) V_s$$

A high value of input resistance is desirable so that the amplifier will not excessively load the signal source.

If $R_s \ll R_{in(tot)}$, then $V_b \cong V_s$ where V_b is the input voltage, V_{in} , to the amplifier.



6-3

THE COMMON-EMITTER AMPLIFIER

Total Output Resistance

➤ The output resistance of any system is defined as the resistance R_o (Z_o) determined when $V_i = 0$.

when $V_i = 0$, $I_i = I_b = 0$, resulting in an open-circuit equivalence for the current source.

$$Z_o = R_C \parallel r_o$$

If $r_o \geq 10R_C$, the approximation $R_C \parallel r_o \cong R_C$ is frequently applied, and

$$Z_o \cong R_C \quad r_o \geq 10R_C$$


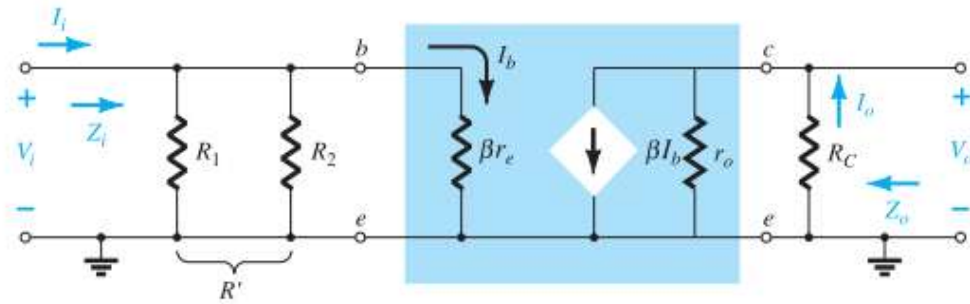


FIG. 5.27

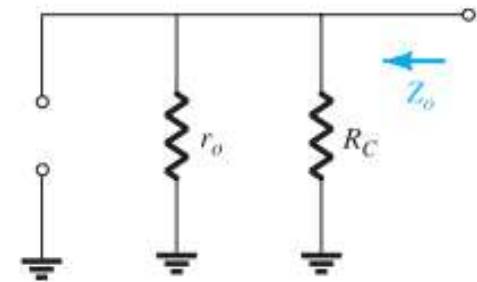Substituting the r_e equivalent circuit into the ac equivalent network of Fig. 5.26.



Voltage Gain


The gain is the ratio of ac output voltage at the collector (V_c) to ac input voltage at the base (V_b).

$$V_o = -(\beta I_b)(R_C \parallel r_o)$$

$$I_b = \frac{V_i}{\beta r_e}$$

$$V_o = -\beta \left(\frac{V_i}{\beta r_e} \right) (R_C \parallel r_o)$$

$$\frac{V_c}{V_b}$$

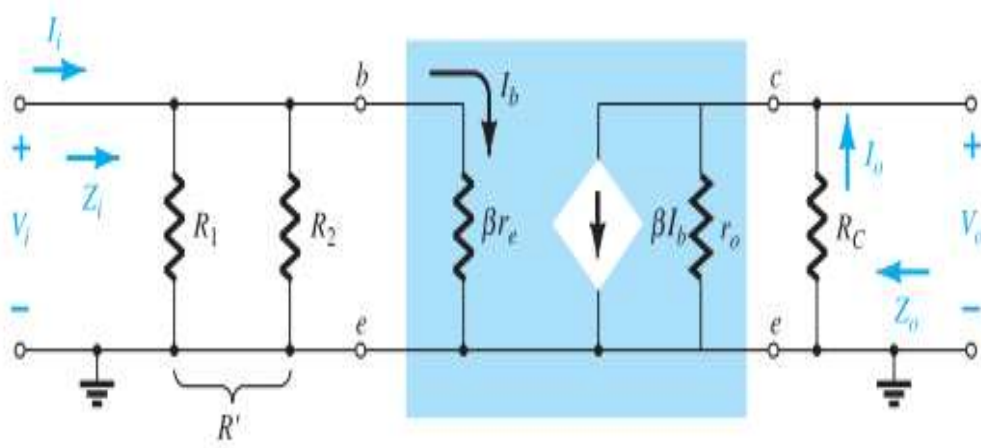

the voltage gain from base to collector.

$$A_v = \frac{V_o}{V_i} = \frac{-R_C \parallel r_o}{r_e}$$

Phase Relationship

V_o and V_i .

The negative sign of Eq. (5.15) reveals a 180° phase shift between

For $r_o \geq 10R_C$,


$$A_v = \frac{V_o}{V_i} \cong -\frac{R_C}{r_e}$$

$r_o \geq 10R_C$

To get the overall gain of the amplifier from the source voltage to collector, the attenuation of the input circuit must be included

Attenuation and the Overall Gain
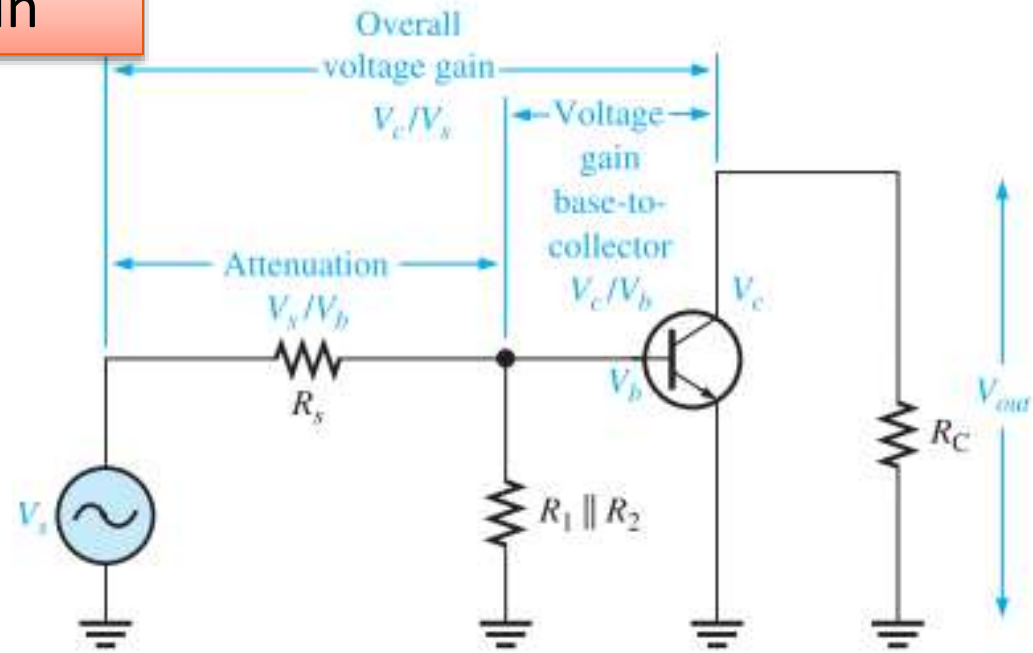
$$\text{Attenuation} = \frac{V_s}{V_b} = \frac{R_s + R_{in(tot)}}{R_{in(tot)}}$$



Overall Voltage Gain

$$A'_v = \left(\frac{V_c}{V_b}\right)\left(\frac{V_b}{V_s}\right) = \frac{V_c}{V_s}$$



Effect of a Load on the Voltage Gain

When a resistor, R_L , is connected to the output through the coupling capacitor C_3 , as shown in Figure 6–17(a), it creates a load on the circuit.

$$R_c = \frac{R_C R_L}{R_C + R_L}$$

Replacing R_C with R_c in the voltage gain expression gives


$$A_v = \frac{R_c}{r'_e}$$

When $R_c < R_C$ because of R_L , the voltage gain is reduced.


However, if $R_L \gg R_C$ then:

$$R_c \cong R_C$$

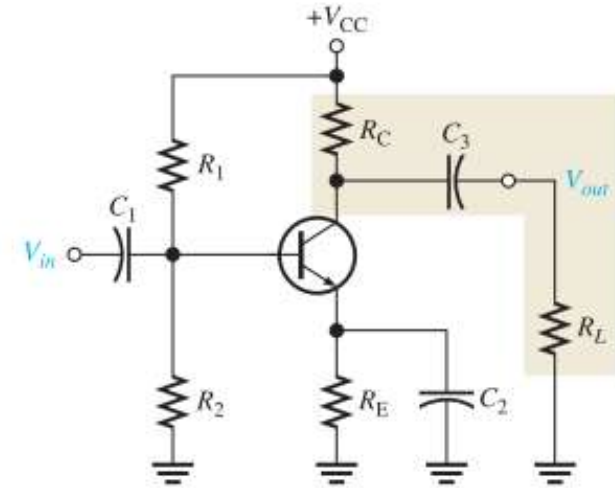and the load has very little effect on the gain.




(a) Complete amplifier

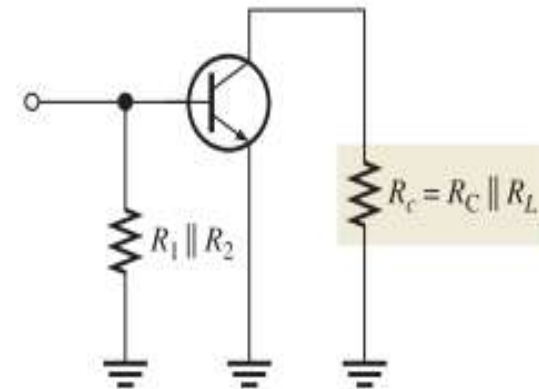

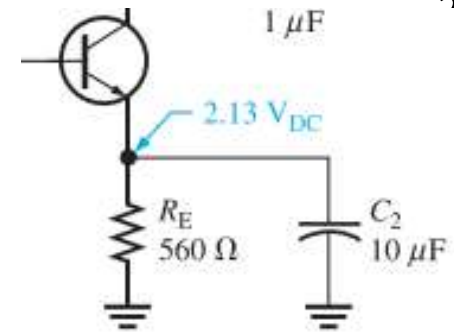(b) AC equivalent ($X_{C1} = X_{C2} = X_{C3} = 0$)

Effect of the Emitter Bypass Capacitor on Voltage Gain

- ✓ The emitter bypass capacitor, which is C2 in Figure , provides an **effective short** to the ac signal around the emitter resistor, thus **keeping the emitter at ac ground**



- The value of the bypass capacitor must be **large enough** so that its reactance over the frequency range of the amplifier is very small (Ideally 0 ohms) compared to RE.
- A good rule-of-thumb is that the capacitive reactance, X_C , of the bypass capacitor should be at least 10 times smaller than RE at the minimum frequency for which the amplifier must operate

EXAMPLE 6-4


$$10X_C \leq R_E$$

Select a minimum value for the emitter bypass capacitor, C_2 , in Figure 6-16 if the amplifier must operate over a frequency range from 200 Hz to 10 kHz.

$$X_{C2} = \frac{R_E}{10} = \frac{560 \Omega}{10} = 56 \Omega$$

Determine the capacitance value at the minimum frequency of 200 Hz as follows
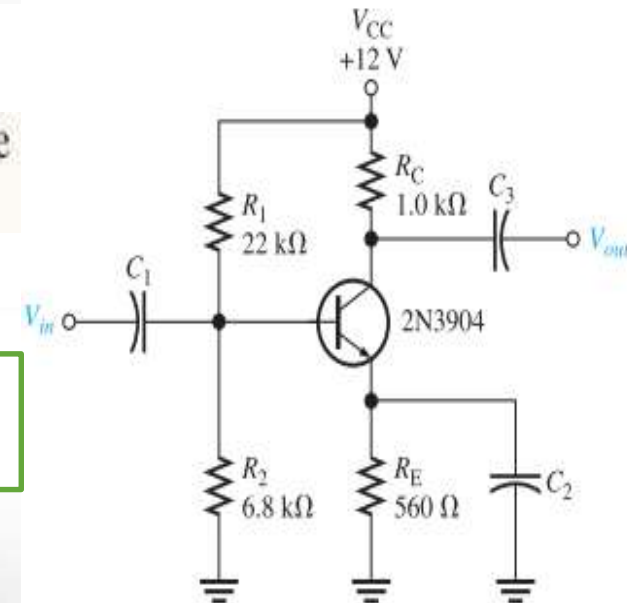
$$C_2 = \frac{1}{2\pi f X_{C2}} = \frac{1}{2\pi(200 \text{ Hz})(56 \Omega)} = 14.2 \mu\text{F}$$



Effect of the Emitter Bypass Capacitor on Voltage Gain

Voltage Gain Without the Bypass Capacitor

- ✓ **Without** the bypass capacitor, the emitter is no longer at ac ground.
- ✓ Instead, R_E is seen by the ac signal between the emitter and ground and effectively adds to r_e' in the voltage gain formula and **reduces the gain**:

$$A_v = \frac{R_C}{r_e' + R_E}$$

Proof (Page 288- Boylstad)


EXAMPLE 6-5

Calculate the base-to-collector voltage gain of the amplifier in Figure 6-16 both without and with an emitter bypass capacitor if there is no load resistor.

$$r_e' = 6.58 \Omega$$

Without C_2 , the gain is
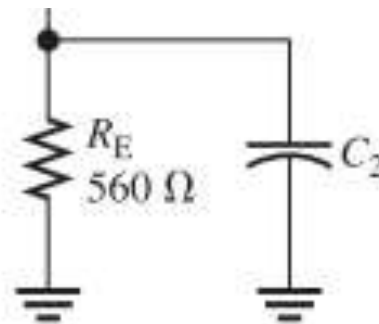
$$A_v = \frac{R_C}{r_e' + R_E} = \frac{1.0 \text{ k}\Omega}{567 \Omega} = 1.76$$



With C_2 , the gain is

$$A_v = \frac{R_C}{r_e'} = \frac{1.0 \text{ k}\Omega}{6.58 \Omega} = 152$$



Stability of the Voltage Gain

- ✓ Stability is a measure of how well an amplifier maintains its design values over changes in temperature or for a transistor with a different B .
- ✓ Although bypassing R_E does produce the maximum voltage gain, there is a stability problem because the ac voltage gain is dependent on r_e

$$A_v = R_C / r_e'$$

- ✓ Since r_e depends on I_E and on temperature, the gain is unstable over changes in temperature
- ✓ With no bypass capacitor, the gain is decreased because R_E is now in the ac circuit and the gain became:

$$A_v = \frac{R_C}{r_e' + R_E} \cong \frac{R_C}{R_E}$$

- **How to minimize the effect of r_e without reducing the voltage gain to its minimum value.**

Swamping




Swamping RE effect on the Gain

- Swamping is a compromise between having a bypass capacitor across RE and having no bypass capacitor at all.
- In a swamped amplifier, RE is partially bypassed so that a reasonable gain can be achieved, and the effect of re on the gain is greatly reduced or eliminated.

$$A_v = \frac{R_C}{r'_e + R_{E1}}$$

- If RE1 is at least ten times larger than re then the effect of re is minimized and the approximate voltage gain for the swamped amplifier is:

$$A_v \cong \frac{R_C}{R_{E1}}$$

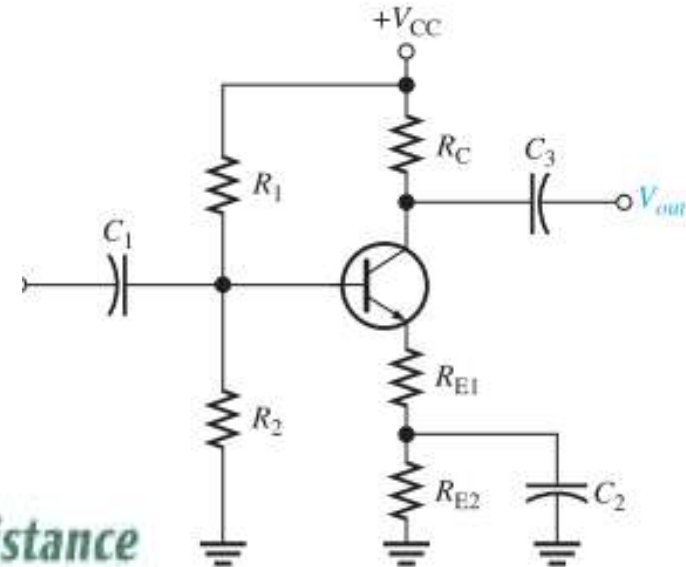

The Effect of Swamping on the Amplifier's Input Resistance

$$R_{in(base)} = \beta_{ac}(r'_e + R_{E1})$$

