

Digital Logic Design

Combinational Logic (Karnuph Maps)


Simplification

- Simplification using Algebra
- Simplification using Karnaugh Maps (K-Maps)


Simplification using Algebra

$$\begin{aligned} F &= X'YZ + X'YZ' + XZ \\ &= X'Y(Z+Z') + XZ \\ &= X'Y \cdot 1 + XZ \\ &= X'Y + XZ \end{aligned}$$

 - Simplification may mean different things
- here it means less number of literals



 (a) $F = \bar{X}YZ + \bar{X}Y\bar{Z} + XZ$



(b) $F = \bar{X}Y + XZ$

Simplification Revisited

- Algebraic methods for minimization is limited:
 - No formal steps, need experience.
 - No guarantee that a minimum is reached
 - Easy to make mistakes
- Karnaugh maps (k-maps) is an alternative convenient way for minimization:
 - A graphical technique
 - Introduced by Maurice Karnaugh in 1953
- K-maps for up to 4 variables are straightforward to build
- Building higher order K-maps (5 or 6 variable) are a bit more cumbersome
- Simplified expression produced by K-maps are in SOP or POS forms

Gray Code & Truth Table Adjacencies

- Remember that Only one bit changes with each number increment in gray codes

A	B	F
0	0	1
0	1	1
1	0	0
1	1	0

These minterms are adjacent in a gray code sense – they differ by only one bit.

We can apply :

$$F = A'B' + A'B = A'(B'+B) = A' (1) = A'$$

A	B	F
0	0	0
0	1	1
1	0	0
1	1	1

- When we group adjacent minterms (gray codes), we Keep common literal only!

Same idea:

$$F = A'B + AB = B$$

Keep common literal only!


K-Map

A	B	F
0	0	0
0	1	1
1	0	0
1	1	1

A different way to draw a truth table !

Take advantage of adjacency and gray codes

$$F = A'B + AB = B$$

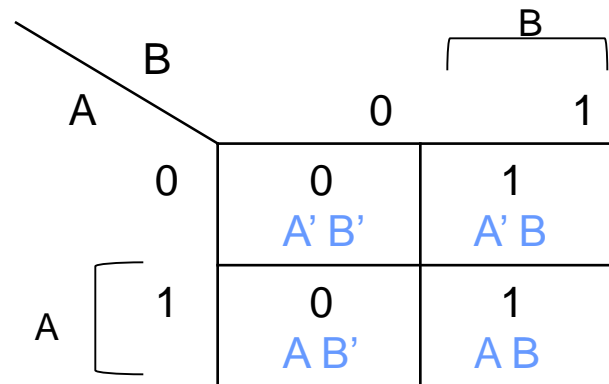

Keep common literal only!

Minimization (Simplification) with K-maps

1. Draw a K-map
2. Combine maximum number of 1's following rules:
 1. Only adjacent squares can be combined
 2. All 1's must be covered
 3. Covering rectangles must be of size 1,2,4,8, ... 2^n
3. Check if all covering are really needed
4. Read off the SOP expression

2-variable K-map

- Given a function with 2 variables: $F(X,Y)$, the total number of minterms are equal to 4:

$$m_0, m_1, m_2, m_3$$

- The size of the k-map is always equal to the total number of minterms.

- Each entry of the k-map corresponds to one minterm for the function:
- Row 0 represents: $X'Y'$, $X'Y$
- Row 1 represents: XY' , XY


		Y	0	1
X	0		m_0	m_1
	1		m_2	m_3

		Y	0	1
X	0		0	1
	1		2	3

Example 1

For a given function $F(X,Y)$ with the following truth table, minimize it using k-maps

X	Y	F
0	0	0
0	1	0
1	0	1
1	1	1

 

Combining all the 1's in only the adjacent squares

The final reduced expression is given by the common literals from the combination:

- Therefore, since for the combination, Y has different values (0, 1), and X has a fixed value of 1,

The reduced function is: $F(X,Y) = X$


Example 2

Q. Simplify the function $F(X,Y) = \sum m(1,2,3)$

Sol. This function has 2 variables, and three 1-squares (three minterms where function is 1)

$$F = m_1 + m_2 + m_3$$

 Note: The 1-squares can be combined more than once




Y is the common literal in the adjacent 1-squares

X is the common literal

Minimized expression: $F = X + Y$

2 variable K-Maps (Adjacency)

 In an n -variable k-map, each square is adjacent to exactly n other squares




Q: What if you have 1 in all squares?

The boolean function does not depend on the variable , so it is a fixed logic 1

3-variable K-maps

 - For 3-variable functions, the k-maps are larger and look different.
- Total number of minterms that need to be accommodated in the k-map = 8



To maintain adjacency neighbors don't have more than 1 different bit

3-variable K-maps

		BC			
		00	01	11	10
A	0	m_0	m_1	m_3	m_2
	1	m_4	m_5	m_7	m_6

Note: You can only combine a power of 2 adjacent 1-squares. For e.g. 2, 4, 8, 16 squares. You cannot combine 3, 7 or 5 squares

		BC			
		00	01	11	10
A	0	m_0	m_1	m_3	m_2
	1	m_4	m_5	m_7	m_6

- Minterms m_0, m_2, m_4, m_6 can be combined as m_0 and m_2 are adjacent to each other, m_4 and m_6 are adjacent to each other
- m_0 and m_4 are also adjacent to each other, m_2 and m_6 are also adjacent to each other

Example 1

Simplify $F = \sum m(1, 3, 4, 6)$ using K-map

		BC			
		00	01	11	10
A	0	0	1	1	2
	1	4	5	7	6

Diagram illustrating a Karnaugh map for the function $F = \sum m(1, 3, 4, 6)$. The map is a 2x4 grid with rows labeled A (0 and 1) and columns labeled BC (00, 01, 11, 10). The cells contain the following values:

- Row A=0: (0,00)=0, (0,01)=1, (0,11)=1, (0,10)=2
- Row A=1: (1,00)=4, (1,01)=5, (1,11)=7, (1,10)=6

The minterms 1, 3, 4, and 6 are marked with bold '1's in the cells (0,01), (0,11), (1,00), and (1,10) respectively. Brackets labeled B and C indicate groupings of the minterms.

Example 1

Simplify $F = \sum m(1, 3, 4, 6)$ using K-map

$$F = A'C + AC'$$

A 2x4 Karnaugh map for variables A, B, and C. The vertical axis is labeled 'A' with values 0 and 1. The horizontal axis is labeled 'BC' with values 00, 01, 11, and 10. The cells are numbered 0 through 7. The cells containing 1 are (A=0, BC=01), (A=0, BC=11), (A=1, BC=00), and (A=1, BC=10). Brackets indicate groupings: a horizontal bracket labeled 'B' covers the top row (A=0), and a vertical bracket labeled 'C' covers the left two columns (BC=00, 01).

A \ BC	00	01	11	10
0	0	1	3	2
1	4	5	7	6

Example 2

Simplify $F = \sum m(0,1, 2, 4, 6)$ using K-map


		BC			
		00	01	11	10
A	0	1 ⁰	1 ¹		1 ²
	1	1 ⁴			1 ⁶

Diagram illustrating the K-map for the function $F = \sum m(0,1, 2, 4, 6)$. The K-map is a 2x4 grid with rows labeled A (0 and 1) and columns labeled BC (00, 01, 11, 10). The cells containing 1s are at (A=0, BC=00), (A=0, BC=01), (A=0, BC=10), (A=1, BC=00), and (A=1, BC=10). The cells are numbered 0 through 7 in blue. A bracket labeled 'B' spans the columns 11 and 10. A bracket labeled 'C' spans the columns 00 and 01.

Example 2

Simplify $F = \sum m(0,1, 2, 4, 6)$ using K-map




$$F = A'B' + C'$$

 

3 variable K-Maps (Adjacency)

A 3-variable map has 12 possible groups of 2 minterms

 
 
 
They become product terms with 2 literals



3 variable K-Maps (Adjacency)

A 3-variable map has 6 possible groups of 4 minterms

They become product terms with 1 literal

   

4-variable K-maps

A 4-variable function will consist of 16 minterms and therefore a size 16 k-map is needed

Each square is adjacent to 4 other squares

A square by itself will represent a minterm with 4 literals

Combining 2 squares will generate a 3-literal output

Combining 4 squares will generate a 2-literal output

Combining 8 squares will generate a 1-literal output

AB \ CD		C			
		00	01	11	10
A	00	m_0	m_1	m_3	m_2
	01	m_4	m_5	m_7	m_6
	11	m_{12}	m_{13}	m_{15}	m_{14}
	10	m_8	m_9	m_{11}	m_{10}

4-variable K-maps (Adjacency)

AB \ CD	00	01	11	10
00	m_0	m_1	m_3	m_2
01	m_4	m_5	m_7	m_6
11	m_{12}	m_{13}	m_{15}	m_{14}
10	m_8	m_9	m_{11}	m_{10}

Note: You can only combine a power of 2 adjacent 1-squares. For e.g. 2, 4, 8, 16 squares. You cannot combine 3, 7 or 5 squares

- Right column and left column are adjacent; can be combined
- Top row and bottom row are adjacent; can be combined
- Many possible 2, 4, 8 groupings

Example

Minimize the function $F(A,B,C,D) = \sum m(1,3,5,6,7,8,9,11,14,15)$

AB \ CD		C			
		00	01	11	10
A	00		1	1	
	01		1	1	1
	11			1	1
	10	1	1	1	

Diagram illustrating the Karnaugh map for the function $F(A,B,C,D) = \sum m(1,3,5,6,7,8,9,11,14,15)$. The map is a 4x4 grid with rows labeled AB (00, 01, 11, 10) and columns labeled CD (00, 01, 11, 10). The function is 1 for the minterms 1, 3, 5, 6, 7, 8, 9, 11, 14, and 15. The map shows four prime implicants circled in blue: a vertical group of four cells (1, 3, 5, 7) labeled C; a horizontal group of four cells (1, 3, 5, 7) labeled B; a horizontal group of two cells (1, 3) labeled D; and a vertical group of two cells (14, 15) labeled D.

$$F = CD + A'D + BC + AB'C'$$

Example

$$F(A,B,C,D) = \sum m(0,1,2,5,8,9,10)$$

A Karnaugh map for the function $F(A,B,C,D) = \sum m(0,1,2,5,8,9,10)$. The map is a 4x4 grid with rows labeled AB (00, 01, 11, 10) and columns labeled CD (00, 01, 11, 10). The cells containing 1s are at (00,00), (00,01), (00,10), (01,01), (10,00), (10,01), and (10,10). Three prime implicants are highlighted: a horizontal group of three cells (00,00), (00,01), and (00,10) labeled C=1; a vertical group of two cells (00,01) and (10,01) labeled B=1; and a horizontal group of two cells (10,00) and (10,01) labeled D=1.


AB \ CD	00	01	11	10
00	1	1		1
01		1		
11				
10	1	1		1

Example

$$F(A,B,C,D) = \Sigma m(0,1,2,5,8,9,10)$$

Solution:

$$F = B' D' + B' C' + A' C' D$$

 

Using (POS)

$$F(A,B,C,D) = \Sigma m(0,1,2,5,8,9,10)$$

Write F in the simplified product of sums (POS) not (SOP)

Two methods?

You already know one!

AB \ CD		C=1			
		00	01	11	10
A=1	00	1	1		1
	01		1		
	11				
	10	1	1		1

Annotations: A bracket on the right side groups the 01 and 10 rows under the label B=1. A bracket below the 00 and 10 columns is labeled D=1.

Using (POS)

$$F(A,B,C,D) = \Sigma m(0,1,2,5,8,9,10)$$


Write F in the simplified product of sums (POS) not (SOP)

- Follow same rule as before but for the ZEROS

$$F' = AB + CD + BD'$$

- Therefore,

$$F'' = F = (A'+B')(C'+D')(B'+D)$$

 

Don't Cares


- In some cases, the output of the function (1 or 0) is not specified for certain input combinations either because
 - The input combination never occurs (Example BCD codes), or
 - We don't care about the output of this particular combination
- Such functions are called **incompletely specified functions**
- Unspecified minterms for these functions are called **don't cares**
- While minimizing a k-map with don't care minterms, their values can be selected to be either (1 or 0) depending on what is needed for achieving a minimized output.

Example

$$F = \sum m(1, 3, 7) + \sum d(0, 5)$$

Circle the x's that help get bigger groups of 1's (or 0's if POS).

Don't circle the x's that don't help.

 

$$F = C$$

Example 2

$$F(A, B, C, D) = \sum m(1, 3, 7, 11, 15) + \sum d(0, 2, 5)$$

-Two possible solutions!

-Both acceptable.

-All 1's covered

		C				B
		00	01	11	10	
A	00	X	1	1	X	}
	01	0	X	1	0	
	11	0	0	1	0	
	10	0	0	1	0	
		D				

(a) $F = CD + \bar{A} \bar{B}$

		C				B
		00	01	11	10	
A	00	X	1	1	X	}
	01	0	X	1	0	
	11	0	0	1	0	
	10	0	0	1	0	
		D				

(b) $F = CD + \bar{A} D$


Src: Mano's Textbook

5-variable K-maps

DE		A=0				A=1			
		00	01	11	10	00	01	11	10
BC	00	m_0	m_1	m_3	m_2	m_{16}	m_{17}	m_{19}	m_{18}
	01	m_4	m_5	m_7	m_6	m_{20}	m_{21}	m_{23}	m_{22}
	11	m_{12}	m_{13}	m_{15}	m_{14}	m_{28}	m_{29}	m_{31}	m_{30}
	10	m_8	m_9	m_{11}	m_{10}	m_{24}	m_{25}	m_{27}	m_{26}

- 32 minterms require 32 squares in the k-map
- Minterms 0-15 belong to the squares with variable A=0, and minterms 16-32 belong to the squares with variable A=1
- Each square in A' is also adjacent to a square in A (one is above the other)
- Minterm 4 is adjacent to 20, and minterm 15 is to 31

NAND Gate is Universal

 



- Therefore, we can build all functions we learned so far using NAND gates ONLY (*Exercise: Prove that NOT can be built with NAND*)
- NAND is a UNIVERSAL gate

Rules for 2-Level NAND Implementations

1. Simplify the function and express it in sum-of-products form
2. Draw a NAND gate for each product term (with 2 literals or more)
3. Draw a single NAND gate at the 2nd level (in place of the OR gate)
4. A term with single literal requires a NOT

Implementation using NANDs

Example: Consider $F = AB + CD$

  


Proof:


$$\begin{aligned} F &= F'' = ((AB)' \cdot (CD)')' \\ &= ((AB)')' + ((CD)')' \\ &= AB + CD \end{aligned}$$

Implementation using NANDs

 
Consider $F = \sum m(1,2,3,4,5,7)$ – Implement using NAND gates



$$F(X, Y) = Z + XY' + X'Y$$

 

NOR Gate is Universal

 



- Therefore, we can build all functions we learned so far using NOR gates ONLY (*Exercise: Prove that NOT can be built with NOR*)
- NOR is a UNIVERSAL gate

Rules for 2-Level NOR Implementations

1. Simplify the function and express it in product of sums form
2. Draw a NOR gate (using OR-NOT symbol) for each sum term (with 2 literals or more)
3. Draw a single NOR gate (using NOT-AND symbol) the 2nd level (in place of the AND gate)
4. A term with single literal requires a NOT


Implementation using NOR gates

Consider $F = (A+B)(C+D)E$

  



Implementation using NOR gates

 Consider $F = \sum m(1,2,3,5,7)$ – Implement using NOR gates



$$F'(X,Y) = Y'Z' + XZ', \text{ or}$$

$$F(X,Y) = (Y+Z)(X'+Z)$$

  

Combinational Circuits

- Two classes of logic circuits:
 - Combinational Circuits
 - Sequential Circuits
- A **Combinational circuit** consists of logic gates
 - Output depends only on input
- A **Sequential circuit** consists of logic gates and memory
 - Output depends on current inputs and previous ones (stored in memory)
 - Memory defines the state of the circuit.

Combinational Circuits



- A combinational circuit has:
 - n Boolean inputs (1 or more),
 - m Boolean outputs (1 or more)
 - logic gates mapping the inputs to the outputs
- How to design a combinational circuit?
 - Use all the information and tools you learned
 - Binary system, Boolean Algebra, K-Maps, etc.
 - Follow the step-by-step procedure given next

Design Procedure

1. Specification

- Write a specification for the circuit if one is not already available
- Specify/Label input and output

2. Formulation

- Derive a truth table or initial Boolean equations that define the required relationships between the inputs and outputs, if not in the specification

3. Optimization

- Apply 2-level and multiple-level optimization (Boolean Algebra, K-Map, software)
- Draw a logic diagram for the resulting circuit using ANDs, ORs, and inverters

Design Procedure (Cont.)

4. Technology Mapping

- Map the logic diagram to the implementation technology selected (e.g. map into NANDs or NORs)

5. Verification

- Verify the correctness of the final design manually or using simulation

Practical Considerations:

- Cost of gates (Number)
- Maximum allowed delay
- Fanin/Fanout

Example 1 (cont.)

Question: Design a circuit that has a 3-bit input and a single output (F) specified as follows:

- $F = 0$, when the input is less than $(5)_{10}$
- $F = 1$, otherwise

Solution:

Step 1 (Specification):

- Label the inputs (3 bits) as X, Y, Z
 - X is the most significant bit, Z is the least significant bit
- The output (1 bit) is F:
 - $F = 1 \rightarrow (101)_2, (110)_2, (111)_2$
 - $F = 0 \rightarrow$ other inputs

Example 1 (cont.)

Step 2 (Formulation)

Obtain Truth table


X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Step 3 (Optimization)

X \ YZ	00	01	11	10
0	0	0	0	0
1	0	1	1	1

$$F = XZ + XY$$


Circuit Diagram

 

SOP can be implemented using all NAND circuit

Example 2

Question (BCD-to-Seven-Segment Decoder)

 



src: Mano's book

- A seven-segment display is digital readout found in electronic devices like clocks, TVs, etc.
 - Made of seven light-emitting diodes (LED) segments; each segment is controlled separately.
- **A BCD-to-Seven-Segment decoder** is a combinational circuit
 - Accepts a decimal digit in BCD (input)
 - Generates appropriate outputs for the segments to display the input decimal digit (output)

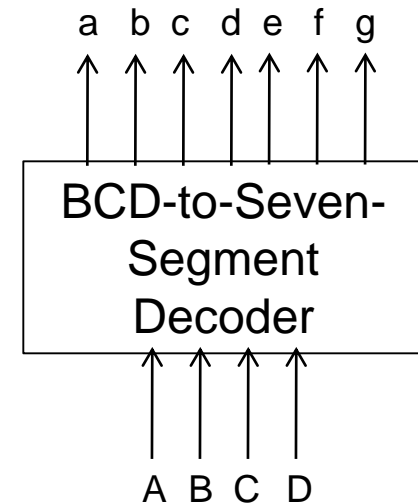 Example 2 (cont.)

Step 1 (Specification):

- 4 inputs (A, B, C, D)
- 7 outputs (a, b, c, d, e, f, g)



Example 2 (cont.)

Step 2 (Formulation)

Decimal	BCD Input				7 Segment Decoder						
	A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	0	0	1	1
10-15	All Other Inputs				0	0	0	0	0	0	0

Invalid
BCD
codes
=
No Light



Example 2 (cont.)

Step 3 (Optimization)

	CD	00	01	11	10
AB	00	1	0	1	1
	01	0	1	1	1
	11	0	0	0	0
	10	1	1	0	0

a

	CD	00	01	11	10
AB	00	1	1	1	1
	01	1	0	1	0
	11	0	0	0	0
	10	1	1	0	0

b

	CD	00	01	11	10
AB	00	1	1	1	0
	01	1	1	1	1
	11	0	0	0	0
	10	1	1	0	0

c

	CD	00	01	11	10
AB	00	1	0	1	1
	01	0	1	0	1
	11	0	0	0	0
	10	1	1	0	0

d

	CD	00	01	11	10
AB	00	1	0	0	1
	01	0	0	0	1
	11	0	0	0	0
	10	1	0	0	0

e

	CD	00	01	11	10
AB	00	1	0	0	0
	01	1	1	0	1
	11	0	0	0	0
	10	1	1	0	0

f

	CD	00	01	11	10
AB	00	0	0	1	1
	01	1	1	0	1
	11	0	0	0	0
	10	1	1	0	0

g

Example 2 (cont.)

Step 3 (Optimization) (cont.)

$$a = A'C + A'BD + AB'C' + B'C'D'$$

$$b = A'B' + A'C'D' + A'CD + B'C'$$

$$c = A'B + B'C' + A'C' + A'D$$

$$d = A'CD' + A'B'C + B'C'D' + AB'C' + A'BC'D$$

$$e = A'CD' + B'C'D'$$

$$f = A'BC' + A'C'D' + A'BD' + AB'C'$$

$$g = A'CD' + A'B'C + A'BC' + AB'C'$$

Exercise: Draw the circuit