

Digital Logic Design

Combinational Logic Part (3)

Half Adder

Design an Adder for 1-bit numbers?

1. Specification:

2 inputs (X,Y)

2 outputs (C,S)

2. Formulation:

X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

3. Optimization/Circuit

X \ Y	0	1
0		1
1	1	

$$S = YX' + XY'$$

$$= X \oplus Y$$

X \ Y	0	1
0		
1		1

$$C = XY$$

Half Adder

Design an Adder for 1-bit numbers?

1. Specification:


2 inputs (X,Y)

2 outputs (C,S)

2. Formulation:

X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

3. Optimization/Circuit

 

Full Adder

A combinational circuit that adds 3 input bits to generate a Sum bit and a Carry bit

X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Sum

X \ YZ	00	01	11	10
0	0	1	0	1
1	1	0	1	0

$$S = X'Y'Z + X'YZ' + XY'Z' + XYZ$$

Carry

X \ YZ	00	01	11	10
0	0	0	1	0
1	0	1	1	1

$$C = XY + YZ + XZ$$

Full Adder = can be implemented with 2 Half Adders

Manipulating the Equations:

$$S = X'Y'Z + X'YZ' + XY'Z' + XYZ$$

$$= (X'Y' + XY)Z + (X'Y + XY')Z'$$

$$= (X \oplus Y)'Z + (X \oplus Y)Z'$$


$$= (X \oplus Y) \oplus Z$$

$$C = XY + XZ + YZ = XY + XZ(Y + Y') + YZ(X + X')$$

$$= XY + XYZ + XY'Z + X'YZ + XYZ$$

$$= XY(1 + Z) + Z(XY' + X'Y)$$

$$= XY + Z(X \oplus Y)$$

 

Bigger Adders

- How to build an adder for n-bit numbers?
 - Example: 4-Bit Adder
 - Inputs ?
9 inputs
 - Outputs ?
5 outputs
 - What is the size of the truth table?
512 rows!
 - How many functions to optimize?
5 functions

Binary Parallel Adder

$$\begin{array}{r} 1\ 0\ 0\ 0 \leftarrow \text{Carry in} \\ 0\ 1\ 0\ 1 \\ +\ 0\ 1\ 1\ 0 \\ \hline 1\ 0\ 1\ 1 \end{array}$$


To add n-bit numbers:

- Use n Full-Adders in parallel
- The carries propagates as in addition by hand
- This is an example of a **hierarchical design**
 - The circuit is broken into small blocks

Binary Parallel Adder

To add n-bit numbers:

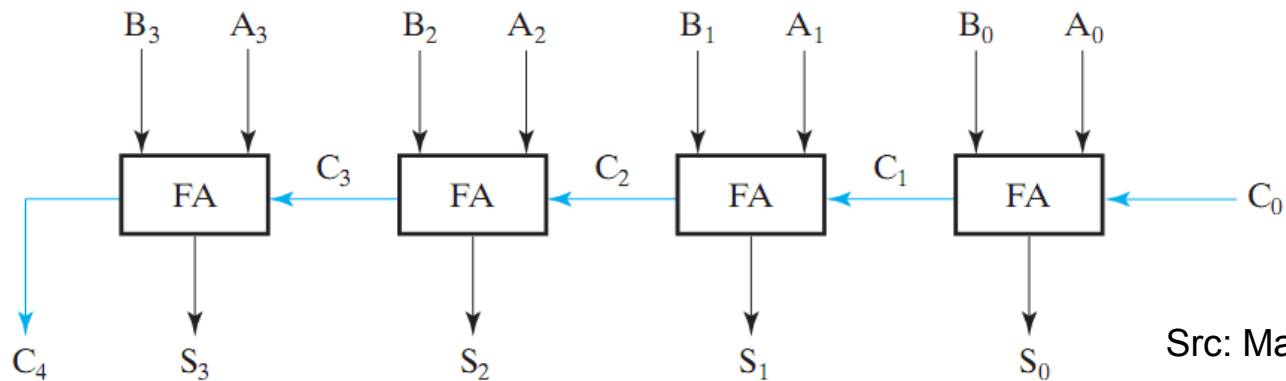- Use n Full-Adders in parallel
- The carries propagate from stage to stage (delay)




Src: Mano's Book

This adder is called *ripple carry adder*

Subtraction (2's Complement)

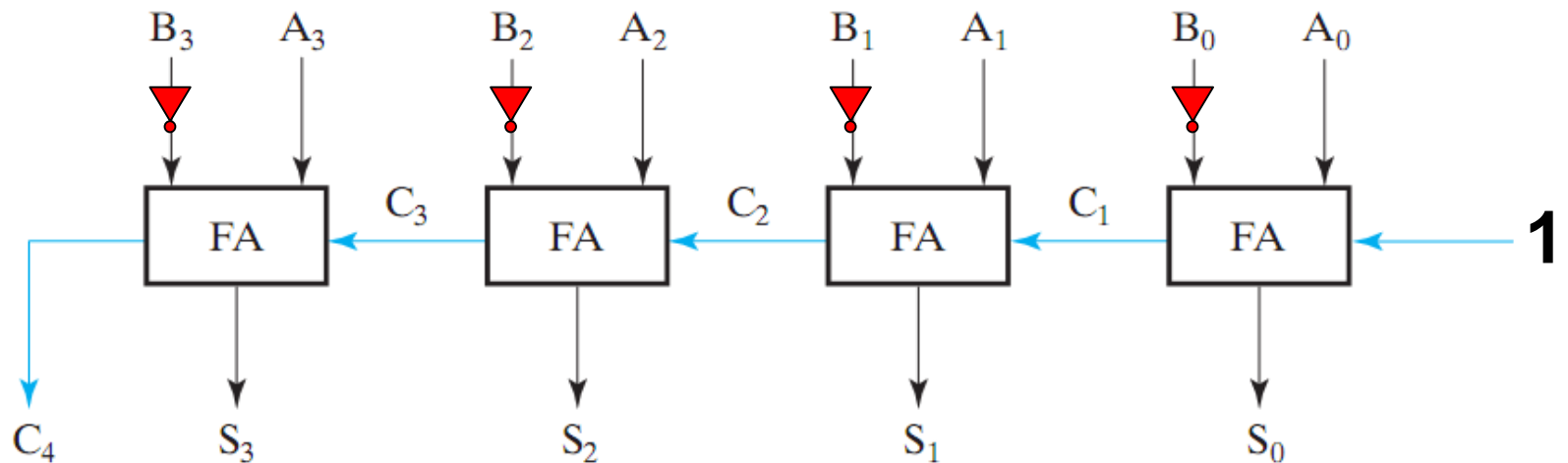How to build a subtractor using 2's complement?



Src: Mano's Book

$$S = A + (-B)$$

Functional Blocks


- Digital systems consists of many components (blocks)
- Useful blocks needed in many designs
 - Arithmetic blocks
 - Decoders
 - Encoders
 - Multiplexers

Examples
of
MSI devices



iPhone motherboard (torontophonerepair.com)


Decoder

 

- Information is represented by binary codes
- **Decoding** - the conversion of an n -bit input code to an m -bit output code with $n \leq m \leq 2^n$ such that each valid code word produces a unique output code
- Circuits that perform decoding are called **decoders**
- A decoder is a minterm generator


Decoder (Uses)

Decode a 3-bit op-codes:

 


Load a
Add b
Store c
.
.

Home automation:

 

Decoder with Enable

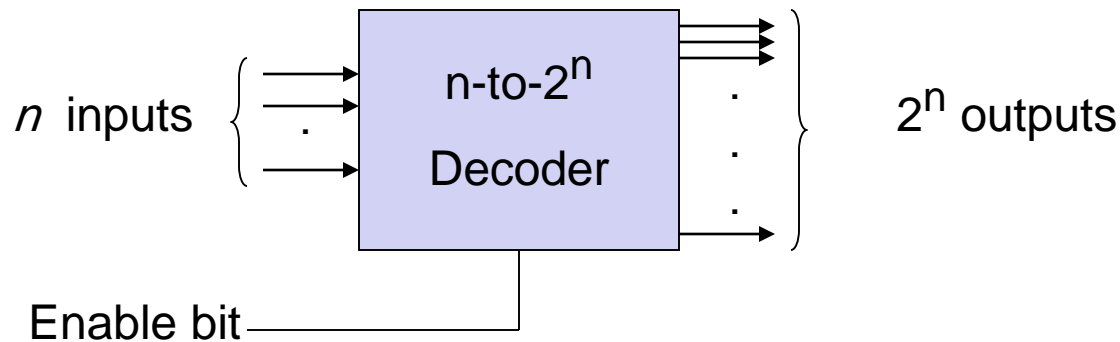- A decoder can have an additional input signal called the enable which enables or disables the output generated by the decoder



2-to-4 Decoder


A 2-to-4 Decoder

2 inputs (A_1, A_0)

$2^2 = 4$ outputs (D_3, D_2, D_1, D_0)

Truth Table

A_1	A_0	D_0	D_1	D_2	D_3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

 


Src: Mano's book

2-to-4 Decoder with Enable



Truth Table

EN	A ₁	A ₀	D ₀	D ₁	D ₂	D ₃
0	X	X	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1


 


Src: Mano's book

3-to-8 Decoder

 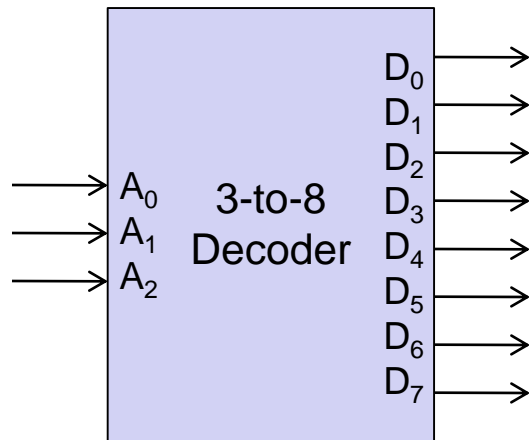

3-to-8 Decoder (using 2 2-to-4 decoders)

 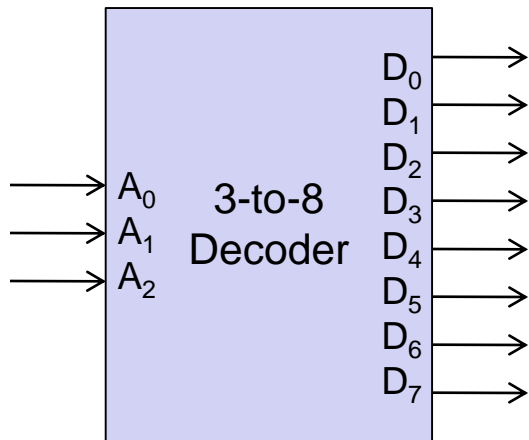

Decoder-Based Combinational Circuits

- A Decoder generates all the minterms
- A boolean function can be expressed as a sum of minterms
- Any boolean function can be implemented using a decoder and an OR gate.
- **Note: The Boolean function must be represented as minterms (not minimized form)**

Decoder-Based Combinational Circuits (Example)


X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = \sum m (1,2,4,7)$$

$$C = \sum m (3,5,6,7)$$


3 inputs and 8 possible minterms

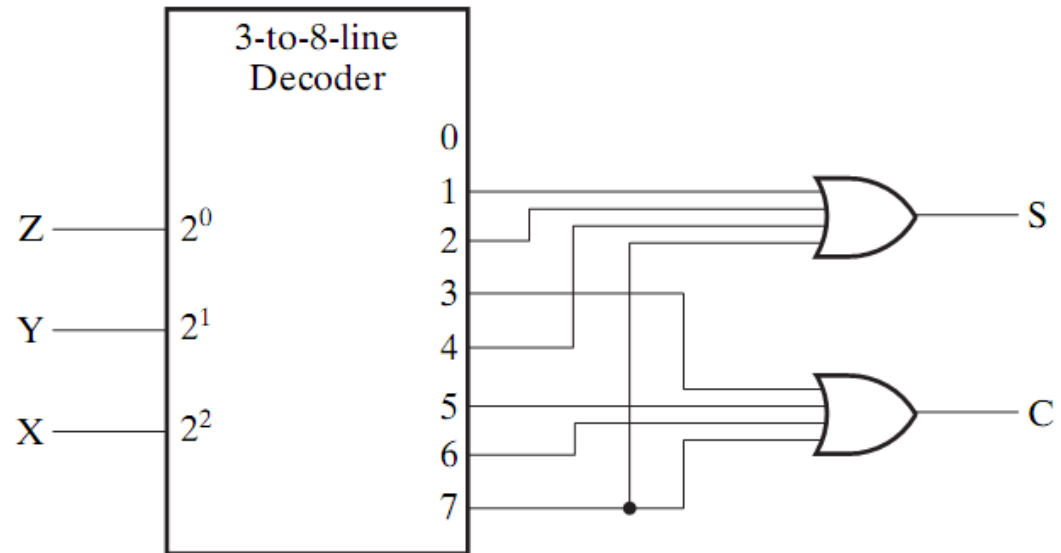3-to-8 decoder can be used for implementing this circuit




Src: Mano's book

Encoder

 

- **Encoding** - the opposite of decoding - the conversion of an m -bit input code to a n -bit output code with $n \leq m \leq 2^n$ such that each valid code word produces a unique output code
- Circuits that perform encoding are called **encoders**
- An encoder has 2^n (or fewer) input lines and n output lines which generate the binary code corresponding to the input values
- Typically, an encoder converts a code containing exactly one bit that is 1 to a binary code corresponding to the position in which the 1 appears.


8-to-3 Encoder

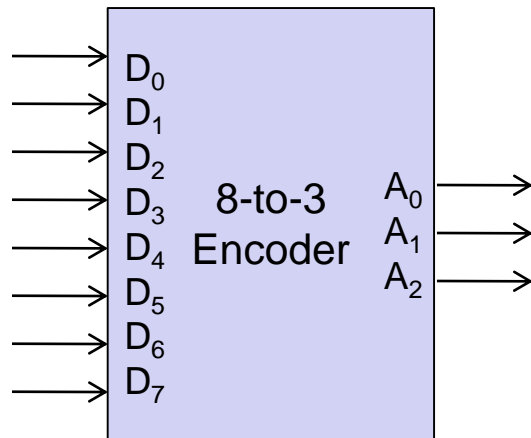

Description:


- $2^3 = 8$ inputs, 3 outputs
- one input = 1, others = 0's
- Each input generate unique binary code

8-to-3 Encoder (truth table)

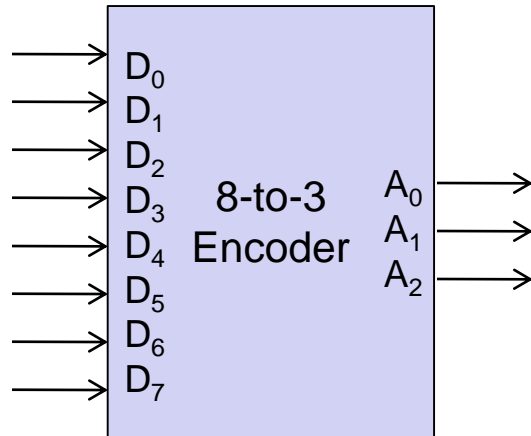


inputs								outputs		
D_7	D_6	D_5	D_4	D_3	D_2	D_1	D_0	A_2	A_1	A_0
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

8-to-3 Encoder (truth table)

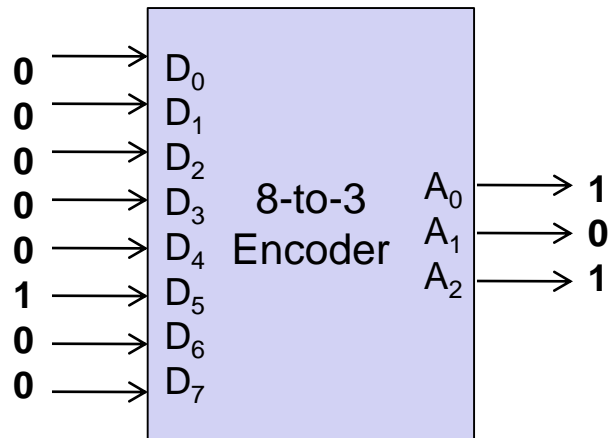


inputs								outputs		
D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	A ₂	A ₁	A ₀
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

8-to-3 Encoder (truth table)

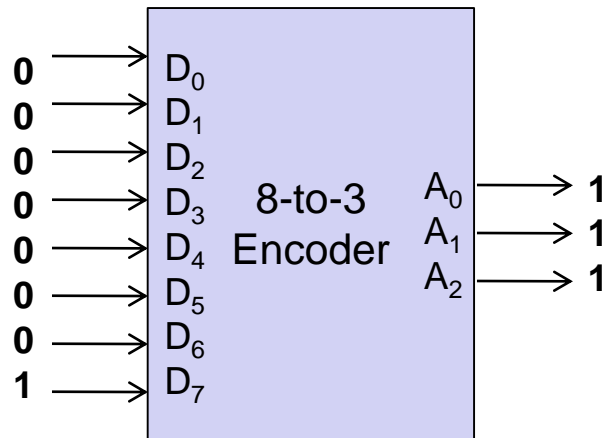

inputs								outputs		
D_7	D_6	D_5	D_4	D_3	D_2	D_1	D_0	A_2	A_1	A_0
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

8-to-3 Encoder (equations)

 

Output equations:

$$A_0 = ?$$


$$A_1 = ?$$

$$A_2 = ?$$

inputs								outputs		
D_7	D_6	D_5	D_4	D_3	D_2	D_1	D_0	A_2	A_1	A_0
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

Note: This truth table is not complete! Why?

8-to-3 Encoder (equations)

 

inputs								outputs		
D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	A ₂	A ₁	A ₀
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1


Output equations:

$$A_0 = D_1 + D_3 + D_5 + D_7$$

$$A_1 = ?$$

$$A_2 = ?$$

8-to-3 Encoder (equations)

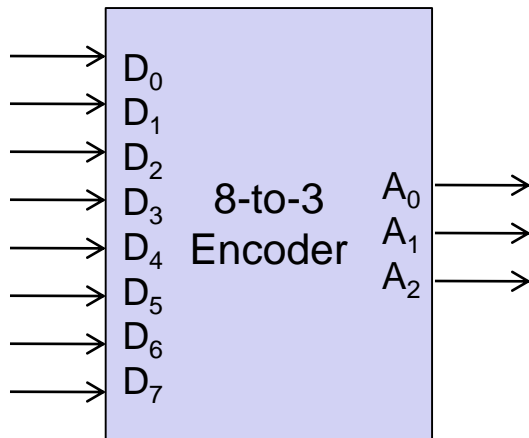

inputs								outputs		
D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	A ₂	A ₁	A ₀
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1


Output equations:

$$A_0 = D_1 + D_3 + D_5 + D_7$$

$$A_1 = D_2 + D_3 + D_6 + D_7$$

$$A_2 = ?$$

8-to-3 Encoder (equations)

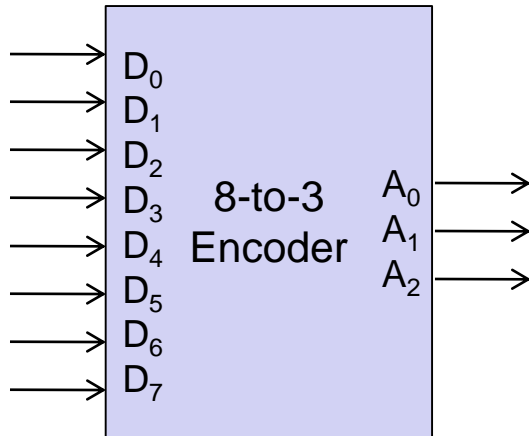

Output equations:


$$A_0 = D_1 + D_3 + D_5 + D_7$$

$$A_1 = D_2 + D_3 + D_6 + D_7$$

$$A_2 = D_4 + D_5 + D_6 + D_7$$

inputs								outputs		
D_7	D_6	D_5	D_4	D_3	D_2	D_1	D_0	A_2	A_1	A_0
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

8-to-3 Encoder (circuit)

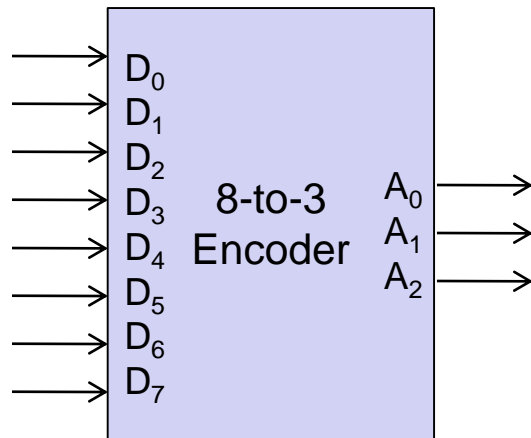


Output equations:

$$A_0 = D_1 + D_3 + D_5 + D_7$$

$$A_1 = D_2 + D_3 + D_6 + D_7$$

$$A_2 = D_4 + D_5 + D_6 + D_7$$

 

8-to-3 Encoder (limitations)

Two Limitations:

1. Two or more inputs = 1
 - Example: $D_3 = D_6 = 1$
 - $A_2A_1A_0 = 111$ **X**
2. All inputs = 0
 - Same as $D_0 = 1$


inputs								outputs		
D_7	D_6	D_5	D_4	D_3	D_2	D_1	D_0	A_2	A_1	A_0
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

Priority Encoder

- Address the previous two limitations
 1. Two or more inputs = 1
Consider the bit with highest priority
 2. All inputs = 0
Add another output v to indicate this combination


Multiplexers

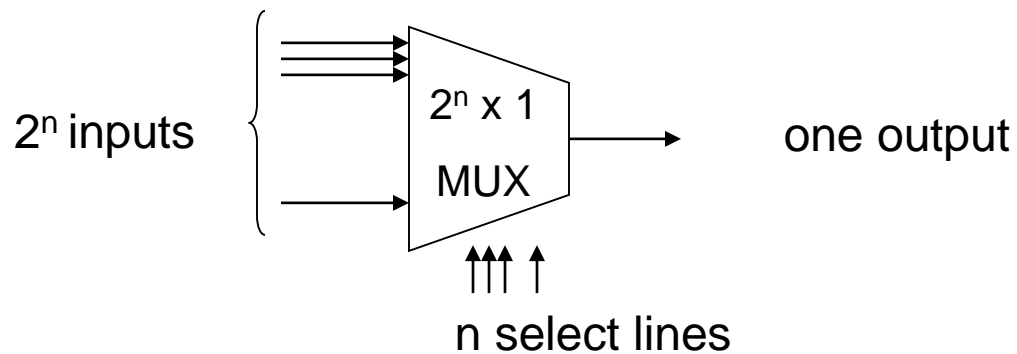- A combinational circuit
- Has a single output
- Directs one of 2^n input to the output
- Choosing which input is done using n select lines



2x1 MUX

 - A 2x1 multiplexer (MUX) has 2 inputs, 1 output and 1 select line



- $Y=D_0$ for $S_0=0$, and $Y=D_1$ for $S_0=1$
- Minimizing will result in: $Y = S_0'.D_0 + S_0.D_1$
- **Exercise: Draw the circuit?**

4x1 MUX


- A 4x1 MUX has 4 input lines (D_0, D_1, D_2, D_3), 1 output Y , and 2 Select Lines (S_0, S_1)
- The output for different select values is defined as:

$$S_0S_1 = 00, Y = D_0$$

$$S_0S_1 = 01, Y = D_1$$

$$S_0S_1 = 10, Y = D_2$$


$$S_0S_1 = 11, Y = D_3$$

 


- $Y = \overline{S_1}\overline{S_0}D_0 + \overline{S_1}S_0D_1 + S_1\overline{S_0}D_2 + S_1S_0D_3$
- The output Y depends on the minterms of the Select lines
- **Exercise: Draw the circuit?**

DeMultiplexer

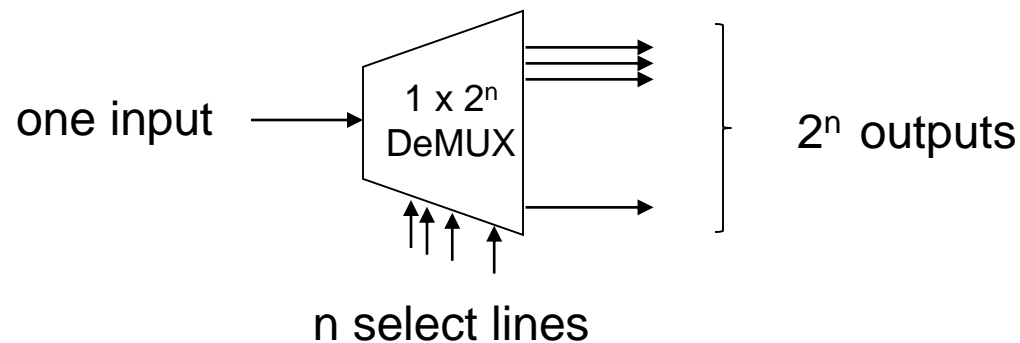- Performs the inverse operation of a MUX
- It has one input and 2^n outputs
- The input is passed to one of the outputs based on the n select line



1x2 DeMUX

 

The circuit has an input E, the outputs are given by:


$$D_0 = E, \text{ if } S=0$$

$$D_1 = E, \text{ if } S=1$$

$$D_0 = \overline{S} E$$

$$D_1 = S E$$

1x4 DeMUX

 

The circuit has an input E , the outputs are given by:

$$D_0 = E, \text{ if } S_0 S_1 = 00$$

$$D_0 = S_1' S_0' E$$

$$D_1 = E, \text{ if } S_0 S_1 = 01$$

$$D_1 = S_1' S_0 E$$


$$D_2 = E, \text{ if } S_0 S_1 = 10$$

$$D_2 = S_1 S_0' E$$

$$D_3 = E, \text{ if } S_0 S_1 = 11$$

$$D_3 = S_1 S_0 E$$

DeMUX vs Decoder

 


- A 1x4 DeMUX is equivalent to a 2x4 Decoder with an Enable
 - Think of $S_1 S_0$ as the decoder's input
 - Think of E as the decoder's enable
- In general, a DeMux is equivalent to a Decoder with an Enable

DeMUX vs Decoder

2x4 Decoder Truth Table

EN	A ₁	A ₀	D ₀	D ₁	D ₂	D ₃
0	X	X	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

 


Src: Mano's book

DeMUX vs Decoder

2x4 Decoder Truth Table

EN	A ₁	A ₀	D ₀	D ₁	D ₂	D ₃
0	X	X	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

 

To convert a 2x4 Decoder with an Enable to a 1x4 DeMux:

- Assign DeMux's input (actual data) to EN
- Assign DeMux's selection lines (S₁, S₀) to the inputs A₁, A₀

Src: Mano's book