

Electrical Circuits (2)



Lecture 8 Transient Analysis Part(2)

Dr.Eng. Basem ElHalawany

First-Order RL Transient Step-Response


- The switch “S” is closed at $t = 0$
- Apply KVL to the circuit in figure:

$$Ri + L \frac{di}{dt} = V$$

- Rearranging and using “D” operator notation :

$$\left(D + \frac{R}{L}\right)i = \frac{V}{L}$$

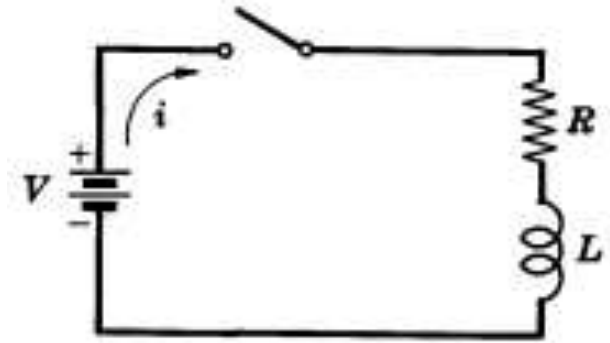This Equation is a first order, linear differential equation



1. Complementary (Transient) Solution

The auxiliary equation is : $m + \frac{R}{L} = 0$

$$i = Ae^{mt} = Ae^{-\frac{R}{L}t}$$

$$\tau = \frac{R}{L}$$

Time constant

2. Particular (Steady-State) Solution

The steady-state value of the current for DC source is :

$$I_{ss} = \frac{V}{R}$$

First-Order RL Transient Step-Response

➤ The total solution is:

$$i = Ae^{\frac{-R}{L}t} + \frac{V}{R}$$

Since The initial current is zero:

$$0 = A + \frac{V}{R}$$



$$i = -\frac{V}{R}e^{-(R/L)t} + \frac{V}{R} = \frac{V}{R}(1 - e^{-(R/L)t})$$

➤ The voltage across the resistor is:

$$v_R = Ri = V(1 - e^{-(R/L)t})$$

➤ The voltage across the inductor is:
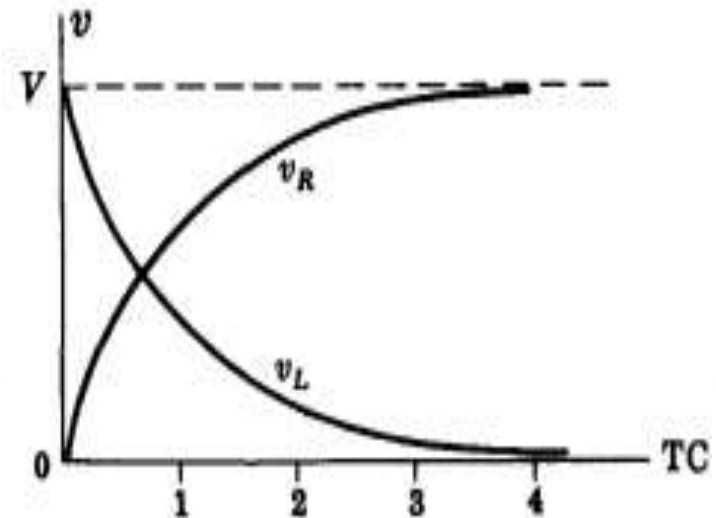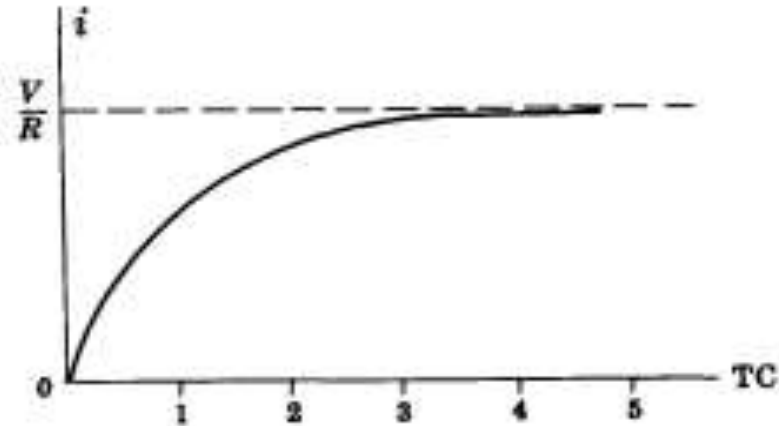
$$v_L = L \frac{di}{dt} = L \frac{d}{dt} \left\{ \frac{V}{R}(1 - e^{-(R/L)t}) \right\} = Ve^{-(R/L)t}$$




$$v_R + v_L = V(1 - e^{-(R/L)t}) + Ve^{-(R/L)t} = V$$



First-Order RL Transient (Discharge)

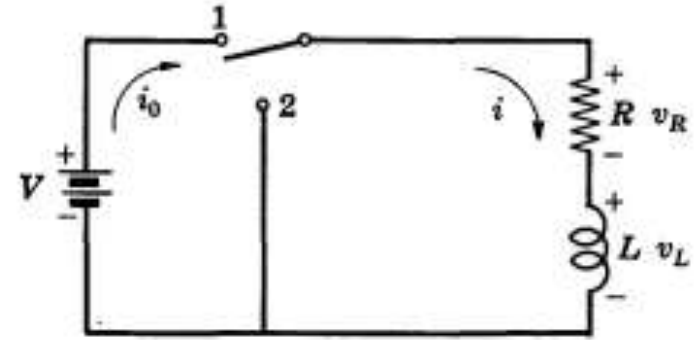- The RL circuit shown in Figure contains an initial current of (V/R)
- The Switch "S" is moved to position "2" at $t=0$





$$L \frac{di}{dt} + Ri = 0 \quad \text{or} \quad \left(D + \frac{R}{L} \right) i = 0$$

- The solution is the transient (Complementary) part only.

$$i = ce^{-(R/L)t}$$

- Using the initial condition of the current, we get:

$$i = \frac{V}{R} e^{-(R/L)t}$$

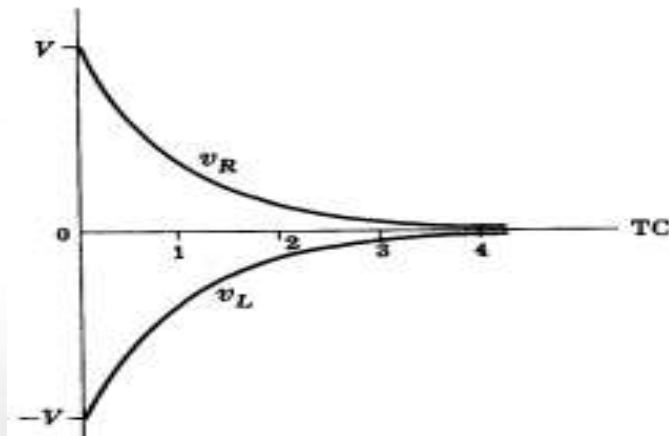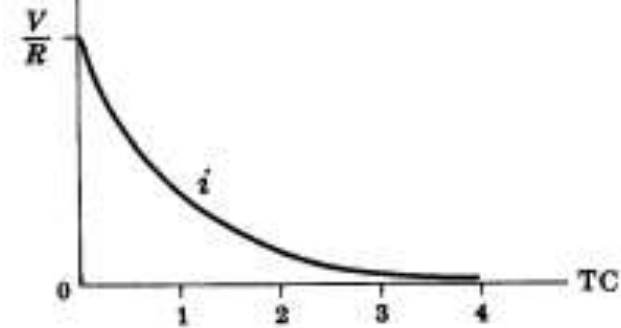

- The corresponding voltages across the resistance and inductance are

$$v_R = Ri = Ve^{-(R/L)t}$$

$$v_L = L \frac{di}{dt} = -Ve^{-(R/L)t}$$



Examples

A series RL circuit with $R = 50$ ohms and $L = 10$ h has a constant voltage $V = 100$ v applied at $t = 0$ by the closing of a switch. Find (a) the equations for i , v_R and v_L , (b) the current at $t = .5$ seconds and (c) the time at which $v_R = v_L$.

(a) The differential equation for the given circuit is

$$50i + 10 \frac{di}{dt} = 100 \quad \text{or} \quad (D + 5)i = 10$$

the complete solution is $i = i_c + i_p = ce^{-5t} + 2$

At $t = 0$, $i_0 = 0$ and $0 = c(1) + 2$ or $c = -2$. Then

$$i = 2(1 - e^{-5t})$$


$$v_R = Ri = 100(1 - e^{-5t})$$

$$v_L = L \frac{di}{dt} = 100e^{-5t}$$



Examples

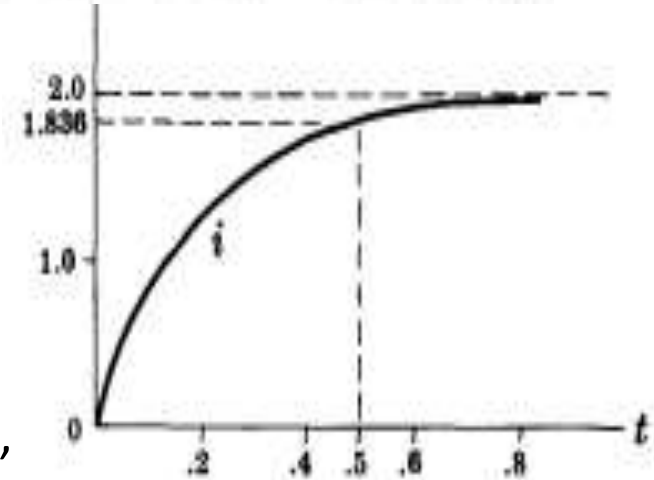(b) Put $t = .5$ sec in (3) and obtain $i = 2(1 - e^{-5(.5)}) = 2(1 - .082) = 1.836$ amp.




(b) For the two voltage to be equal:
each must be 50 volts since the applied voltage is 100,

$$v_L = 50 = 100e^{-5t}.$$

$$e^{-5t} = .5 \text{ or } 5t = .693,$$


$$t = .1386 \text{ sec.}$$

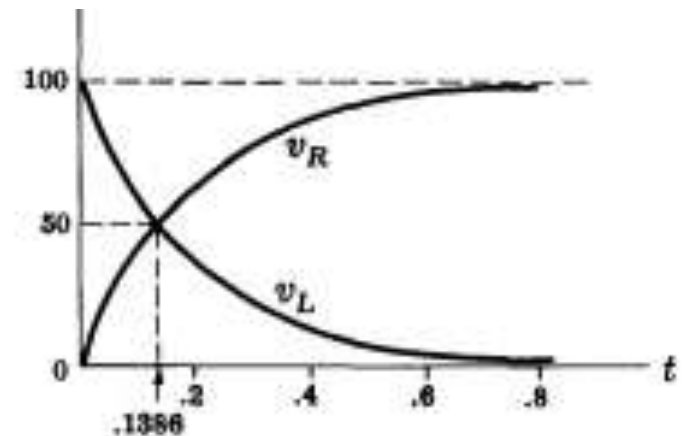

Second-Order RLC Transient (Step Response)

- The Switch “S” is closed at $t=0$
- Applying KVL will produce the following Integro-Differential equation:
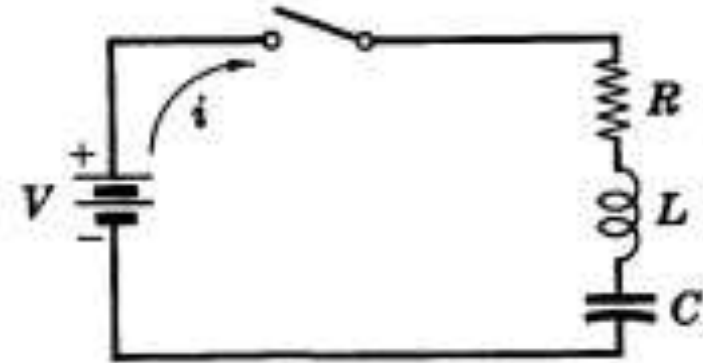
$$Ri + L \frac{di}{dt} + \frac{1}{C} \int i dt = V$$



- Differentiating, we obtain

$$L \frac{d^2i}{dt^2} + R \frac{di}{dt} + \frac{i}{C} = 0 \quad \text{or} \quad \left(D^2 + \frac{R}{L}D + \frac{1}{LC} \right) i = 0$$

This **second order**, linear differential equation is of the **homogeneous** type with a **particular solution of zero**.

- ✓ The complementary function can be one of **three different types** according to **the roots of the auxiliary equation** which depends upon the relative magnitudes of R, L and C.



$$m^2 + \frac{R}{L}m + \frac{1}{LC} = 0$$

Second-Order RLC Transient (Step Response)

We can Rewrite the auxiliary equation as:

$$m^2 + \frac{R}{L}m + \frac{1}{LC} = 0$$

$$m^2 + 2\zeta\omega_0 m + \omega_0^2 = 0$$

ζ : exponential damping ratio

ω_0 : undamped natural frequency

$$\begin{cases} \frac{R}{L} = 2\zeta\omega_0 \\ \frac{1}{\sqrt{LC}} = \omega_0 \end{cases}$$

➤ The roots of the equation (or natural frequencies):

$$\begin{cases} m_1 = -\zeta\omega_0 + \omega_0\sqrt{\zeta^2 - 1} \\ m_2 = -\zeta\omega_0 - \omega_0\sqrt{\zeta^2 - 1} \end{cases}$$

$$\begin{cases} m_1 = -\frac{R}{2L} + \sqrt{\frac{R^2}{4L^2} - \frac{1}{LC}} \\ m_2 = -\frac{R}{2L} - \sqrt{\frac{R^2}{4L^2} - \frac{1}{LC}} \end{cases}$$

$$\begin{cases} m_1 = -\sigma + \sqrt{\sigma^2 - \omega_0^2} \\ m_2 = -\sigma - \sqrt{\sigma^2 - \omega_0^2} \end{cases}$$



Second-Order RLC Transient (Step Response)

Case 1: Overdamped,

$$\zeta > 1$$

$\Rightarrow m_1, m_2$ are real and unequal

$$\frac{R}{2L} > \frac{1}{\sqrt{LC}}$$

$$\sigma^2 > \omega_0^2$$

$$\begin{cases} m_1 = -\zeta\omega_0 + \omega_0\sqrt{\zeta^2 - 1} \\ m_2 = -\zeta\omega_0 - \omega_0\sqrt{\zeta^2 - 1} \end{cases}$$

Natural response is the sum of two decaying exponentials:

$$i_{tr} = K_1 e^{m_1 t} + K_2 e^{m_2 t}$$

Case 2: Critically damped,

$$\zeta = 1$$

$\Rightarrow m_1, m_2$ are real and equal.

$$\frac{R}{2L} = \frac{1}{\sqrt{LC}}$$

$$\sigma^2 = \omega_0^2$$

$$m_1 = m_2 = -\omega_0$$

$$x_c(t) = e^{m_1 t} (B_1 + B_2 t)$$

Use the initial conditions to get the constants

Usually it is reduced to:

$$x_c(t) = B.t.e^{m_1 t}$$

Case 3: Underdamped,

$$\zeta < 1$$

$$\frac{R}{2L} < \frac{1}{\sqrt{LC}}$$

$$\sigma^2 < \omega_o^2$$


$\Rightarrow m_1, m_2$ are complex and conjugate.

$$\begin{cases} m_1 = -\sigma + j\omega_d = (-\zeta\omega_0) + j(\omega_0\sqrt{1-\zeta^2}) \\ m_2 = -\sigma - j\omega_d = (-\zeta\omega_0) - j(\omega_0\sqrt{1-\zeta^2}) \end{cases}$$

Natural response is an exponentially damped oscillatory response:
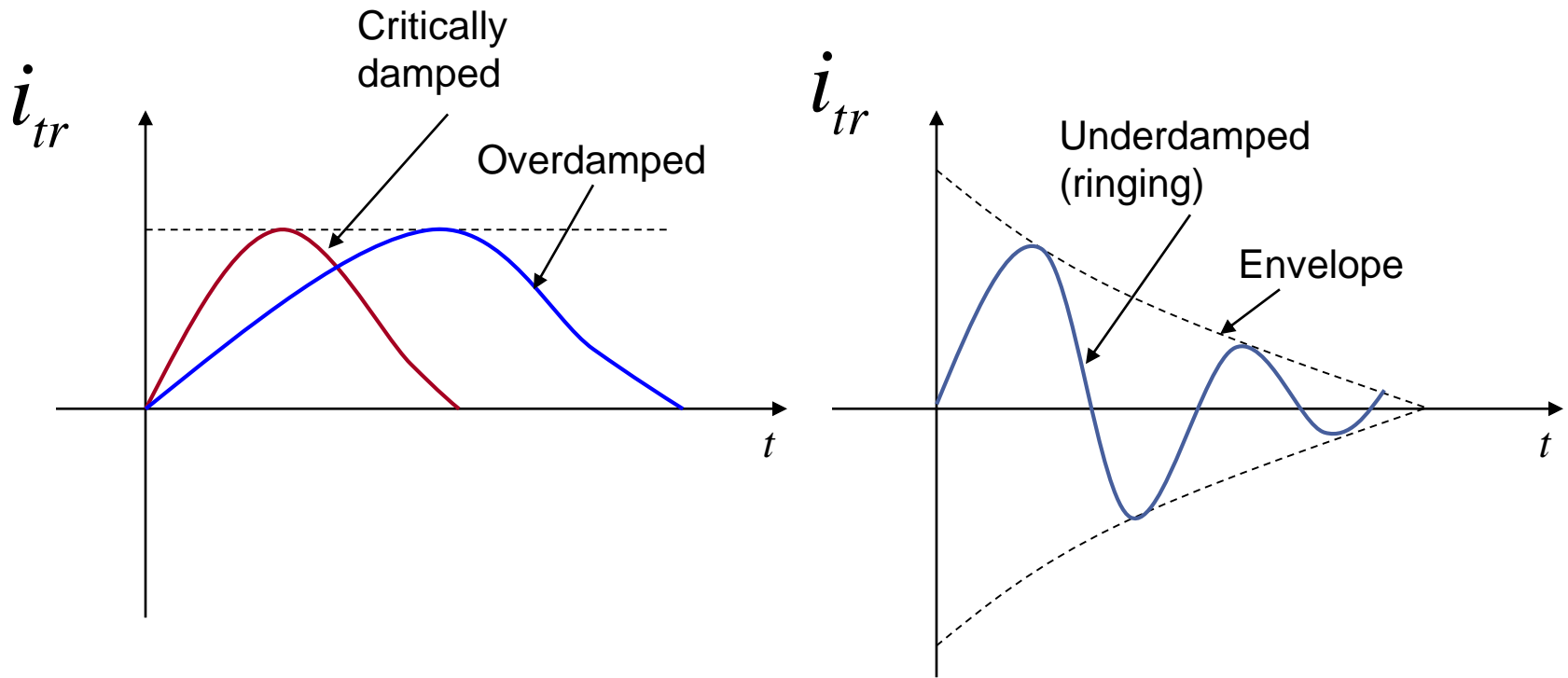
$$i_{tr} = e^{-\sigma t} \{ A_1 \cos(\omega_d t) + A_2 \sin(\omega_d t) \}$$





- ✓ The current in all cases contains the exponential decaying factor (damping factor) assuring that the final value is zero
- ✓ In other words, assuring that the complementary function decays in a relatively short time.




Alternating Current Transients

RL Sinusoidal Transient

$$Ri + L \frac{di}{dt} = V_{\max} \sin(\omega t + \phi)$$
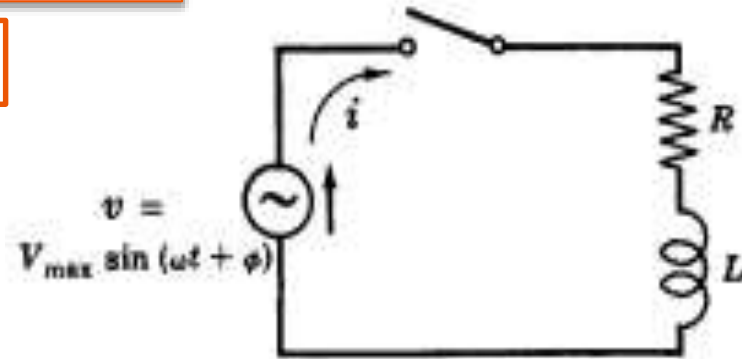
$$\left(D + \frac{R}{L}\right)i = \frac{V_{\max}}{L} \sin(\omega t + \phi)$$



1. Complementary (Transient) Solution is the solution of the homogeneous 1st order DE

The same as before, The auxiliary equation is :

$$m + \frac{R}{L} = 0$$

The complementary function is $i_c = ce^{-(R/L)t}$

2. Particular (Steady-State) Solution

The steady-state value of the current for ac source is :

$$I_{ss} = \frac{V_{\max}}{\sqrt{X_L^2 + R^2}} \sin(\omega t + \phi - \tan^{-1}(\omega L / R))$$



Alternating Current Transients

RL Sinusoidal Transient

The complete solution is

$$i = i_c + i_p = ce^{-(R/L)t} + \frac{V_{\max}}{\sqrt{R^2 + \omega^2 L^2}} \sin(\omega t + \phi - \tan^{-1} \omega L/R)$$

Use the initial condition to find the value of c

$$i_0 = 0 = c(1) + \frac{V_{\max}}{\sqrt{R^2 + \omega^2 L^2}} \sin(\phi - \tan^{-1} \omega L/R)$$

$$c = \frac{-V_{\max}}{\sqrt{R^2 + \omega^2 L^2}} \sin(\phi - \tan^{-1} \omega L/R)$$


Substituting by the constant values, we get:

$$i = e^{-(R/L)t} \left[\frac{-V_{\max}}{\sqrt{R^2 + \omega^2 L^2}} \sin(\phi - \tan^{-1} \omega L/R) \right] + \frac{V_{\max}}{\sqrt{R^2 + \omega^2 L^2}} \sin(\omega t + \phi - \tan^{-1} \omega L/R) \quad (5)$$



Alternating Current Transients

RC Sinusoidal Transient

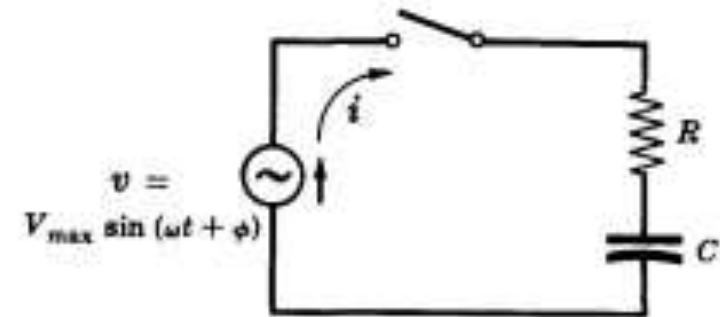

$$i = e^{-t/RC} \left[\frac{V_{\max}}{R} \sin \phi - \frac{V_{\max}}{\sqrt{R^2 + (1/\omega C)^2}} \sin(\phi + \tan^{-1} 1/\omega CR) \right] + \frac{V_{\max}}{\sqrt{R^2 + (1/\omega C)^2}} \sin(\omega t + \phi + \tan^{-1} 1/\omega CR)$$



Alternating Current Transients


RLC Sinusoidal Transient

➤ Particular (Steady-State) Solution

$$i_p = \frac{V_{\max}}{\sqrt{R^2 + (1/\omega C - \omega L)^2}} \sin\left(\omega t + \phi + \tan^{-1} \frac{(1/\omega C - \omega L)}{R}\right)$$

➤ Complementary(Transient) Solution

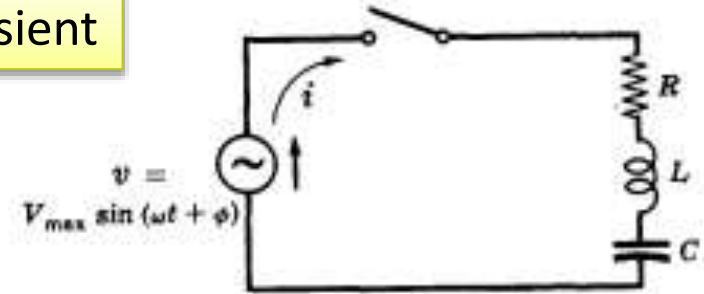The complementary function is identical to that of the DC series RLC circuit examined previously where the result was overdamped, critically damped or oscillatory, depending upon R, L and C.



For the complete analysis
Check Chapter 16 Schaum Series (Old version)




Transient Analysis using Laplace Transform

- Laplace transform is considered one of the most important tools in Electrical Engineering
- It can be used for:
 - ✓ Solving differential equations
 - ✓ Circuit analysis (Transient and general circuit analysis)
 - ✓ Digital Signal processing in Communications and
 - ✓ Digital Control



Transient Analysis using Laplace Transform

Circuit Elements in the “S” Domain

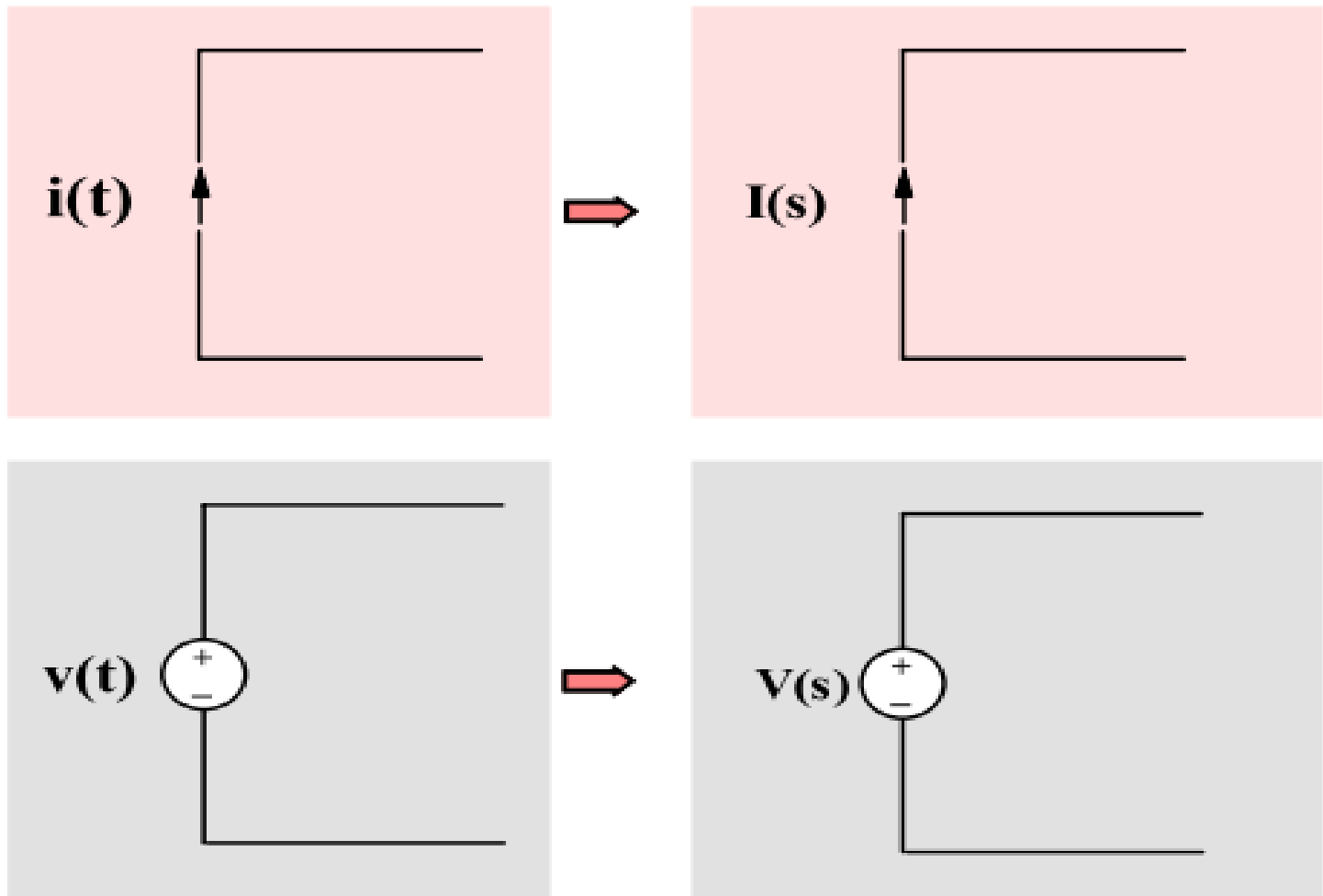

Circuit Elements in the “S” Domain



Circuit Element Modeling

The method used so far follows the steps:

1. Write the differential equation model
2. Use Laplace transform to convert the model to an algebraic form

1.0 Resistance


Resistor

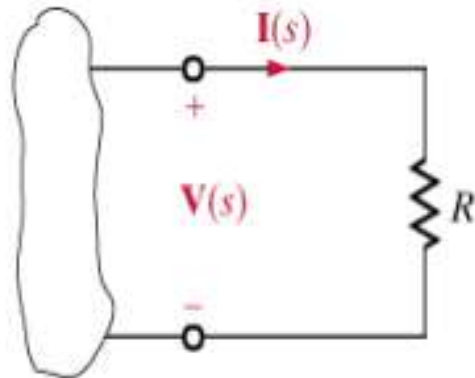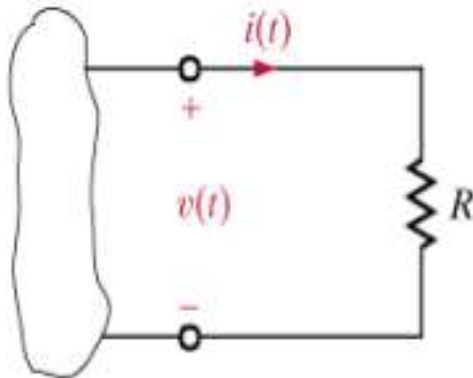

$$v(t) = Ri(t) \Rightarrow V(s) = RI(s)$$


Circuit Elements in the “S” Domain

2.0 Inductor

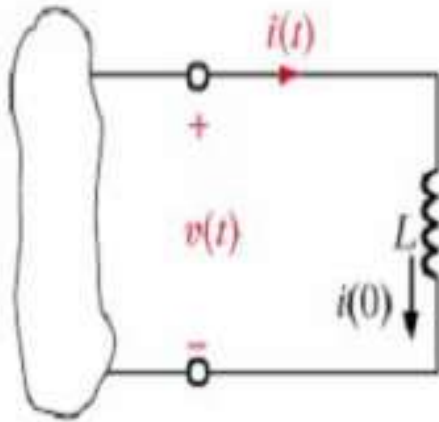

$$v(t) = L \frac{di}{dt}(t)$$

\Rightarrow


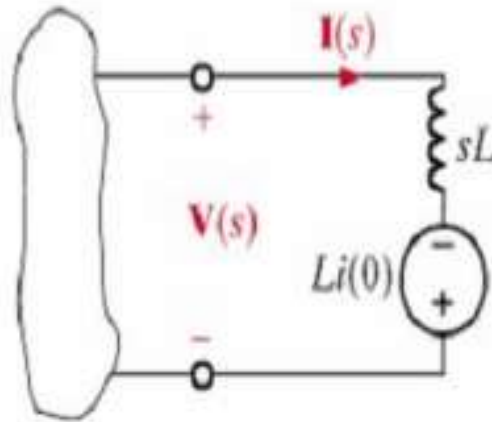


$$V(s) = LsI(s) - Li(0)$$



Circuit Elements in the “S” Domain

3.0 Capacitor

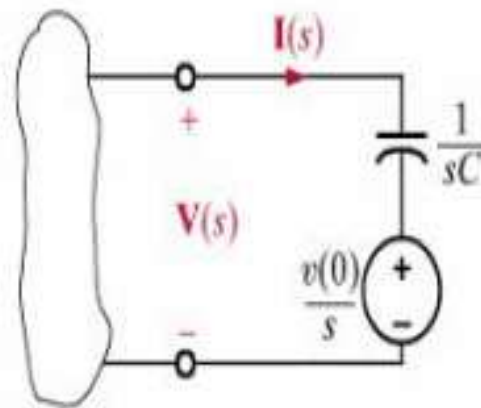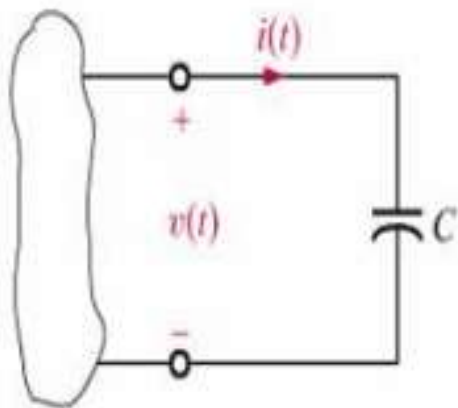

$$v_c(t) = \frac{1}{C} \int_0^t i(t) dt + v_c(0)$$

$$V(s) = \frac{1}{Cs} I(s) + \frac{v(0)}{s}$$



First-Order RL Transient (Step-Response)

- The switch “S” is closed at $t = 0$ to allow the step voltage to excite the circuit
- Apply KVL to the circuit in figure:

$$Ri + L \frac{di}{dt} = V$$

- Apply Laplace Transform on both sides


$$R.I(s) + L[s.I(s) - i(0)] = \frac{V}{s}$$

$i(0) = 0$ >> initial value of the current at $t = 0$

$$I(s).[R + sL] = \frac{V}{s}$$

$$I(s) = \frac{V}{s[R + sL]} = \frac{V/L}{s[s + R/L]}$$

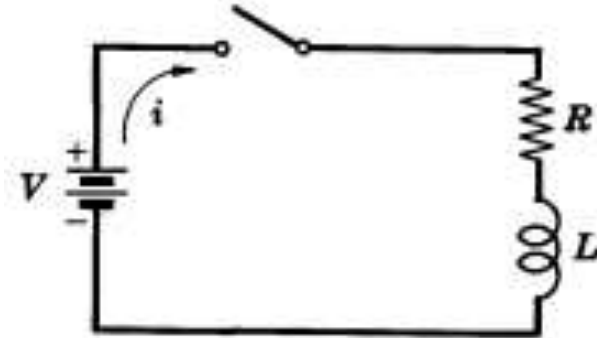- Apply the inverse Laplace Transform technique to get the expression of the current $i(t)$



First-Order RL Transient (Step-Response)

➤ Use the partial fraction technique

$$I(s) = \frac{V/L}{s[s + R/L]} = \frac{A_1}{s} + \frac{A_2}{s + R/L}$$

➤ Multiply both sides by $s.(s + R/L)$

$$V/L = A_1.(s + R/L) + A_2.s$$

$$\dots\dots = (A_1 + A_2).s + A_1 \cdot \frac{R}{L}$$

$$A_1 = V/R \quad A_2 = -V/R$$

➤ So, the current in s-domain is given by:

➤ Apply the inverse Laplace transform :

The same as last lecture

OR

$$A_1 = \{s * I(s)\} |_{s=0} = \frac{V}{R}$$

$$A_2 = \{(s + R/L) * I(s)\} |_{s=-R/L} = -\frac{V}{R}$$

both sides Compare the coefficients

$$I(s) = \frac{V}{R} \left(\frac{1}{s} - \frac{1}{s + R/L} \right)$$

$$i(t) = \frac{V}{R} \left(1 - e^{-\frac{R}{L}t} \right); t > 0$$



First-Order RL Transient (Discharge)

- The RL circuit shown in Figure contains an initial current of (V/R)
- The Switch "S" is moved to position "2" at $t=0$

$$L \frac{di}{dt} + Ri = 0$$

- Apply Laplace Transform on both sides

$$R.I(s) + L[s.I(s) - i(0)] = 0$$

$i(0) = V/R$ >> initial value of the current at $t = 0$

$$R.I(s) + L[s.I(s) - \frac{V}{R}] = 0$$




$$I(s) = \frac{V/R}{[s + R/L]}$$

- Apply the inverse Laplace transform :

$$i(t) = \frac{V}{R} \cdot e^{-\frac{R}{L}t} = I_o \cdot e^{-\frac{R}{L}t}; t > 0$$

- The same as before

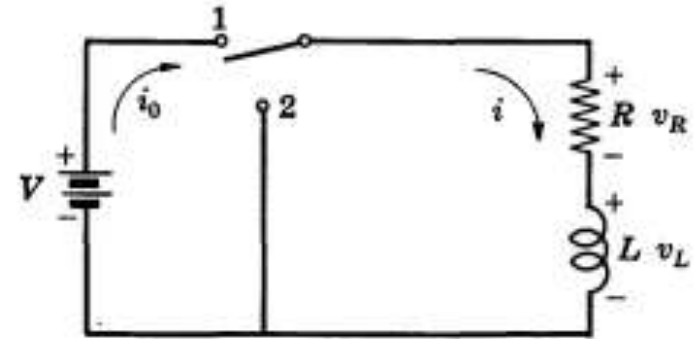

First-Order RC Transient (Step-Response)

- Assume the switch S is closed at $t = 0$
- Apply KVL to the series RC circuit shown:

$$\left[\frac{1}{C} \int i(t) \cdot dt + v_c(0) \right] + R \cdot i(t) = V$$

- Apply Laplace Transform on both sides

$$\left[\frac{I(s)}{Cs} + \frac{v_c(0)}{s} \right] + R \cdot I(s) = \frac{V}{s}$$

$V_c(0) = 0$ >> initial value of the voltage at $t = 0$


$$I(s) \cdot \left[R + \frac{1}{Cs} \right] = \frac{V}{s}$$

$$I(s) = \frac{V/s}{\left[R + \frac{1}{Cs} \right]} = \frac{V/R}{\left[s + \frac{1}{RC} \right]}$$

- Apply the inverse Laplace Transform technique to get the expression of the current $i(t)$

$$i(t) = \frac{V}{R} e^{-\frac{1}{RC}t}; t > 0$$

The same as last lecture

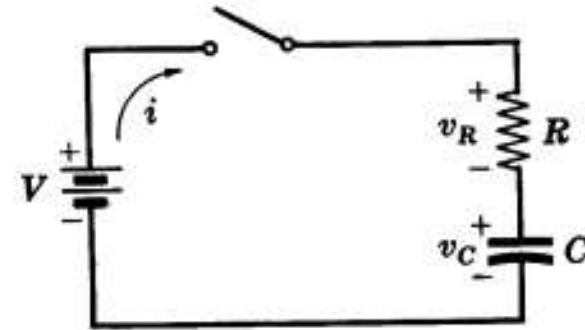

Second-Order RLC Transient (Step Response)

- The Switch "S" is closed at $t=0$
- Applying KVL will produce the following Integro-Differential equation:

$$\left[\frac{1}{C} \int i(t) \cdot dt + v_c(0) \right] + L \frac{di(t)}{dt} + R \cdot i(t) = V$$

- Apply Laplace Transform on both sides

$$\left[\frac{I(s)}{Cs} + \frac{v_c(0)}{s} \right] + L \cdot [s \cdot I(s) - i(0)] + R \cdot I(s) = \frac{V}{s}$$

$$I(s) = \frac{\frac{V}{s}}{\left[R + sL + \frac{1}{Cs} \right]} = \frac{\frac{V}{L}}{\left[s^2 + s \cdot \left(\frac{R}{L} \right) + \frac{1}{LC} \right]}$$


Assume:

$$v_c(0) = 0 \quad \& \quad i(0) = 0$$

- To convert this to time-domain, it will depend on the roots of the denominator which could be expressed as:

$(s-S_1) \cdot (s-S_2) \gggggg$ similar to last lecture $(m-m_1) \cdot (m-m_2)$
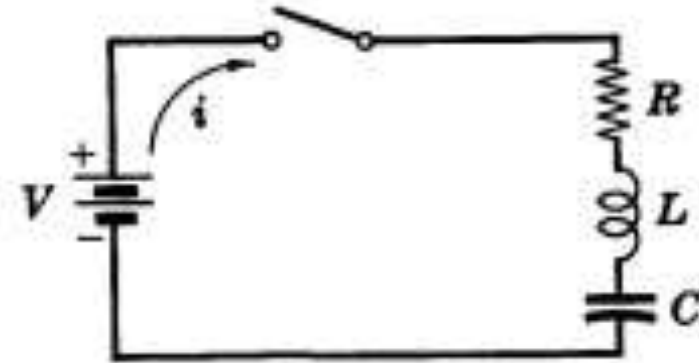
$$m^2 + \frac{R}{L}m + \frac{1}{LC} = 0$$



Second-Order RLC Transient (Step Response)

$$S_{1,2} = \frac{-R}{2L} \mp \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

ζ : exponential damping ratio

ω_0 : undamped natural frequency

$$S_{1,2} = -\zeta\omega_0 \mp \omega_0\sqrt{\zeta^2 - 1}$$

$$S_{1,2} = -\sigma \mp \sqrt{\sigma^2 - \omega_0^2}$$

➤ Apply Partial Fraction:

$$I(s) = \frac{V/L}{[s^2 + s.(R/L) + 1/LC]} = \frac{A}{s - S_1} + \frac{B}{s - S_2}$$

$$A = (s - S_1).I(s) \Big|_{s=S_1} = \frac{V}{2L.\omega_0\sqrt{\zeta^2 - 1}}$$

$$B = (s - S_2).I(s) \Big|_{s=S_2} = \frac{-V}{2L.\omega_0\sqrt{\zeta^2 - 1}} = -A$$

$$I(s) = \frac{V}{2L.\omega_0\sqrt{\zeta^2 - 1}} \cdot \left[\frac{1}{s - S_1} - \frac{1}{s - S_2} \right]$$



Second-Order RLC Transient (Step Response)

➤ Apply Partial According to the values of the roots , we have 3 scenarios:

1. Over-damped Case

i.e. Two real distinct roots

$$i(t) = \frac{V}{2L\omega_o \sqrt{\zeta^2 - 1}} \cdot [e^{s_1 t} - e^{s_2 t}]$$

2. Critically-damped Case

i.e. Two real equal roots $\sigma = \omega_o$

$$s_1 = s_2 = -\sigma = \frac{-R}{2L}$$

$$I(s) = \frac{V/L}{[s^2 + s \cdot (R/L) + 1/LC]} = \frac{V/L}{(S - s_1)^2} = \frac{V/L}{(S + \sigma)^2} = \frac{V/L}{(S + \omega_o)^2}$$

Convert by inverse L.T:

$$\frac{1}{(S + a)^n} \Leftrightarrow \frac{t^{n-1}}{(n-1)!} \cdot e^{-at}$$

$$i(t) = \frac{V}{L} \cdot t \cdot e^{s_1 t} = \frac{V}{L} \cdot t \cdot e^{-\omega_o t}$$



Second-Order RLC Transient (Step Response)

3. Under-damped Case

i.e. Two Complex-conjugate roots


$$s_{1,2} = -\sigma \mp \sqrt{\sigma^2 - \omega_0^2} = -\sigma \mp j\omega_d$$

$$i(t) = e^{\sigma \cdot t} [A_1 \cos(\omega_d t) + A_2 \sin(\omega_d t)]$$

$$\dots = Ae^{\sigma \cdot t} \left[\frac{A_1}{A} \cos(\omega_d t) + \frac{A_2}{A} \sin(\omega_d t) \right]$$

$$\dots = Ae^{\sigma \cdot t} [\sin \psi \cdot \cos(\omega_d t) + \cos \psi \cdot \sin(\omega_d t)]$$
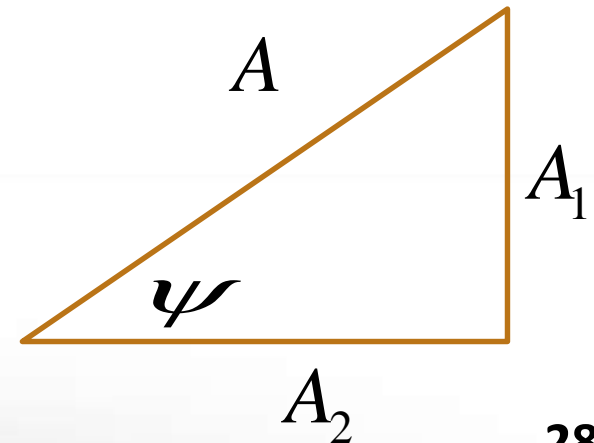
$$\dots = Ae^{\sigma \cdot t} \sin(\omega_d t + \psi)$$



RL Sinusoidal Transient

$R = 5 \text{ ohms}$, $L = 0.01 \text{ H}$, $V_m = 100 \text{ volts}$, $\phi = 0$, $\omega = 500$

$$Ri + L \frac{di}{dt} = V_{\max} \sin(\omega t + \phi)$$

➤ Apply Laplace Transform on both sides

$$R.I(s) + L[s.I(s) - i(0)] = 100 \frac{\omega}{s^2 + \omega^2}$$

$i(0) = 0$ >> initial value of the current at $t = 0$


$$I(s) \cdot \left[L \left(s + \frac{R}{L} \right) \right] = 100 \frac{\omega}{s^2 + \omega^2}$$

$$I(s) = \frac{100 \cdot \omega}{L \cdot (s^2 + \omega^2) \cdot \left(s + \frac{R}{L} \right)} = \frac{5 \times 10^6}{(s^2 + \omega^2) \cdot (s + 500)}$$

$$S_1 = -500$$

$$S_2 = -j\omega$$

$$S_3 = j\omega$$

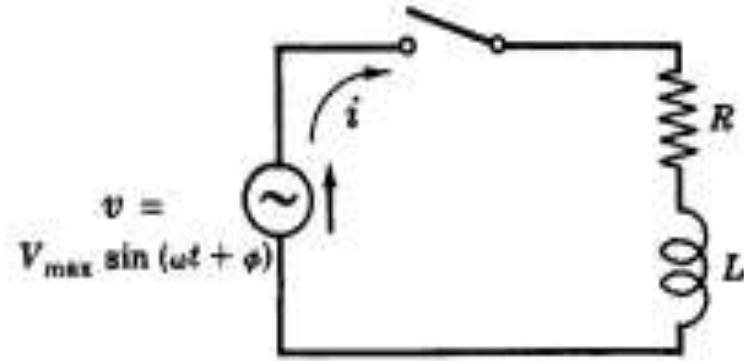

RL Sinusoidal Transient

➤ Use Partial Fraction:

$$I(s) = \frac{5 \times 10^6}{(s^2 + \omega^2) \cdot (s + 500)} = \frac{A_1}{s - j\omega} + \frac{A_2}{s + j\omega} + \frac{A_3}{s + 500}$$

OR

$$= \frac{B_1 s + B_2}{s^2 + \omega^2} + \frac{A_3}{s + 500}$$

Compare to find the constants:


$$I(s) = \frac{10[-s + 500]}{s^2 + \omega^2} + \frac{10}{s + 500} = 10 \cdot \frac{500}{s^2 + 500^2} - 10 \cdot \frac{s}{s^2 + 500^2} + \frac{10}{s + 500}$$

➤ Use Inverse L.T. $i(t) = 10 \cdot \sin(500t) - 10 \cdot \cos(500t) + 10 \cdot e^{-500t}$

$$i(t) = 10 \cdot [\sin(500t) - \cos(500t)] + 10 \cdot e^{-500t}$$

$$A = \sqrt{1^2 + (-1)^2} = \sqrt{2}$$
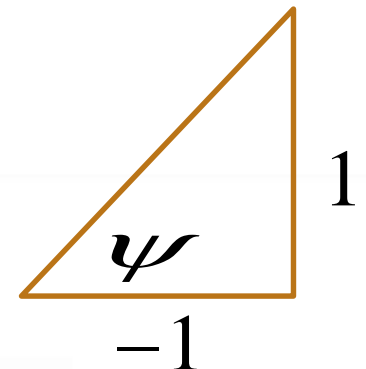
$$\psi = \tan^{-1} \left(\frac{1}{-1} \right) = 45^\circ$$





$$i(t) = 10 \cdot \sqrt{2} \cdot \sin(500t - 45^\circ) + 10 \cdot e^{-500t} = I_{s.s} + I_{tr}$$



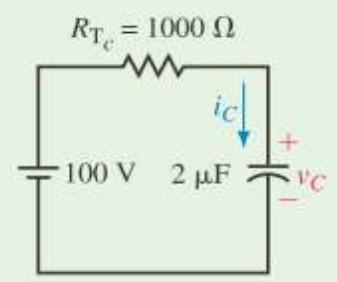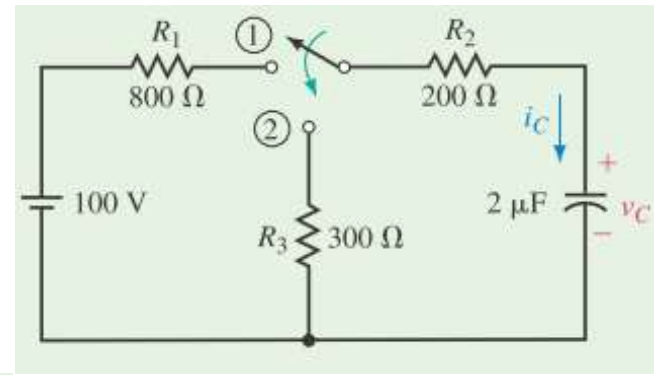Examples

The capacitor of Figure 11–24(a) is uncharged. The switch is moved to position 1 for 10 ms, then to position 2, where it remains.




$R_{T_c} = 1000 \Omega$

$\tau_c = (R_1 + R_2)C = (1 \text{ k}\Omega)(2 \mu\text{F}) = 2.0 \text{ ms.}$

a. $v_C = E(1 - e^{-t/\tau_c}) = 100(1 - e^{-500t}) \text{ V}$

b. $i_C = \frac{E}{R_{T_c}} e^{-t/\tau_c} = \frac{100}{1000} e^{-500t} = 100e^{-500t} \text{ mA}$

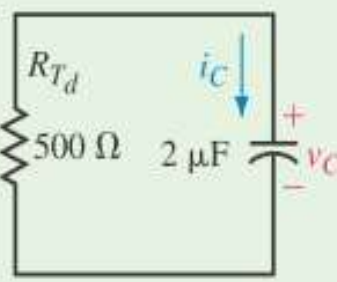(b) Charging circuit
 $R_{T_c} = R_1 + R_2$





R_{T_d}

$\tau_d = (500 \Omega)(2 \mu\text{F}) = 1.0 \text{ ms}$

$v_C = V_0 e^{-t/\tau_d} = 100e^{-1000t} \text{ V}$

$i_C = -\frac{V_0}{R_2 + R_3} e^{-t/\tau_d} = -\frac{100}{500} e^{-1000t} = -200e^{-1000t} \text{ mA}$

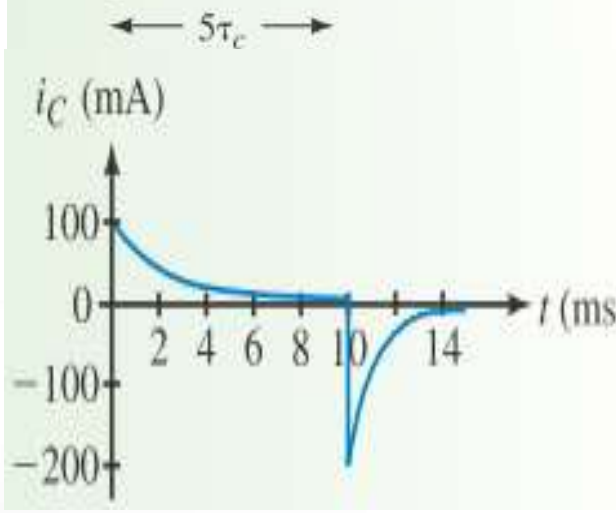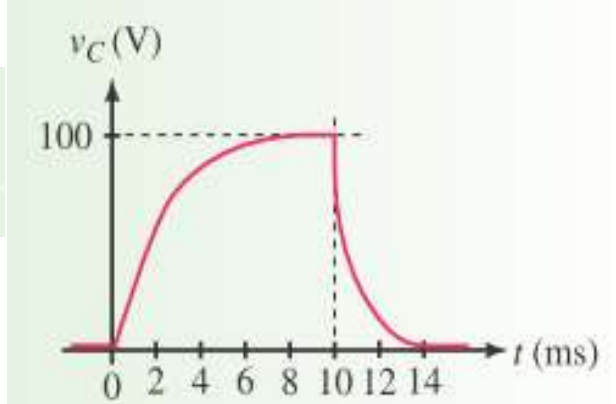(c) Discharging circuit
 $V_0 = 100 \text{ V at } t = 0 \text{ s}$



Note that discharge is more rapid than charge since $\tau_d < \tau_c$.

Check EXAMPLE 11–12 ,13 Miller