



BENHA UNIVERSITY  
FACULTY OF ENGINEERING AT SHOUBRA

**ECE-312**

**Electronic Circuits (A)**

Lecture #2

BJT Review

**Instructor:**

**Dr. Ahmad El-Banna**



OCTOBER 2014


© Ahmad El-Banna

# Agenda


- 1 Transistor Construction & Operation
- 2 Transistor Configurations
- 3 Transistor Testing & Terminal Identification

# Transistor Construction


- Basic BJT Constructions

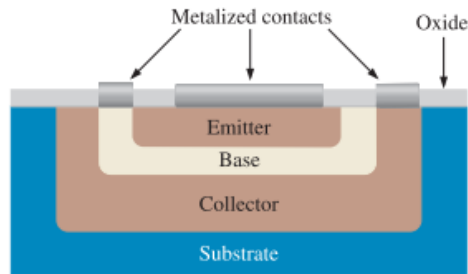

(a) Basic epitaxial planar structure

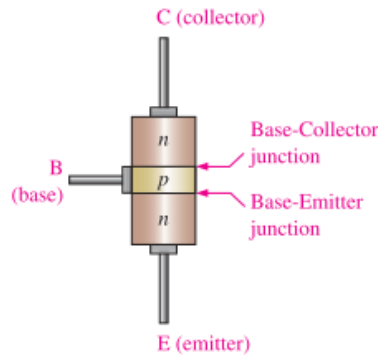


(b) npn

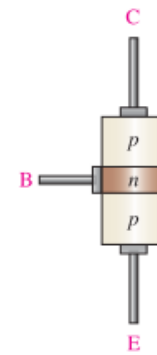


(c) pnp

- Basic BJT symbols and Currents

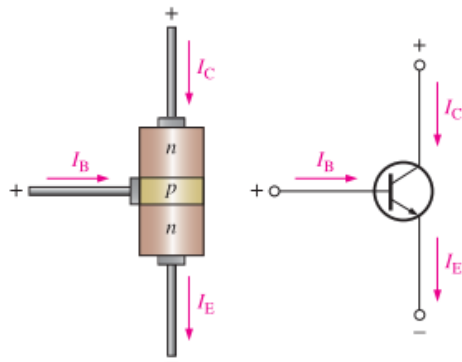

(a) npn

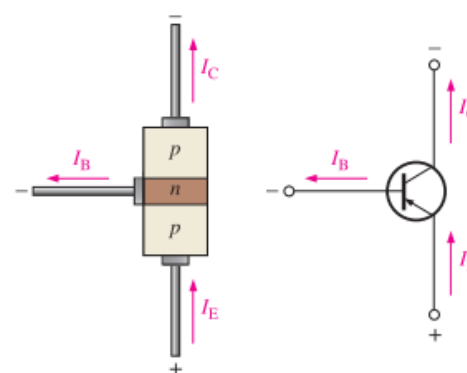


(b) pnp

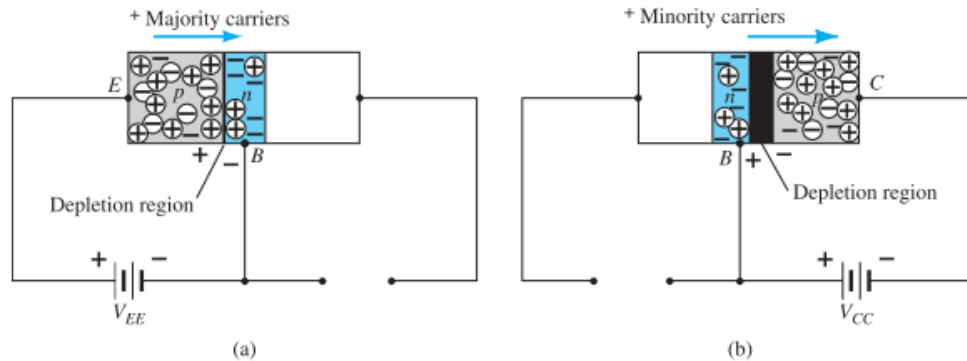
# Transistor Operation

- Basic Operation using *pn*p transistor.

- Biasing a transistor:
  - (a) forward-bias
  - (b) reverse-bias.



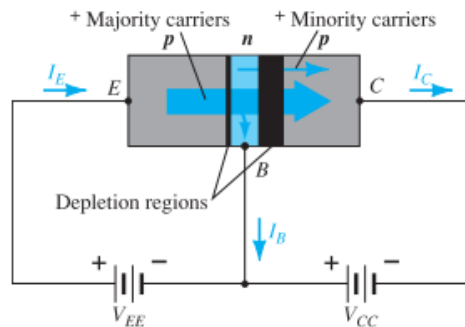- Majority and minority carrier flow of a *pn*p transistor.



$$I_E = I_C + I_B$$

$$I_C = I_{C_{\text{majority}}} + I_{C_{\text{minority}}}$$


- Common Base
- Common Emitter
- Common Collector

# BJT CONFIGURATIONS




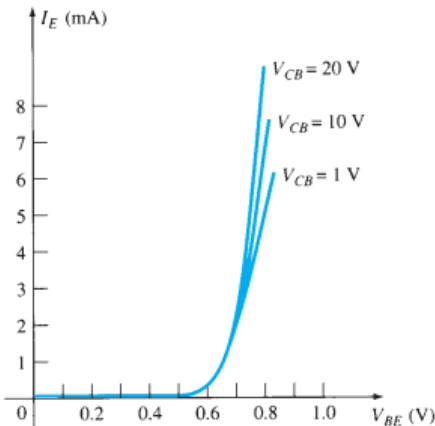
# Configurations: Common Base

- Notation and symbols used with the common-base configuration: (a) pnp transistor; (b) npn transistor.



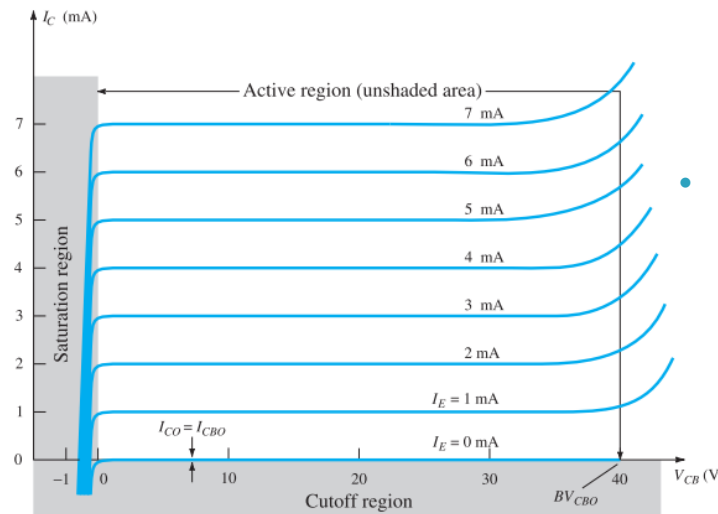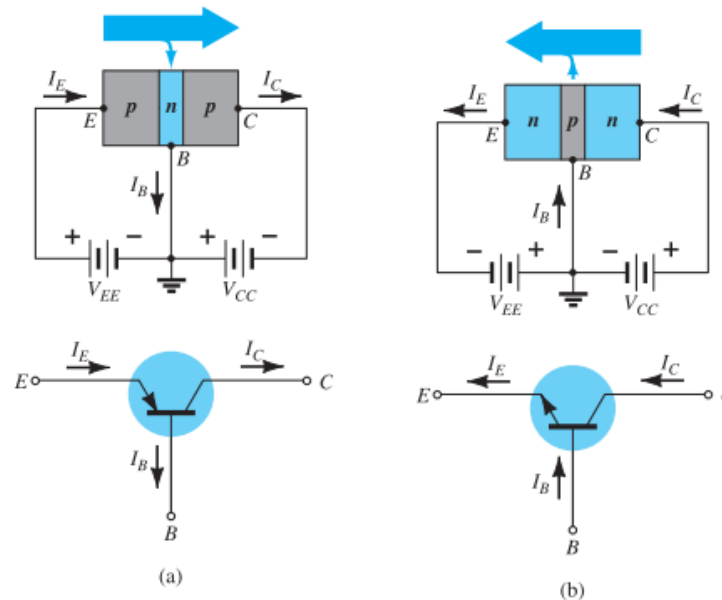- Input or driving point characteristics for a common-base silicon transistor amplifier.



- Output or collector characteristics for a common-base transistor amplifier.

# Configurations: Common Base..

- Formulas:

$$I_C \cong I_E$$


$$\alpha_{dc} = \frac{I_C}{I_E}$$

$$\alpha_{ac} = \frac{\Delta I_C}{\Delta I_E} \Big|_{V_{CB}=\text{constant}}$$

$$V_{BE} \cong 0.7 \text{ V}$$





$$I_C = \alpha I_E + I_{CBO}$$

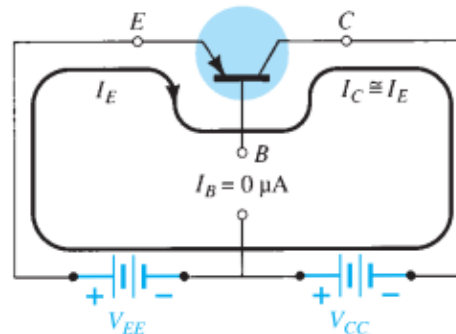- Biasing of a CB pnp tr. in the active region:




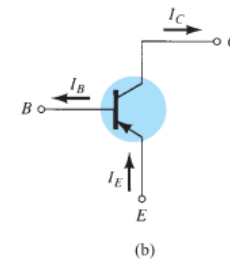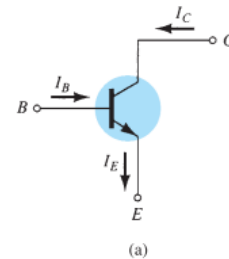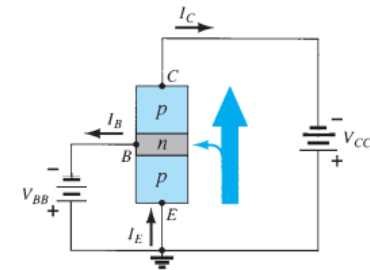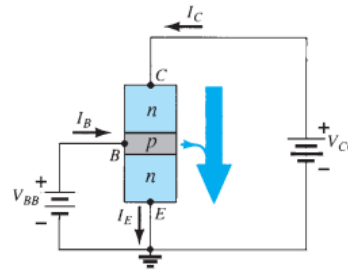
# Configurations: Common Emitter

- Notation and symbols used with the common-emitter configuration:
  - (a) pnp transistor
  - (b) npn transistor.



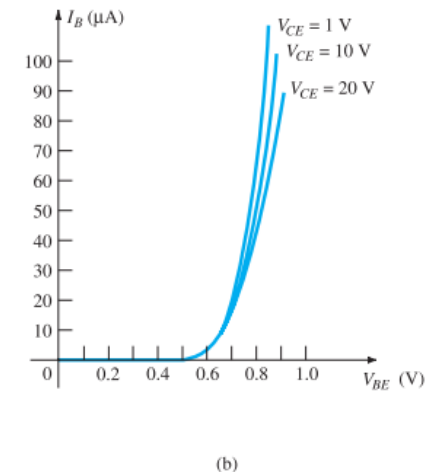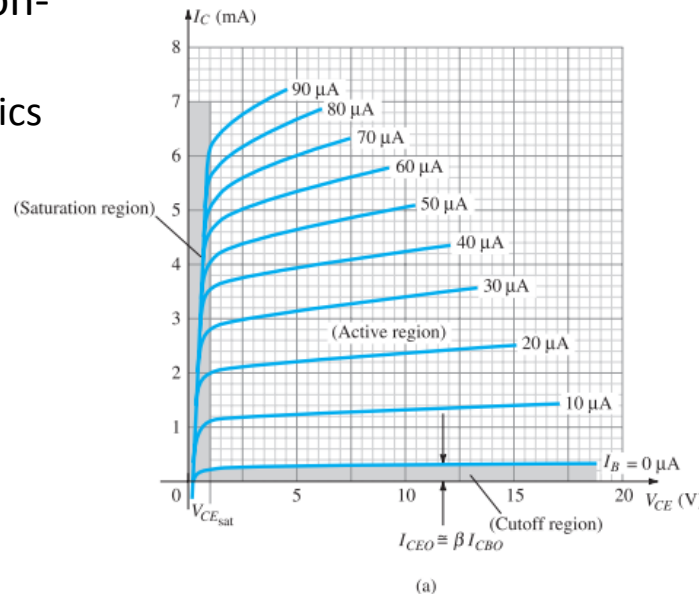- Characteristics of a silicon transistor in the common-emitter configuration:
  - (a) collector characteristics
  - (b) base characteristics.





# Configurations: Common Emitter..

- Formulas:

$$\beta_{dc} = \frac{I_C}{I_B}$$

$$\alpha = \frac{\beta}{\beta + 1}$$

$$I_{CEO} \cong \beta I_{CBO}$$


$$\beta_{ac} = \left. \frac{\Delta I_C}{\Delta I_B} \right|_{V_{CE}=\text{constant}}$$

$$\beta = \frac{\alpha}{1 - \alpha}$$

$$I_C = \beta I_B$$





$$I_E = (\beta + 1)I_B$$

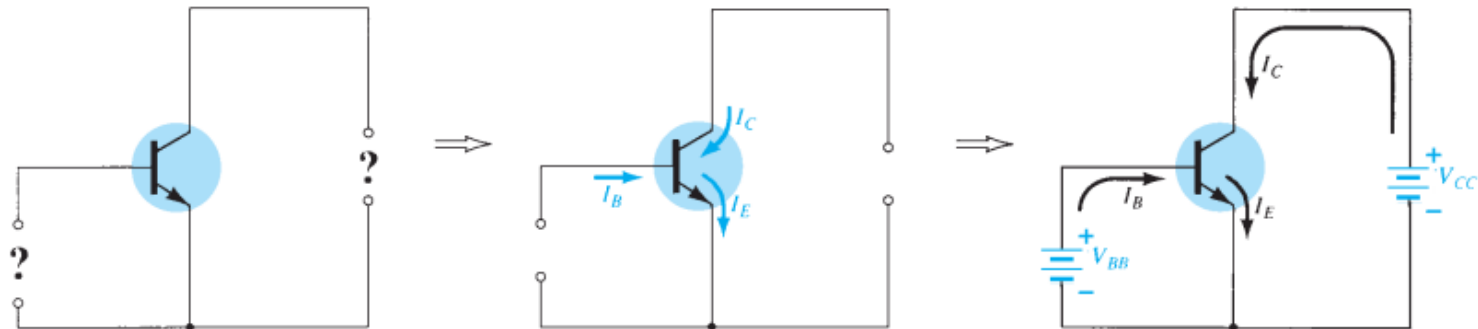- Biasing of a CE npn tr. in the active region:



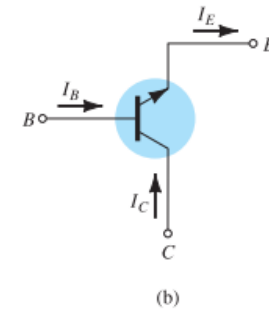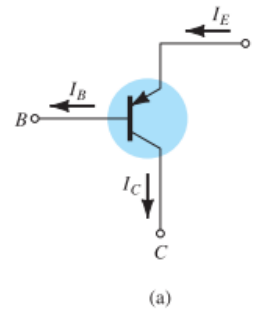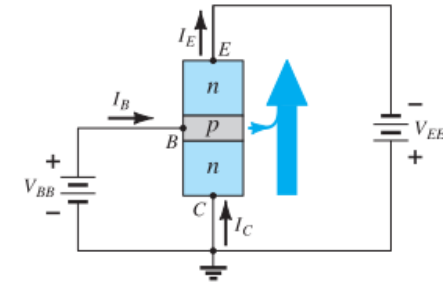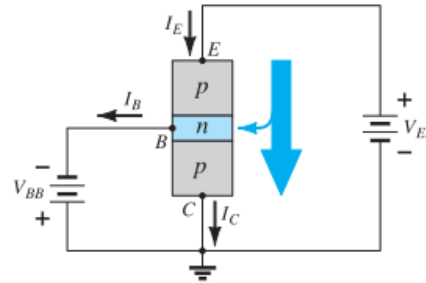
# Configurations: Common Collector

- Notation and symbols used with the common-collector configuration: (a) pnp transistor; (b) npn transistor.



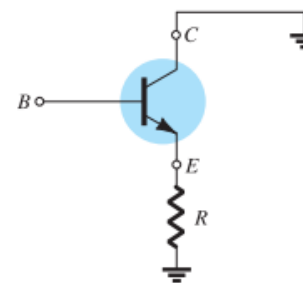- Common-collector configuration used for impedance-matching purposes.



# Configurations: Common Collector..

- Formulas:


$$P_{C_{\max}} = V_{CE} I_C$$

$$I_{CEO} \cong I_C \cong I_{C_{\max}}$$

$$V_{CE_{\text{sat}}} \cong V_{CE} \cong V_{CE_{\max}}$$

$$V_{CE} I_C \cong P_{C_{\max}}$$

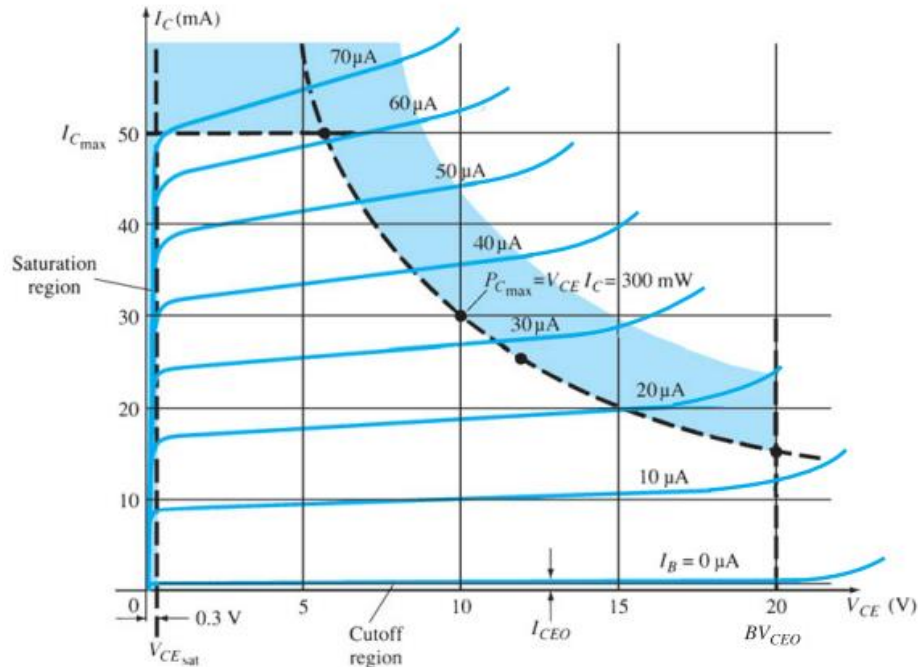- Defining the linear (undistorted) region of operation for a transistor.



- Transistor Spec. Sheets
- Transistor Testing
- Transistor Casing and terminals identification
- Transistor Development

## PRACTICAL VIEW



# Transistor Specification Sheets

## MAXIMUM RATINGS

Rating	Symbol	2N4123	Unit
Collector-Emitter Voltage	$V_{CEO}$	30	Vdc
Collector-Base Voltage	$V_{CBO}$	40	Vdc
Emitter-Base Voltage	$V_{EBO}$	5.0	Vdc
Collector Current – Continuous	$I_C$	200	mA <sub>dc</sub>
Total Device Dissipation @ $T_A = 25^\circ\text{C}$ Derate above $25^\circ\text{C}$	$P_D$	625 5.0	mW mW $^\circ\text{C}$
Operating and Storage Junction Temperature Range	$T_j, T_{stg}$	-55 to +150	$^\circ\text{C}$

## THERMAL CHARACTERISTICS

Characteristic	Symbol	Max	Unit
Thermal Resistance, Junction to Case	$R_{\theta JC}$	83.3	$^\circ\text{C/W}$
Thermal Resistance, Junction to Ambient	$R_{\theta JA}$	200	$^\circ\text{C/W}$

## ELECTRICAL CHARACTERISTICS ( $T_A = 25^\circ\text{C}$ unless otherwise noted)

Characteristic	Symbol	Min	Max	Unit
----------------	--------	-----	-----	------

## OFF CHARACTERISTICS

Collector-Emitter Breakdown Voltage (1) ( $I_C = 1.0 \text{ mA}_{dc}, I_E = 0$ )	$V_{(BR)CEO}$	30		Vdc
Collector-Base Breakdown Voltage ( $I_C = 10 \mu\text{A}_{dc}, I_E = 0$ )	$V_{(BR)CBO}$	40		Vdc
Emitter-Base Breakdown Voltage ( $I_E = 10 \mu\text{A}_{dc}, I_C = 0$ )	$V_{(BR)EBO}$	5.0	-	Vdc
Collector Cutoff Current ( $V_{CB} = 20 \text{ Vdc}, I_E = 0$ )	$I_{CBO}$	-	50	nA <sub>dc</sub>
Emitter Cutoff Current ( $V_{BE} = 3.0 \text{ Vdc}, I_C = 0$ )	$I_{EBO}$	-	50	nA <sub>dc</sub>

## ON CHARACTERISTICS

DC Current Gain(1) ( $I_C = 2.0 \text{ mA}_{dc}, V_{CE} = 1.0 \text{ Vdc}$ ) ( $I_C = 50 \text{ mA}_{dc}, V_{CE} = 1.0 \text{ Vdc}$ )	$h_{FE}$	50 25	150 -	-
Collector-Emitter Saturation Voltage(1) ( $I_C = 50 \text{ mA}_{dc}, I_B = 5.0 \text{ mA}_{dc}$ )	$V_{CE(sat)}$	-	0.3	Vdc
Base-Emitter Saturation Voltage(1) ( $I_C = 50 \text{ mA}_{dc}, I_B = 5.0 \text{ mA}_{dc}$ )	$V_{BE(sat)}$	-	0.95	Vdc

## SMALL-SIGNAL CHARACTERISTICS

Current-Gain – Bandwidth Product ( $I_C = 10 \text{ mA}_{dc}, V_{CE} = 20 \text{ Vdc}, f = 100 \text{ MHz}$ )	$f_T$	250		MHz
Output Capacitance ( $V_{CB} = 5.0 \text{ Vdc}, I_E = 0, f = 100 \text{ MHz}$ )	$C_{obo}$	-	4.0	pF
Input Capacitance ( $V_{BE} = 0.5 \text{ Vdc}, I_C = 0, f = 100 \text{ kHz}$ )	$C_{ibo}$	-	8.0	pF
Collector-Base Capacitance ( $I_E = 0, V_{CB} = 5.0 \text{ V}, f = 100 \text{ kHz}$ )	$C_{cb}$	-	4.0	pF
Small-Signal Current Gain ( $I_C = 2.0 \text{ mA}_{dc}, V_{CE} = 10 \text{ Vdc}, f = 1.0 \text{ kHz}$ )	$h_{fe}$	50	200	-
Current Gain – High Frequency ( $I_C = 10 \text{ mA}_{dc}, V_{CE} = 20 \text{ Vdc}, f = 100 \text{ MHz}$ ) ( $I_C = 2.0 \text{ mA}_{dc}, V_{CE} = 10 \text{ V}, f = 1.0 \text{ kHz}$ )	$h_{fe}$	2.5 50	- 200	-
Noise Figure ( $I_C = 100 \mu\text{A}_{dc}, V_{CE} = 5.0 \text{ Vdc}, R_S = 1.0 \text{ k ohm}, f = 1.0 \text{ kHz}$ )	NF	-	6.0	dB

(1) Pulse Test: Pulse Width = 300  $\mu\text{s}$ , Duty Cycle = 2.0%



# Transistor Specification Sheets..

**h PARAMETERS**  
 $V_{CE} = 10 \text{ V}, f = 1 \text{ kHz}, T_A = 25^\circ\text{C}$

Figure 1 – Current Gain


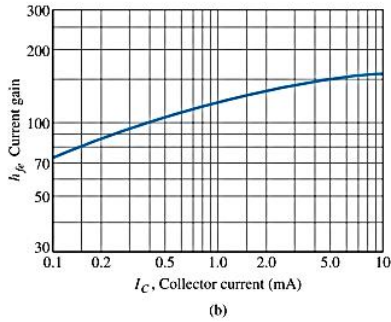


Figure 3 – Capacitance

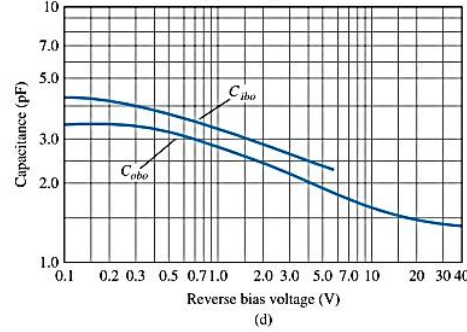

## STATIC CHARACTERISTICS

Figure 2 – DC Current Gain

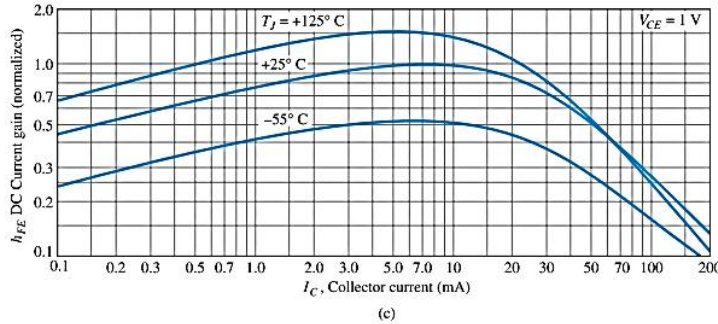


Figure 6 – Source Resistance


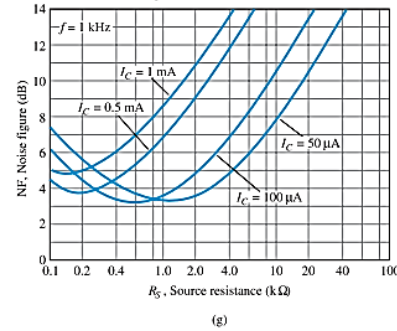


Figure 7 – Input Impedance

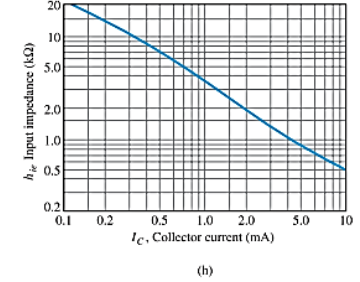

## AUDIO SMALL SIGNAL CHARACTERISTICS

### NOISE FIGURE

$(V_{CE} = 5 \text{ Vdc}, T_A = 25^\circ\text{C})$   
 Bandwidth = 1.0 Hz

Figure 8 – Voltage Feedback Ratio

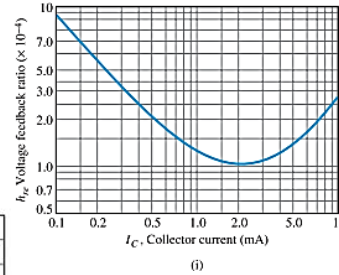


Figure 9 – Output Admittance

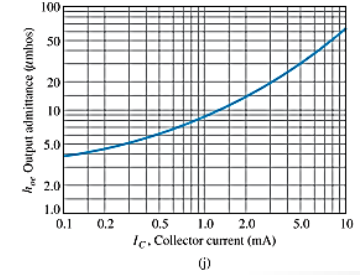


Figure 4 – Switching Times



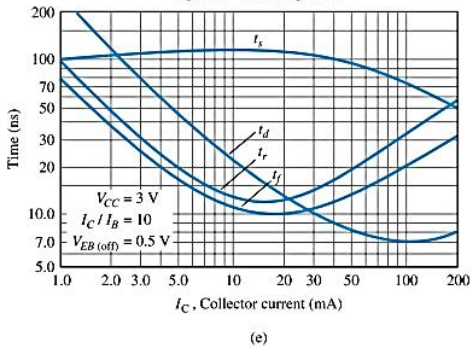



Figure 5 – Frequency Variations

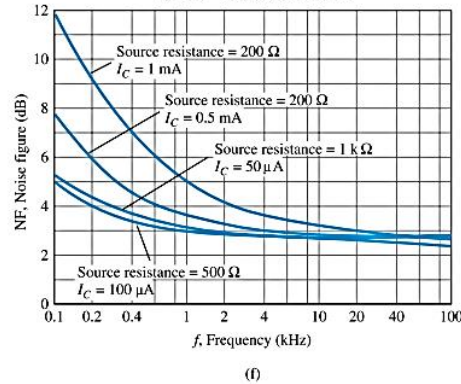

# Transistor Testing using Curve Tracer

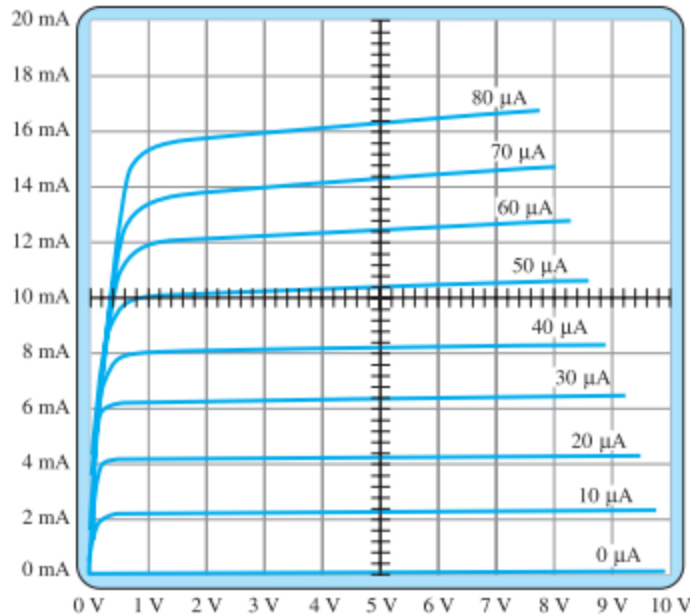

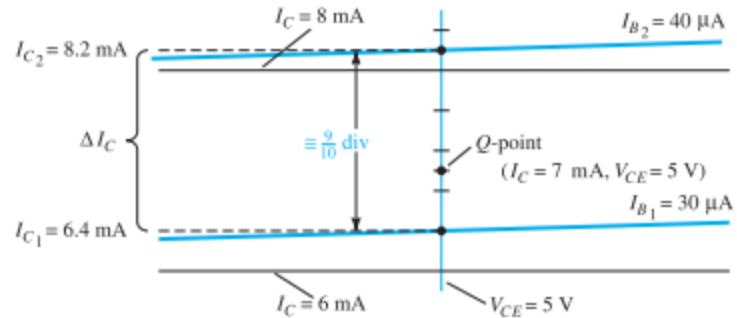- Vertical per div 2 mA
- Horizontal per div 1 V
- Per Step 10 μA
- $\beta$  or gm per div 200



Determining  $\beta_{ac}$  for the transistor characteristics of 2N3904 npn transistor at  $I_C = 7 \text{ mA}$  and  $V_{CE} = 5 \text{ V}$ .

$$\beta_{ac} = \frac{9}{10} \text{ div} \left( \frac{200}{\text{div}} \right) = 180$$



- Check the beta value:

$$\beta_{ac} = \frac{\Delta I_C}{\Delta I_B} \Big|_{V_{CE}=\text{constant}}$$

$$\begin{aligned} \beta_{ac} &= \frac{\Delta I_C}{\Delta I_B} \Big|_{V_{CE}=\text{constant}} = \frac{I_{C_2} - I_{C_1}}{I_{B_2} - I_{B_1}} = \frac{8.2 \text{ mA} - 6.4 \text{ mA}}{40 \mu\text{A} - 30 \mu\text{A}} \\ &= \frac{1.8 \text{ mA}}{10 \mu\text{A}} = 180 \end{aligned}$$
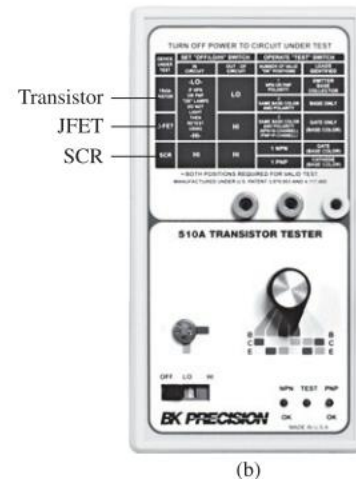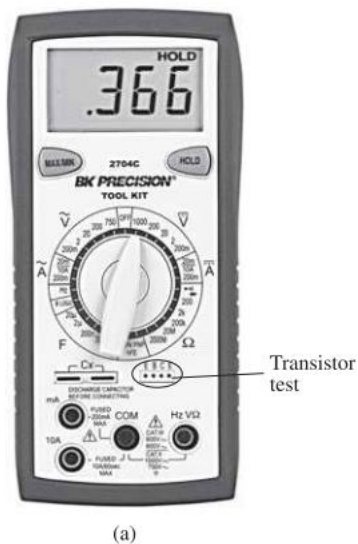
# Transistor Testing using Transistor Tester


- Transistor testers:
  - (a) digital meter
  - (b) dedicated testers.





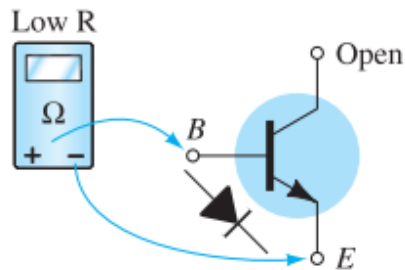
# Transistor Testing using Ohmmeter

- Checking the forward-biased base-to-emitter junction of an *npn* transistor.



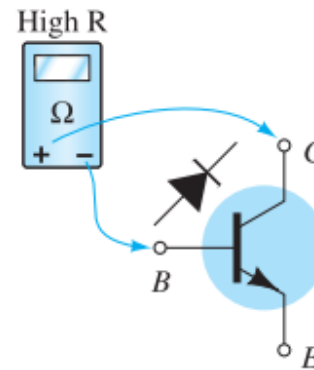- Checking the reverse-biased base-to-collector junction of an *npn* transistor.




# Transistor Casing

- Various types of general-purpose or switching transistors:
  - (a) low power
  - (b) medium power
  - (c) medium to high power.



(a)

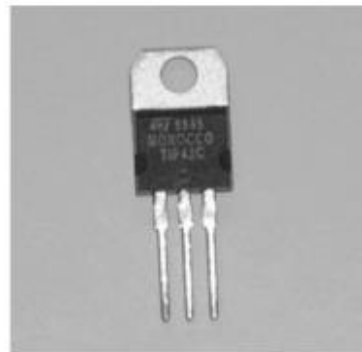


(b)




(c)

# Terminal Identification

- Transistor terminal identification.

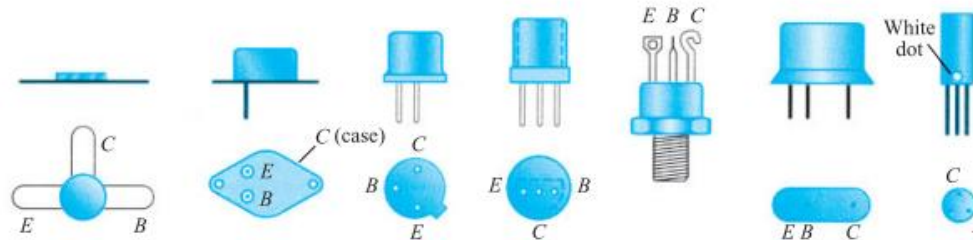

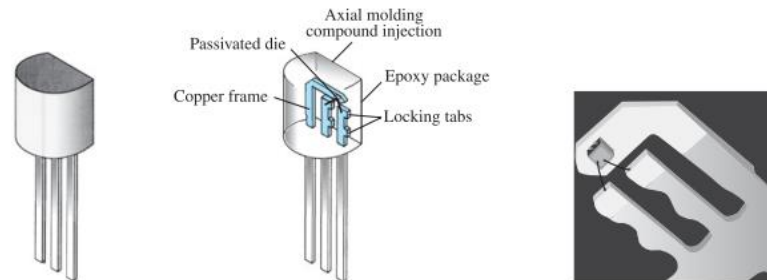- Internal construction of a Fairchild transistor in a TO-92 package.




- Type Q2T2905 Texas Instruments quad pnp silicon transistor:

- Appearance
- pin connections.




(a)

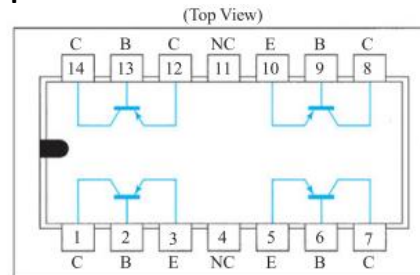

(b)
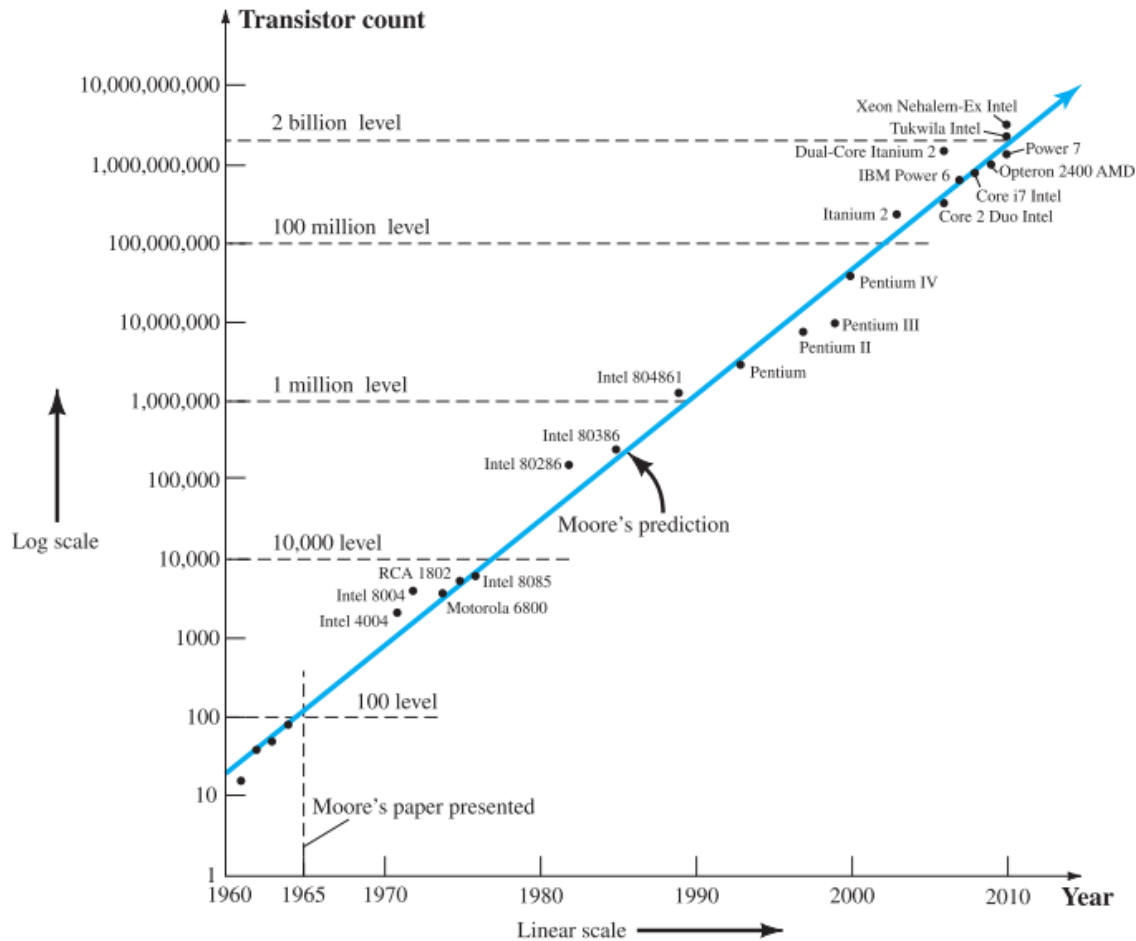
# Transistor Development

- Transistor IC count versus time for the period 1960 to the present



- For more details, refer to:
  - Chapter 3 at R. Boylestad, **Electronic Devices and Circuit Theory**, 11<sup>th</sup> edition, Prentice Hall.
  - Text books for ECE-121.
- The lecture is available online at:
  - [https://speakerdeck.com/ahmad\\_elbanna](https://speakerdeck.com/ahmad_elbanna)
- For inquires, send to:
  - [ahmad.elbanna@fes.bu.edu.eg](mailto:ahmad.elbanna@fes.bu.edu.eg)
  - [ahmad.elbanna@ejust.edu.eg](mailto:ahmad.elbanna@ejust.edu.eg)