



BENHA UNIVERSITY
FACULTY OF ENGINEERING AT SHOUBRA

ECE-312
Electronic Circuits (A)

Lecture # 5
Hybrid Equivalent Model

Instructor:
Dr. Ahmad El-Banna



كلية الهندسة بشبرا

NOVEMBER 2014

© Ahmad El-Banna

Agenda

- Two-Port Systems Approach
- Cascaded Systems
- The Hybrid Equivalent Model
- Approximate & Complete h-model
- Hybrid π Model
- Troubleshooting and Practical Applications



TWO PORT SYSTEMS APPROACH



(3)

2-Port System

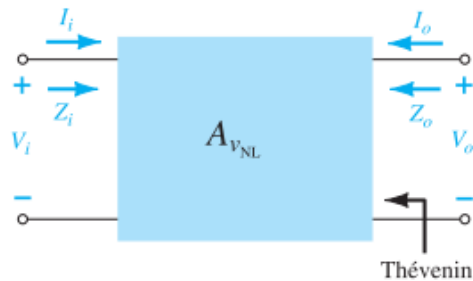


FIG. 5.61
Two-port system.

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$



where

$$z_{11} \stackrel{\text{def}}{=} \frac{V_1}{I_1} \bigg|_{I_2=0}$$

$$z_{12} \stackrel{\text{def}}{=} \frac{V_1}{I_2} \bigg|_{I_1=0}$$

$$z_{21} \stackrel{\text{def}}{=} \frac{V_2}{I_1} \bigg|_{I_2=0}$$

$$z_{22} \stackrel{\text{def}}{=} \frac{V_2}{I_2} \bigg|_{I_1=0}$$

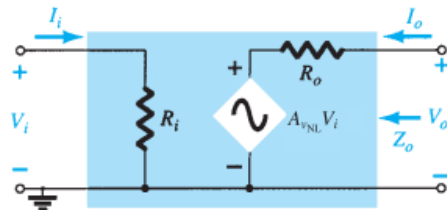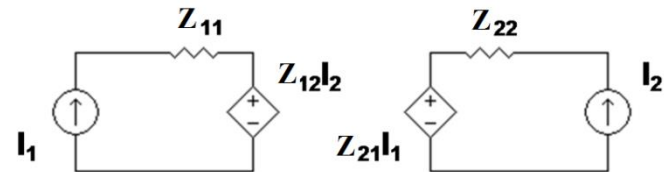


$$V_o = A_{VNL} V_i$$

$$Z_o = R_o$$

$$Z_i = R_i$$

FIG. 5.62

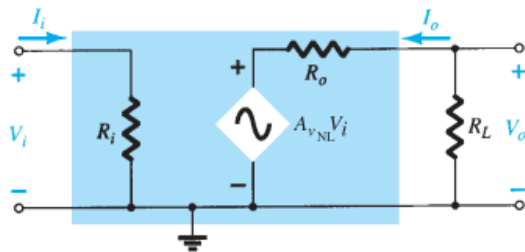Substituting the internal elements for the two-port system of Fig. 5.61.



$$V_o = \frac{R_L A_{VNL} V_i}{R_L + R_o}$$

$$A_{V_L} = \frac{V_o}{V_i} = \frac{R_L}{R_L + R_o} A_{VNL}$$

$$A_{i_L} = \frac{I_o}{I_i} = \frac{-V_o/R_L}{V_i/Z_i} = -\frac{V_o}{V_i} \frac{Z_i}{R_L}$$

$$A_{i_L} = -A_{V_L} \frac{Z_i}{R_L}$$

FIG. 5.63

Applying a load to the two-port system of Fig. 5.62.

2-Port System..

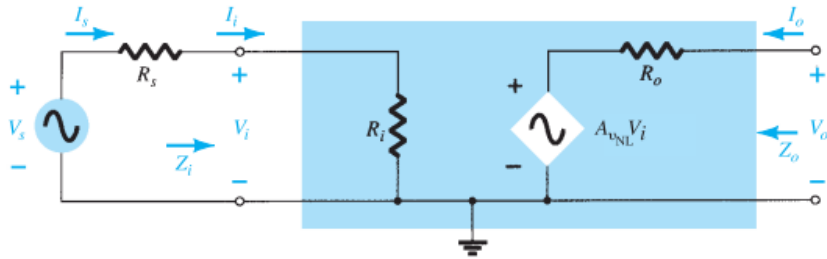


FIG. 5.64

Including the effects of the source resistance R_s .

$$V_i = \frac{R_i V_s}{R_i + R_s}$$

$$V_o = A_{vNL} V_i$$

$$V_o = A_{vNL} \frac{R_i}{R_i + R_s} V_s$$

$$A_{v_s} = \frac{V_o}{V_s} = \frac{R_i}{R_i + R_s} A_{vNL}$$

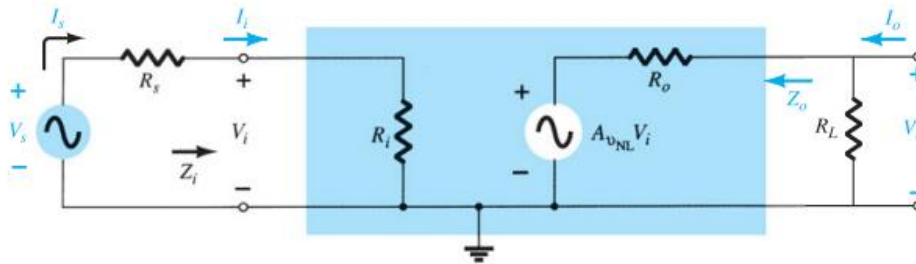


FIG. 5.65

Considering the effects of R_s and R_L on the gain of an amplifier.

$$\frac{V_i}{V_s} = \frac{R_i}{R_i + R_s}$$

$$V_o = \frac{R_L}{R_L + R_o} A_{vNL} V_i$$

$$A_{v_L} = \frac{V_o}{V_i} = \frac{R_L A_{vNL}}{R_L + R_o} = \frac{R_L}{R_L + R_o} A_{vNL}$$

$$A_{v_s} = \frac{V_o}{V_s} = \frac{V_o}{V_i} \cdot \frac{V_i}{V_s}$$

$$A_{v_s} = \frac{V_o}{V_s} = \frac{R_i}{R_i + R_s} \cdot \frac{R_L}{R_L + R_o} A_{vNL}$$

$$A_{i_L} = -A_{v_L} \frac{R_i}{R_L}$$

$$A_{i_s} = -A_{v_s} \frac{R_s + R_i}{R_L}$$




CASCADED SYSTEMS



(6)

Cascaded Systems


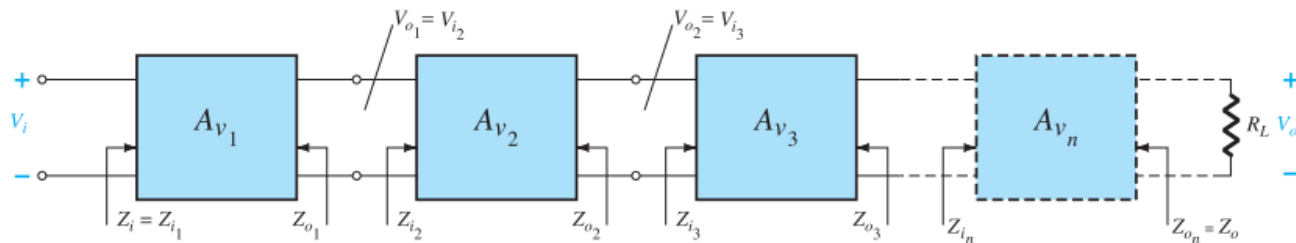


$$A_{vT} = A_{v1} \cdot A_{v2} \cdot A_{v3} \cdot \dots$$

$$A_{iT} = -A_{vT} \frac{Z_{i1}}{R_L}$$

FIG. 5.67
Cascaded system.

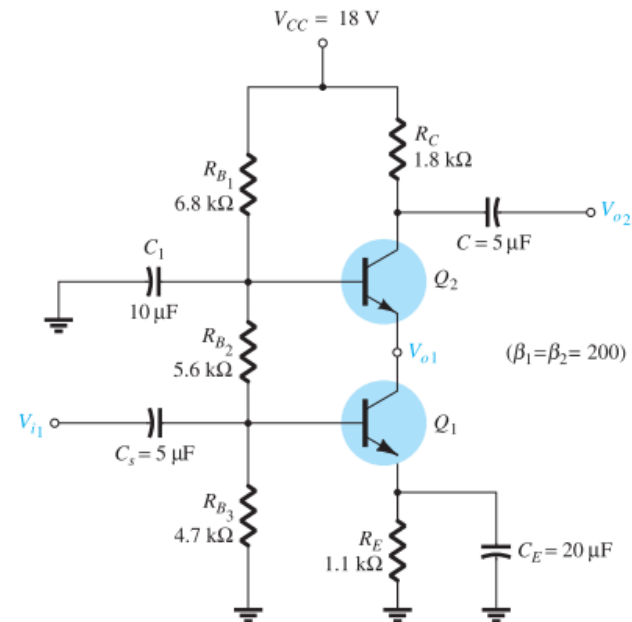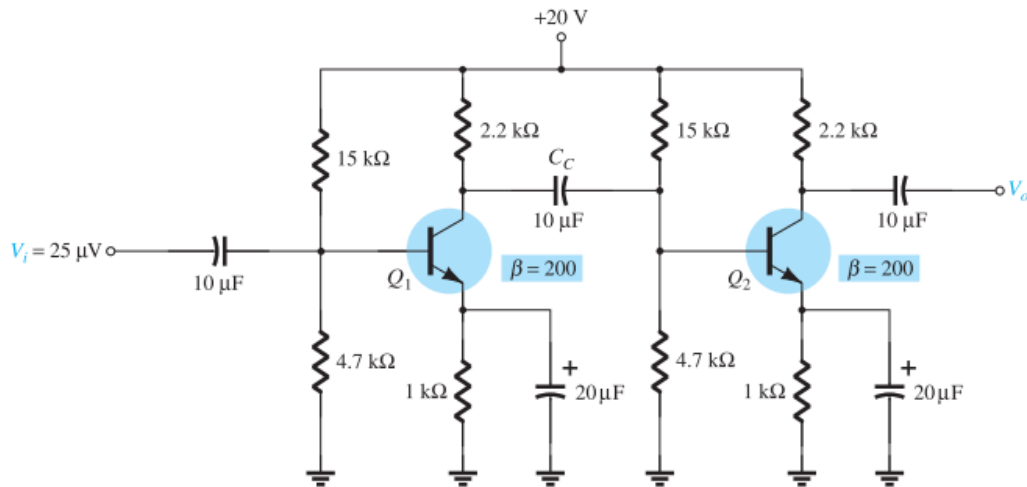- Examples: RC Coupled ct & Cascode ct
- Check Examples: 5.15 & 5.16



THE HYBRID EQUIVALENT MODEL



(8)

The Hybrid Equivalent Model

- The r_e model has the advantage that the parameters are defined by the actual operating conditions,
- the parameters of the hybrid equivalent circuit are defined in general terms for any operating conditions.

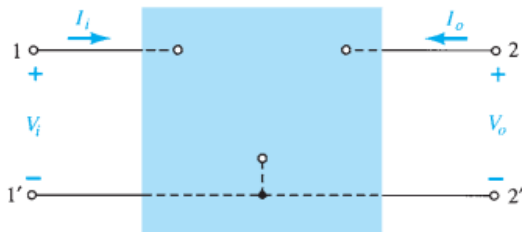


FIG. 5.93
Two-port system.

$$V_i = h_{11}I_i + h_{12}V_o$$

$$I_o = h_{21}I_i + h_{22}V_o$$

$$h_{11} = \left. \frac{V_i}{I_i} \right|_{V_o=0}$$

ohms



short-circuit input-impedance parameter

$$h_{12} = \left. \frac{V_i}{V_o} \right|_{I_i=0}$$

unitless



open-circuit reverse transfer voltage ratio parameter

$$h_{21} = \left. \frac{I_o}{I_i} \right|_{V_o=0}$$

unitless



short-circuit forward transfer current ratio parameter

$$h_{22} = \left. \frac{I_o}{V_o} \right|_{I_i=0}$$

siemens



short-circuit forward transfer current ratio parameter

		Min.	Max.	
Input impedance ($I_C = 1$ mA dc, $V_{CE} = 10$ V dc, $f = 1$ kHz)	h_{ie}	0.5	7.5	k Ω
Voltage feedback ratio ($I_C = 1$ mA dc, $V_{CE} = 10$ V dc, $f = 1$ kHz)	h_{re}	0.1	8.0	$\times 10^{-4}$
Small-signal current gain ($I_C = 1$ mA dc, $V_{CE} = 10$ V dc, $f = 1$ kHz)	h_{fe}	20	250	—
Output admittance ($I_C = 1$ mA dc, $V_{CE} = 10$ V dc, $f = 1$ kHz)	h_{oe}	1.0	30	μ S

FIG. 5.92

Hybrid parameters for the 2N4400 transistor.



Transistor Hybrid Equivalent ct

$$V_i = h_{11}I_i + h_{12}V_o$$

$$I_o = h_{21}I_i + h_{22}V_o$$

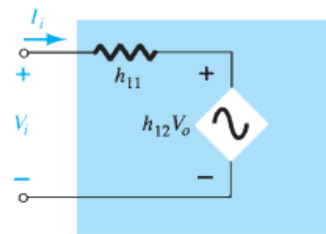


FIG. 5.94

Hybrid input equivalent circuit.

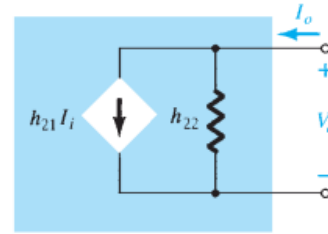


FIG. 5.95

Hybrid output equivalent circuit.

• For Transistor:

$h_{11} \rightarrow$ input resistance $\rightarrow h_i$

$h_{12} \rightarrow$ reverse transfer voltage ratio $\rightarrow h_r$

$h_{21} \rightarrow$ forward transfer current ratio $\rightarrow h_f$

$h_{22} \rightarrow$ output conductance $\rightarrow h_o$

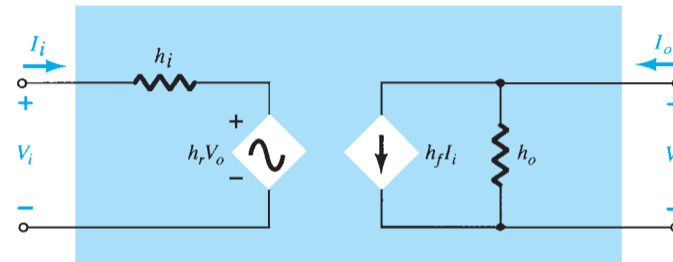


FIG. 5.96

Complete hybrid equivalent circuit.

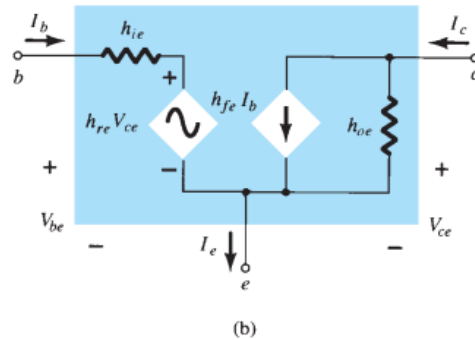
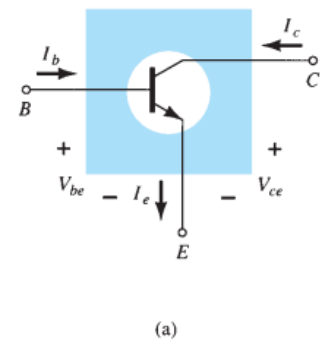


FIG. 5.97

Common-emitter configuration: (a) graphical symbol; (b) hybrid equivalent circuit.


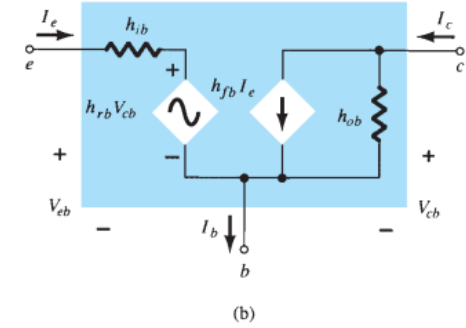


FIG. 5.98

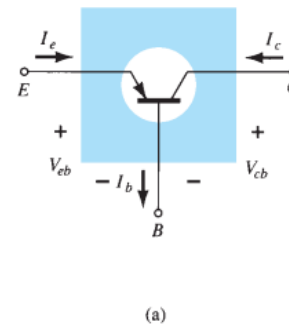Common-base configuration: (a) graphical symbol; (b) hybrid equivalent circuit.



Hybrid vs. r_e model

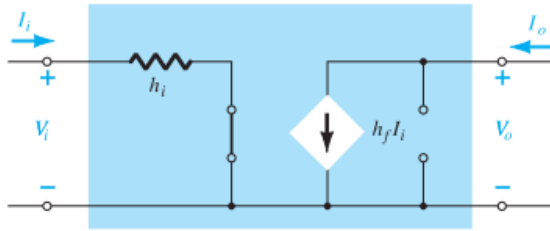


FIG. 5.99

Effect of removing h_{re} and h_{oe} from the hybrid equivalent circuit.

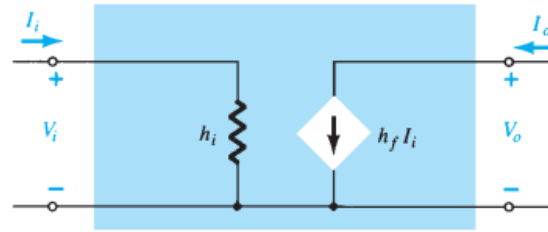


FIG. 5.100

Approximate hybrid equivalent model.

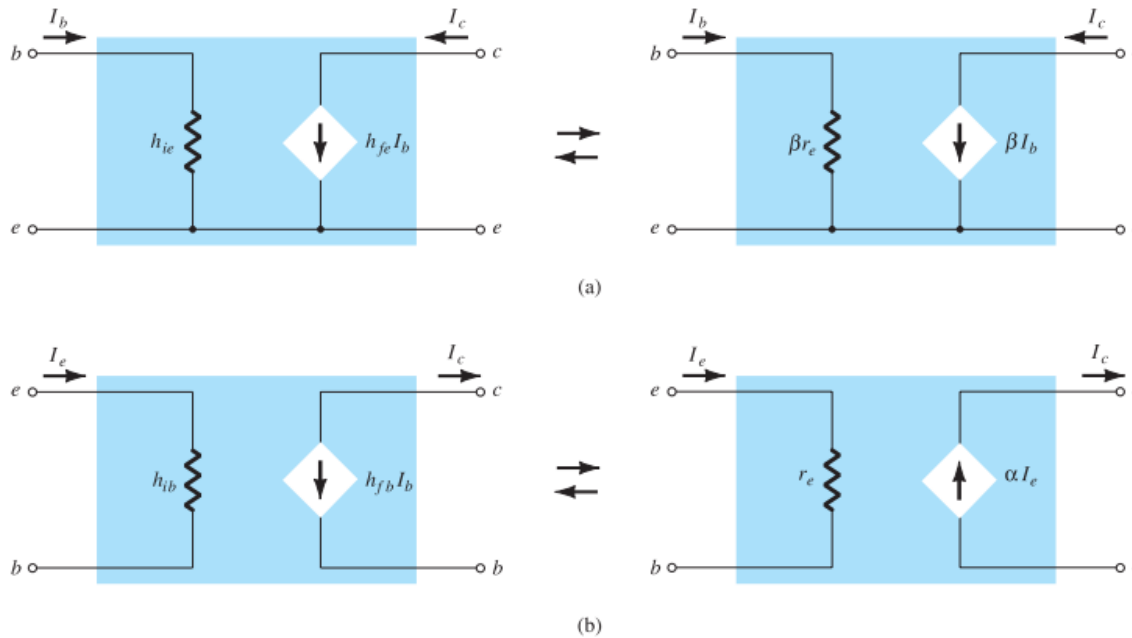


FIG. 5.101

Hybrid versus r_e model: (a) common-emitter configuration; (b) common-base configuration.

$$h_{ie} = \beta r_e$$

$$h_{fe} = \beta_{ac}$$

$$h_{ib} = r_e$$

$$h_{fb} = -\alpha \cong -1$$



APPROXIMATE & COMPLETE H-MODEL



Approximate h-model

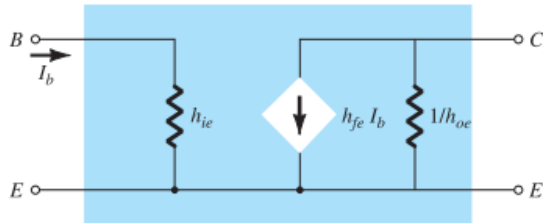


FIG. 5.104

Approximate common-emitter hybrid equivalent circuit.

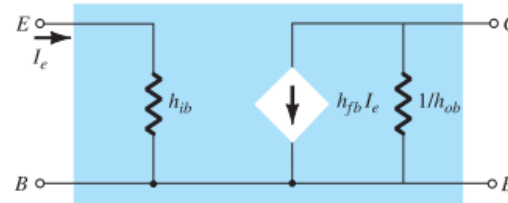


FIG. 5.105

Approximate common-base hybrid equivalent circuit.

- Fixed Bias ct

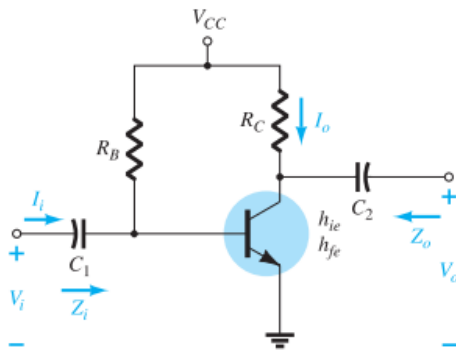


FIG. 5.106

Fixed-bias configuration.

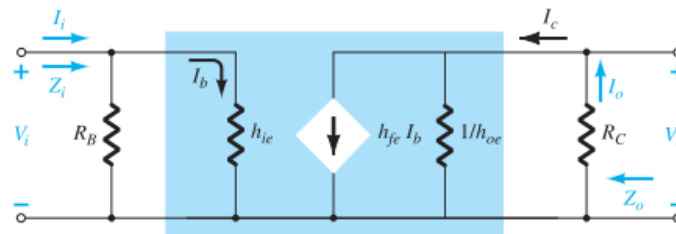


FIG. 5.107

Substituting the approximate hybrid equivalent circuit into the ac equivalent network of Fig. 5.106.

$$Z_i = R_B \parallel h_{ie}$$

$$Z_o = R_C \parallel 1/h_{oe}$$

$$R' = 1/h_{oe} \parallel R_C$$

$$V_o = -I_o R' = -I_C R'$$

$$= -h_{fe} I_b R'$$

$$I_b = \frac{V_i}{h_{ie}}$$

$$V_o = -h_{fe} \frac{V_i}{h_{ie}} R'$$


$$A_v = \frac{V_o}{V_i} = -\frac{h_{fe}(R_C \parallel 1/h_{oe})}{h_{ie}}$$

$$A_i = \frac{I_o}{I_i} \cong h_{fe}$$

- Check other configurations !!



Complete h-model

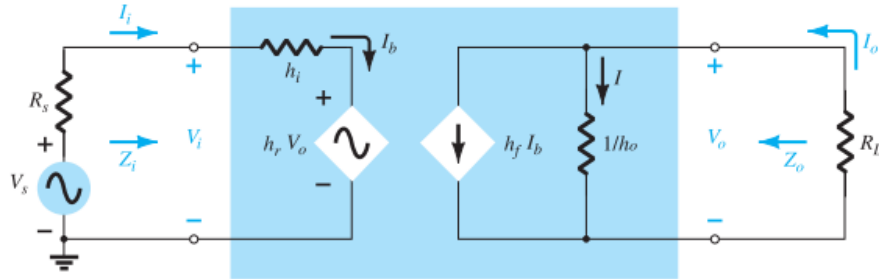

Current Gain, $A_i = I_o/I_i$

$$I_o = h_f I_b + I = h_f I_i + \frac{V_o}{1/h_o} = h_f I_i + h_o V_o$$

Substituting $V_o = -I_o R_L$ gives

$$I_o = h_f I_i - h_o R_L I_o$$

Rewriting the equation above, we have

$$I_o + h_o R_L I_o = h_f I_i$$

and

$$I_o(1 + h_o R_L) = h_f I_i$$

so that

$$A_i = \frac{I_o}{I_i} = \frac{h_f}{1 + h_o R_L}$$

Voltage Gain, $A_v = V_o/V_i$

$$V_i = I_i h_i + h_r V_o$$

$$I_i = (1 + h_o R_L) I_o / h_f$$

$$\text{and } I_o = -V_o / R_L$$

$$V_i = \frac{-(1 + h_o R_L) h_i}{h_f R_L} V_o + h_r V_o$$

$$A_v = \frac{V_o}{V_i} = \frac{-h_f R_L}{h_i + (h_i h_o - h_f h_r) R_L}$$

Input Impedance, $Z_i = V_i/I_i$

$$V_i = h_i I_i + h_r V_o$$

$$V_o = -I_o R_L$$

$$V_i = h_i I_i - h_r R_L I_o$$

$$A_i = \frac{I_o}{I_i}$$

$$I_o = A_i I_i$$

$$V_i = h_i I_i - h_r R_L A_i I_i$$

$$Z_i = \frac{V_i}{I_i} = h_i - h_r R_L A_i \quad A_i = \frac{h_f}{1 + h_o R_L}$$

$$Z_i = \frac{V_i}{I_i} = h_i - \frac{h_f h_r R_L}{1 + h_o R_L}$$

Output Impedance, $Z_o = V_o/I_o$

$$V_s = 0$$

$$I_i = -\frac{h_r V_o}{R_s + h_i}$$

$$I_o = h_f I_i + h_o V_o = -\frac{h_f h_r V_o}{R_s + h_i} + h_o V_o$$

$$Z_o = \frac{V_o}{I_o} = \frac{1}{h_o - [h_f h_r / (h_i + R_s)]}$$



HYBRID π MODEL



Hybrid π Model

It includes parameters that do not appear in the other two models primarily to provide a more accurate model for high-frequency effects.

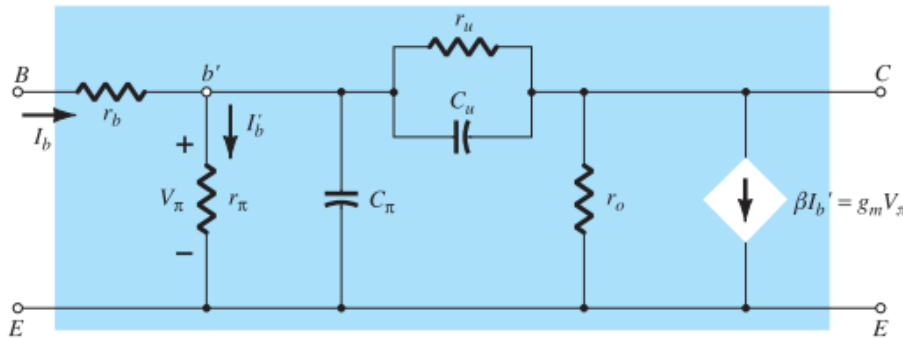


FIG. 5.123

Giacoletto (or hybrid π) high-frequency transistor small-signal ac equivalent circuit.

$$g_m = \frac{1}{r_e}$$

$$r_o = \frac{1}{h_{oe}}$$

$$r_\pi = \beta r_e$$

$$\frac{r_\pi}{r_\pi + r_u} \cong \frac{r_\pi}{r_u} \cong h_{re}$$

- The resistance r_π (using the symbol π to agree with the hybrid π terminology) is simply βr_e as introduced for the common-emitter r_e model.
- The output resistance r_o is the output resistance normally appearing across an applied load.
- The resistance r_b includes the base contact, base bulk, and base spreading resistance levels.
- The resistance r_u (the subscript u refers to the *union* it provides between collector and base terminals) is a very large resistance and provides a feedback path from output to input circuits in the equivalent model.
- All the capacitors are stray parasitic capacitors between the various junctions of the device.
- The controlled source can be a voltage-controlled current source (VCCS) or a current-controlled current source (CCCS), depending on the parameters employed.

$$\beta I_b' = \frac{1}{r_e} \cdot r_e \beta I_b' = g_m I_b' \beta r_e = g_m (I_b' r_\pi) = g_m V_\pi$$



VARIATIONS OF TRANSISTOR PARAMETERS

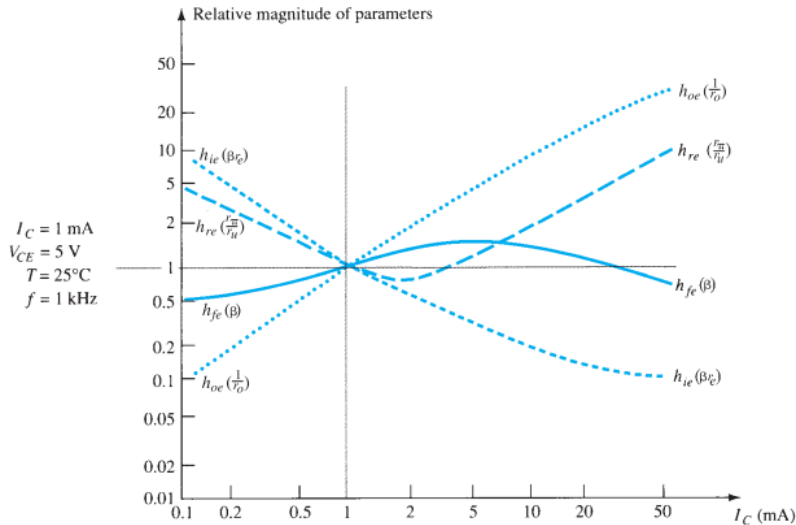


FIG. 5.124

Hybrid parameter variations with collector current.

- The parameter $h_{fe}(\beta)$ varies the least of all the parameters of a transistor equivalent circuit when plotted against variations in collector current.
- All the parameters of a hybrid transistor equivalent circuit increase with temperature.

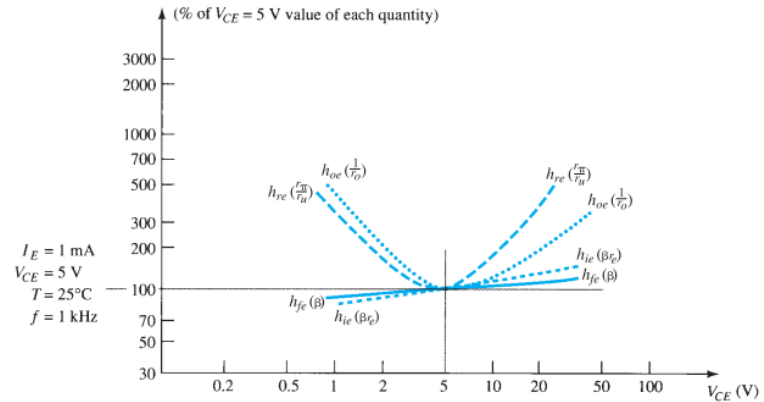


FIG. 5.125

Hybrid parameter variations with collector-emitter potential.

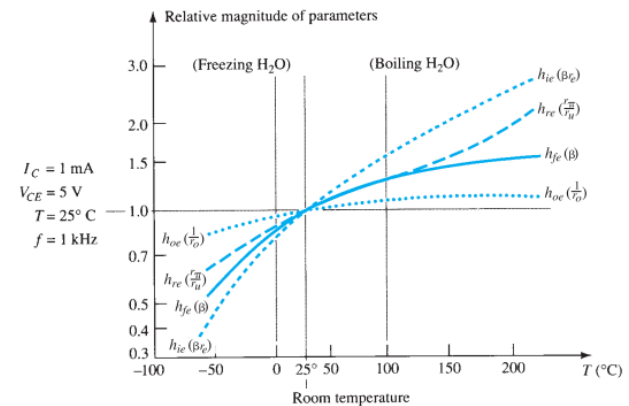


FIG. 5.126

Hybrid parameter variations with temperature.



TROUBLESHOOTING & PRACTICAL APPLICATIONS



Troubleshooting

- In general, if a system is not working properly, first disconnect the ac source and check the dc biasing levels.

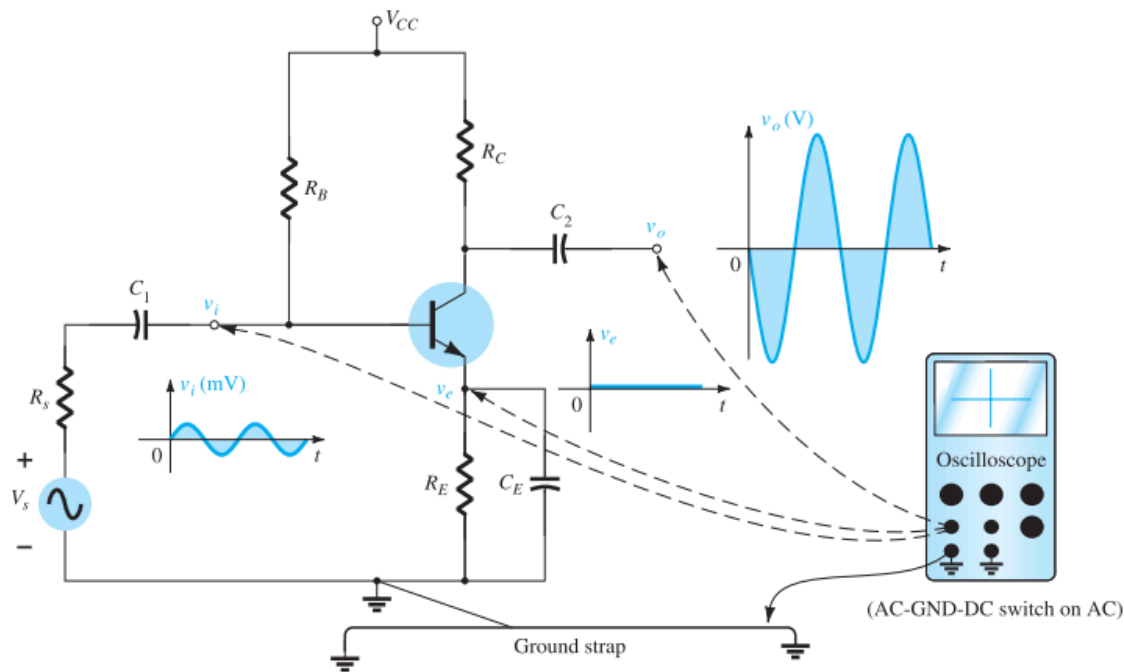


FIG. 5.128

Using the oscilloscope to measure and display various voltages of a BJT amplifier.

PRACTICAL APPLICATIONS

- Audio Mixer

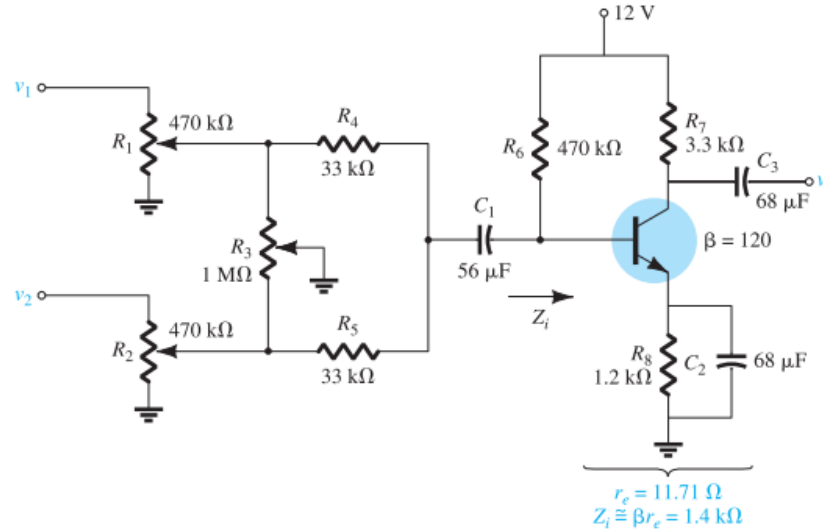


FIG. 5.130
Audio mixer.

- Preamplifier

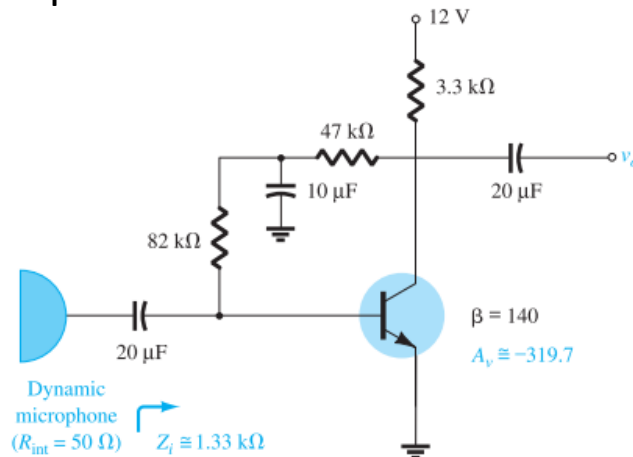


FIG. 5.133

Preamplifier for a dynamic microphone.

- Random-Noise Generator !
- Sound-Modulated Light Source !

→ Report: com3_14_R02_xx
Deadline: 17 Nov. @11:59 pm

- For more details, refer to:
 - Chapter 5 at R. Boylestad, **Electronic Devices and Circuit Theory**, 11th edition, Prentice Hall.
- The lecture is available online at:
 - <http://bu.edu.eg/staff/ahmad.elbanna-courses/11966>
- For inquires, send to:
 - ahmad.elbanna@feng.bu.edu.eg