



BENHA UNIVERSITY
FACULTY OF ENGINEERING AT SHOUBRA

ECE-312
Electronic Circuits (A)

Lecture # 6

General Frequency Considerations

Instructor:
Dr. Ahmad El-Banna



كلية الهندسة بشبرا

NOVEMBER 2014

© Ahmad El-Banna

Agenda

- Introduction
- Logarithms and Decibels
- General Frequency Considerations
- Normalization Process

INTRODUCTION



(3)

Introduction

- The analysis thus far has been limited to a particular frequency.
- We will now investigate the frequency effects introduced by the larger capacitive elements of the network at low frequencies and the smaller capacitive elements of the active device at high frequencies.
- Because the analysis will extend through a wide frequency range, the logarithmic scale will be defined and used throughout the analysis.
- In addition, because industry typically uses a decibel scale on its frequency plots, the concept of the decibel is introduced.

LOGARITHMS AND DECIBELS



(5)

Logarithms

- We use it to cover a wide range.

$$a = b^x, \quad x = \log_b a$$

$$\text{Common logarithm: } x = \log_{10} a$$

$$\text{Natural logarithm: } y = \log_e a$$

$$\log_e a = 2.3 \log_{10} a$$

$\log_{10} 10^0$	= 0
$\log_{10} 10$	= 1
$\log_{10} 100$	= 2
$\log_{10} 1,000$	= 3
$\log_{10} 10,000$	= 4
$\log_{10} 100,000$	= 5
$\log_{10} 1,000,000$	= 6
$\log_{10} 10,000,000$	= 7
$\log_{10} 100,000,000$	= 8
etc.	

$$\log_{10} 1 = 0$$




$$\log_{10} \frac{a}{b} = \log_{10} a - \log_{10} b$$

$$\log_{10} \frac{1}{b} = -\log_{10} b$$

$$\log_{10} ab = \log_{10} a + \log_{10} b$$



Semi-log graph paper

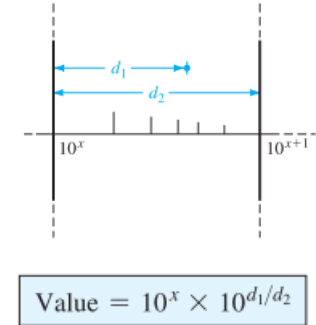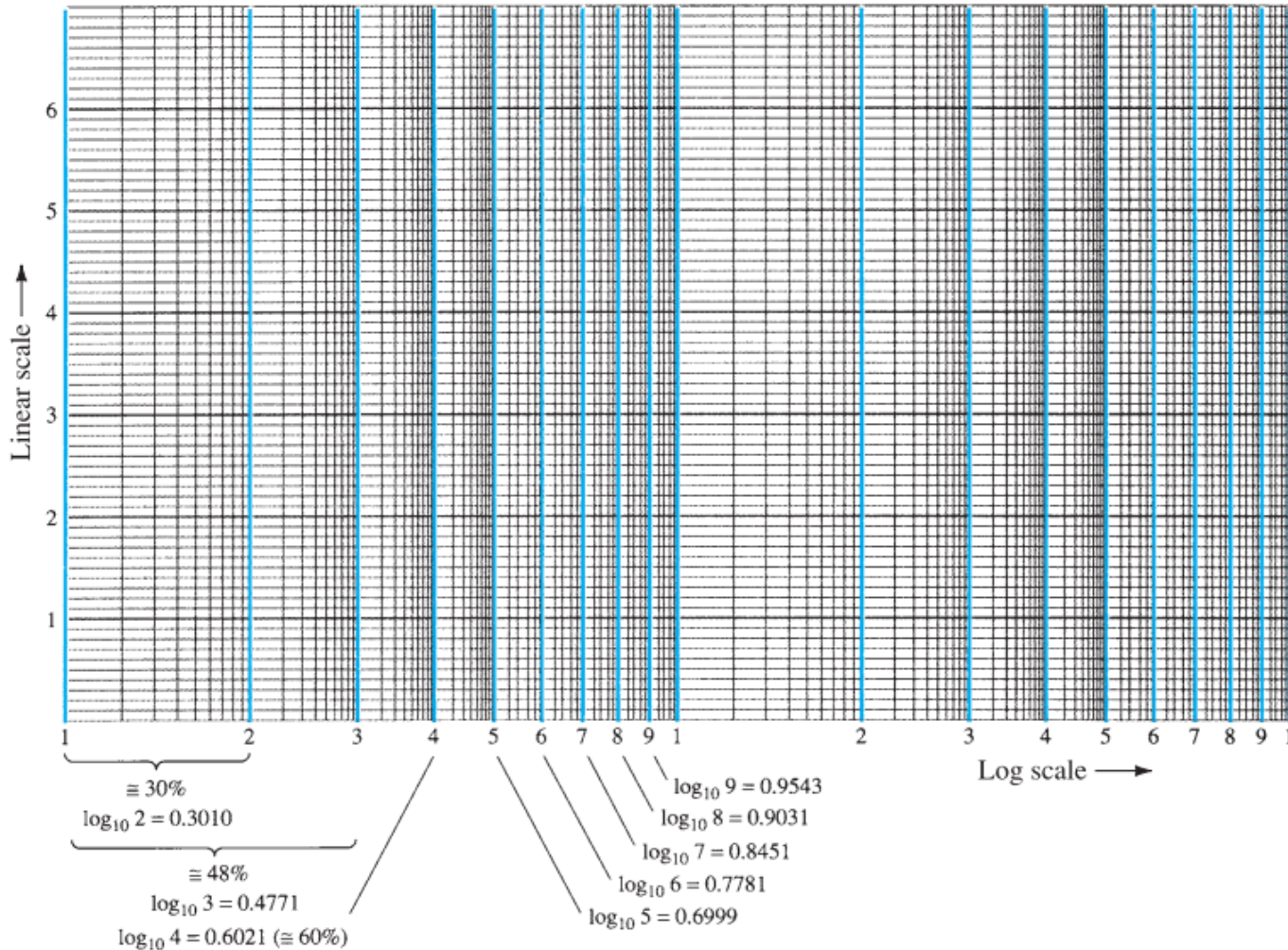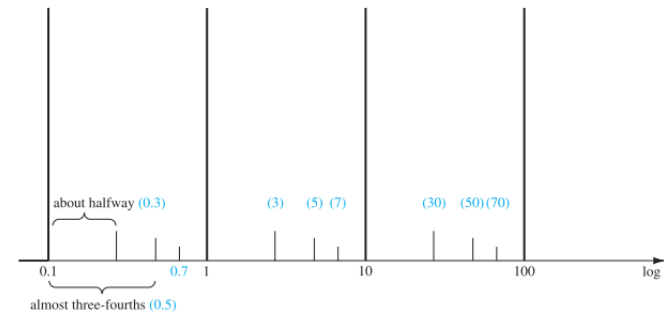

Decibels

- **Power Levels**

$$G = \log_{10} \frac{P_2}{P_1} \quad \text{bel}$$

$$G_{\text{dB}} = 10 \log_{10} \frac{P_2}{P_1} \quad \text{dB}$$

$$G_{\text{dBm}} = 10 \log_{10} \frac{P_2}{1 \text{ mW}} \Big|_{600 \Omega} \quad \text{dBm}$$

$$G_{\text{dB}} = 10 \log_{10} \frac{P_2}{P_1} = 10 \log_{10} \frac{V_2^2/R_i}{V_1^2/R_i} = 10 \log_{10} \left(\frac{V_2}{V_1} \right)^2$$

$$G_{\text{dB}} = 20 \log_{10} \frac{V_2}{V_1} \quad \text{dB}$$

- **Human Auditory Response !**

- **Cascaded Stages**

$$|A_{v_T}| = |A_{v_1}| \cdot |A_{v_2}| \cdot |A_{v_3}| \cdots |A_{v_n}|$$

$$G_{\text{dB}_T} = G_{\text{dB}_1} + G_{\text{dB}_2} + G_{\text{dB}_3} + \cdots + G_{\text{dB}_n} \quad \text{dB}$$

- **Voltage Gains versus dB Levels**

Comparing $A_v = \frac{V_o}{V_i}$ to dB

Voltage Gain, V_o/V_i	dB Level
0.5	-6
0.707	-3
1	0
2	6
10	20
40	32
100	40
1000	60
10,000	80
etc.	



GENERAL FREQUENCY CONSIDERATIONS



(9)

Low, High & Mid Frequency Range

Variation in $X_C = \frac{1}{2\pi fC}$ with frequency for a 1- μ F capacitor

f	X_C	
10 Hz	15.91 k Ω	} Range of possible effect
100 Hz	1.59 k Ω	
1 kHz	159 Ω	
10 kHz	15.9 Ω	
100 kHz	1.59 Ω	} Range of lesser concern (\cong short-circuit equivalence)
1 MHz	0.159 Ω	
10 MHz	15.9 m Ω	
100 MHz	1.59 m Ω	

Variation in $X_C = \frac{1}{2\pi fC}$ with frequency for a 5 pF capacitor

f	X_C	
10 Hz	3,183 M Ω	} Range of lesser concern (\cong open-circuit equivalent)
100 Hz	318.3 M Ω	
1 kHz	31.83 M Ω	
10 kHz	3.183 M Ω	
100 kHz	318.3 k Ω	} Range of possible effect
1 MHz	31.83 k Ω	
10 MHz	3.183 k Ω	
100 MHz	318.3 Ω	

- The larger capacitors of a system will have an important impact on the response of a system in the **low-frequency range** and can be ignored for the high-frequency region.
- The smaller capacitors of a system will have an important impact on the response of a system in the **high-frequency range** and can be ignored for the low-frequency region.
- The effect of the capacitive elements in an amplifier are ignored for the **mid-frequency** range when important quantities such as the gain and impedance levels are determined.

Typical Frequency Response

$$P_{o_{mid}} = \frac{|V_o|^2}{R_o} = \frac{|A_{v_{mid}} V_i|^2}{R_o}$$

$$P_{o_{HPF}} = \frac{|0.707 A_{v_{mid}} V_i|^2}{R_o} = 0.5 \frac{|A_{v_{mid}} V_i|^2}{R_o}$$

$$P_{o_{HPF}} = 0.5 P_{o_{mid}}$$

$$\text{bandwidth (BW)} = f_H - f_L$$

The band frequencies define a level where the gain or quantity of interest will be 70.7% of its maximum value.

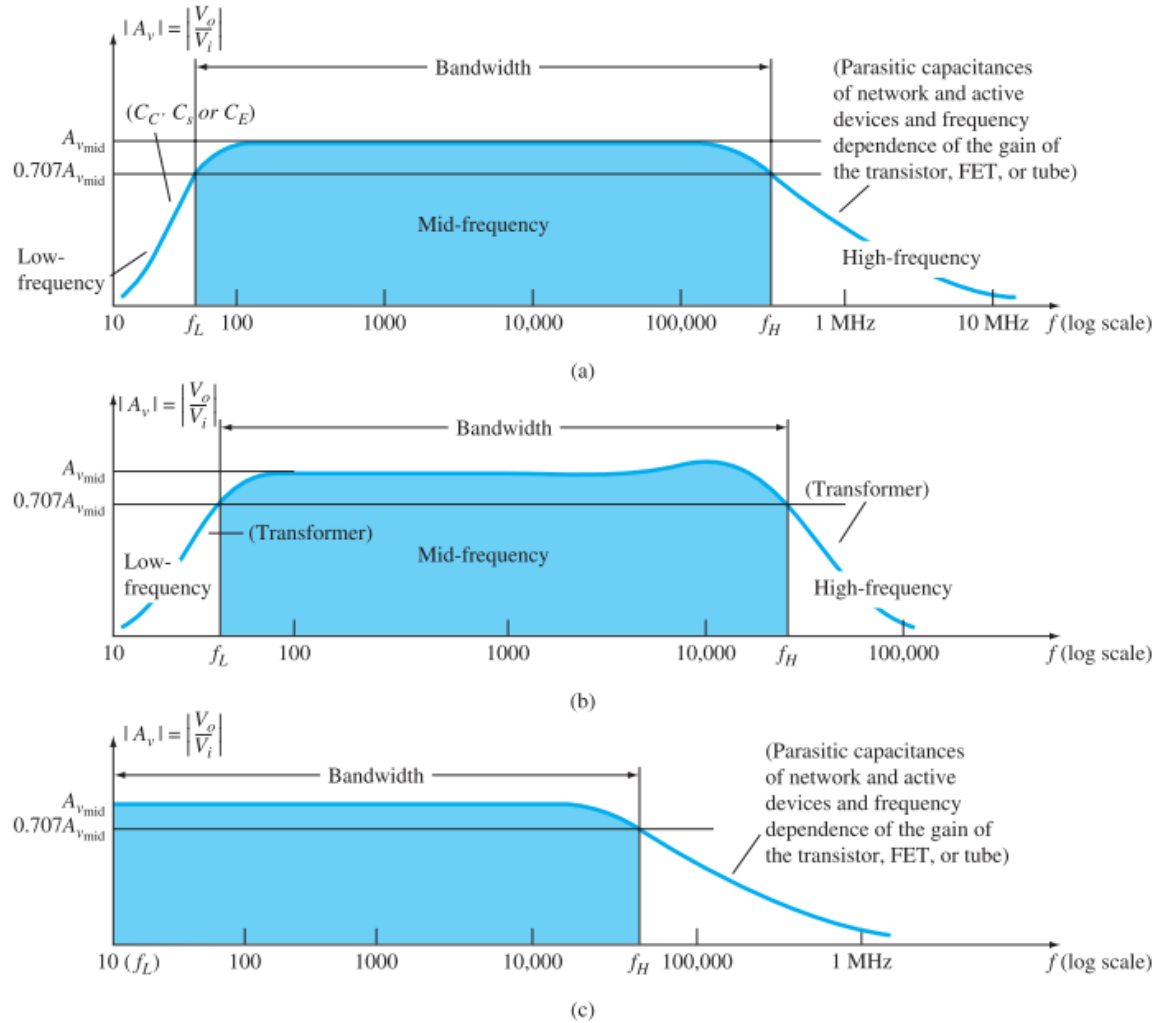


FIG. 9.8

Gain versus frequency: (a) RC-coupled amplifiers; (b) transformer-coupled amplifiers; (c) direct-coupled amplifiers.



NORMALIZATION PROCESS



- Normalized plot

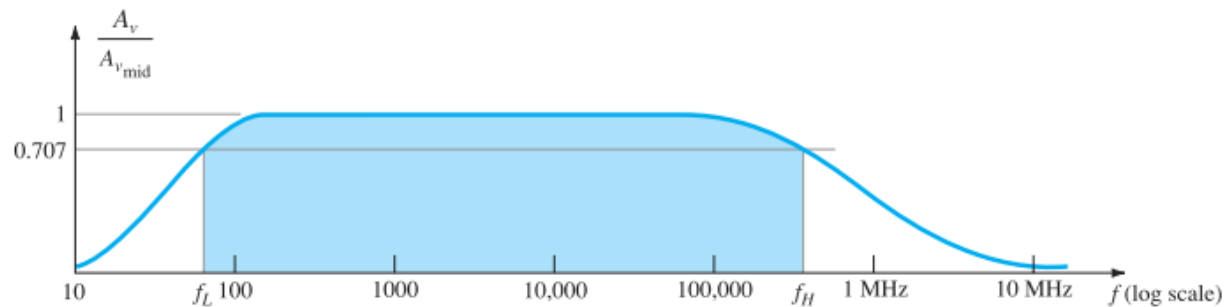


FIG. 9.9

Normalized gain versus frequency plot.

- Decibel plot

$$\left. \frac{A_v}{A_{v_{mid}}} \right|_{dB} = 20 \log_{10} \frac{A_v}{A_{v_{mid}}}$$

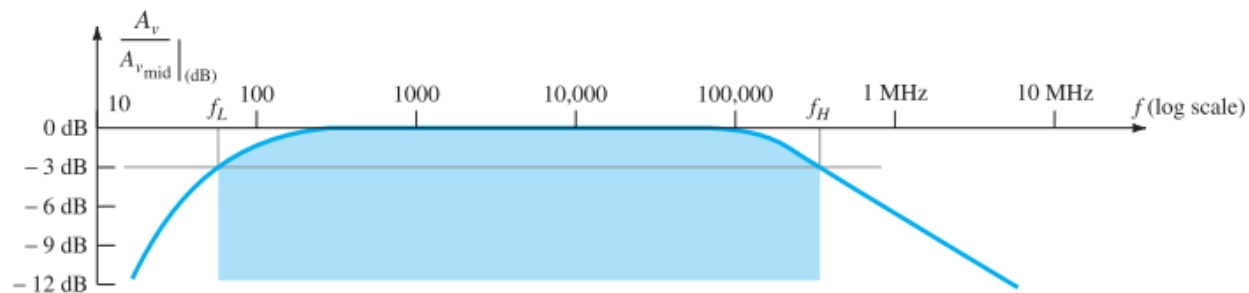


FIG. 9.12

Decibel plot of the normalized gain versus frequency plot of Fig. 9.9.

- Phase plot

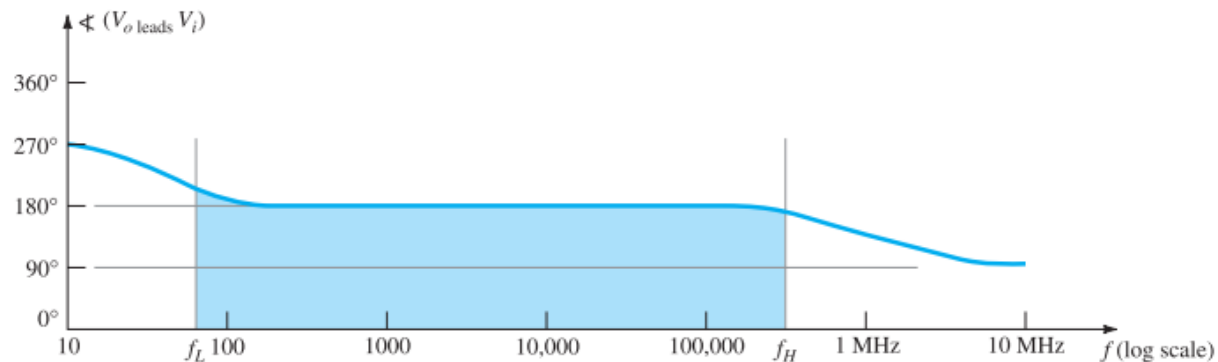


FIG. 9.13

Phase plot for an RC-coupled amplifier system.

- For more details, refer to:
 - Chapter 9 at R. Boylestad, **Electronic Devices and Circuit Theory**, 11th edition, Prentice Hall.
- The lecture is available online at:
 - <http://bu.edu.eg/staff/ahmad.elbanna-courses/11966>
- For inquires, send to:
 - ahmad.elbanna@feng.bu.edu.eg