



BENHA UNIVERSITY  
FACULTY OF ENGINEERING AT SHOUBRA

**ECE-312**  
**Electronic Circuits (A)**

Lecture # 10  
Power Amplifiers (Class C & D)

**Instructor:**  
**Dr. Ahmad El-Banna**



كلية الهندسة بشبرا

DECEMBER 2014

© Ahmad El-Banna

# Agenda



Amplifier Distortion



Power Transistor Heat Sinking



Class C & Class D Amplifiers

# AMPLIFIER DISTORTION



( 3 )

# Amplifier Distortion

- A pure sinusoidal signal has a single frequency at which the voltage varies positive and negative by equal amounts. Any signal varying over less than the full 360° cycle is considered to have distortion.
- Distortion can occur because the device characteristic is not linear, in which case non-linear or **amplitude distortion** occurs.
- Distortion can also occur because the circuit elements and devices respond to the input signal differently at various frequencies, this being **frequency distortion**.
- One technique for describing distorted but period waveforms uses Fourier analysis

- Harmonic Distortion

A signal is considered to have harmonic distortion when there are harmonic frequency components

$$\% \text{ } n\text{th harmonic distortion} = \% D_n = \frac{|A_n|}{|A_1|} \times 100\%$$

$A_1$  : amplitude of the fundamental frequency

$A_n$  : amplitude of the  $n$ th frequency component

- Total Harmonic Distortion

$$\% \text{ THD} = \sqrt{D_2^2 + D_3^2 + D_4^2 + \dots} \times 100\%$$

# Harmonic Distortion

- Second Harmonic Distortion

$$i_C \approx I_{CQ} + I_0 + I_1 \cos \omega t + I_2 \cos 2\omega t$$

At point 1 ( $\omega t = 0$ ),

$$i_C = I_{C_{max}} = I_{CQ} + I_0 + I_1 \cos 0 + I_2 \cos 0$$

$$I_{C_{max}} = I_{CQ} + I_0 + I_1 + I_2$$

At point 2 ( $\omega t = \pi/2$ ),

$$i_C = I_{CQ} = I_{CQ} + I_0 + I_1 \cos \frac{\pi}{2} + I_2 \cos \frac{2\pi}{2}$$

$$I_{CQ} = I_{CQ} + I_0 - I_2$$

At point 3 ( $\omega t = \pi$ ),

$$i_C = I_{C_{min}} = I_{CQ} + I_0 + I_1 \cos \pi + I_2 \cos 2\pi$$

$$I_{C_{min}} = I_{CQ} + I_0 - I_1 + I_2$$

Solving the preceding three equations simultaneously gives the following results:

$$I_0 = I_2 = \frac{I_{C_{max}} + I_{C_{min}} - 2I_{CQ}}{4}, \quad I_1 = \frac{I_{C_{max}} - I_{C_{min}}}{2}$$

$$D_2 = \left| \frac{I_2}{I_1} \right| \times 100\%$$

$$D_2 = \left| \frac{\frac{1}{2}(I_{C_{max}} + I_{C_{min}}) - I_{CQ}}{I_{C_{max}} - I_{C_{min}}} \right| \times 100\%$$

In a similar manner,

$$D_2 = \left| \frac{\frac{1}{2}(V_{CE_{max}} + V_{CE_{min}}) - V_{CEQ}}{V_{CE_{max}} - V_{CE_{min}}} \right| \times 100\%$$

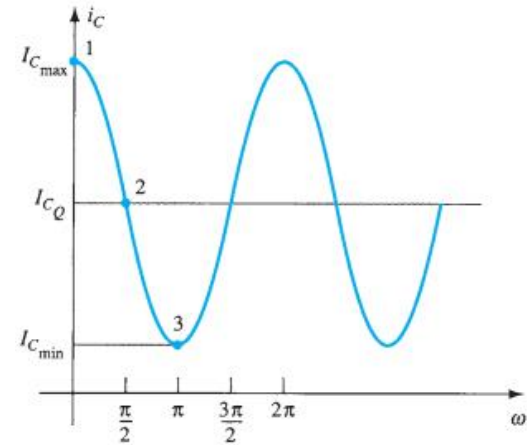


FIG. 12.20

Waveform for obtaining second harmonic distortion.

- Power of a Signal Having Distortion


$$P_1 = \frac{I_1^2 R_C}{2}$$

$$P = (I_1^2 + I_2^2 + I_3^2 + \dots) \frac{R_C}{2}$$

$$P = (1 + D_2^2 + D_3^2 + \dots) I_1^2 \frac{R_C}{2} = (1 + \text{THD}^2) P_1$$



# Graphical Description of Harmonic Components of a Distorted Signal

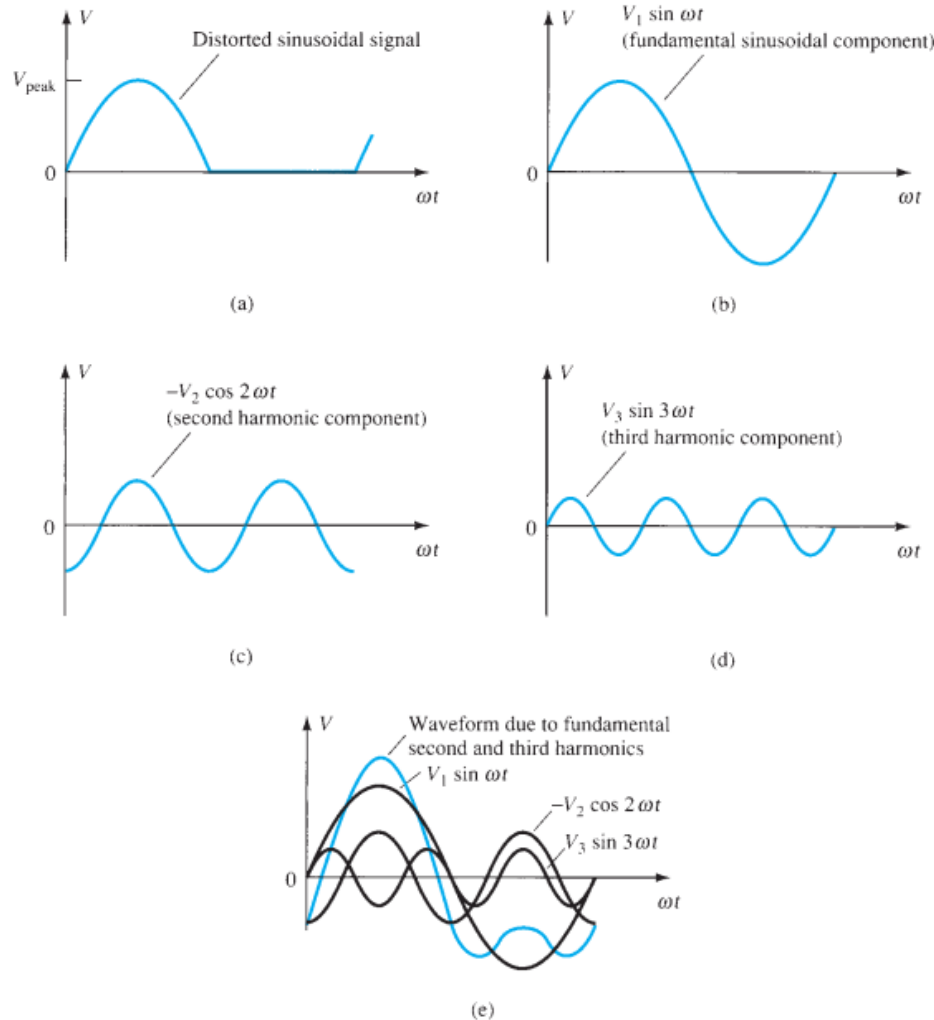

**FIG. 12.21**

Graphical representation of a distorted signal through the use of harmonic components.

# POWER TRANSISTOR HEAT SINKING



# Power Transistor Heat Sinking

- The maximum power handled by a particular device and the temperature of the transistor junctions are related since the power dissipated by the device causes an increase in temperature at the junction of the device.

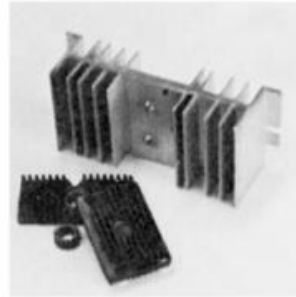


FIG. 12.22

Typical power heat sinks.

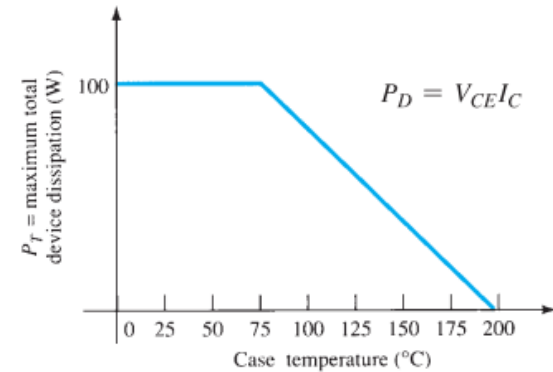


FIG. 12.23

Typical power derating curve for silicon transistors.

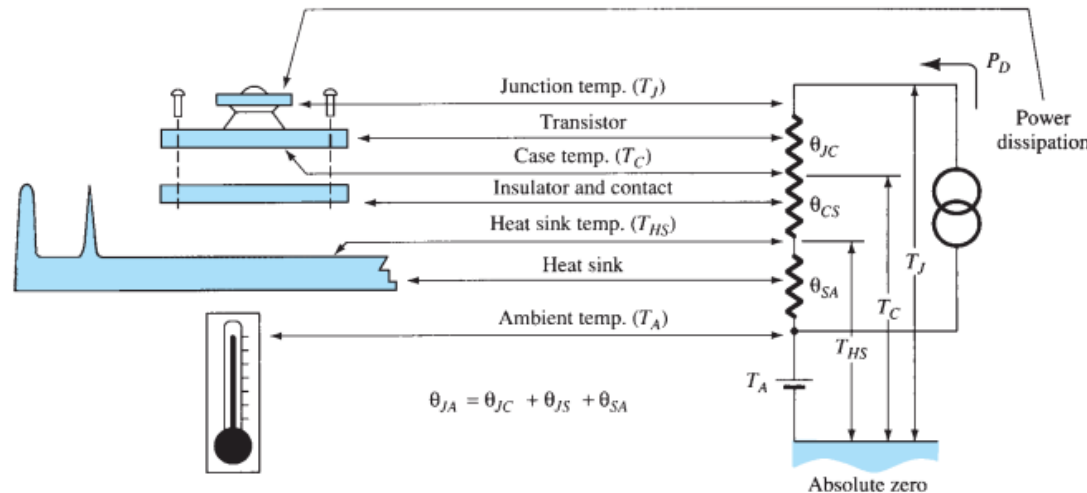


FIG. 12.24

Thermal-to-electrical analogy.

- $\theta_{JA}$  = total thermal resistance (junction to ambient)
- $\theta_{JC}$  = transistor thermal resistance (junction to case)
- $\theta_{CS}$  = insulator thermal resistance (case to heat sink)
- $\theta_{SA}$  = heat-sink thermal resistance (heat sink to ambient)

$$\theta_{JA} = \theta_{JC} + \theta_{CS} + \theta_{SA}$$

$$T_J = P_D \theta_{JA} + T_A$$






# CLASS C & CLASS D AMPLIFIERS



# Class C Amplifier


- Although class A, class AB, and class B amplifiers are most used as power amplifiers, class D amplifiers are popular because of their very high efficiency.
- Class C amplifiers, although not used as audio amplifiers, do find use in tuned circuits as in communications.
- The tuned circuit in the output, however, will provide a full cycle of output signal for the fundamental or resonant frequency of the tuned circuit ( L and C tank circuit) of the output.
- This type of operation is therefore limited to use at one fixed frequency, as occurs in a communications circuit, for example.

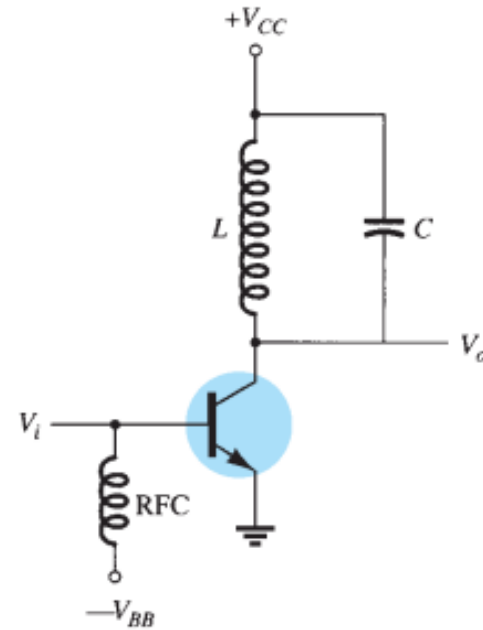

**FIG. 12.25**


*Class C amplifier circuit.*

# Class D Amplifier

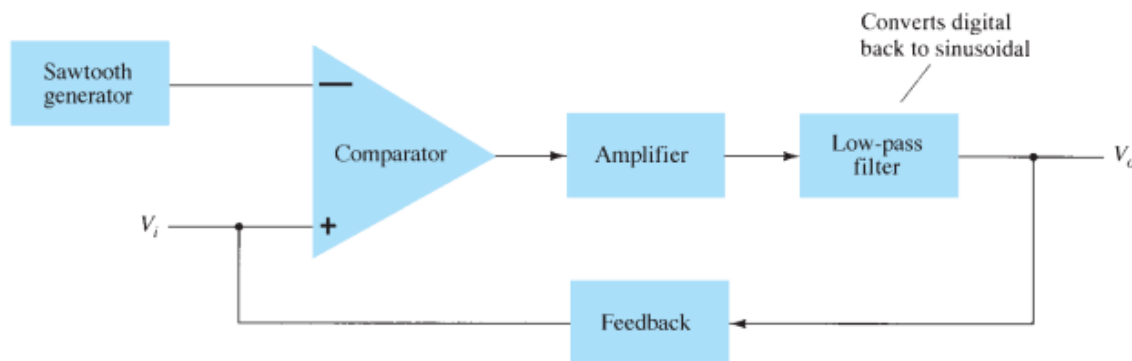

**FIG. 12.27**  
Block diagram of class D amplifier.

- Class D amplifier is designed to operate with digital or pulse-type signals.
- An efficiency of over 90% is achieved, making it desirable in power amplifiers.
- It is necessary to convert any input signal into a pulse-type waveform before using it to drive a large power load and to convert the signal back into a sinusoidal-type signal to recover the original signal.

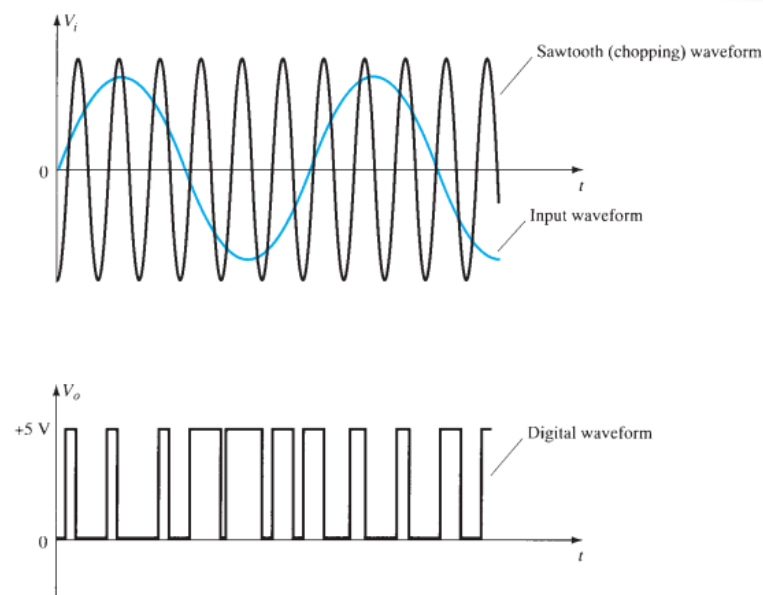

**FIG. 12.26**  
Chopping of a sinusoidal waveform to produce a digital waveform.

- For more details, refer to:
  - Chapter 12 at R. Boylestad, **Electronic Devices and Circuit Theory**, 11<sup>th</sup> edition, Prentice Hall.
- The lecture is available online at:
  - <http://bu.edu.eg/staff/ahmad.elbanna-courses/11966>
- For inquires, send to:
  - [ahmad.elbanna@feng.bu.edu.eg](mailto:ahmad.elbanna@feng.bu.edu.eg)