



BENHA UNIVERSITY
FACULTY OF ENGINEERING AT SHOUBRA

ECE-312
Electronic Circuits (A)

Lecture # 12
Oscillators (LC Circuits)

Instructor:
Dr. Ahmad El-Banna



كلية الهندسة بشبرا

DECEMBER 2014

© Ahmad El-Banna

Agenda

- 1 The Colpitts Oscillator
- 2 The Clapp Oscillator
- 3 The Hartley Oscillator
- 4 The Armstrong Oscillator
- 5 Crystal-Controlled Oscillators

THE COLPITTS OSCILLATOR




Colpitts Oscillator

- LC feedback elements are normally used in oscillators that require higher frequencies of oscillation.
- Also, because of the frequency limitation (lower unity-gain frequency) of most op-amps, discrete transistors (BJT or FET) are often used as the gain element in LC oscillators.
- Colpitts oscillator uses an LC circuit in the feedback loop to provide the necessary phase shift and to act as a resonant filter that passes only the desired frequency of oscillation.

$$f_r \cong \frac{1}{2\pi\sqrt{LC_T}}$$

$$C_T = \frac{C_1 C_2}{C_1 + C_2}$$

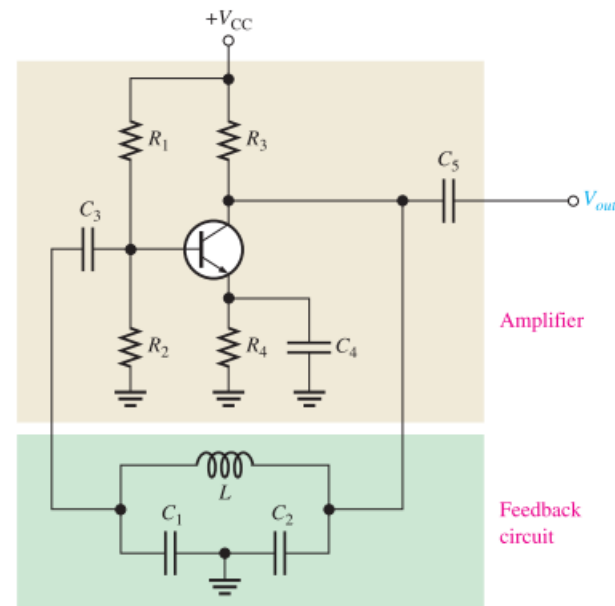

Conditions for Oscillation and Start-Up



$$B = \frac{V_f}{V_{out}} \cong \frac{IX_{C1}}{IX_{C2}} = \frac{X_{C1}}{X_{C2}} = \frac{1/(2\pi f_r C_1)}{1/(2\pi f_r C_2)}$$

$$B = \frac{C_2}{C_1} \quad A_v = \frac{C_1}{C_2}$$

- Loading of the Feedback Circuit Affects the Frequency of Oscillation

→ Z_{in} of the amplifier loads the feed-back circuit and lowers its Q, thus lowering the resonant frequency.

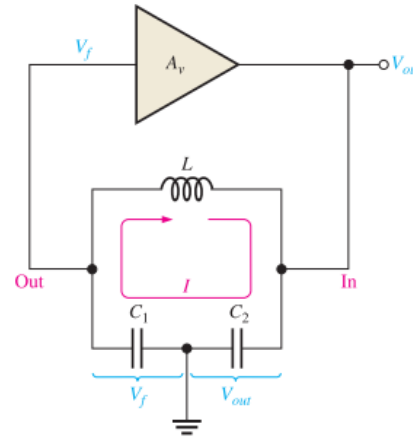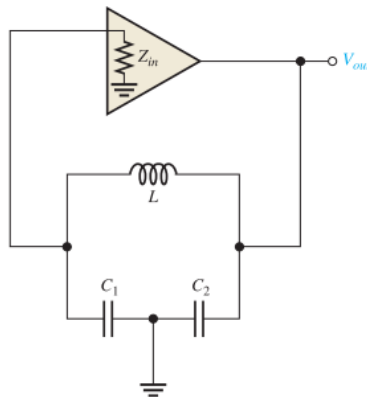
$$f_r = \frac{1}{2\pi\sqrt{LC_T}} \sqrt{\frac{Q^2}{Q^2 + 1}}$$




◀ FIGURE 16-17

The attenuation of the tank circuit is the output of the tank (V_f) divided by the input to the tank (V_{out}). $B = V_f/V_{out} = C_2/C_1$. For $A_v B > 1$, A_v must be greater than C_1/C_2 .

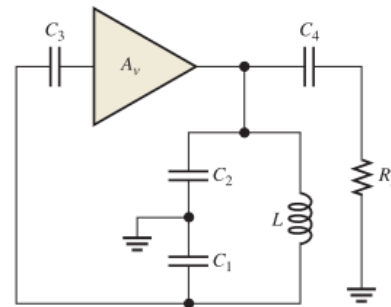→ A FET can be used in place of a BJT, as shown in Figure 16-19, to minimize the loading effect of the transistor's input impedance.



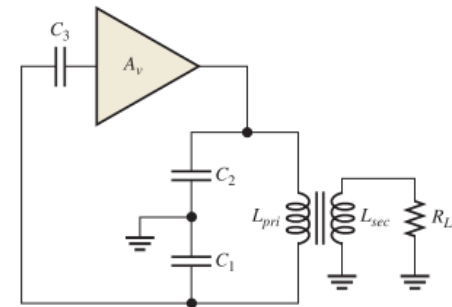(a) A load capacitively coupled to oscillator output can reduce circuit Q and f_r .



(b) Transformer coupling of load can reduce loading effect by impedance transformation.

▲ FIGURE 16-20

Oscillator loading.



THE CLAPP OSCILLATOR



Clapp Oscillator


- The Clapp oscillator is a variation of the Colpitts with addition of C_3 .

$$C_T = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}}$$

$$(Q > 10) \longrightarrow f_r \cong \frac{1}{2\pi\sqrt{LC_T}}$$

If C_3 is much smaller than C_1 and C_2 ,

$$(f_r \cong 1/(2\pi\sqrt{LC_3})).$$

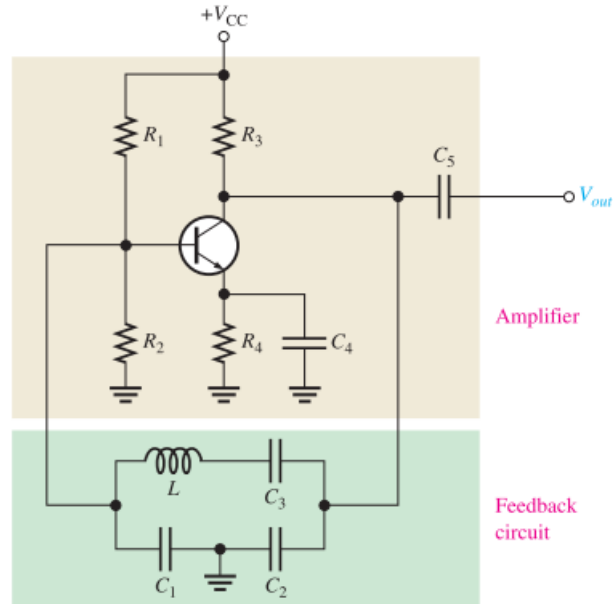

- Since C_1 and C_2 are both connected to ground at one end, the junction capacitance of the transistor and other stray capacitances appear in parallel with C_1 and C_2 to ground, altering their effective values.
- C_3 is not affected, however, and thus provides a more accurate and stable frequency of oscillation.

THE HARTLEY OSCILLATOR



Hartley Oscillator


- The Hartley oscillator is similar to the Colpitts except that the feedback circuit consists of two series inductors and a parallel capacitor

$$Q > 10 \quad f_r \cong \frac{1}{2\pi\sqrt{L_T C}}$$

$$L_T = L_1 + L_2$$

$$B \cong \frac{L_1}{L_2}$$

$$A_v \cong \frac{L_2}{L_1}$$

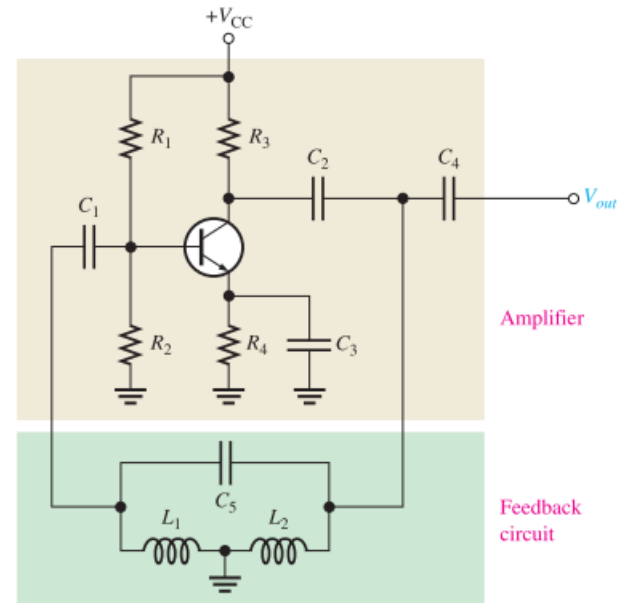

- Loading of the tank circuit has the same effect in the Hartley as in the Colpitts; that is, the Q is decreased and thus f_r decreases.


THE ARMSTRONG OSCILLATOR



Armstrong Oscillator

- This type of LC feedback oscillator uses transformer coupling to feed back a portion of the signal voltage.
- It is sometimes called a “tickler” oscillator in reference to the transformer secondary or “tickler coil” that provides the feedback to keep the oscillation going.
- The Armstrong is less common than the Colpitts, Clapp, and Hartley, mainly because of the disadvantage of transformer size and cost.
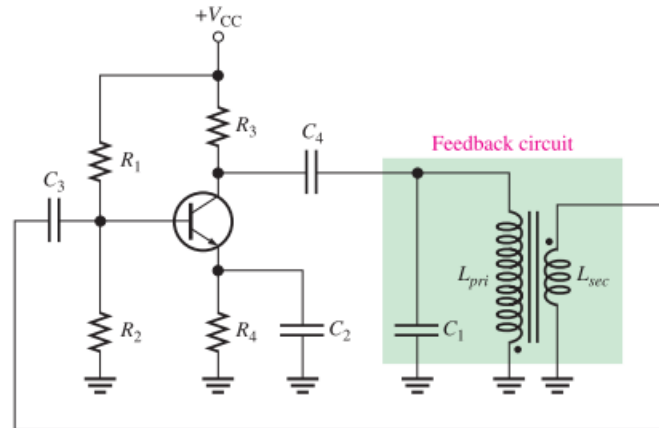
$$f_r = \frac{1}{2\pi\sqrt{L_{pri}C_1}}$$




CRYSTAL-CONTROLLED OSCILLATORS



Crystal-Controlled Oscillators

- The most stable and accurate type of feedback oscillator uses a **piezoelectric crystal** in the feedback loop to control the frequency.
- Quartz is one type of crystalline substance found in nature that exhibits a property called the piezoelectric effect.
- When a changing mechanical stress is applied across the crystal to cause it to vibrate, a voltage develops at the frequency of mechanical vibration.
- Conversely, when an ac voltage is applied across the crystal, it vibrates at the frequency of the applied voltage.
- The greatest vibration occurs at the crystal's natural resonant frequency, which is determined by the physical dimensions and by the way the crystal is cut.


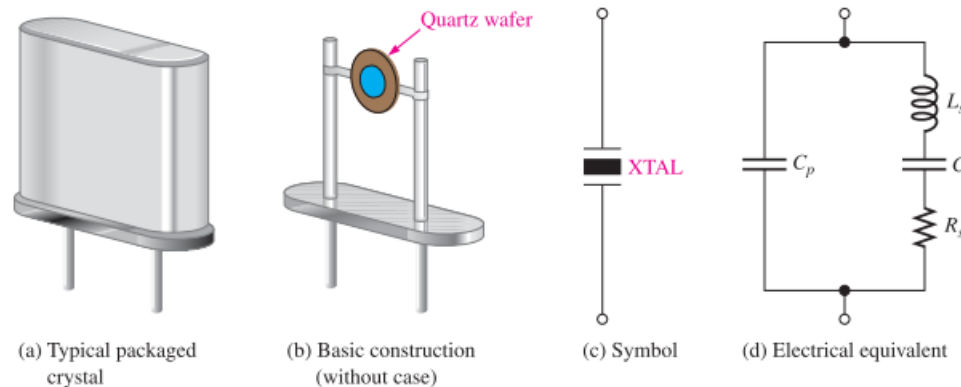


Basic crystal oscillators

- A great advantage of the crystal is that it exhibits a very high Q.
- The impedance of the crystal is minimum at the series resonant frequency, thus providing maximum feedback.
- a crystal is used as a series resonant tank circuit.
- The crystal tuning capacitor, C_c is used to “fine tune” the oscillator frequency by “pulling” the resonant frequency of the crystal slightly up or down.

Modes:

- Piezoelectric crystals can oscillate in either of two modes—fundamental or overtone.
- The **fundamental** frequency of a crystal is the lowest frequency at which it is naturally resonant.
- The fundamental frequency depends on the crystal’s mechanical dimensions, type of cut, .. etc.
- Usually it’s less than 20 MHz.
- **Overtone**s are approximate integer multiples of the fundamental frequency.
- Many crystal oscillators are available in integrated circuit packages.

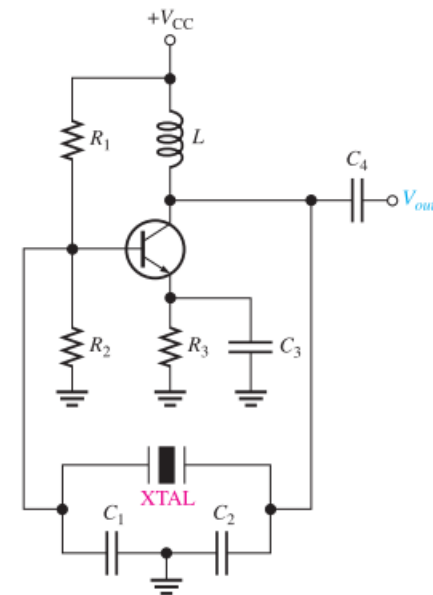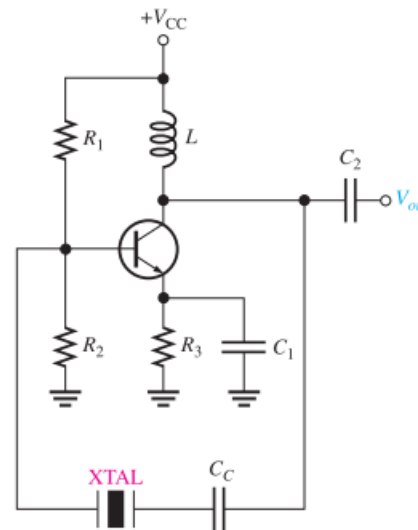

- For more details, refer to:
 - Chapter 16 at T. Floyd, **Electronic Devices**, 9th edition.
 - http://www.electronics-tutorials.ws/oscillator/rc_oscillator.html
 - ➔ • <http://www.electronics-tutorials.ws/oscillator/oscillators.html>
- The lecture is available online at:
 - <http://bu.edu.eg/staff/ahmad.elbanna-courses/11966>
- For inquiries, send to:
 - ahmad.elbanna@feng.bu.edu.eg