



BENHA UNIVERSITY
FACULTY OF ENGINEERING AT SHOUBRA

ECE-322
Electronic Circuits (A)

Lecture #14
Feedback Amplifiers

Instructor:
Dr. Ahmad El-Banna



FALL 2016

© Ahmad El-Banna

Agenda



FB Amplifiers Structure

Different Topologies

Examples


Practical Feedback Circuits

FEEDBACK AMPLIFIER BASICS



Feedback Amplifier

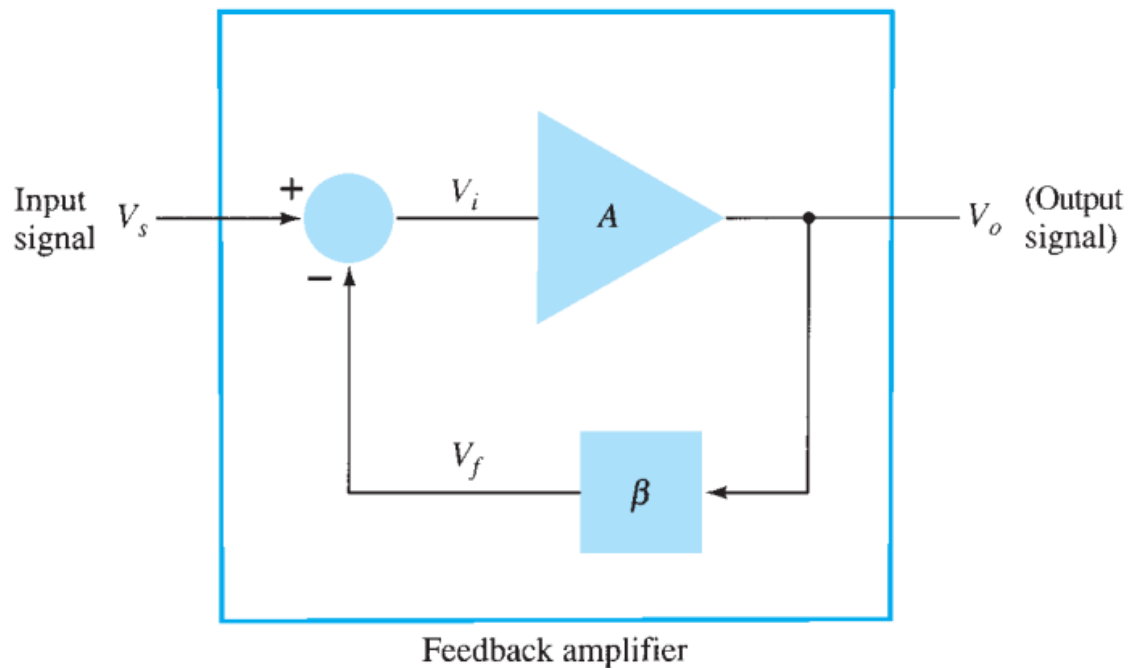- Block diagram of a typical feedback amplifier



- Types:
 1. Negative feedback.
 2. Positive feedback.


Feedback Amplifier

- **Depending on** the relative **polarity** of the signal being fed back into a circuit, one may have **negative** or **positive** feedback.
- **Positive** feedback drives a circuit into **oscillation** as in various types of oscillator circuits.
- **Negative** feedback results in decreased voltage gain, for which a number of circuit **features** are **improved**.
- Some **improvements** of negative feedback are :
 1. Higher input impedance.
 2. Lower output impedance.
 3. Better stabilized voltage gain.
 4. Improved frequency response.
 5. Reduced noise.
 6. More linear operation.




FEEDBACK CONNECTION TYPES

1. Voltage-series feedback

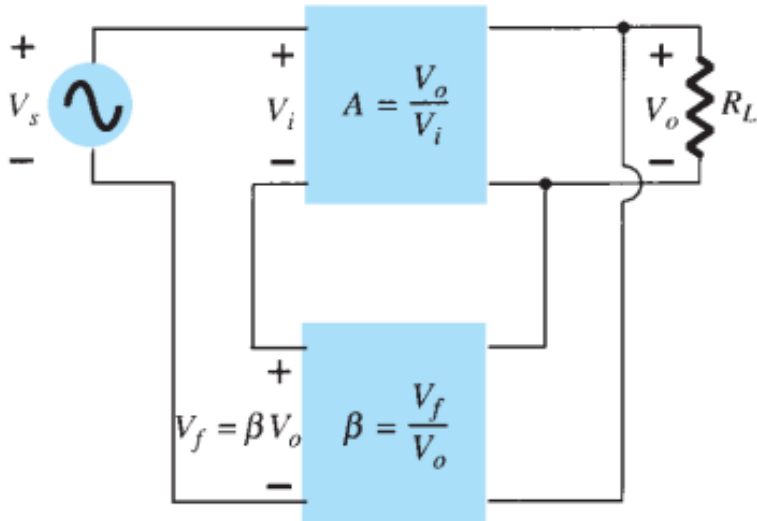


2. Voltage-shunt feedback

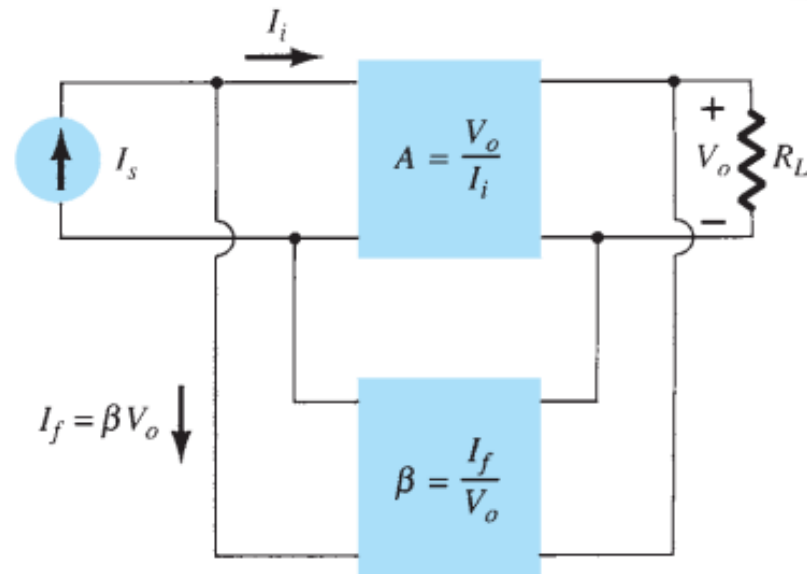


FEEDBACK CONNECTION TYPES..

3. Current-series feedback

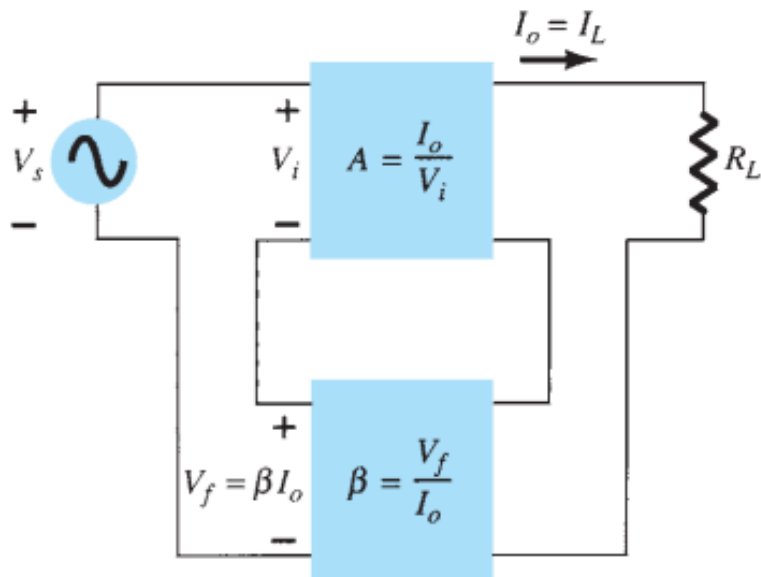

4. Current-shunt feedback

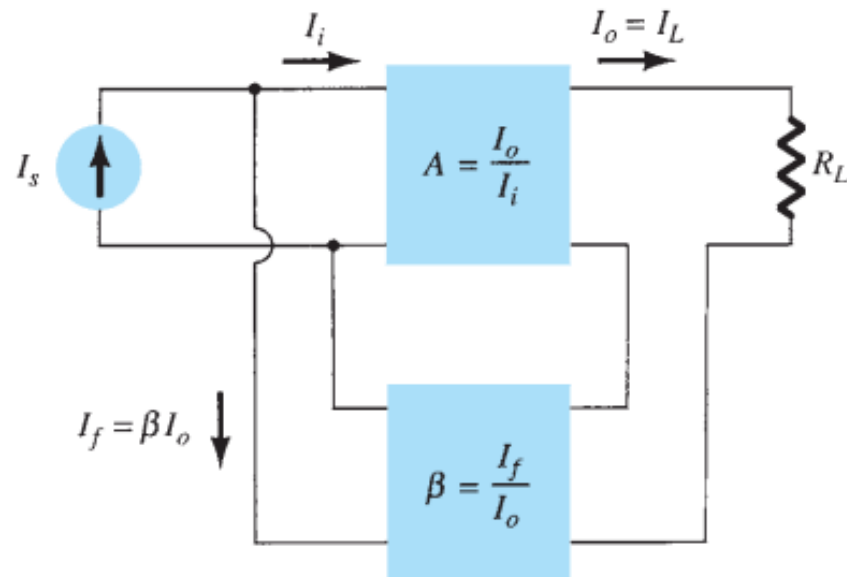

Parameters improvement

Effect of Feedback Connection on Input and Output Impedance

Voltage-Series	Current-Series	Voltage-Shunt	Current-Shunt
$Z_{if} = Z_i(1 + \beta A)$ (increased)	$Z_i(1 + \beta A)$ (increased)	$\frac{Z_i}{1 + \beta A}$ (decreased)	$\frac{Z_i}{1 + \beta A}$ (decreased)
$Z_{of} = \frac{Z_o}{1 + \beta A}$ (decreased)	$Z_o(1 + \beta A)$ (increased)	$\frac{Z_o}{1 + \beta A}$ (decreased)	$Z_o(1 + \beta A)$ (increased)

Effect of feedback on gain:

$$A_f = \frac{A}{1 + \beta A}$$

Parameters improvement ..

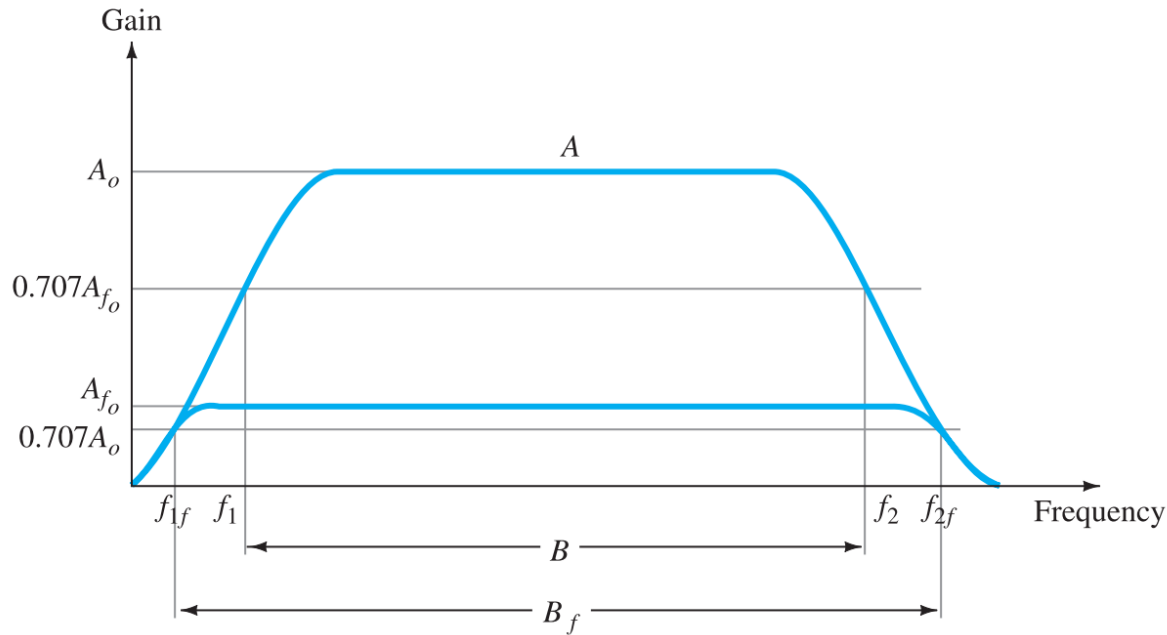


FIG. 14.6

Effect of negative feedback on gain and bandwidth.

Gain Stability with Feedback

$$A_f = \frac{A}{1 + \beta A}$$

$$\left| \frac{dA_f}{A_f} \right| = \frac{1}{|1 + \beta A|} \left| \frac{dA}{A} \right|$$

$$\left| \frac{dA_f}{A_f} \right| \cong \left| \frac{1}{\beta A} \right| \left| \frac{dA}{A} \right| \quad \text{for } \beta A \gg 1$$

FEEDBACK CONNECTION TYPES...

- **Series** feedback connections tend to **increase** the **input resistance**, whereas **shunt** feed-back connections tend to **decrease** the **input resistance**.
- **Voltage** feedback tends to **decrease** the **output impedance**, whereas **current** feedback tends to **increase** the **output impedance**.

Example

EXAMPLE 14.1 Determine the voltage gain, input, and output impedance with feedback for voltage-series feedback having $A = -100$, $R_i = 10 \text{ k}\Omega$, and $R_o = 20 \text{ k}\Omega$ for feedback of (a) $\beta = -0.1$ and (b) $\beta = -0.5$.

Solution: Using Eqs. (14.2), (14.4), and (14.6), we obtain

$$\text{a. } A_f = \frac{A}{1 + \beta A} = \frac{-100}{1 + (-0.1)(-100)} = \frac{-100}{11} = -9.09$$

$$Z_{if} = Z_i(1 + \beta A) = 10 \text{ k}\Omega (11) = 110 \text{ k}\Omega$$

$$Z_{of} = \frac{Z_o}{1 + \beta A} = \frac{20 \times 10^3}{11} = 1.82 \text{ k}\Omega$$

$$\text{b. } A_f = \frac{A}{1 + \beta A} = \frac{-100}{1 + (-0.5)(-100)} = \frac{-100}{51} = -1.96$$

$$Z_{if} = Z_i(1 + \beta A) = 10 \text{ k}\Omega (51) = 510 \text{ k}\Omega$$

$$Z_{of} = \frac{Z_o}{1 + \beta A} = \frac{20 \times 10^3}{51} = 392.16 \Omega$$

Practical Feedback Circuits

Voltage-Series Feedback

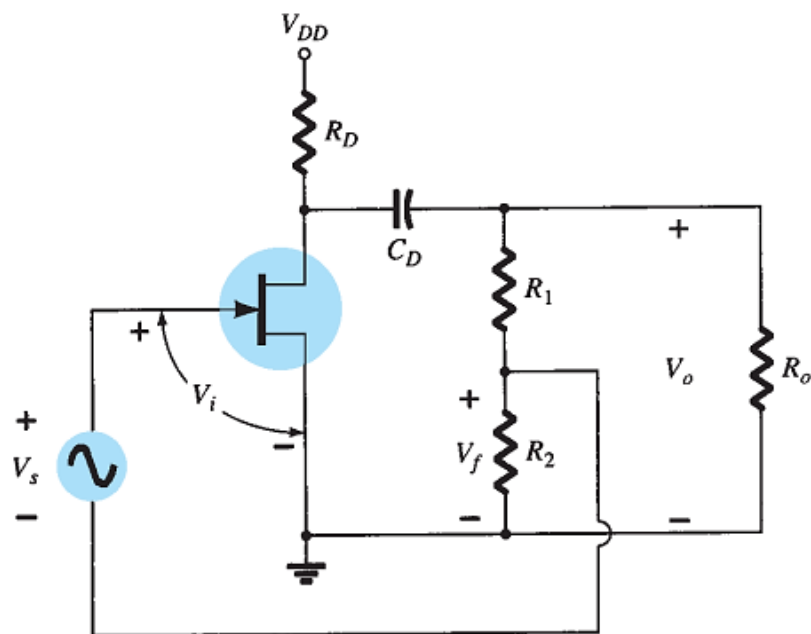


FIG. 14.7

FET amplifier stage with voltage-series feedback.

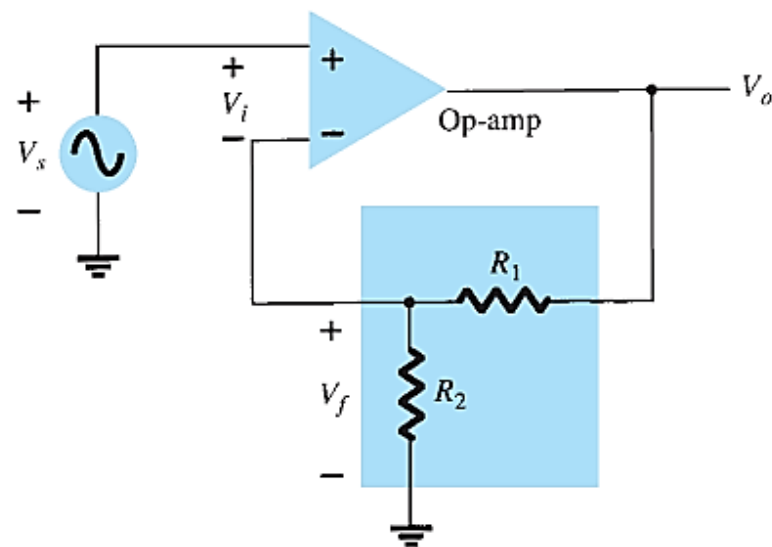


FIG. 14.8

Voltage-series feedback in an op-amp connection.

Voltage-Series Feedback circuit

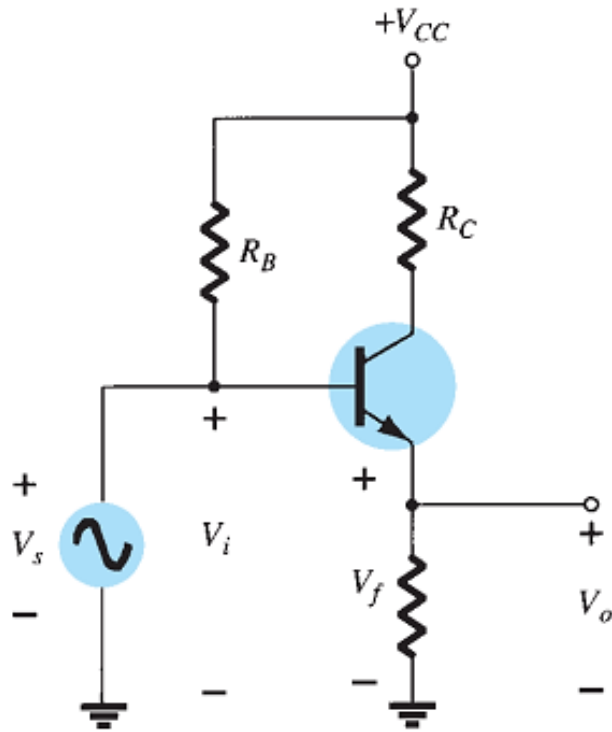


FIG. 14.9

Voltage-series feedback circuit
(emitter-follower).

$$A = \frac{V_o}{V_s} = \frac{h_{fe} I_b R_E}{V_s} = \frac{h_{fe} R_E (V_s / h_{ie})}{V_s} = \frac{h_{fe} R_E}{h_{ie}}$$

$$\beta = \frac{V_f}{V_o} = 1$$

$$A_f = \frac{V_o}{V_s} = \frac{A}{1 + \beta A} = \frac{h_{fe} R_E / h_{ie}}{1 + (1)(h_{fe} R_E / h_{ie})}$$

$$= \frac{h_{fe} R_E}{h_{ie} + h_{fe} R_E}$$

For $h_{fe} R_E \gg h_{ie}$, $A_f \cong 1$

Current-Series Feedback circuit

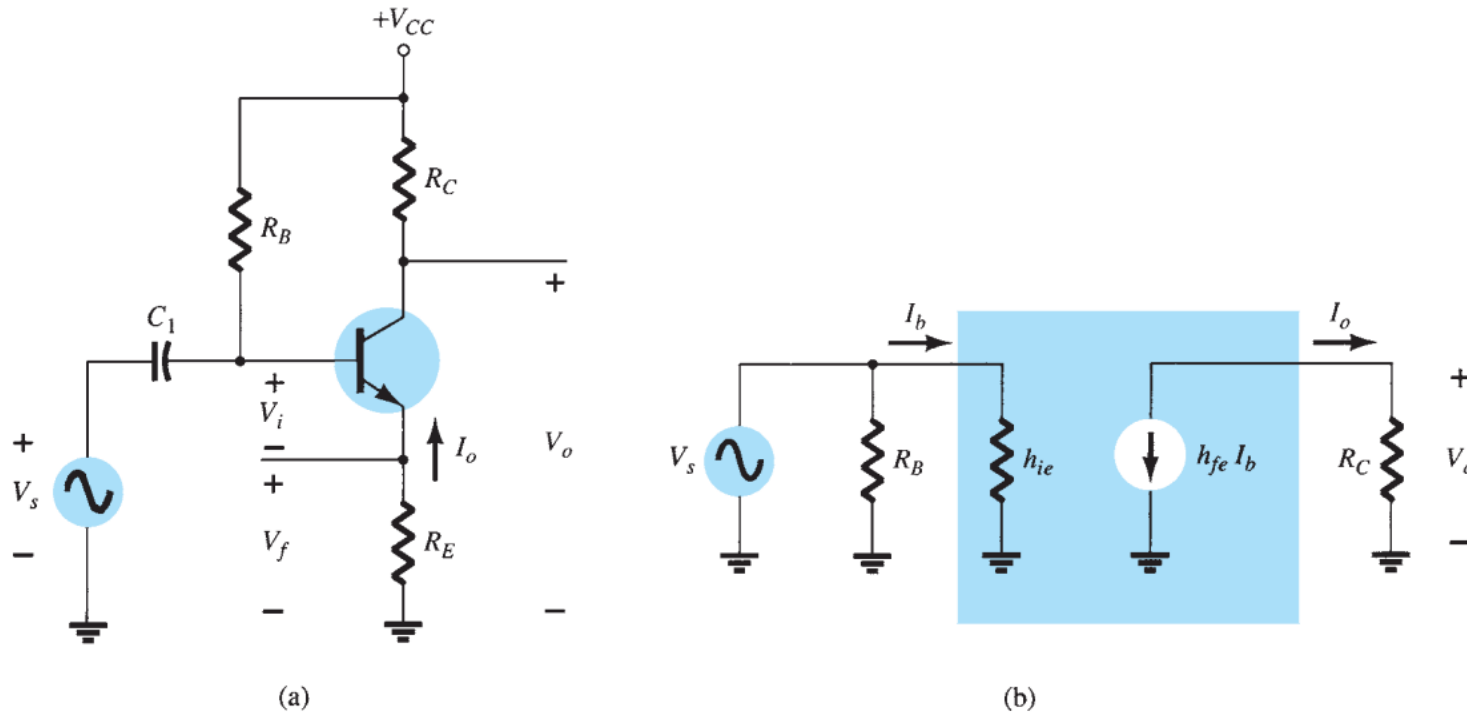


FIG. 14.10

Transistor amplifier with unbypassed emitter resistor (R_E) for current-series feedback: (a) amplifier circuit; (b) ac equivalent circuit without feedback.

Current-Series Feedback circuit

Without Feedback Referring to the basic format of Fig. 14.2a and summarized in Table 14.1, we have

$$A = \frac{I_o}{V_i} = \frac{-I_b h_{fe}}{I_b h_{ie} + R_E} = \frac{-h_{fe}}{h_{ie} + R_E} \quad (14.16)$$

$$\beta = \frac{V_f}{I_o} = \frac{-I_o R_E}{I_o} = -R_E \quad (14.17)$$

The input and output impedances are, respectively,

$$Z_i = R_B \parallel (h_{ie} + R_E) \cong h_{ie} + R_E \quad (14.18)$$

$$Z_o = R_C \quad (14.19)$$

With Feedback

$$A_f = \frac{I_o}{V_s} = \frac{A}{1 + \beta A} = \frac{-h_{fe}/h_{ie}}{1 + (-R_E)\left(\frac{-h_{fe}}{h_{ie} + R_E}\right)} \cong \frac{-h_{fe}}{h_{ie} + h_{fe}R_E} \quad (14.20)$$

The input and output impedances are calculated as specified in Table 14.2:

$$Z_{if} = Z_i(1 + \beta A) \cong h_{ie} \left(1 + \frac{h_{fe}R_E}{h_{ie}}\right) = h_{ie} + h_{fe}R_E \quad (14.21)$$

$$Z_{of} = Z_o(1 + \beta A) = R_C \left(1 + \frac{h_{fe}R_E}{h_{ie}}\right) \quad (14.22)$$


The voltage gain A with feedback is

$$A_{vf} = \frac{V_o}{V_s} = \frac{I_o R_C}{V_s} = \left(\frac{I_o}{V_s}\right) R_C = A_f R_C \cong \frac{-h_{fe}R_C}{h_{ie} + h_{fe}R_E} \quad (14.23)$$



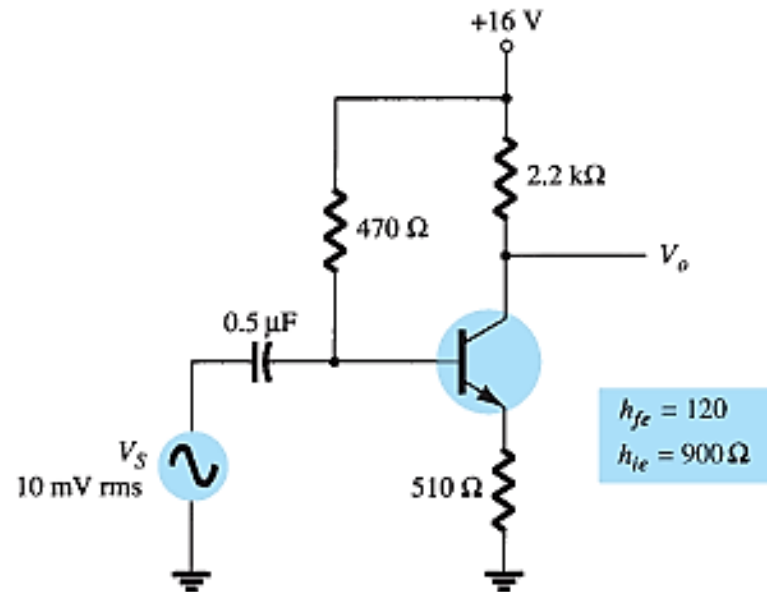Example

- Calculate the voltage gain of the shown circuit.



Solution: Without feedback,

$$A = \frac{I_o}{V_i} = \frac{-h_{fe}}{h_{ie} + R_E} = \frac{-120}{900 + 510} = -0.085$$

$$\beta = \frac{V_f}{I_o} = -R_E = -510$$

The factor $(1 + \beta A)$ is then

$$1 + \beta A = 1 + (-0.085)(-510) = 44.35$$

The gain with feedback is then

$$A_f = \frac{I_o}{V_s} = \frac{A}{1 + \beta A} = \frac{-0.085}{44.35} = -1.92 \times 10^{-3}$$

and the voltage gain with feedback A_{vf} is

$$A_{vf} = \frac{V_o}{V_s} = A_f R_C = (-1.92 \times 10^{-3})(2.2 \times 10^3) = -4.2$$

Without feedback ($R_E = 0$), the voltage gain is

$$A_v = \frac{-R_C}{r_e} = \frac{-2.2 \times 10^3}{7.5} = -293.3$$



- For more details, refer to:
 - Chapter 14 at Boylestad, **Electronic Circuits and Devices**, 11th edition.
- The lecture is available online at:
 - <http://bu.edu.eg/staff/ahmad.elbanna-courses/11966>
- For inquiries, send to:
 - ahmad.elbanna@feng.bu.edu.eg