



- Significant equations sheet is attached.
- Answer all the following questions

- No. of questions : 5
- Total Mark: 90 Marks

**Question (1) (12 Marks)**

Choose the correct answer:

- 1- Which of the h-parameters corresponds to  $r_e$  in a common-base configuration?  
a.  $h_{fb}$                       b.  $h_{fb}$                       c.  $h_{ib}$                       d.  $h_{ob}$
- 2- The loaded voltage gain of an amplifier is always more than the no-load level.  
a. True                      b. False
- 3- By what other name(s) are the cutoff frequencies in a frequency response plot called?  
a. Corner frequency      b. Break frequency      c. Half-power frequency      d. All of the above
- 4- A change in frequency by a factor of \_\_\_\_\_ is equivalent to 1 octave.  
a. 2                      b. 10                      c. 5                      d. 20
- 5- By how much does the output signal vary for a class AB power amplifier?  
a.  $360^\circ$                       b.  $180^\circ$                       c. between  $180^\circ$  and  $360^\circ$                       d. Less than  $180^\circ$
- 6- Calculate the effective resistance seen looking into the primary of a 20:1 transformer connected to an  $8\Omega$  load.  
a.  $3.2\text{ K}\Omega$                       b.  $3.0\text{ K}\Omega$                       c.  $2.8\text{ K}\Omega$                       d.  $1.8\text{ K}\Omega$
- 7- An oscillator differs from an amplifier because the oscillator  
a. has more gain                      b. requires no input signal                      c. requires no dc supply
- 8- A phase-shift oscillator has  
a. three RC circuits                      b. three LC circuits                      c. a T-type circuit

**Question (2) (20 Marks)**

- 1- Sketch the complete hybrid, hybrid  $\pi$  and  $r_e$  models for a common-emitter *npn* transistor. Given  $r_b=3\Omega$ ,  $r_\pi=1.6\text{k}\Omega$ ,  $r_u=20\text{M}\Omega$ ,  $C_u=1\text{pF}$ ,  $C_\pi=5\text{pF}$ ,  $\beta=100$ ,  $h_{oe}=18\mu\text{S}$ .
- 2- A four-stage amplifier has a lower 3-dB frequency for an individual stage of  $f_1=40\text{ Hz}$ . What is the value of  $f_1$  for this full amplifier?
- 3- The feedback capacitance of an inverting amplifier is  $20\text{ pF}$ . What is the Miller capacitance at the input and the output if the gain of the amplifier is  $-120$ ?
- 4- Discuss cross-over distortion and state how we can solve it.

**Question (3) (22 Marks)**

- 1- For the small-signal amplifier circuit of Fig. 1,
  - a. Determine  $r_e$ ,  $Z_i$  and  $A_v$ .
  - b. Determine the lower and higher cut-off frequencies.
  - c. Sketch the low-frequency and the high-frequency responses.
  - d. Sketch the phase response.
- 2- For the power amplifier circuit of Fig. 2 and for an input of  $10\text{ V rms}$ , calculate
  - a. The input power
  - b. The output power
  - c. The power handled by each output transistor
  - d. The circuit efficiency

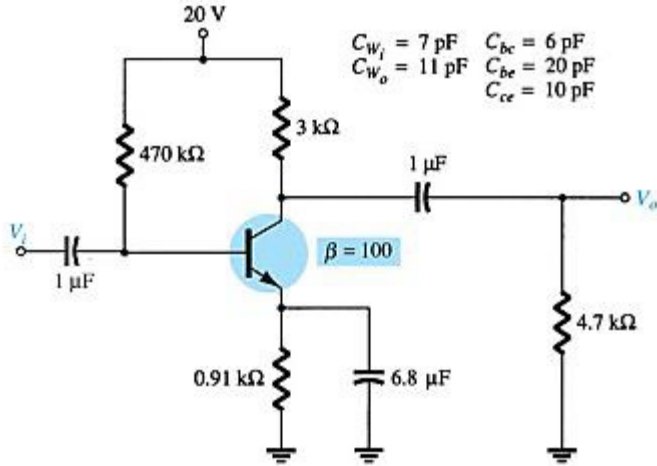


Fig. 1

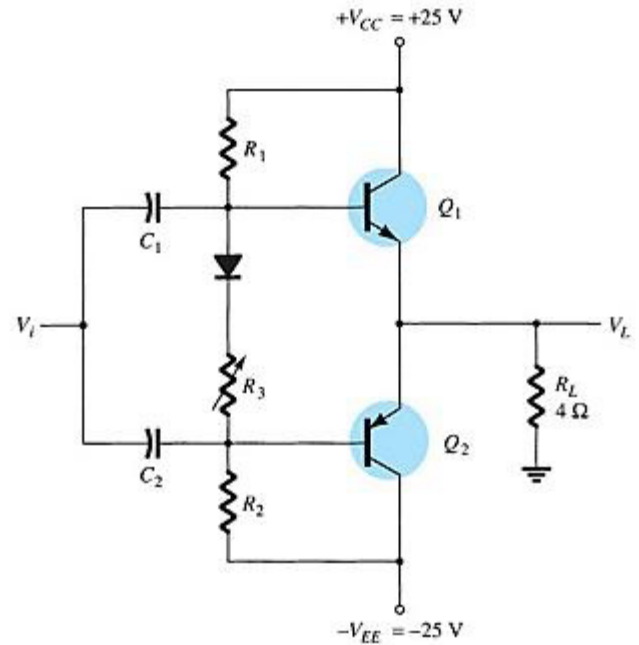


Fig. 2

**Question (4) (16 Marks)**

- 1- What are the conditions required to sustain oscillation? And what is the condition required for oscillation to begin?
- 2- What are the purposes of a tuned amplifier? Give examples of its applications.
- 3- A tuned circuit has resonance frequency of 800 kHz and a bandwidth of 10 kHz. What is the value of its Q-factor? What's the sharpness of resonance?
- 4- Calculate the resonance frequency of a Hartley oscillator with the elements of the tank circuit as  $L_1 = 1.5$  mH,  $L_2 = 10$  mH and  $C = 470$  pF.

**Question (5) (20 Marks)**

- 1- Design a two stages RC coupled BJT Audio Amplifier to provide a gain of 60 dB to a typical dynamic microphone signal with frequency ranges from 300 Hz to 3.5 KHz.
- 2- Design an 850 kHz local oscillator to be used in modulator circuits.

***Good Luck,  
Dr. Ahmad El-Banna***

# SIGNIFICANT EQUATIONS

**1 Semiconductor Diodes**  $W = QV$ ,  $1 \text{ eV} = 1.6 \times 10^{-19} \text{ J}$ ,  $I_D = I_s (e^{V_D/nV_T} - 1)$ ,  $V_T = kT/q$ ,  $T_K = T_C + 273^\circ$ ,  
 $k = 1.38 \times 10^{-23} \text{ J/K}$ ,  $V_K \cong 0.7 \text{ V (Si)}$ ,  $V_K \cong 0.3 \text{ V (Ge)}$ ,  $V_K \cong 1.2 \text{ V (GaAs)}$ ,  $R_D = V_D/I_D$ ,  $r_d = 26 \text{ mV}/I_D$ ,  $r_{av} = \Delta V_d/\Delta I_d|_{\text{pt. to pt.}}$ ,  
 $P_D = V_D I_D$ ,  $T_C = (\Delta V_Z/V_Z)/(T_1 - T_0) \times 100\%/^\circ\text{C}$

**2 Diode Applications** Silicon:  $V_K \cong 0.7 \text{ V}$ , germanium:  $V_K \cong 0.3 \text{ V}$ , GaAs:  $V_K \cong 1.2 \text{ V}$ ; half-wave:  $V_{dc} = 0.318 V_m$ ;  
 full-wave:  $V_{dc} = 0.636 V_m$

**3 Bipolar Junction Transistors**  $I_E = I_C + I_B$ ,  $I_C = I_{C_{\text{majority}}} + I_{C_{\text{minority}}}$ ,  $I_C \cong I_E$ ,  $V_{BE} = 0.7 \text{ V}$ ,  $\alpha_{dc} = I_C/I_E$ ,  $I_C = \alpha I_E + I_{CBO}$ ,  
 $\alpha_{ac} = \Delta I_C/\Delta I_E$ ,  $I_{CEO} = I_{CBO}/(1 - \alpha)$ ,  $\beta_{dc} = I_C/I_B$ ,  $\beta_{ac} = \Delta I_C/\Delta I_B$ ,  $\alpha = \beta/(\beta + 1)$ ,  $\beta = \alpha/(1 - \alpha)$ ,  $I_C = \beta I_B$ ,  $I_E = (\beta + 1)I_B$ ,  
 $P_{C_{\text{max}}} = V_{CE} I_C$

**4 DC Biasing—BJTs** In general:  $V_{BE} = 0.7 \text{ V}$ ,  $I_C \cong I_E$ ,  $I_C = \beta I_B$ ; fixed-bias:  $I_B = (V_{CC} - V_{BE})/R_B$ ,  $V_{CE} = V_{CC} - I_C R_C$ ,  
 $I_{C_{\text{sat}}} = V_{CC}/R_C$ ; emitter-stabilized:  $I_B = (V_{CC} - V_{BE})/(R_B + (\beta + 1)R_E)$ ,  $R_i = (\beta + 1)R_E$ ,  $V_{CE} = V_{CC} - I_C(R_C + R_E)$ ,  
 $I_{C_{\text{sat}}} = V_{CC}/(R_C + R_E)$ ; voltage-divider: exact:  $R_{Th} = R_1 \parallel R_2$ ,  $E_{Th} = R_2 V_{CC}/(R_1 + R_2)$ ,  $I_B = (E_{Th} - V_{BE})/(R_{Th} + (\beta + 1)R_E)$ ,  
 $V_{CE} = V_{CC} - I_C(R_C + R_E)$ , approximate:  $\beta R_E \geq 10R_2$ ,  $V_B = R_2 V_{CC}/(R_1 + R_2)$ ,  $V_E = V_B - V_{BE}$ ,  $I_C \cong I_E = V_E/R_E$ ; voltage-feedback:  
 $I_B = (V_{CC} - V_{BE})/(R_B + \beta(R_C + R_E))$ ; common-base:  $I_B = (V_{EE} - V_{BE})/R_E$ ; switching transistors:  $t_{on} = t_r + t_d$ ,  $t_{off} = t_s + t_f$ ;  
 stability:  $S(I_{CO}) = \Delta I_C/\Delta I_{CO}$ ; fixed-bias:  $S(I_{CO}) = \beta + 1$ ; emitter-bias:  $S(I_{CO}) = (\beta + 1)(1 + R_B/R_E)/(1 + \beta + R_B/R_E)$ ;  
 voltage-divider:  $S(I_{CO}) = (\beta + 1)(1 + R_{Th}/R_E)/(1 + \beta + R_{Th}/R_E)$ ; feedback-bias:  $S(I_{CO}) = (\beta + 1)(1 + R_B/R_C)/(1 + \beta + R_B/R_C)$ ,  
 $S(V_{BE}) = \Delta I_C/\Delta V_{BE}$ ; fixed-bias:  $S(V_{BE}) = -\beta/R_B$ ; emitter-bias:  $S(V_{BE}) = -\beta/(R_B + (\beta + 1)R_E)$ ; voltage-divider:  $S(V_{BE}) =$   
 $-\beta/(R_{Th} + (\beta + 1)R_E)$ ; feedback bias:  $S(V_{BE}) = -\beta/(R_B + (\beta + 1)R_C)$ ,  $S(\beta) = \Delta I_C/\Delta \beta$ ; fixed-bias:  $S(\beta) = I_{C_1}/\beta_1$ ;  
 emitter-bias:  $S(\beta) = I_{C_1}(1 + R_B/R_E)/(\beta_1(1 + \beta_2 + R_B/R_E))$ ; voltage-divider:  $S(\beta) = I_{C_1}(1 + R_{Th}/R_E)/(\beta_1(1 + \beta_2 + R_{Th}/R_E))$ ;  
 feedback-bias:  $S(\beta) = I_{C_1}(1 + R_B/R_C)/(\beta_1(1 + \beta_2 + R_B/R_C))$ ,  $\Delta I_C = S(I_{CO}) \Delta I_{CO} + S(V_{BE}) \Delta V_{BE} + S(\beta) \Delta \beta$

**5 BJT AC Analysis**  $r_e = 26 \text{ mV}/I_E$ ; CE fixed-bias:  $Z_i \cong \beta r_e$ ,  $Z_o \cong R_C$ ,  $A_v = -R_C/r_e$ ; voltage-divider bias:  $Z_i = R_1 \parallel R_2 \parallel \beta r_e$ ,  $Z_o \cong R_C$ ,  
 $A_v = -R_C/r_e$ ; CE emitter-bias:  $Z_i \cong R_B \parallel \beta R_E$ ,  $Z_o \cong R_C$ ,  $A_v \cong -R_C/R_E$ ; emitter-follower:  $Z_i \cong R_B \parallel \beta R_E$ ,  $Z_o \cong r_e$ ,  $A_v \cong 1$ ;  
 common-base:  $Z_i \cong R_E \parallel r_e$ ,  $Z_o \cong R_C$ ,  $A_v \cong R_C/r_e$ ; collector feedback:  $Z_i \cong r_e/(1/\beta + R_C/R_F)$ ,  $Z_o \cong R_C \parallel R_F$ ,  $A_v = -R_C/r_e$ ; collector  
 dc feedback:  $Z_i \cong R_{F_1} \parallel \beta r_e$ ,  $Z_o \cong R_C \parallel R_{F_2}$ ,  $A_v = -(R_{F_2} \parallel R_C)/r_e$ ; effect of load impedance:  $A_v = R_L A_{v_{NL}}/(R_L + R_o)$ ,  $A_i = -A_v Z_i/R_L$ ;  
 effect of source impedance:  $V_i = R_i V_s/(R_i + R_s)$ ,  $A_{v_s} = R_i A_{v_{NL}}/(R_i + R_s)$ ,  $I_s = V_s/(R_s + R_i)$ ; combined effect of load and source  
 impedance:  $A_v = R_L A_{v_{NL}}/(R_L + R_o)$ ,  $A_{v_s} = (R_i/(R_i + R_s))(R_L/(R_L + R_o))A_{v_{NL}}$ ,  $A_i = -A_v R_i/R_L$ ,  $A_{i_s} = -A_{v_s}(R_s + R_i)/R_L$ ; cascode  
 connection:  $A_v = A_{v_1} A_{v_2}$ ; Darlington connection:  $\beta_D = \beta_1 \beta_2$ ; emitter-follower configuration:  $I_B = (V_{CC} - V_{BE})/(R_B + \beta_D R_E)$ ,  
 $I_C \cong I_E \cong \beta_D I_B$ ,  $Z_i = R_B \parallel \beta_1 \beta_2 R_E$ ,  $A_i = \beta_D R_B/(R_B + \beta_D R_E)$ ,  $A_v \cong 1$ ,  $Z_o = r_{e_1}/\beta_2 + r_{e_2}$ ; basic amplifier configuration:  $Z_i = R_1 \parallel R_2 \parallel Z'_i$ ,  
 $Z'_i = \beta_1(r_{e_1} + \beta_2 r_{e_2})$ ,  $A_i = \beta_D(R_1 \parallel R_2)/(R_1 \parallel R_2 + Z'_i)$ ,  $A_v = \beta_D R_C/Z'_i$ ,  $Z_o = R_C \parallel r_{o_2}$ ; feedback pair:  $I_{B_1} = (V_{CC} - V_{BE_1})/(R_B + \beta_1 \beta_2 R_C)$ ,  
 $Z_i = R_B \parallel Z'_i$ ,  $Z'_i = \beta_1 r_{e_1} + \beta_1 \beta_2 R_C$ ,  $A_i = -\beta_1 \beta_2 R_B/(R_B + \beta_1 \beta_2 R_C)$ ,  $A_v = \beta_2 R_C/(r_e + \beta_2 R_C) \cong 1$ ,  $Z_o \cong r_{e_1}/\beta_2$ .

**6 Field-Effect Transistors**  $I_G = 0 \text{ A}$ ,  $I_D = I_{DSS}(1 - V_{GS}/V_P)^2$ ,  $I_D = I_s$ ,  $V_{GS} = V_P(1 - \sqrt{I_D/I_{DSS}})$ ,  $I_D = I_{DSS}/4$  (if  $V_{GS} = V_P/2$ ),  
 $I_D = I_{DSS}/2$  (if  $V_{GS} \cong 0.3 V_P$ ),  $P_D = V_{DS} I_D$ ,  $r_d = r_o/(1 - V_{GS}/V_P)^2$ ; MOSFET:  $I_D = k(V_{GS} - V_T)^2$ ,  $k = I_{D(on)}/(V_{GS(on)} - V_T)^2$

**7 FET Biasing** Fixed-bias:  $V_{GS} = -V_{GG}$ ,  $V_{DS} = V_{DD} - I_D R_D$ ; self-bias:  $V_{GS} = -I_D R_S$ ,  $V_{DS} = V_{DD} - I_D(R_S + R_D)$ ,  $V_S = I_D R_S$ ;  
 voltage-divider:  $V_G = R_2 V_{DD}/(R_1 + R_2)$ ,  $V_{GS} = V_G - I_D R_S$ ,  $V_{DS} = V_{DD} - I_D(R_D + R_S)$ ; common-gate configuration:  $V_{GS} = V_{SS} - I_D R_S$ ,  
 $V_{DS} = V_{DD} + V_{SS} - I_D(R_D + R_S)$ ; special case:  $V_{GS_Q} = 0 \text{ V}$ :  $I_{D_Q} = I_{DSS}$ ,  $V_{DS} = V_{DD} - I_D R_D$ ,  $V_D = V_{DS}$ ,  $V_S = 0 \text{ V}$ . enhancement-type  
 MOSFET:  $I_D = k(V_{GS} - V_{GS(Th)})^2$ ,  $k = I_{D(on)}/(V_{GS(on)} - V_{GS(Th)})^2$ ; feedback bias:  $V_{DS} = V_{GS}$ ,  $V_{GS} = V_{DD} - I_D R_D$ ; voltage-divider:  
 $V_G = R_2 V_{DD}/(R_1 + R_2)$ ,  $V_{GS} = V_G - I_D R_S$ ; universal curve:  $m = |V_P|/I_{DSS} R_S$ ,  $M = m \times V_G/|V_P|$ ,  $V_G = R_2 V_{DD}/(R_1 + R_2)$

**8 FET Amplifiers**  $g_m = y_{fs} = \Delta I_D/\Delta V_{GS}$ ,  $g_{m0} = 2I_{DSS}/|V_P|$ ,  $g_m = g_{m0}(1 - V_{GS}/V_P)$ ,  $g_m = g_{m0} \sqrt{I_D/I_{DSS}}$ ,  $r_d = 1/y_{os} =$   
 $\Delta V_{DS}/\Delta I_D|_{V_{GS}=\text{constant}}$ ; fixed-bias:  $Z_i = R_G$ ,  $Z_o \cong R_D$ ,  $A_v = -g_m R_D$ ; self-bias (bypassed  $R_s$ ):  $Z_i = R_G$ ,  $Z_o \cong R_D$ ,  $A_v = -g_m R_D$ ; self-bias  
 (unbypassed  $R_s$ ):  $Z_i = R_G$ ,  $Z_o = R_D$ ,  $A_v \cong -g_m R_D/(1 + g_m R_s)$ ; voltage-divider bias:  $Z_i = R_1 \parallel R_2$ ,  $Z_o = R_D$ ,  $A_v = -g_m R_D$ ; source follower:  
 $Z_i = R_G$ ,  $Z_o = R_S \parallel 1/g_m$ ,  $A_v \cong g_m R_S/(1 + g_m R_S)$ ; common-gate:  $Z_i = R_S \parallel 1/g_m$ ,  $Z_o \cong R_D$ ,  $A_v = g_m R_D$ ; enhancement-type MOSFETs:  
 $g_m = 2k(V_{GS_Q} - V_{GS(Th)})$ ; drain-feedback configuration:  $Z_i \cong R_F/(1 + g_m R_D)$ ,  $Z_o \cong R_D$ ,  $A_v \cong -g_m R_D$ ; voltage-divider bias:  $Z_i = R_1 \parallel R_2$ ,  
 $Z_o \cong R_D$ ,  $A_v \cong -g_m R_D$ .

**9 BJT and JFET Frequency Response**  $\log_e a = 2.3 \log_{10} a$ ,  $\log_{10} 1 = 0$ ,  $\log_{10} a/b = \log_{10} a - \log_{10} b$ ,  $\log_{10} 1/b = -\log_{10} b$ ,  
 $\log_{10} ab = \log_{10} a + \log_{10} b$ ,  $G_{dB} = 10 \log_{10} P_2/P_1$ ,  $G_{dBm} = 10 \log_{10} P_2/1 \text{ mW}|_{600 \Omega}$ ,  $G_{dB} = 20 \log_{10} V_2/V_1$ ,  
 $G_{dB_T} = G_{dB_1} + G_{dB_2} + \dots + G_{dB_n}$ ,  $P_{oHPF} = 0.5 P_{o\text{mid}}$ ,  $BW = f_1 - f_2$ ; low frequency (BJT):  $f_{LS} = 1/2\pi(R_s + R_i)C_s$ ,  
 $f_{LC} = 1/2\pi(R_o + R_L)C_C$ ,  $f_{LE} = 1/2\pi R_e C_E$ ,  $R_e = R_E \parallel (R_s/\beta + r_e)$ ,  $R_s' = R_s \parallel R_1 \parallel R_2$ , FET:  $f_{LG} = 1/2\pi(R_{sig} + R_i)C_G$ ,  
 $f_{LC} = 1/2\pi(R_o + R_L)C_C$ ,  $f_{LS} = 1/2\pi R_{eq} C_S$ ,  $R_{eq} = R_S \parallel 1/g_m(r_d \cong \infty \Omega)$ ; Miller effect:  $C_{M_i} = (1 - A_v)C_f$ ,  $C_{M_o} = (1 - 1/A_v)C_f$ ;  
high frequency (BJT):  $f_{H_i} = 1/2\pi R_{Th_i} C_i$ ,  $R_{Th_i} = R_s \parallel R_1 \parallel R_2 \parallel R_i$ ,  $C_i = C_{w_i} + C_{be} + (1 - A_v)C_{bc}$ ,  $f_{H_o} = 1/2\pi R_{Th_o} C_o$ ,  
 $R_{Th_o} = R_C \parallel R_L \parallel r_o$ ,  $C_o = C_{W_o} + C_{ce} + C_{M_o}$ ,  $f_{\beta} \cong 1/2\pi \beta_{mid} r_e (C_{be} + C_{bc})$ ,  $f_T = \beta_{mid} f_{\beta}$ ; FET:  $f_{H_i} = 1/2\pi R_{Th_i} C_i$ ,  $R_{Th_i} = R_{sig} \parallel R_G$ ,  
 $C_i = C_{W_i} + C_{gs} + C_{M_i}$ ,  $C_{M_i} = (1 - A_v)C_{gd} f_{H_o} = 1/2\pi R_{Th_o} C_o$ ,  $R_{Th_o} = R_D \parallel R_L \parallel r_d$ ,  $C_o = C_{W_o} + C_{ds} + C_{M_o}$ ,  $C_{M_o} = (1 - 1/A_v)C_{gd}$ ;  
multistage:  $f_1' = f_1/\sqrt{2^{1/n} - 1}$ ,  $f_2' = (\sqrt{2^{1/n} - 1})f_2$ ; square-wave testing:  $f_{H_i} = 0.35/t_r$ , % tilt =  $P\% = ((V - V')/V) \times 100\%$ ,  
 $f_{L_o} = (P/\pi)f_s$

**10 Operational Amplifiers**  $CMRR = A_d/A_c$ ;  $CMRR(\log) = 20 \log_{10}(A_d/A_c)$ ; constant-gain multiplier:  $V_o/V_1 = -R_f/R_1$ ;  
noninverting amplifier:  $V_o/V_1 = 1 + R_f/R_1$ ; unity follower:  $V_o = V_1$ ; summing amplifier:  $V_o = -[(R_f/R_1)V_1 + (R_f/R_2)V_2 + (R_f/R_3)V_3]$ ;  
integrator:  $v_o(t) = -(1/R_1 C_1) \int v_1 dt$

**11 Op-Amp Applications** Constant-gain multiplier:  $A = -R_f/R_1$ ; noninverting:  $A = 1 + R_f/R_1$ ; voltage summing:  
 $V_o = -[(R_f/R_1)V_1 + (R_f/R_2)V_2 + (R_f/R_3)V_3]$ ; high-pass active filter:  $f_{oL} = 1/2\pi R_1 C_1$ ; low-pass active filter:  $f_{oH} = 1/2\pi R_1 C_1$

## 12 Power Amplifiers

Power in:  $P_i = V_{CC} I_{CQ}$

power out:  $P_o = V_{CE} I_C = I_C^2 R_C = V_{CE}^2 / R_C$  rms  
 $= V_{CE} I_C / 2 = (I_C^2 / 2) R_C = V_{CE}^2 / (2 R_C)$  peak  
 $= V_{CE} I_C / 8 = (I_C^2 / 8) R_C = V_{CE}^2 / (8 R_C)$  peak-to-peak

efficiency:  $\% \eta = (P_o / P_i) \times 100\%$ ; maximum efficiency: Class A, series-fed = 25%; Class A, transformer-coupled = 50%; Class B,  
push-pull = 78.5%; transformer relations:  $V_2/V_1 = N_2/N_1 = I_1/I_2$ ,  $R_2 = (N_2/N_1)^2 R_1$ ; power output:  $P_o = [(V_{CE\text{max}} - V_{CE\text{min}}) (I_{C\text{max}} - I_{C\text{min}})] / 8$ ;  
class B power amplifier:  $P_i = V_{CC} [(2/\pi) I_{\text{peak}}]$ ;  $P_o = V_L^2(\text{peak}) / (2 R_L)$ ;  $\% \eta = (\pi/4) [V_L(\text{peak}) / V_{CC}] \times 100\%$ ;  
 $P_Q = P_{2Q} / 2 = (P_i - P_o) / 2$ ; maximum  $P_o = V_{CC}^2 / 2 R_L$ ; maximum  $P_i = 2 V_{CC}^2 / \pi R_L$ ; maximum  $P_{2Q} = 2 V_{CC}^2 / \pi^2 R_L$ ; % total harmonic  
distortion (% THD) =  $\sqrt{D_2^2 + D_3^2 + D_4^2 + \dots} \times 100\%$ ; heat-sink:  $T_j = P_D \theta_{JA} + T_A$ ,  $\theta_{JA} = 40^\circ \text{C/W}$  (free air);  
 $P_D = (T_j - T_A) / (\theta_{JC} + \theta_{CS} + \theta_{SA})$

**13 Linear-Digital ICs** Ladder network:  $V_o = [(D_0 \times 2^0 + D_1 \times 2^1 + D_2 \times 2^2 + \dots + D_n \times 2^n) / 2^n] V_{\text{ref}}$ ;  
555 oscillator:  $f = 1.44(R_A + 2R_B)C$ ; 555 monostable:  $T_{\text{high}} = 1.1 R_A C$ ; VCO:  $f_o = (2/R_1 C_1) [(V^+ - V_C) / V^+]$ ; phase-  
locked loop (PLL):  $f_o = 0.3/R_1 C_1$ ,  $f_L = \pm 8 f_o / V$ ,  $f_C = \pm (1/2\pi) \sqrt{2\pi f_L / (3.6 \times 10^3) C_2}$

**14 Feedback and Oscillator Circuits**  $A_f = A/(1 + \beta A)$ ; series feedback;  $Z_{if} = Z_f(1 + \beta A)$ ; shunt feedback:  $Z_{if} = Z_i/(1 + \beta A)$ ;  
voltage feedback:  $Z_{of} = Z_o/(1 + \beta A)$ ; current feedback;  $Z_{of} = Z_o(1 + \beta A)$ ; gain stability:  $dA_f/A_f = 1/(|1 + \beta A|)(dA/A)$ ; oscillator;  
 $\beta A = 1$ ; phase shift:  $f = 1/2\pi RC\sqrt{6}$ ,  $\beta = 1/29$ ,  $A > 29$ ; FET phase shift:  $|A| = g_m R_L$ ,  $R_L = R_D r_d / (R_D + r_d)$ ; transistor phase shift:  
 $f = (1/2\pi RC)[1/\sqrt{6 + 4(R_C/R)}]$ ,  $h_{fe} > 23 + 29(R_C/R) + 4(R/R_C)$ ; Wien bridge:  $R_3/R_4 = R_1/R_2 + C_2/C_1$ ,  $f_o = 1/2\pi \sqrt{R_1 C_1 R_2 C_2}$ ;  
tuned:  $f_o = 1/2\pi \sqrt{L C_{eq}}$ ,  $C_{eq} = C_1 C_2 / (C_1 + C_2)$ , Hartley:  $L_{eq} = L_1 + L_2 + 2M$ ,  $f_o = 1/2\pi \sqrt{L_{eq} C}$

**15 Power Supplies (Voltage Regulators)** Filters:  $r = V_r(\text{rms}) / V_{dc} \times 100\%$ , V.R. =  $(V_{NL} - V_{FL}) / V_{FL} \times 100\%$ ,  $V_{dc} = V_m - V_r(\text{p-p})/2$ ,  
 $V_r(\text{rms}) = V_r(\text{p-p})/2\sqrt{3}$ ,  $V_r(\text{rms}) \cong (I_{dc}/4\sqrt{3})(V_{dc}/V_m)$ ; full-wave, light load  $V_r(\text{rms}) = 2.4 I_{dc}/C$ ,  $V_{dc} = V_m - 4.17 I_{dc}/C$ ,  $r =$   
 $(2.4 I_{dc} C V_{dc}) \times 100\% = 2.4/R_L C \times 100\%$ ,  $I_{\text{peak}} = T/T_1 \times I_{dc}$ ; RC filter:  $V_{dc} = R_L V_{dc} / (R + R_L)$ ,  $X_C = 2.653/C(\text{half-wave})$ ,  $X_C =$   
 $1.326/C(\text{full-wave})$ ,  $V_r(\text{rms}) = (X_C/\sqrt{R^2 + X_C^2})$ ; regulators:  $IR = (I_{NL} - I_{FL})/I_{FL} \times 100\%$ ,  $V_L = V_Z(1 + R_1/R_2)$ ,  $V_o =$   
 $V_{\text{ref}}(1 + R_2/R_1) + I_{\text{adj}} R_2$

**16 Other Two-Terminal Devices** Varactor diode:  $C_T = C(0)/(1 + |V_r/V_T|^n)$ ,  $TC_C = (\Delta C/C_o)(T_1 - T_0) \times 100\%$ ; photodiode:  
 $W = h\nu$ ,  $\lambda = \nu/f$ ,  $1 \text{ lm} = 1.496 \times 10^{-10} \text{ W}$ ,  $1 \text{ \AA} = 10^{-10} \text{ m}$ ,  $1 \text{ fc} = 1 \text{ lm}/\text{ft}^2 = 1.609 \times 10^{-9} \text{ W}/\text{m}^2$

**17 npn and Other Devices** Diac:  $V_{BR_1} = V_{BR_2} \pm 0.1 V_{BR_2}$  UJT:  $R_{BB} = (R_{B_1} + R_{B_2})|_{I_E=0}$ ,  $V_{R_{B_1}} = \eta V_{BB}|_{I_E=0}$ ,  
 $\eta = R_{B_1}/(R_{B_1} + R_{B_2})|_{I_E=0}$ ,  $V_P = \eta V_{BB} + V_D$ ; phototransistor:  $I_C \cong h_{fe} I_{\lambda}$ ; PUT:  $\eta = R_{B_1}/(R_{B_1} + R_{B_2})$ ,  $V_P = \eta V_{BB} + V_D$