

**Mid Term Exam (Open Book)**

**Time Allowed: 75 min**

**[Sample A]**

**(1) For the voltage-divider biasing circuit, discuss the condition required to perform the approximate analysis.**

**(2) Design a BJT Audio Amplifier with following specifications:**

- The amplifier consists of two direct coupled stages with total gain of 57 dB.
- It uses a capacitor to couple a microphone signal with internal resistance of 1k $\Omega$  and frequency band between 300 Hz and 3.5 KHz.
- It drives an 8  $\Omega$  speaker through a coupling transformer of 1:3 turns ratio.
- The speaker signal should be in-phase with the microphone one.

**Plot the low frequency response of the first stage of that amplifier.**

Good Luck,  
Dr. Ahmad El-Banna

**Mid Term Exam (Open Book)**

**Time Allowed: 75 min**

**[Sample B]**

**(1) Discuss the condition required to use a bjt transistor in a switching circuit.**

**(2) Design a BJT Audio Amplifier with following specifications:**

- The amplifier consists of two direct coupled stages with total gain of 50 dB.
- It uses a capacitor to couple a microphone signal with internal resistance of 1k $\Omega$  and frequency band between 400 Hz and 4 KHz.
- It drives a 4  $\Omega$  speaker through a coupling transformer of 1:2 turns ratio.
- The speaker signal should be out of phase with the microphone one.

**Plot the low frequency response of the first stage of that amplifier.**

Good Luck,  
Dr. Ahmad El-Banna