



BENHA UNIVERSITY
FACULTY OF ENGINEERING AT SHOUBRA

Post-Graduate
ECE-606
CAD of Electronics

Lecture #2
VHDL Basics

Instructor:
Dr. Ahmad El-Banna




DECEMBER 2014

© Ahmad El-Banna

Agenda

Quick introduction to VHDL

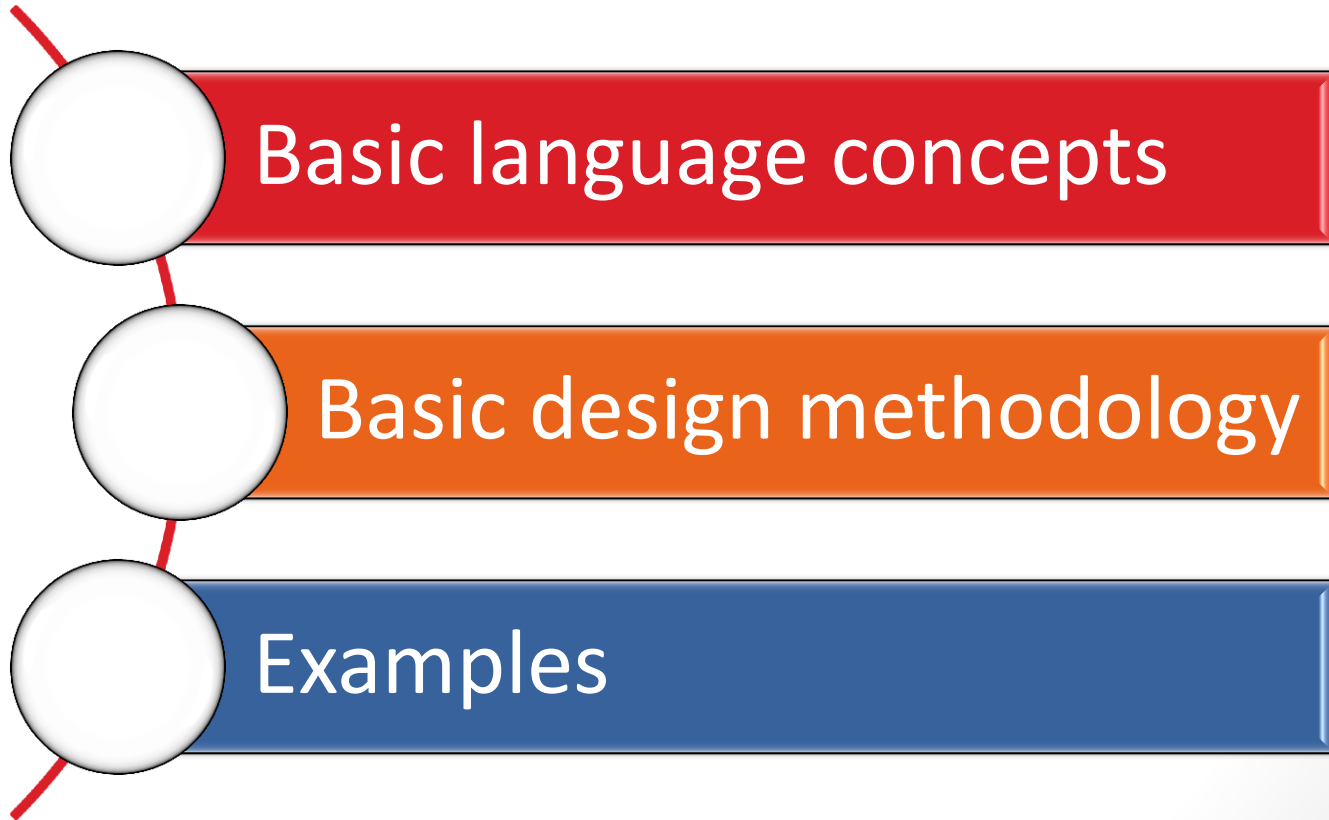

VHDL

- Hardware description languages (HDL)
 - Language to describe hardware
 - Two popular languages
 - VHDL: **V**ery **H**igh Speed Integrated Circuits **H**ardware **D**escription Language
 - Developed by DOD from 1983
 - IEEE Standard 1076-1987/1993/200x
 - Based on the ADA language
 - Verilog
 - IEEE Standard 1364-1995/2001/2005
 - Based on the C language
- Applications of HDL:
 - Model and document digital systems
 - Different levels of abstraction
 - Behavioral, structural, etc.
 - Verify design
 - Synthesize circuits
 - Convert from higher abstraction levels to lower abstraction levels

Modeling Digital Systems


- VHDL is for coding models of a digital system...
- Reasons for modeling
 - requirements specification
 - documentation
 - testing using simulation
 - formal verification
 - synthesis
 - class assignments
- Goal
 - most 'reliable' design process, with minimum cost and time
 - avoid design errors!

Basic VHDL Concepts

- Main Terms
 - Interfaces -- i.e. ports
 - Behavior
 - Structure
 - Test Benches
 - Analysis, simulation
 - Synthesis
- VHDL is a programming language that allows one to model and develop complex digital systems in a dynamic environment.
- Object Oriented methodology -- modules can be used and reused.
- Allows you to designate in/out ports (bits) and specify behavior or response of the system.
- But VHDL is NOT C ...
There are some similarities, as with any programming language, but syntax and logic are quite different; so get over it !!



3 ways to DO IT -- the VHDL way

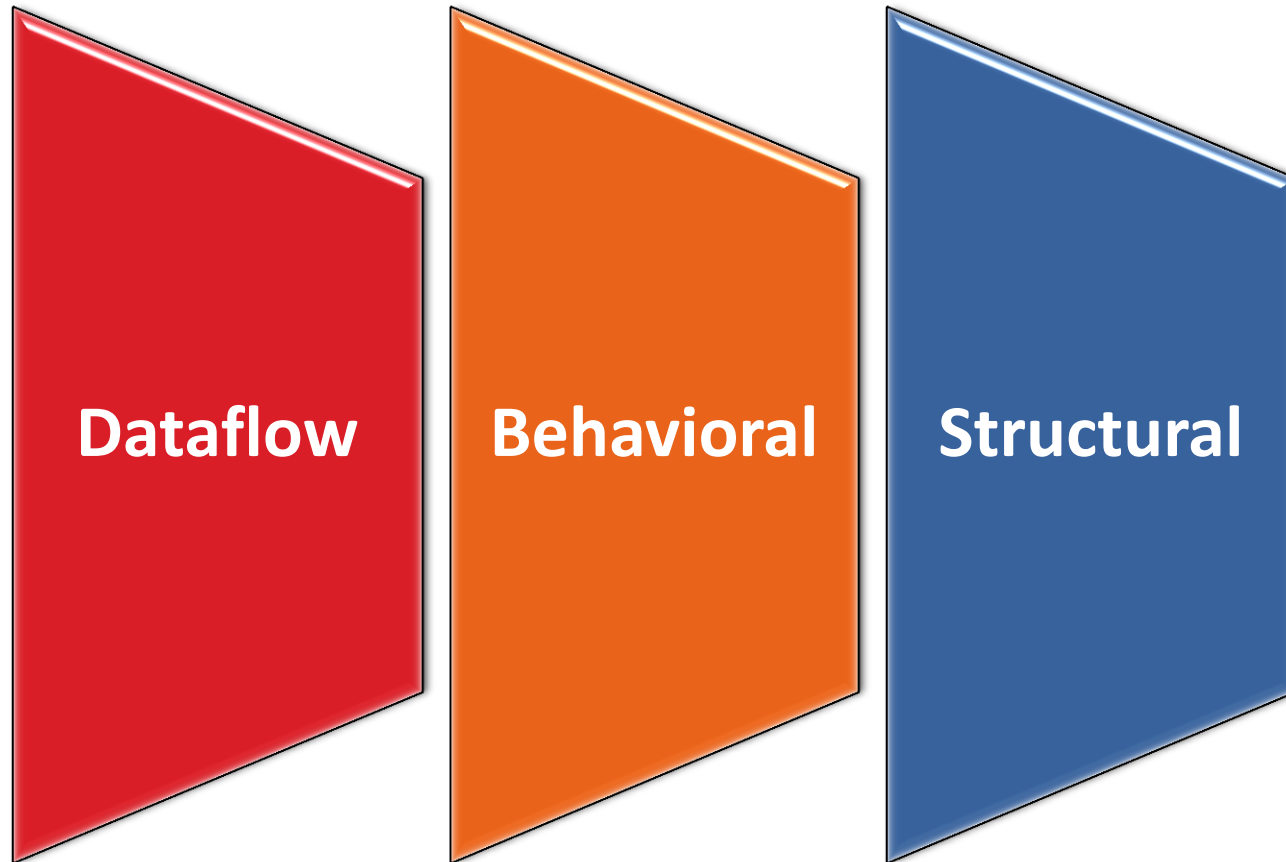

Modeling the Dataflow way

- uses statements that defines the actual flow of data.....

such as,

$x \leq y$ -- this is NOT less than equal to
 -- told you its not C

this assigns the boolean signal x to the value of boolean signal y... i.e.

$x = y$

this will occur whenever y changes....


Jumping right in to a Model

- lets look at a d - flip-flop model -- doing it the dataflow way.....
ignore the extra junk for now --

```
entity dff_flow is
  port (
    d      :in  bit;
    rn     :in  bit;
    clrn   :in  bit;
    q      :out bit;
    qbar   :out bit;
  );
end dff_flow;
architecture arch1 of dff_flow is
begin
  q <= not prn Or (clrn And d);  % this is the DATAFLOW %
  qbar <= prn And (not clrn Or not d);  % STUFF %
end arch1;
```


Modeling Interfaces

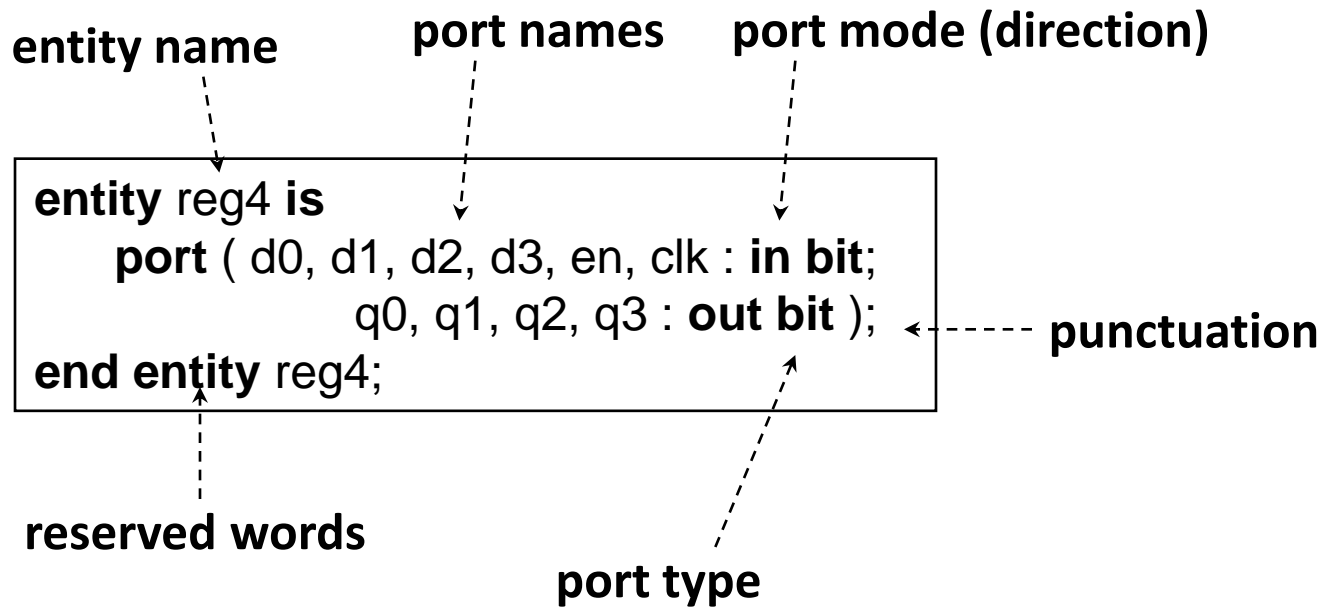
- *Entity* declaration
 - describes the input/output *ports* of a module



Modeling the Behavior way

- *Architecture body*
 - describes an implementation of an entity
 - may be several per entity
- *Behavioral architecture*
 - describes the algorithm performed by the module
 - contains
 - *process statements*, each containing
 - *sequential statements*, including
 - *signal assignment statements* and
 - *wait statements*

Example

 

- Example: my_ckt
 - Inputs: A, B, C
 - Outputs: X, Y
- VHDL description:

```
entity my_ckt is
port (
    A: in bit;
    B: in bit;
    S: in bit;
    X: out bit;
    Y: out bit);
end my_ckt ;
```

□ Functional Spec.

- Behavior for output X:
 - When S = 0
X <= A
 - When S = 1
X <= B
- Behavior for output Y:
 - When X = 0 and S = 0
Y <= '1'
 - Else
Y <= '0'

VHDL Architecture

- VHDL description (sequential behavior):

```
architecture arch_name of my_ckt is
begin
  p1: process (A,B,S)
  begin
    if (S='0') then
      X <= A;
    else
      X <= B;
    end if;

    if ((X = '0') and (S = '0')) then
      Y <= '1';
    else
      Y <= '0';
    end if;

  end process p1;
end;
```

Error: Signals defined as output ports can only be driven and not read

VHDL Architecture..

```
architecture behav_seq of my_ckt is
```

```
signal Xtmp: bit;
```

```
begin
```

```
  p1: process (A,B,S,Xtmp)
```

```
    begin
```

```
      if (S='0') then
```

```
        Xtmp <= A;
```

```
      else
```

```
        Xtmp <= B;
```

```
      end if;
```

```
      if ((Xtmp = '0') and (S = '0')) then
```

```
        Y <= '1';
```

```
      else
```

```
        Y <= '0';
```

```
      end if;
```

```
      X <= Xtmp;
```

```
    end process p1;
```

```
end;
```

Signals can only be defined in this place before the **begin** keyword

General rule: Include all signals in the sensitivity list of the process which either appear in relational comparisons or on the right side of the assignment operator inside the process construct.

In our example:

Xtmp and **S** occur in relational comparisons
A, **B** and **Xtmp** occur on the right side of the assignment operators

VHDL Architecture...

- VHDL description (concurrent behavior):

```
architecture behav_conc of my_ckt is
```

```
    signal Xtmp: bit;
```

```
begin
```

```
    Xtmp <= A when (S='0') else  
           B;
```

```
    Y <= '1' when ((Xtmp = '0') and (S = '0')) else  
           '0';
```


```
    X <= Xtmp;
```

```
end ;
```

Modeling the Structural way

- *Structural* architecture
 - implements the module as a composition of subsystems
 - contains
 - *signal declarations*, for internal interconnections
 - the entity ports are also treated as signals
 - *component instances*
 - instances of previously declared entity/architecture pairs
 - *port maps* in component instances
 - connect signals to component ports

Structural way Example

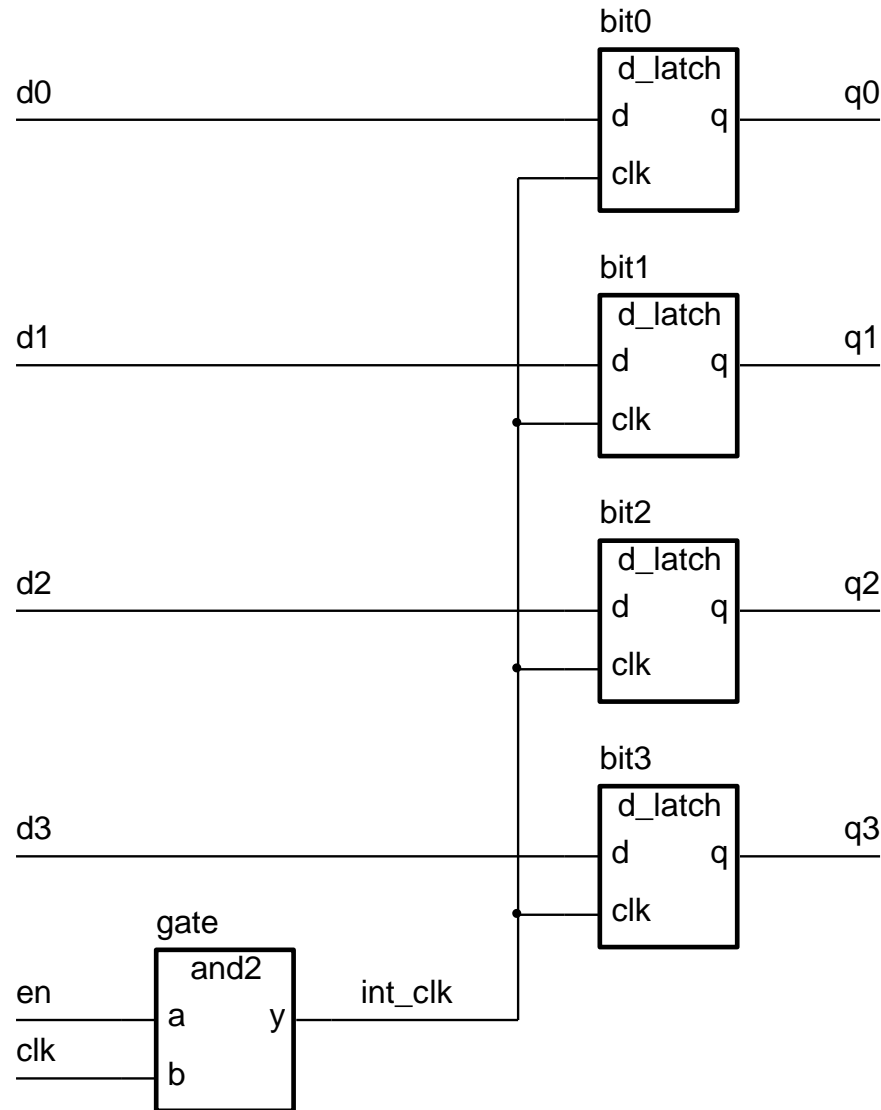

Structural way..

- First declare D-latch and and-gate entities and architectures

notice semicolon placements -- odd as it is, omit from last statement

```
entity d_latch is  
    port ( d, clk : in bit; q : out bit );  
end entity d_latch;
```

```
architecture basic of d_latch is  
begin
```

```
    process (clk, d)  
    begin  
        if clk = '1' then  
            q <= d after 2 ns;  
        end if;  
    end process;
```

```
end basic;
```

```
entity and2 is  
    port ( a, b : in bit; y : out bit );  
end entity and2;
```

```
architecture basic of and2 is  
begin
```

```
    process (a, b)  
    begin  
        y <= a and b after 2 ns;  
    end process ;
```

```
end basic;
```

Structural way...

- Declare corresponding components in register architecture body

```
architecture struct of reg4 is  
  component d_latch  
    port ( d, clk : in bit; q : out bit );  
  end component;  
  component and2  
    port ( a, b : in bit; y : out bit );  
  end component;  
  signal int_clk : bit;  
  
  ...
```

Structural way....


- Now use them to implement the register

```
...  
begin  
    bit0 : d_latch  
        port map ( d0, int_clk, q0 );  
    bit1 : d_latch  
        port map ( d1, int_clk, q1 );  
    bit2 : d_latch  
        port map ( d2, int_clk, q2 );  
    bit3 : d_latch  
        port map ( d3, int_clk, q3 );  
    gate : and2  
        port map ( en, clk, int_clk );  
end struct;
```

Mixed Behavior and Structure

- An architecture can contain both behavioral and structural parts
 - process statements and component instances
 - collectively called *concurrent statements*
 - processes can read and assign to signals
- Example: register-transfer-level (RTL) Model
 - data path described structurally
 - control section described behaviorally

Mixed Example

 

Assignment: Install the FPGA Advantage[®] tool and model this example on it !

Mixed Example

```
entity multiplier is
```

```
    port ( clk, reset : in bit;  
          multiplicand, multiplier : in integer;  
          product : out integer );
```

```
end multiplier;
```

```
architecture mixed of multiplier is
```

```
    signal partial_product, full_product : integer;  
    signal arith_control, result_en, mult_bit, mult_load : bit;
```

```
begin
```

```
    arith_unit : entity work.shift_adder(behavior)  
        port map ( addend => multiplicand, augend => full_product,  
                  sum => partial_product,  
                  add_control => arith_control );
```

```
    result : entity work.reg(behavior)  
        port map ( d => partial_product, q => full_product,  
                  en => result_en, reset => reset );
```

```
    ...
```

Mixed Example..

```
...
multiplier_sr : entity work.shift_reg(behavior)
  port map ( d => multiplier, q => mult_bit,
            load => mult_load, clk => clk );
product <= full_product;

process (clk, reset)
  -- variable declarations for control_section
  -- ...
begin
  -- sequential statements to assign values to control signals
  -- ...
end process;
end mixed;
```

Test Bench your Model

- Testing a design by simulation
- Use a *test bench* model
 - a Model that uses your Model
 - apply test sequences to your inputs
 - monitors values on output signals
 - either using simulator
 - or with a process that verifies correct operation
 - or logic analyzer

Analysis

- Check for syntax and logic errors
 - syntax: grammar of the language
 - logic: how your Model responds to stimuli
- Analyze each *design unit* separately
 - entity declaration
 - architecture body
 - ...
 - put each design unit in a separate file -- *helps a lot.*
- Analyzed design units are placed in a *library*
 - make sure your Model is truly OOP

Simulation

- Discrete event simulation
 - time advances in discrete steps
 - when signal values change—*events* occur
- A processes is *sensitive* to events on input signals
 - specified in wait statements
 - resumes and schedules new values on output signals
 - schedules *transactions*
 - *event* on a signal if value changes


Simulation Algorithm

- Initialization phase
 - each signal is given its initial value
 - simulation time set to 0
 - for each process
 - activate
 - execute until a wait statement, then suspend
 - execution usually involves scheduling transactions on signals for later times

Simulation Algorithm..

- Simulation cycle
 - advance simulation time to time of next transaction
 - for each transaction at this time
 - update signal value
 - event if new value is different from old value
 - for each process sensitive to any of these events, or whose “wait for ...” time-out has expired
 - resume
 - execute until a wait statement, then suspend
- Simulation finishes when there are no further scheduled transactions

Basic Design Methodology

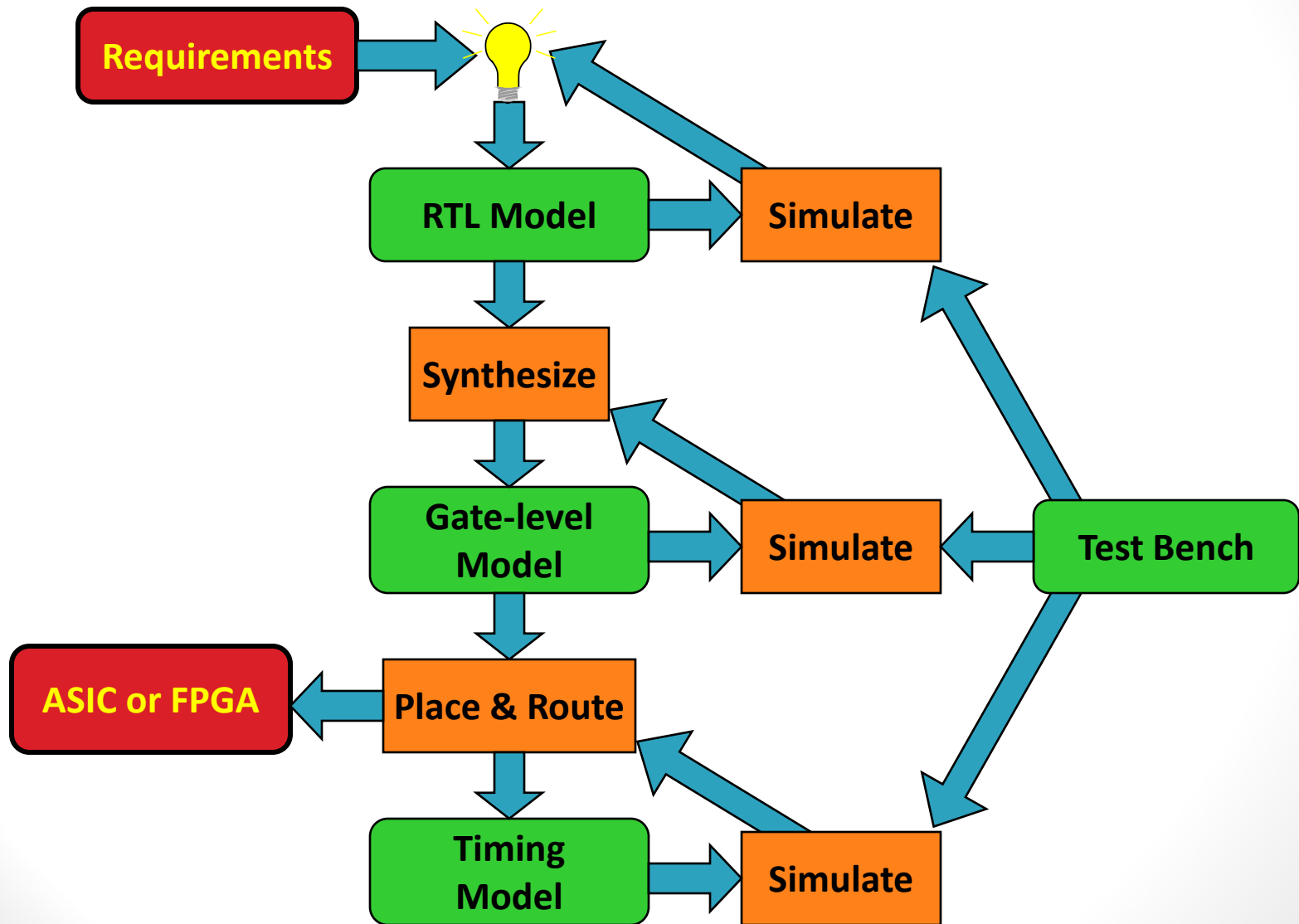

- For more details, refer to:
 - VHDL Tutorial: Learn by Example *by Weijun Zhang*
 - ➔ • <http://esd.cs.ucr.edu/labs/tutorial/>
 - “**Introduction to VHDL**” presentation by Dr. Adnan Shaout, *The University of Michigan-Dearborn*
 - **The VHDL Cookbook**, Peter J. Ashenden, *1st edition, 1990.*
- The lecture is available online at:
 - <http://bu.edu.eg/staff/ahmad.elbanna-courses>
- For inquires, send to:
 - ahmad.elbanna@feng.bu.edu.eg