



INTEGRATED TECHNICAL EDUCATION CLUSTER
AT ALAMEERIA

J-601-1448

Electronic Principals

Lecture #5

FET Biasing & AC Analysis

Instructor:

Dr. Ahmad El-Banna



Agenda

Note!

Same concepts of the BJT, so we will just overview the FET transistors.

- Construction and Characteristics
- FET Biasing
- Design and Troubleshooting
- JFET small signal Model
- FET Amplifier Networks
- Practical Applications

CONSTRUCTION AND CHARACTERISTICS



Construction

- One of the most important characteristics of the FET is its high input impedance.
- FETs are more temperature stable than BJT, and FETs are usually smaller than BJTs, making them particularly useful in integrated-circuit (IC) chips.

 


FIG. 6.1

(a) Current-controlled and (b) voltage-controlled amplifiers.

 


FIG. 6.4

Water analogy for the JFET control mechanism.

 


FIG. 6.3

Junction field-effect transistor (JFET).

 


FIG. 6.14

JFET symbols: (a) n-channel; (b) p-channel.



Construction..

N-channel

 


FIG. 6.5

JFET at $V_{GS} = 0\text{ V}$ and $V_{DS} > 0\text{ V}$.

 


FIG. 6.6

Varying reverse-bias potentials across the p-n junction of an n-channel JFET.

 


FIG. 6.8

Pinch-off ($V_{GS} = 0\text{ V}$, $V_{DS} = V_P$).

$$r_d = \frac{r_o}{(1 - V_{GS}/V_P)^2}$$

 


FIG. 6.7

I_D versus V_{DS} for $V_{GS} = 0\text{ V}$.

 


FIG. 6.11

n-Channel JFET characteristics with $I_{DSS} = 8\text{ mA}$ and $V_P = -4\text{ V}$.



Characteristics & Equations

 
 


FIG. 6.17

Obtaining the transfer curve from the drain characteristics.

TABLE 6.2

JFET	BJT
$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$	$I_C = \beta I_B$
$I_D = I_S$	$I_C \cong I_E$
$I_G \cong 0$ A	$V_{BE} \cong 0.7$ V

$$\text{When } V_{GS} = 0 \text{ V, } I_D = I_{DSS}$$

$$\text{When } V_{GS} = V_P, I_D = 0 \text{ mA}$$

$$I_D = I_{DSS} |_{V_{GS}=0 \text{ V}}$$

$$I_D = 0 \text{ A} |_{V_{GS}=V_P}$$

$$V_{GS} = V_P \left(1 - \sqrt{\frac{I_D}{I_{DSS}}} \right)$$

$$P_D = V_{DS} I_D$$

Depletion-Type MOSFET

- There is no direct electrical connection between the gate terminal and the channel of a MOSFET.
- It is the insulating layer of SiO_2 in the MOSFET construction that accounts for the very desirable high input impedance of the device.

 


FIG. 6.24

n-Channel depletion-type MOSFET.

 


FIG. 6.26

Drain and transfer characteristics for an n-channel depletion-type MOSFET.

 


FIG. 6.30

Graphic symbols for: (a) n-channel depletion-type MOSFETs and (b) p-channel depletion-type MOSFETs.



Depletion-Type MOSFET

$$V_{DG} = V_{DS} - V_{GS}$$

$$V_{DS_{sat}} = V_{GS} - V_T$$

$$I_D = k(V_{GS} - V_T)^2$$

$$k = \frac{I_{D(on)}}{(V_{GS(on)} - V_T)^2}$$

 


FIG. 6.39

Symbols for: (a) n-channel enhancement-type MOSFETs and (b) p-channel enhancement-type MOSFETs.

 


FIG. 6.33

Channel formation in the n-channel enhancement-type MOSFET.

Other MOSFETs

- VMOS AND UMOS POWER MOSFETs

 


FIG. 6.43

(a) VMOS MOSFET; (b) UMOS MOSFET.

- MESFET

 


FIG. 6.47

Basic construction of an n-channel MESFET.

 


FIG. 6.49

Symbol and basic biasing arrangement for an n-channel MESFET.

- CMOS

 


FIG. 6.44

CMOS with the connections indicated in Fig. 6.45.

 


FIG. 6.45

CMOS inverter.



FET BIASING



FIXED-BIAS CONFIGURATION

$$I_G \cong 0 \text{ A}$$

$$V_{R_G} = I_G R_G = (0 \text{ A}) R_G = 0 \text{ V}$$

$$-V_{GG} - V_{GS} = 0$$

$$V_{GS} = -V_{GG}$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$+V_{DS} + I_D R_D - V_{DD} = 0$$

$$V_{DS} = V_{DD} - I_D R_D$$

$$V_S = 0 \text{ V}$$

$$V_{DS} = V_D - V_S$$


$$V_D = V_{DS} + V_S = V_{DS} + 0 \text{ V}$$

$$V_D = V_{DS}$$

$$V_{GS} = V_G - V_S$$

$$V_G = V_{GS} + V_S = V_{GS} + 0 \text{ V}$$

$$V_G = V_{GS}$$

 

Example

EXAMPLE 7.1 Determine the following for the network of Fig. 7.6:

- V_{GS_Q}
- I_{D_Q}
- V_{DS}
- V_D
- V_G
- V_S

 


FIG. 7.6
Example 7.1.

Graphical Approach The resulting Shockley curve and the vertical line at $V_{GS} = -2$ V are provided in Fig. 7.7. It is certainly difficult to read beyond the second place without

 


FIG. 7.7

Graphical solution for the network of Fig. 7.6.

significantly increasing the size of the figure, but a solution of 5.6 mA from the graph of Fig. 7.7 is quite acceptable.

a. Therefore,

$$V_{GS_Q} = -V_{GG} = -2 \text{ V}$$

b. $I_{D_Q} = 5.6 \text{ mA}$

c. $V_{DS} = V_{DD} - I_D R_D = 16 \text{ V} - (5.6 \text{ mA})(2 \text{ k}\Omega)$
 $= 16 \text{ V} - 11.2 \text{ V} = 4.8 \text{ V}$

d. $V_D = V_{DS} = 4.8 \text{ V}$

e. $V_G = V_{GS} = -2 \text{ V}$

f. $V_S = 0 \text{ V}$

The results clearly confirm the fact that the mathematical and graphical approaches generate solutions that are quite close.

Solution:

Mathematical Approach

a. $V_{GS_Q} = -V_{GG} = -2 \text{ V}$

b. $I_{D_Q} = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2 = 10 \text{ mA} \left(1 - \frac{-2 \text{ V}}{-8 \text{ V}}\right)^2$
 $= 10 \text{ mA} (1 - 0.25)^2 = 10 \text{ mA} (0.75)^2 = 10 \text{ mA} (0.5625)$
 $= 5.625 \text{ mA}$

c. $V_{DS} = V_{DD} - I_D R_D = 16 \text{ V} - (5.625 \text{ mA})(2 \text{ k}\Omega)$
 $= 16 \text{ V} - 11.25 \text{ V} = 4.75 \text{ V}$

d. $V_D = V_{DS} = 4.75 \text{ V}$

e. $V_G = V_{GS} = -2 \text{ V}$

f. $V_S = 0 \text{ V}$

Voltage-Divider Bias

$$I_G \cong 0 \text{ A}$$

$$V_G = \frac{R_2 V_{DD}}{R_1 + R_2}$$

$$V_G - V_{GS} - V_{R_S} = 0$$

$$V_{GS} = V_G - V_{R_S}$$

$$V_{GS} = V_G - I_D R_S$$

$$V_{GS} = V_G - I_D R_S$$


$$= V_G - (0 \text{ mA}) R_S$$

$$V_{GS} = V_G |_{I_D=0 \text{ mA}}$$

$$V_{GS} = V_G - I_D R_S$$

$$0 \text{ V} = V_G - I_D R_S$$

$$I_D = \frac{V_G}{R_S} |_{V_{GS}=0 \text{ V}}$$

 

$$V_{DS} = V_{DD} - I_D (R_D + R_S)$$

$$V_D = V_{DD} - I_D R_D$$

$$V_S = I_D R_S$$

$$I_{R_1} = I_{R_2} = \frac{V_{DD}}{R_1 + R_2}$$

Example

EXAMPLE 7.4 Determine the following for the network of Fig. 7.21:

- I_{DQ} and V_{GSQ} .
- V_D .
- V_S .
- V_{DS} .
- V_{DG} .

 


FIG. 7.21
Example 7.4.

Solution:

- a. For the transfer characteristics, if $I_D = I_{DSS}/4 = 8 \text{ mA}/4 = 2 \text{ mA}$, then $V_{GS} = V_P/2 = -4 \text{ V}/2 = -2 \text{ V}$. The resulting curve representing Shockley's equation appears in Fig. 7.22. The network equation is defined by

$$\begin{aligned} V_G &= \frac{R_2 V_{DD}}{R_1 + R_2} \\ &= \frac{(270 \text{ k}\Omega)(16 \text{ V})}{2.1 \text{ M}\Omega + 0.27 \text{ M}\Omega} \\ &= 1.82 \text{ V} \end{aligned}$$

and

$$\begin{aligned} V_{GS} &= V_G - I_D R_S \\ &= 1.82 \text{ V} - I_D(1.5 \text{ k}\Omega) \end{aligned}$$

 


FIG. 7.22

Determining the Q -point for the network of Fig. 7.21.

When $I_D = 0 \text{ mA}$,

$$V_{GS} = +1.82 \text{ V}$$

When $V_{GS} = 0 \text{ V}$,

$$I_D = \frac{1.82 \text{ V}}{1.5 \text{ k}\Omega} = 1.21 \text{ mA}$$

The resulting bias line appears on Fig. 7.22 with quiescent values of

$$I_{DQ} = 2.4 \text{ mA}$$

and

$$V_{GSQ} = -1.8 \text{ V}$$

- $V_D = V_{DD} - I_D R_D$
 $= 16 \text{ V} - (2.4 \text{ mA})(2.4 \text{ k}\Omega)$
 $= 10.24 \text{ V}$
- $V_S = I_D R_S = (2.4 \text{ mA})(1.5 \text{ k}\Omega)$
 $= 3.6 \text{ V}$
- $V_{DS} = V_{DD} - I_D(R_D + R_S)$
 $= 16 \text{ V} - (2.4 \text{ mA})(2.4 \text{ k}\Omega + 1.5 \text{ k}\Omega)$
 $= 6.64 \text{ V}$
 or $V_{DS} = V_D - V_S = 10.24 \text{ V} - 3.6 \text{ V}$
 $= 6.64 \text{ V}$

- e. Although seldom requested, the voltage V_{DG} can easily be determined using

$$\begin{aligned} V_{DG} &= V_D - V_G \\ &= 10.24 \text{ V} - 1.82 \text{ V} \\ &= 8.42 \text{ V} \end{aligned}$$

DESIGN AND TROUBLESHOOTING



Design Example

EXAMPLE 7.14 For the network of Fig. 7.51, the levels of V_{DQ} and I_{DQ} are specified. Determine the required values of R_D and R_S . What are the closest standard commercial values?

 


FIG. 7.51
Example 7.14.

$$R_{\text{unknown}} = \frac{V_R}{I_R}$$

Solution: As defined by Eq. (7.42),

$$R_D = \frac{V_{R_D}}{I_{D_Q}} = \frac{V_{DD} - V_{D_Q}}{I_{D_Q}}$$

$$= \frac{20 \text{ V} - 12 \text{ V}}{2.5 \text{ mA}} = \frac{8 \text{ V}}{2.5 \text{ mA}} = 3.2 \text{ k}\Omega$$

and

Plotting the transfer curve in Fig. 7.52 and drawing a horizontal line at $I_{D_Q} = 2.5 \text{ mA}$ results in $V_{GS_Q} = -1 \text{ V}$, and applying $V_{GS} = -I_D R_S$ establishes the level of R_S :

$$R_S = \frac{-(V_{GS_Q})}{I_{D_Q}} = \frac{-(-1 \text{ V})}{2.5 \text{ mA}} = 0.4 \text{ k}\Omega$$

The nearest standard commercial values are

$$R_D = 3.2 \text{ k}\Omega \Rightarrow 3.3 \text{ k}\Omega$$

$$R_S = 0.4 \text{ k}\Omega \Rightarrow 0.39 \text{ k}\Omega$$

 


FIG. 7.52

Determining V_{GS_Q} for the network of Fig. 7.51.

Troubleshooting

The level of V_{DS} is typically between 25% and 75% of V_{DD} .

The continuity of a network can be checked simply by measuring the voltage across any resistor of the network.

 


FIG. 7.55


Checking the dc operation of the JFET self-bias configuration.

JFET SMALL SIGNAL MODEL



JFET small signal Model
 
$$g_m = \frac{\Delta I_D}{\Delta V_{GS}}$$



$$g_m = \frac{2I_{DSS}}{|V_P|} \left[1 - \frac{V_{GS}}{V_P} \right]$$

 


FIG. 8.8




JFET ac equivalent circuit.

$$Z_i(\text{JFET}) = \infty \Omega$$

$$Z_o(\text{JFET}) = r_d = \frac{1}{g_{os}} = \frac{1}{y_{os}}$$

$$r_d = \left. \frac{\Delta V_{DS}}{\Delta I_D} \right|_{V_{GS}=\text{constant}}$$

Fixed-Bias Configuration

   

$$Z_i = R_G$$

$$Z_o = R_D \parallel r_d$$

$$Z_o \cong R_D \quad r_d \geq 10R_D$$



$$A_v = \frac{V_o}{V_i} = -g_m (r_d \parallel R_D)$$

$$A_v = \frac{V_o}{V_i} = -g_m R_D \quad r_d \geq 10R_D$$

phase shift of 180° between input and output voltages.



VOLTAGE-DIVIDER CONFIGURATION

  

$$Z_i = R_1 \parallel R_2$$

$$Z_o = r_d \parallel R_D$$

$$Z_o \cong R_D \quad r_d \geq 10R_D$$

$$V_{gs} = V_i$$

$$V_o = -g_m V_{gs} (r_d \parallel R_D)$$

$$A_v = \frac{V_o}{V_i} = \frac{-g_m V_{gs} (r_d \parallel R_D)}{V_{gs}}$$

$$A_v = \frac{V_o}{V_i} = -g_m (r_d \parallel R_D)$$

$$A_v = \frac{V_o}{V_i} \cong -g_m R_D \quad r_d \geq 10R_D$$



FET AMPLIFIER NETWORKS



Design FET Amplifier Network

EXAMPLE 8.14 Choose the values of R_D and R_S for the network of Fig. 8.44 that will result in a gain of 8 using a relatively high level of g_m for this device defined at $V_{GS_Q} = \frac{1}{4}V_P$.

 


FIG. 8.44

Network for desired voltage gain in Example 8.14.

Solution: The operating point is defined by

$$V_{GS_Q} = \frac{1}{4}V_P = \frac{1}{4}(-4 \text{ V}) = -1 \text{ V}$$

and
$$I_D = I_{DSS} \left(1 - \frac{V_{GS_Q}}{V_P}\right)^2 = 10 \text{ mA} \left(1 - \frac{(-1 \text{ V})}{(-4 \text{ V})}\right)^2 = 5.625 \text{ mA}$$

Determining g_m , we obtain

$$\begin{aligned} g_m &= g_{m0} \left(1 - \frac{V_{GS_Q}}{V_P}\right) \\ &= 5 \text{ mS} \left(1 - \frac{(-1 \text{ V})}{(-4 \text{ V})}\right) = 3.75 \text{ mS} \end{aligned}$$

The magnitude of the ac voltage gain is determined by

$$|A_v| = g_m(R_D \parallel r_d)$$

Substituting known values results in

$$8 = (3.75 \text{ mS})(R_D \parallel r_d)$$

so that

$$R_D \parallel r_d = \frac{8}{3.75 \text{ mS}} = 2.13 \text{ k}\Omega$$

The level of r_d is defined by

$$r_d = \frac{1}{g_{os}} = \frac{1}{20 \mu\text{S}} = 50 \text{ k}\Omega$$

and

$$R_D \parallel 50 \text{ k}\Omega = 2.13 \text{ k}\Omega$$

with the result that

$$R_D = 2.2 \text{ k}\Omega$$

which is a standard value.

The level of R_S is determined by the dc operating conditions as follows:





$$\begin{aligned} V_{GS_Q} &= -I_D R_S \\ -1 \text{ V} &= -(5.625 \text{ mA})R_S \end{aligned}$$

and





$$R_S = \frac{1 \text{ V}}{5.625 \text{ mA}} = 177.8 \Omega$$

The closest standard value is **180 Ω** . In this example, R_S does not appear in the ac design because of the shorting effect of C_S .

Summary Table

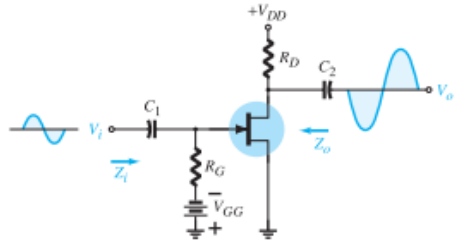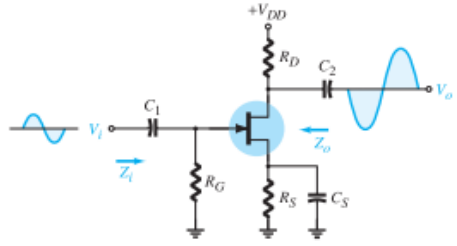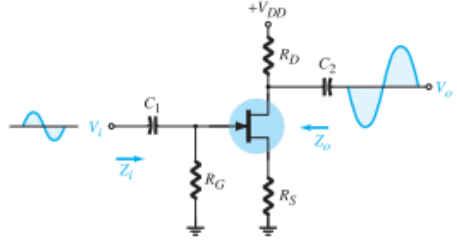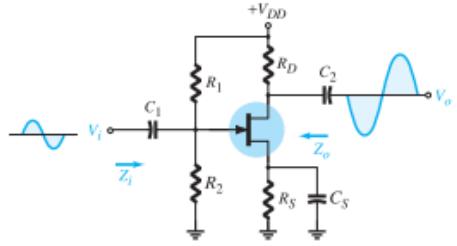Configuration	Z_i	Z_o	$A_v = \frac{V_o}{V_i}$
Fixed-bias [JFET or D-MOSFET] 	High (10 MΩ) $= R_G$	Medium (2 kΩ) $= R_D \parallel r_d$ $\cong R_D$ ($r_d \geq 10 R_D$)	Medium (-10) $= -g_m(r_d \parallel R_D)$ $\cong -g_m R_D$ ($r_d \geq 10 R_D$)
Self-bias bypassed R_S [JFET or D-MOSFET] 	High (10 MΩ) $= R_G$	Medium (2 kΩ) $= R_D \parallel r_d$ $\cong R_D$ ($r_d \geq 10 R_D$)	Medium (-10) $= -g_m(r_d \parallel R_D)$ $\cong -g_m R_D$ ($r_d \geq 10 R_D$)
Self-bias unbypassed R_S [JFET or D-MOSFET] 	High (10 MΩ) $= R_G$	$= \frac{\left[1 + g_m R_S + \frac{R_S}{r_d}\right] R_D}{\left[1 + g_m R_S + \frac{R_S}{r_d} + \frac{R_D}{r_d}\right]}$ $\cong R_D$ ($r_d \geq 10 R_D$ or $r_d = \infty$)	Low (-2) $= \frac{g_m R_D}{1 + g_m R_S + \frac{R_D + R_S}{r_d}}$ $\cong \frac{-g_m R_D}{1 + g_m R_S}$ ($r_d \geq 10(R_D + R_S)$)
Voltage-divider bias [JFET or D-MOSFET] 	High (10 MΩ) $= R_1 \parallel R_2$	Medium (2 kΩ) $= R_D \parallel r_d$ $\cong R_D$ ($r_d \geq 10 R_D$)	Medium (-10) $= -g_m(r_d \parallel R_D)$ $\cong -g_m R_D$ ($r_d \geq 10 R_D$)

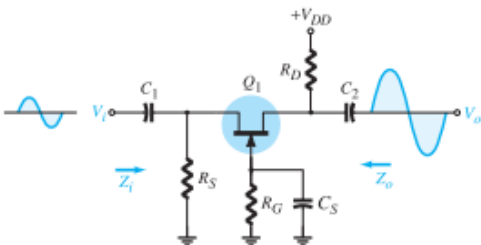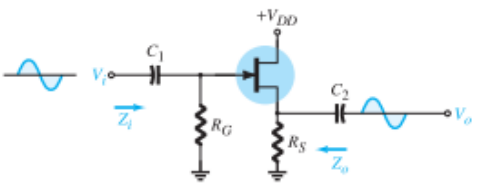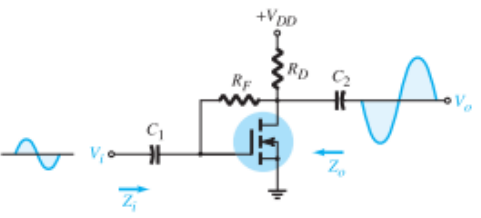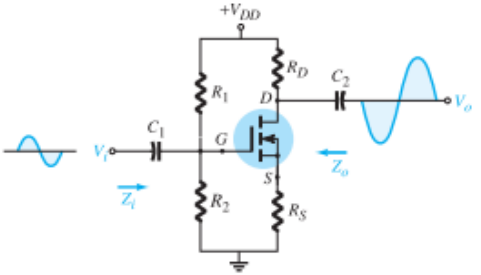


Configuration	Z_i	Z_o	$A_v = \frac{V_o}{V_i}$
Common-gate [JFET or D-MOSFET] 	Low (1 kΩ) $= R_S \parallel \left[\frac{r_d + R_D}{1 + g_m r_d} \right]$ $\cong R_S \parallel \frac{1}{g_m}$ <small>($r_d \geq 10 R_D$)</small>	Medium (2 kΩ) $= R_D \parallel r_d$ $\cong R_D$ <small>($r_d \geq 10 R_D$)</small>	Medium (+10) $= \frac{g_m R_D + \frac{R_D}{r_d}}{1 + \frac{R_D}{r_d}}$ $\cong g_m R_D$ <small>($r_d \geq 10 R_D$)</small>
Source-follower [JFET or D-MOSFET] 	High (10 MΩ) $= R_G$	Low (100 kΩ) $= r_d \parallel R_S \parallel 1/g_m$ $\cong R_S \parallel 1/g_m$ <small>($r_d \geq 10 R_S$)</small>	Low (<1) $= \frac{g_m (r_d \parallel R_S)}{1 + g_m (r_d \parallel R_S)}$ $\cong \frac{g_m R_S}{1 + g_m R_S}$ <small>($r_d \geq 10 R_S$)</small>
Drain-feedback bias E-MOSFET 	Medium (1 MΩ) $= \frac{R_F + r_d \parallel R_D}{1 + g_m (r_d \parallel R_D)}$ $\cong \frac{R_F}{1 + g_m R_D}$ <small>($r_d \geq 10 R_D$)</small>	Medium (2 kΩ) $= R_F \parallel r_d \parallel R_D$ $\cong R_D$ <small>($R_F, r_d \geq 10 R_D$)</small>	Medium (-10) $= -g_m (R_F \parallel r_d \parallel R_D)$ $\cong -g_m R_D$ <small>($R_F, r_d \geq 10 R_D$)</small>
Voltage-divider bias E-MOSFET 	Medium (1 MΩ) $= R_1 \parallel R_2$	Medium (2 kΩ) $= R_D \parallel r_d$ $\cong R_D$ <small>($r_d \geq 10 R_D$)</small>	Medium (-10) $= -g_m (r_d \parallel R_D)$ $\cong -g_m R_D$ <small>($r_d \geq 10 R_D$)</small>



Cascaded Configuration


 
$$A_v = A_{v_1}A_{v_2} = (-g_{m_1}R_{D_1})(-g_{m_2}R_{D_2}) = g_{m_1}g_{m_2}R_{D_1}R_{D_2}$$



PRACTICAL APPLICATIONS



Three-Channel Audio Mixer

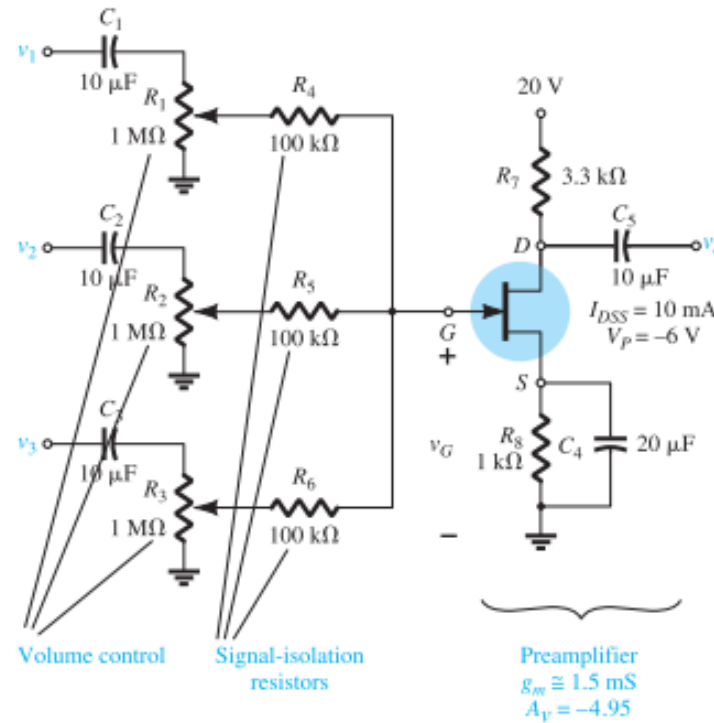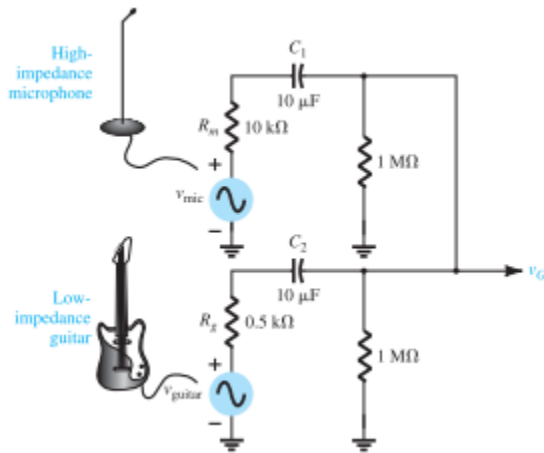

Motion Detection System

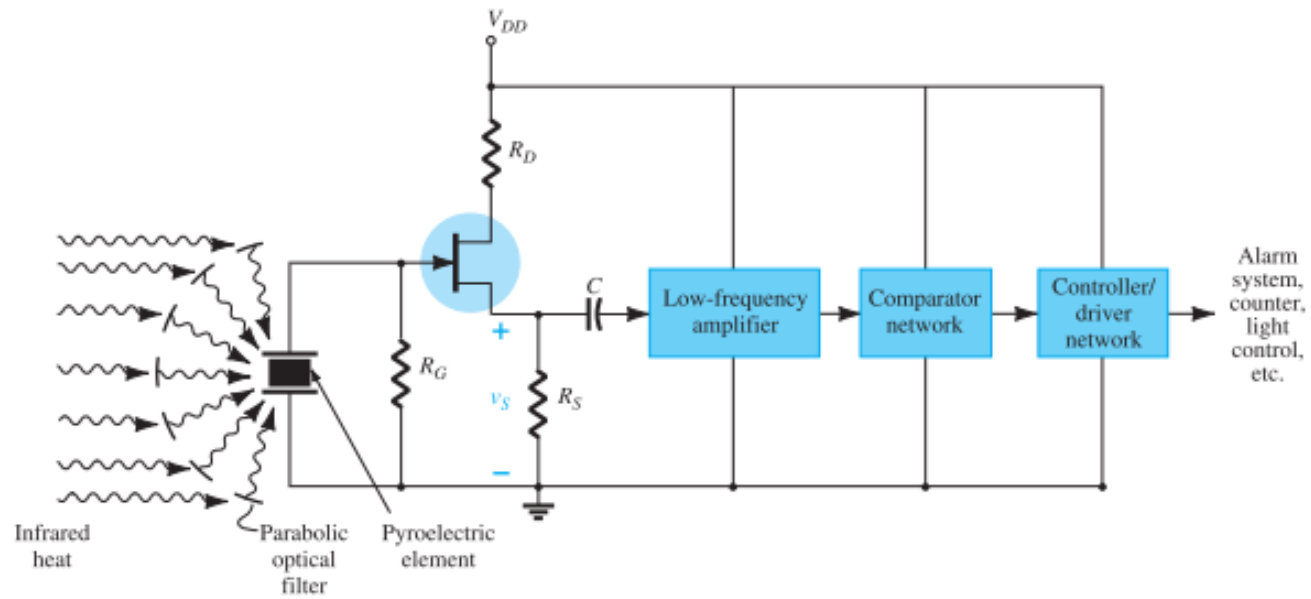


FIG. 8.59

Passive infrared (PIR) motion-detection system.

- For more details, refer to:
 - Chapter 6,7,8, Electronic Devices and Circuits, Boylestad.
- The lecture is available online at:
 - https://speakerdeck.com/ahmad_elbanna
- For inquires, send to:
 - ahmad.elbanna@feng.bu.edu.eg