



INTEGRATED TECHNICAL EDUCATION CLUSTER
AT ALAMEERIA

J-601-1448

Electronic Principles

Lecture #6

Power Supplies (Voltage Regulators)

Instructor:

Dr. Ahmad El-Banna




Agenda

- Introduction
- General Filter Considerations
- Discrete Transistor Voltage Regulator
- IC Voltage Regulators

INTRODUCTION



Introduction

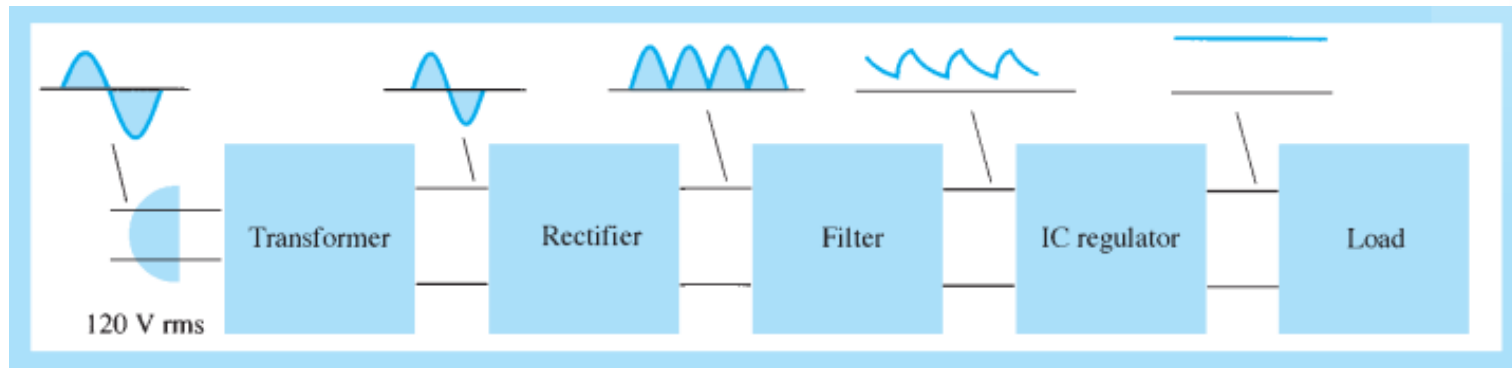

Block diagram showing parts of a power supply.

GENERAL FILTER CONSIDERATIONS



Ripple Voltage

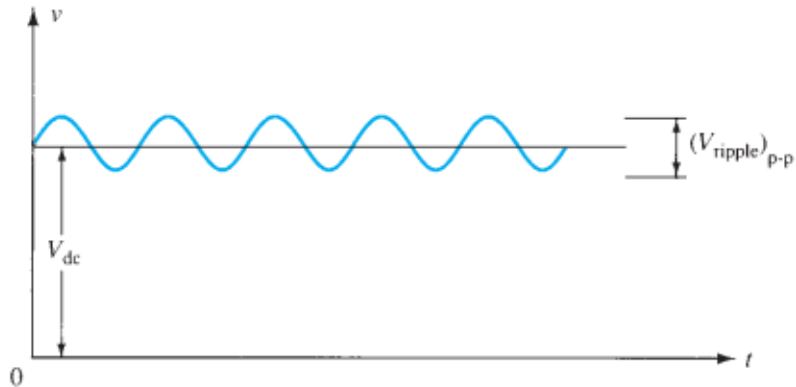


FIG. 15.2

Filter voltage waveform showing dc and ripple voltages.

$$r = \frac{\text{ripple voltage (rms)}}{\text{dc voltage}} = \frac{V_r(\text{rms})}{V_{dc}} \times 100\%$$

Voltage regulation is given by

$$\text{Voltage regulation} = \frac{\text{no-load voltage} - \text{full-load voltage}}{\text{full-load voltage}}$$

$$\% \text{V.R.} = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100\%$$

Capacitor Filter


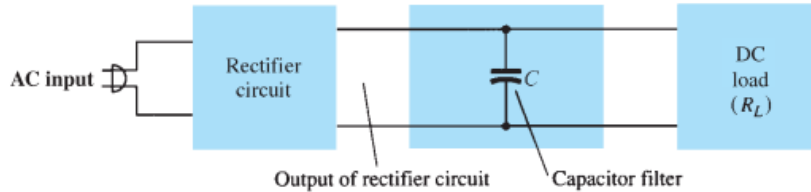


FIG. 15.3
Basic capacitor filter.

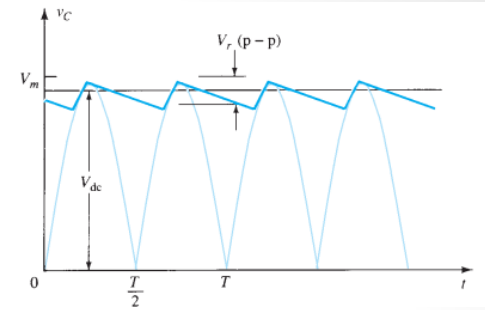

Ripple Voltage V_r (RMS)

$$V_{r(\text{rms})} = \frac{I_{\text{dc}}}{4\sqrt{3}fC} = \frac{2.4I_{\text{dc}}}{C} = \frac{2.4V_{\text{dc}}}{R_L C}$$

$$V_{\text{dc}} = V_m - \frac{I_{\text{dc}}}{4fC} = V_m - \frac{4.17I_{\text{dc}}}{C}$$

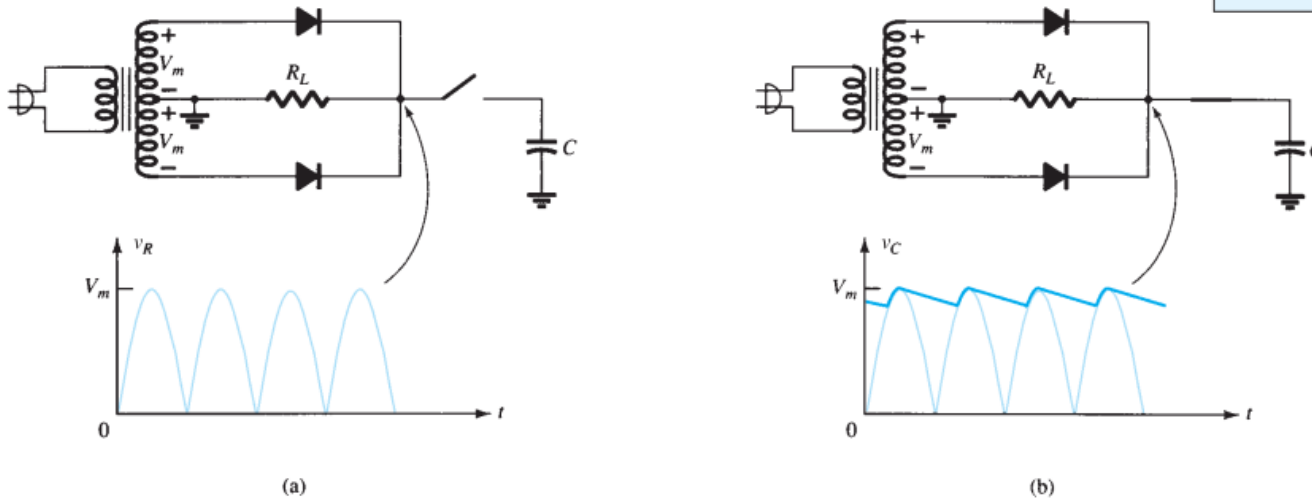


FIG. 15.4
Capacitor filter operation: (a) full-wave rectifier voltage; (b) filtered output voltage.



RC Filter

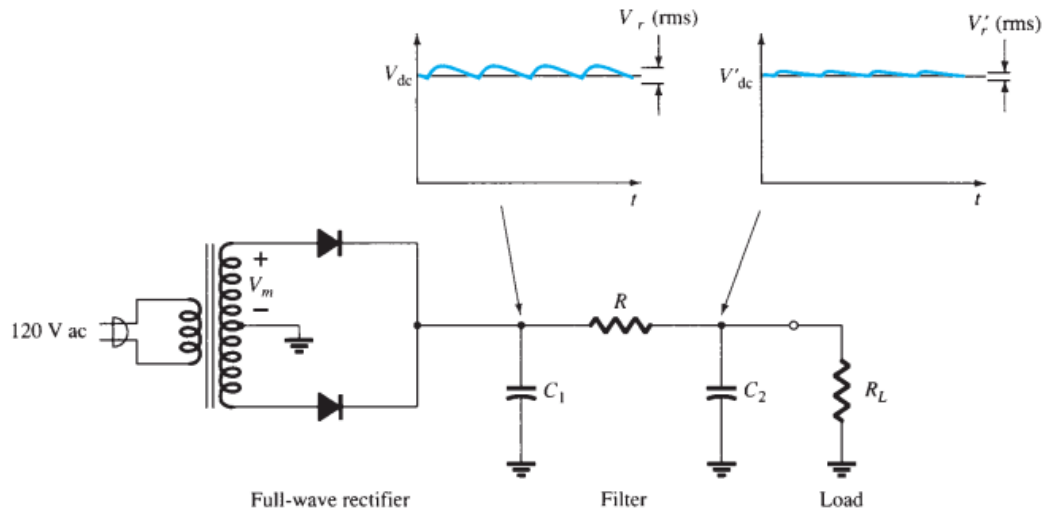


FIG. 15.9

Full-wave rectifier and RC filter circuit.

$$V'_{dc} = \frac{R_L}{R + R_L} V_{dc}$$

$$V'_r(\text{rms}) \approx \frac{X_C}{R} V_r(\text{rms})$$

DISCRETE TRANSISTOR VOLTAGE REGULATOR



Series Voltage Regulator

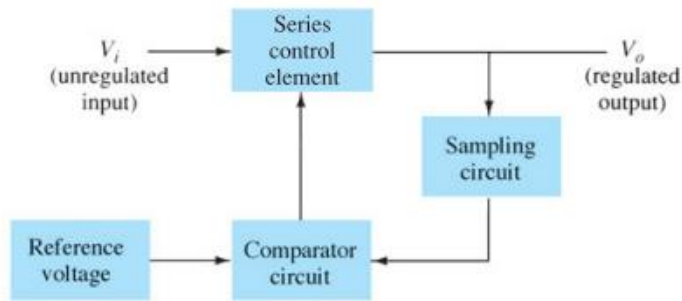


FIG. 15.12

Series regulator block diagram.

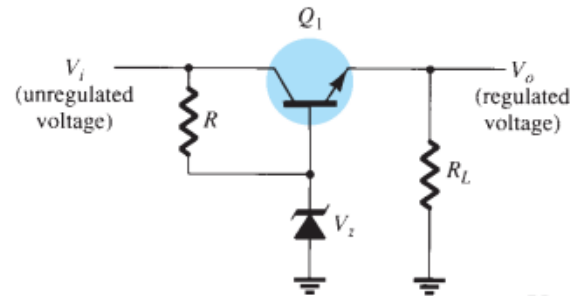


FIG. 15.13

Series regulator circuit.

$$V_o = V_Z - V_{BE}$$

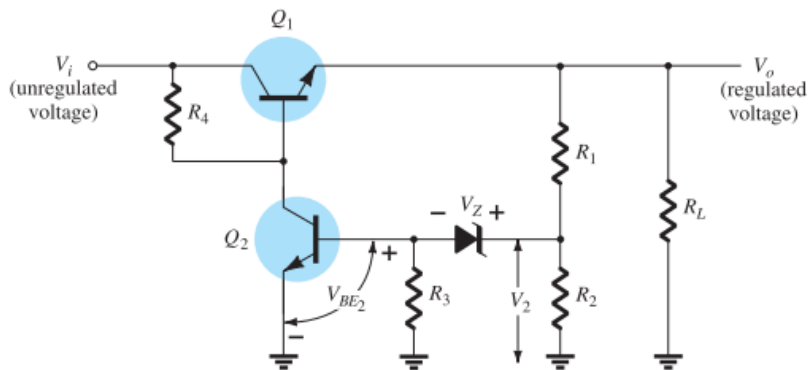


FIG. 15.15

Improved series regulator circuit.

$$V_o = \frac{R_1 + R_2}{R_2} (V_Z + V_{BE_2})$$

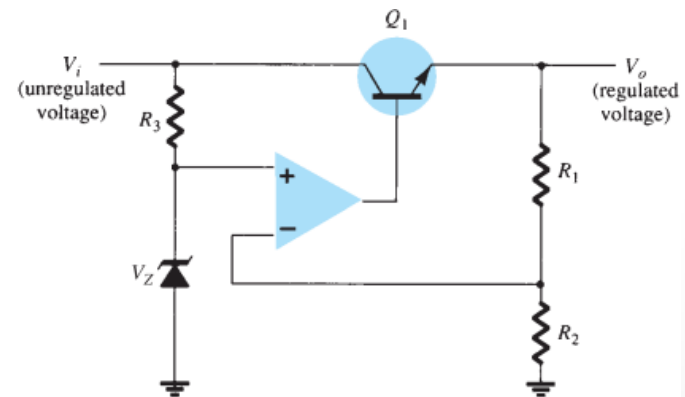


FIG. 15.16

Op-amp series regulator circuit.

$$V_o = \left(1 + \frac{R_1}{R_2}\right) V_Z$$

Shunt Voltage Regulator

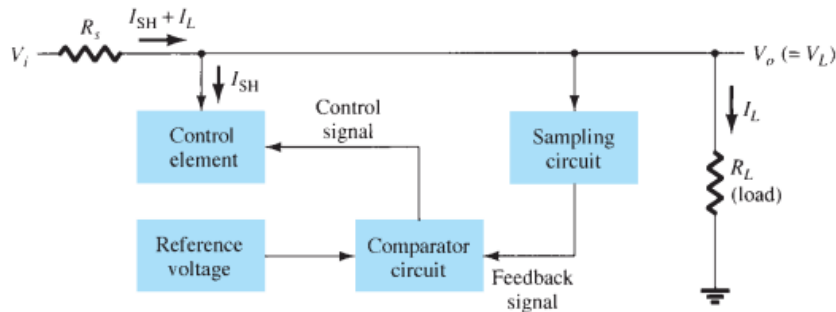


FIG. 15.20

Block diagram of shunt voltage regulator.

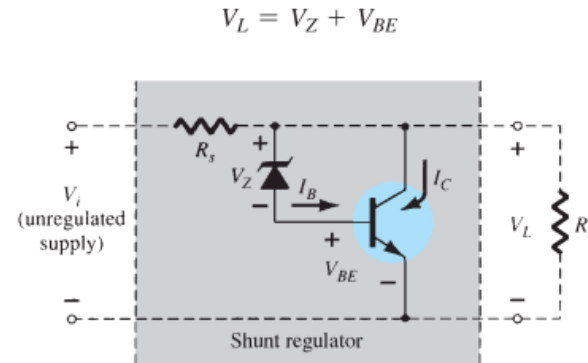


FIG. 15.21

Transistor shunt voltage regulator.

$$V_o = V_L = V_Z + V_{BE2} + V_{BE1}$$

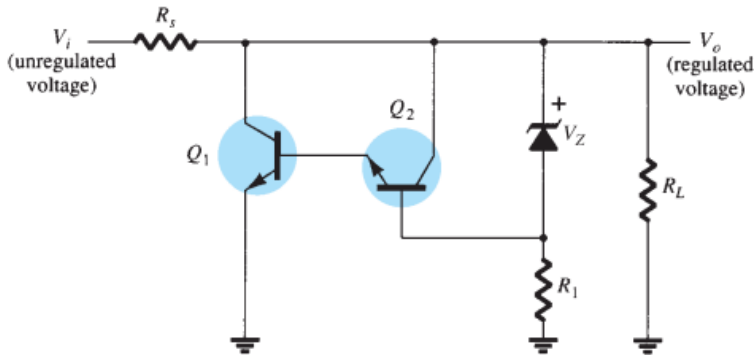


FIG. 15.23

Improved shunt voltage regulator circuit.

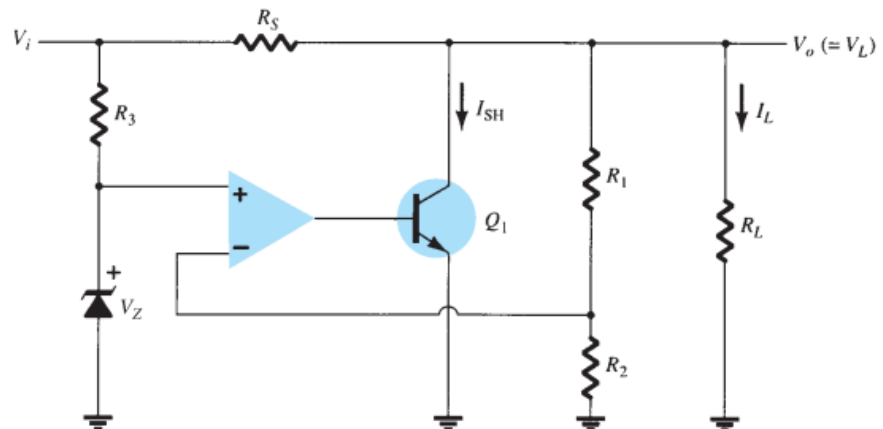


FIG. 15.24

Shunt voltage regulator using an op-amp.

IC VOLTAGE REGULATORS



Three-Terminal Voltage Regulators

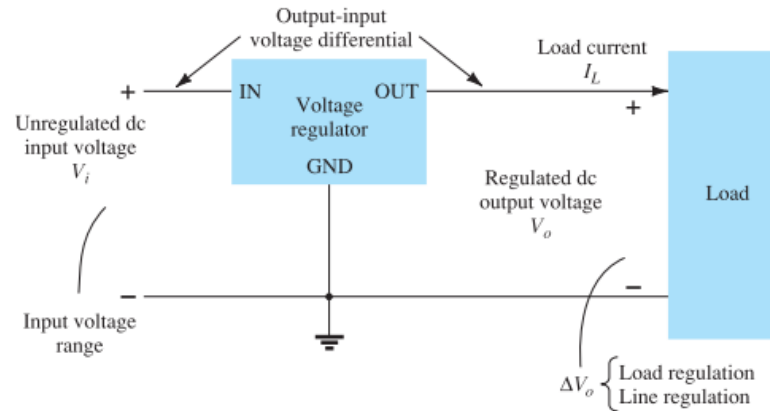


FIG. 15.25

Block representation of three-terminal voltage regulator.

- Fixed-Positive-Voltage Regulators

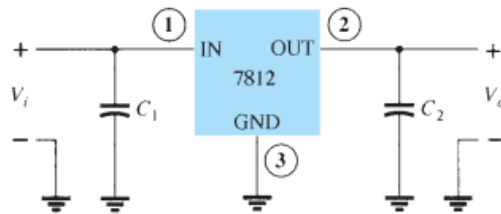


FIG. 15.26

Connection of a 7812 voltage regulator.

TABLE 15.1

Positive-Voltage Regulators in the 7800 Series

| IC Part | Output Voltage (V) | Minimum V_i (V) |
|---------|--------------------|-------------------|
| 7805 | +5 | 7.3 |
| 7806 | +6 | 8.3 |
| 7808 | +8 | 10.5 |
| 7810 | +10 | 12.5 |
| 7812 | +12 | 14.6 |
| 7815 | +15 | 17.7 |
| 7818 | +18 | 21.0 |
| 7824 | +24 | 27.1 |


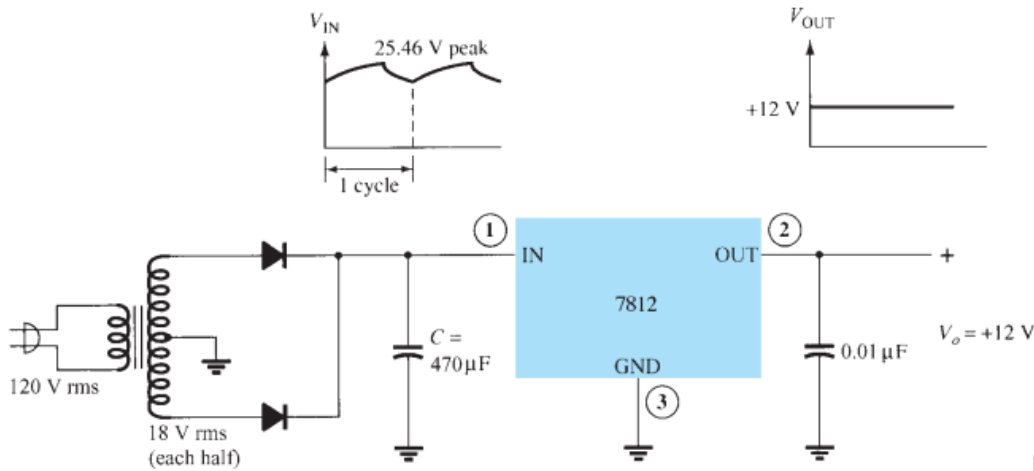


FIG. 15.27
A +12 V power supply.

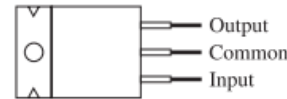

| Nominal output voltage | Regulator |
|------------------------|-----------|
| 5 V | 7805 |
| 6 V | 7806 |
| 8 V | 7808 |
| 10 V | 7810 |
| 12 V | 7812 |
| 15 V | 7815 |
| 18 V | 7818 |
| 24 V | 7824 |

Absolute maximum ratings:

Input voltage 40 V
 Continuous total dissipation 2 W
 Operating free-air temperature range -65 to 150°C

µA 7812C electrical characteristics:

| Parameter | Min. | Typ. | Max. | Units |
|------------------------------|------|-------|------|-------|
| Output voltage | 11.5 | 12 | 12.5 | V |
| Input regulation | | 3 | 120 | mV |
| Ripple rejection | 55 | 71 | | dB |
| Output regulation | | 4 | 100 | mV |
| Output resistance | | 0.018 | | Ω |
| Dropout voltage | | 2.0 | | V |
| Short-circuit output current | | 350 | | mA |
| Peak output current | | 2.2 | | A |

- Fixed-Negative-Voltage Regulators

TABLE 15.2

Negative-Voltage Regulators in 7900 Series

| IC Part | Output Voltage (V) | Minimum V_i (V) |
|---------|--------------------|-------------------|
| 7905 | -5 | -7.3 |
| 7906 | -6 | -8.4 |
| 7908 | -8 | -10.5 |
| 7909 | -9 | -11.5 |
| 7912 | -12 | -14.6 |
| 7915 | -15 | -17.7 |
| 7918 | -18 | -20.8 |
| 7924 | -24 | -27.1 |



Adjustable-Voltage Regulators

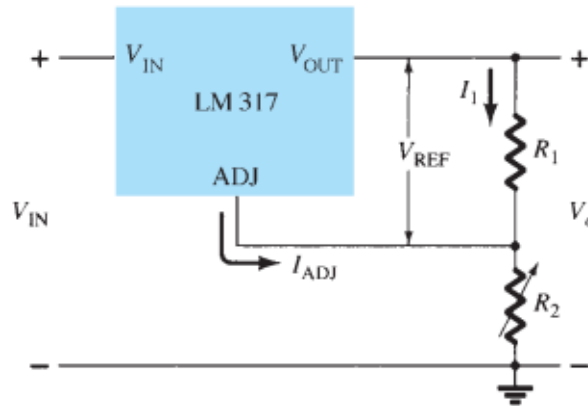


FIG. 15.30

Connection of LM317 adjustable-voltage regulator.

$$V_o = V_{\text{ref}} \left(1 + \frac{R_2}{R_1} \right) + I_{\text{adj}} R_2$$

- For more details, refer to:
 - Chapter 15, Electronic Devices and Circuits, Boylestad.
- The lecture is available online at:
 - https://speakerdeck.com/ahmad_elbanna
- For inquiries, send to:
 - ahmad.elbanna@feng.bu.edu.eg