



INTEGRATED TECHNICAL EDUCATION CLUSTER  
AT ALAMEERIA

**J-601-1448**

**Electronic Principals**

Lecture #7

BJT and JFET Frequency Response

**Instructor:**

**Dr. Ahmad El-Banna**



# Agenda


- Introduction
- General Frequency Considerations
- Low Frequency Analysis- Bode Plot
- BJT & JFET Amplifiers Low Frequency Analysis
- Miller Effect
- BJT & JFET Amplifiers High Frequency Response

# INTRODUCTION


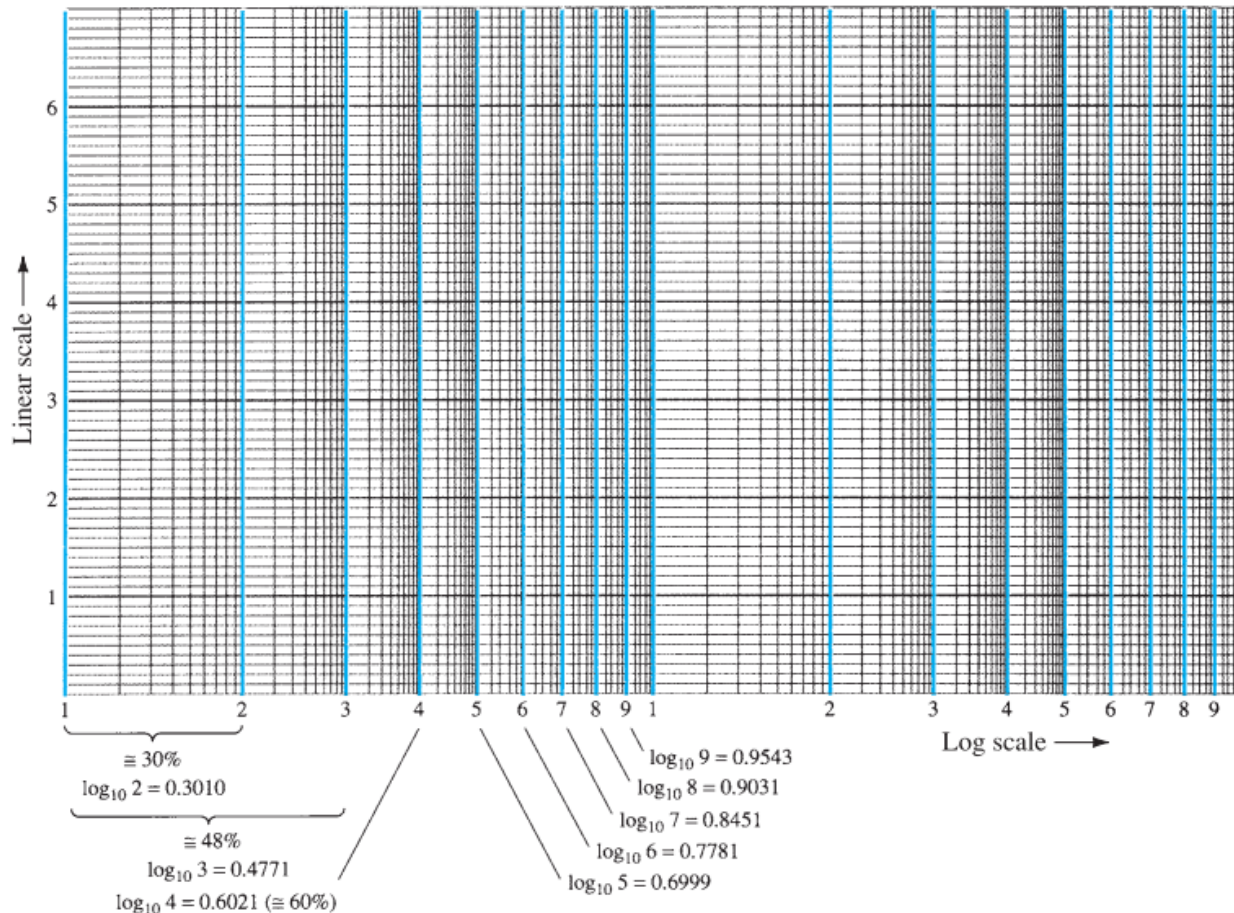
# Introduction

- We will now investigate the frequency effects introduced by the larger capacitive elements of the network at low frequencies and the smaller capacitive elements of the active device at high frequencies



# Decibels

- Power Levels

$$G = \log_{10} \frac{P_2}{P_1} \quad \text{bel}$$

$$G_{\text{dB}} = 10 \log_{10} \frac{P_2}{P_1} \quad \text{dB}$$

$$G_{\text{dBm}} = 10 \log_{10} \frac{P_2}{1 \text{ mW}} \Big|_{600 \Omega} \quad \text{dBm}$$

$$G_{\text{dB}} = 10 \log_{10} \frac{P_2}{P_1} = 10 \log_{10} \frac{V_2^2/R_i}{V_1^2/R_i} = 10 \log_{10} \left( \frac{V_2}{V_1} \right)^2$$

$$G_{\text{dB}} = 20 \log_{10} \frac{V_2}{V_1} \quad \text{dB}$$

- Cascaded Stages

$$|A_{v_T}| = |A_{v_1}| \cdot |A_{v_2}| \cdot |A_{v_3}| \cdots |A_{v_n}|$$

$$G_{\text{dB}_T} = G_{\text{dB}_1} + G_{\text{dB}_2} + G_{\text{dB}_3} + \cdots + G_{\text{dB}_n} \quad \text{dB}$$

- Voltage gain versus dB levels

Comparing  $A_v = \frac{V_o}{V_i}$  to dB

Voltage Gain, $V_o/V_i$	dB Level
0.5	-6
0.707	-3
1	0
2	6
10	20
40	32
100	40
1000	60
10,000	80
etc.	

# GENERAL FREQUENCY CONSIDERATIONS



# Low, High & Mid Frequency Range

Variation in  $X_C = \frac{1}{2\pi fC}$  with frequency for a 1- $\mu$ F capacitor

$f$	$X_C$	
10 Hz	15.91 k $\Omega$	} Range of possible effect
100 Hz	1.59 k $\Omega$	
1 kHz	159 $\Omega$	
10 kHz	15.9 $\Omega$	
100 kHz	1.59 $\Omega$	} Range of lesser concern ( $\cong$ short-circuit equivalence)
1 MHz	0.159 $\Omega$	
10 MHz	15.9 m $\Omega$	
100 MHz	1.59 m $\Omega$	

Variation in  $X_C = \frac{1}{2\pi fC}$  with frequency for a 5 pF capacitor

$f$	$X_C$	
10 Hz	3,183 M $\Omega$	} Range of lesser concern ( $\cong$ open-circuit equivalent)
100 Hz	318.3 M $\Omega$	
1 kHz	31.83 M $\Omega$	
10 kHz	3.183 M $\Omega$	
100 kHz	318.3 k $\Omega$	} Range of possible effect
1 MHz	31.83 k $\Omega$	
10 MHz	3.183 k $\Omega$	
100 MHz	318.3 $\Omega$	

- The larger capacitors of a system will have an important impact on the response of a system in the **low-frequency range** and can be ignored for the high-frequency region.
- The smaller capacitors of a system will have an important impact on the response of a system in the **high-frequency range** and can be ignored for the low-frequency region.
- The effect of the capacitive elements in an amplifier are ignored for the **mid-frequency** range when important quantities such as the gain and impedance levels are determined.

# Typical Frequency Response




$$P_{o_{mid}} = \frac{|V_o|^2}{R_o} = \frac{|A_{v_{mid}} V_i|^2}{R_o}$$

$$P_{o_{HPF}} = \frac{|0.707 A_{v_{mid}} V_i|^2}{R_o} = 0.5 \frac{|A_{v_{mid}} V_i|^2}{R_o}$$

$$P_{o_{HPF}} = 0.5 P_{o_{mid}}$$

$$\text{bandwidth (BW)} = f_H - f_L$$

The band frequencies define a level where the gain or quantity of interest will be 70.7% of its maximum value.

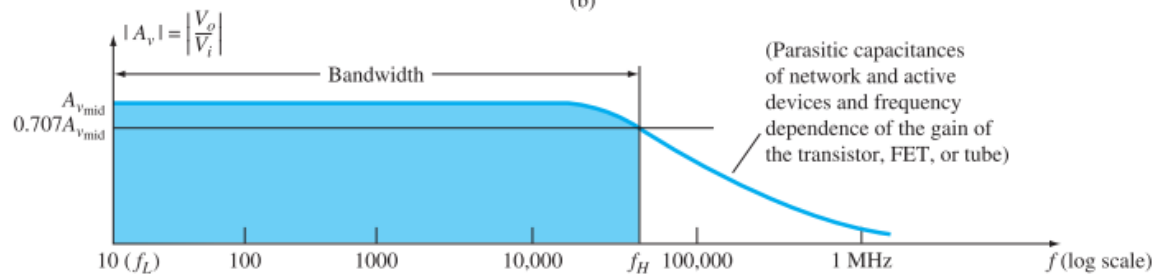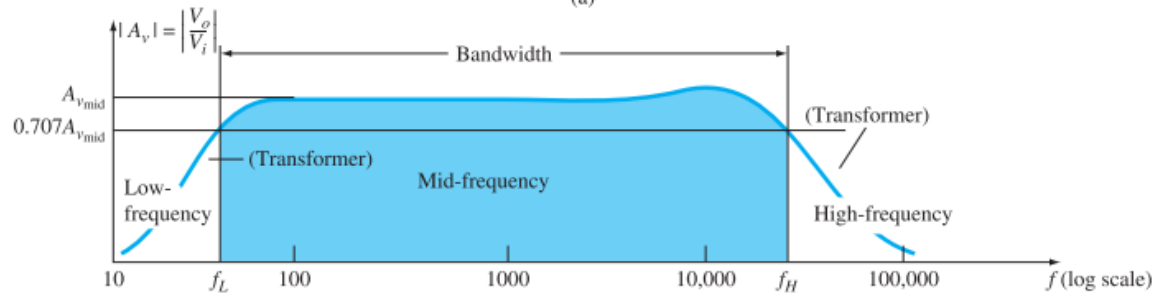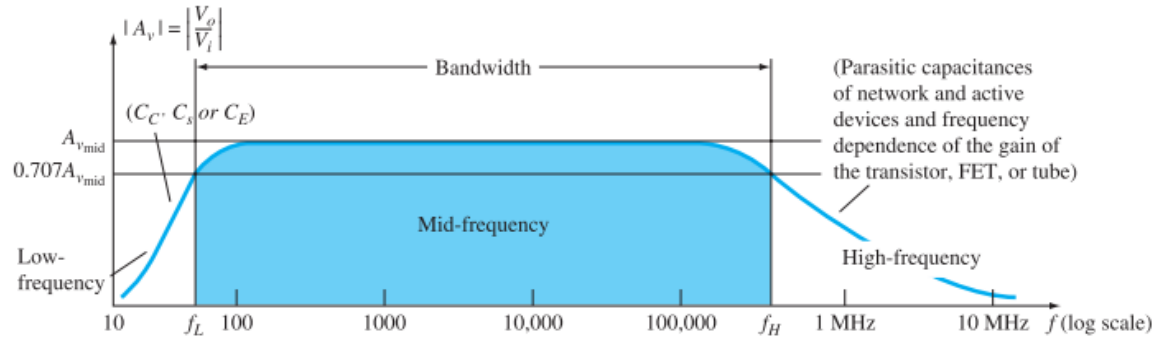


**FIG. 9.8**

Gain versus frequency: (a) RC-coupled amplifiers; (b) transformer-coupled amplifiers; (c) direct-coupled amplifiers.






- Normalized plot

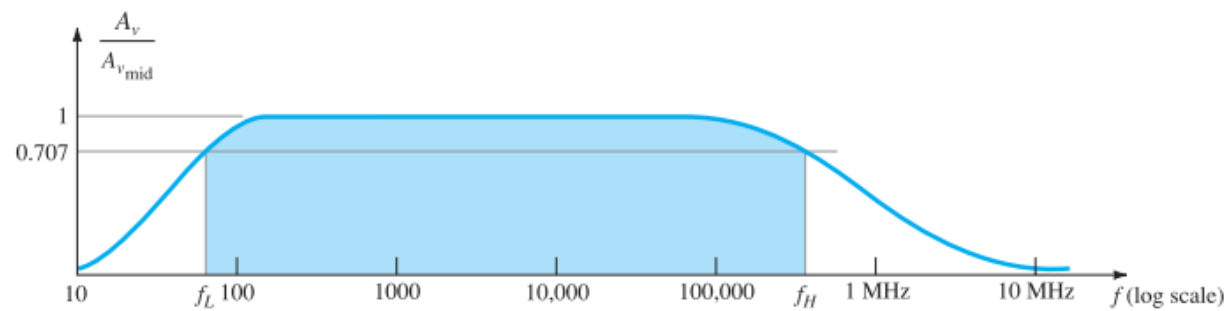

**FIG. 9.9**  
Normalized gain versus frequency plot.


- Decibel plot

$$\left. \frac{A_v}{A_{v_{mid}}} \right|_{dB} = 20 \log_{10} \frac{A_v}{A_{v_{mid}}}$$

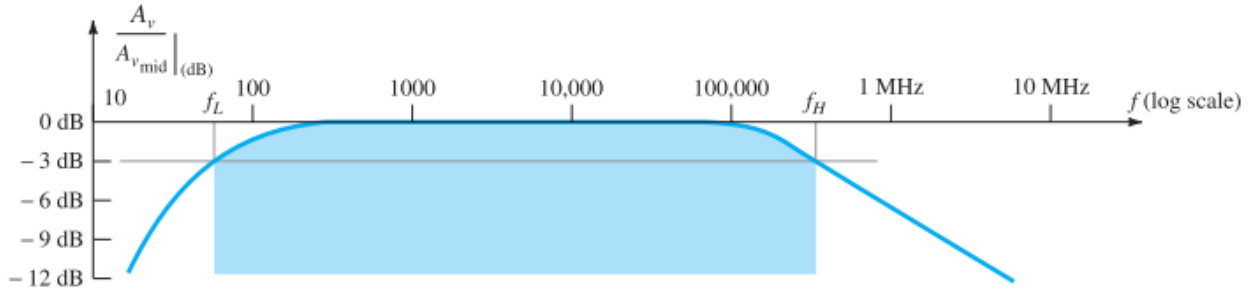

**FIG. 9.12**  
Decibel plot of the normalized gain versus frequency plot of Fig. 9.9.

- Phase plot

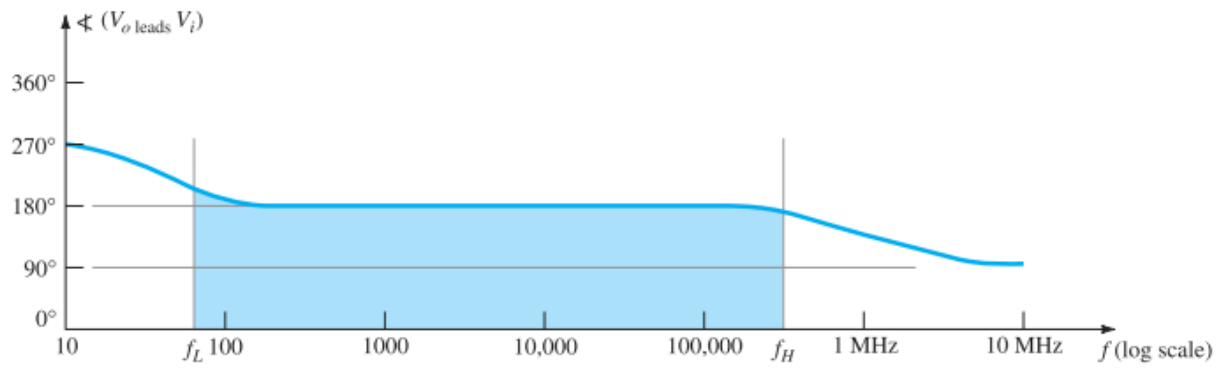

**FIG. 9.13**  
Phase plot for an RC-coupled amplifier system.




# LOW FREQUENCY ANALYSIS- BODE PLOT



# Defining the Low Cutoff Frequency


- In the low-frequency region of the single-stage BJT or FET amplifier, it is the RC combinations formed by the network capacitors  $C_C$ ,  $C_E$ , and  $C_S$  and the network resistive parameters that determine the cutoff frequencies

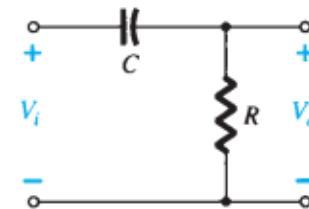

**FIG. 9.14**


*RC combination that will define a low-cutoff frequency.*

- Voltage-Divider Bias Config.

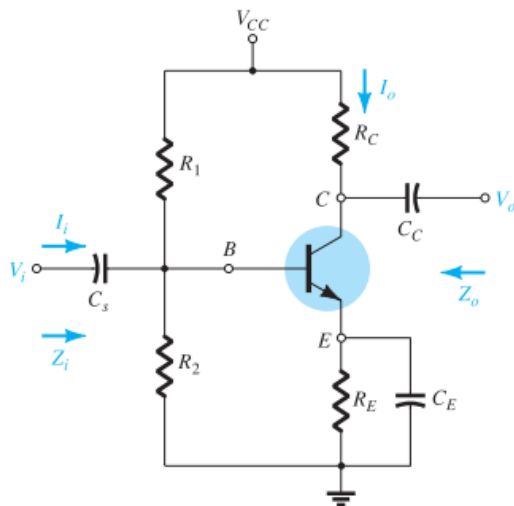

**FIG. 9.15**


*Voltage-divider bias configuration.*

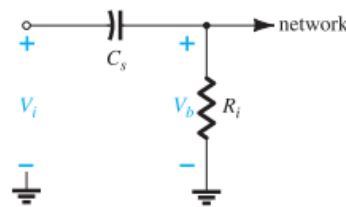

**FIG. 9.16**

*Equivalent input circuit for the network of Fig. 9.15.*

$$Z_i = R_i = R_1 \parallel R_2 \parallel \beta r_e$$

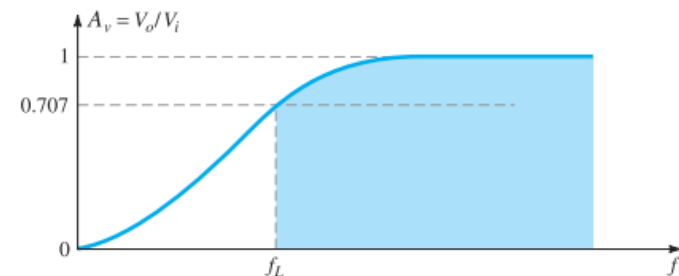

**FIG. 9.19**

*Low-frequency response for the RC circuit of Fig. 9.14.*

$$X_C = \frac{1}{2\pi f_L C} = R$$

$$f_L = \frac{1}{2\pi RC}$$

# Bode Plot

$$A_{v(\text{dB})} = 20 \log_{10} \frac{1}{\sqrt{1 + (f_L/f)^2}}$$

For frequencies where  $f \ll f_L$  or  $(f_L/f)^2 \gg 1$ ,

$$A_{v(\text{dB})} = -20 \log_{10} \frac{f_L}{f} \quad f \ll f_L$$

At  $f = f_L$ :  $\frac{f_L}{f} = 1$  and  $-20 \log_{10} 1 = 0 \text{ dB}$

At  $f = \frac{1}{2}f_L$ :  $\frac{f_L}{f} = 2$  and  $-20 \log_{10} 2 \cong -6 \text{ dB}$

At  $f = \frac{1}{4}f_L$ :  $\frac{f_L}{f} = 4$  and  $-20 \log_{10} 4 \cong -12 \text{ dB}$

At  $f = \frac{1}{10}f_L$ :  $\frac{f_L}{f} = 10$  and  $-20 \log_{10} 10 = -20 \text{ dB}$

- Phase Angle:

$$\theta = \tan^{-1} \frac{f_L}{f}$$

- A change in frequency by a factor of two, equivalent to **one octave**, results in a 6-dB change in the ratio, as shown by the change in gain from  $f_L/2$  to  $f_L$ .
- For a 10:1 change in frequency, equivalent to **one decade**, there is a 20-dB change in the ratio, as demonstrated between the frequencies of  $f_L/10$  and  $f_L$ .
- The piecewise linear plot of the asymptotes and associated breakpoints is called a Bode plot of the magnitude versus frequency.


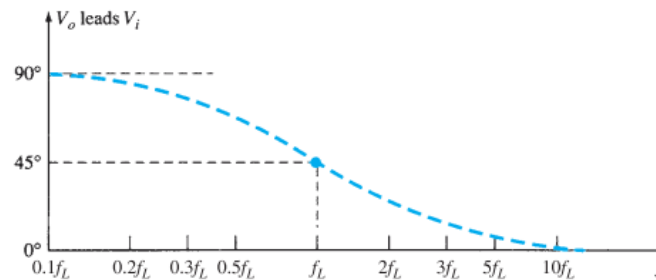


FIG. 9.22

Phase response for the RC circuit of Fig. 9.14.
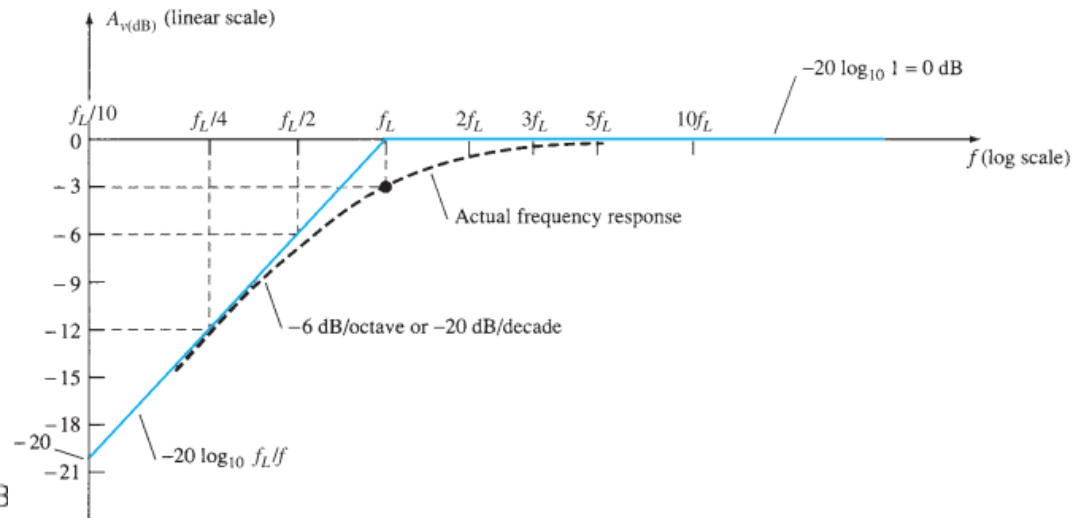
# BJT & JFET AMPLIFIERS LOW FREQUENCY ANALYSIS



# Loaded BJT Amplifier

In the voltage-divider ct.  
 → the capacitors  $C_s$ ,  $C_C$ ,  
 and  $C_E$  will determine the  
 low-frequency response.

$$f_L = \max(f_{Ls}, f_{Lc}, f_{LE})$$

→  $C_s$ :

$$V_b = \frac{R_i V_i}{R_i - jX_{C_s}}$$

$$f_{Ls} = \frac{1}{2\pi R_i C_s} \quad R_i = R_1 \parallel R_2 \parallel \beta r_e$$

$$A_v = \frac{V_o}{V_i} = \frac{1}{1 - j(f_{Ls}/f)}$$

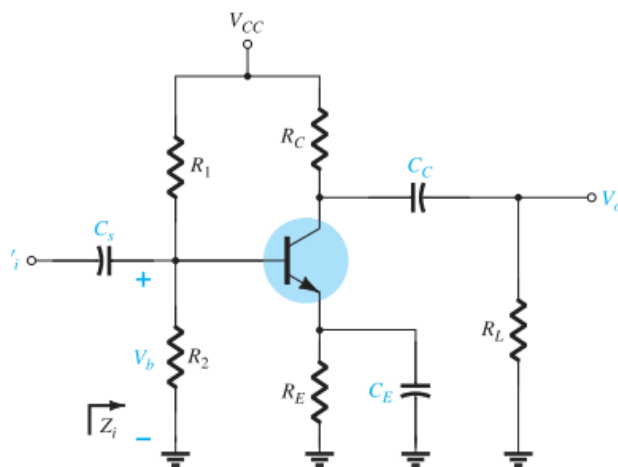


FIG. 9.25

Loaded BJT amplifier with capacitors that affect the low-frequency response.

→  $C_C$ :

$$f_{Lc} = \frac{1}{2\pi(R_o + R_L)C_C}$$

$$R_o = R_C \parallel r_o$$

→  $C_E$ :

$$f_{LE} = \frac{1}{2\pi R_e C_E}$$

$$R_e = R_E \parallel \left( \frac{R_1 \parallel R_2}{\beta} + r_e \right)$$

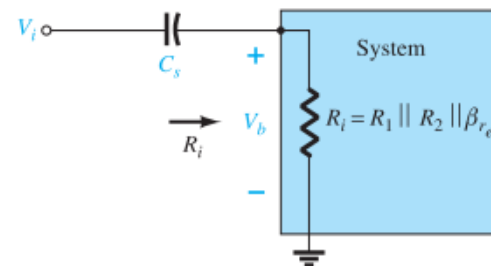


FIG. 9.26

Determining the effect of  $C_s$  on the low-frequency response.

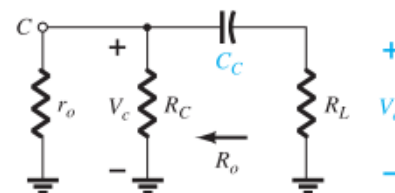


FIG. 9.28

Localized ac equivalent for  $C_C$  with  $V_i = 0$  V.


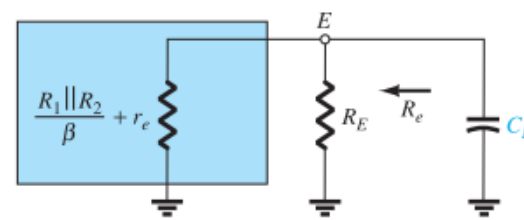


FIG. 9.30


Localized ac equivalent of  $C_E$ .

# Impact of $R_s$

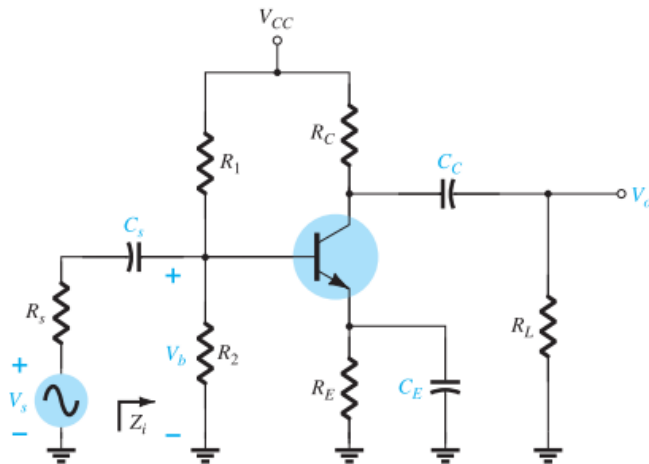

**FIG. 9.32**

Determining the effect of  $R_s$  on the low-frequency response of a BJT amplifier.

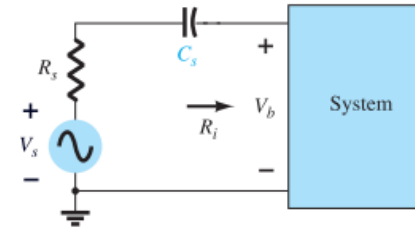

**FIG. 9.33**

Determining the effect of  $C_s$  on the low-frequency response.


$$f_{L_s} = \frac{1}{2\pi(R_i + R_s)C_s}$$

$$f_{L_C} = \frac{1}{2\pi(R_o + R_L)C_C}$$

$$f_{L_E} = \frac{1}{2\pi R_e C_E}$$

$$R_e = R_E \left\| \left( \frac{R'_s}{\beta} + r_e \right) \right. \text{ and } R'_s = R_s \parallel R_1 \parallel R_2$$

# Example

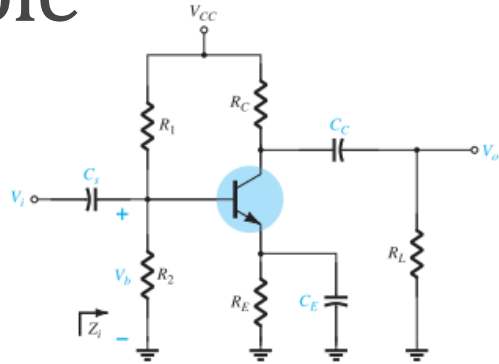

$$C_s = 10 \mu\text{F}, \quad C_E = 20 \mu\text{F}, \quad C_C = 1 \mu\text{F}$$

$$R_1 = 40 \text{ k}\Omega, \quad R_2 = 10 \text{ k}\Omega, \quad R_E = 2 \text{ k}\Omega, \quad R_C = 4 \text{ k}\Omega,$$

$$R_L = 2.2 \text{ k}\Omega$$

## EXAMPLE 9.12

- Repeat the analysis of Example 9.11 but with a source resistance  $R_s$  of 1 k $\Omega$ . The gain of interest will now be  $V_o/V_s$  rather than  $V_o/V_i$ . Compare results.
- Sketch the frequency response using a Bode plot.
- Verify the results using PSpice.

**Solution:** a. The dc conditions remain the same:

$$r_e = 15.76 \Omega \text{ and } \beta r_e = 1.576 \text{ k}\Omega$$

**Midband Gain**  $A_v = \frac{V_o}{V_i} = \frac{-R_C \parallel R_L}{r_e} \cong -90$  as before

The input impedance is given by

$$Z_i = R_i = R_1 \parallel R_2 \parallel \beta r_e$$

$$= 40 \text{ k}\Omega \parallel 10 \text{ k}\Omega \parallel 1.576 \text{ k}\Omega$$

$$\cong 1.32 \text{ k}\Omega$$

and from Fig. 9.35,

$$V_b = \frac{R_i V_s}{R_i + R_s}$$

$$\text{or } \frac{V_b}{V_s} = \frac{R_i}{R_i + R_s} = \frac{1.32 \text{ k}\Omega}{1.32 \text{ k}\Omega + 1 \text{ k}\Omega} = 0.569$$

so that

$$A_{v_s} = \frac{V_o}{V_s} = \frac{V_o}{V_i} \cdot \frac{V_b}{V_s} = (-90)(0.569)$$

$$= -51.21$$

**C<sub>s</sub>**  $R_i = R_1 \parallel R_2 \parallel \beta r_e = 40 \text{ k}\Omega \parallel 10 \text{ k}\Omega \parallel 1.576 \text{ k}\Omega \cong 1.32 \text{ k}\Omega$

$$f_{L_s} = \frac{1}{2\pi(R_s + R_i)C_s} = \frac{1}{(6.28)(1 \text{ k}\Omega + 1.32 \text{ k}\Omega)(10 \mu\text{F})}$$

$$f_{L_s} \cong 6.86 \text{ Hz vs. } 12.06 \text{ Hz without } R_s$$

**C<sub>C</sub>**  $f_{L_C} = \frac{1}{2\pi(R_C + R_L)C_C}$

$$= \frac{1}{(6.28)(4 \text{ k}\Omega + 2.2 \text{ k}\Omega)(1 \mu\text{F})}$$

$$\cong 25.68 \text{ Hz as before}$$


**C<sub>E</sub>**  $R'_s = R_s \parallel R_1 \parallel R_2 = 1 \text{ k}\Omega \parallel 40 \text{ k}\Omega \parallel 10 \text{ k}\Omega \cong 0.889 \text{ k}\Omega$

$$R_e = R_E \parallel \left( \frac{R'_s}{\beta} + r_e \right) = 2 \text{ k}\Omega \parallel \left( \frac{0.889 \text{ k}\Omega}{100} + 15.76 \Omega \right)$$

$$= 2 \text{ k}\Omega \parallel (8.89 \Omega + 15.76 \Omega) = 2 \text{ k}\Omega \parallel 24.65 \Omega \cong 24.35 \Omega$$

$$f_{L_E} = \frac{1}{2\pi R_e C_E} = \frac{1}{(6.28)(24.35 \Omega)(20 \mu\text{F})} = \frac{10^6}{3058.36}$$
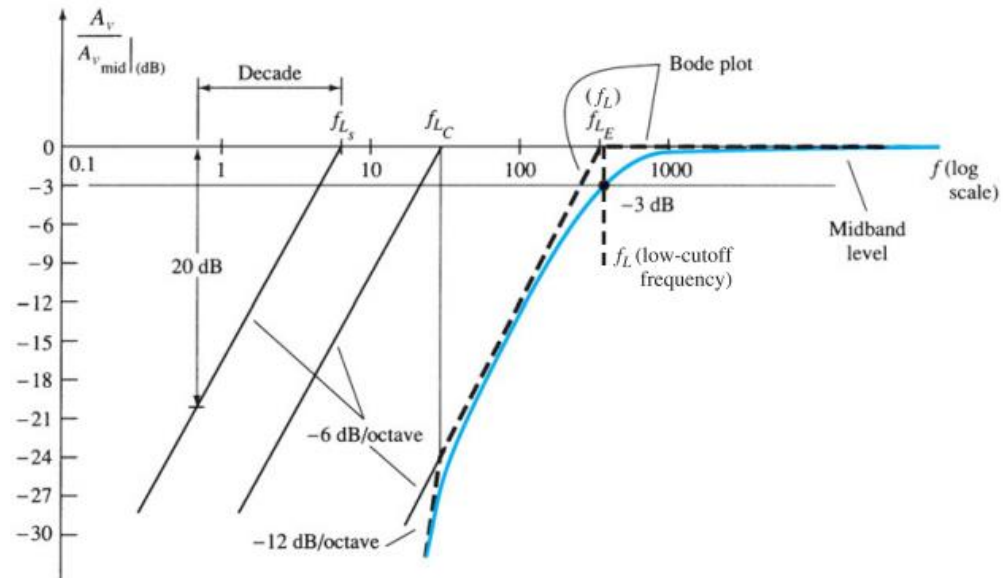
$$\cong 327 \text{ Hz vs. } 87.13 \text{ Hz without } R_s.$$



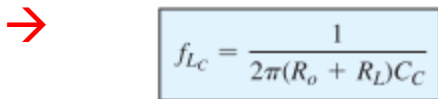


**FIG. 9.36**

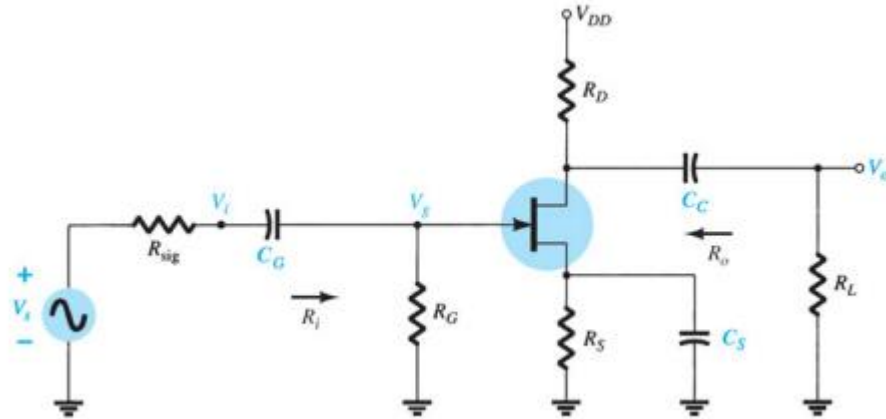
Low-frequency plot for the network of Example 9.12.



# FET Amplifier

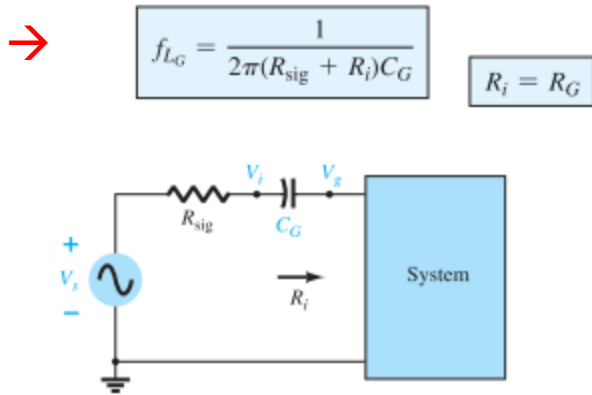


$$R_o = R_D \parallel r_d$$

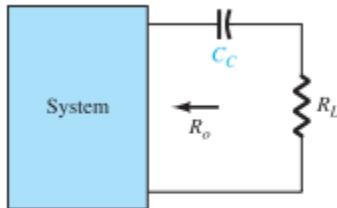


**FIG. 9.39**

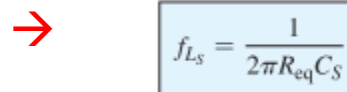Determining the effect of  $C_C$  on the low-frequency response.



$$R_{eq} = \frac{R_S}{1 + R_S(1 + g_m r_d)/(r_d + R_D \parallel R_L)}$$

$$R_{eq} = R_S \parallel \frac{1}{g_m} \quad r_d \approx \infty \Omega$$

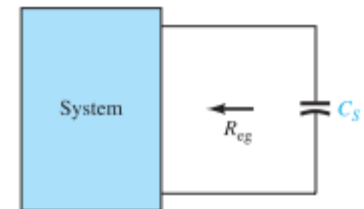

**FIG. 9.40**

Determining the effect of  $C_S$  on the low-frequency response.

# MILLER EFFECT



# Miller input capacitance

$$C_{M_i} = (1 - A_v)C_f$$

- In the high-frequency region, the capacitive elements of importance are the interelectrode (between-terminals) capacitances internal to the active device and the wiring capacitance between leads of the network.
- For any inverting amplifier, the input capacitance will be increased by a Miller effect capacitance sensitive to the gain of the amplifier and the interelectrode (parasitic) capacitance between the input and output terminals of the active device.

Applying Kirchoff's current law gives

$$I_i = I_1 + I_2$$

Using Ohm's law yields

$$I_i = \frac{V_i}{Z_i}, \quad I_1 = \frac{V_i}{R_i}$$

and

$$I_2 = \frac{V_i - V_o}{X_{C_f}} = \frac{V_i - A_v V_i}{X_{C_f}} = \frac{(1 - A_v)V_i}{X_{C_f}}$$

Substituting, we obtain

$$\frac{V_i}{Z_i} = \frac{V_i}{R_i} + \frac{(1 - A_v)V_i}{X_{C_f}}$$

and



$$\frac{1}{Z_i} = \frac{1}{R_i} + \frac{1}{X_{C_f}/(1 - A_v)}$$

but

$$\frac{X_{C_f}}{1 - A_v} = \frac{1}{\underbrace{\omega(1 - A_v)C_f}_{C_M}} = X_{C_M}$$

and

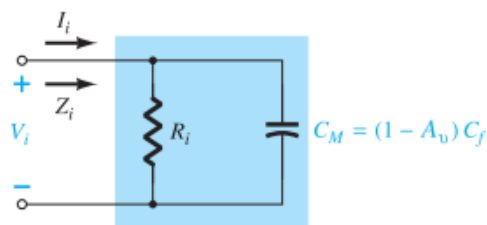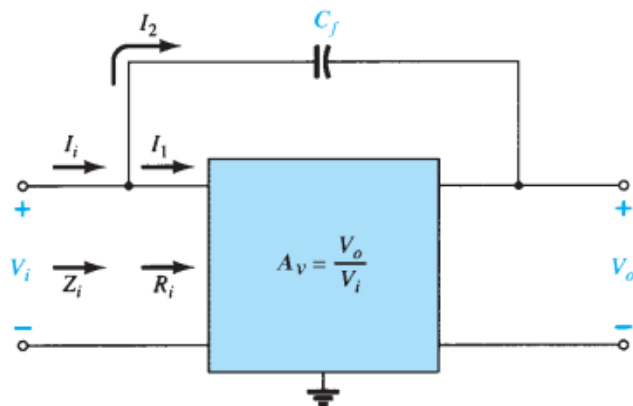
$$\frac{1}{Z_i} = \frac{1}{R_i} + \frac{1}{X_{C_M}}$$


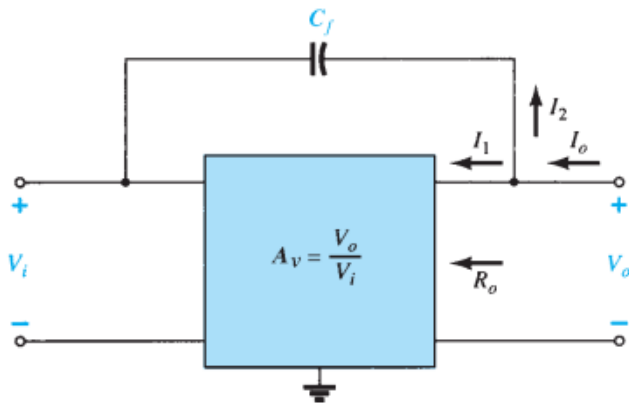
# Miller output capacitance

$$C_{M_o} = \left(1 - \frac{1}{A_v}\right) C_f$$

- A positive value for  $A_v$  would result in a negative capacitance (for  $A_v > 1$ ).
- For noninverting amplifiers such as the common-base and emitter-follower configurations, the Miller effect capacitance is not a contributing concern for high-frequency applications.
- The Miller effect will also increase the level of output capacitance, which must also be considered when the high-frequency cutoff is determined.



$$I_o = I_1 + I_2$$

$$I_1 = \frac{V_o}{R_o} \quad \text{and} \quad I_2 = \frac{V_o - V_i}{X_{C_f}}$$

The resistance  $R_o$  is usually sufficiently large to permit ignoring the first term of the equation compared to the second term and assuming that

$$I_o \cong \frac{V_o - V_i}{X_{C_f}}$$

Substituting  $V_i = V_o/A_v$  from  $A_v = V_o/V_i$  results in

$$I_o = \frac{V_o - V_o/A_v}{X_{C_f}} = \frac{V_o(1 - 1/A_v)}{X_{C_f}}$$

and

$$\frac{I_o}{V_o} = \frac{1 - 1/A_v}{X_{C_f}}$$

or

$$\frac{V_o}{I_o} = \frac{X_{C_f}}{1 - 1/A_v} = \frac{1}{\omega C_f(1 - 1/A_v)} = \frac{1}{\omega C_{M_o}}$$

$$C_{M_o} = \left(1 - \frac{1}{A_v}\right) C_f$$

$$C_{M_o} \cong C_f \quad |A_v| \gg 1$$


# BJT & JFET AMPLIFIERS HIGH FREQUENCY RESPONSE



# High Frequency Response


- At the high-frequency end, there are two factors that define the 3-dB cutoff point:
  1. the network capacitance (parasitic and introduced)
  2. the frequency dependence of  $h_{fe}$  ( $\beta$ ).

- For RC circuit:

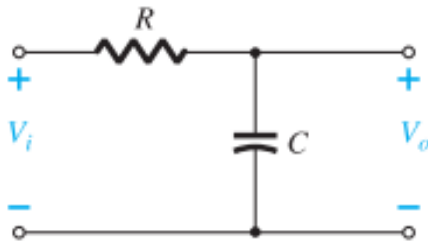

**FIG. 9.45**

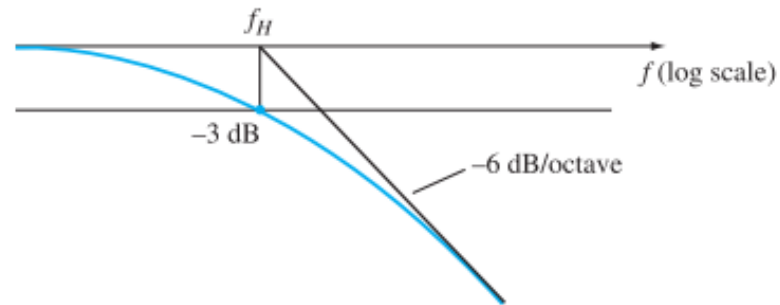
*RC combination that will define a high-cutoff frequency.*



$$A_v = \frac{1}{1 + j(f/f_H)}$$
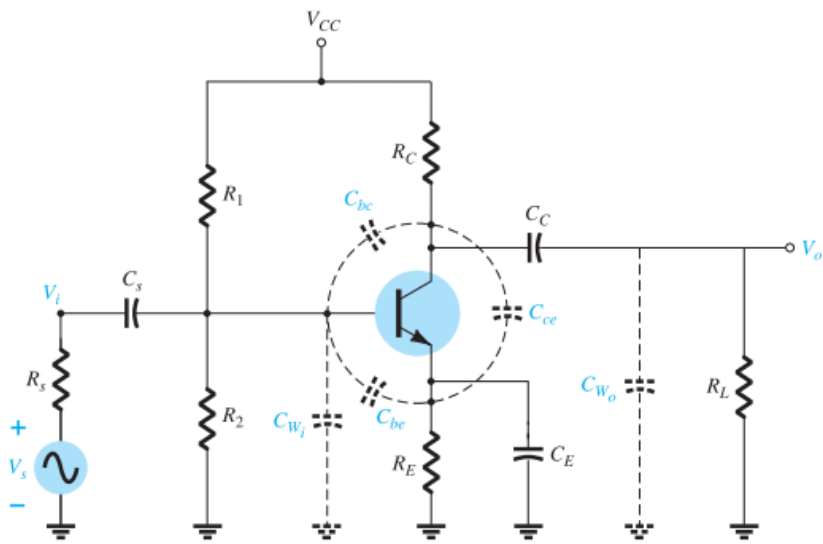
# 1. Network Parameters :

- At high frequencies, the various parasitic capacitances ( $C_{be}$ ,  $C_{bc}$ ,  $C_{ce}$ ) of the transistor are included with the wiring capacitances ( $C_{Wi}$ ,  $C_{Wo}$ ).



$$f_{H_i} = \frac{1}{2\pi R_{Th_i} C_i}$$

$$R_{Th_i} = R_s \parallel R_1 \parallel R_2 \parallel \beta r_e$$

$$C_i = C_{W_i} + C_{be} + C_{M_i} = C_{W_i} + C_{be} + (1 - A_v)C_{bc}$$

$$f_{H_o} = \frac{1}{2\pi R_{Th_o} C_o}$$




$$R_{Th_o} = R_C \parallel R_L \parallel r_o$$

$$C_o = C_{W_o} + C_{ce} + C_{M_o}$$

$$C_o = C_{W_o} + C_{ce} + (1 - 1/A_v)C_{bc}$$

$$1 \gg 1/A_v$$

$$C_o \cong C_{W_o} + C_{ce} + C_{bc}$$

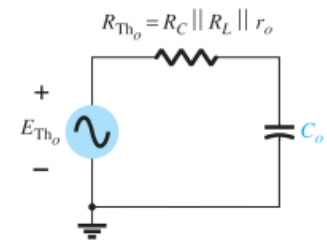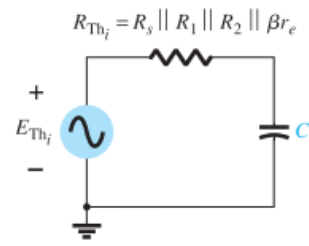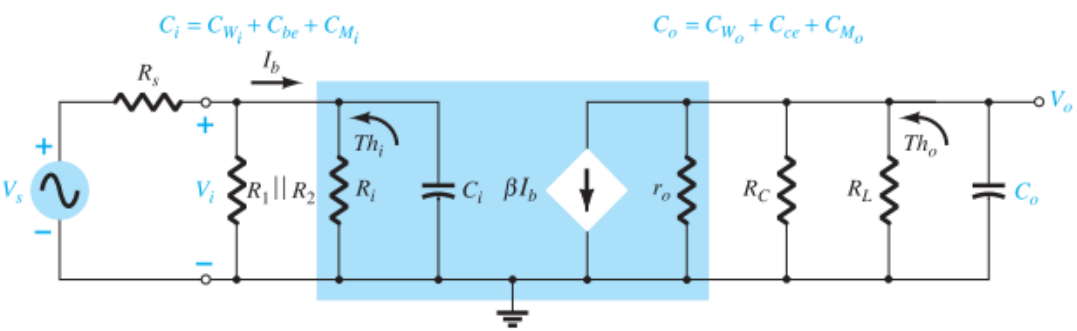

# 2. $h_{fe}$ (or $\beta$ ) Variation

- The variation of  $h_{fe}$  (or  $\beta$ ) with frequency approaches the following relationship:

$$h_{fe} = \frac{h_{fe\text{mid}}}{1 + j(f/f_\beta)}$$

- The quantity,  $f_\beta$ , is determined by a set of parameters employed in the hybrid  $\pi$  model

$$f_\beta (\text{often appearing as } f_{h_{fe}}) = \frac{1}{2\pi r_\pi (C_\pi + C_u)}$$

$$f_\beta = \frac{1}{h_{fe\text{mid}}} \frac{1}{2\pi r_e (C_\pi + C_u)}$$

- $f_\beta$  is a function of the bias configuration.
- the small change in  $h_{fb}$  for the chosen frequency range, revealing that the common-base configuration displays improved high-frequency characteristics over the common-emitter configuration.


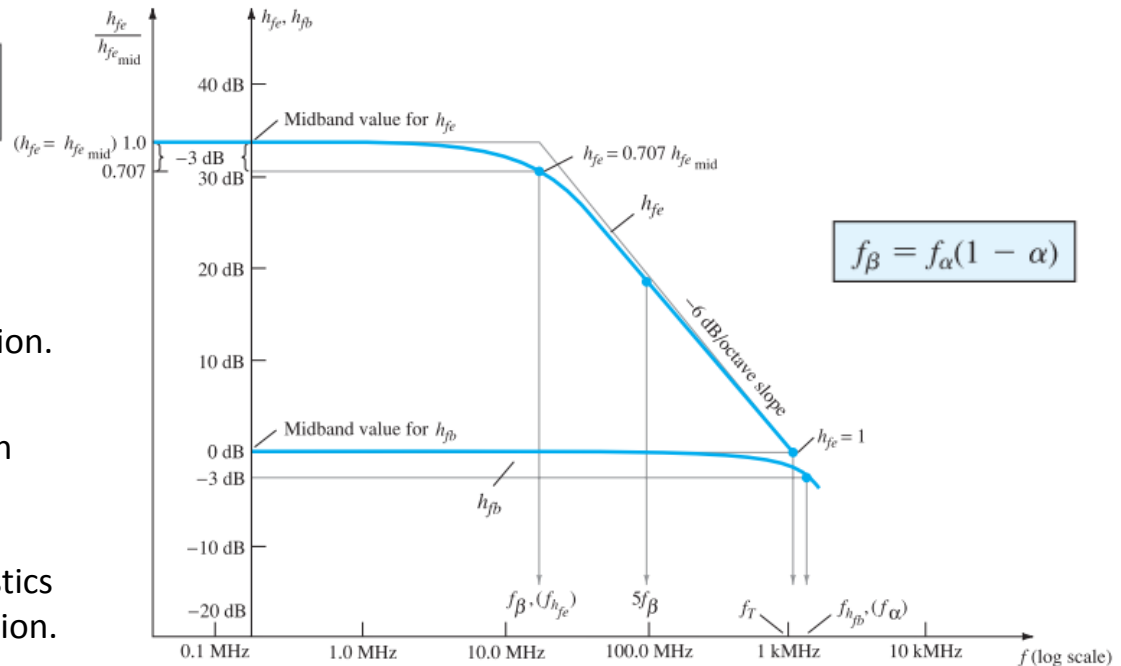


FIG. 9.51  $h_{fe}$  and  $h_{fb}$  versus frequency in the high-frequency region.

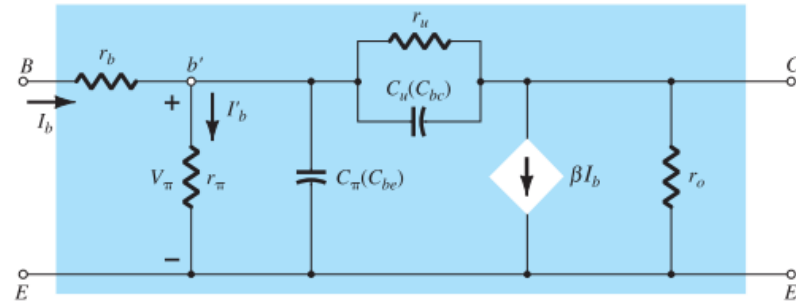



# Example

**EXAMPLE 9.14** Use the network of Fig. 9.47 with the same parameters as in Example 9.12, that is,

$$R_s = 1 \text{ k}\Omega, R_1 = 40 \text{ k}\Omega, R_2 = 10 \text{ k}\Omega, R_E = 2 \text{ k}\Omega, R_C = 4 \text{ k}\Omega, R_L = 2.2 \text{ k}\Omega$$


$$C_s = 10 \text{ }\mu\text{F}, C_C = 1 \text{ }\mu\text{F}, C_E = 20 \text{ }\mu\text{F}$$

$$h_{fe} = 100, r_o = \infty \text{ }\Omega, V_{CC} = 20 \text{ V}$$

with the addition of

$$C_{\pi}(C_{be}) = 36 \text{ pF}, C_u(C_{bc}) = 4 \text{ pF}, C_{ce} = 1 \text{ pF}, C_{W_i} = 6 \text{ pF}, C_{W_o} = 8 \text{ pF}$$

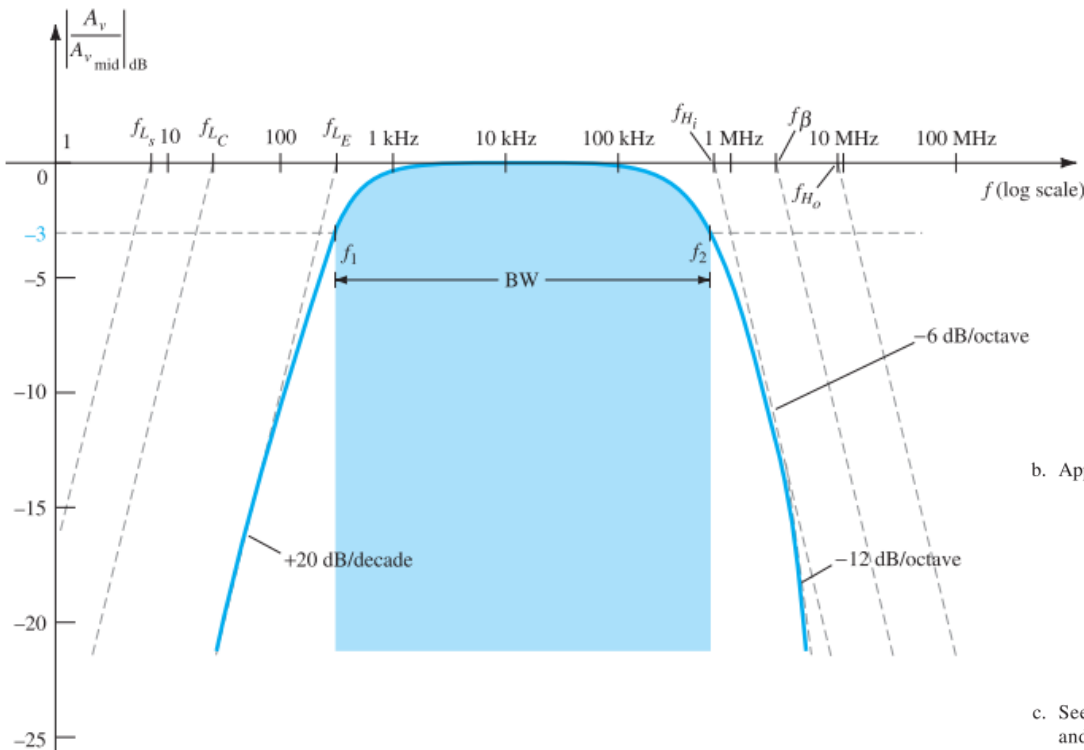- Determine  $f_{H_i}$  and  $f_{H_o}$ .
- Find  $f_{\beta}$  and  $f_T$ .
- Sketch the frequency response for the low- and high-frequency regions using the results of Example 9.12 and the results of parts (a) and (b).



## Solution:

- a. From Example 9.12:

$$\beta r_e = 1.576 \text{ k}\Omega, \quad A_{v_{mid}}(\text{amplifier—not including effects of } R_s) = -90$$

$$\text{and} \quad R_{Th_i} = R_s \parallel R_1 \parallel R_2 \parallel \beta r_e = 1 \text{ k}\Omega \parallel 40 \text{ k}\Omega \parallel 10 \text{ k}\Omega \parallel 1.576 \text{ k}\Omega$$

$$\cong 0.57 \text{ k}\Omega$$

$$\text{with} \quad C_i = C_{W_i} + C_{be} + (1 - A_v)C_{bc}$$

$$= 6 \text{ pF} + 36 \text{ pF} + [1 - (-90)]4 \text{ pF}$$

$$= 406 \text{ pF}$$

$$f_{H_i} = \frac{1}{2\pi R_{Th_i} C_i} = \frac{1}{2\pi(0.57 \text{ k}\Omega)(406 \text{ pF})}$$

$$= \mathbf{687.73 \text{ kHz}}$$

$$R_{Th_o} = R_C \parallel R_L = 4 \text{ k}\Omega \parallel 2.2 \text{ k}\Omega = 1.419 \text{ k}\Omega$$

$$C_o = C_{W_o} + C_{ce} + C_{M_o} = 8 \text{ pF} + 1 \text{ pF} + \left(1 - \frac{1}{-90}\right)4 \text{ pF}$$

$$= 13.04 \text{ pF}$$

$$f_{H_o} = \frac{1}{2\pi R_{Th_o} C_o} = \frac{1}{2\pi(1.419 \text{ k}\Omega)(13.04 \text{ pF})}$$

$$= \mathbf{8.6 \text{ MHz}}$$

- b. Applying Eq. (9.63) gives

$$f_{\beta} = \frac{1}{2\pi h_{fe_{mid}} r_e (C_{be} + C_{bc})}$$

$$= \frac{1}{2\pi(100)(15.76 \text{ }\Omega)(36 \text{ pF} + 4 \text{ pF})} = \frac{1}{2\pi(100)(15.76 \text{ }\Omega)(40 \text{ pF})}$$

$$= \mathbf{2.52 \text{ MHz}}$$

$$f_T = h_{fe_{mid}} f_{\beta} = (100)(2.52 \text{ MHz})$$

$$= \mathbf{252 \text{ MHz}}$$

- c. See Fig. 9.54. The corner frequency  $f_{H_i}$  will determine the high cutoff frequency and the bandwidth of the amplifier. The upper cutoff frequency is very close to 600 kHz.


# Gain-Bandwidth Product

- There is a Figure of Merit applied to amplifiers called the Gain-Bandwidth Product (GBP) that is commonly used to initiate the design process of an amplifier.
- It provides important information about the relationship between the gain of the amplifier and the expected operating frequency range.

$$GBP = A_{v_{mid}} BW$$

$$BW = f_H - f_L \cong f_H$$

$$f_T = A_{v_{mid}} f_H \quad (\text{Hz})$$

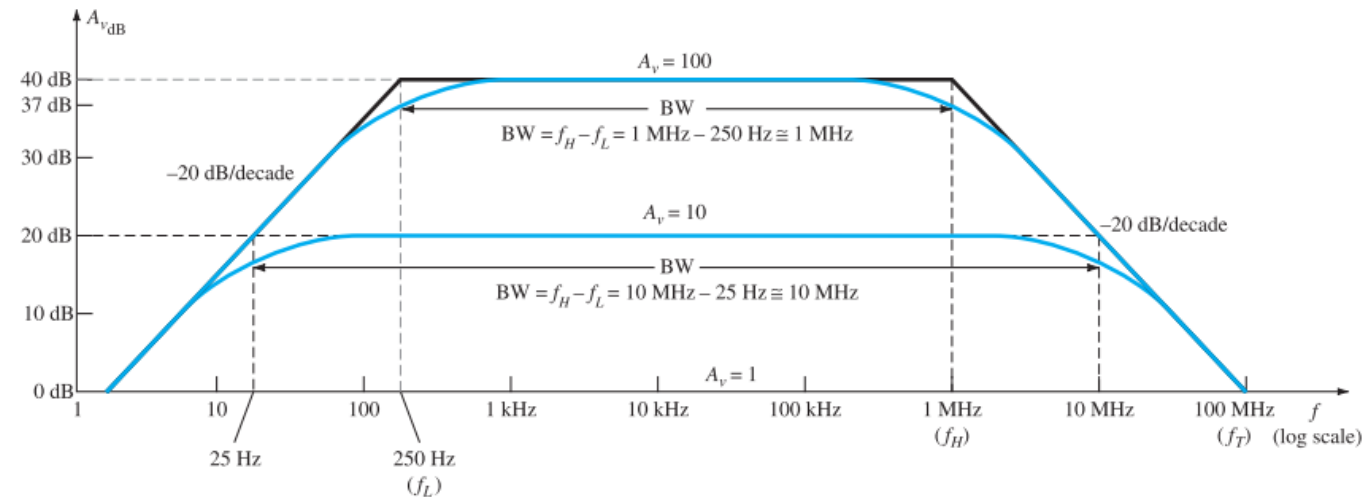



**FIG. 9.53**

*Finding the bandwidth at two different gain levels.*

- at any level of gain the product of the two remains a constant.
- the frequency  $f_T$  is called the unity-gain frequency and is always equal to the product of the midband gain of an amplifier and the bandwidth at any level of gain.



# FET Amplifier

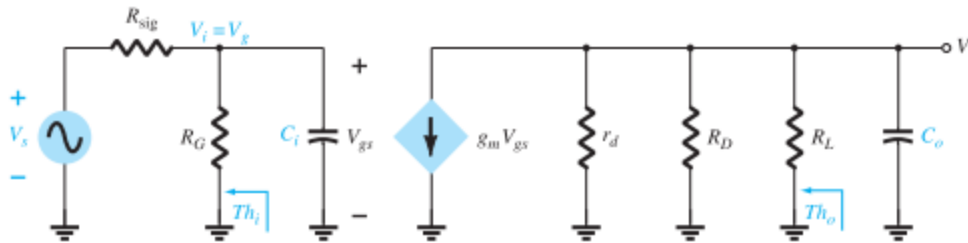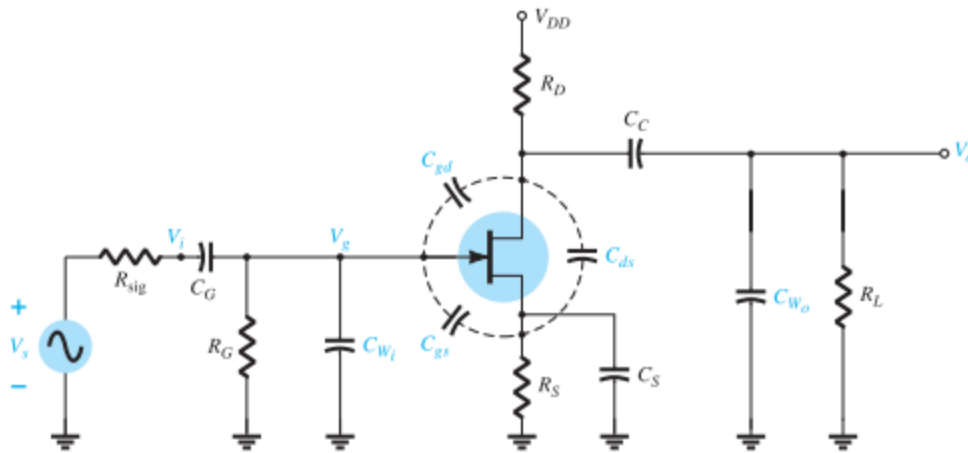

$$f_{H_i} = \frac{1}{2\pi R_{Th_i} C_i}$$

$$R_{Th_i} = R_{sig} \parallel R_G$$

$$C_i = C_{W_i} + C_{gs} + C_{M_i}$$

$$C_{M_i} = (1 - A_v) C_{gd}$$

$$f_{H_o} = \frac{1}{2\pi R_{Th_o} C_o}$$

$$R_{Th_o} = R_D \parallel R_L \parallel r_d$$

$$C_o = C_{W_o} + C_{ds} + C_{M_o}$$

$$C_{M_o} = \left(1 - \frac{1}{A_v}\right) C_{gd}$$

- For more details, refer to:
  - Chapter 9, Electronic Devices and Circuits, Boylestad.
- The lecture is available online at:
  - [https://speakerdeck.com/ahmad\\_elbanna](https://speakerdeck.com/ahmad_elbanna)
- For inquiries, send to:
  - [ahmad.elbanna@feng.bu.edu.eg](mailto:ahmad.elbanna@feng.bu.edu.eg)