



BENHA UNIVERSITY
FACULTY OF ENGINEERING AT SHOUBRA

ECE-322
Electronic Circuits (B)

Lecture #2
Operational Amplifiers

Instructor:
Dr. Ahmad El-Banna



Agenda



- 1 Introduction
- 2 Op-Amps Input Modes and Parameters
- 3 Op-Amps with Negative Feedback
- 4 Bias Current and Offset Voltage
- 5 Open & Closed Loop Frequency Responses

INTRODUCTION




Introduction to Op-Amps

- Early operational amplifiers (op-amps) were used primarily to perform mathematical operations such as addition, subtraction, integration, and differentiation—thus the term **operational**.
- These early devices were constructed with vacuum tubes and worked with high voltages.
- Today's op-amps are linear integrated circuits (**ICs**) that use relatively low dc supply voltages and are reliable and inexpensive.

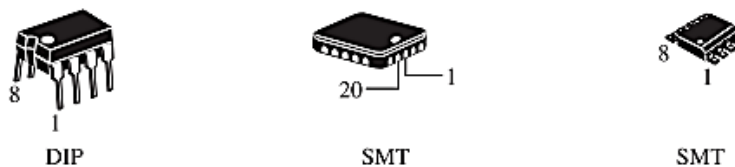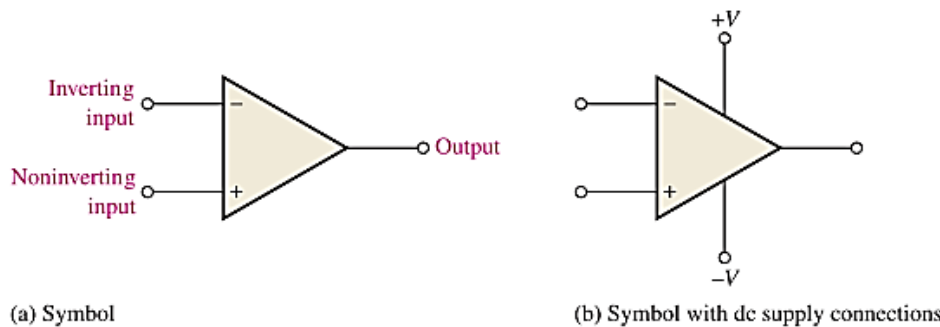


(c) Typical packages. Pin 1 is indicated by a notch or dot on dual in-line (DIP) and surface-mount technology (SMT) packages, as shown.

Ideal & Practical Op-Amp

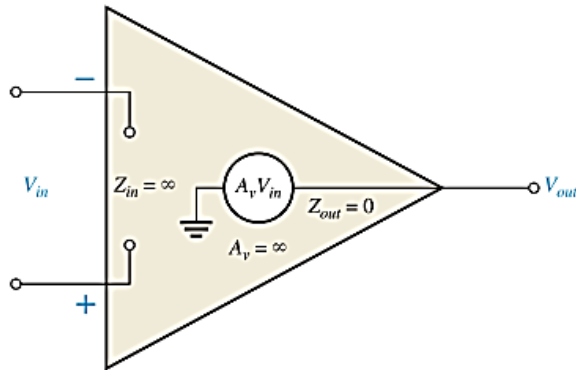


(a) Ideal op-amp representation

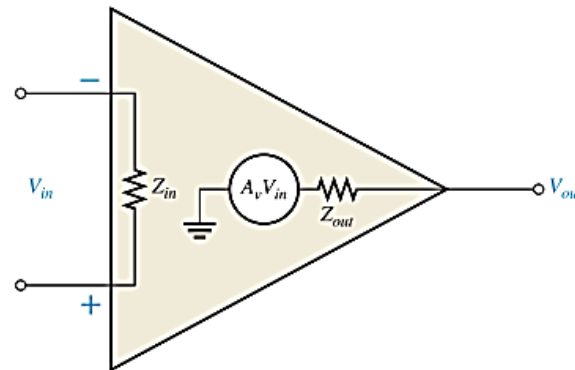


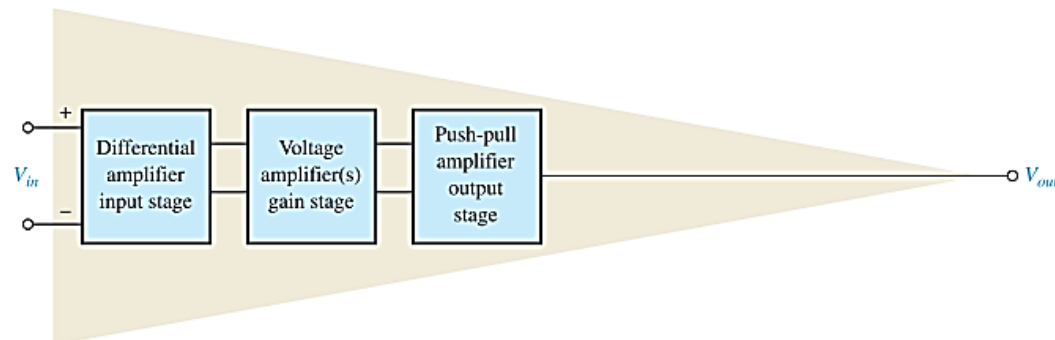(b) Practical op-amp representation

- **Internal Block Diagram of an Op-Amp**



741 Op-Amp Internal Circuit

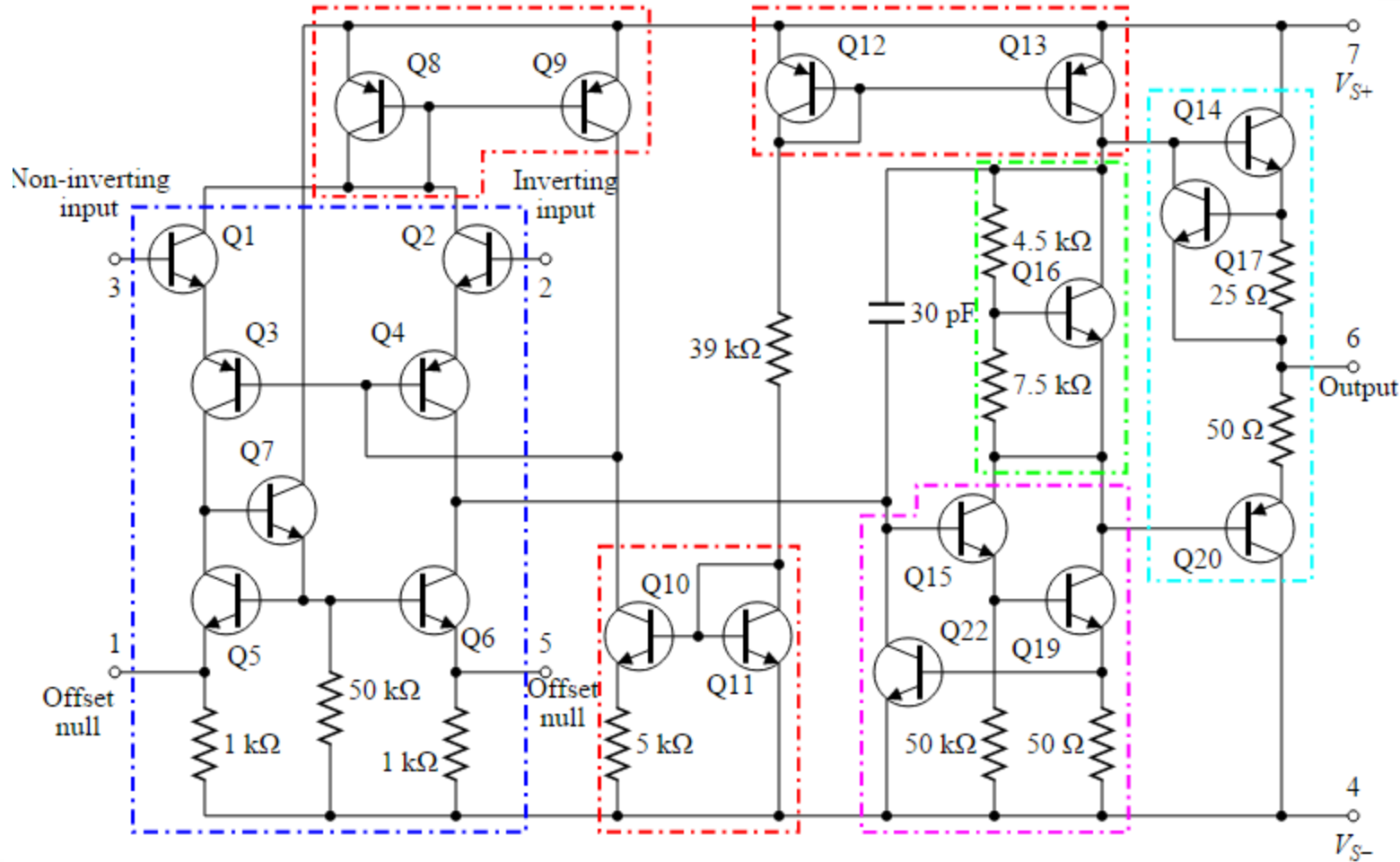

A component-level diagram of the common 741 op-amp. Dotted lines outline: current mirrors (red); differential amplifier (blue); class A gain stage (magenta); voltage level shifter (green); output stage (cyan).




OP-AMPS INPUT MODES AND PARAMETERS




Input Signal Modes


- Single-ended differential mode

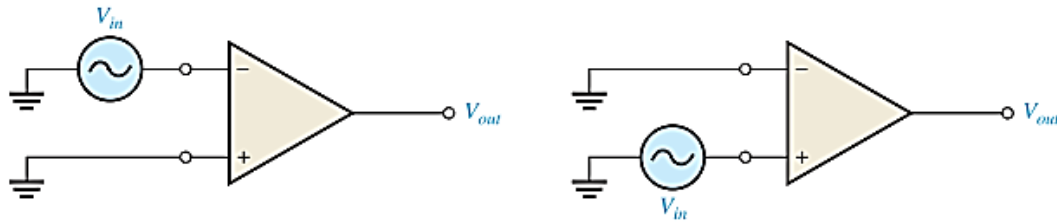

- Double-ended differential mode

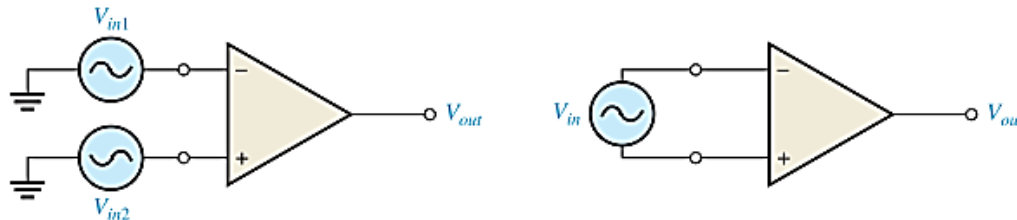

- Common-mode operation

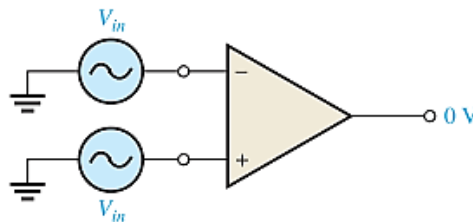

Op-Amp Parameters

Common-Mode Rejection Ratio

- The common-mode rejection ratio, **CMRR**:

It's the ratio of the open-loop differential voltage gain, A_{ol} , to the common-mode gain, A_{cm} .

$$CMRR = \frac{A_{ol}}{A_{cm}}$$

$$CMRR = 20 \log \left(\frac{A_{ol}}{A_{cm}} \right)$$

- *Open-loop voltage gain* can range up to 200,000 (106 dB) and is not a well-controlled parameter.
- Datasheets often refer to the open-loop voltage gain as the *large-signal voltage gain*.
- A CMRR of 100,000, for example, means that the desired input signal (differential) is amplified 100,000 times more than the unwanted noise (common-mode).

Op-Amp Parameters..

Maximum Output Voltage Swing ($V_{O(p-p)}$)

- With no input signal, the output of an op-amp is ideally 0 V. This is called the quiescent output voltage.
- When an input signal is applied, the ideal limits of the peak-to-peak output signal are $\pm V_{CC}$.
- In practice this ideal can be approached but never reached.
- $V_{O_{pp}}$ varies with the load connected to the op-amp and increases directly with load resistance.

Example: $V_{O(p-p)}$ of ± 13 V for $V_{CC} = \pm 15$ V when $R_L = 2$ k Ω
Fairchild KA741
 $V_{O(p-p)}$ increases to ± 14 V when $R_L = 10$ k Ω

Input Offset Voltage:


- The ideal op-amp produces zero volts out for zero volts in.
- In a practical op-amp, a small dc voltage, $V_{OUT(error)}$, appears at the output when no differential input voltage is applied.
- Its primary cause is a slight mismatch of the base-emitter voltages of the differential amplifier input stage of an op-amp.
- The input offset voltage, V_{OS} , is the differential dc voltage required between the inputs to force the output to zero volts
- Typical values V_{OS} , are in the range of 2 mV or less.

Op-Amp Parameters

Input Bias Current



- The input bias current is the dc current required by the inputs of the amplifier to properly operate the first stage.
- Input bias current is the average of the two op-amp input currents
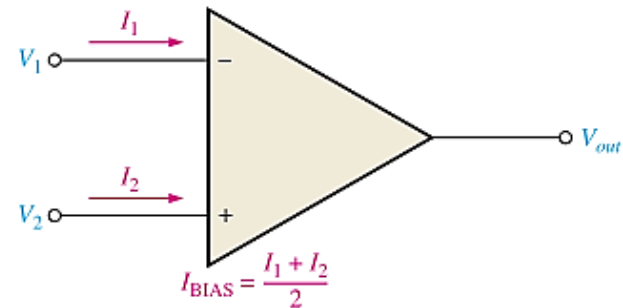
$$I_{\text{BIAS}} = \frac{I_1 + I_2}{2}$$



Input Impedance

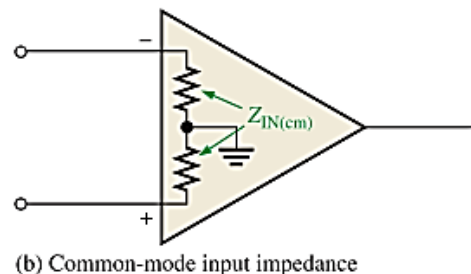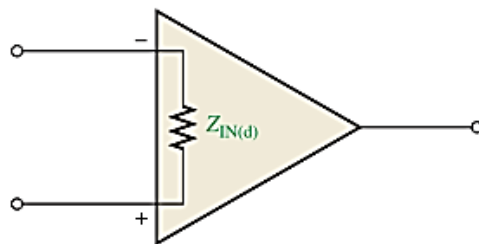- The differential input impedance is the total resistance between the inverting and the non-inverting inputs.
- The common-mode input impedance is the resistance between each input and ground and is measured by determining the change in bias current for a given change in common-mode input voltage.



Op-Amp Parameters...

Input Offset Current


- Ideally, the two input bias currents are equal, and thus their difference is zero.
- In a practical op-amp, the bias currents are not exactly equal.
- The input offset current, I_{OS} , is the difference of the input bias currents, expressed as an absolute value.

$$I_{OS} = |I_1 - I_2|$$

$$V_{OS} = I_1 R_{in} - I_2 R_{in} = (I_1 - I_2) R_{in}$$


$$V_{OS} = I_{OS} R_{in}$$

$$V_{OUT(error)} = A_v I_{OS} R_{in}$$

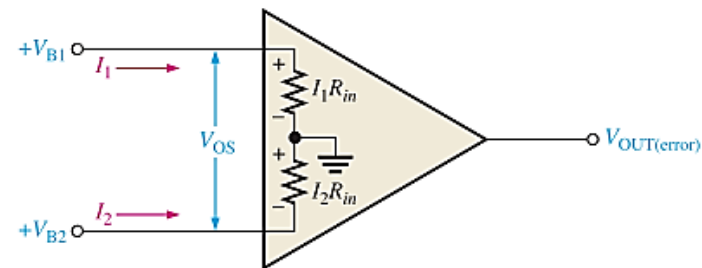

Output Impedance

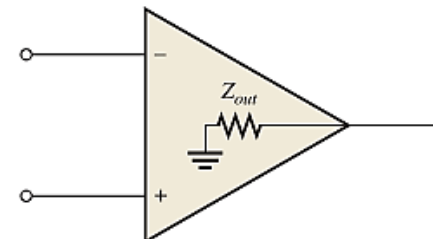- The output impedance is the resistance viewed from the output terminal of the op-amp




Op-Amp Parameters....

Slew Rate


- The maximum rate of change of the output voltage in response to a step input voltage is the slew rate of an op-amp.
- The slew rate is dependent upon the high-frequency response of the amplifier stages within the op-amp.

$$\text{Slew rate} = \frac{\Delta V_{out}}{\Delta t}$$

- **Slew-rate measurement**

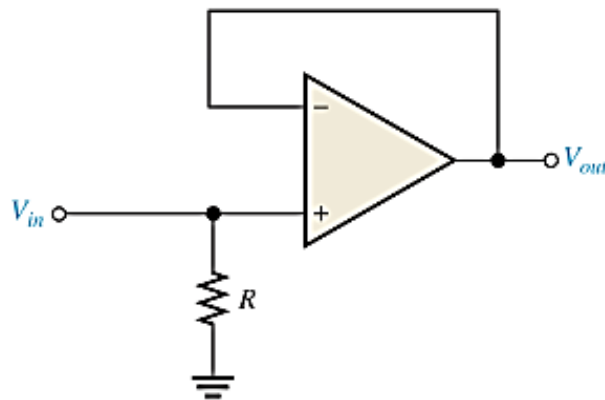

(a) Test circuit

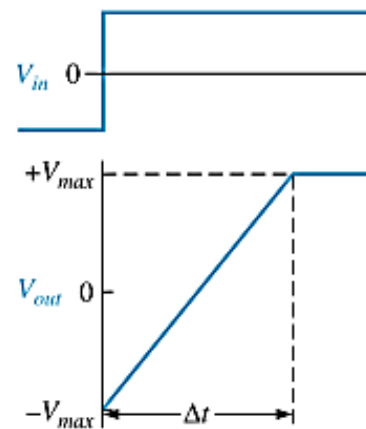

(b) Step input voltage and the resulting output voltage


Op-Amp Parameters.....

Frequency Response

- The internal amplifier stages that make up an op-amp have voltage gains limited by junction capacitances.
- An op-amp has no internal coupling capacitors, however; therefore, the low-frequency response extends down to dc (0 Hz).

Noise Specification

- Noise has become a more important issue !
- Noise is defined as an unwanted signal that affects the quality of a desired signal.
- There are two basic forms of noise.
- At low frequencies, noise is inversely proportional to the frequency; this is called $1/f$ noise or “**pink noise**”.
- Above a critical noise frequency, the noise becomes flat and is spread out equally across the frequency spectrum; this is called “**white noise**”.
- The power distribution of noise is measured in watts per hertz (W/Hz).

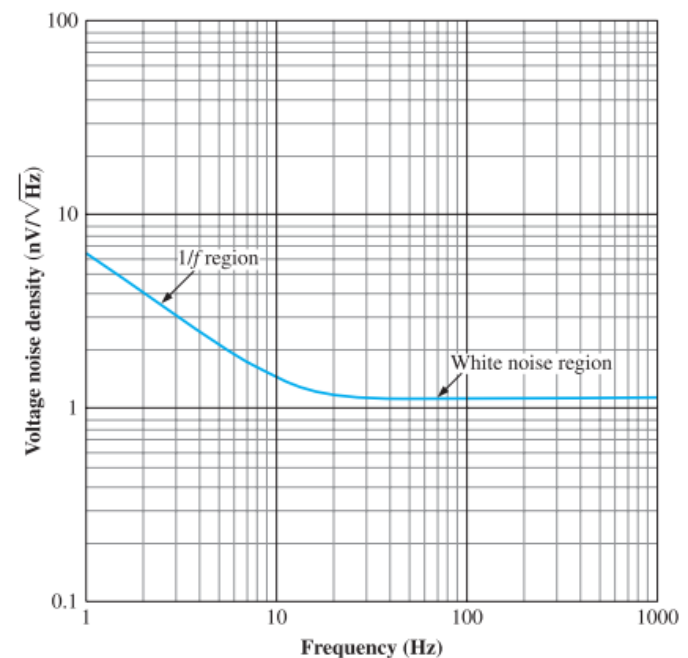



A Comparison of for some representative op-amps Parameters.
Check the reference !

OP-AMPS WITH NEGATIVE FEEDBACK



Why Use Negative Feedback?

- **Negative feedback** is the process whereby a portion of the output voltage of an amplifier is returned to the input with a phase angle that opposes (or subtracts from) the input signal.
- Open-loop voltage gain of a typical op-amp is very high.
- Therefore, an extremely small input voltage drives the op-amp into its saturated output states.
- In fact, even the input offset voltage of the op-amp can drive it into saturation.

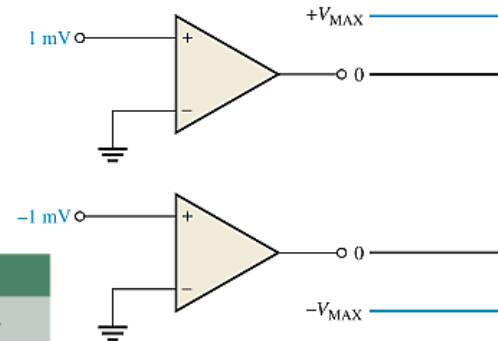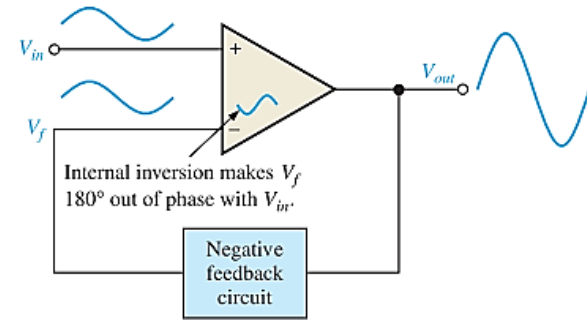

	VOLTAGE GAIN	INPUT Z	OUTPUT Z	BANDWIDTH
Without negative feedback	A_{ol} is too high for linear amplifier applications	Relatively high (see Table 12-1)	Relatively low	Relatively narrow (because the gain is so high)
With negative feedback	A_{cl} is set to desired value by the feedback circuit	Can be increased or reduced to a desired value depending on type of circuit	Can be reduced to a desired value	Significantly wider




OP-AMPS WITH NEGATIVE FEEDBACK

- An op-amp can be connected using negative feedback to stabilize the gain and increase frequency response.
- The closed-loop voltage gain is the voltage gain of an op-amp with external feedback.
- The closed-loop voltage gain is determined by the external component values and can be precisely controlled by them.

- **Non-inverting Amplifier**

$$A_{cl(NI)} = 1 + \frac{R_f}{R_i}$$

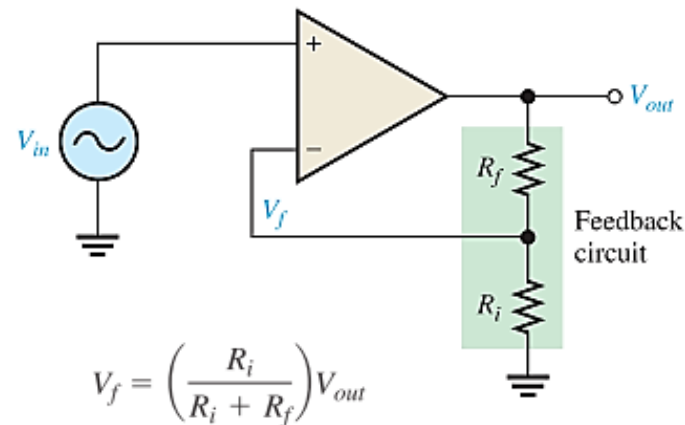


Assignment: Derive the A_{cl} for Non-inverting and Inverting Amplifiers.

OP-AMPS WITH NEGATIVE FEEDBACK..



- Voltage-Follower

$$A_{cl(VF)} = 1$$

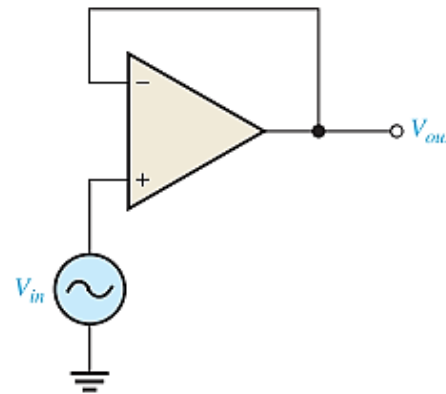

- Inverting Amplifier

$$A_{cl(I)} = -\frac{R_f}{R_i}$$

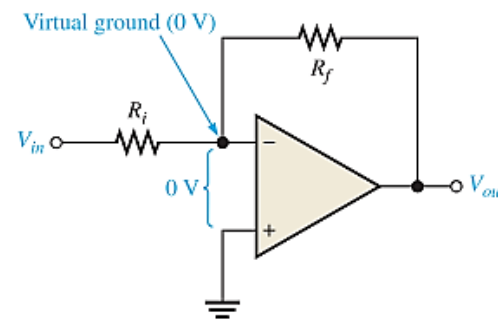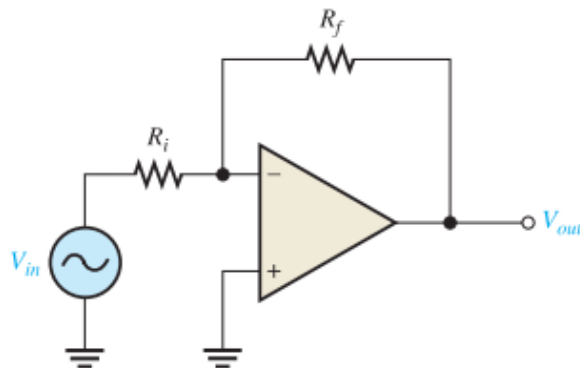


EFFECTS OF NEGATIVE FEEDBACK ON OP-AMP IMPEDANCES

- Non-inverting Amplifier**

$$Z_{in(NI)} = (1 + A_{ol}B)Z_{in}$$
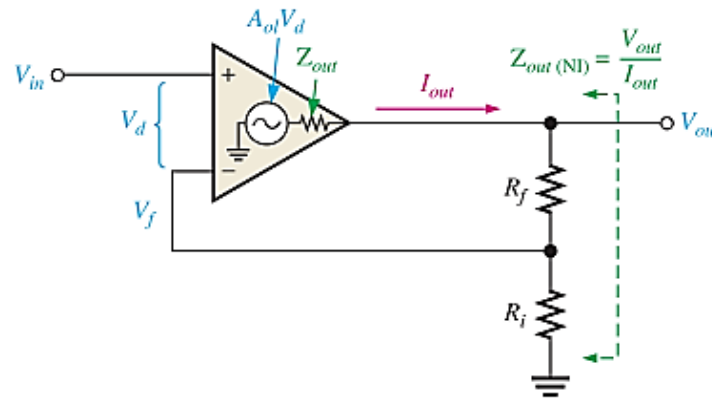
$$Z_{out(NI)} = \frac{Z_{out}}{1 + A_{ol}B}$$



- Voltage Follower**


$$Z_{in(VF)} = (1 + A_{ol})Z_{in}$$

$$Z_{out(VF)} = \frac{Z_{out}}{1 + A_{ol}}$$

- Inverting Amplifier**

$$Z_{in(I)} \cong R_i$$
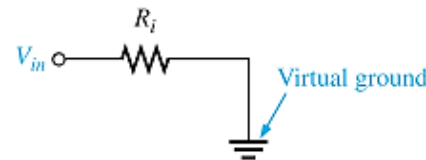
$$Z_{out(I)} = \frac{Z_{out}}{1 + A_{ol}B}$$




- Certain deviations from the ideal op-amp must be recognized because of their effects on its operation.
- Transistors within the op-amp must be biased so that they have the correct values of base and collector currents and collector-to-emitter voltages.
- The ideal op-amp has no input current at its terminals; but in fact, the practical op-amp has small input bias currents typically in the nA range.
- Also, small internal imbalances in the transistors effectively produce a small offset voltage between the inputs.


BIAS CURRENT AND OFFSET VOLTAGE




Effect of Input Bias Current

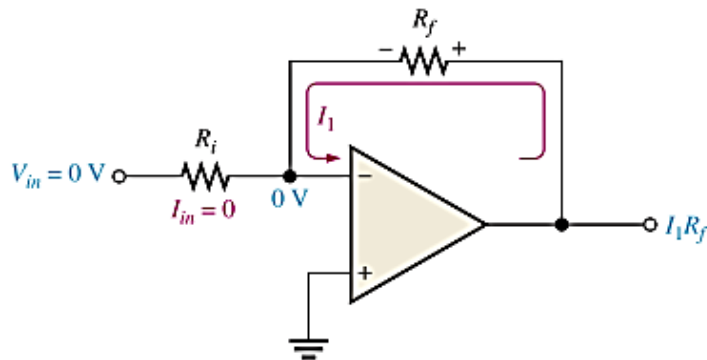

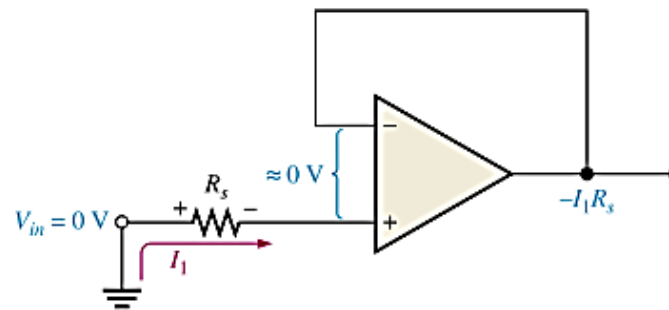(a) Input bias current creates output error voltage ($I_1 R_f$) in an inverting amplifier.




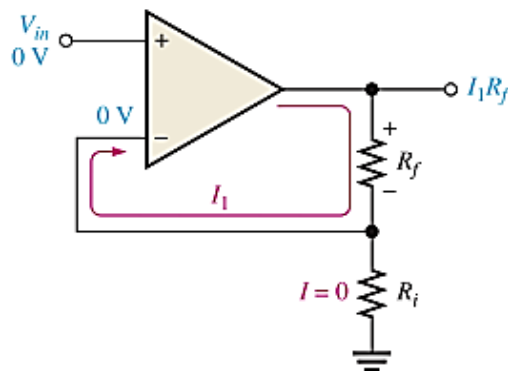
(b) Input bias current creates output error voltage in a voltage-follower.




◀ **FIGURE 12-30**

Input bias current creates output error voltage in a noninverting amplifier.

Bias Current Compensation

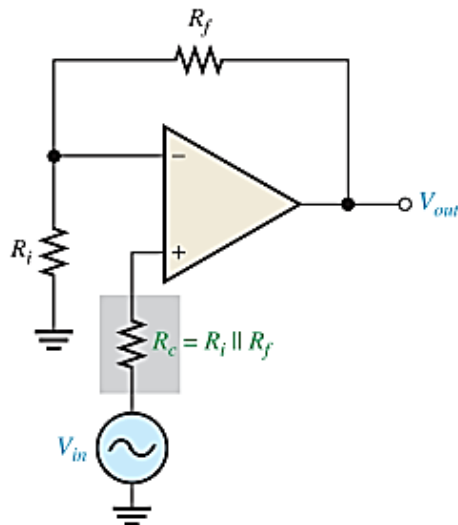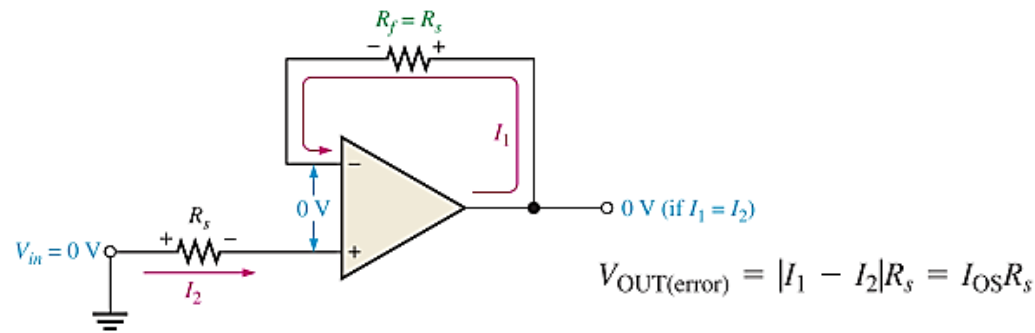

(a) Noninverting amplifier

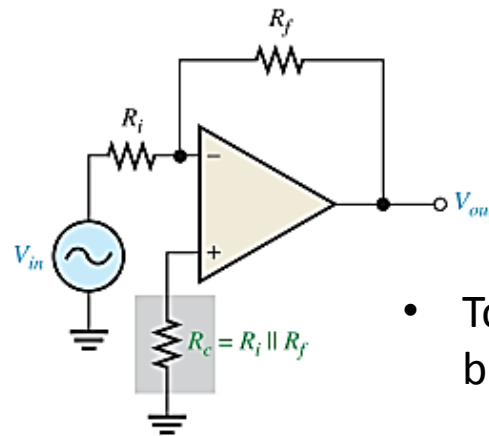


(b) Inverting amplifier

- To compensate for the effect of bias , a resistor R_c is added.
- Use of a BIFET Op-Amp to Eliminate the Need for Bias Current Compensation


Effect of Input Offset Voltage

$$V_{OUT(error)} = A_{cl}V_{IO}$$

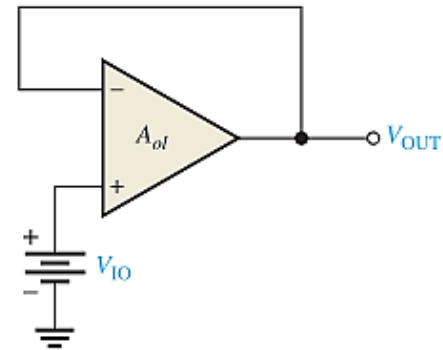


▲ FIGURE 12-33
Input offset voltage equivalent.


Input Offset Voltage Compensation

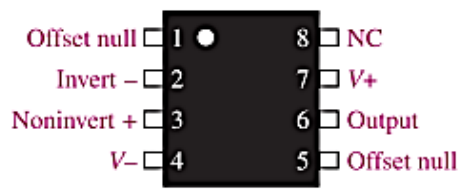

(a) 8-pin DIP or SMT package

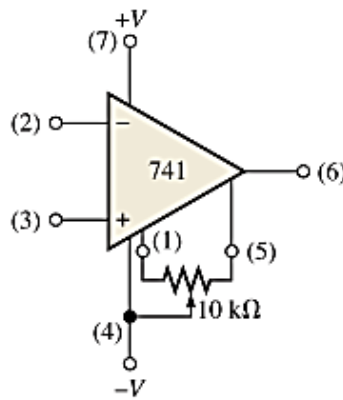

(b) External potentiometer

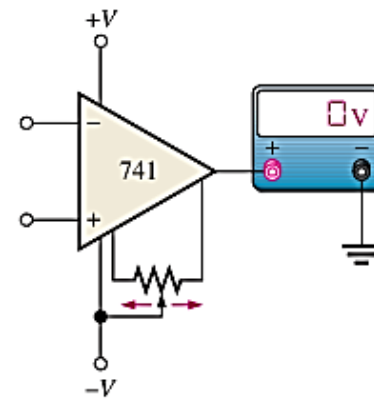


(c) Adjust for zero output

▲ FIGURE 12-34
Input offset voltage compensation for a 741 op-amp.

OPEN & CLOSED LOOP FREQUENCY RESPONSES



Open-Loop Frequency & Phase Responses

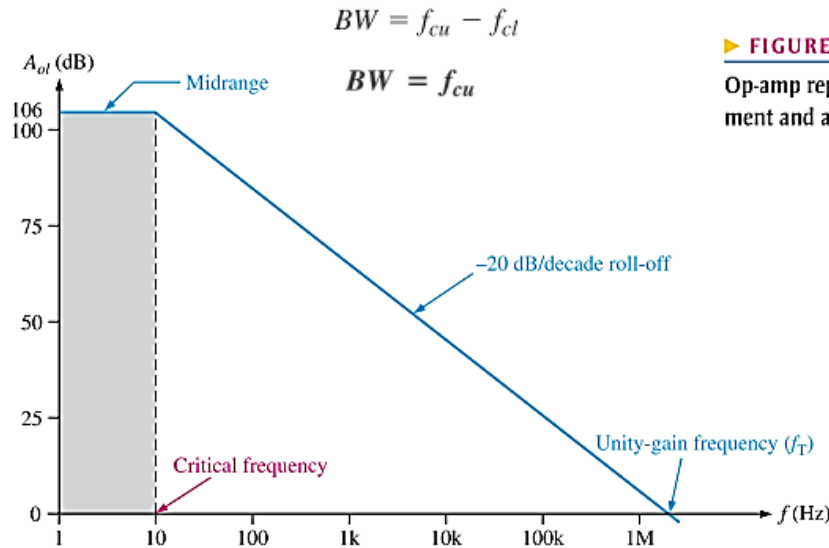


▲ FIGURE 12-36




Ideal plot of open-loop voltage gain versus frequency for a typical op-amp. The frequency scale is logarithmic.

► FIGURE 12-38

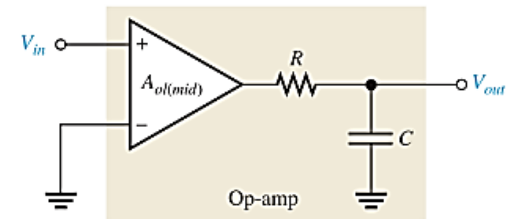Op-amp represented by a gain element and an internal RC circuit.



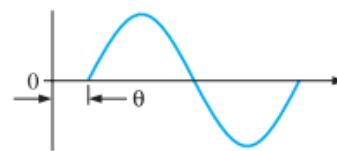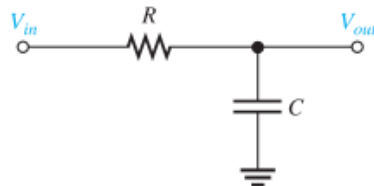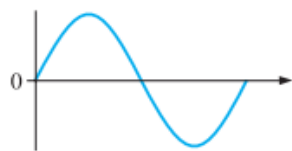
$$A_{ol} = \frac{A_{ol(mid)}}{\sqrt{1 + f^2/f_c^2}}$$




$$\theta = -\tan^{-1}\left(\frac{f}{f_c}\right)$$

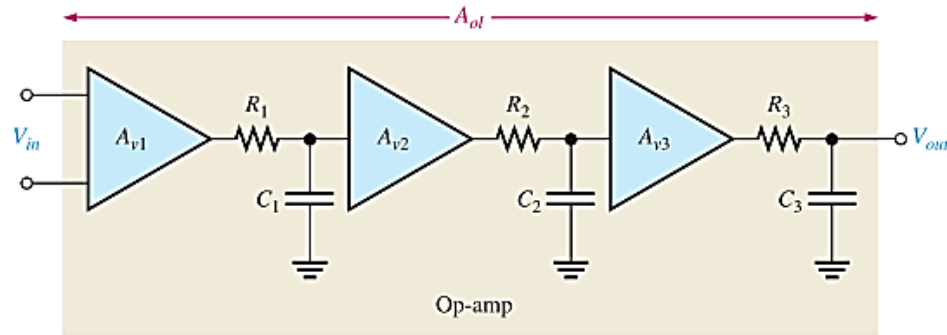
Overall Frequency & Phase Responses (Open-Loop)



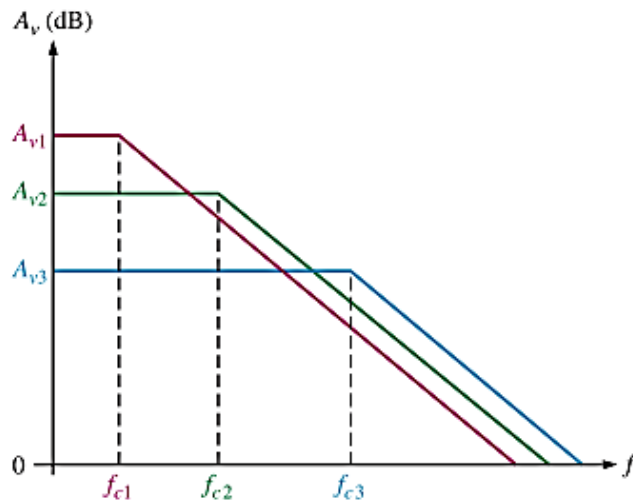(a) Representation of an op-amp with three internal stages



(b) Individual responses

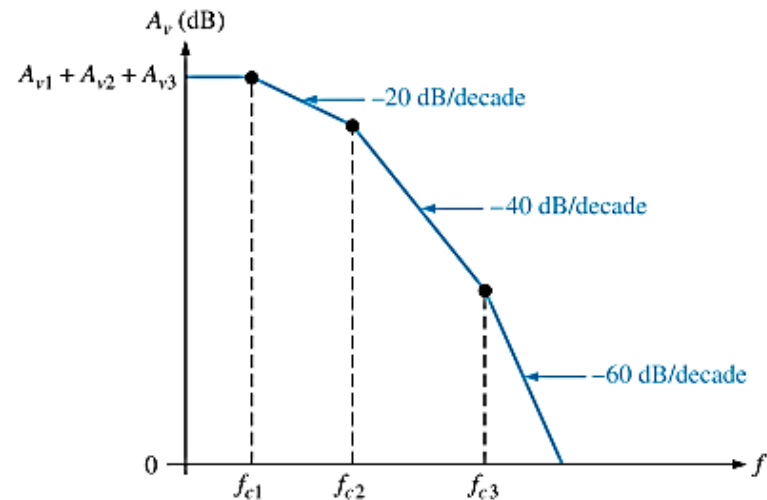

(c) Composite response

$$\theta_{tot} = -\tan^{-1}\left(\frac{f}{f_{c1}}\right) - \tan^{-1}\left(\frac{f}{f_{c2}}\right) - \tan^{-1}\left(\frac{f}{f_{c3}}\right)$$




CLOSED-LOOP FREQUENCY RESPONSE

► FIGURE 12-42

Closed-loop gain compared to open-loop gain.

$$f_{c(cl)} = f_{c(ol)}(1 + BA_{ol(mid)})$$


$$BW_{cl} = BW_{ol}(1 + BA_{ol(mid)})$$

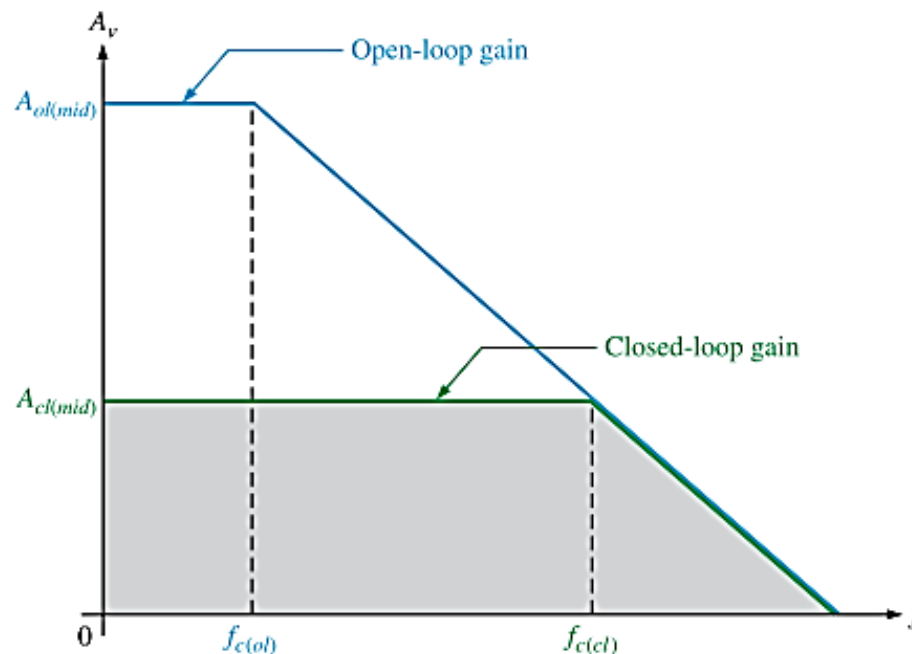

- The **gain-bandwidth product** is always equal to the frequency at which the op-amp's open-loop gain is unity or 0 dB (unity-gain bandwidth, f_T).


$$f_T = A_{cl}f_{c(cl)}$$

Troubleshooting

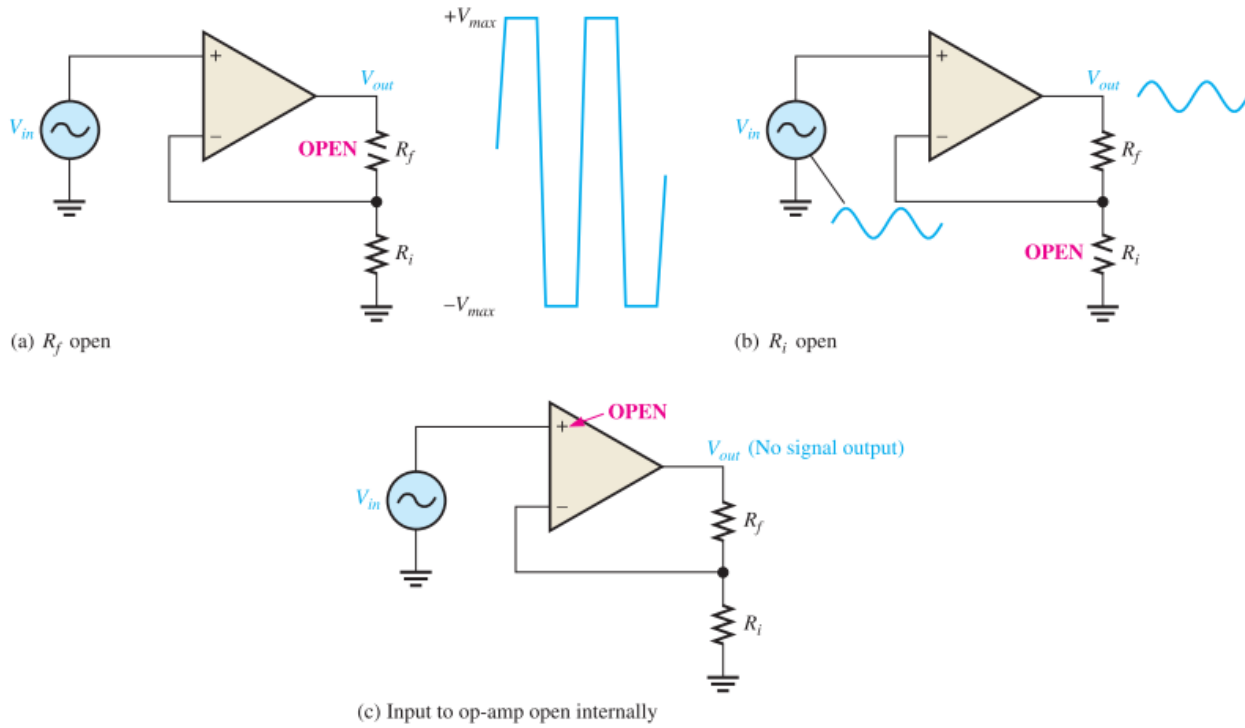

▲ FIGURE 12-44

Faults in the noninverting amplifier.

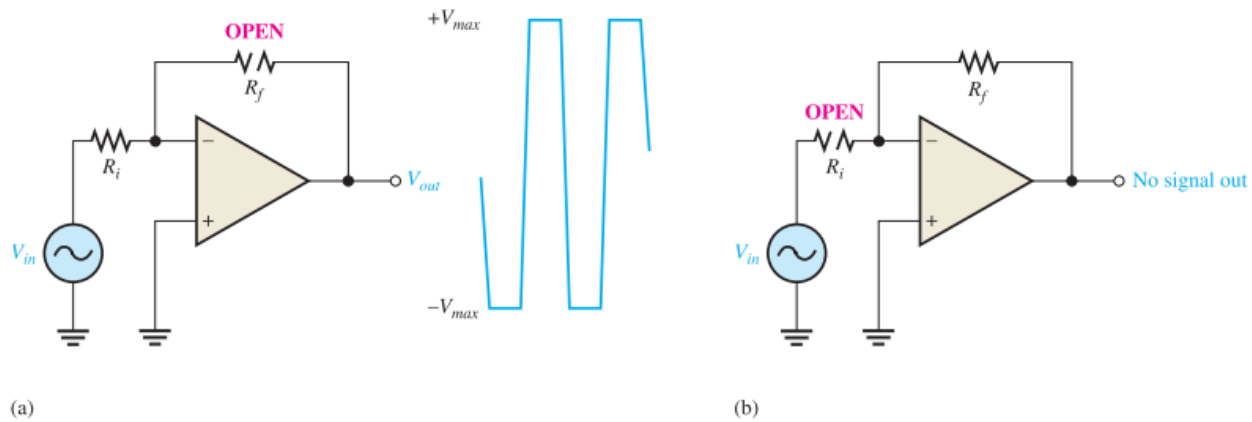

▲ FIGURE 12-45

Faults in the inverting amplifier.

- For more details, refer to:
 - Chapter 12, T. Floyd, **Electronic Devices**, 9th edition.
- The lecture is available online at:
 - <http://bu.edu.eg/staff/ahmad.elbanna-courses/12135>
- For inquires, send to:
 - ahmad.elbanna@feng.bu.edu.eg