



BENHA UNIVERSITY
FACULTY OF ENGINEERING AT SHOUBRA

ECE-322
Electronic Circuits (B)

Lecture #7
Voltage Regulators

Instructor:
Dr. Ahmad El-Banna



Agenda

Voltage Regulation

Basic Linear Series Regulators

Basic Linear Shunt Regulators

Intro. to Switching Regulators

VOLTAGE REGULATION



Intro.

- **Two basic categories** of voltage regulation are:
 - Line regulation
 - Load regulation
- The **purpose of line regulation** is to maintain a nearly **constant output** voltage **when the input** voltage **varies**.
- The **purpose of load regulation** is to maintain a nearly **constant output** voltage **when the load** **varies**.


Line Regulation

- When the ac input (line) voltage of a power supply changes, an electronic circuit called a **regulator** maintains a nearly constant output voltage.
- **Line regulation** can be defined as the percentage change in the output voltage for a given change in the input voltage

$$\text{Line regulation} = \left(\frac{\Delta V_{\text{OUT}}}{\Delta V_{\text{IN}}} \right) 100\%$$

- Line regulation can also be expressed in units of %/V
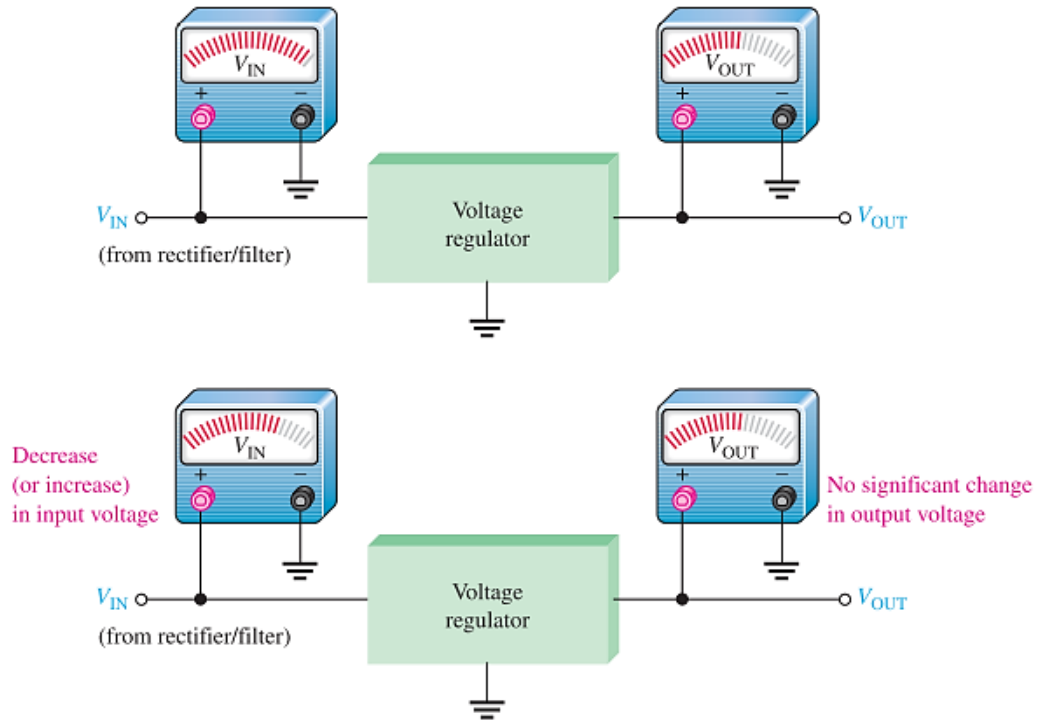
$$\text{Line regulation} = \frac{(\Delta V_{\text{OUT}}/V_{\text{OUT}})100\%}{\Delta V_{\text{IN}}}$$





Load Regulation

- Load regulation can be defined as the percentage change in output voltage for a given change in load current.
- One way to express load regulation is as a percentage change in output voltage from no-load (NL) to full-load (FL).

$$\text{Load regulation} = \left(\frac{V_{NL} - V_{FL}}{V_{FL}} \right) 100\%$$

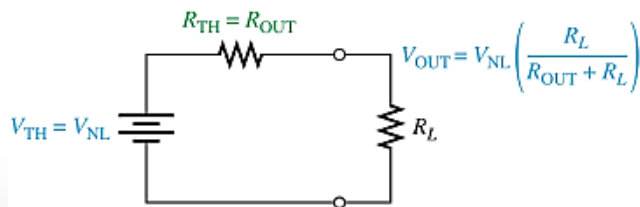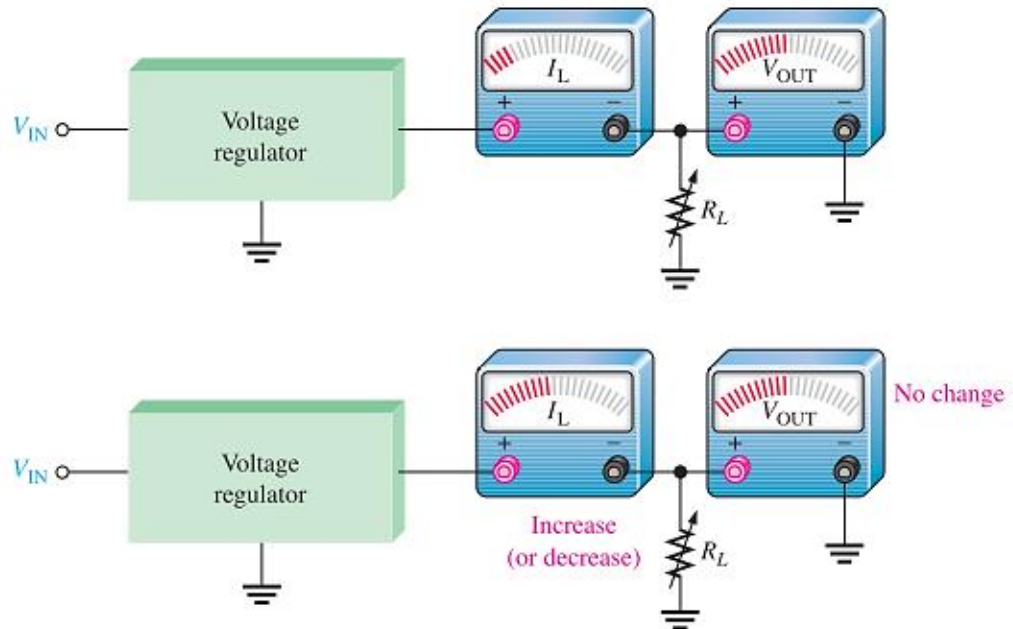- The load regulation can be expressed as a percentage change in output voltage for each mA change in load current.
- Using R_{OUT} , Thevenin equivalent circuit for a power supply with a load resistor.



$$\text{Load regulation} = \left(\frac{R_{OUT}}{R_{FL}} \right) 100\%$$



BASIC LINEAR SERIES REGULATORS





(7)

Regulators Classification

- The fundamental classes of voltage regulators are:
 - linear regulators
 - switching regulators
- Both of these are available in integrated circuit form.
- Two basic types of linear regulator are
 - series regulator
 - shunt regulator


Series Voltage Regulator

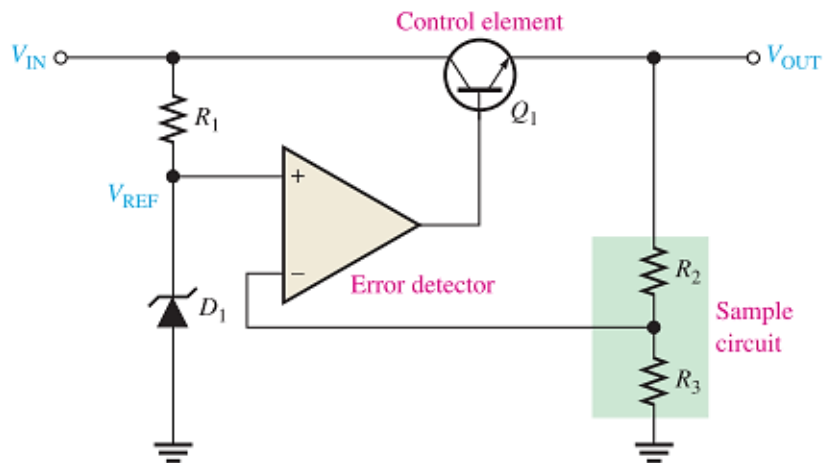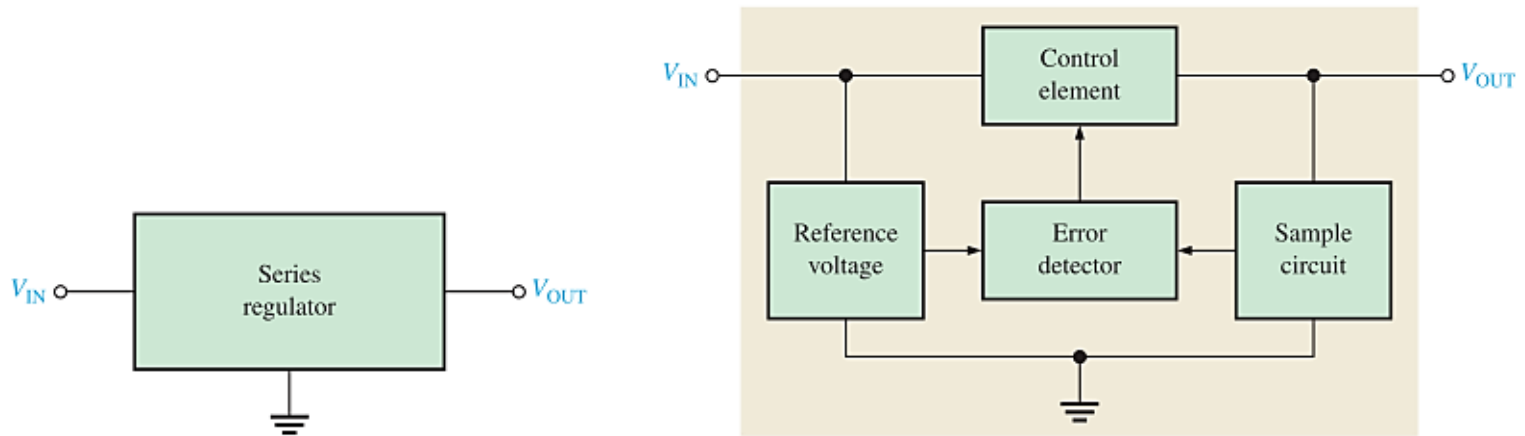

Basic op-amp series regulator


Regulating Action

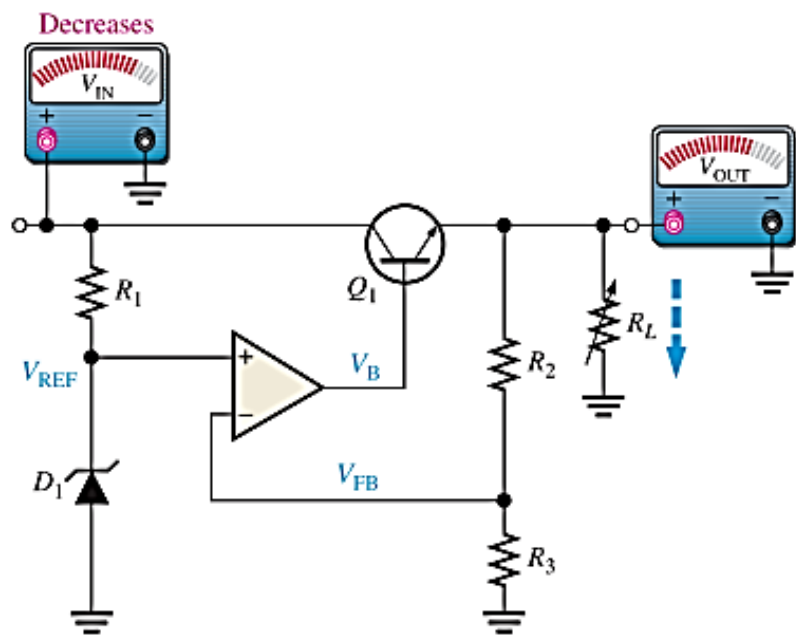- Illustration of series regulator action that keeps V_{OUT} constant when V_{IN} or R_L changes.



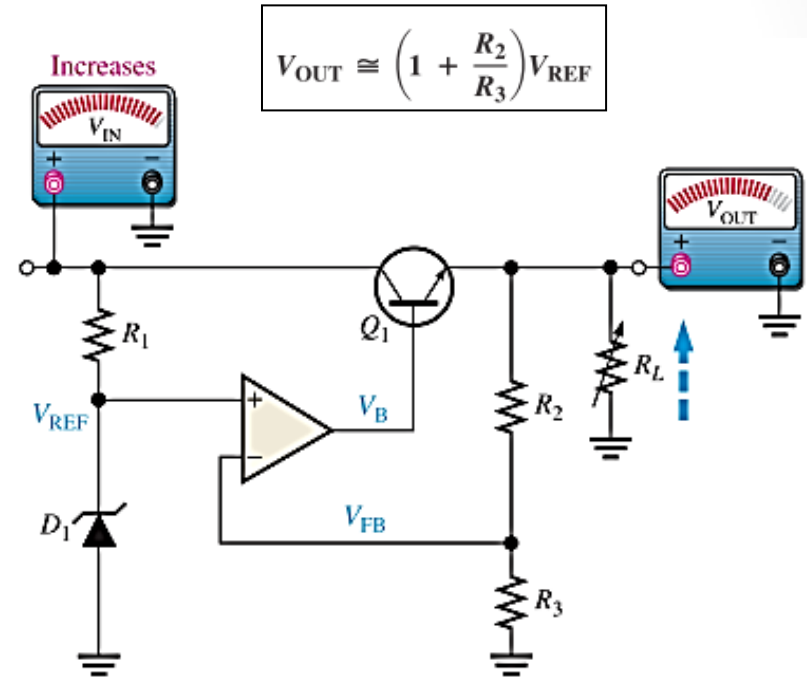(a) When V_{IN} or R_L decreases, V_{OUT} attempts to decrease. The feedback voltage, V_{FB} , also attempts to decrease, and as a result, the op-amp's output voltage V_B attempts to increase, thus compensating for the attempted decrease in V_{OUT} by increasing the Q_1 emitter voltage. Changes in V_{OUT} are exaggerated for illustration.

When V_{IN} (or R_L) stabilizes at its new lower value, the voltages return to their original values, thus keeping V_{OUT} constant as a result of the negative feedback.




(b) When V_{IN} or R_L increases, V_{OUT} attempts to increase. The feedback voltage, V_{FB} , also attempts to increase, and as a result, V_B , applied to the base of the control transistor, attempts to decrease, thus compensating for the attempted increase in V_{OUT} by decreasing the Q_1 emitter voltage.

When V_{IN} (or R_L) stabilizes at its new higher value, the voltages return to their original values, thus keeping V_{OUT} constant as a result of the negative feedback.

Short-Circuit or Overload Protection

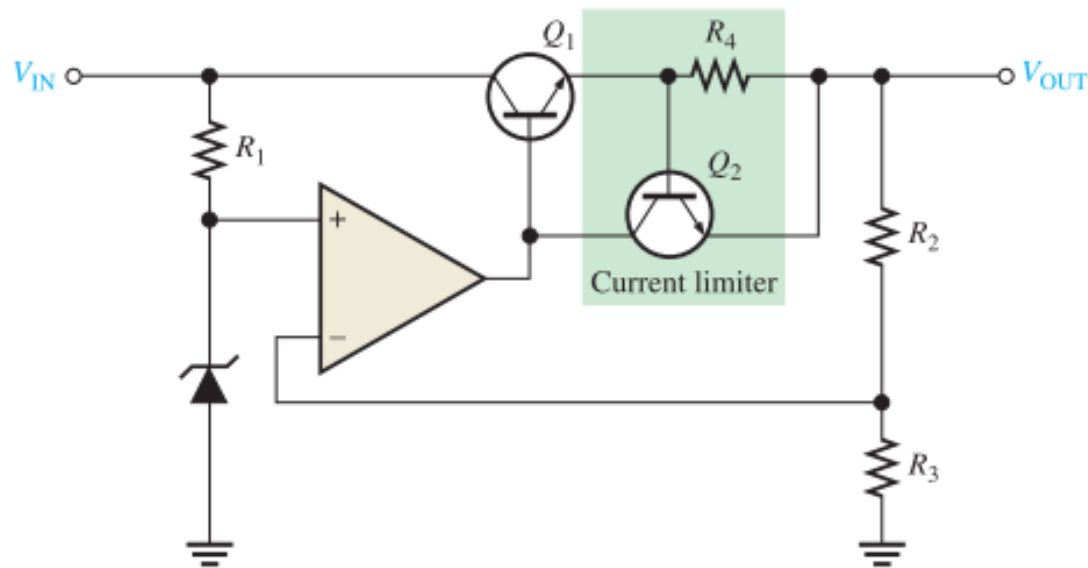- If an **excessive** amount of **load current** is drawn, the series-pass **transistor** can be quickly damaged or **destroyed**.
- Most regulators use some type of excess **current protection** in the form of a current-limiting mechanism.
- one method of current limiting to prevent overloads called **constant-current limiting**.





$$I_{L(\max)} = \frac{0.7 \text{ V}}{R_4}$$

BASIC LINEAR SHUNT REGULATORS




Shunt Regulator

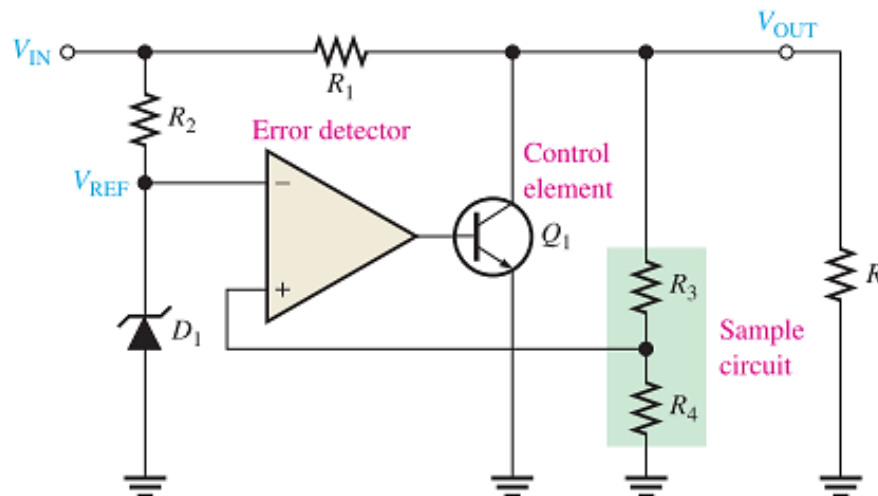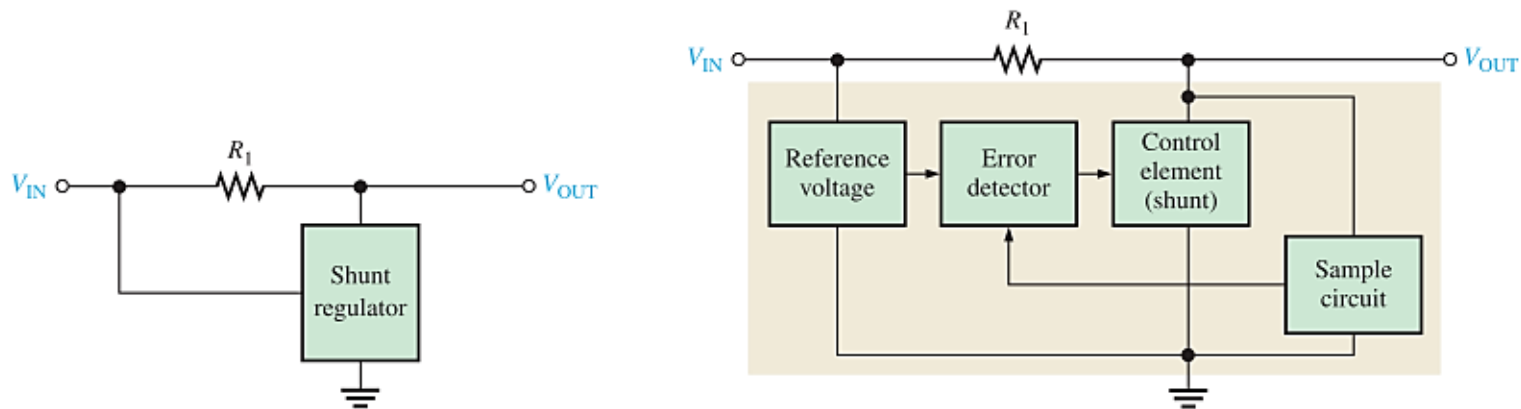- In the shunt regulator, the control element is a transistor in parallel (shunt) with the load.




Regulating Action

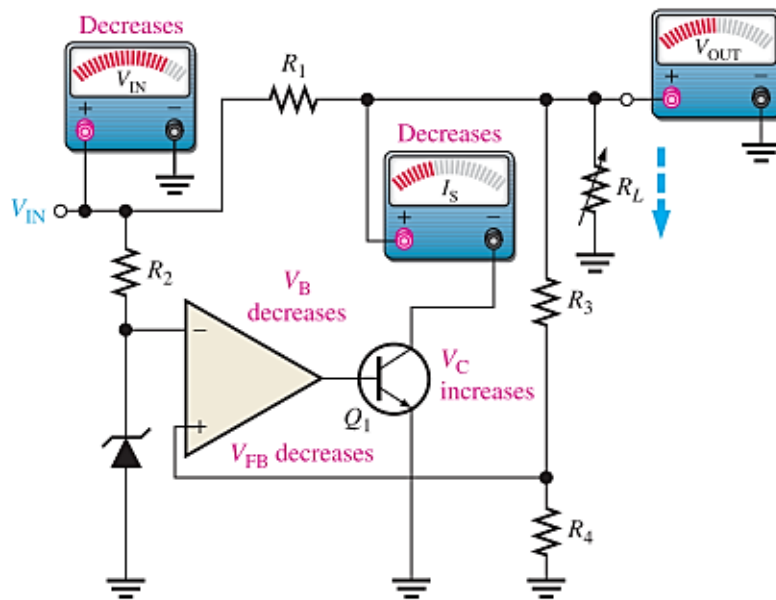- Sequence of responses when V_{OUT} tries to decrease as a result of a decrease in R_L or V_{IN} (opposite responses for an attempted increase)



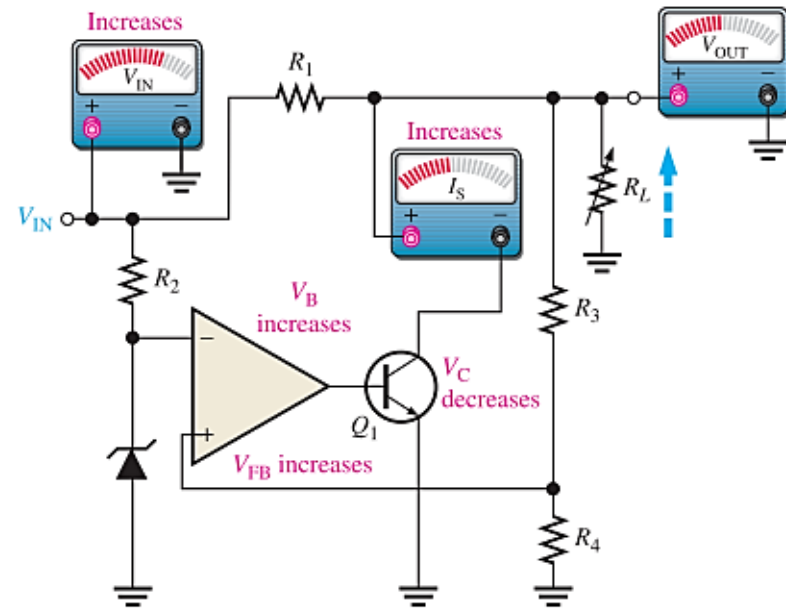(a) Response to a decrease in V_{IN} or R_L



(b) Response to an increase in V_{IN} or R_L

$$\Delta I_S = \frac{\Delta V_{IN}}{R_1}$$

$$I_{L(max)} = \frac{V_{IN}}{R_1}$$

- It offers inherent short-circuit protection

INTRO. TO SWITCHING REGULATORS



Switching Regulators

- The two types of **linear regulators**, series and shunt, have **control elements (transistors)** that are **conducting all the time**, with the amount of conduction varied as demanded by changes in the output voltage or current.
- The **switching regulator** is different because the **control element** operates as a **switch**.
- A much **greater efficiency** can be realized with a switching type of voltage regulator than with the linear types because the transistor switches on and off and dissipates power only when it is on.
- Efficiencies can be greater than **90%**.
- **Three basic configurations** of switching regulators are **step-down, step-up, and inverting**.
- In **some cases**, such as a **laptop computer**, **all three types may be employed** for various parts of the system.
- For **example**, the **display** typically will use an **inverting** type, the **microprocessor** would use a **step-down** type, and the **disk** drive may use a **step-up** type.



- For more details, refer to:
 - Chapter 17, T. Floyd, **Electronic Devices**, 9th edition.
- The lecture is available online at:
 - <http://bu.edu.eg/staff/ahmad.elbanna-courses/12135>
- For inquires, send to:
 - ahmad.elbanna@feng.bu.edu.eg