



BENHA UNIVERSITY
FACULTY OF ENGINEERING AT SHOUBRA

ECE-291 **Electronic Engineering**

Lecture #3 (2 weeks) Transistors


Instructor:
Dr. Ahmad El-Banna




Agenda

- BJT Structure
- Basic Operation
- Transistor as an Amplifier
- Transistor as a Switch
- DC & AC Analysis

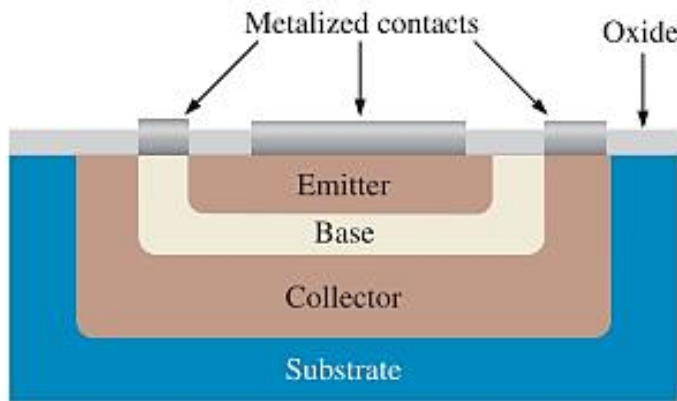
BIPOLAR JUNCTION TRANSISTOR (BJT) STRUCTURE



(a) Basic epitaxial planar structure

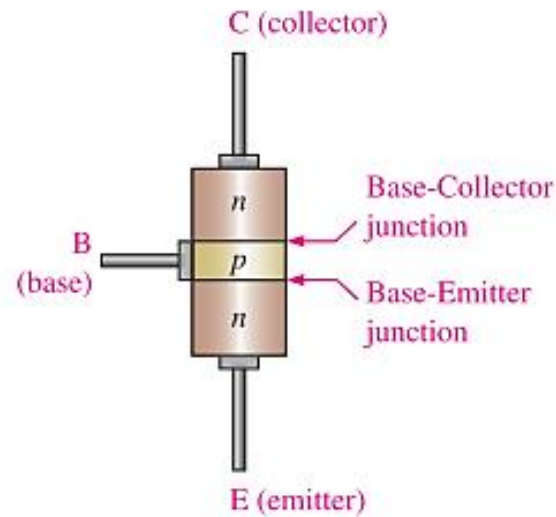


(b) npn

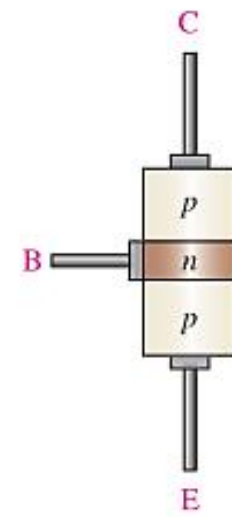


(c) pnp

BJT symbol

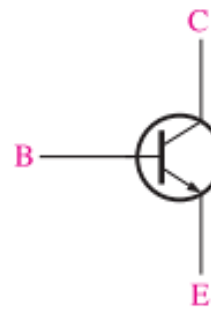


(a) npn

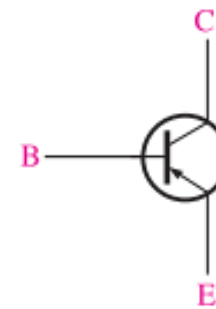


(b) pnp

Transistor Packages


General Purpose

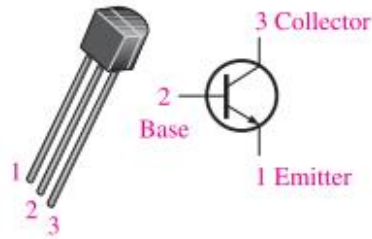

(a) TO-92

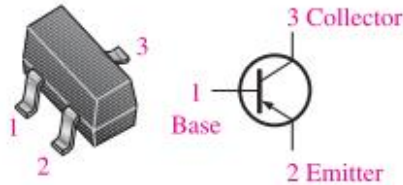

(b) SOT-23



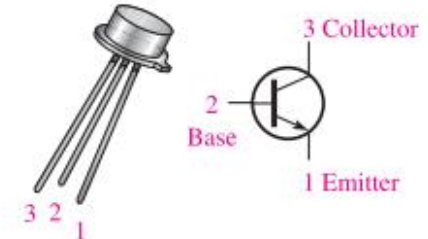


(c) TO-18. Emitter is closest to tab.


Multiple Transistor Package



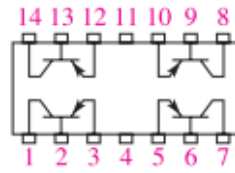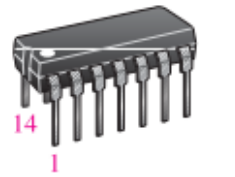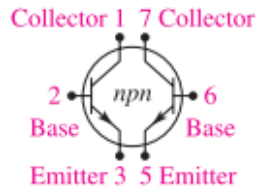
(a) Dual metal can. Emitters are closest to tab.



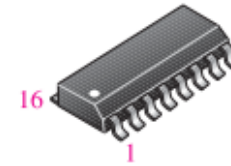
(b) Quad dual in-line (DIP) and quad flat-pack. Dot indicates pin 1.



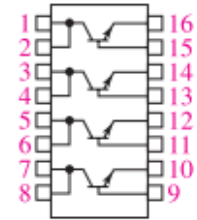
(c) Quad small outline (SO) package for surface-mount technology




Power Transistors

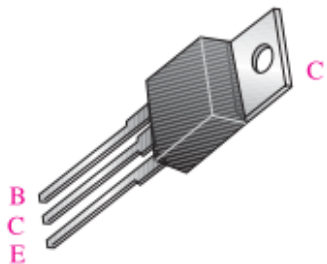


(a) TO-220

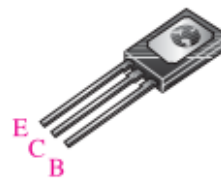

(b) TO-225

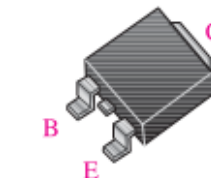



(c) D-Pack

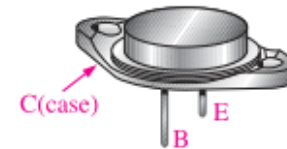

(d) TO-3



Basic Operation

- **Biasing & Operation**

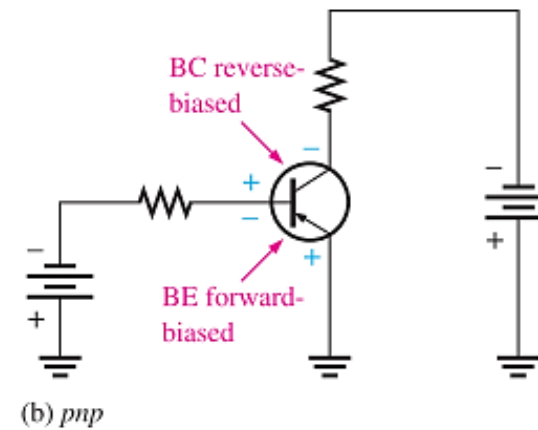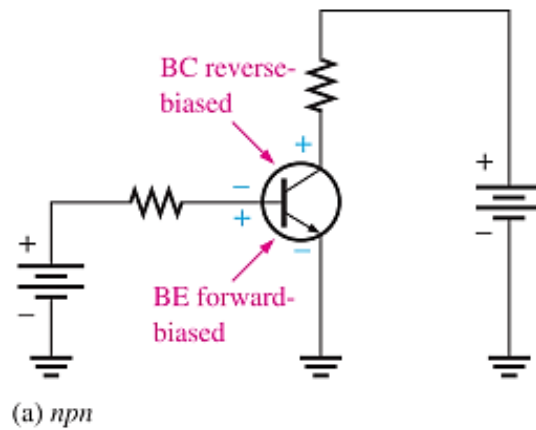

- **Transistor Currents**


$$I_E = I_C + I_B$$

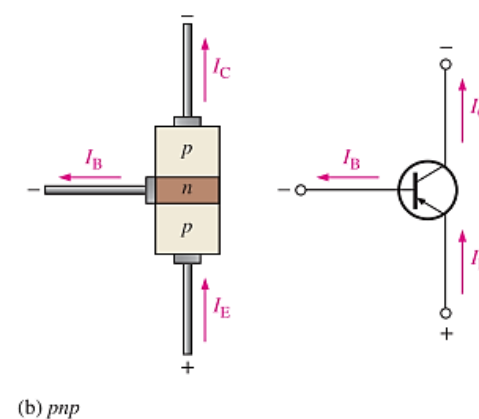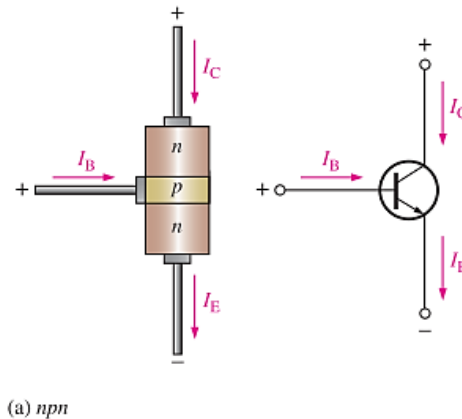

BJT Configurations

Configuration	Input	Output
Common Emitter	Base	Collector
Common Base	Emitter	Collector
Common Collector	Base	Emitter

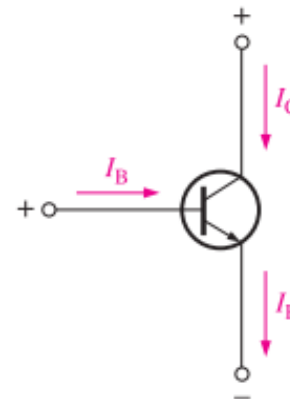- Base terminal can't be output
- Collector terminal can't be input



BJT Parameters

$$\beta_{DC} = \frac{I_C}{I_B}$$

- The dc current gain of a transistor is the ratio of the dc collector current (I_C) to the dc base current (I_B) and is designated dc **beta** (β_{DC}).

$$h_{FE} = \beta_{DC}$$

- Typical values of β_{DC} range from less than 20 to 200 or higher.
- β_{DC} is usually designated as an equivalent hybrid (h) parameter, h_{FE} , on transistor datasheets.

$$\alpha_{DC} = \frac{I_C}{I_E}$$

- The ratio of the dc collector current (I_C) to the dc emitter current (I_E) is the dc alpha (α_{DC}).

Transistor DC Model

I_B : dc base current


I_E : dc emitter current

I_C : dc collector current

V_{BE} : dc voltage at base with respect to emitter

V_{CB} : dc voltage at collector with respect to base

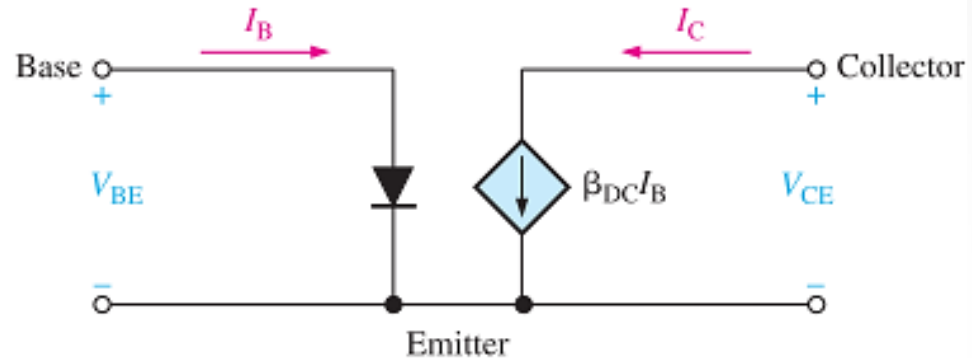V_{CE} : dc voltage at collector with respect to emitter




$$V_{BE} \cong 0.7 \text{ V}$$

$$V_{R_B} = V_{BB} - V_{BE}$$

$$V_{R_B} = I_B R_B$$

$$I_B R_B = V_{BB} - V_{BE}$$

$$I_B = \frac{V_{BB} - V_{BE}}{R_B}$$

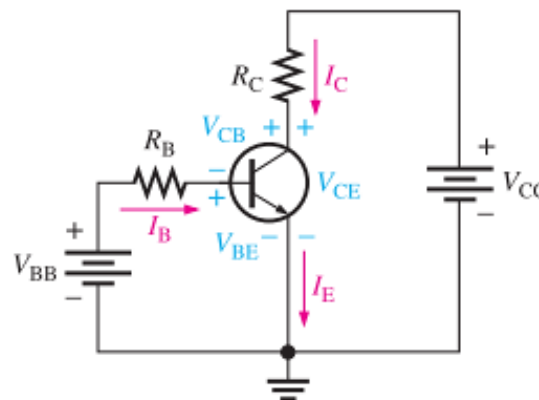

$$V_{CE} = V_{CC} - V_{R_C}$$

$$V_{R_C} = I_C R_C$$

$$I_C = \beta I_B$$




$$V_{CE} = V_{CC} - I_C R_C$$

$$V_{CB} = V_{CE} - V_{BE}$$


Collector characteristic curves

Operation Regions

- Active
- Cut-off
- Saturation

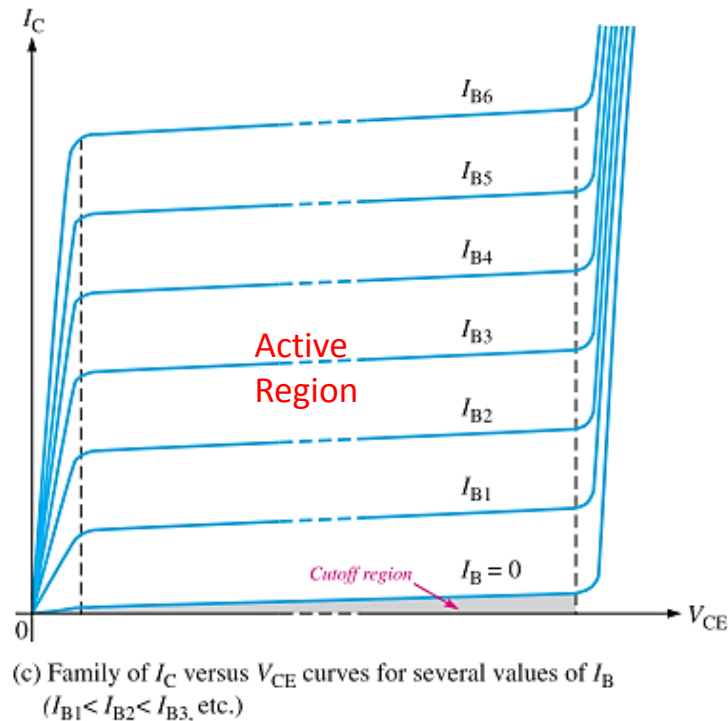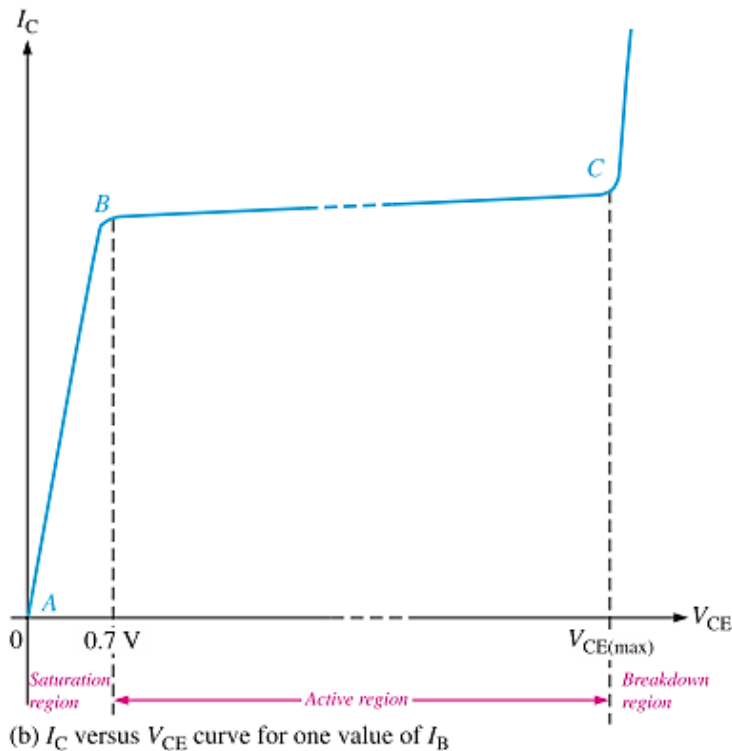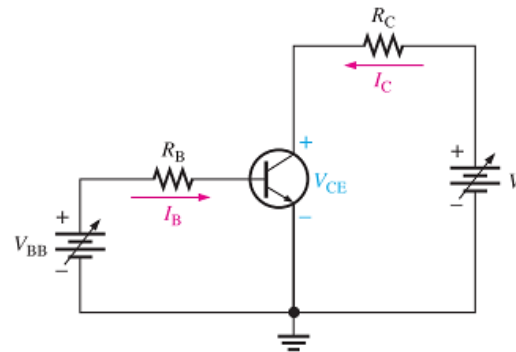

BJT as an Amplifier

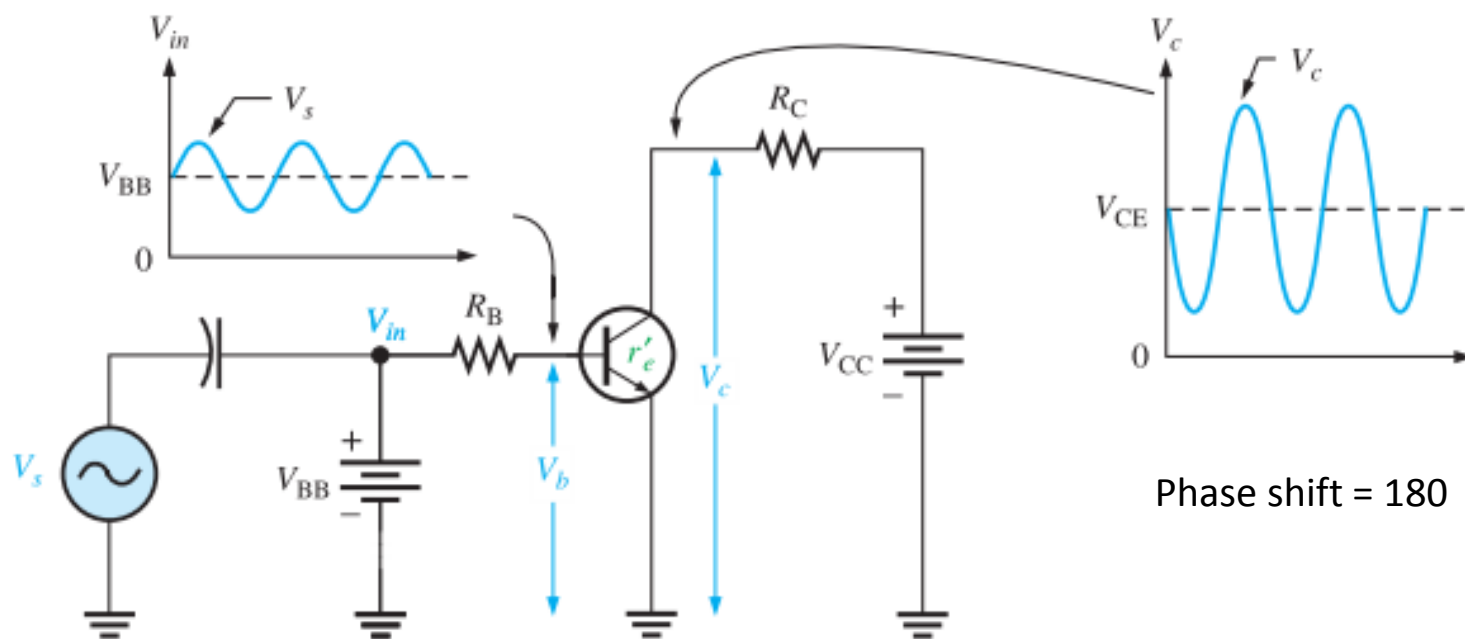

Voltage gain magnitude:



$$A_v \cong \frac{R_C}{r'_e}$$

$$r_e = 26 \text{ mV} / I_E$$

$$I_E = I_C + I_B$$




BJT as a Switch

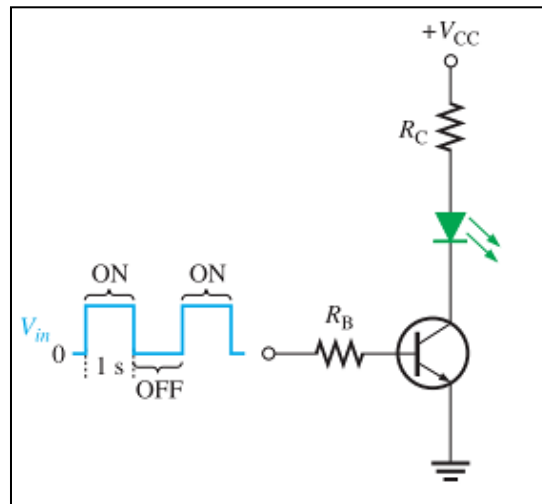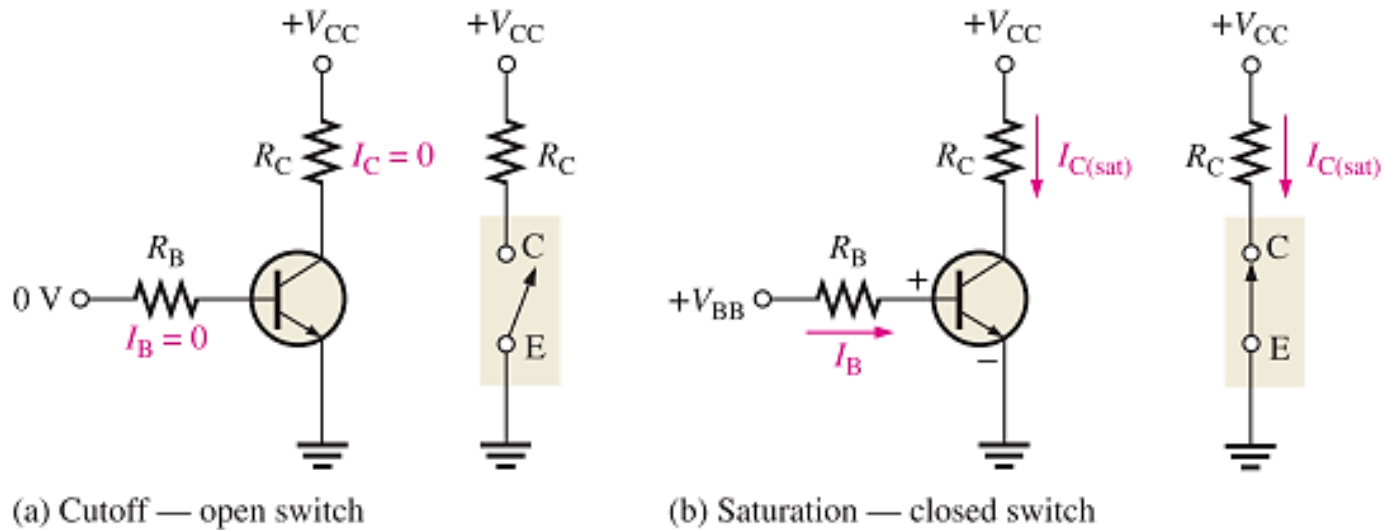


The Phototransistor




$$I_C = \beta_{DC} I_\lambda$$

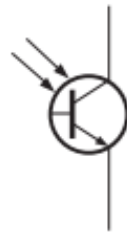

(a) Schematic symbol

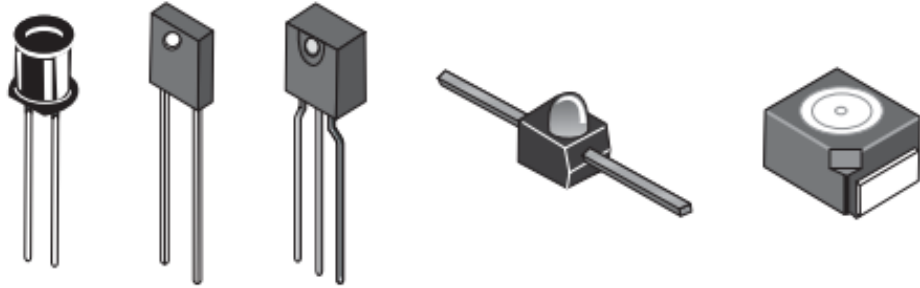


(b) Typical packages

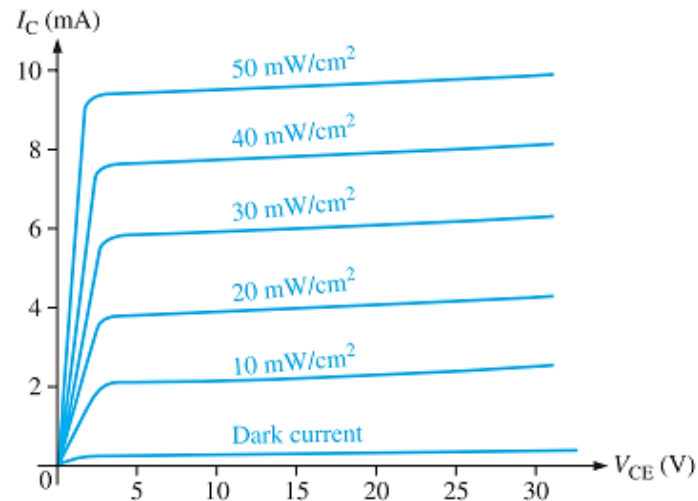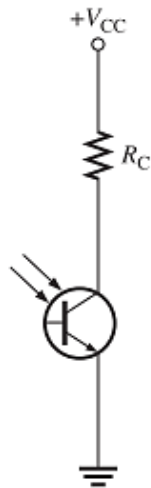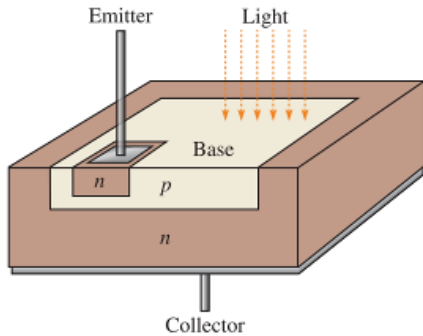


Phototransistor Application

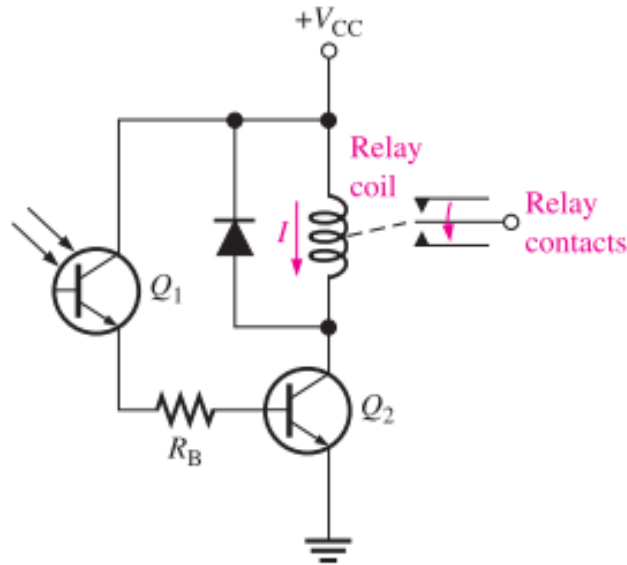Relay circuits driven by a phototransistor



(a) Light activated

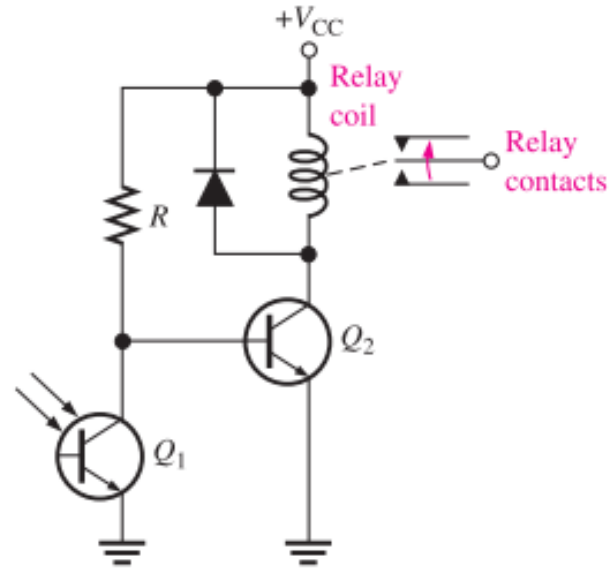

(b) Light deactivated




- A **relay** is an electrically operated switch.
- **relays** use an electromagnet to mechanically operate a switch




Optocouplers


- **Basic optocouplers**

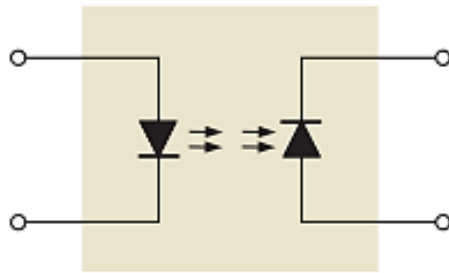


(a) LED-to-photodiode

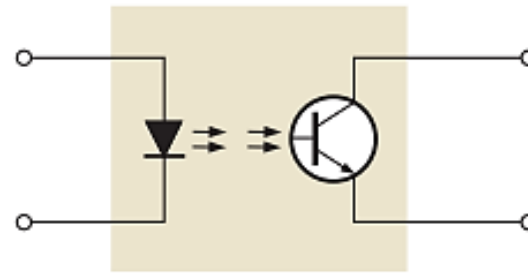

(b) LED-to-phototransistor

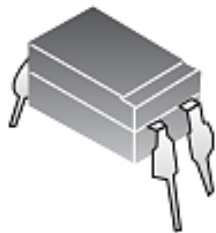

(a) Dual-in-line

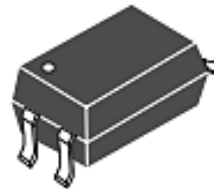

(b) Surface-mount



(c) Ball-grid

Examples of optocoupler packages

Project



Motion Detection Alarm

LED
Transmitter

Phototransistor
Circuit


Alarm
Circuit

555 Timer Siren Circuit

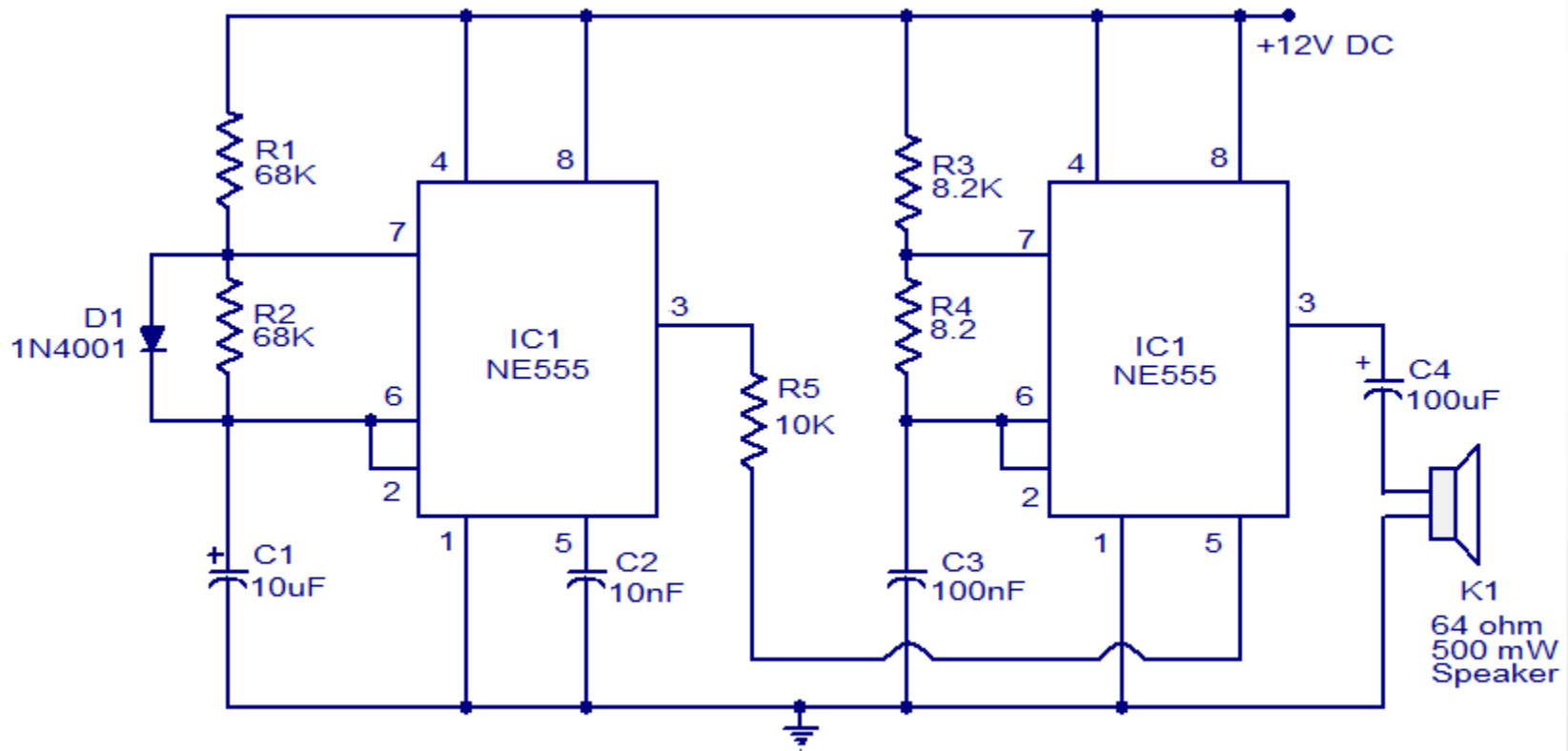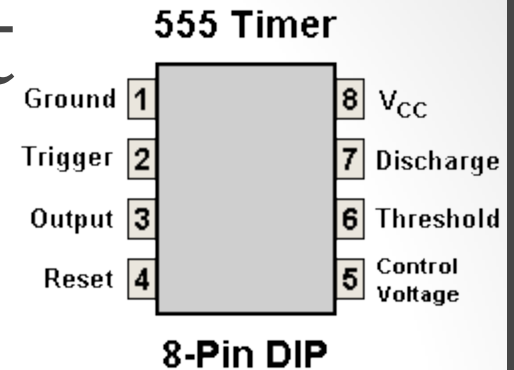

www.circuitstoday.com


Siren Using Op-Amp

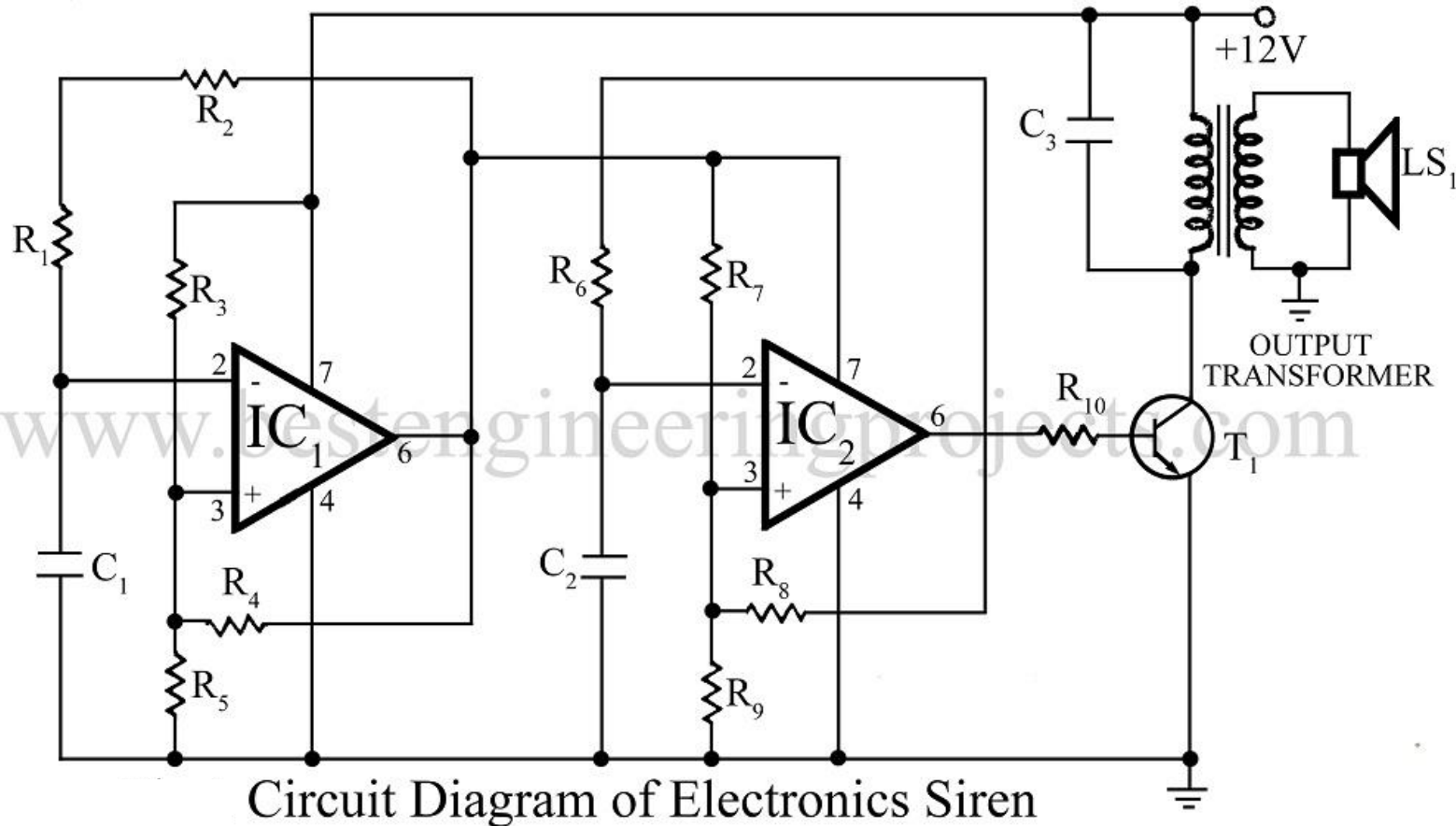


<http://bestengineeringprojects.com/electronics-projects/electronic-siren/>

Transistor Bias Circuit

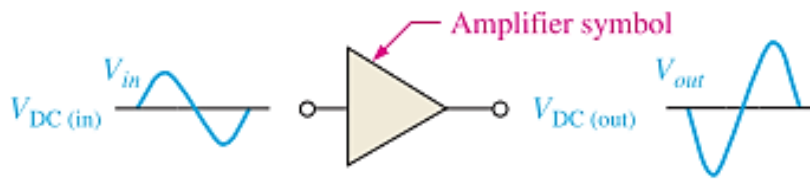
- What's Biasing?
 - Bias establishes the dc operating point (Q-point) for proper linear operation of an amplifier.
- Why?
 - If an amplifier is not biased with correct dc voltages on the input and output, it can go into saturation or cutoff when an input signal is applied.



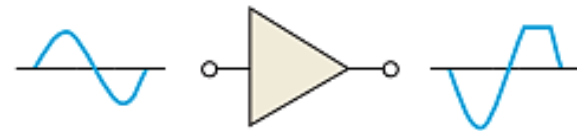(a) Linear operation: larger output has same shape as input except that it is inverted




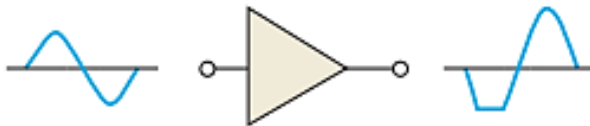(b) Nonlinear operation: output voltage limited (clipped) by cutoff





(c) Nonlinear operation: output voltage limited (clipped) by saturation



Q-point Adjustment

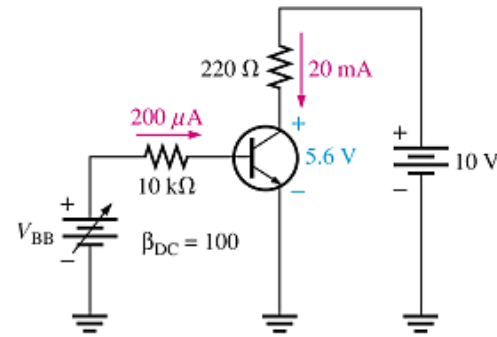


(a) $I_B = 200 \mu\text{A}$

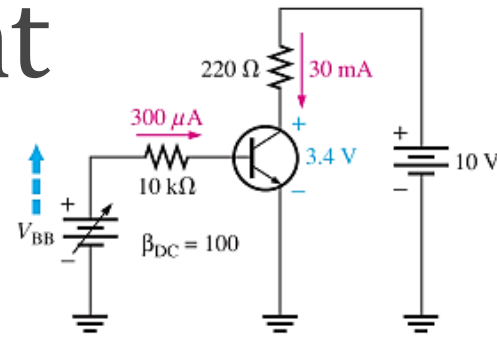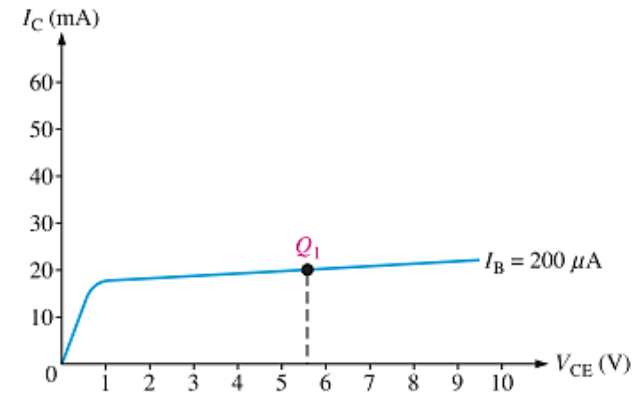

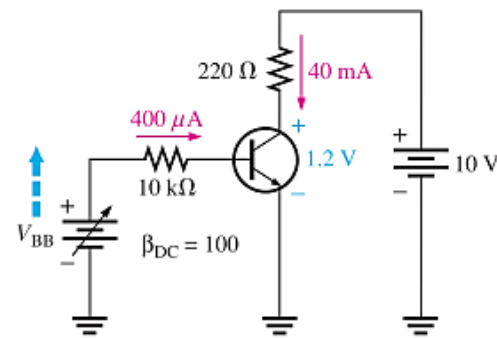
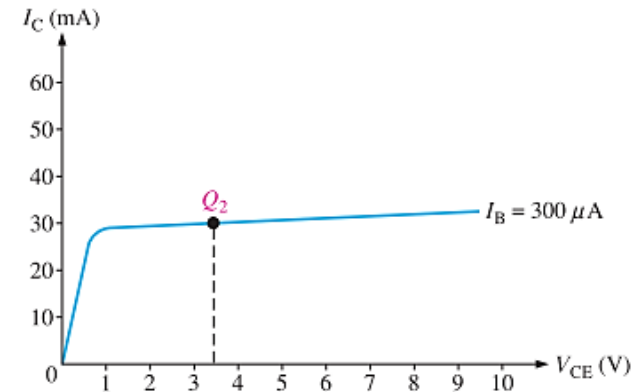
(b) Increase I_B to $300 \mu\text{A}$ by increasing V_{BB}



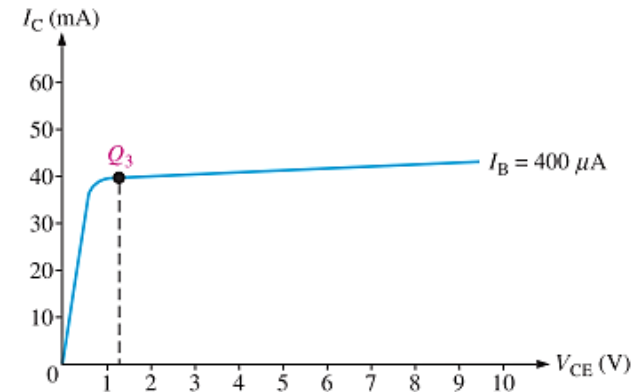
(c) Increase I_B to $400 \mu\text{A}$ by increasing V_{BB}



DC Load Line

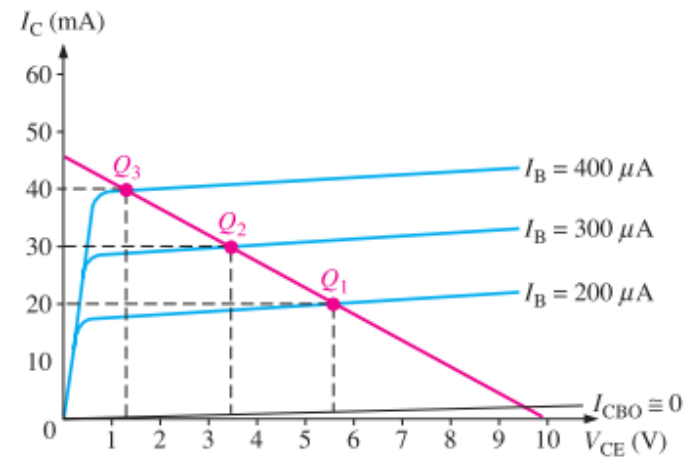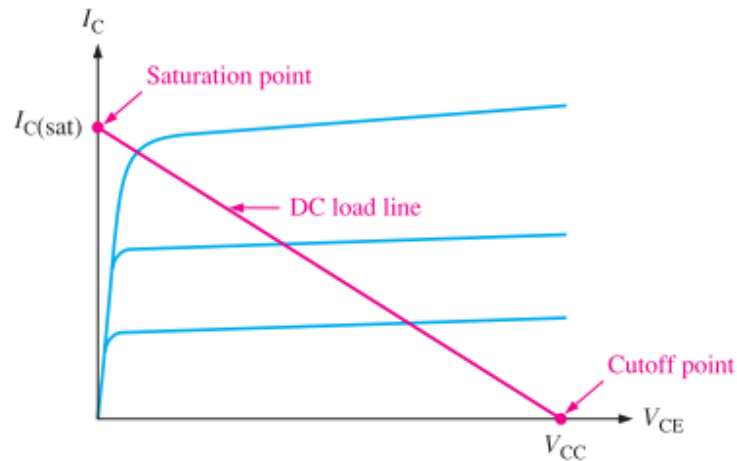

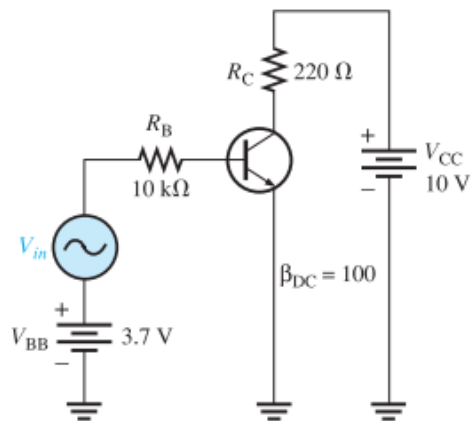
- Variations in collector current and collector-to-emitter voltage as a result of a variation in base current.




$$I_{BQ} = \frac{V_{BB} - 0.7 \text{ V}}{R_B} = \frac{3.7 \text{ V} - 0.7 \text{ V}}{10 \text{ k}\Omega} = 300 \mu\text{A}$$


$$I_{CQ} = \beta_{DC} I_{BQ} = (100)(300 \mu\text{A}) = 30 \text{ mA}$$
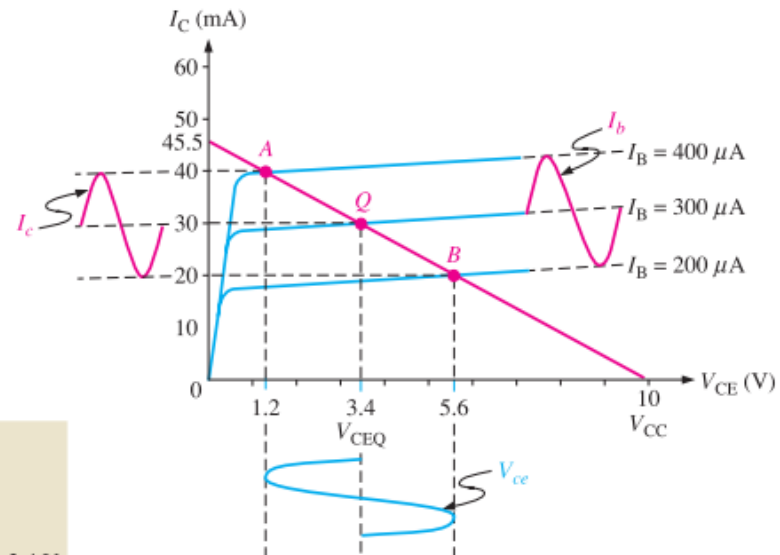
$$V_{CEQ} = V_{CC} - I_{CQ} R_C = 10 \text{ V} - (30 \text{ mA})(220 \Omega) = 3.4 \text{ V}$$



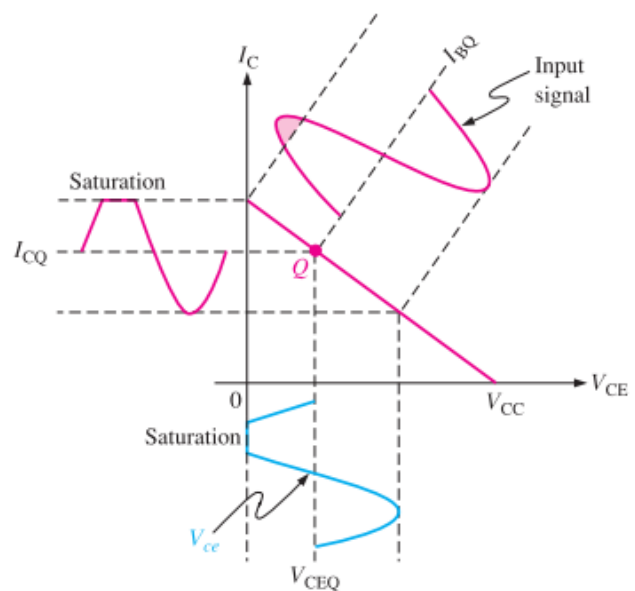


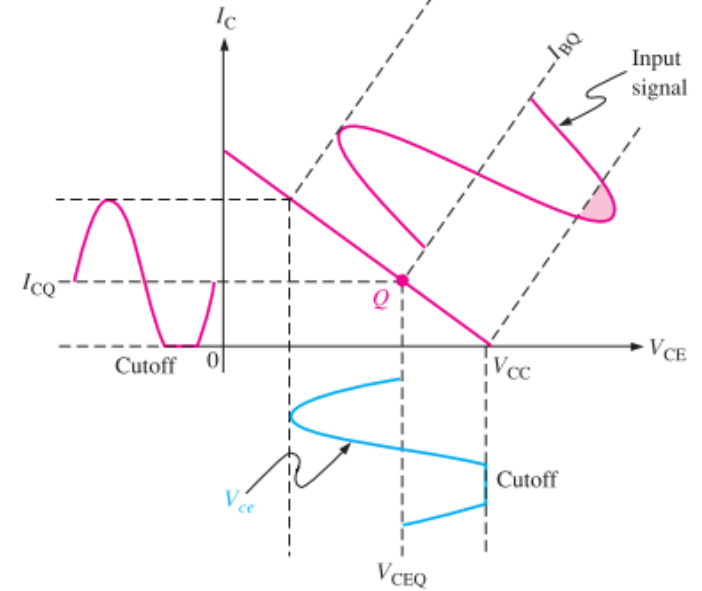(a) Transistor is driven into saturation because the Q-point is too close to saturation for the given input signal.



(b) Transistor is driven into cutoff because the Q-point is too close to cutoff for the given input signal.


Waveform Distortion

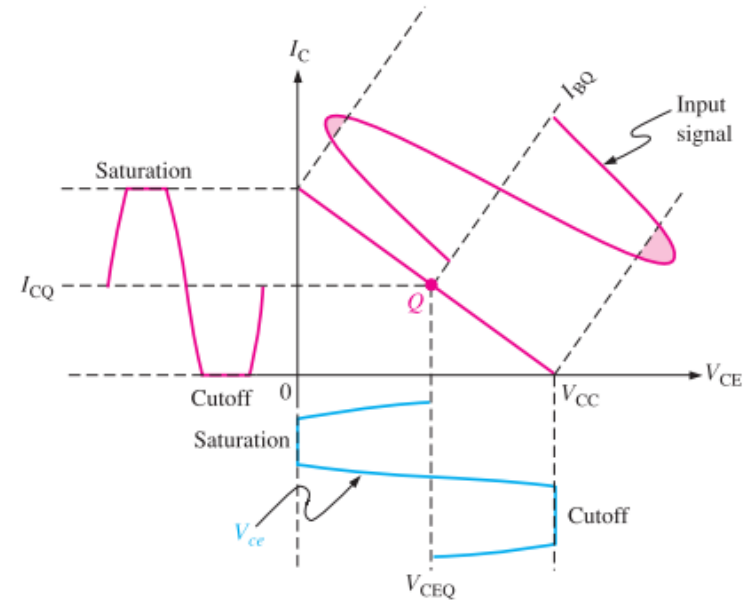

(c) Transistor is driven into both saturation and cutoff because the input signal is too large.



VOLTAGE-DIVIDER BIAS

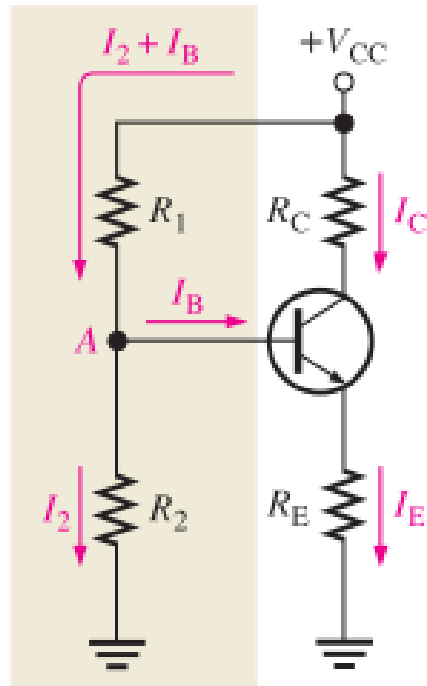

$$V_B \cong \left(\frac{R_2}{R_1 + R_2} \right) V_{CC}$$


$$V_E = V_B - V_{BE}$$

$$I_C \cong I_E = \frac{V_E}{R_E}$$

$$V_C = V_{CC} - I_C R_C$$

$$V_{CE} = V_C - V_E$$

Loading Effects of Voltage-Divider Bias

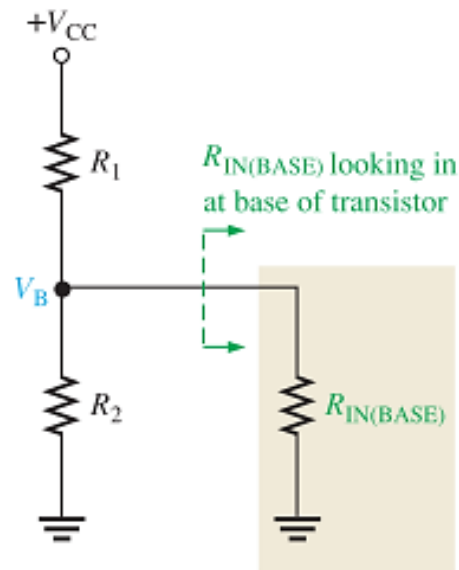

Stiff:

$$R_{IN(BASE)} \cong 10R_2$$

$$V_B \cong \left(\frac{R_2}{R_1 + R_2} \right) V_{CC}$$


Not stiff:

$$R_{IN(BASE)} < 10R_2$$

$$V_B = \left(\frac{R_2 \parallel R_{IN(BASE)}}{R_1 + R_2 \parallel R_{IN(BASE)}} \right) V_{CC}$$

$$R_{IN(BASE)} = \frac{\beta_{DC} V_B}{I_E}$$

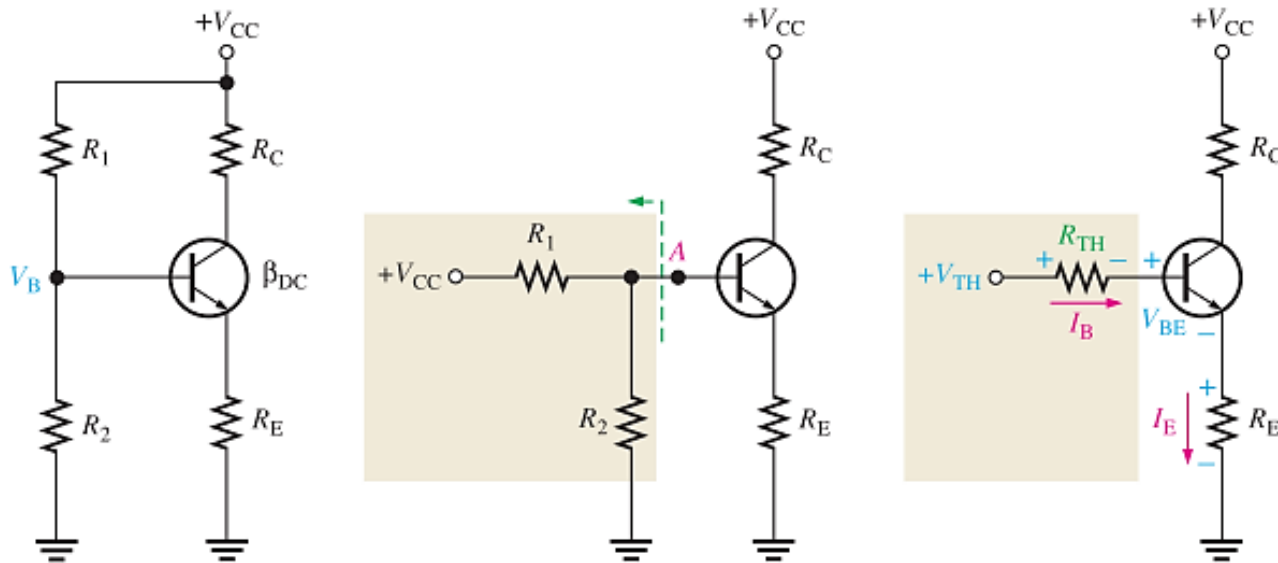Thevenin's Theorem Applied to Voltage-Divider Bias



$$V_{TH} = \left(\frac{R_2}{R_1 + R_2} \right) V_{CC}$$

$$R_{TH} = \frac{R_1 R_2}{R_1 + R_2}$$



$$V_{TH} - V_{R_{TH}} - V_{BE} - V_{R_E} = 0$$

$$V_{TH} = I_B R_{TH} + V_{BE} + I_E R_E$$

$$V_{TH} = I_E (R_E + R_{TH} / \beta_{DC}) + V_{BE}$$

$$I_E = \frac{V_{TH} - V_{BE}}{R_E + R_{TH} / \beta_{DC}}$$

Linear Amplifier

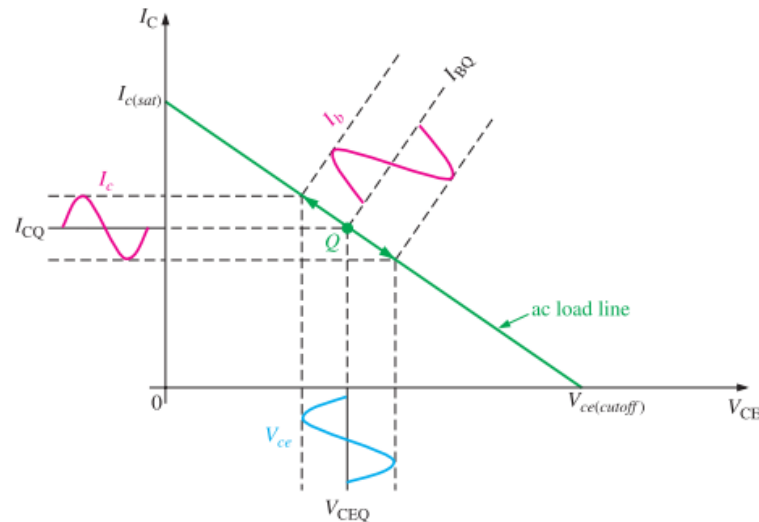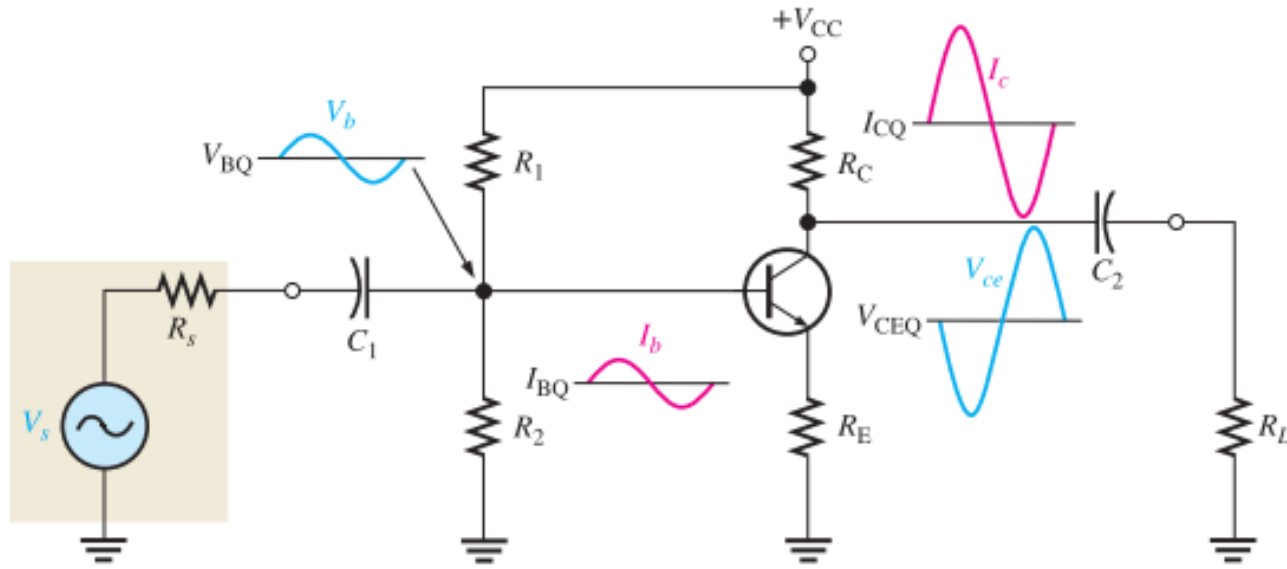



C.E. AC Analysis

- **DC Analysis:**

Capacitors \rightarrow Open Circuit
(See before)

- **AC Analysis:**

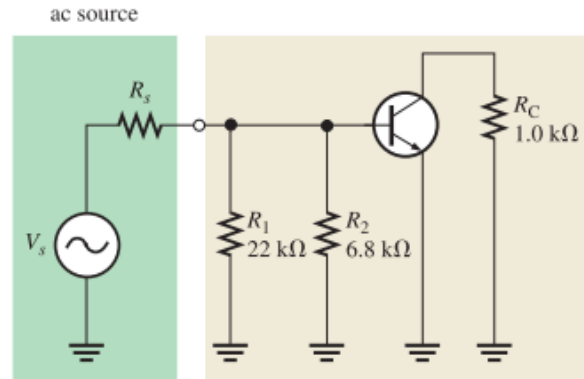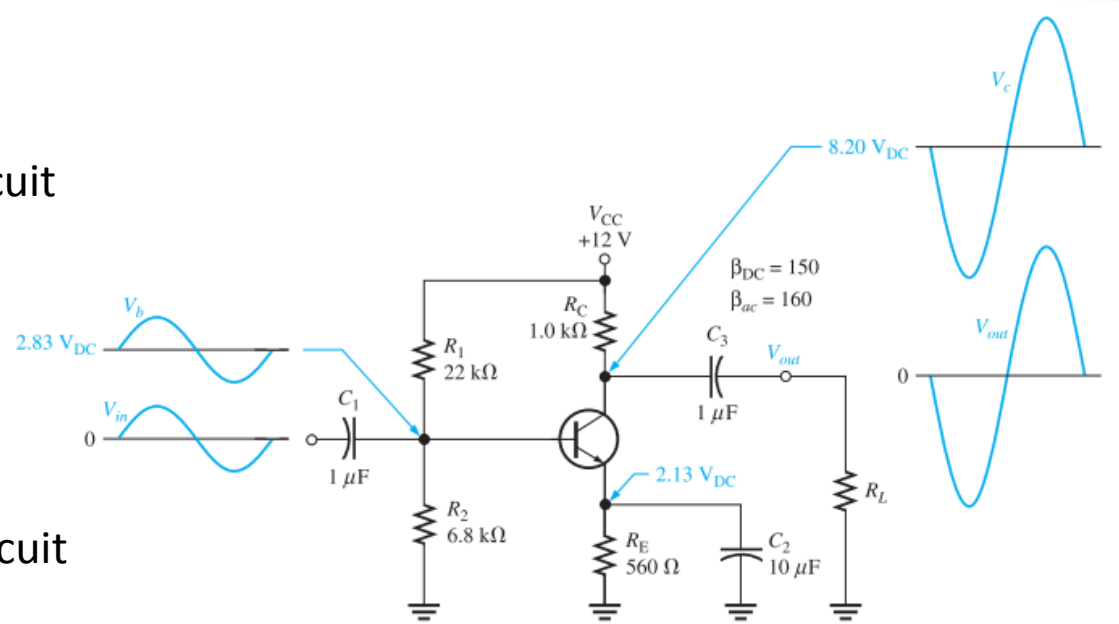Capacitors \rightarrow short Circuit
DC supply \rightarrow ground



AC r-parameter Model


Input resistance $R_{in(base)} = \beta_{ac} r'_e$

Output resistance $R_{out} \cong R_C$

Voltage gain $A_v = \frac{R_C}{r'_e}$

Current gain $A_i = \frac{I_c}{I_s}$

Power gain $A_p = A'_v A_i$

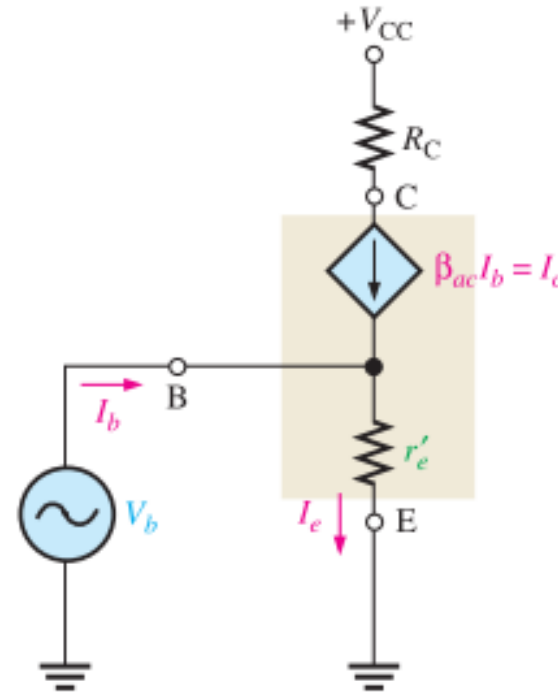


Multistage Amplifier


$$A'_v = A_{v1}A_{v2}A_{v3} \dots A_{v_n}$$

$$A_{v(\text{dB})} = 20 \log A_v$$
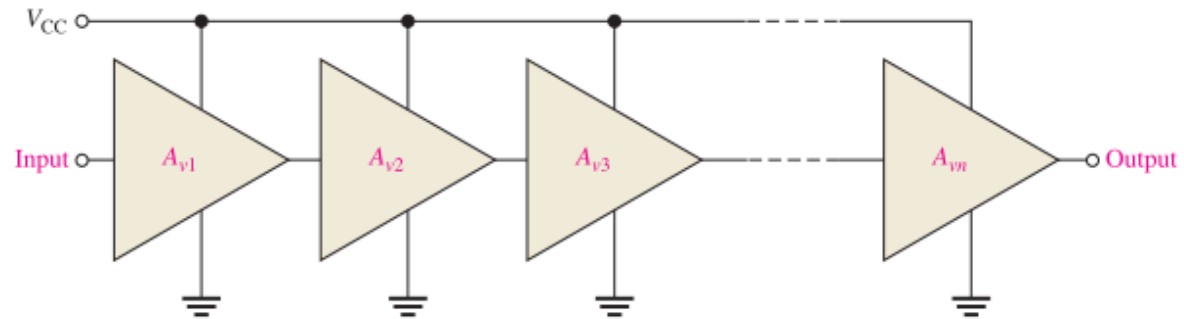
$$A'_{v(\text{dB})} = A_{v1(\text{dB})} + A_{v2(\text{dB})} + \dots + A_{v_n(\text{dB})}$$



- A two-stage common-emitter amplifier.

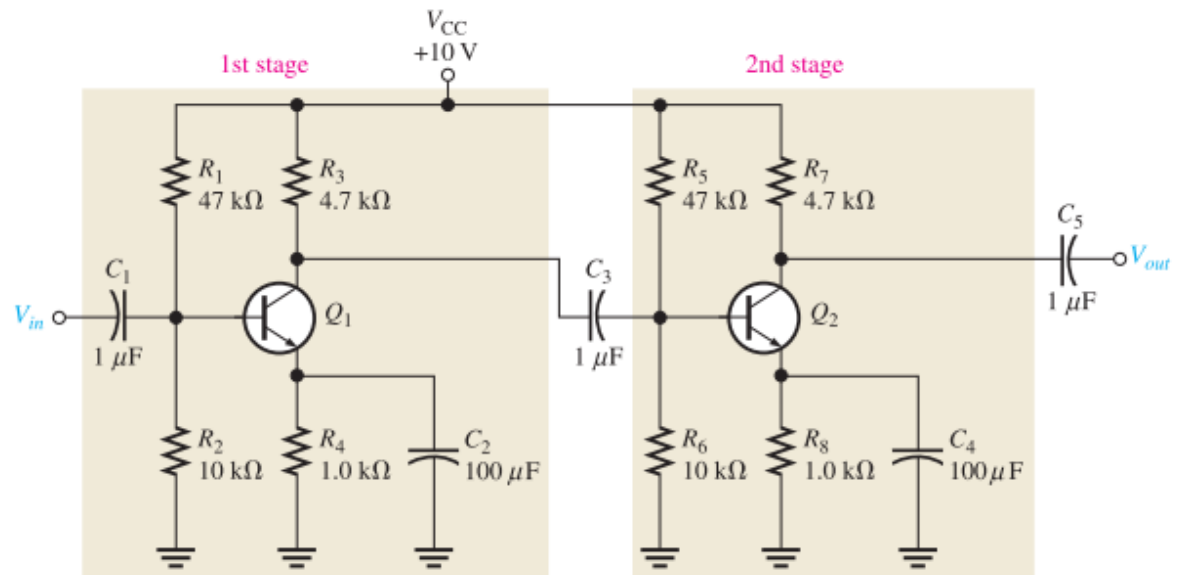


$\beta_{DC} = \beta_{ac} = 150$ for Q_1 and Q_2



Project II


Audio Preamplifier for PA System

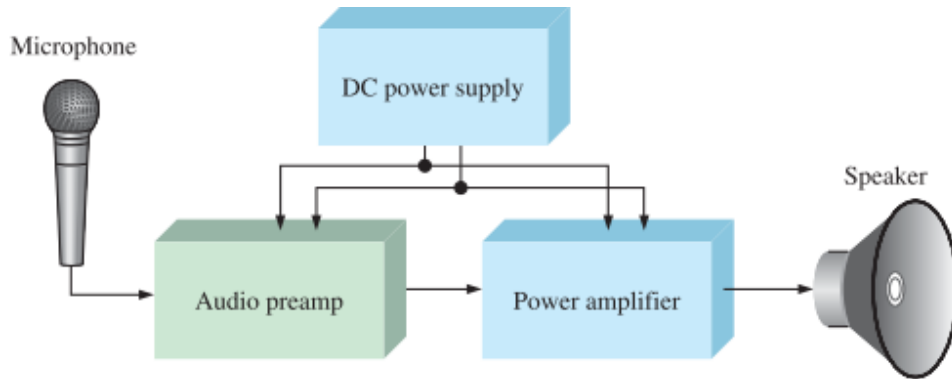


(a) PA system block diagram



(b) Physical configuration

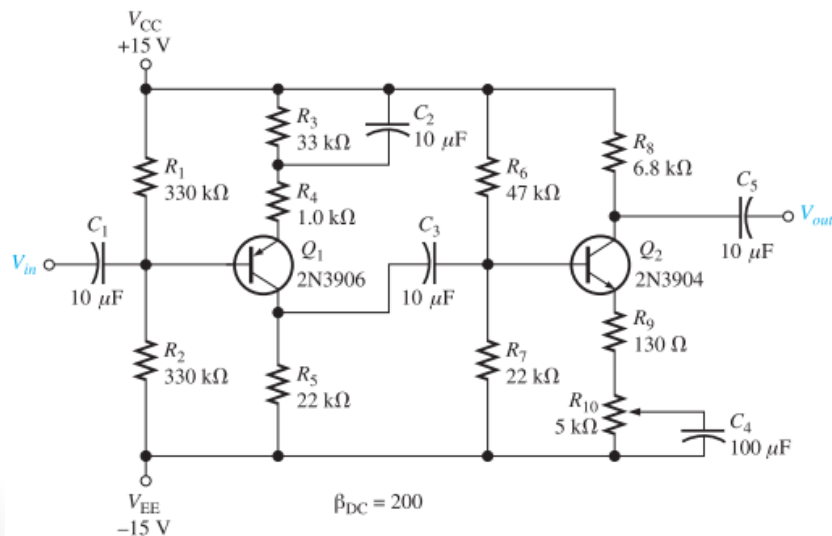

Pre AMP, chapter 4

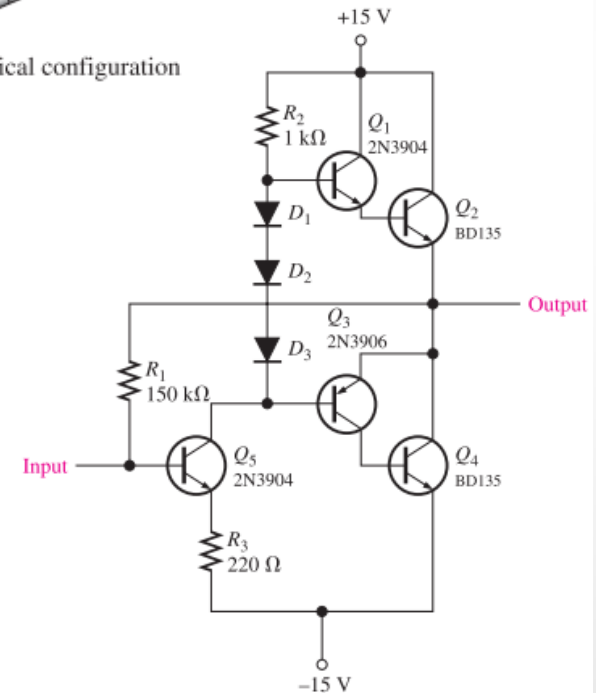

Class AB Power AMP, chapter 7



- For more details, refer to:
 - Chapters 4-6, T. Floyd, **Electronic Devices and Circuit Theory**, 11th edition, Prentice Hall.
- The lecture is available online at:
 - <http://bu.edu.eg/staff/ahmad.elbanna-courses/12136>
- For inquires, send to:
 - ahmad.elbanna@feng.bu.edu.eg