



BENHA UNIVERSITY
FACULTY OF ENGINEERING AT SHOUBRA

ECE-291
Electronic Engineering

Lecture #5
Basics of Digital Logic Design

Instructor:
Dr. Ahmad El-Banna



Agenda



Basic Concepts

Logic Gates

Examples of Logic Circuits

Digital logic is the foundation for digital computers!

BASIC CONCEPTS



Digital Electronics

- **Digital electronic circuits**, are electronics that represent signals by **discrete** bands of analog **levels**, rather than by continuous ranges (as used in analogue electronics).
- In most cases the number of **states** is **two**.
- They are represented by **two voltage bands**: one near a reference value (typically termed as "**ground**" or zero volts), and the other a value near the **supply** voltage.
- These correspond to the "false" ("**0**") and "true" ("**1**") values of the **Boolean** domain, respectively, yielding **binary** code.

Boolean Algebra	Boolean Logic	Voltage State
Logic "1"	True (T)	High (H)
Logic "0"	False (F)	Low (L)



Digital Electronics..

Advantages:

- Digital techniques are useful because it is easier to get an electronic device to switch into one of a number of known states than to accurately reproduce a continuous range of values.
- Signals represented digitally can be transmitted without degradation due to noise.
- Computer-controlled digital systems can be controlled by software, allowing new functions to be added without changing hardware.

Disadvantage:

- In some cases, digital circuits use more energy than analog circuits to accomplish the same tasks, thus producing more heat which increases the complexity of the circuits such as the inclusion of heat sinks.



Digital Electronics...

- A digital circuit is often constructed from small electronic circuits called **logic gates** that can be used to create combinational logic.
- Each logic gate represents a **function of boolean logic**.
- A logic gate is an arrangement of electrically controlled switches, better known as **transistors**.
- Logic gates often use the **fewest number of transistors** in order to reduce their size, power consumption and cost, and increase their reliability.
- **Integrated circuits** are the **least expensive** way to make logic gates in large volumes. Integrated circuits are usually designed by engineers using electronic design automation software



Classification of Integrated Circuits


- Small Scale Integration or (SSI) – Contain up to 10 transistors or a few gates within a single package such as AND, OR, NOT gates.
- Medium Scale Integration or (MSI) – between 10 and 100 transistors or tens of gates within a single package and perform digital operations such as adders, decoders, counters, flip-flops and multiplexers.
- Large Scale Integration or (LSI) – between 100 and 1,000 transistors or hundreds of gates and perform specific digital operations such as I/O chips, memory, arithmetic and logic units.
- Very-Large Scale Integration or (VLSI) – between 1,000 and 10,000 transistors or thousands of gates and perform computational operations such as processors, large memory arrays and programmable logic devices.
- Super-Large Scale Integration or (SLSI) – between 10,000 and 100,000 transistors within a single package and perform computational operations such as microprocessor chips, micro-controllers, basic PICs and calculators.
- Ultra-Large Scale Integration or (ULSI) – more than 1 million transistors – the big boys that are used in computers CPUs, GPUs, video processors, micro-controllers, FPGAs and complex PICs.



LOGIC GATES



BASIC LOGIC BLOCK (GATE)

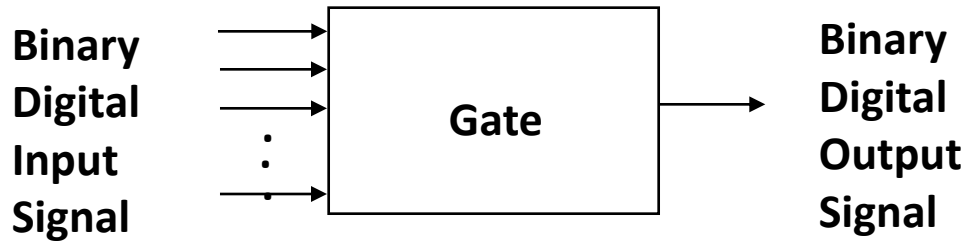

- **Types of Basic Logic Blocks**

- **Combinational Logic Block**

- Logic Blocks whose output logic value depends only on the input logic values

- **Sequential Logic Block**

- Logic Blocks whose output logic value depends on the input values and the state (stored information) of the blocks


- **Functions of Gates can be described by**

- Truth Table
 - Boolean Function
 - Karnaugh Map

NOT Gate -- Inverter


If A is NOT true, then Q is true

- The Logic NOT Gate Truth Table

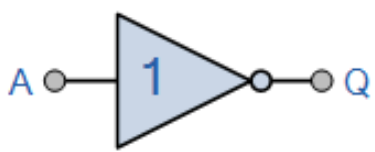
Symbol	Truth Table	
 <p>Inverter or NOT Gate</p>	A	Q
	0	1
	1	0
Boolean Expression $Q = \text{not } A$ or \bar{A}	Read as inverse of A gives Q	

NOT Gate – Inverter..

- Transistor NOT Gate

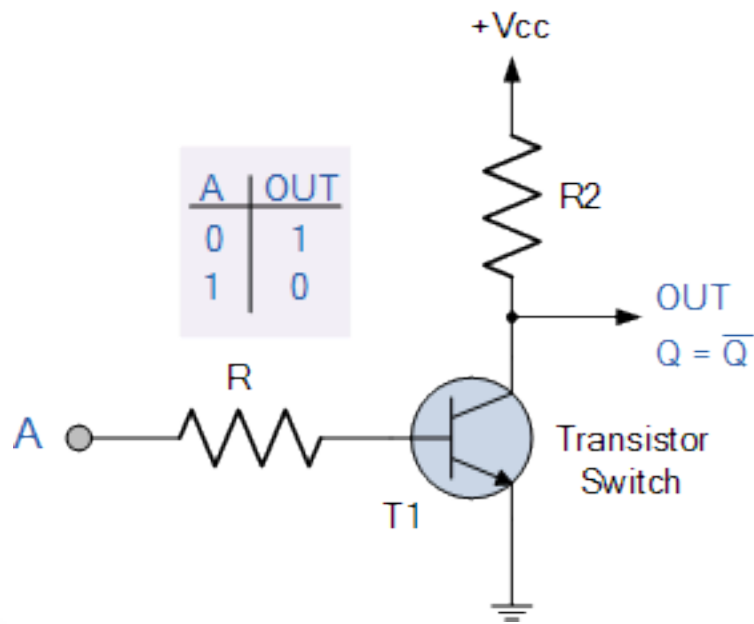



- 7404 NOT Gate or Inverter

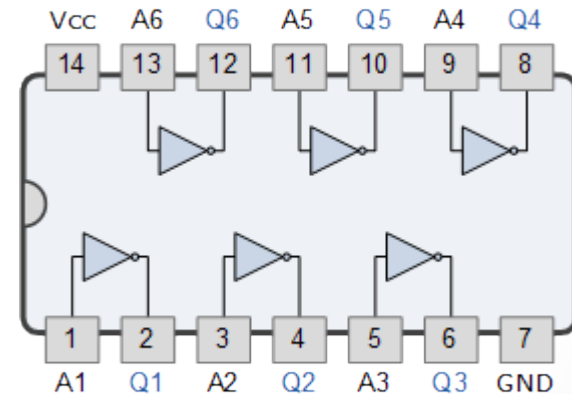

OR Gate


If either A or B is true, then Q is true

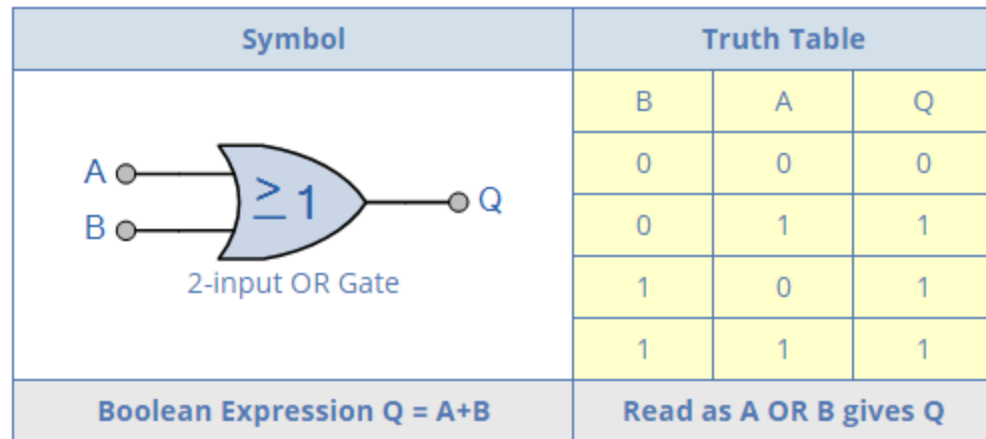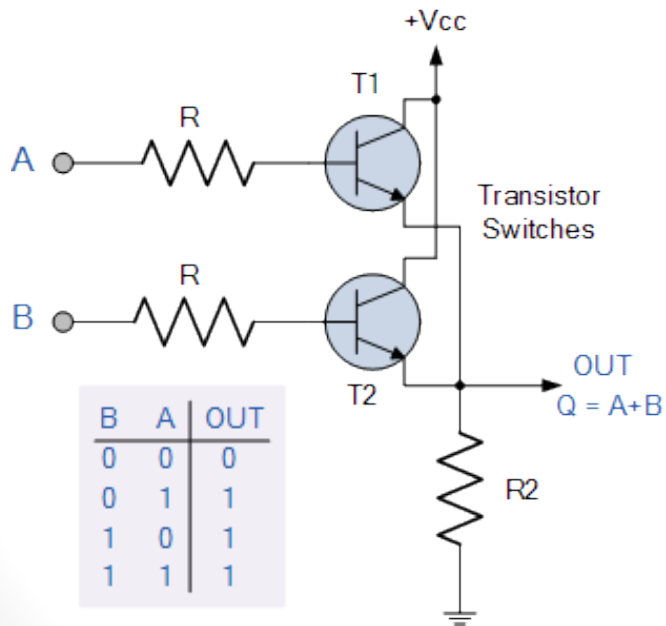- 2-input Transistor OR Gate
- The 2-input Logic OR Gate




OR Gate..

- The 3-input Logic OR Gate

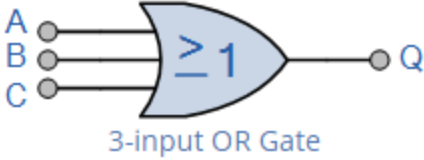Symbol	Truth Table			
 <p>3-input OR Gate</p>	C	B	A	Q
	0	0	0	0
	0	0	1	1
	0	1	0	1
	0	1	1	1
	1	0	0	1
	1	0	1	1
	1	1	0	1
	1	1	1	1
Boolean Expression $Q = A+B+C$	Read as A OR B OR C gives Q			

- Multi-input OR Gate

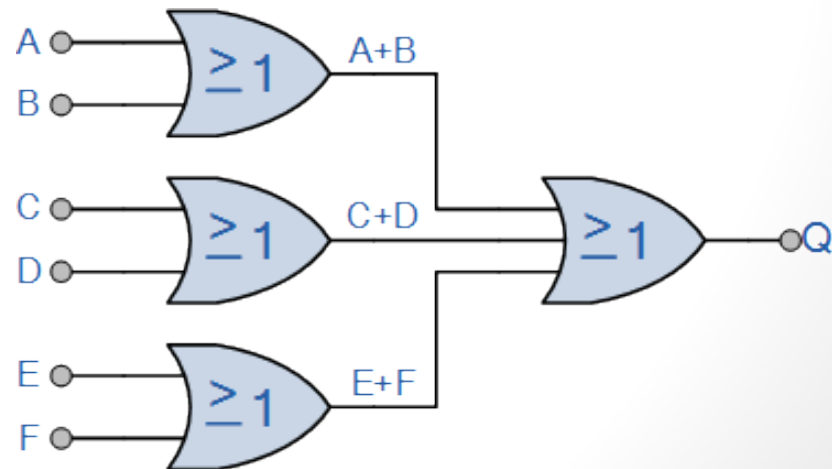



6-input "OR" Function



AND Gate


If both A and B are true, then Q is true

Symbol	Truth Table		
 <p>2-input AND Gate</p>	B	A	Q
	0	0	0
	0	1	0
	1	0	0
	1	1	1
Boolean Expression $Q = A.B$	Read as A AND B gives Q		


Symbol	Truth Table			
 <p>3-input AND Gate</p>	C	B	A	Q
	0	0	0	0
	0	0	1	0
	0	1	0	0
	0	1	1	0
	1	0	0	0
	1	0	1	0
	1	1	0	0
	1	1	1	1
	Boolean Expression $Q = A.B.C$	Read as A AND B AND C gives Q		

AND Gate..

- 2-input Transistor AND Gate

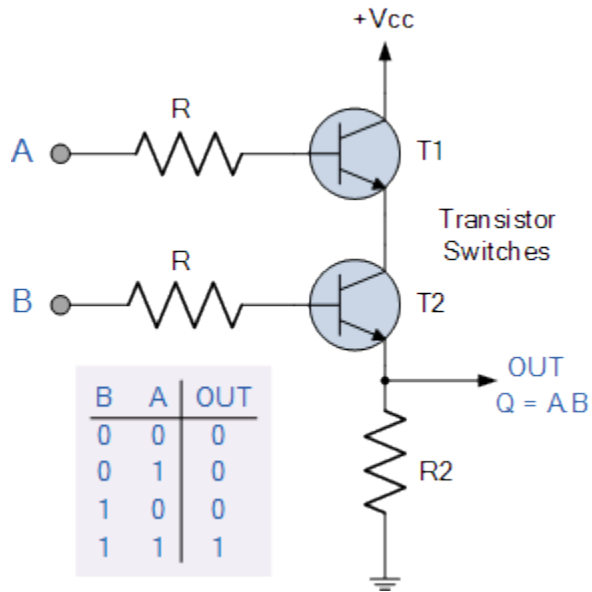


- Multi-input AND Gate

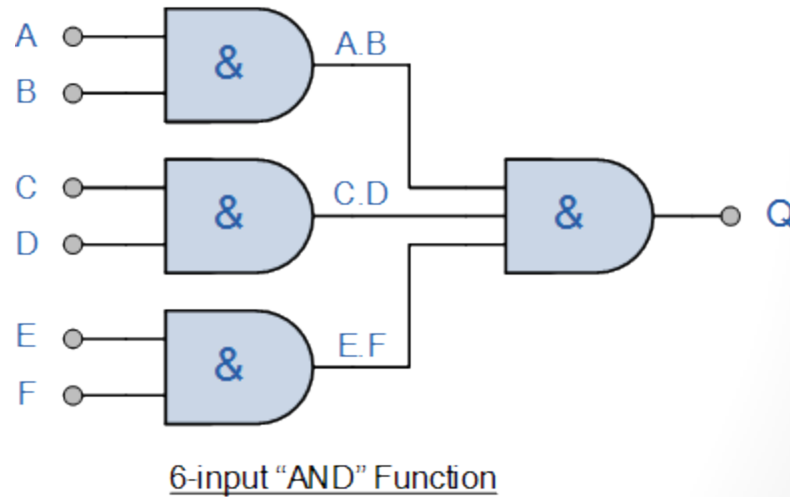

OR/AND Gates using diodes

OR

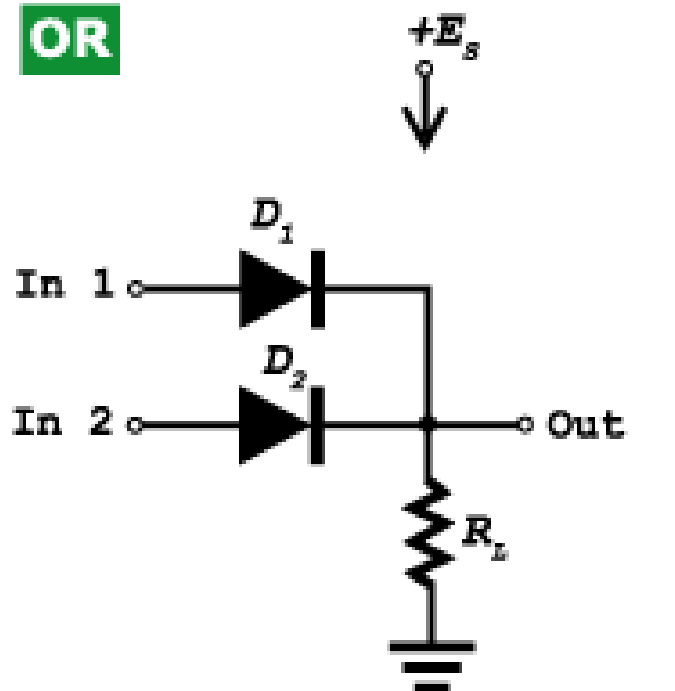

In 1	In 2	Out
0	0	0
0	1	1
1	0	1
1	1	1


0
0
1
1

0
1
0
1

0
1
1
1

0 - 0V
1 - Es

AND

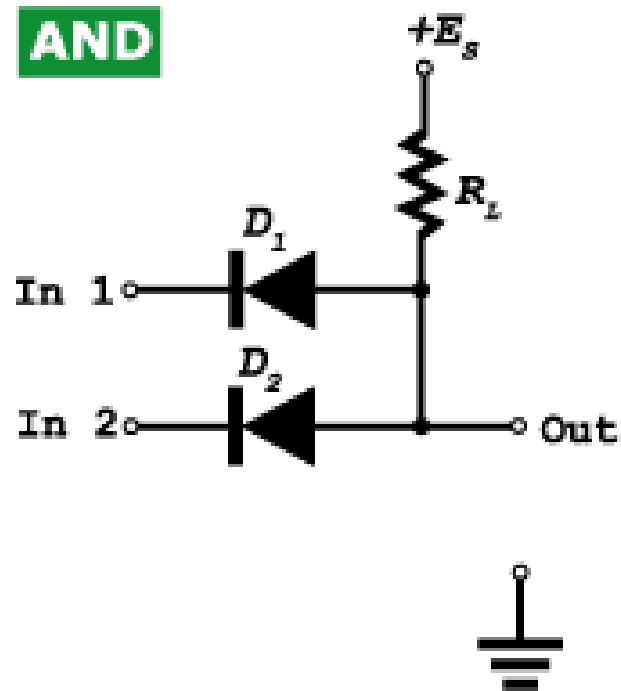

In 1	In 2	Out
0	0	0
0	1	0
1	0	0
1	1	1


0
0
1
1

0
1
0
1


0
0
0
1

74xx IC


- 7432 Quad 2-input Logic OR Gate

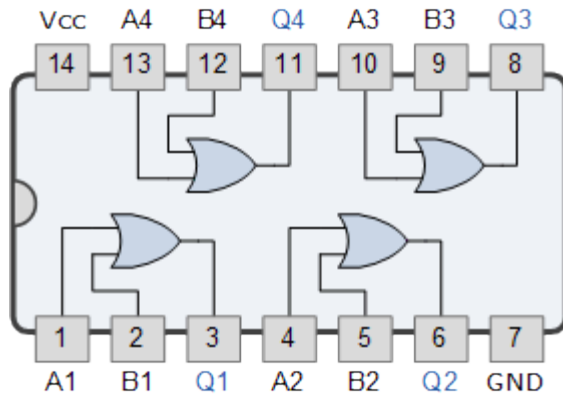



- 7408 Quad 2-input AND Gate

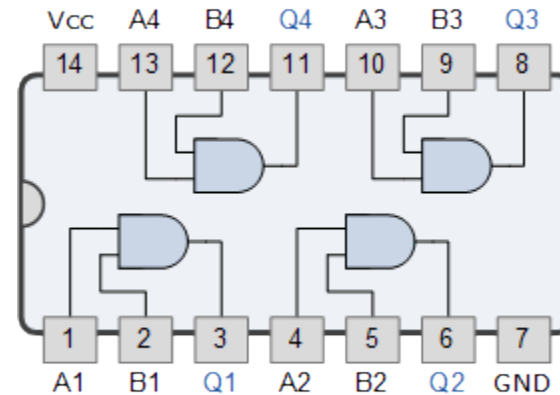


NOR Gate

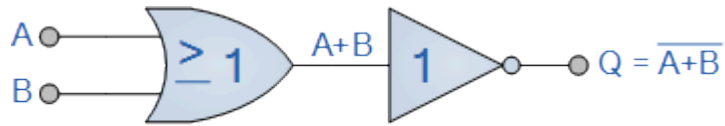


2-input "OR" gate plus a "NOT" gate

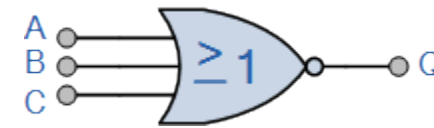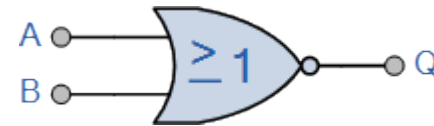





B	A	OUT
0	0	1
0	1	0
1	0	0
1	1	0

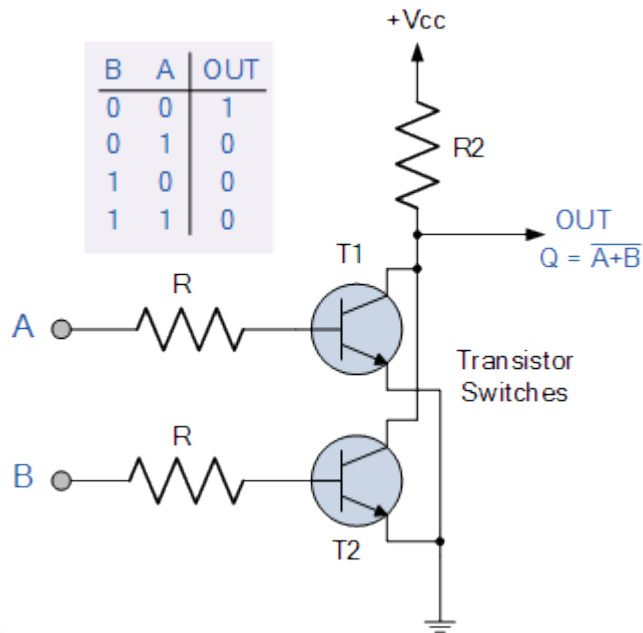


7402 Quad 2-input NOR Gate

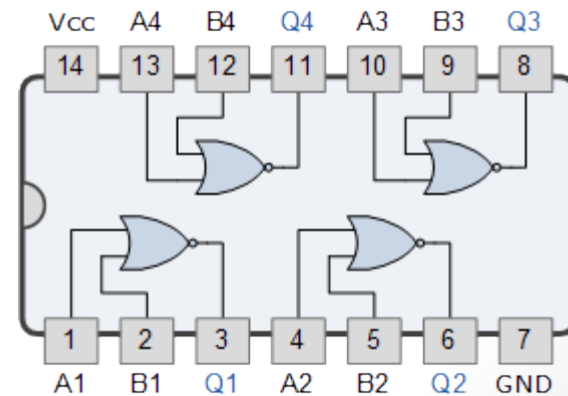

NAND Gate

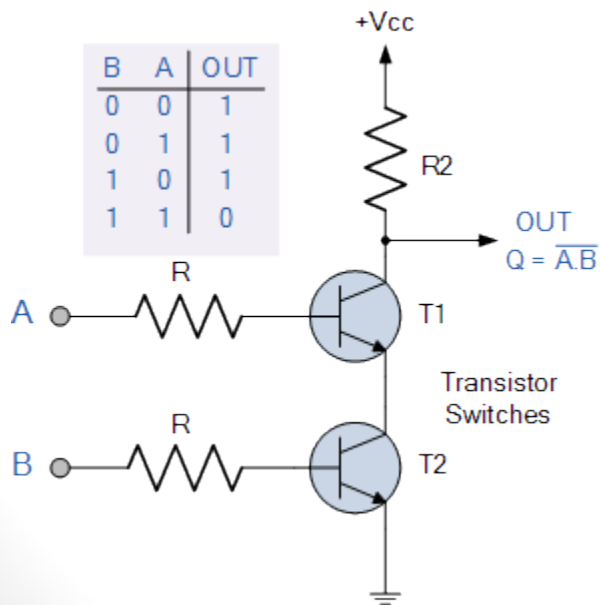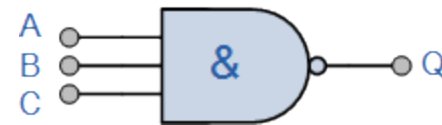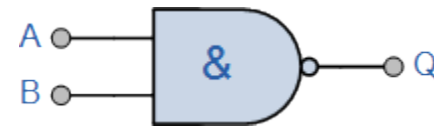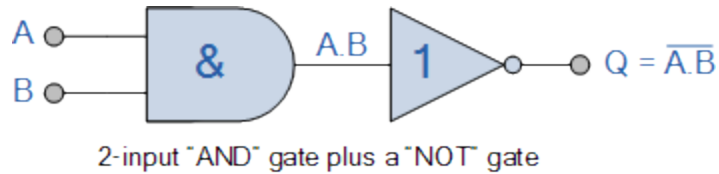


7400 Quad 2-input Logic NAND Gate

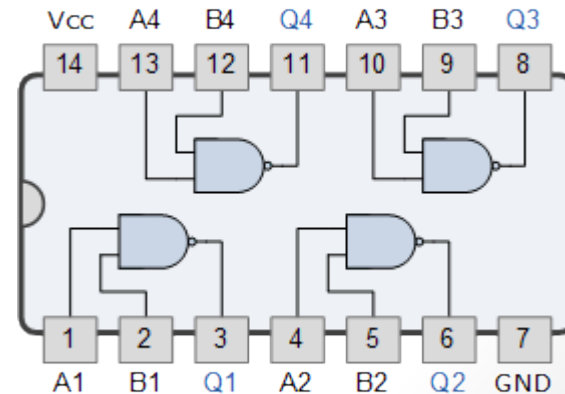


NOR & NAND Universal Gate

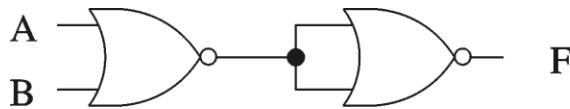
- Any gate can be constructed using them.




OR gate

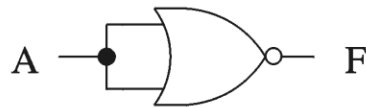


NOT gate

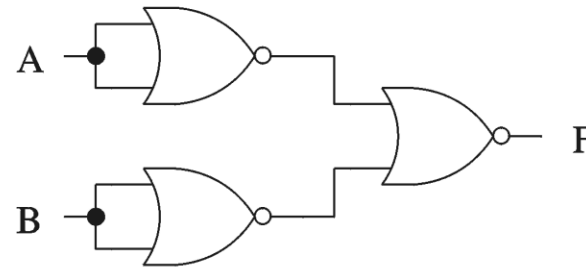


AND gate

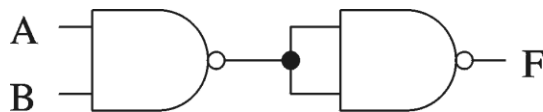

AND gate

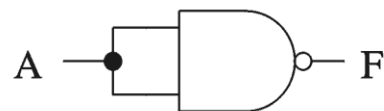



NOT gate

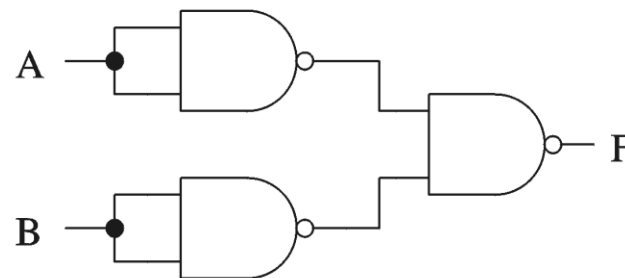


OR gate

XOR and XNOR Gates

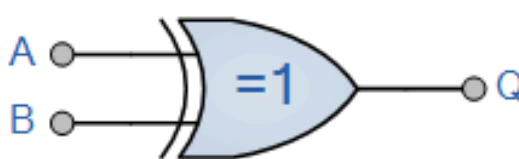Symbol	Truth Table		
 <p>2-input Ex-OR Gate</p>	B	A	Q
	0	0	0
	0	1	1
	1	0	1
	1	1	0
Boolean Expression $Q = A \oplus B$	A OR B but NOT BOTH gives Q		

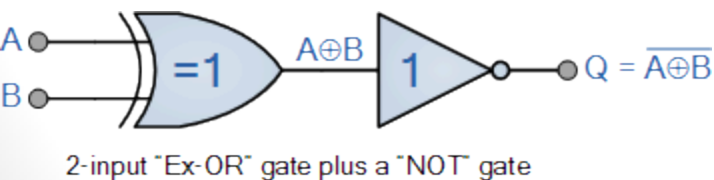

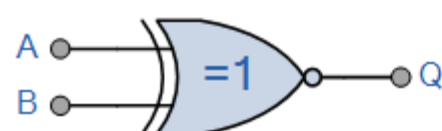Symbol	Truth Table		
 <p>2-input Ex-NOR Gate</p>	B	A	Q
	0	0	1
	0	1	0
	1	0	0
	1	1	1
Boolean Expression $Q = \overline{A \oplus B}$	Read if A AND B the SAME gives Q		



Truth Table Summary

Inputs		Truth Table Outputs For Each Gate					
A	B	AND	NAND	OR	NOR	EX-OR	EX-NOR
0	0	0	1	0	1	0	1
0	1	0	1	1	0	1	0
1	0	0	1	1	0	1	0
1	1	1	0	1	0	0	1

Truth Table Output for Single-input Gates		
A	NOT	Buffer
0	1	0
1	0	1



EXAMPLES OF LOGIC CIRCUITS




Example of a Logic Function

3-input majority function

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

- Logical expression form

$$F = AB + BC + AC$$

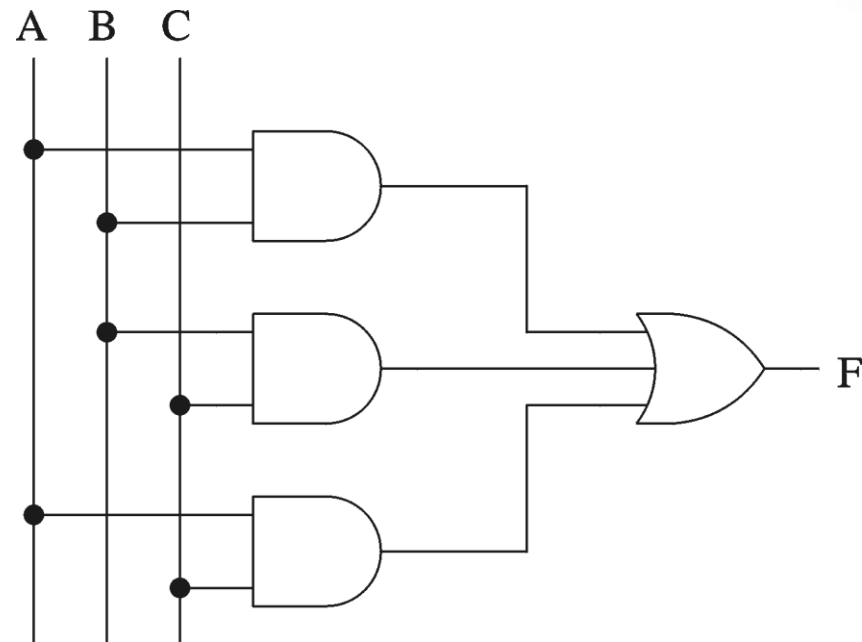


Multiplexers

- An Example of Combinational Circuit
- Output depends only on the current inputs

4-data input MUX

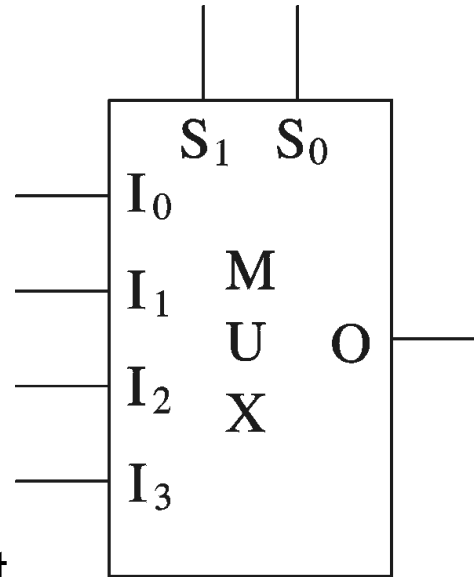- Multiplexer
 - 2^n data inputs
 - n selection inputs
 - a single output
- Selection input determines the input that should be connected to the output




S_1	S_0	O
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3


SR Latch

- A Sequential example
 - Output depends on current as well as past inputs
- Can remember a bit
- Level-sensitive (not edge-sensitive)

A NOR gate implementation of SR latch

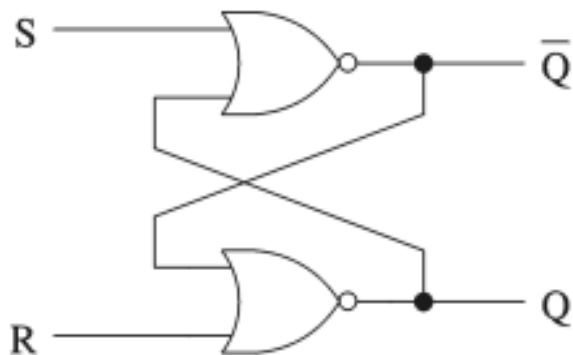

(a) Circuit diagram

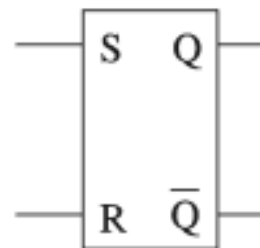

(b) Logic symbol

S	R	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	0

(c) Truth table

- For more details, refer to:
 - **Digital Logic Tutorial**, found online at http://www.electronics-tutorials.ws/logic/logic_1.html
 - Other Digital Logic online Tutorials & wiki.
 - Reference books:
 - M. Mano, **Digital-Design**, 4th ed.
 - **Fundamentals of Computer Organization and Design.**
- The lecture is available online at:
 - <http://bu.edu.eg/staff/ahmad.elbanna-courses/12136>
- For inquires, send to:
 - ahmad.elbanna@feng.bu.edu.eg