



FACULTY OF ENGINEERING
DEPARTMENT OF ELECTRONICS AND COMMUNICATIONS

GEE336

Electronic Circuits II

Lecture #6

Sinusoidal Oscillators

Instructor:

Dr. Ahmad El-Banna



Agenda



Introduction

Feedback Oscillators


Oscillators with RC Feedback Circuits

- Wien-bridge & Phase-shift & Quadrature Osc.

INTRODUCTION

Introduction


- An **oscillator** is a circuit that produces a periodic waveform on its output with only the dc supply voltage as an input.
 - The output voltage can be either **sinusoidal** or **non sinusoidal**, depending on the type of oscillator.
 - Two major classifications for oscillators are **feedback** oscillators and **relaxation** oscillators.
- an oscillator converts electrical energy from the dc power supply to periodic waveforms.

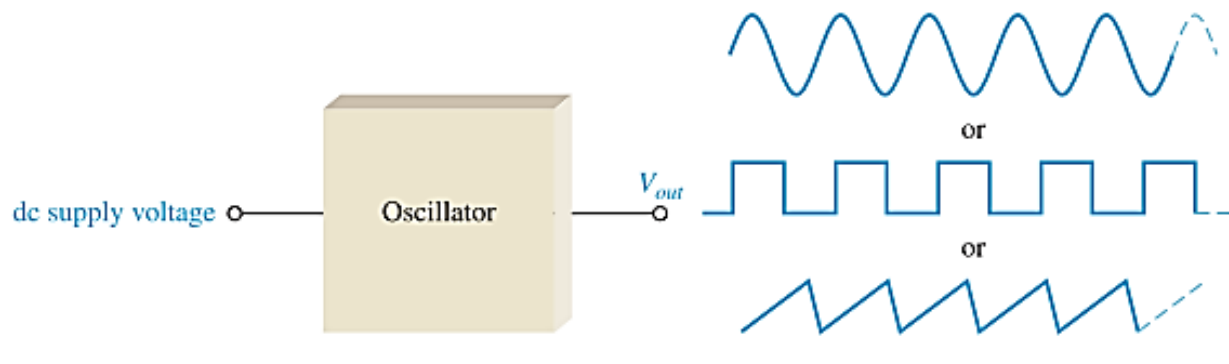



FEEDBACK OSCILLATORS

Positive feedback

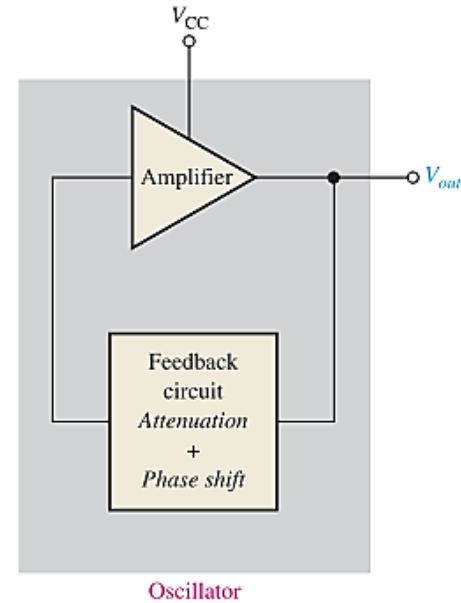- Positive feedback is characterized by the condition wherein a portion of the output voltage of an amplifier is fed back to the input with no net phase shift, resulting in a reinforcement of the output signal.




Basic elements of a feedback oscillator.

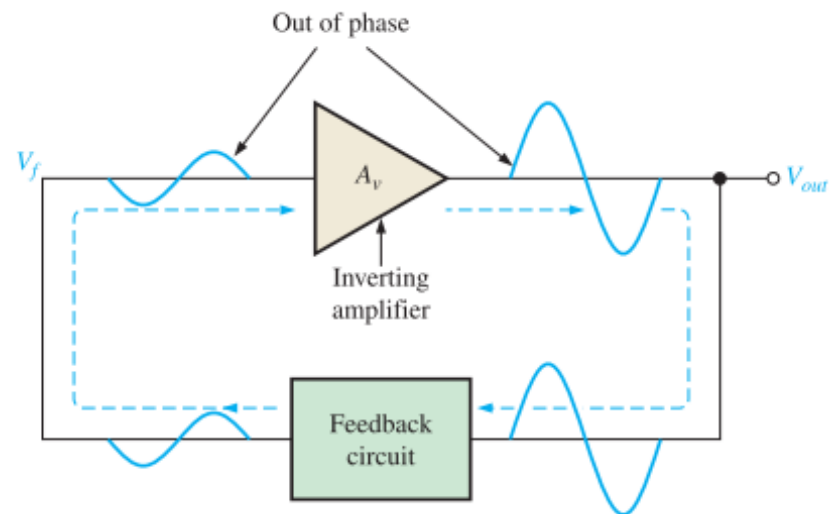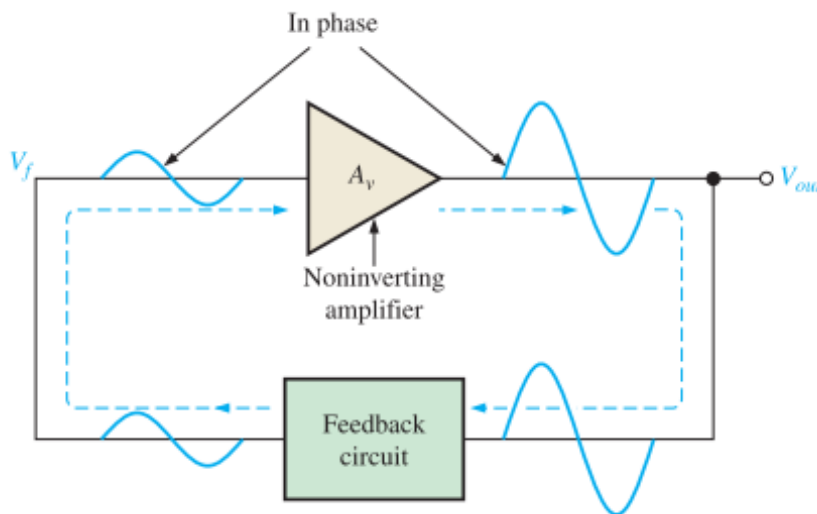


Conditions for Oscillation

- Two conditions:
 1. The phase shift around the feedback loop must be effectively 0° .
 2. The voltage gain, A_{cl} around the closed feedback loop (loop gain) must equal 1 (unity).

$$A_{cl} = A_v B$$

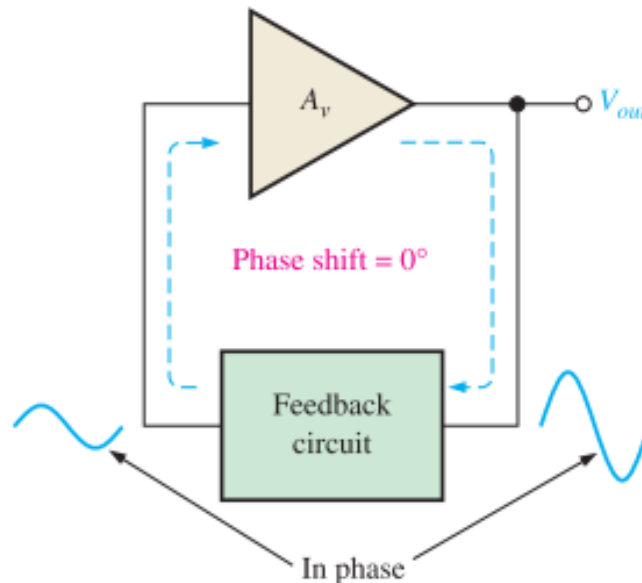

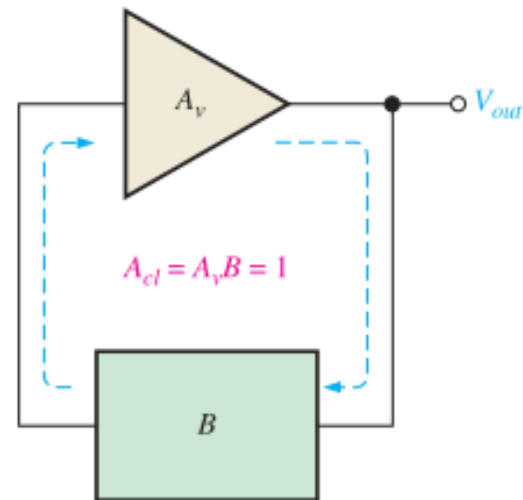
(a) The phase shift around the loop is 0° .



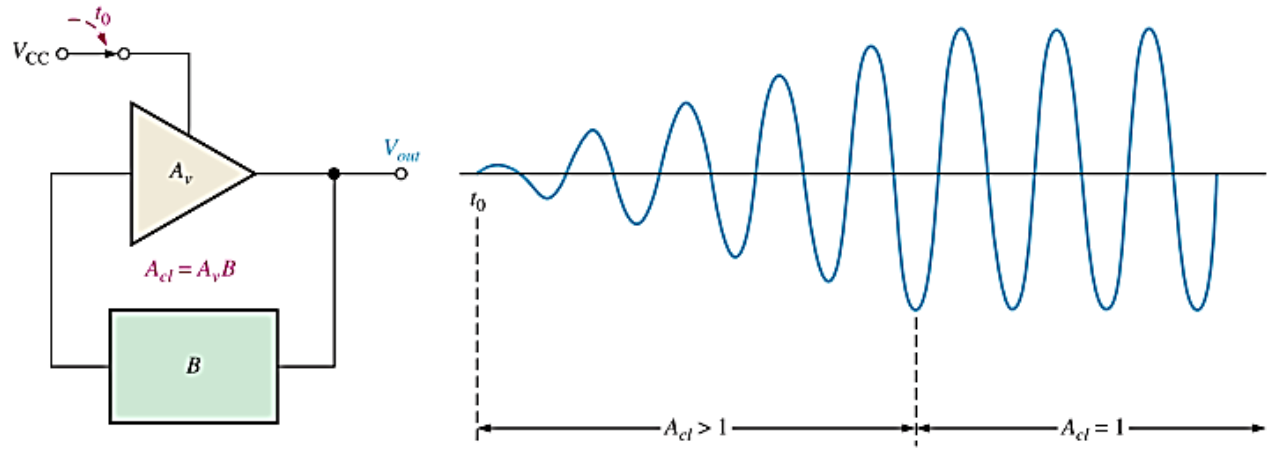(b) The closed loop gain is 1.

Start-Up Conditions

- For oscillation to begin, the voltage gain around the positive feedback loop must be greater than 1 so that the amplitude of the output can build up to a desired level.
- The gain must then decrease to 1 so that the output stays at the desired level and oscillation is sustained.
- Initially, a small positive feedback voltage develops from thermally produced broad-band noise in the resistors or other components or from power supply turn-on transients.



Wien-bridge oscillator

Phase-shift oscillator

Quadrature oscillator

OSCILLATORS WITH RC FEEDBACK CIRCUITS



The Wien-Bridge Oscillator

- Generally, RC feedback oscillators are used for frequencies up to about 1 MHz.
- The Wien-bridge is by far the most widely used type of RC feedback oscillator for this range of frequencies.

$$R_1 = R_2 \text{ and } X_{C1} = X_{C2}$$


$$\frac{V_{out}}{V_{in}} = \frac{1}{3}$$

$$f_r = \frac{1}{2\pi RC}$$

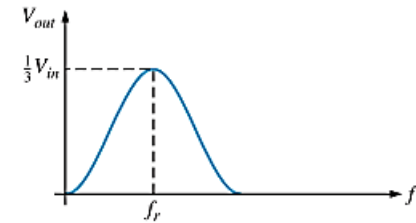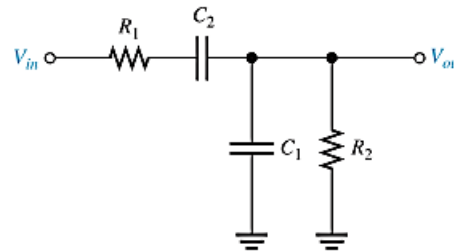


Lead-lag circuit and its response curve

• Basic Circuit

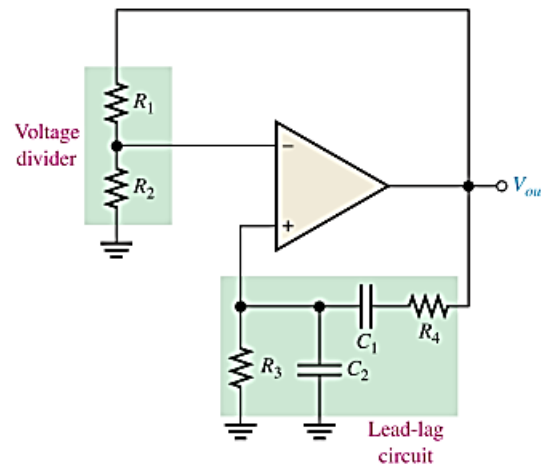

(a)


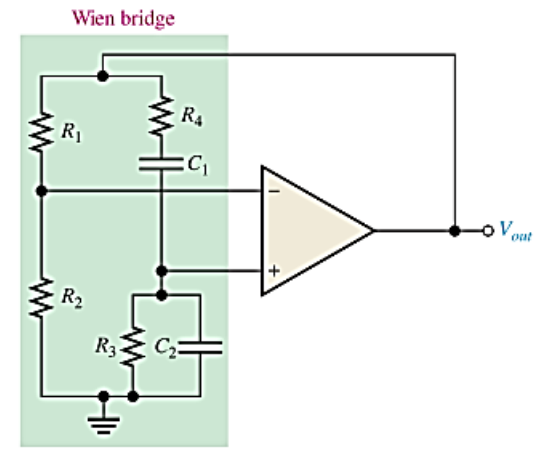


(b) Wien bridge circuit combines a voltage divider and a lead-lag circuit.

▲ FIGURE 16-7

The Wien-bridge oscillator schematic drawn in two different but equivalent ways.

The Wien-Bridge Oscillator..

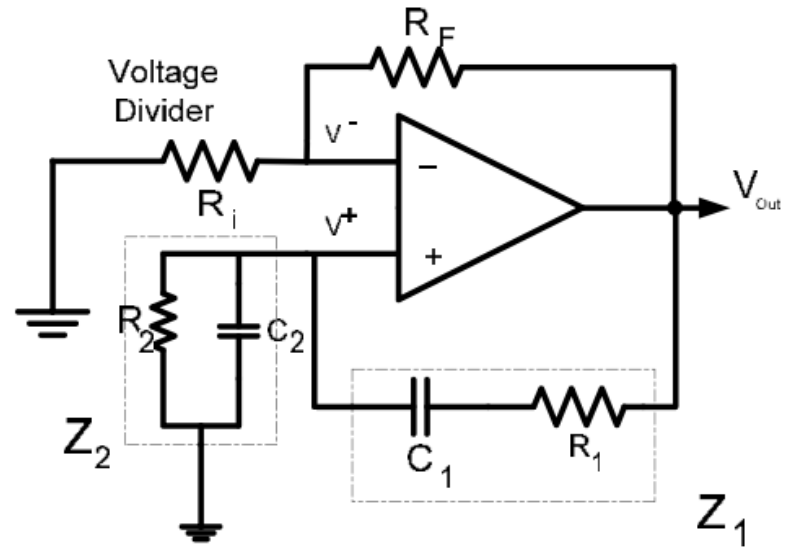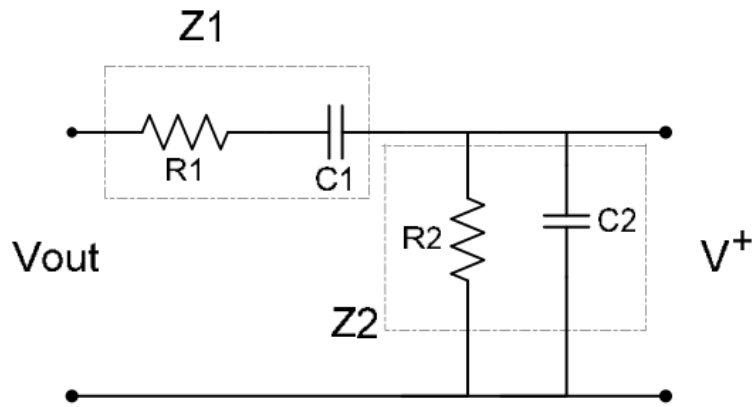

$$Z_1 = R_1 - \frac{j}{\omega c_1} \quad \dots\dots\dots(1)$$

$$Z_2 = R_2 \parallel -\frac{j}{\omega c_2} = \frac{R_2 \times \frac{-j}{\omega c_2}}{R_2 - \frac{j}{\omega c_2}} \quad \dots\dots\dots(2) \quad \div \left(\frac{-j}{\omega c_2} \right)$$

$$\therefore Z_2 = \frac{R_2}{j\omega R_2 C_2 + 1} \quad \dots\dots\dots(3)$$

The Wien-Bridge Oscillator...

$$\beta = \frac{V^+}{V_{out}} = \frac{Z_2}{Z_1 + Z_2} = \frac{\left(\frac{R_2}{j\omega R_2 C_2 + 1}\right)}{\left(R_1 - \frac{j}{\omega C_1}\right) + \left(\frac{R_2}{j\omega R_2 C_2 + 1}\right)} \dots\dots\dots(4)$$

$$\beta = \frac{V^+}{V_{out}} = \frac{\left(\frac{R_2}{j\omega R_2 C_2 + 1}\right)}{\left(\frac{R_1 + j\omega R_1 R_2 C_2 + \frac{R_2 C_2}{C_1} - \frac{j}{\omega C_1} + R_2}{j\omega R_2 C_2 + 1}\right)} \dots\dots\dots(5)$$

$$\beta = \frac{V^+}{V_{out}} = \frac{R_2}{\left(R_1 + R_2 + R_2 \times \frac{C_2}{C_1}\right) + j\left(\omega R_1 R_2 C_2 - \frac{1}{\omega C_1}\right)} \dots\dots\dots(6)$$

The Wien-Bridge Oscillator....

In order for V^+ to have the same phase as V_{out} , this ratio must be a purely real number. Therefore, the imaginary part in Equation (6) must be zero. Setting the imaginary part equal to zero and solving for ω gives us the oscillation frequency:

$$\omega_o R_1 R_2 C_2 - \frac{1}{\omega_o C_1} = 0 \Rightarrow \omega_o R_1 R_2 C_2 = \frac{1}{\omega_o C_1} \Rightarrow \omega_o^2 = \frac{1}{R_1 R_2 C_1 C_2} \dots(7)$$

$$\omega_o = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}} \dots\dots\dots(8)$$

$$f = f_0 = \frac{1}{2\pi \sqrt{R_1 R_2 C_1 C_2}} \dots\dots\dots(9)$$

$R_1 = R_2 = R$ and $C_1 = C_2 = C$.

$$f = f_o = \frac{1}{2\pi RC} \dots\dots\dots(10)$$

The Wien-Bridge Oscillator.....

When $R_1 = R_2 = R$ and $C_1 = C_2 = C$, the feedback ratio at the oscillation frequency is:

$$\beta = \frac{R}{R + R + R \times \frac{C}{C} + j0} = \frac{R}{3R} = \frac{1}{3} \dots\dots\dots(11)$$

Therefore, the amplifier must provide a gain of 3 to make the magnitude of the loop gain unity and sustain oscillation.

$$A = \frac{1}{\beta} = 3 \dots\dots\dots(12)$$

For non-inverting amplifier:

$$A = 1 + \frac{R_F}{R_i} = 3 \Rightarrow \frac{R_F}{R_i} = 2 \dots\dots\dots(13)$$


The Wien-Bridge Oscillator.....

- Positive Feedback Conditions for Oscillation


$$A_{cl} = 3 \longrightarrow A_{cl} = 1 + (R_1/R_2)$$

choose $R_1 = 2R_2$
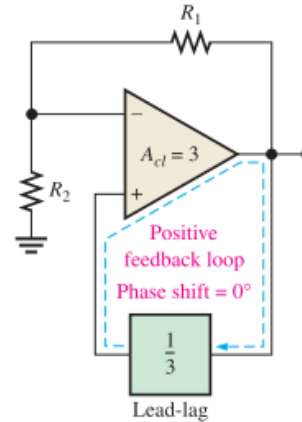
$$A_{cl} = \frac{R_1 + R_2}{R_2} = \frac{2R_2 + R_2}{R_2} = \frac{3R_2}{R_2} = 3$$



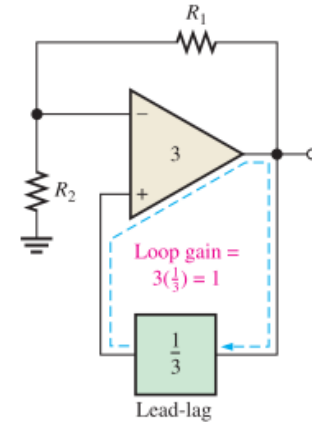
(a) The phase shift around the loop is 0°.




(b) The voltage gain around the loop is 1.

- Start-Up Conditions

$$(A_{cl} > 3)$$

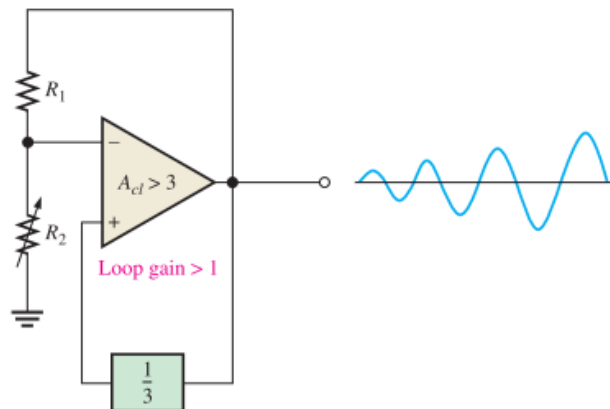

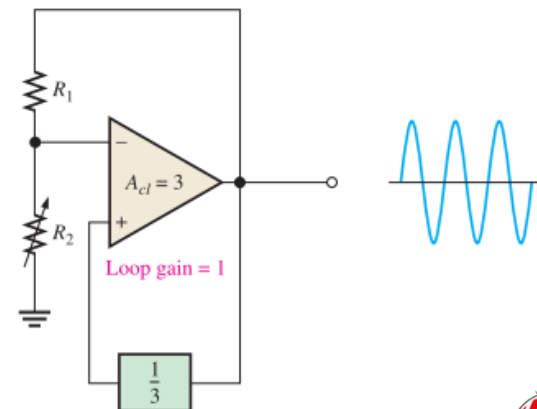(a) Loop gain greater than 1 causes output to build up.



(b) Loop gain of 1 causes a sustained constant output.

Self-starting Wien-bridge oscillator


Using a form of automatic gain control (AGC)

1- When dc power is first applied, both zener diodes appear as opens.

$$A_{cl} = \frac{R_1 + R_2 + R_3}{R_2} = \frac{3R_2 + R_3}{R_2} = 3 + \frac{R_3}{R_2}$$

2- When the zeners conduct, they short out R_3 and $A_{cl} = 3$

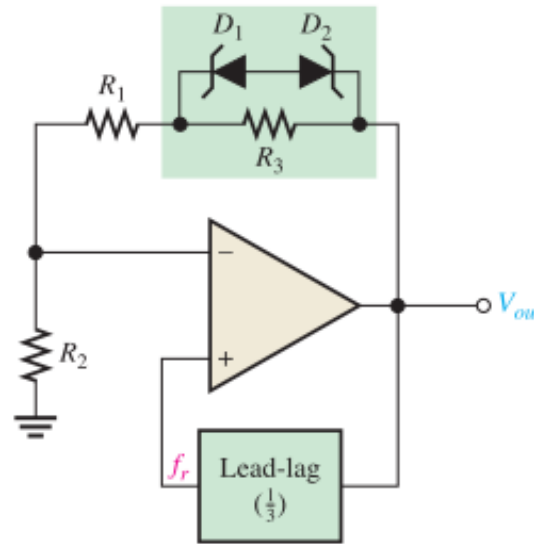
- The zener feedback is simple, it suffers from the nonlinearity of the zener diodes that occurs in order to control gain.
- A better method to control the gain uses a JFET as a voltage-controlled resistor in a negative feedback path.



◀ **FIGURE 16-10**
Self-starting Wien-bridge oscillator using back-to-back zener diodes.

The Phase-Shift Oscillator

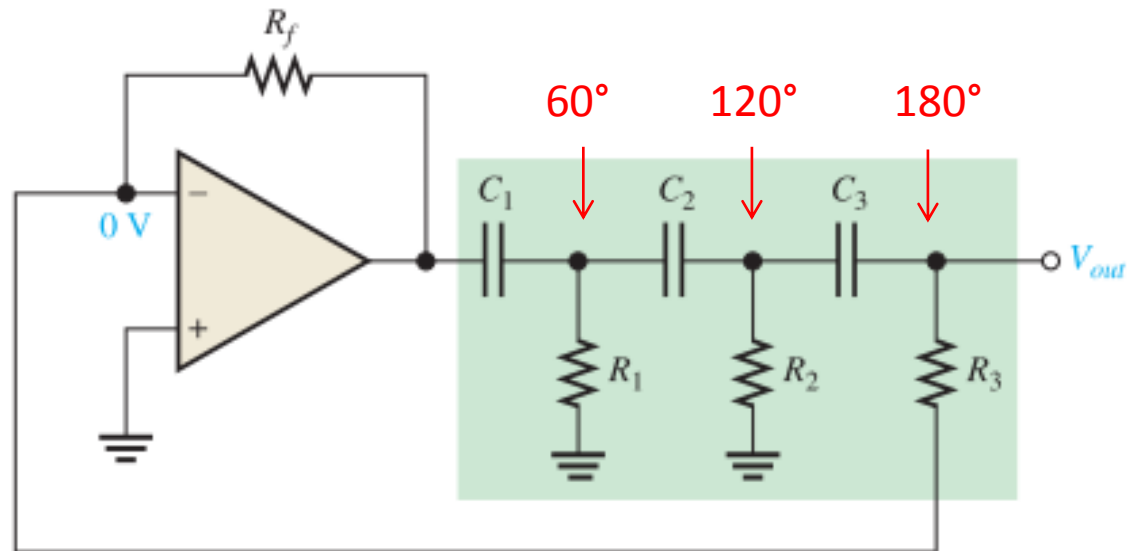
- Each of the three RC circuits in the feedback loop can provide a maximum phase shift approaching 90° .
- Oscillation occurs at the frequency where the total phase shift through the three RC circuits is 180° .
- The inversion of the op-amp itself provides the additional 180° to meet the requirement for oscillation of a 360° (or 0°) phase shift around the feedback loop.



$$B = \frac{1}{29} \quad \text{where } B = R_3/R_f$$

$$R_1 = R_2 = R_3 = R \text{ and } C_1 = C_2 = C_3 = C. \quad f_r = \frac{1}{2\pi\sqrt{6RC}}$$

The Phase-Shift Oscillator..

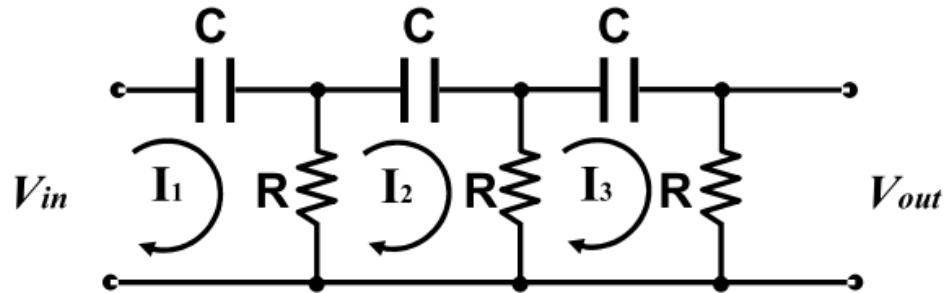

$$\left(R - \frac{j}{2\pi fC}\right)I_1 - RI_2 + 0I_3 = V_{in} \quad \dots(1)$$

$$-RI_1 + \left(2R - \frac{j}{2\pi fC}\right)I_2 - RI_3 = 0 \quad \dots(2)$$

$$0I_1 - RI_2 + \left(2R - \frac{j}{2\pi fC}\right)I_3 = 0 \quad \dots(3)$$

In order to get V_{out} , we must solve for I_3 using **determinates**.

$$\beta = \frac{V_{out}}{V_{in}} = \frac{RI_3}{V_{in}} = \frac{1}{\left(1 - \frac{j}{2\pi fRC}\right)\left(2 - \frac{j}{2\pi fRC}\right)^2 - \left(3 - \frac{2j}{2\pi fRC}\right)} \quad \dots(4)$$

The Phase-Shift Oscillator...

Combining the real terms and the imaginary terms separately.

$$\beta = \frac{V_{out}}{V_{in}} = \frac{1}{\left(1 - \frac{5}{(2\pi f)^2 R^2 C^2}\right) - j\left(\frac{6}{2\pi f RC} - \frac{1}{(2\pi f)^3 R^3 C^3}\right)} \dots\dots\dots(5)$$

In order to have a 180° phase shift through the network, the first term must be a negative number and the value of imaginary term must be equal **zero** at the frequency of oscillation f_o .

$$\therefore \frac{6}{2\pi f_o RC} - \frac{1}{(2\pi f_o)^3 R^3 C^3} = 0 \dots\dots(6)$$

Solving for f_o .

$$\boxed{f_o = \frac{1}{2\pi \sqrt{6} RC}} \dots\dots\dots(7)$$

The Phase-Shift Oscillator....

Since the imaginary terms is zero.

$$\frac{V_{out}}{V_{in}} = \frac{1}{\left(1 - \frac{5}{(2\pi f_o)^2 R^2 C^2}\right)} = \frac{-1}{29} = \beta \dots\dots\dots(8)$$


Thus the gain for the feedback network, $\beta = \frac{-1}{29}$

∴ The closed-loop gain of op.amp must be (≥ -29)

i.e. $A \geq -29$ and $A\beta = 1$.

Quadrature Oscillator

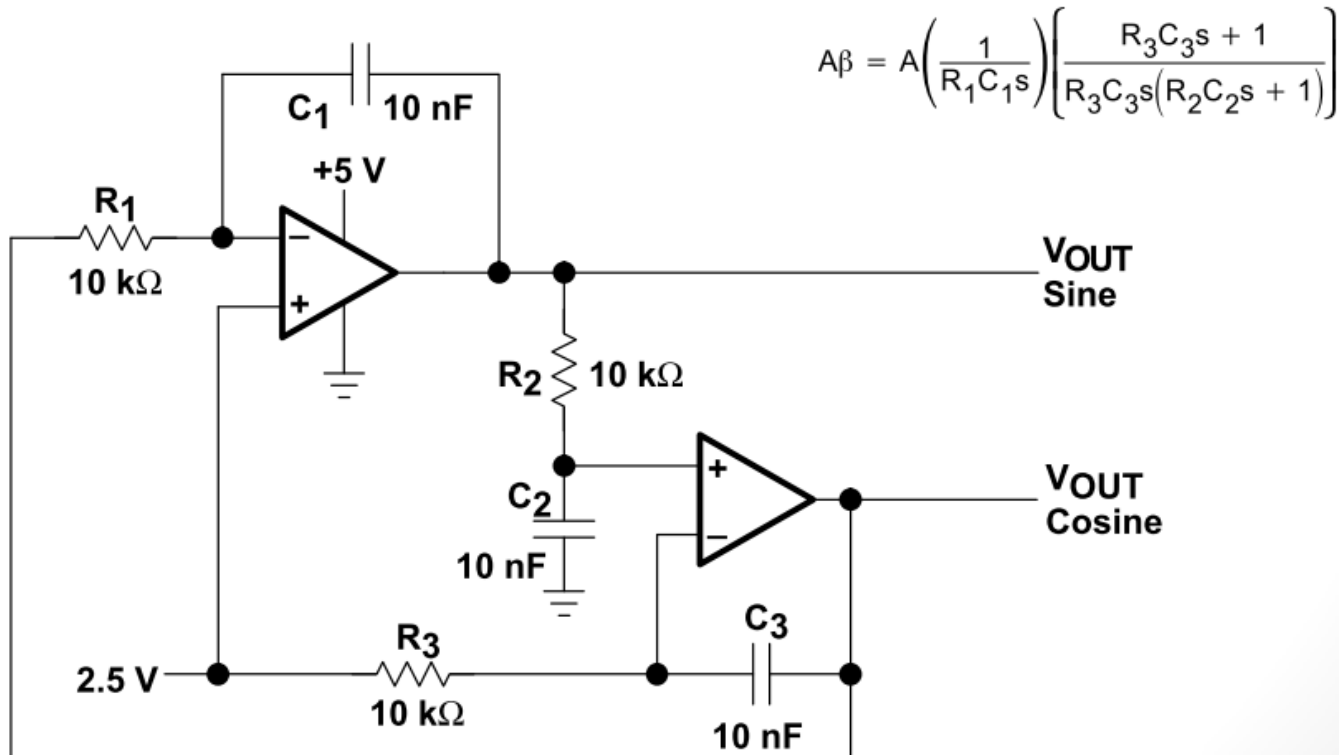- type of phase-shift oscillator, but the three RC sections are configured so each section contributes 90° of phase shift.
- This provides both sine and cosine waveform outputs (the outputs are quadrature, or 90° apart), which is a distinct advantage over other phase-shift oscillators.



- For more details, refer to:
 - Chapter 16 at T. Floyd, **Electronic Devices**, 9th edition.
 - ➔ • http://www.electronics-tutorials.ws/oscillator/rc_oscillator.html
 - <http://www.electronics-tutorials.ws/oscillator/oscillators.html>
- The lecture is available online at:
 - <http://bu.edu.eg/staff/ahmad.elbanna-courses/12884>
- For inquiries, send to:
 - ahmad.elbanna@feng.bu.edu.eg