



FACULTY OF ENGINEERING
DEPARTMENT OF ELECTRONICS AND COMMUNICATIONS

GEE336

Electronic Circuits II

Lecture #7

Active Filters

Instructor:

Dr. Ahmad El-Banna



Agenda

Basic Filter Responses

Filter Response Characteristics

Active LPF, HPF, BPF & BSF

Active Filters Based on Two-Integrators Loop

Active Filters Based Upon Inductor replacement

BASIC FILTER RESPONSES

Intro.


- **Filters** are circuits that are capable of **passing** signals with certain selected **frequencies** while **rejecting** signals with **other** frequencies.
- This property is called **selectivity**.
- **Active** filters use **transistors** or **op-amps** combined with passive RC, RL, or RLC circuits.

- The **passband** of a filter is the range of frequencies that are allowed to pass through the filter with **minimum attenuation**.
- The **critical frequency**, (also called the **cutoff frequency**) defines the **end of the passband** and is normally specified at the point where the response drops (**70.7%**) from the passband response.

- Following the passband is a region called the **transition region** that leads into a region called the **stopband**.
- There is **no precise point** between the transition region and the stopband.





Basic Filter Responses

- Ideal Response

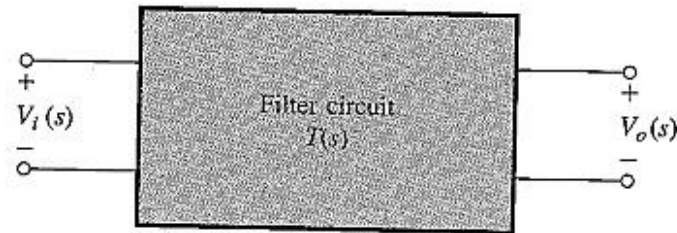

Filter transfer function

$$T(s) \equiv \frac{V_o(s)}{V_i(s)}$$

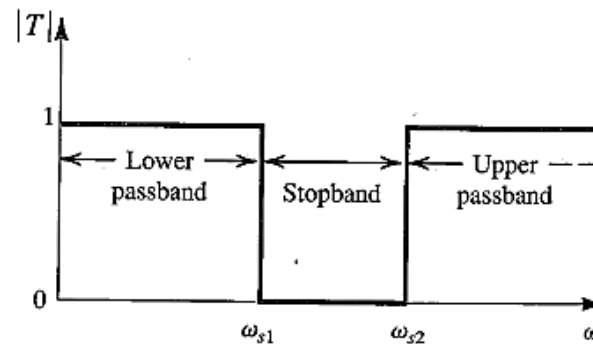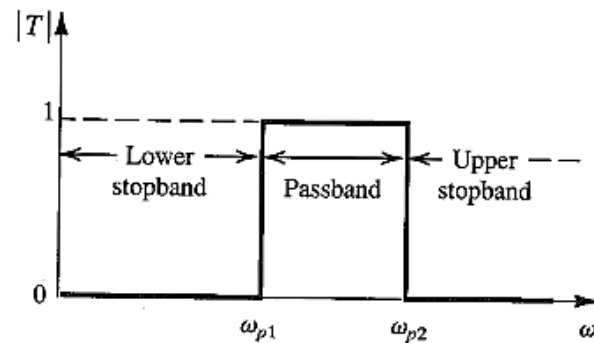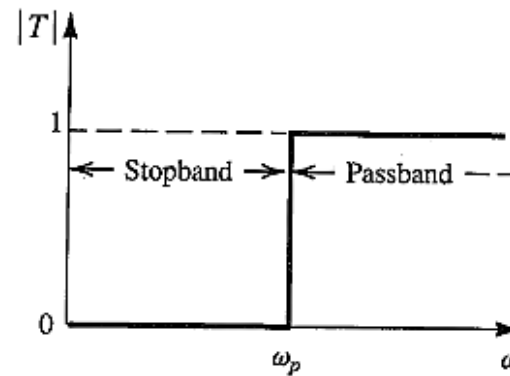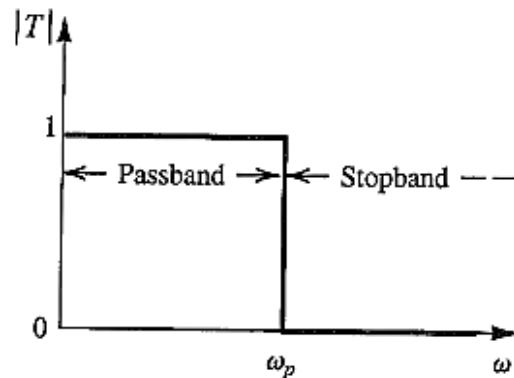


Basic Filter Responses


- Actual filter responses depend on the **number of poles**, a term used with filters to describe the **number of RC circuits** contained in the filter.
- The -20 dB/decade **roll-off** rate for the gain of a basic RC filter means that at a frequency of $10 f_c$, the output will be -20dB (10%) of the input.
- This roll-off rate is **not a good filter characteristic** because too much of the unwanted frequencies (beyond the passband) are allowed through the filter.

Basic Filter Responses

- Low-Pass Filter Response

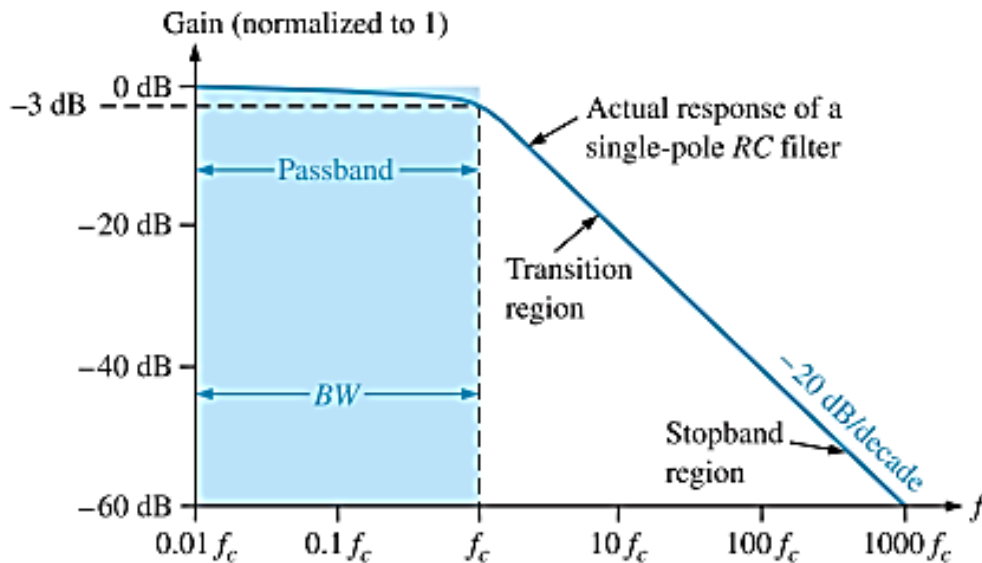

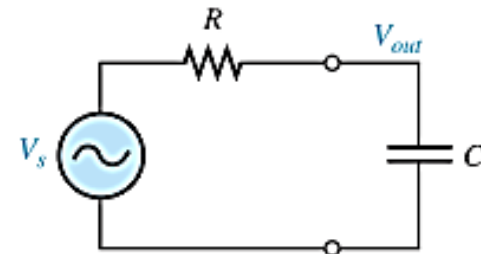(a) Comparison of an ideal low-pass filter response (blue area) with actual response. Although not shown on log scale, response extends down to $f_c = 0$.



(b) Basic low-pass circuit


$$BW = f_c$$

$$f_c = \frac{1}{2\pi RC}$$


$$T(s) = \frac{V_o(s)}{V_i(s)} = \frac{1/sC}{R + 1/sC} = \frac{1}{1 + sCR}$$

Basic Filter Responses..


- High-Pass Filter Response

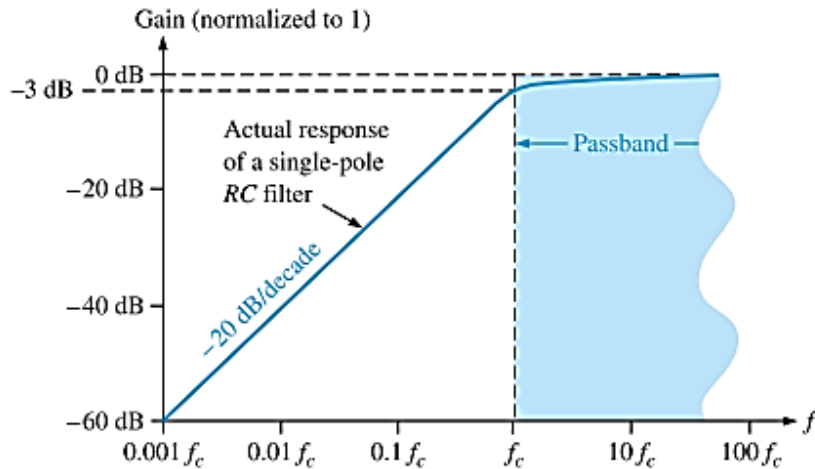

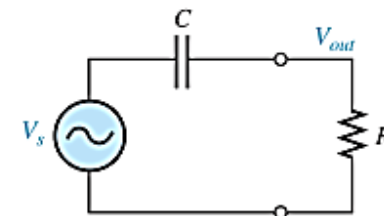(a) Comparison of an ideal high-pass filter response (blue area) with actual response



(b) Basic high-pass circuit

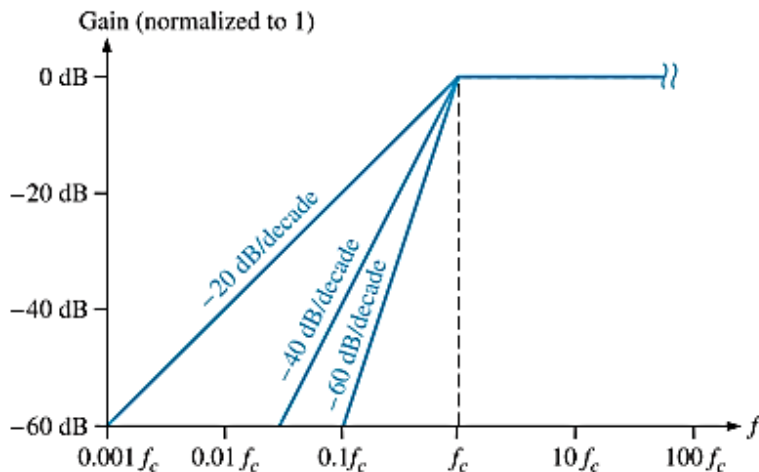


$$f_c = \frac{1}{2\pi RC}$$

Basic Filter Responses...

- **Band-Pass Filter Response**

$$BW = f_{c2} - f_{c1}$$

$$f_0 = \sqrt{f_{c1}f_{c2}}$$

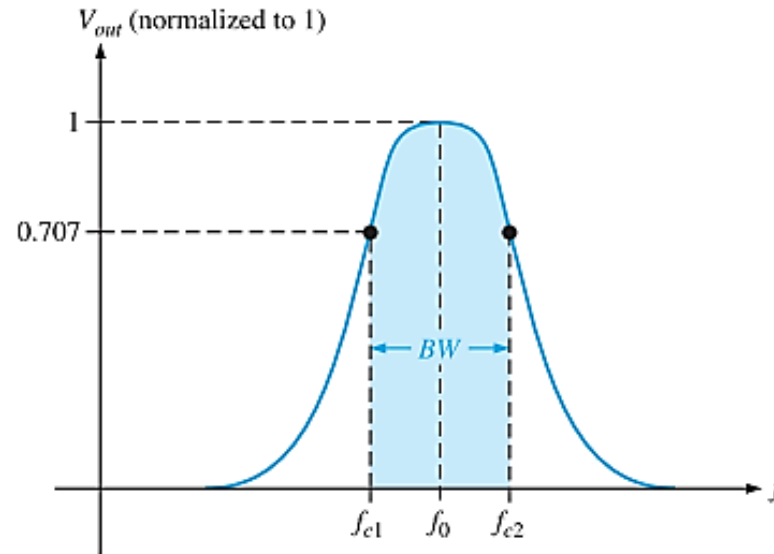


- The **quality factor** (Q) of a band-pass filter is the ratio of the center frequency to the bandwidth.
- The higher the value of Q , the narrower the bandwidth and the better the selectivity for a given value of f_0 .
- Band-pass filters are sometimes classified as **narrow-band** ($Q > 10$) or **wide-band** ($Q < 10$).

$$Q = \frac{f_0}{BW}$$

Basic Filter Responses....

- **Band-Stop Filter Response**

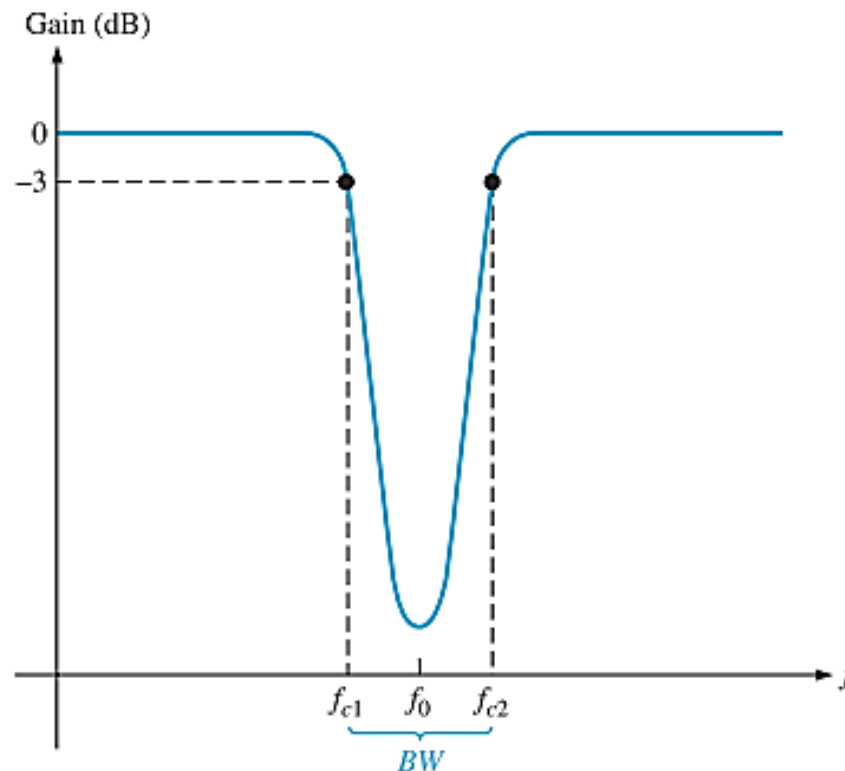
also known as notch, band-reject, or band-elimination filter.



FILTER RESPONSE CHARACTERISTICS

FILTER RESPONSE CHARACTERISTICS

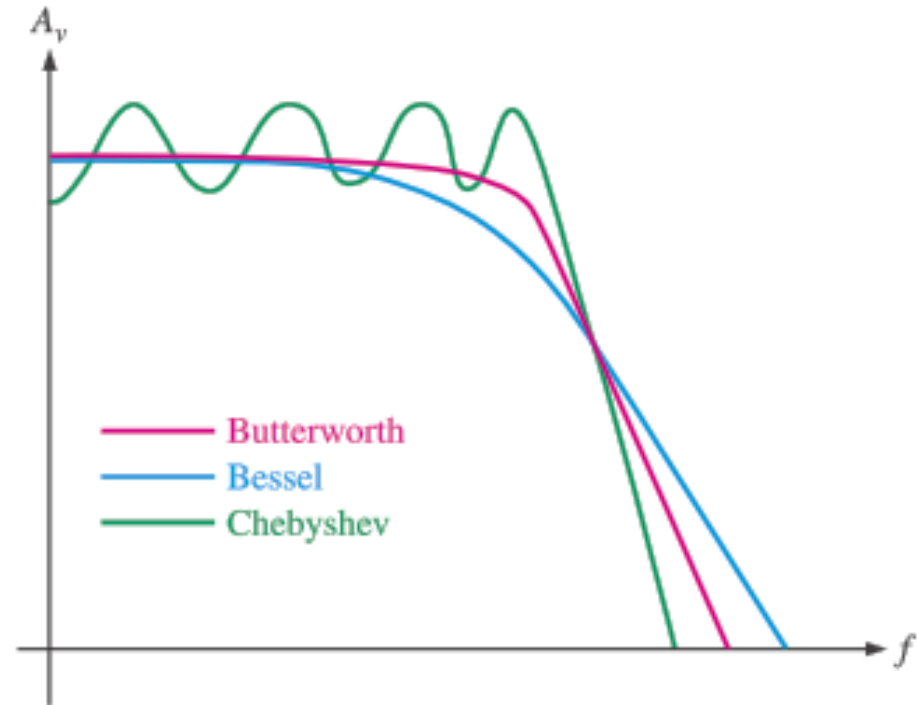- Each type of filter response (low-pass, high-pass, band-pass, or band-stop) can be tailored by **circuit component values** to have either a
 - **Butterworth**,
 - **Chebyshev**, or
 - **Bessel** characteristic.
- Each of these characteristics is identified by the **shape of the response curve**, and each has an advantage in certain applications.



The Butterworth Characteristic

- The Butterworth characteristic provides a **very flat amplitude response** in the passband and a roll-off rate of -20 dB/decade/pole.
- The **phase response is not linear**, and the phase shift (thus, time delay) of signals passing through the filter varies nonlinearly with frequency.
- Therefore, a **pulse** applied to a Butterworth filter will **cause overshoots** on the output because each frequency component of the pulse's rising and falling edges experiences a different time delay.

FILTER RESPONSE CHARACTERISTICS..

The Chebyshev Characteristic


- Filters with the Chebyshev response characteristic are useful when a **rapid roll-off** is required because it provides a roll-off rate greater than -20 dB/decade/pole.
- This is a **greater rate** than that of the Butterworth, so filters can be implemented with the Chebyshev response with **fewer poles** and **less complex** circuitry for a given roll-off rate.
- This type of filter response is characterized by overshoot or **ripples in the passband** (depending on the number of poles) and an even **less linear phase response** than the Butterworth.

The Bessel Characteristic

- The Bessel response exhibits a **linear phase characteristic**, meaning that the phase shift increases linearly with frequency.
- The result is almost **no overshoot on the output** with a pulse input.
- It has the **slowest roll-off** rate.


Critical Frequency and Roll-Off Rate

$$f_c = \frac{1}{2\pi RC}$$

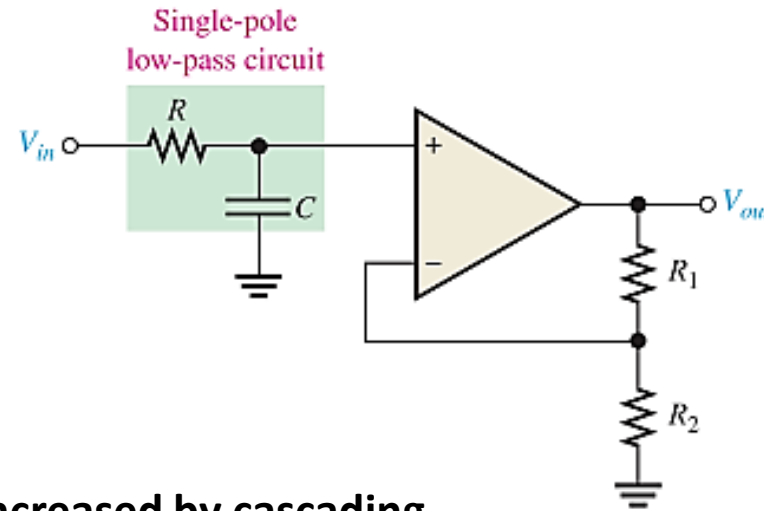

- The number of filter **poles** can be **increased by cascading**.

Example: Third-order (three-pole) filter

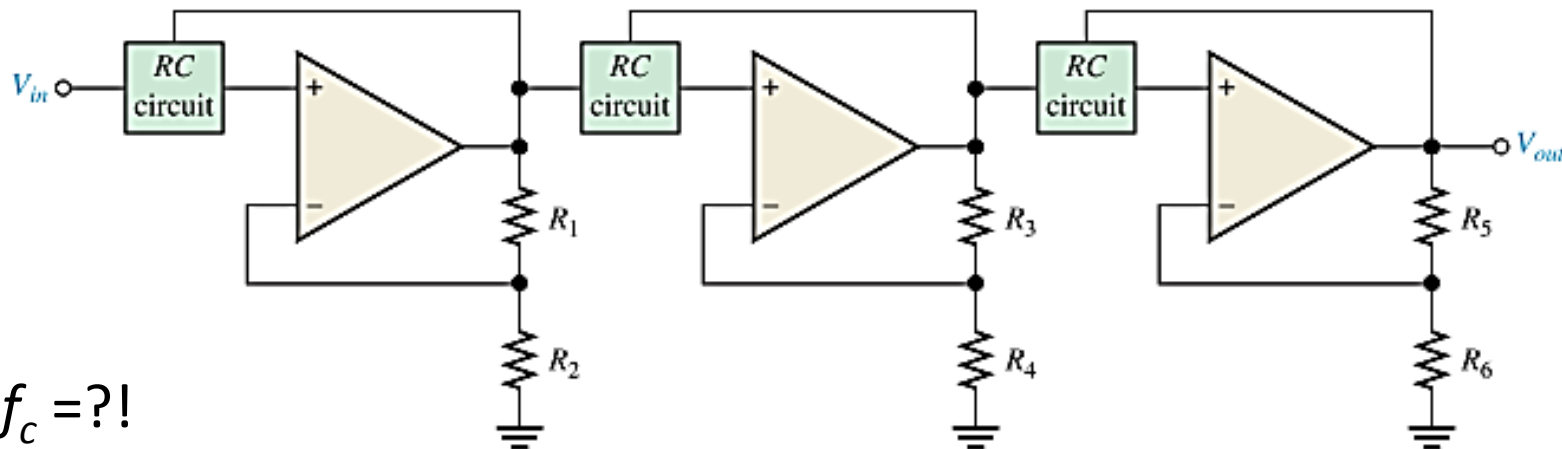



$f_c = ?!$

ACTIVE LOW-PASS FILTERS

Advantages of Op-Amp Active Filters

- Filters that use **op-amps** as the **active element** provide several **advantages** over passive filters (R, L, and C elements only).
 - The op-amp provides **gain**, so the **signal is not attenuated** as it passes through the filter.
 - The high input impedance of the op-amp **prevents excessive loading of the driving source**.
 - The low output impedance of the op-amp **prevents the filter from being affected by the load** that it is driving.
 - Active filters are also **easy to adjust over a wide frequency range** without altering the desired response.

Single-Pole LPF

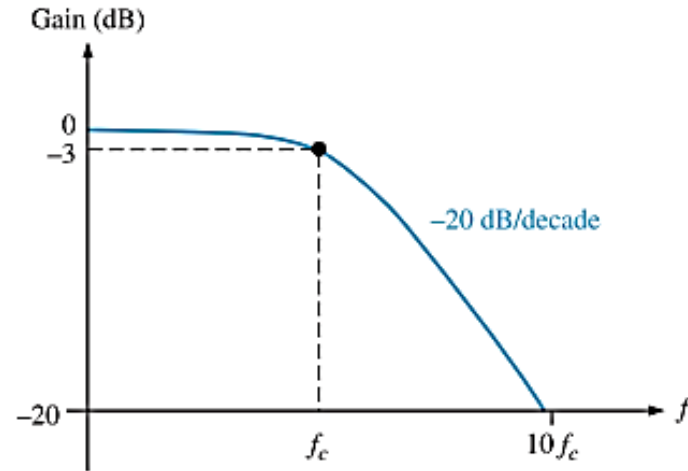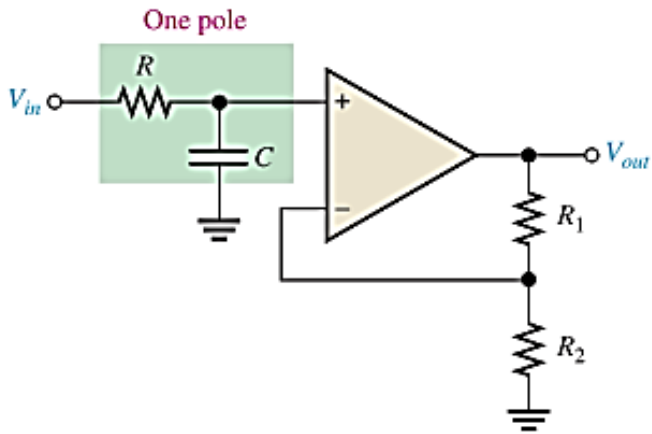


$$A_{cl(NI)} = \frac{R_1}{R_2} + 1$$

$$f_c = \frac{1}{2\pi RC}$$

2-Pole LPF

The Sallen-Key LPF (2nd Order)

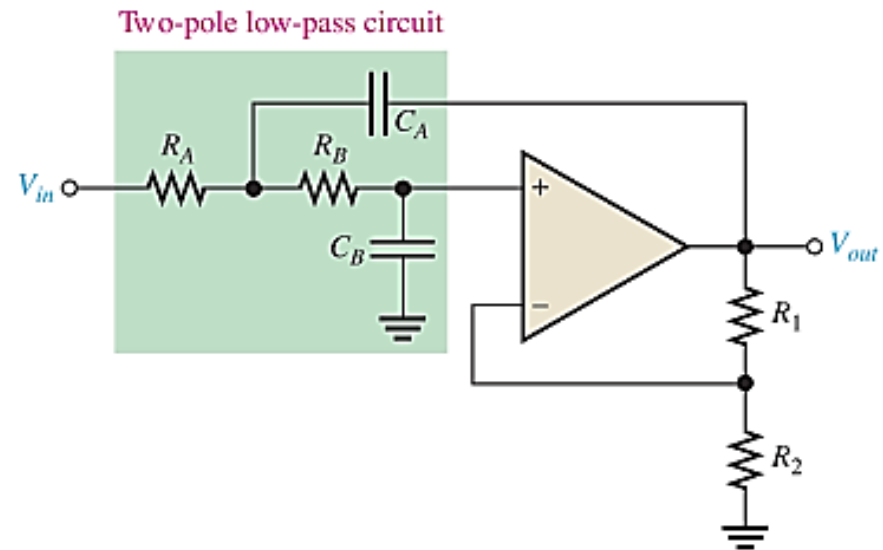- It is used to provide **very high Q factor and passband gain without the use of inductors.**
- It is also known as a **VCVS** (voltage-controlled voltage source) filter.




$$f_c = \frac{1}{2\pi \sqrt{R_A R_B C_A C_B}}$$

$$f_c = \frac{1}{2\pi RC} \quad @ \quad R_A = R_B = R \text{ and } C_A = C_B = C.$$

Assignment:
Derive the f_c equation.


Cascaded LPF

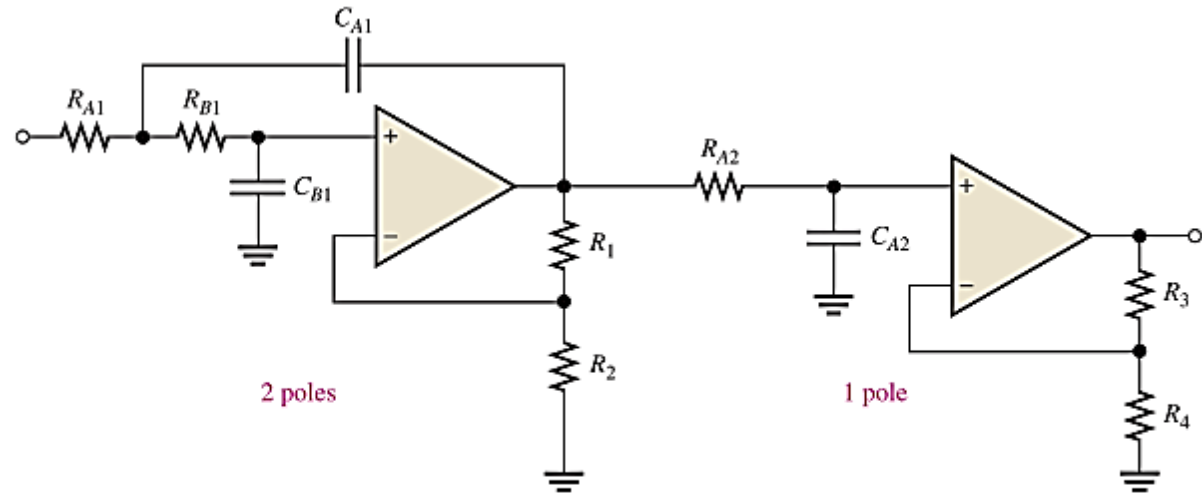- A **three-pole** filter is required to get a **third-order** low-pass response.



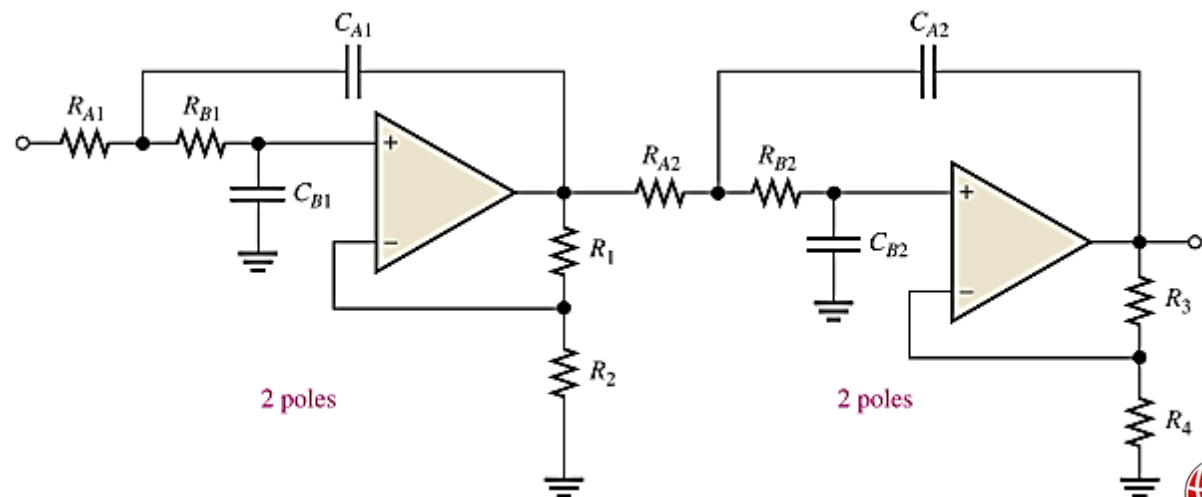(a) Third-order configuration

- A **four-pole** filter is **preferred** because it uses the same number of op-amps to achieve a faster roll-off.





(b) Fourth-order configuration


In high-pass filters, the roles of the capacitor and resistor are reversed in the RC circuits.

ACTIVE HIGH-PASS FILTERS


Single Pole HPF

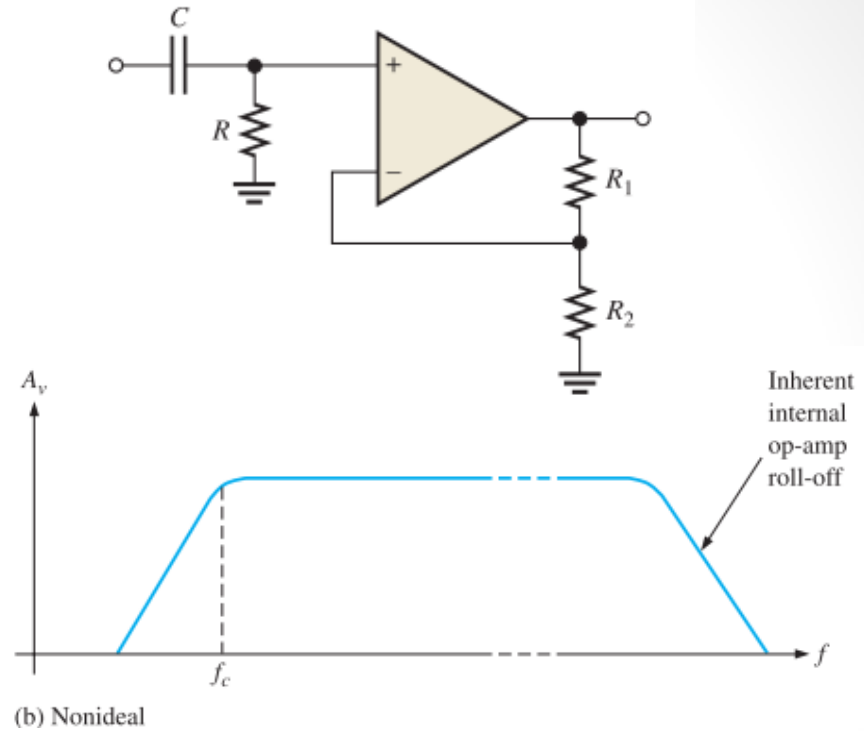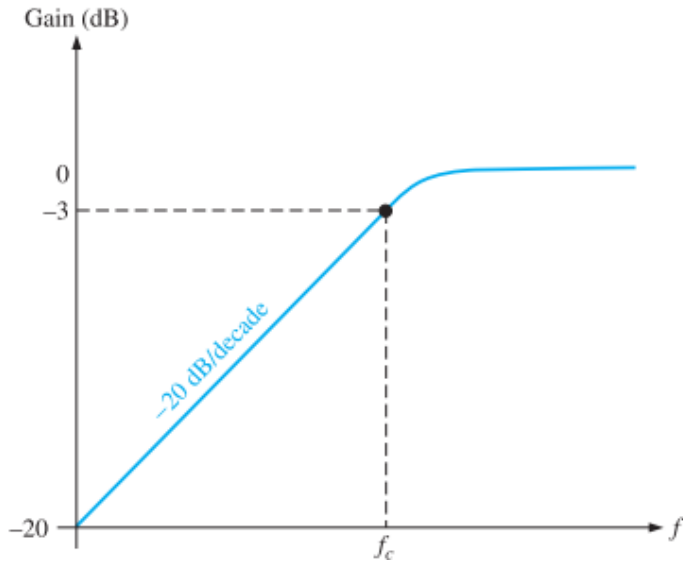

Sallen-Key HPF

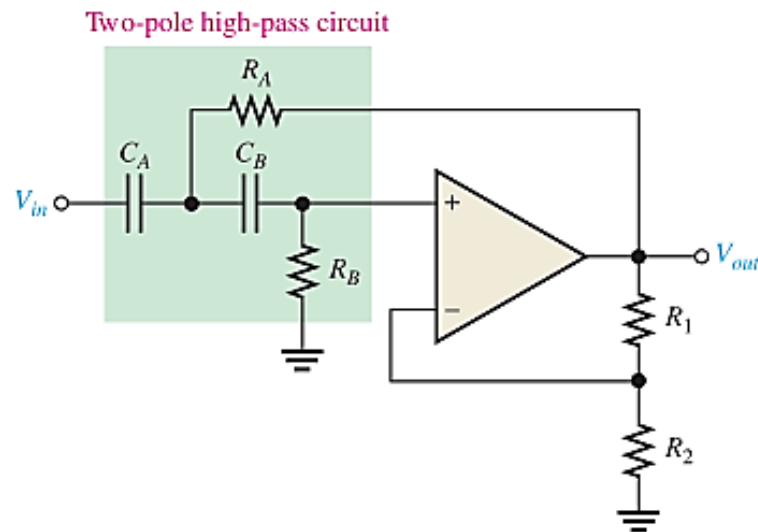


Cascaded HPF

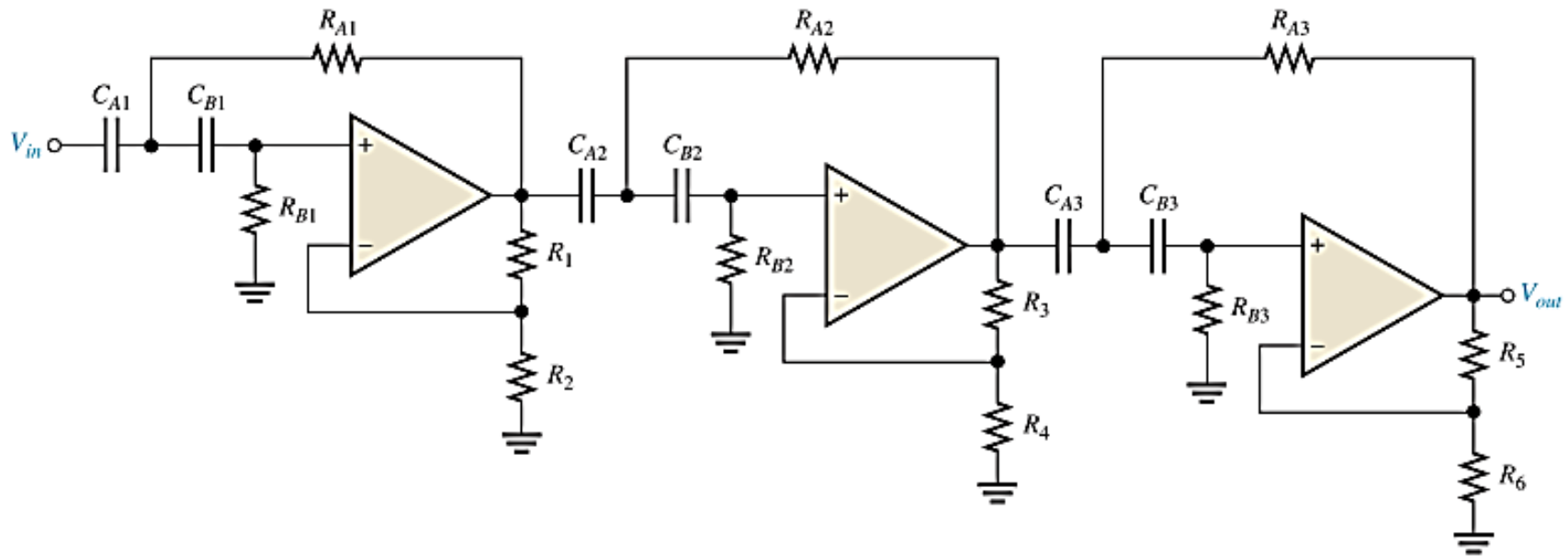

Order = ?
roll-off = ?

ACTIVE BAND-PASS FILTERS

Cascaded Low-Pass and High-Pass Filters

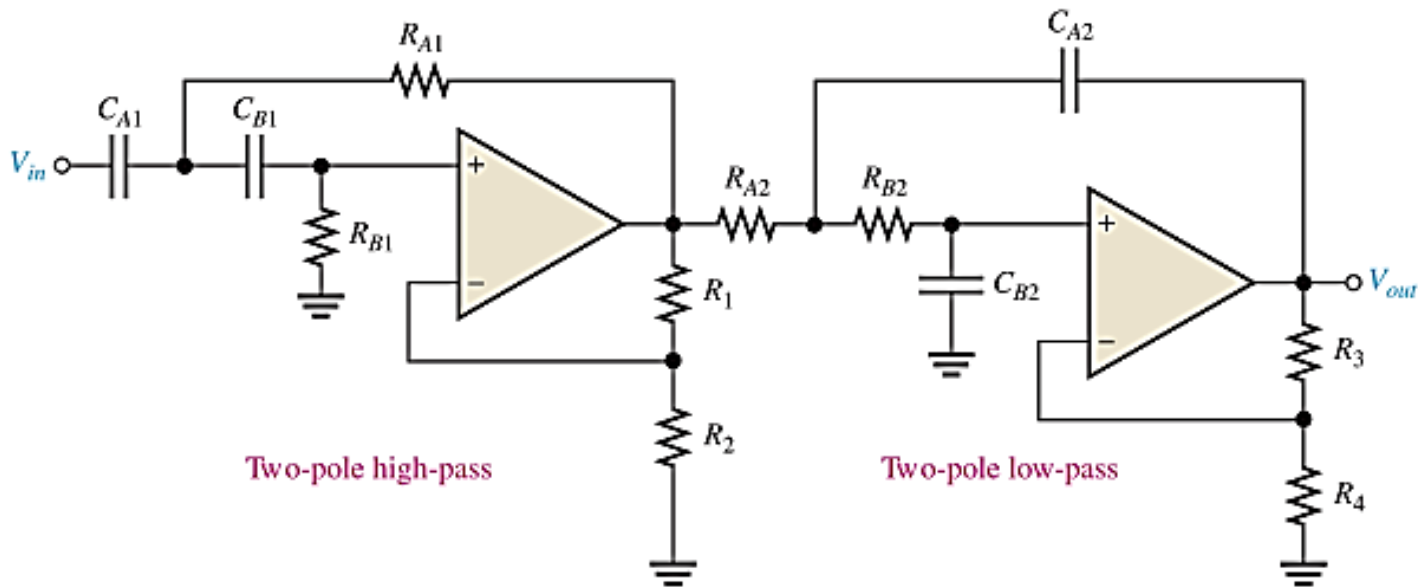


$$f_{c1} = \frac{1}{2\pi \sqrt{R_{A1}R_{B1}C_{A1}C_{B1}}}$$

$$f_{c2} = \frac{1}{2\pi \sqrt{R_{A2}R_{B2}C_{A2}C_{B2}}}$$

$$f_0 = \sqrt{f_{c1}f_{c2}}$$

If equal components,

$$f_c = 1/(2\pi RC).$$

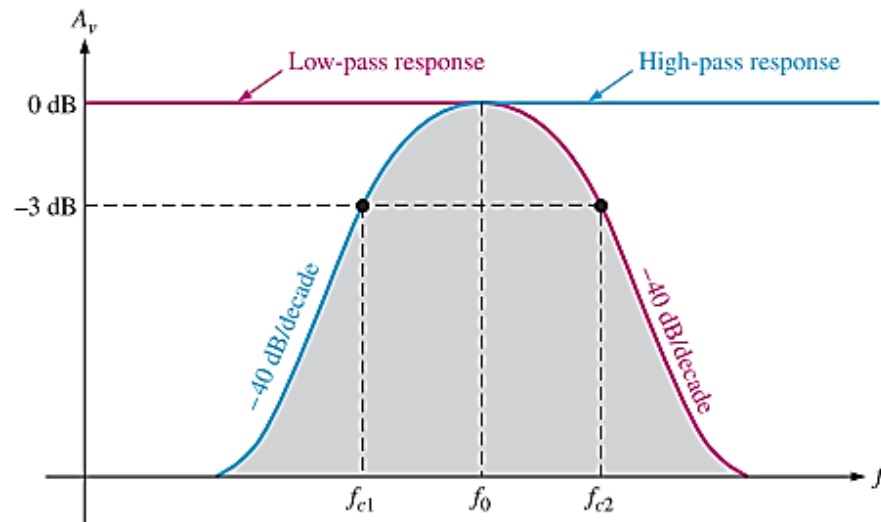

ACTIVE FILTERS BASED ON TWO- INTEGRATORS LOOP

Biquad Filter

(Two-Integrators Loop biquadratic circuit)

- "Biquad" is an abbreviation of "**biquadratic**", which refers to the fact that its **transfer function** is the ratio of two quadratic functions.
- To derive the biquad circuit, consider the 2nd order high pass transfer function

$$\frac{V_{\text{hp}}}{V_i} = \frac{Ks^2}{s^2 + s(\omega_0/Q) + \omega_0^2}$$

Cross multiply and reform,


$$V_{\text{hp}} + \frac{1}{Q}\left(\frac{\omega_0}{s}V_{\text{hp}}\right) + \left(\frac{\omega_0^2}{s^2}V_{\text{hp}}\right) = KV_i$$

$$V_{\text{hp}} = KV_i - \frac{1}{Q}\frac{\omega_0}{s}V_{\text{hp}} - \frac{\omega_0^2}{s^2}V_{\text{hp}}$$

Biquad Filter ..


- Derivation of a block diagram realization of the two-integrator loop biquad
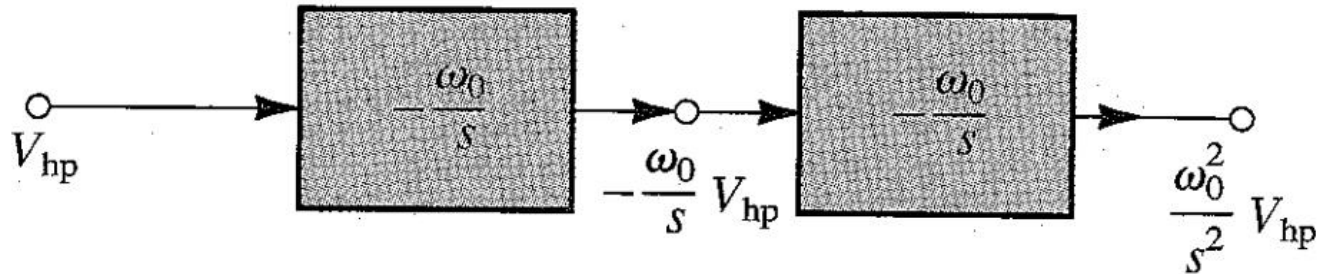
$$V_{hp} + \frac{1}{Q} \left(\frac{\omega_0}{s} V_{hp} \right) + \left(\frac{\omega_0^2}{s^2} V_{hp} \right) = K V_i$$



(a)
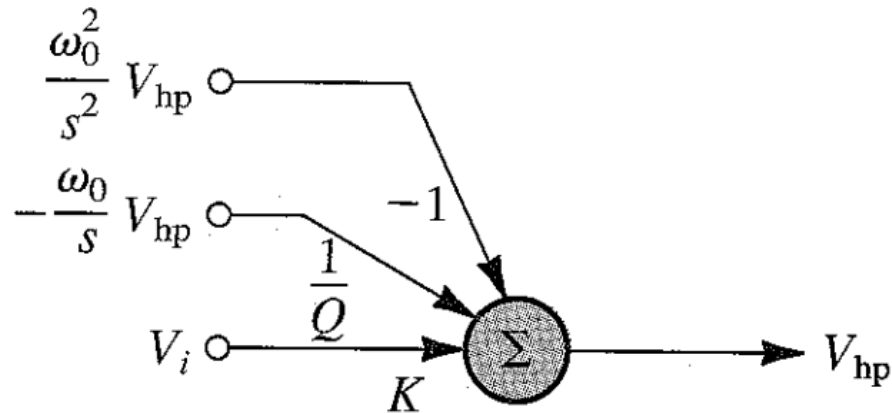
$$V_{hp} = K V_i - \frac{1}{Q} \frac{\omega_0}{s} V_{hp} - \frac{\omega_0^2}{s^2} V_{hp}$$



(b)

Biquad Filter ...

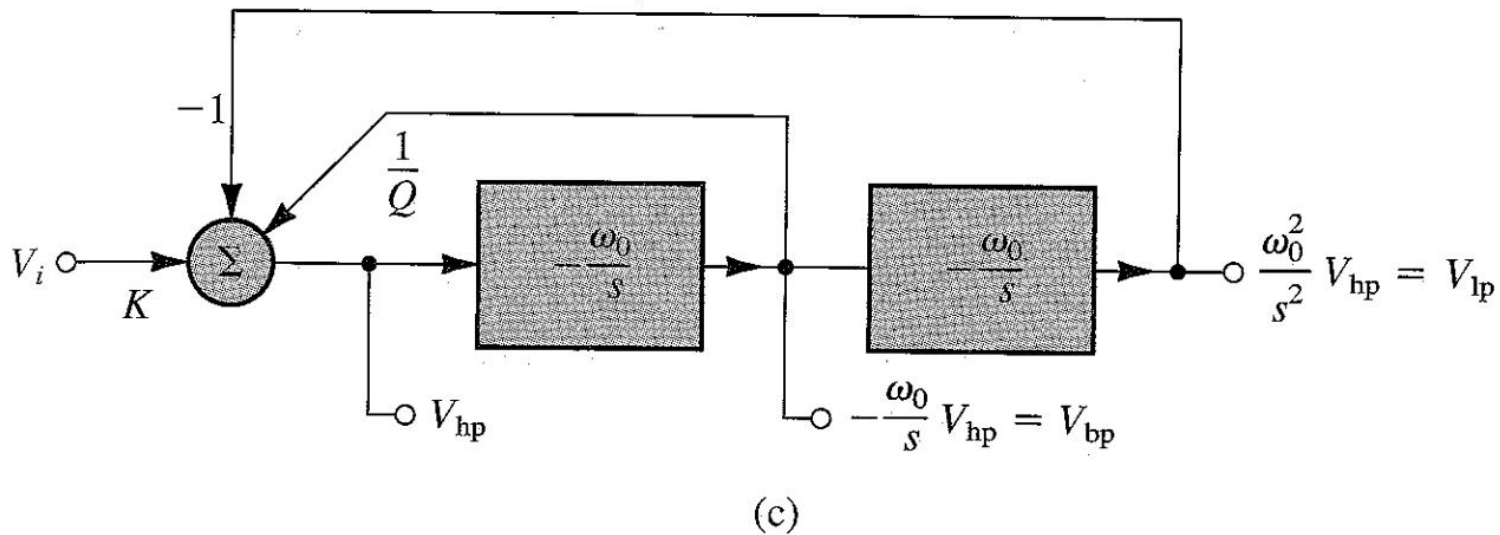


FIGURE 12.23 Derivation of a block diagram realization of the two-integrator-loop biquad.


$$V_{hp} = KV_i - \frac{1}{Q} \frac{\omega_0}{s} V_{hp} - \frac{\omega_0^2}{s^2} V_{hp}$$

$$\frac{(-\omega_0/s)V_{hp}}{V_i} = -\frac{K\omega_0 s}{s^2 + s(\omega_0/Q) + \omega_0^2} = T_{bp}(s)$$

$$\frac{(\omega_0^2/s^2)V_{hp}}{V_i} = \frac{K\omega_0^2}{s^2 + s(\omega_0/Q) + \omega_0^2} = T_{lp}(s)$$

Biquad Filter

(Universal Circuit)

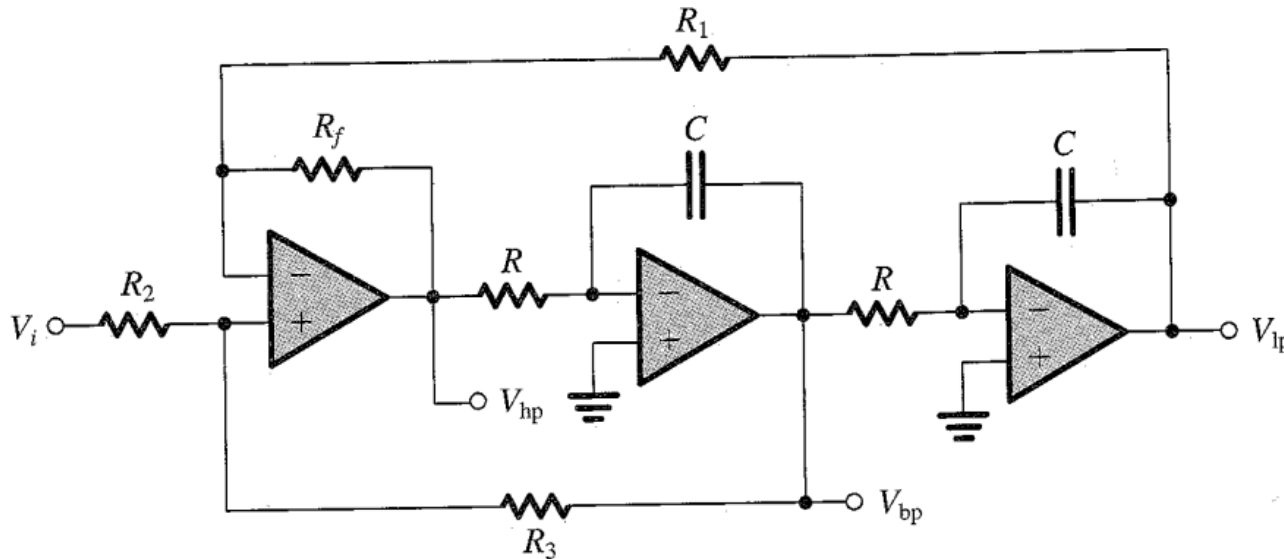

$$V_{hp} = \frac{R_3}{R_2 + R_3} \left(1 + \frac{R_f}{R_1} \right) V_i + \frac{R_2}{R_2 + R_3} \left(1 + \frac{R_f}{R_1} \right) \left(-\frac{\omega_0}{s} V_{hp} \right) - \frac{R_f}{R_1} \left(\frac{\omega_0^2}{s^2} V_{hp} \right)$$


$$R_f/R_1 = 1$$

$$R_3/R_2 = 2Q - 1$$

$$K = 2 - (1/Q)$$

Biquad Filter

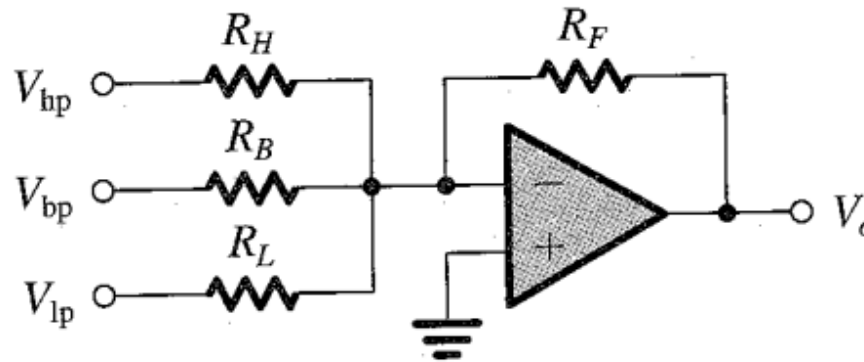- To obtain notch and all-pass function, the three outputs of the biquad are summed with appropriate weights




$$\frac{V_o}{V_i} = -K \frac{(R_F/R_H)s^2 - s(R_F/R_B)\omega_0 + (R_F/R_L)\omega_0^2}{s^2 + s(\omega_0/Q) + \omega_0^2}$$

Notch filter as example, use

$$R_B = \infty \quad \frac{R_H}{R_L} = \left(\frac{\omega_n}{\omega_0}\right)^2$$


ACTIVE FILTERS BASED UPON INDUCTOR REPLACEMENT

2nd order LCR Resonator

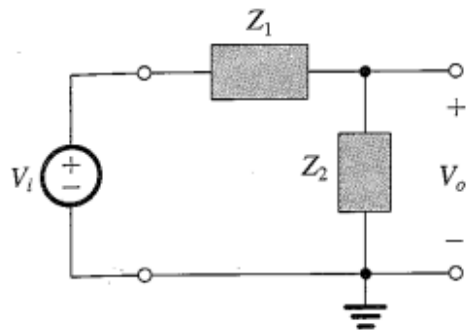

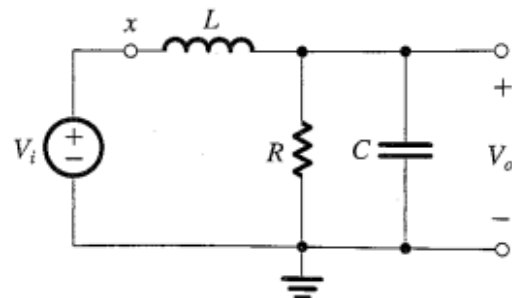
(a) General structure

$$T(s) = \frac{V_o(s)}{V_i(s)} = \frac{Z_2(s)}{Z_1(s) + Z_2(s)}$$



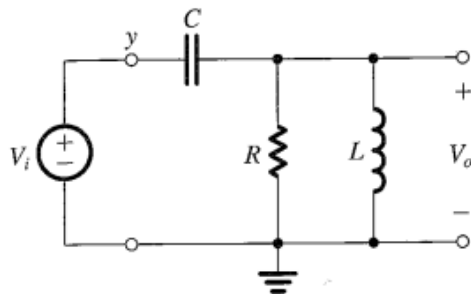(b) LP

$$\begin{aligned} T(s) &\equiv \frac{V_o}{V_i} = \frac{Z_2}{Z_1 + Z_2} = \frac{Y_1}{Y_1 + Y_2} = \frac{1/sL}{(1/sL) + sC + (1/R)} \\ &= \frac{1/LC}{s^2 + s(1/CR) + (1/LC)} \end{aligned}$$




(c) HP

$$T(s) \equiv \frac{V_o}{V_i} = \frac{a_2 s^2}{s^2 + s(\omega_0/Q) + \omega_0^2}$$

2nd order Active Filter based on inductor replacement

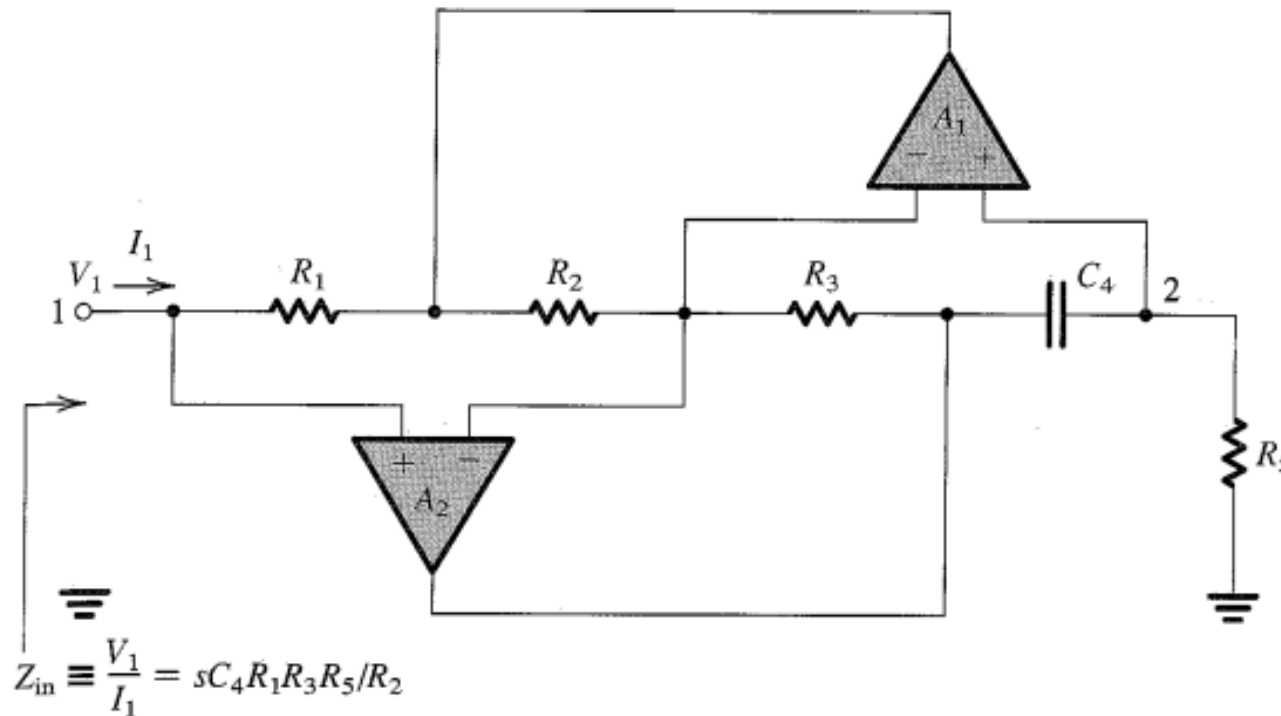The Antoniou Inductance-Simulation Circuit



$$L = C_4R_1R_3R_5/R_2$$

(a) selecting $R_1 = R_2 = R_3 = R_5 = R$ and $C_4 = C$,

$$L = CR^2$$

2nd order Active Filter based on inductor replacement ..

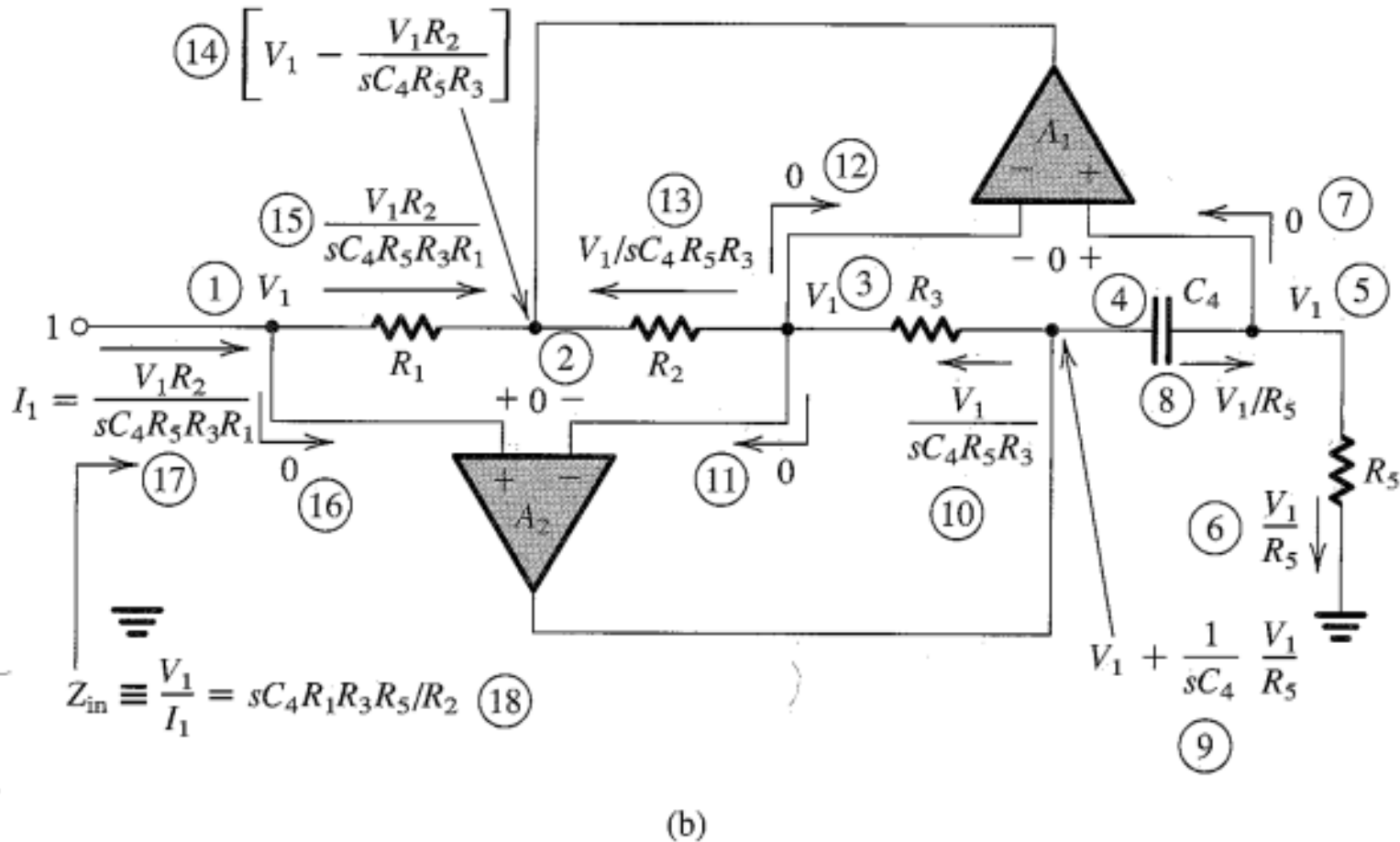


FIGURE 12.20 (a) The Antoniou inductance-simulation circuit. (b) Analysis of the circuit assuming ideal op amps. The order of the analysis steps is indicated by the circled numbers.

2nd order Active Filter based on inductor replacement ...

The Op Amp-RC Resonator




$$\omega_0 = 1/\sqrt{LC_6} = 1/\sqrt{C_4 C_6 R_1 R_3 R_5 / R_2}$$

$$Q = \omega_0 C_6 R_6 = R_6 \sqrt{\frac{C_6}{C_4} \frac{R_2}{R_1 R_3 R_5}}$$

$$C_4 = C_6 = C \text{ and } R_1 = R_2 = R_3 = R_5 = R$$

$$\omega_0 = 1/CR$$


$$Q = R_6/R$$

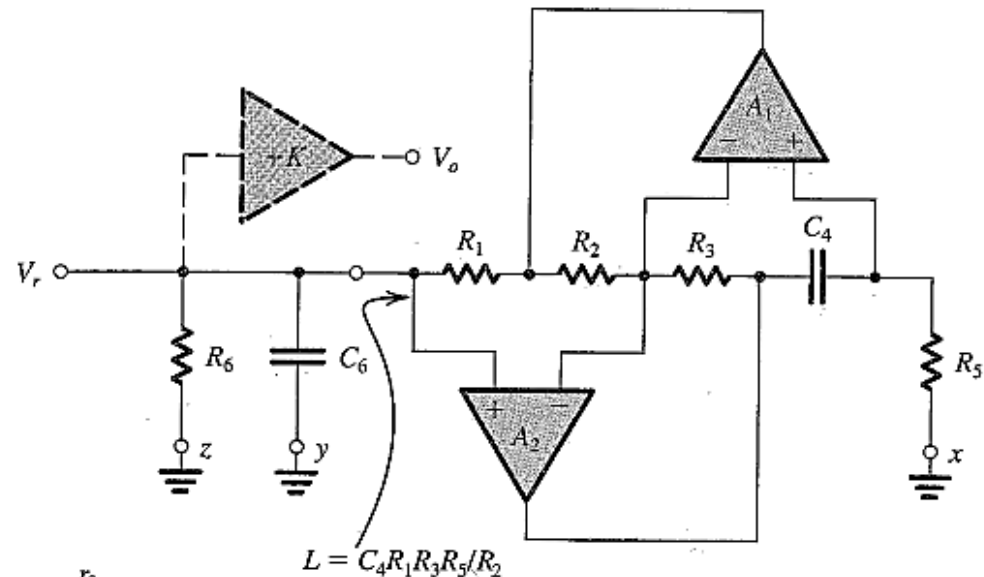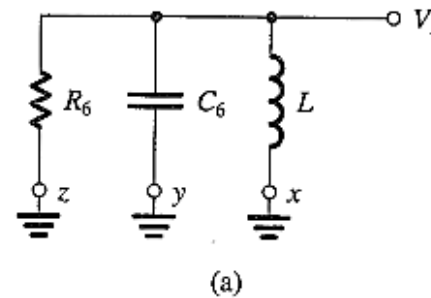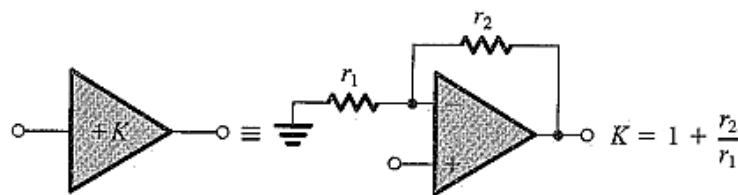

$$L = C_4 R_1 R_3 R_5 / R_2$$

LPF

with inductor replacement circuit

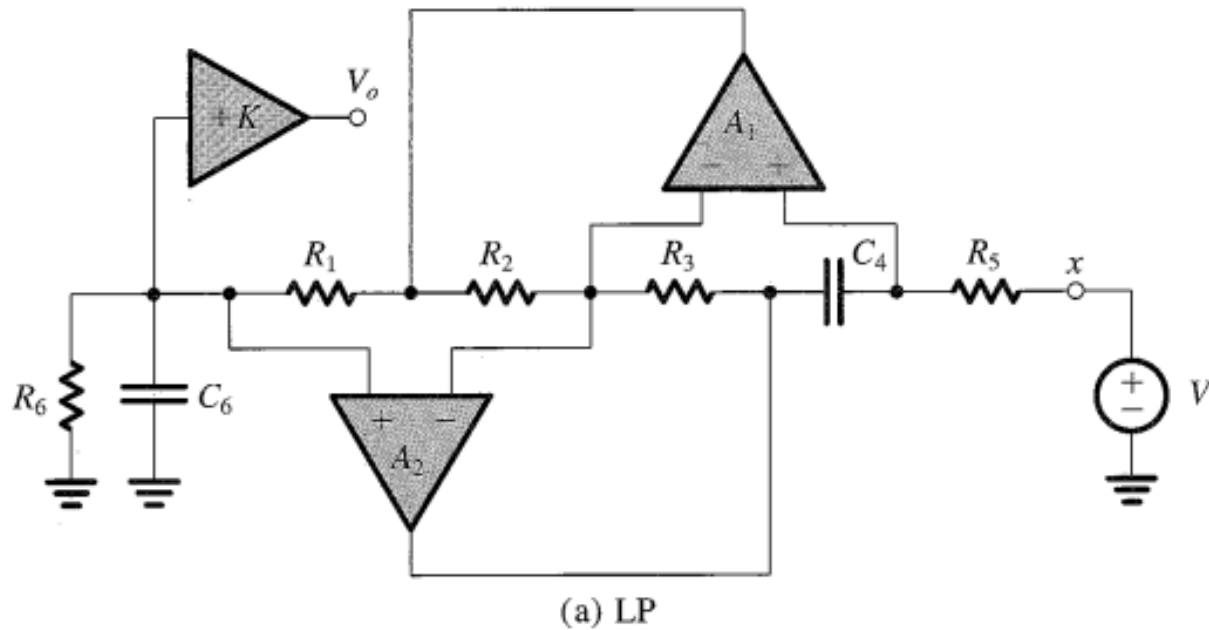

$$T(s) = \frac{KR_2/C_4C_6R_1R_3R_5}{s^2 + s\frac{1}{C_6R_6} + \frac{R_2}{C_4C_6R_1R_3R_5}}$$


$K = \text{DC gain}$

$$\omega_0 = 1/\sqrt{LC_6} = 1/\sqrt{C_4C_6R_1R_3R_5/R_2}$$


$$Q = \omega_0 C_6 R_6 = R_6 \sqrt{\frac{C_6}{C_4} \frac{R_2}{R_1 R_3 R_5}}$$

ACTIVE BAND-STOP FILTERS

Multiple-Feedback Band-Stop Filter

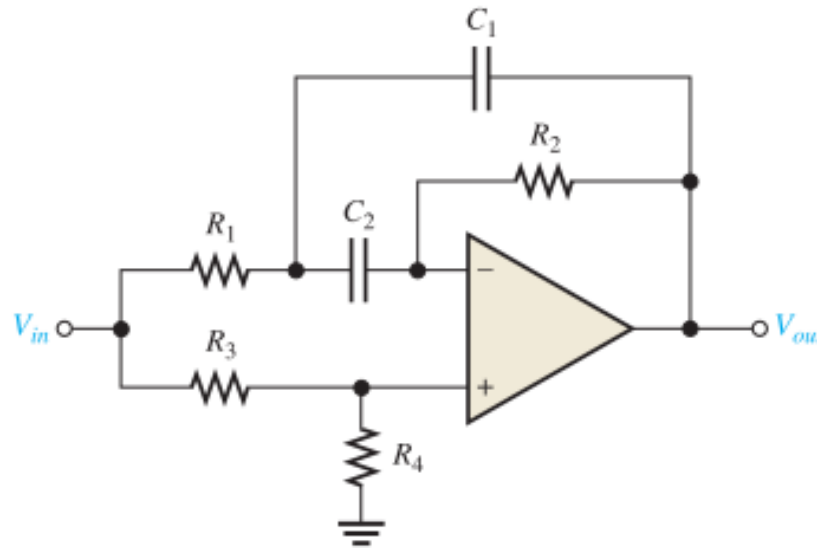

State-Variable Band-Stop Filter

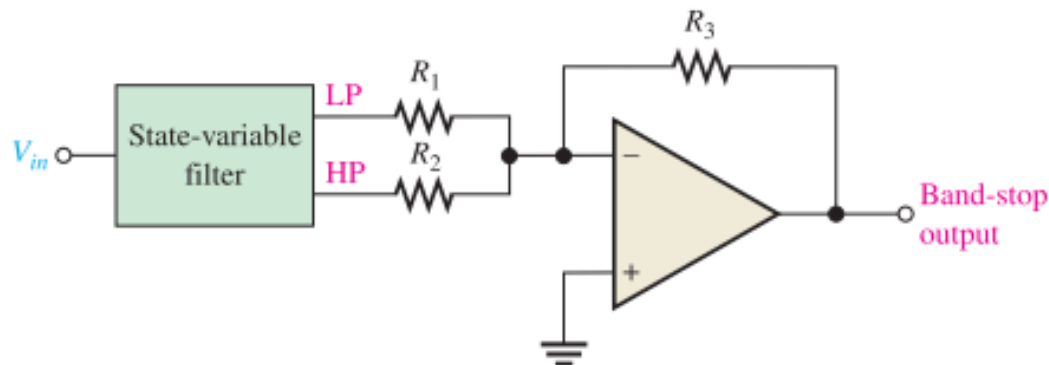

- For more details, refer to:
 - Chapter 15 at T. Floyd, **Electronic Devices**, 9th edition.
 - Chapter 12 at Sedra & Smith, **Microelectronic Circuits**, 5th edition.
- The lecture is available online at:
 - <http://bu.edu.eg/staff/ahmad.elbanna-courses/12884>
- For inquiries, send to:
 - ahmad.elbanna@feng.bu.edu.eg