



FACULTY OF ENGINEERING  
DEPARTMENT OF ELECTRONICS AND COMMUNICATIONS

**GEE336**

**Electronic Circuits II**

Lecture #8

Multivibrators

**Instructor:**

**Dr. Ahmad El-Banna**



# Agenda



## Introduction

- Monostable, bistable & Astable

## Using 555 Timer

## Using Op-AMP

# INTRODUCTION

# Multivibrators types


- Monostable
- Bistable
- Astable

# Multivibrators types..


Input

Output


(No input signal)

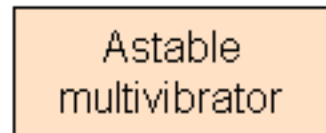



(a)

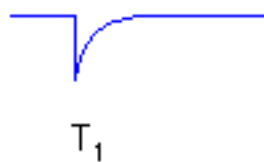

$T_1$

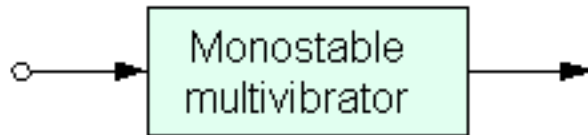


(b)

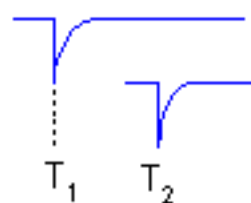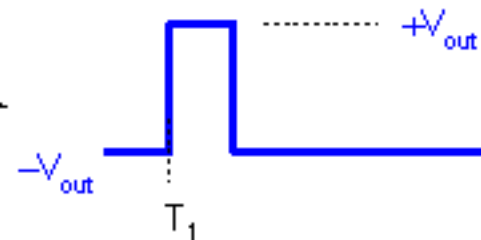


$T_1$

$T_2$

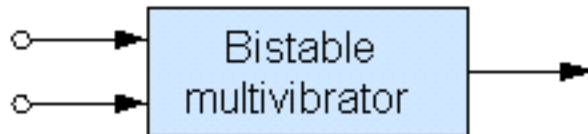


(c)

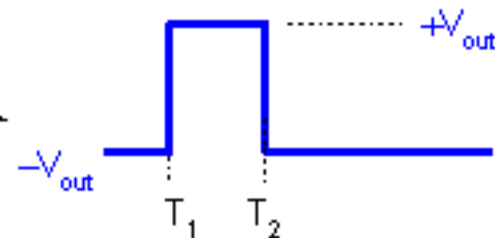

# MULTIVIBRATORS USING 555 TIMER


# 555 timer

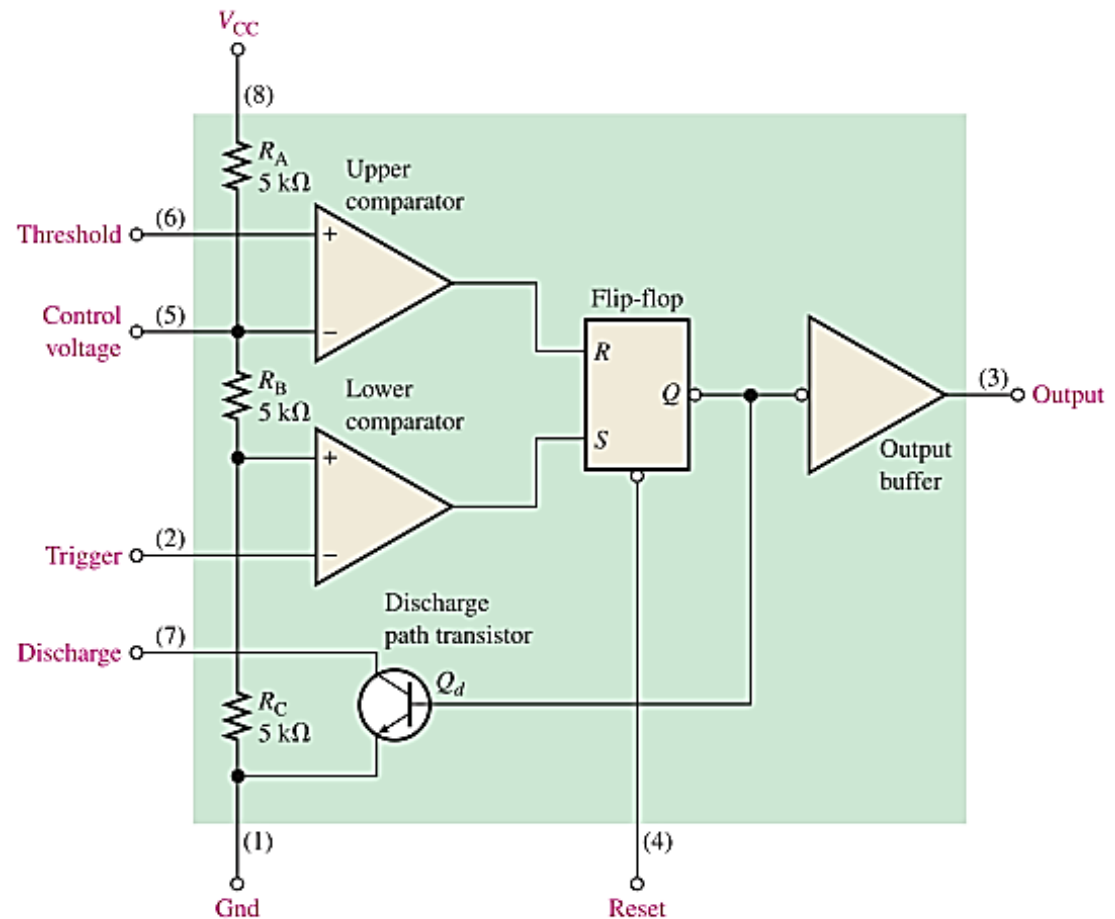

- The 555 timer consists basically of two comparators, a flip-flop, a discharge transistor, and a resistive voltage divider.
- The flip-flop (bistable multivibrator) is a digital device, a two-state device whose output can be at either a high voltage level (set, S) or a low voltage level (reset, R). The state of the output can be changed with proper input signals.

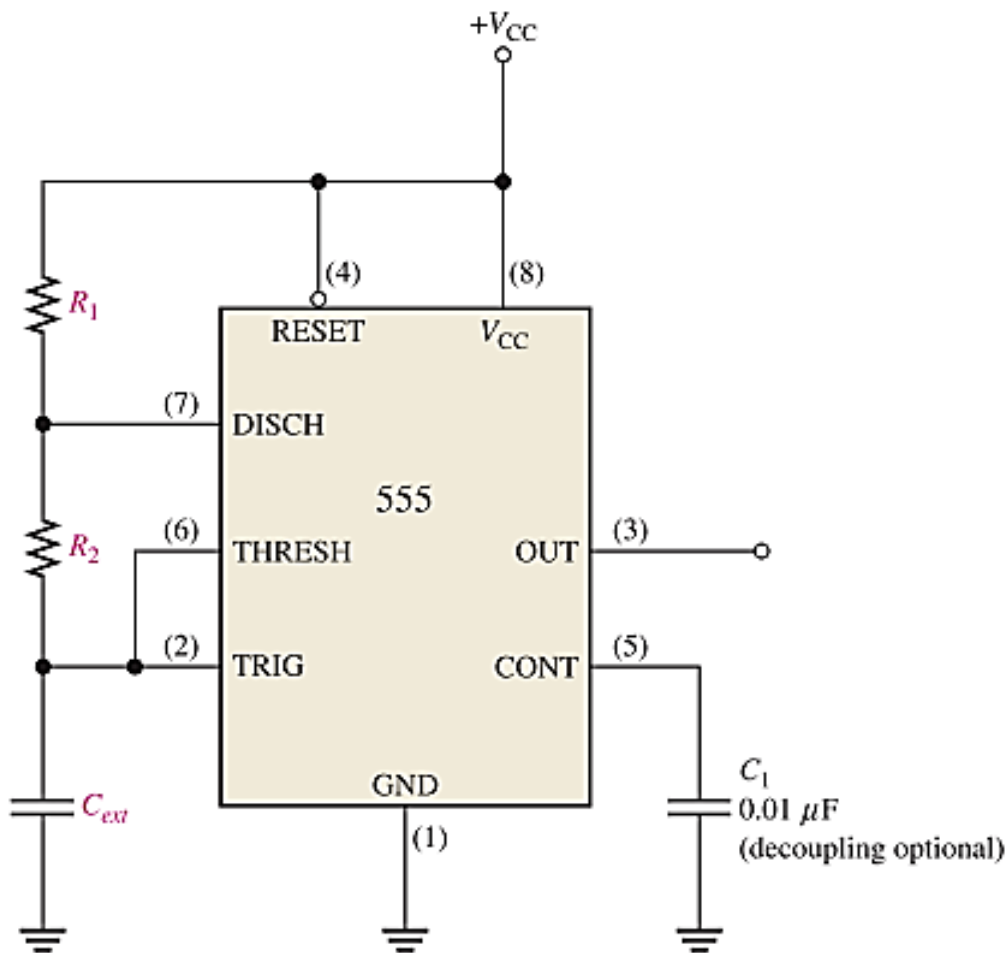
# 555 Astable

555 as an astable or free-running multivibrator, which is essentially a square-wave oscillator.





# 555 Astable..

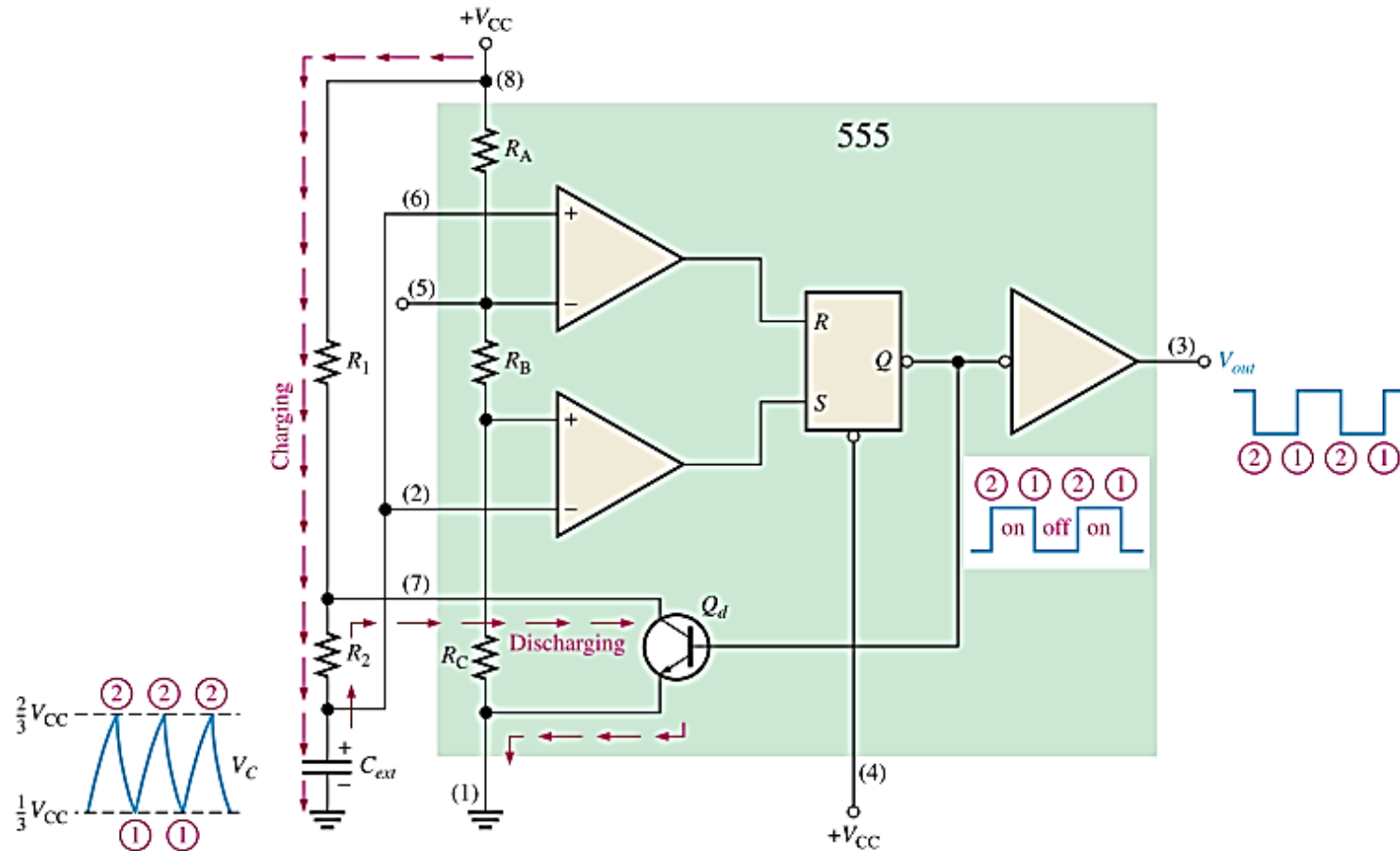

# The frequency of oscillation & Duty cycle

$$f_r = \frac{1.44}{(R_1 + 2R_2)C_{ext}}$$

$$t_H = 0.694(R_1 + R_2)C_{ext}$$

$$t_L = 0.694R_2C_{ext}$$

$$T = t_H + t_L = 0.694(R_1 + 2R_2)C_{ext}$$


$$\text{Duty cycle} = \left(\frac{t_H}{T}\right)100\% = \left(\frac{t_H}{t_H + t_L}\right)100\%$$

$$\text{Duty cycle} = \left(\frac{R_1 + R_2}{R_1 + 2R_2}\right)100\%$$

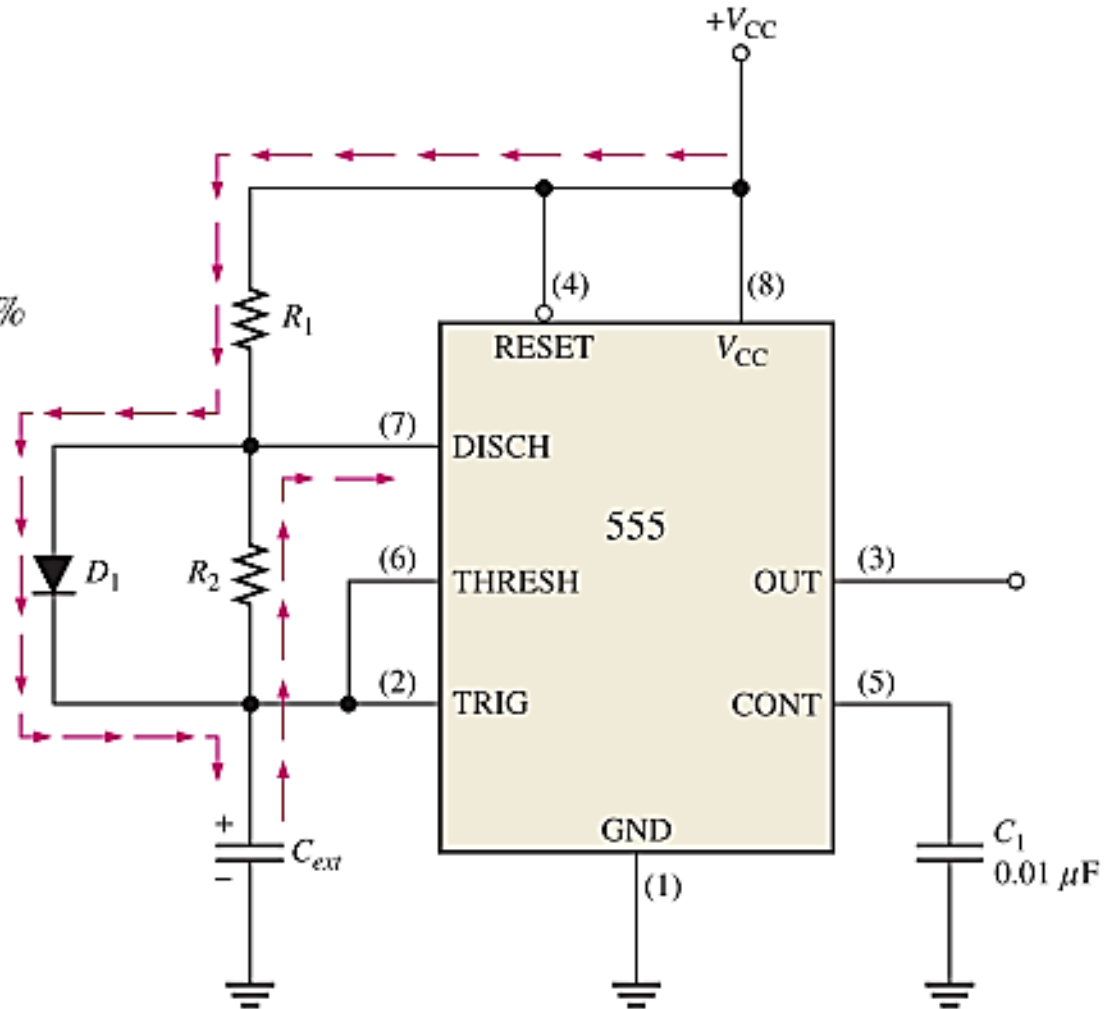
# Duty cycles of less than 50%

$$f_r \cong \frac{1.44}{(R_1 + R_2) C_{ext}}$$


$$\text{Duty cycle} \cong \left( \frac{R_1}{R_1 + R_2} \right) 100\%$$



# 555 Monostable Multivibrator

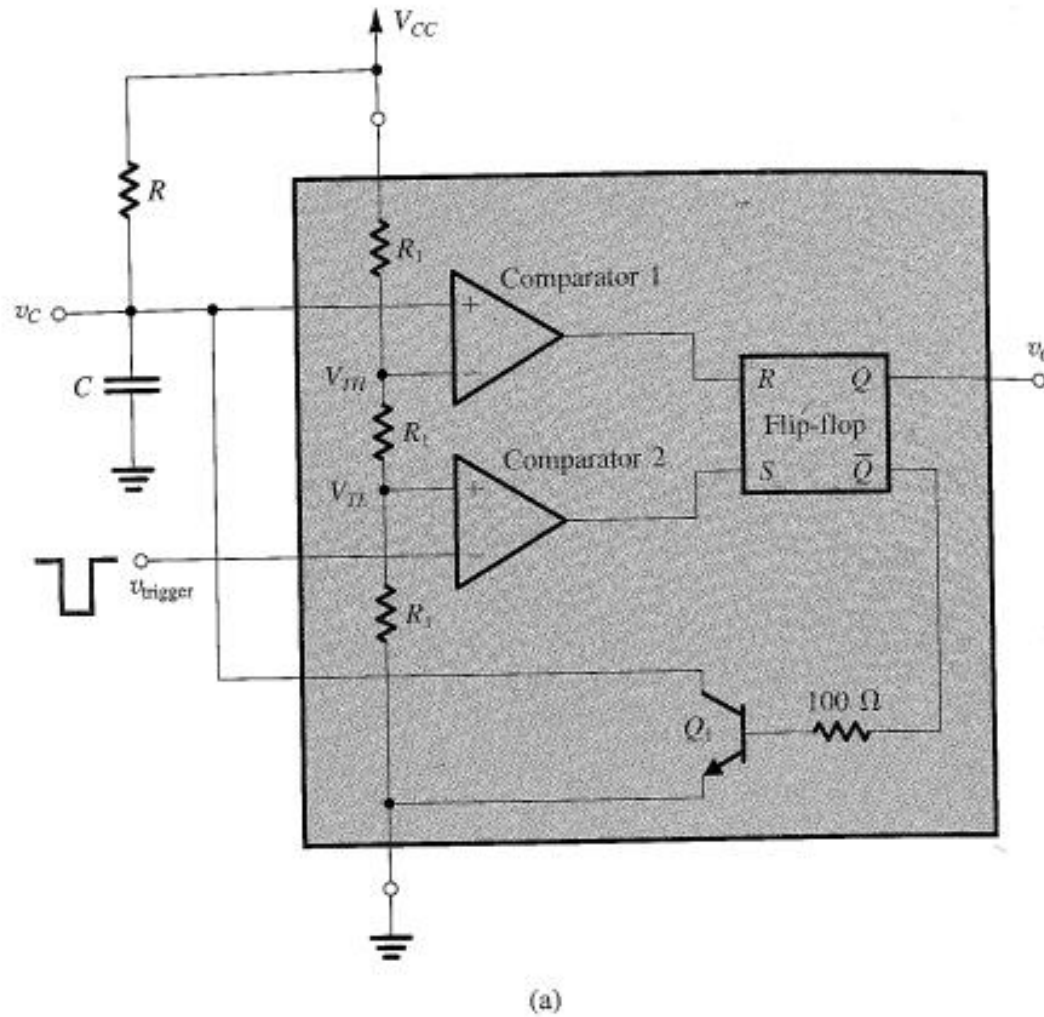

# 555 Monostable Multivibrator..

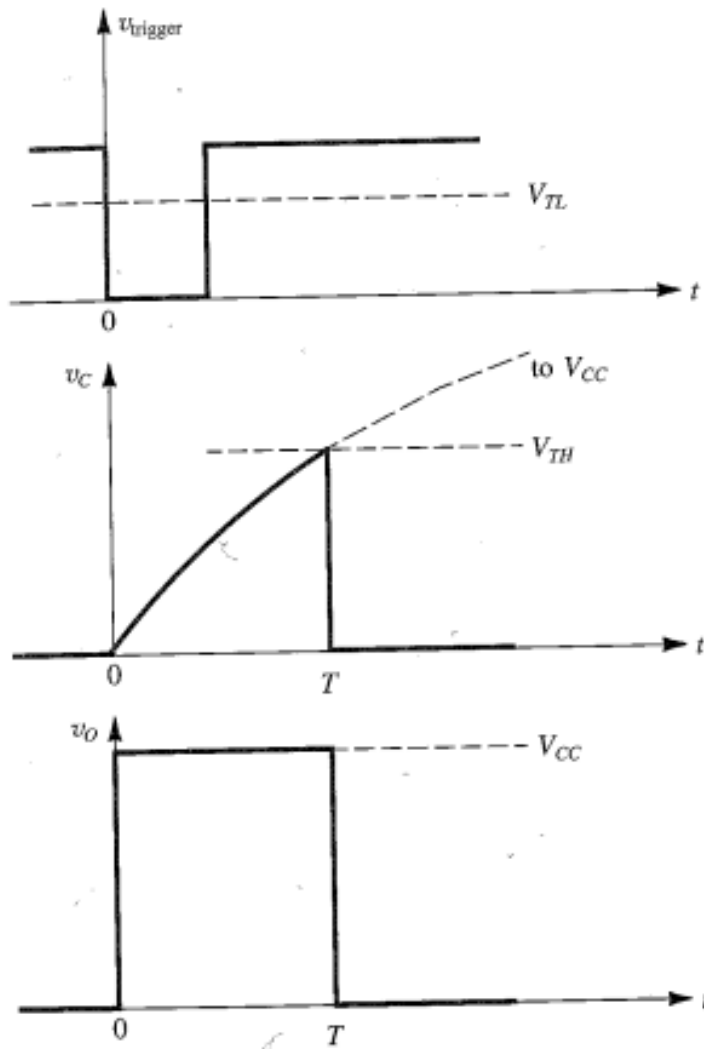





$$v_C = V_{CC}(1 - e^{-t/CR})$$

Substituting  $v_C = V_{TH} = \frac{2}{3}V_{CC}$  at  $t = T$  gives

$$T = CR \ln 3 \approx 1.1CR$$



# MULTIVIBRATORS USING OP-AMP
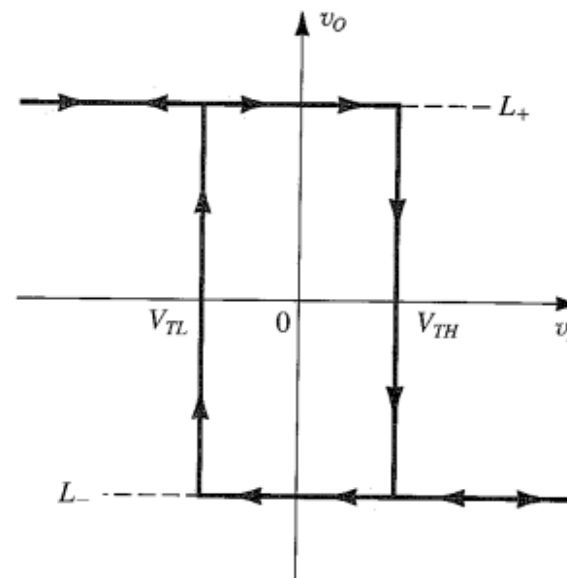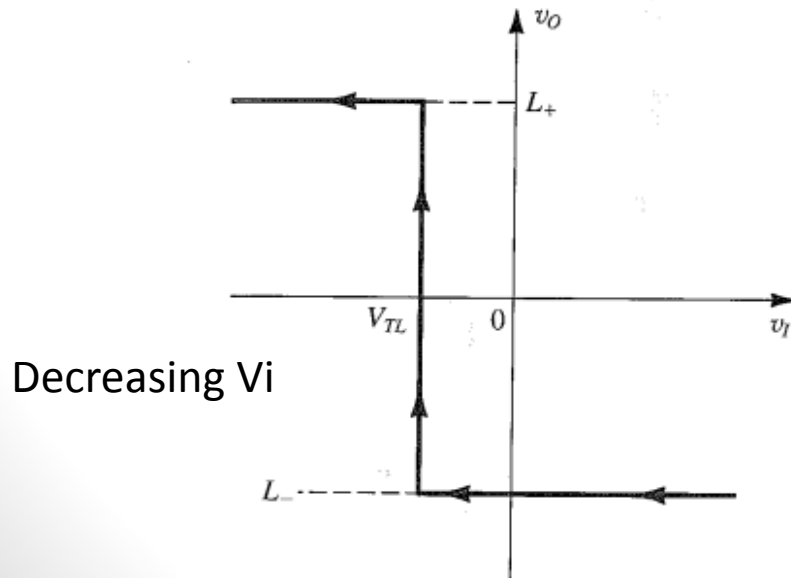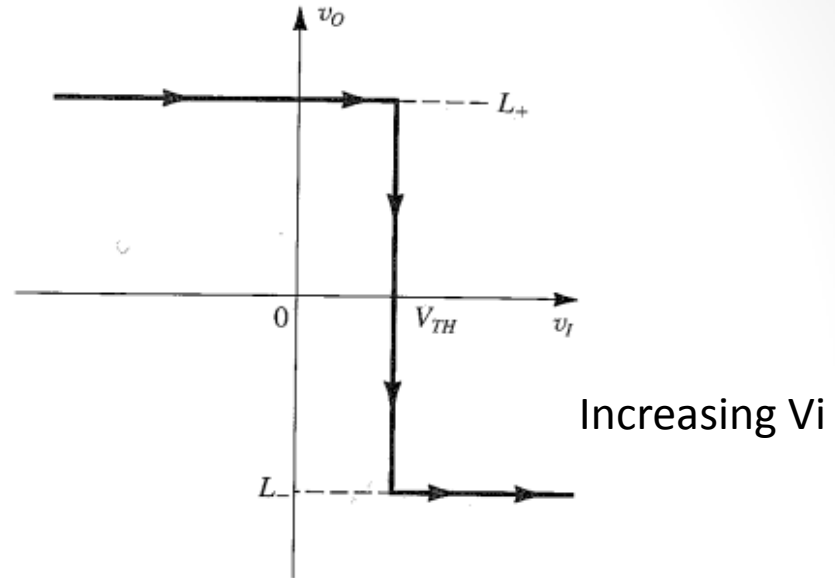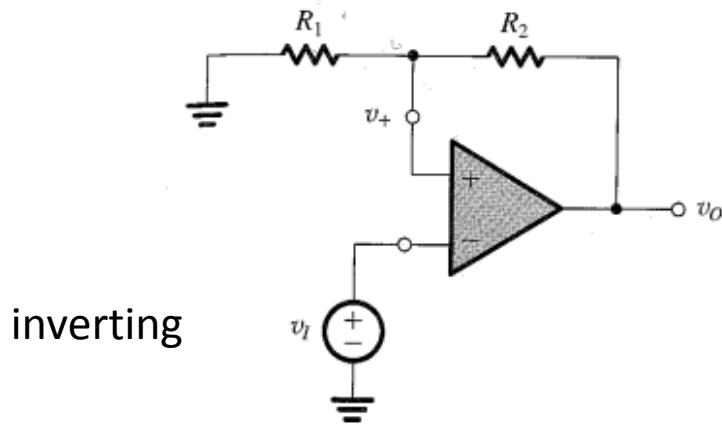
# Bistable Circuit and Transfer Characteristic



Complete Ch/s
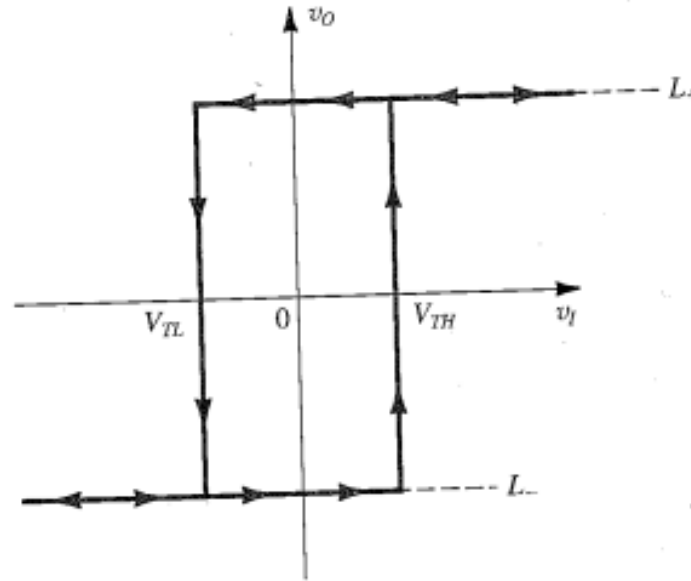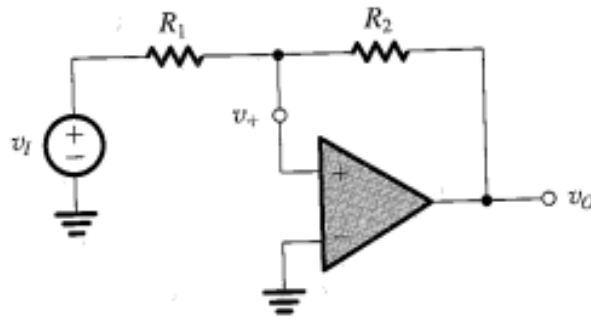
# Bistable with non inverting transfer ch/s



$$v_+ = v_i \frac{R_2}{R_1 + R_2} + v_o \frac{R_1}{R_1 + R_2}$$

$$V_{TL} = -L_+(R_1/R_2)$$




Feed fraction

$$\beta \equiv R_1 / (R_1 + R_2)$$






# Application of bistable as comparator (Schmit-Trigger)


## (Schmit-Trigger)

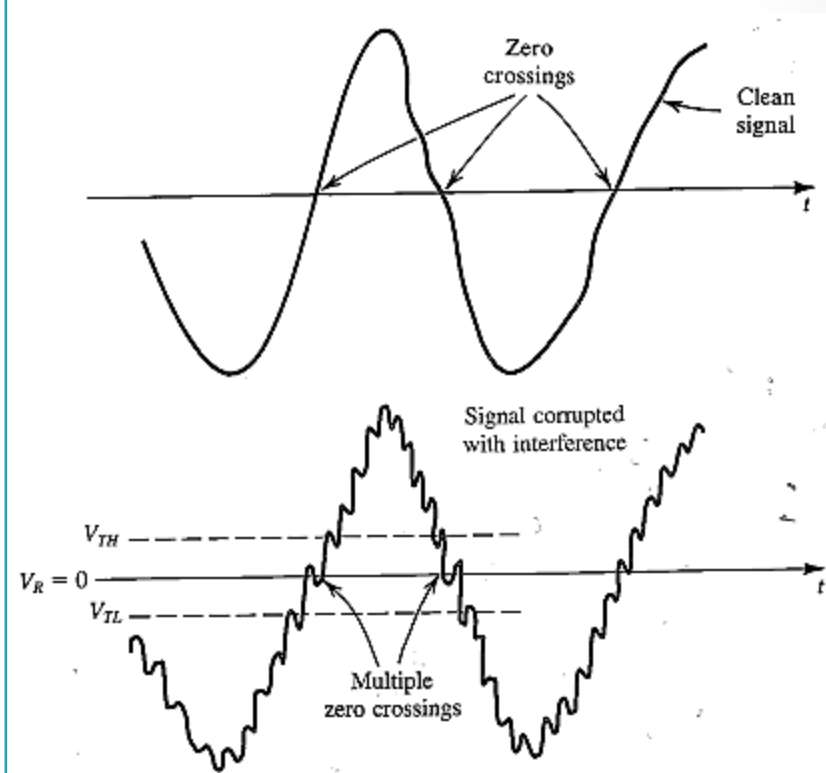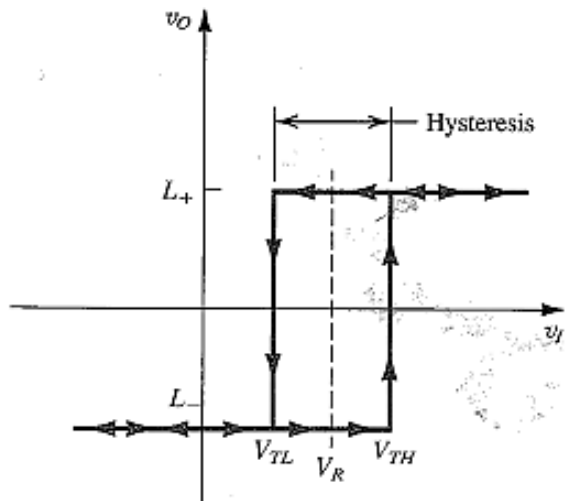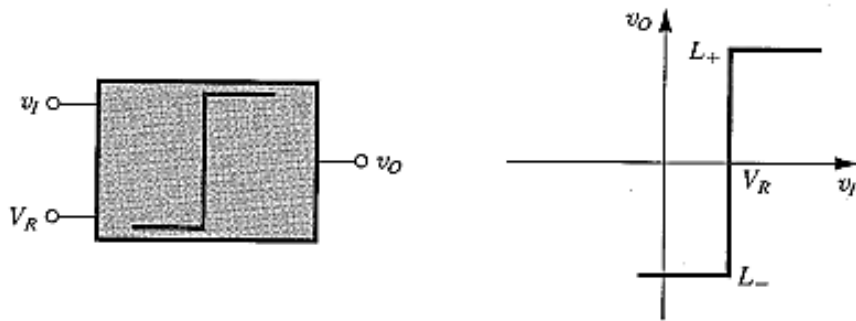

# Astable

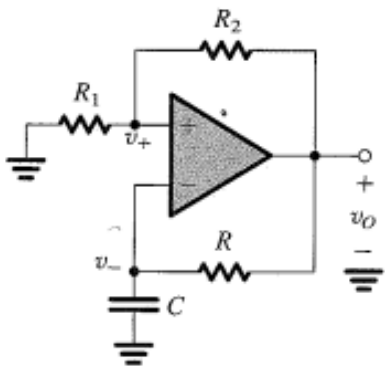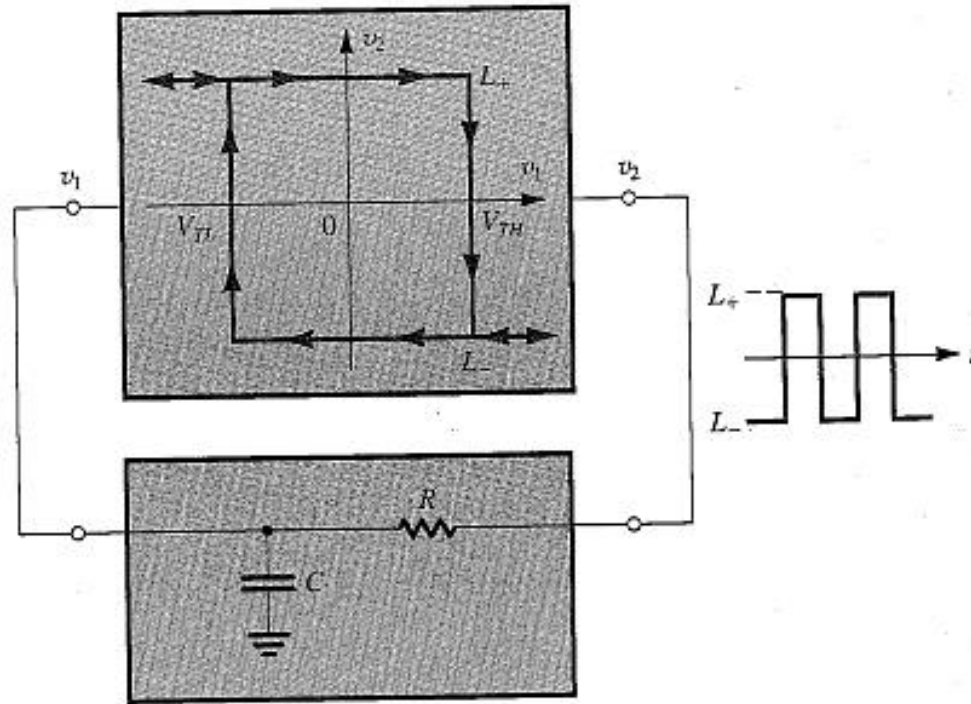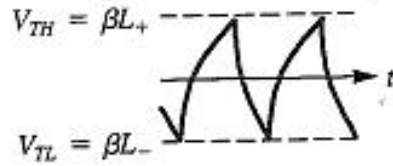

# Astable Circuit ..

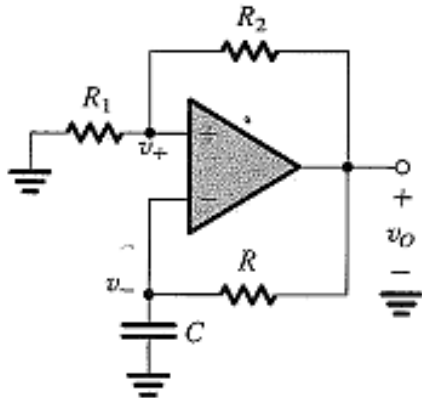

Voltage across capacitor:

$$v_- = L_+ - (L_+ - \beta L_-) e^{-t/\tau}$$

Substituting  $v_- = \beta L_+$  at  $t = T_1$  gives

$$T_1 = \tau \ln \frac{1 - \beta(L_-/L_+)}{1 - \beta}$$




$$v_- = L_- - (L_- - \beta L_+) e^{-t/\tau}$$

$$T_2 = \tau \ln \frac{1 - \beta(L_+/L_-)}{1 - \beta}$$



$$T \doteq T_1 + T_2.$$

$$T = 2\tau \ln \frac{1 + \beta}{1 - \beta}$$

$$\tau = CR.$$

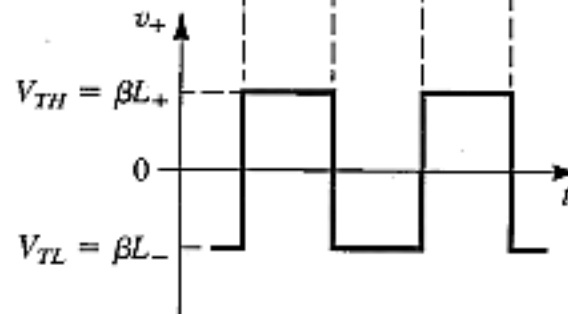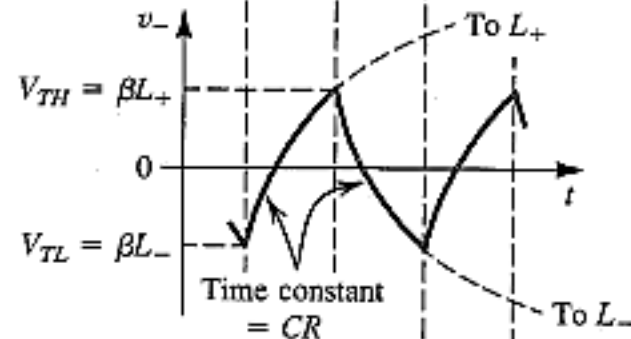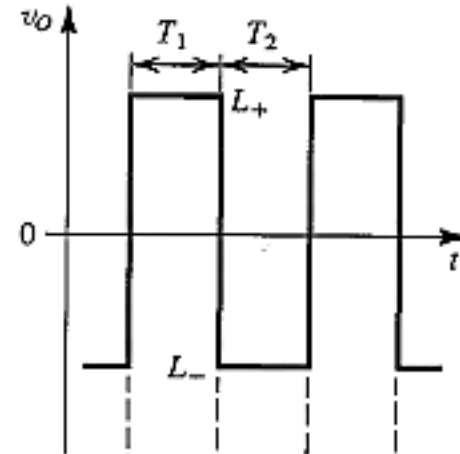

# Monostable circuit

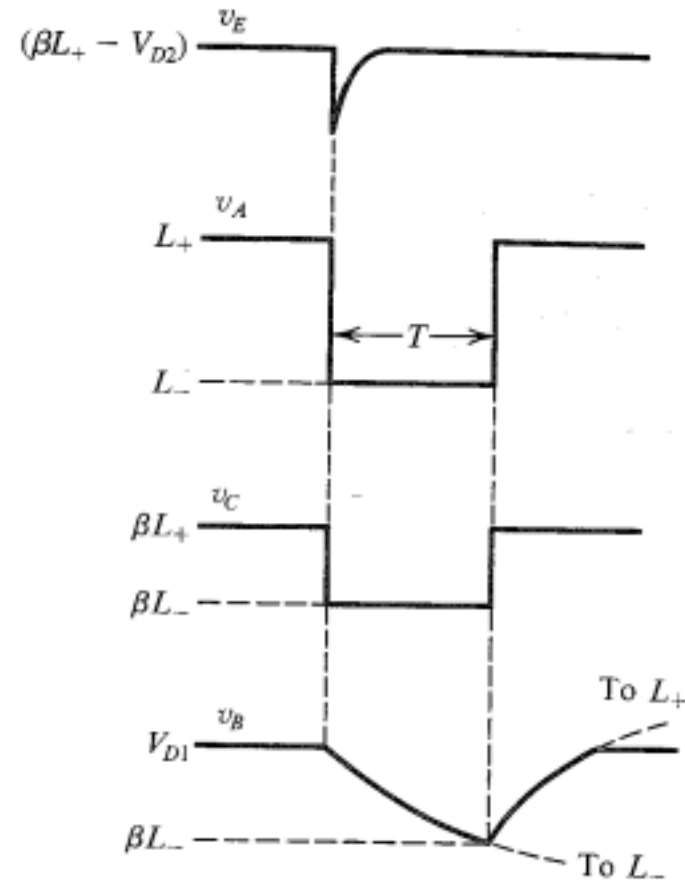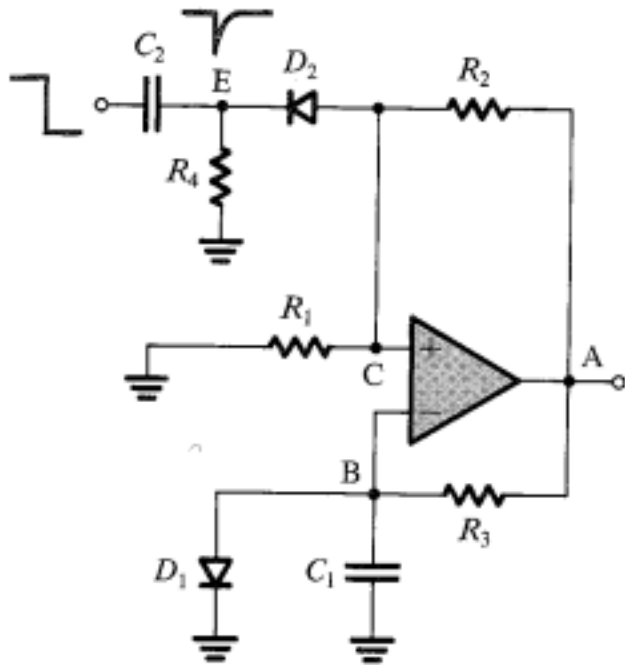

$$v_B(t) = L_- - (L_- - V_{D1})e^{-t/C_1 R_3}$$

by substituting  $v_B(T) = \beta L_-$ ,

$$\beta L_- = L_- - (L_- - V_{D1})e^{-T/C_1 R_3}$$

$$T = C_1 R_3 \ln \left( \frac{V_{D1} - L_-}{\beta L_- - L_-} \right)$$

$$T \approx C_1 R_3 \ln \left( \frac{1}{1 - \beta} \right)$$

- For more details, refer to:
  - Chapter 16 at T. Floyd, **Electronic Devices**, 9<sup>th</sup> edition.
  - Chapter 13 at Sedra, **Microelectronic Circuits**, 5<sup>th</sup> edition.
- The lecture is available online at:
  - <http://bu.edu.eg/staff/ahmad.elbanna-courses/12884>
- For inquiries, send to:
  - [ahmad.elbanna@feng.bu.edu.eg](mailto:ahmad.elbanna@feng.bu.edu.eg)