

Applied Electronics

Instructor:

Dr. Ahmad El-Banna

DAY#2
SUMMER 2016



(1)

Agenda

Transistors Structure

Basic Operation


Bias Circuits (DC Analysis)

Models (AC Analysis)


Troubleshooting

Practical Applications

 
BIPOLAR JUNCTION TRANSISTOR (BJT) STRUCTURE



(a) Basic epitaxial planar structure

 


(b) npn

 


(c) pnp

BJT symbol

 


(a) npn

 


(b) pnp

Transistor Packages


General Purpose

 

(a) TO-92

 

(b) SOT-23



 


(c) TO-18. Emitter is closest to tab.


Multiple Transistor Package



   
(a) Dual metal can. Emitters are closest to tab.



 
(b) Quad dual in-line (DIP) and quad flat-pack. Dot indicates pin 1.



 
(c) Quad small outline (SO) package for surface-mount technology




Power Transistors

 


(a) TO-220

 

(b) TO-225

 


(c) D-Pack

 

(d) TO-3


Basic Operation

- **Biasing & Operation**

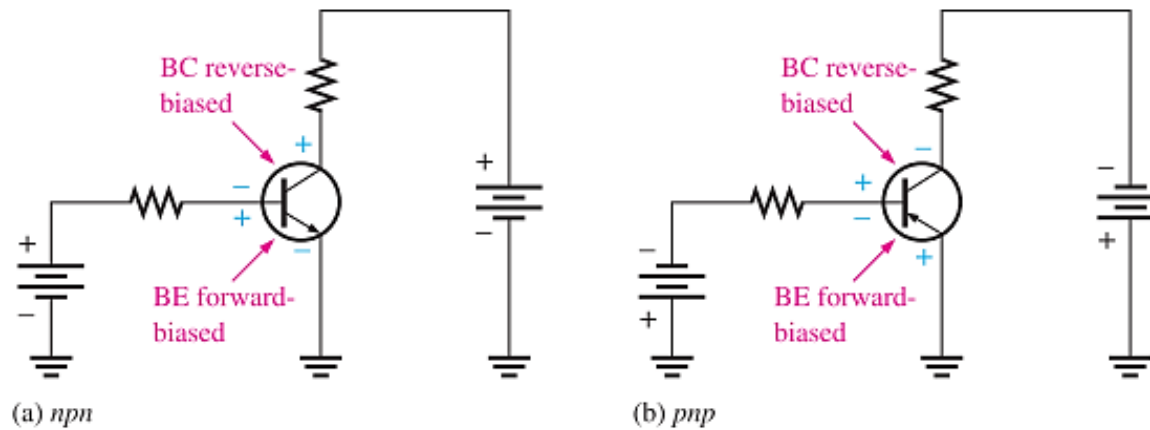

- **Transistor Currents**


$$I_E = I_C + I_B$$

 

BJT Configurations

Configuration	Input	Output
Common Emitter	Base	Collector
Common Base	Emitter	Collector
Common Collector	Base	Emitter

 - Base terminal can't be output
- Collector terminal can't be input



BJT Parameters

$$\beta_{DC} = \frac{I_C}{I_B}$$

- The dc current gain of a transistor is the ratio of the dc collector current (I_C) to the dc base current (I_B) and is designated dc **beta** (β_{DC}).

$$h_{FE} = \beta_{DC}$$

- Typical values of β_{DC} range from less than 20 to 200 or higher.
- β_{DC} is usually designated as an equivalent hybrid (h) parameter, h_{FE} , on transistor datasheets.

$$\alpha_{DC} = \frac{I_C}{I_E}$$

- The ratio of the dc collector current (I_C) to the dc emitter current (I_E) is the dc alpha (α_{DC}).

Transistor DC Model

I_B : dc base current


I_E : dc emitter current

I_C : dc collector current

V_{BE} : dc voltage at base with respect to emitter

V_{CB} : dc voltage at collector with respect to base

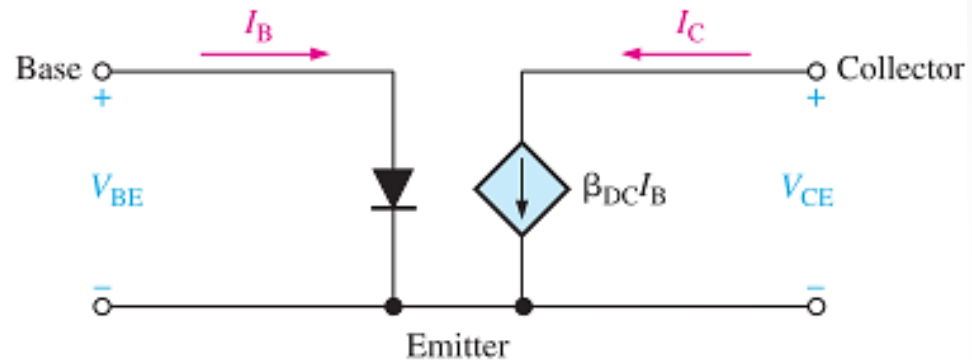V_{CE} : dc voltage at collector with respect to emitter




$$V_{BE} \cong 0.7 \text{ V}$$

$$V_{R_B} = V_{BB} - V_{BE}$$

$$V_{R_B} = I_B R_B$$

$$I_B R_B = V_{BB} - V_{BE}$$

$$I_B = \frac{V_{BB} - V_{BE}}{R_B}$$

 

$$V_{CE} = V_{CC} - V_{R_C}$$

$$V_{R_C} = I_C R_C$$

$$I_C = \beta I_B$$




$$V_{CE} = V_{CC} - I_C R_C$$

$$V_{CB} = V_{CE} - V_{BE}$$


Collector characteristic curves

Operation Regions

- Active
- Cut-off
- Saturation

   

BJT as an Amplifier

 



Voltage gain magnitude:

$$A_v \cong \frac{R_C}{r'_e}$$

$$r_e = 26 \text{ mV} / I_E$$


$$I_E = I_C + I_B$$

BJT as a Switch

 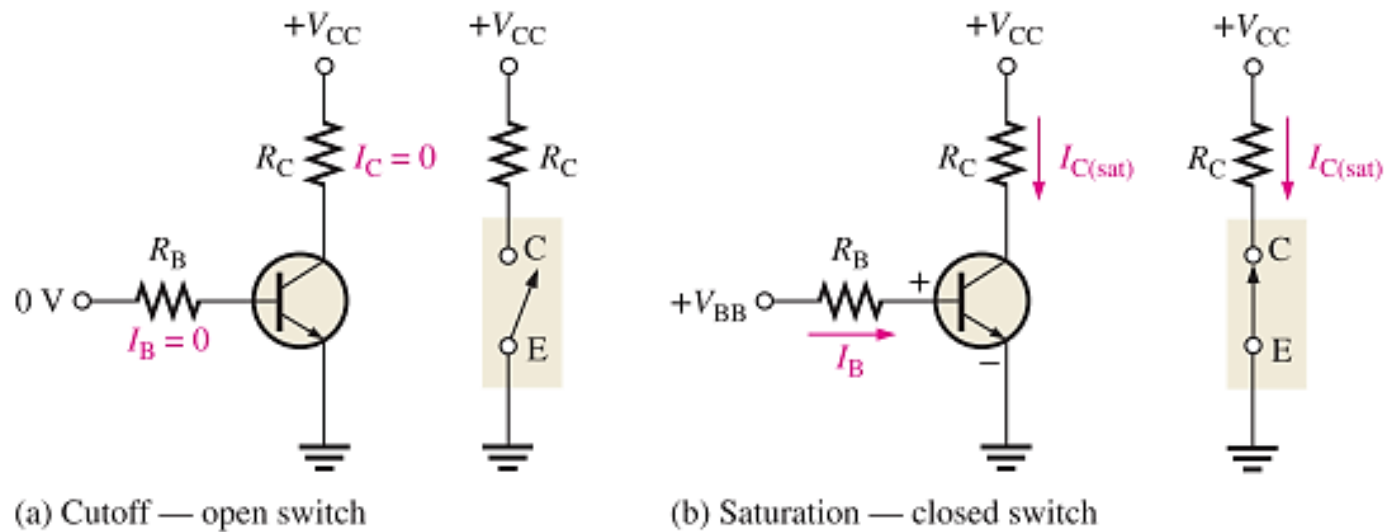


The Phototransistor




$$I_C = \beta_{DC} I_\lambda$$

 

(a) Schematic symbol

 


(b) Typical packages

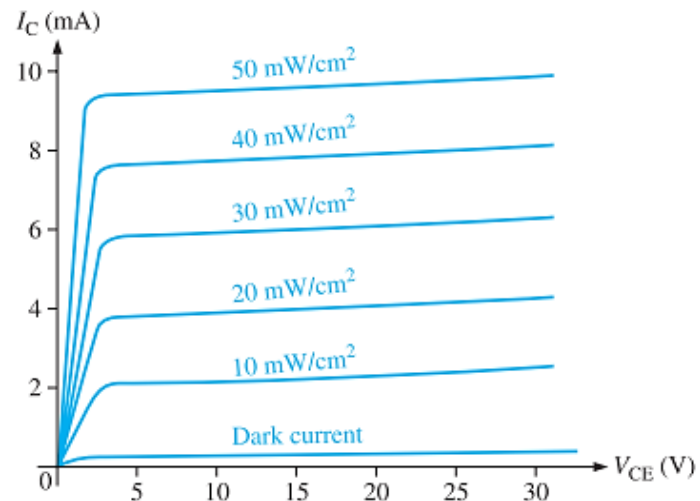  


Phototransistor Application

 Relay circuits driven by a phototransistor



(a) Light activated

 

(b) Light deactivated




- A **relay** is an electrically operated switch.
- **relays** use an electromagnet to mechanically operate a switch




Optocouplers


- **Basic optocouplers**

 


(a) LED-to-photodiode

 


(b) LED-to-phototransistor

 

(a) Dual-in-line

 

(b) Surface-mount

 


(c) Ball-grid

 
Examples of optocoupler packages

Transistor Bias Circuit


- What's Biasing?
 - Bias establishes the dc operating point (Q-point) for proper linear operation of an amplifier.
- Why?
 - If an amplifier is not biased with correct dc voltages on the input and output, it can go into saturation or cutoff when an input signal is applied.



 (a) Linear operation: larger output has same shape as input except that it is inverted









 (b) Nonlinear operation: output voltage limited (clipped) by cutoff





(c) Nonlinear operation: output voltage limited (clipped) by saturation


Q-point Adjustment

      

DC Load Line

  

 
- Variations in collector current and collector-to-emitter voltage as a result of a variation in base current.




$$I_{BQ} = \frac{V_{BB} - 0.7 \text{ V}}{R_B} = \frac{3.7 \text{ V} - 0.7 \text{ V}}{10 \text{ k}\Omega} = 300 \mu\text{A}$$


$$I_{CQ} = \beta_{DC} I_{BQ} = (100)(300 \mu\text{A}) = 30 \text{ mA}$$
 
$$V_{CEQ} = V_{CC} - I_{CQ} R_C = 10 \text{ V} - (30 \text{ mA})(220 \Omega) = 3.4 \text{ V}$$



 


 (a) Transistor is driven into saturation because the Q-point is too close to saturation for the given input signal.




(b) Transistor is driven into cutoff because the Q-point is too close to cutoff for the given input signal.

Waveform Distortion

 

(c) Transistor is driven into both saturation and cutoff because the input signal is too large.

VOLTAGE-DIVIDER BIAS

 

$$V_B \cong \left(\frac{R_2}{R_1 + R_2} \right) V_{CC}$$


$$V_E = V_B - V_{BE}$$

$$I_C \cong I_E = \frac{V_E}{R_E}$$

$$V_C = V_{CC} - I_C R_C$$

$$V_{CE} = V_C - V_E$$

Loading Effects of Voltage-Divider Bias

 

Stiff:

$$R_{IN(BASE)} \cong 10R_2$$

$$V_B \cong \left(\frac{R_2}{R_1 + R_2} \right) V_{CC}$$


Not stiff:

$$R_{IN(BASE)} < 10R_2$$

$$V_B = \left(\frac{R_2 \parallel R_{IN(BASE)}}{R_1 + R_2 \parallel R_{IN(BASE)}} \right) V_{CC}$$

$$R_{IN(BASE)} = \frac{\beta_{DC} V_B}{I_E}$$

 Thevenin's Theorem Applied to Voltage-Divider Bias



$$V_{TH} = \left(\frac{R_2}{R_1 + R_2} \right) V_{CC}$$

$$R_{TH} = \frac{R_1 R_2}{R_1 + R_2}$$

$$V_{TH} - V_{R_{TH}} - V_{BE} - V_{R_E} = 0$$


$$V_{TH} = I_B R_{TH} + V_{BE} + I_E R_E$$

$$V_{TH} = I_E (R_E + R_{TH} / \beta_{DC}) + V_{BE}$$


$$I_E = \frac{V_{TH} - V_{BE}}{R_E + R_{TH} / \beta_{DC}}$$

Other Bias Circuits

Base Bias

 


Emitter Bias

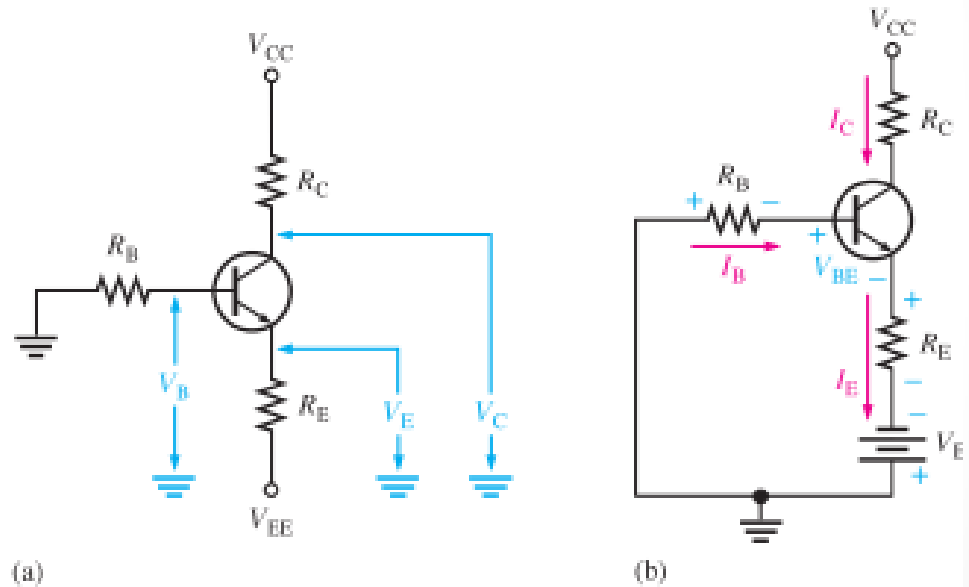


Other Bias Circuits..

Emitter Feedback Bias

 



Collector Feedback Bias

 

Note:

Different bias circuits has different stability levels against beta and/or temperature changes

Linear Amplifier

  



C.E. AC Analysis

- **DC Analysis:**

Capacitors → Open Circuit
(See before)

- **AC Analysis:**

  Capacitors → short Circuit
DC supply → ground



AC r-parameter Model


Input resistance $R_{in(base)} = \beta_{ac} r'_e$

Output resistance $R_{out} \cong R_C$

Voltage gain $A_v = \frac{R_C}{r'_e}$

Current gain $A_i = \frac{I_c}{I_s}$

Power gain $A_p = A'_v A_i$

 


Multistage Amplifier


$$A'_v = A_{v1}A_{v2}A_{v3} \dots A_{vn}$$

$$A_{v(\text{dB})} = 20 \log A_v$$
 
$$A'_{v(\text{dB})} = A_{v1(\text{dB})} + A_{v2(\text{dB})} + \dots + A_{vn(\text{dB})}$$



- A two-stage common-emitter amplifier.

 

$\beta_{DC} = \beta_{ac} = 150$ for Q_1 and Q_2

FET vs. BJT

 


FIG. 6.1

(a) Current-controlled and (b) voltage-controlled amplifiers.

- One of the most important characteristics of the FET is its high input impedance.
- Typical ac voltage gains for BJT amplifiers are a great deal more than for FETs.
- FETs are more temperature stable than BJTs, and FETs are usually smaller than BJTs, making them particularly useful in integrated-circuit (IC) chips.

FET vs. BJT.

 
 


TABLE 6.2

JFET		BJT
$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$	\Leftrightarrow	$I_C = \beta I_B$
$I_D = I_S$	\Leftrightarrow	$I_C \cong I_E$
$I_G \cong 0 \text{ A}$	\Leftrightarrow	$V_{BE} \cong 0.7 \text{ V}$

 


FIG. 6.23

(a) JFET versus (b) BJT.

FET Characteristics

 


FIG. 6.5

JFET at $V_{GS} = 0\text{ V}$ and $V_{DS} > 0\text{ V}$.

 


FIG. 6.6

Varying reverse-bias potentials across the p - n junction of an n -channel JFET.


 


FIG. 6.8

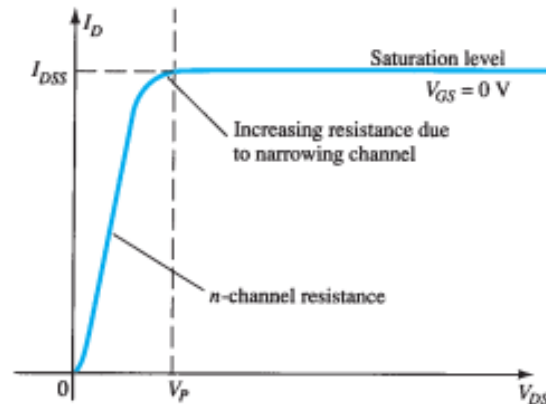Pinch-off ($V_{GS} = 0\text{ V}$, $V_{DS} = V_P$).



JFET & MOSFET Symbol

 


FIG. 6.14

JFET symbols: (a) n-channel; (b) p-channel.

 


FIG. 6.3

Junction field-effect transistor (JFET).

 


FIG. 6.30

Graphic symbols for: (a) n-channel depletion-type MOSFETs and (b) p-channel depletion-type MOSFETs.

 


FIG. 6.24

n-Channel depletion-type MOSFET.

Other MOSFETs

- VMOS AND UMOS POWER MOSFETs

 


FIG. 6.43

(a) VMOS MOSFET; (b) UMOS MOSFET.

- CMOS

 


FIG. 6.44

CMOS with the connections indicated in Fig. 6.45.

- MESFET

 


FIG. 6.47

Basic construction of an n-channel MESFET.

 


FIG. 6.49

Symbol and basic biasing arrangement for an n-channel MESFET.


 


FIG. 6.45

CMOS inverter.


TROUBLESHOOTING

Testing with DMM

 


▲ FIGURE 4-38

A basic transistor bias circuit.

 

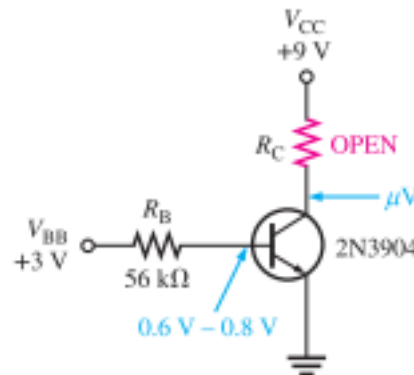
(a) **Fault:** Open base resistor.

Symptoms: Readings from μV to a few mV at base due to floating point. 9 V at collector because transistor is in cutoff.



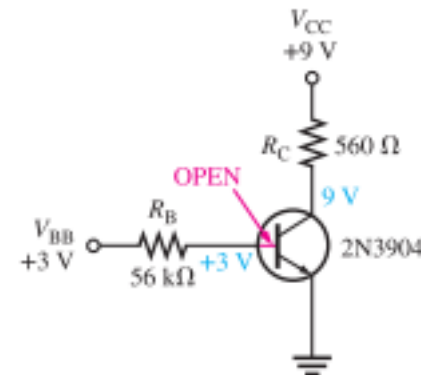(b) **Fault:** Open collector resistor.


Symptoms: A very small voltage may be observed at the collector when a meter is connected due to the current path through the BC junction and the meter resistance.




(c) **Fault:** Base internally open.

Symptoms: 3 V at base lead. 9 V at collector because transistor is in cutoff.


Testing with DMM..

 

 
(d) **Fault:** Collector internally open.
Symptoms: 0.6 V – 0.8 V at base lead due to forward voltage drop across base-emitter junction. 9 V at collector because the open prevents collector current.



 
(e) **Fault:** Emitter internally open.
Symptoms: 3 V at base lead. 9 V at collector because there is no collector current. 0 V at the emitter as normal.



 (f) **Fault:** Open ground connection.
Symptoms: 3 V at base lead. 9 V at collector because there is no collector current. 2.5 V or more at the emitter due to the forward voltage drop across the base-emitter junction. The measuring voltmeter provides a forward current path through its internal resistance.




 (a) Both junctions should typically read 0.7 V when forward-biased.




(b) Both junctions should ideally read OPEN when reverse-biased.

Testing with DMM...

 


▲ FIGURE 4-41

 Typical DMM test of a properly functioning *npn* transistor. Leads are reversed for a *pnp* transistor.



Voltage Divider circuit

 


(a) Faulty circuit

FAULT	DESCRIPTION	V_C	V_E	V_B
1	R_1 open	10 V	0 V	0 V
2	R_E open	10 V	2.50 V	3.20 V
3	Base internally open	10 V	0 V	3.20 V
4	Emitter internally open	10 V	0 V	3.20 V
5	Collector internally open	10 V	0.41 V	1.11 V


(b) Possible faults for circuit in part (a)

▲ FIGURE 5-25

Faults for which $V_C = V_{CC}$.

 

(a) R_C open

 


(b) R_2 open

◀ FIGURE 5-27

Faults for which the transistor is conducting or appears to be conducting.


2-stage Amplifier

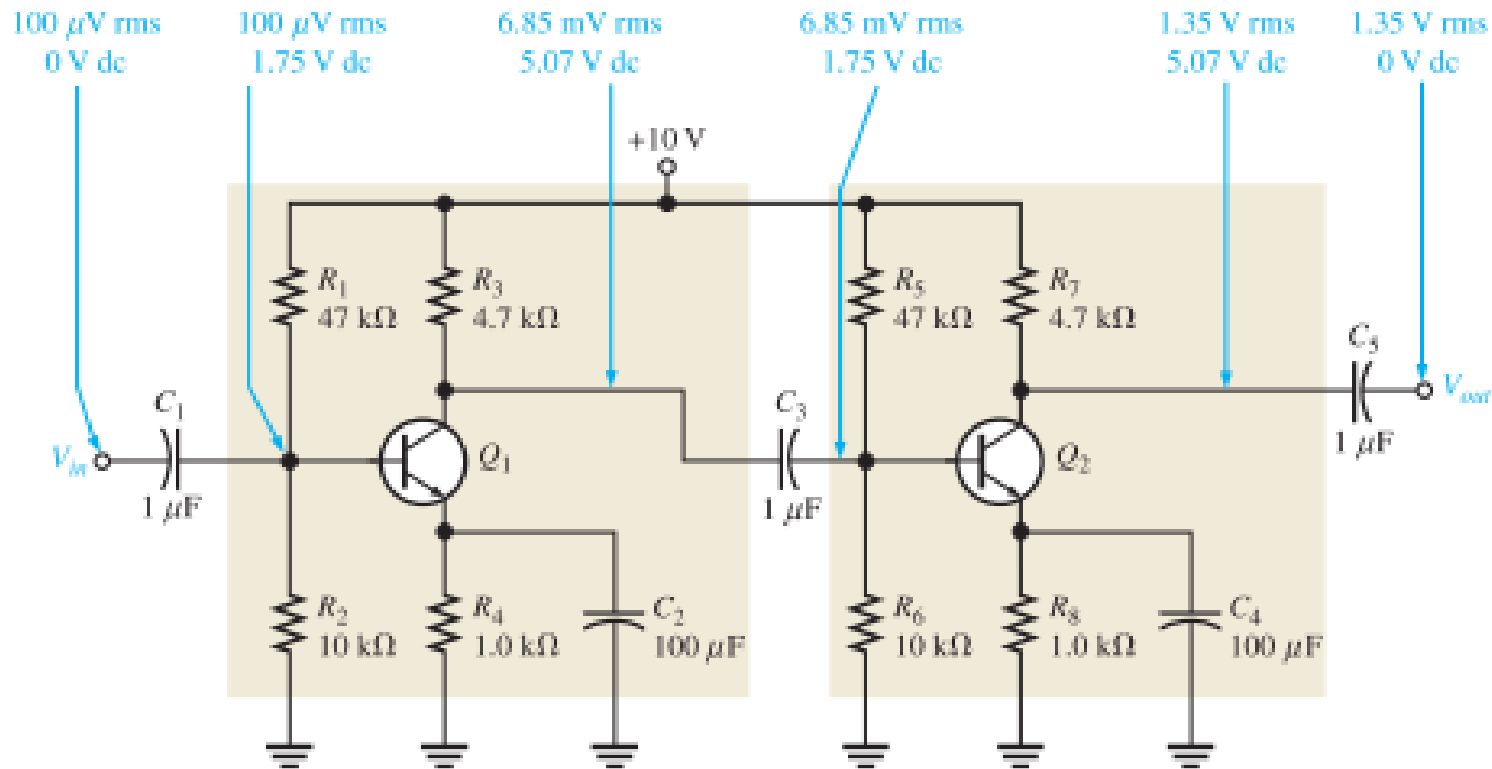

► **FIGURE 6-42**

A two-stage common-emitter amplifier with correct voltages indicated. Both transistors have dc and ac betas of 150. Different values of β will produce slightly different results.

FET circuits

 

◀ **FIGURE 8-56**

Failures in an E-MOSFET circuit with voltage-divider bias.

PRACTICAL APPLICATIONS

Relay Driver

 


FIG. 4.104

Relay driver: (a) absence of protective device; (b) with a diode across the relay coil.

Light Control

 


FIG. 4.105

Using the transistor as a switch to control the on–off states of a bulb: (a) network; (b) effect of low bulb resistance on collector current; (c) limiting resistor.

Maintaining fixed load current


 


FIG. 4.106

 Building a constant-current source assuming ideal BJT characteristics: (a) ideal characteristics; (b) network; (c) demonstrating why I_C remains constant.



Alarm System


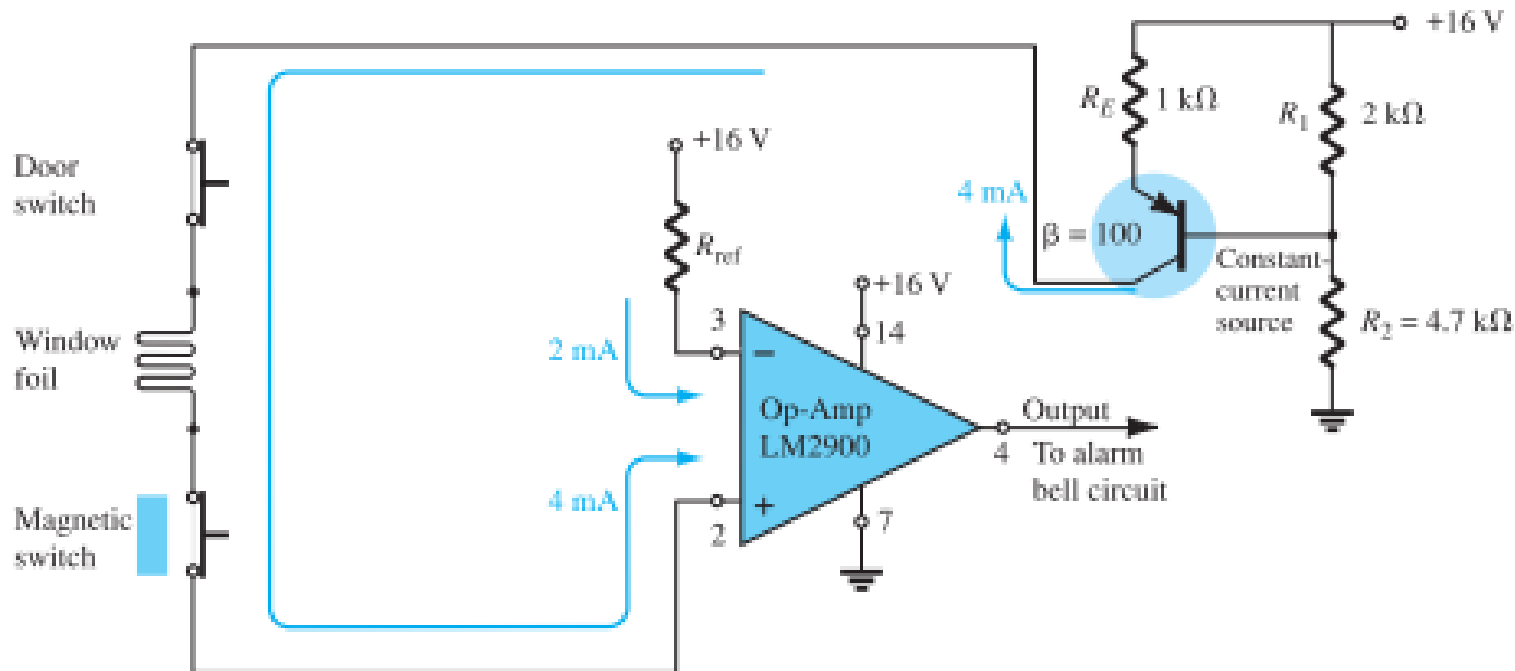


FIG. 4.108

An alarm system with a constant-current source and an op-amp comparator.


Logic gates

 

A	B	C
0	0	0
0	1	1
1	0	1
1	1	1

1 = high
0 = low

(a)

 

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

(b)

FIG. 4.111

BJT logic gates: (a) OR; (b) AND.

Voltage level indicator

 


FIG. 4.112

Voltage level indicator.

Audio Mixer

 


FIG. 5.130

Audio mixer.

Preamplifier

 


FIG. 5.133

Preamplifier for a dynamic microphone.

Voltage controlled resistor


 
 
 
 





FIG. 7.64

JFET voltage-controlled drain resistance: (a) general equivalence; (b) with $V_{GS} = 0 \text{ V}$; (c) with $V_{GS} = -1.5 \text{ V}$.

Security Alarm System

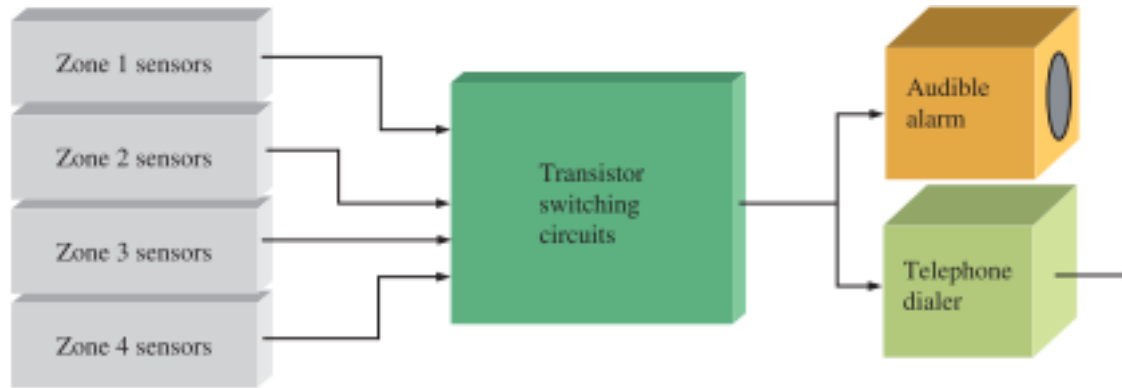



Security Alarm System..

  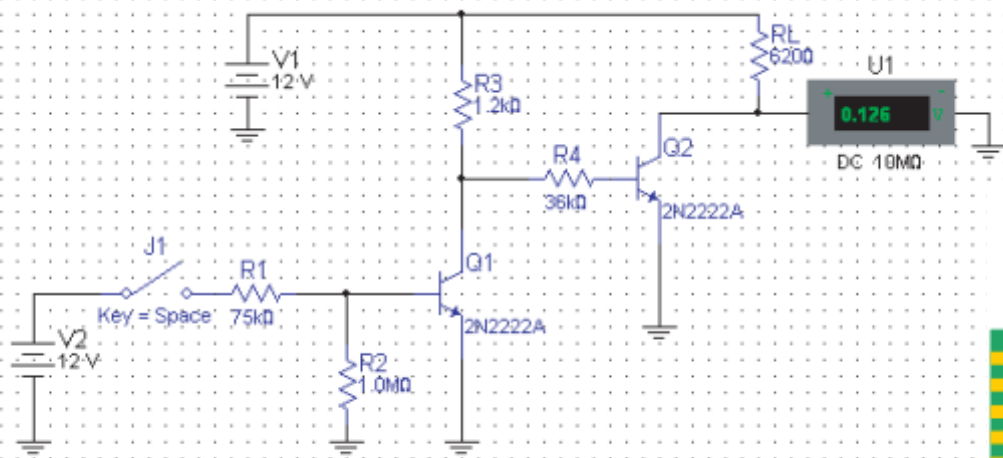

▲ FIGURE 4-51

Simulation of the switching circuit.

Temperature to Voltage Converter

  


(a) Circuit

TEMPERATURE, °C	THERMISTOR RESISTANCE, kΩ
60	1.256
65	1.481
70	1.753
75	2.084
80	2.490



(b) Temperature characteristic of the thermistor for the specified range

Audio Preamplifier



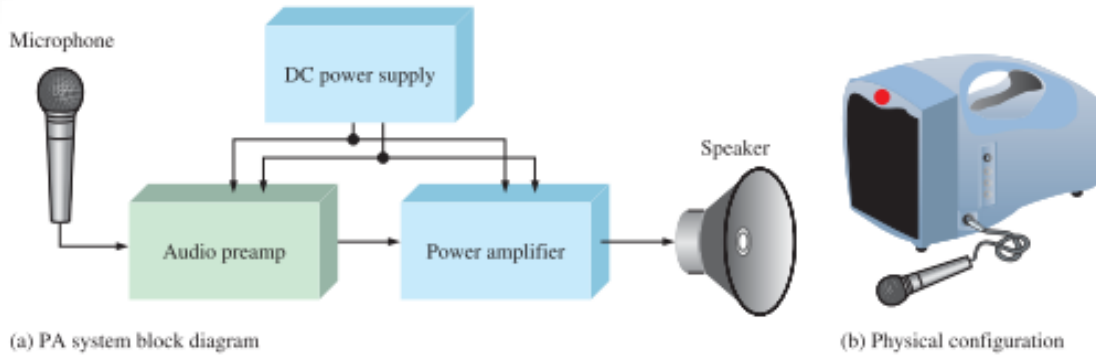


(a) PA system block diagram

(b) Physical configuration

  

Active Antenna

   

References

- Floyd, chapters:4-6,8-9
- Boylestad, chapters: 3-8
- For enquires:
 - ahmad.elbanna@feng.bu.edu.eg