

VHDL in Practice

Instructor:

Dr. Ahmad El-Banna

DAY#2
SUMMER 2016



(1)

Agenda

Test bench

Modeling the Structure way

Structural Example

Behavioral & Structural Example

Test Bench your Model

- Testing a design by simulation
- Use a *test bench* model
 - a Model that uses your Model
 - apply test sequences to your inputs
 - monitors values on output signals
 - either using simulator
 - or with a process that verifies correct operation
 - or logic analyzer

Test Bench of the multiplexer example

-- Test Bench for Multiplexer (ESD figure 2.5)-- by Weijun Zhang, 04/2001
-- four operations are tested in this example.

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;

entity Mux_TB is
    -- empty entity
end Mux_TB;

-----

architecture TB of Mux_TB is
    -- initialize the declared signals
    signal T_I3: std_logic_vector(2 downto 0):="000";
    signal T_I2: std_logic_vector(2 downto 0):="000";
    signal T_I1: std_logic_vector(2 downto 0):="000";
    signal T_I0: std_logic_vector(2 downto 0):="000";
    signal T_O: std_logic_vector(2 downto 0);
    signal T_S: std_logic_vector(1 downto 0);

    component Mux
    port(
        I3:      in std_logic_vector(2 downto 0);
        I2:      in std_logic_vector(2 downto 0);
        I1:      in std_logic_vector(2 downto 0);
        I0:      in std_logic_vector(2 downto 0);
        S:       in std_logic_vector(1 downto 0);
        O:       out std_logic_vector(2 downto 0)
    );
end component;
```

Steps of a testbench:

- entity declaration for your testbench.
- Component Declaration for the Unit Under Test (UUT)
- declare inputs and initialize them
- declare outputs and initialize them
- Clock period definitions
- Stimulus process

Test Bench of the multiplexer example..

```
begin
  U_Mux: Mux port map (T_I3, T_I2, T_I1, T_I0, T_S, T_O);
  process

variable err_cnt: integer :=0;
  begin

    T_I3 <= "001";           -- I0-I3 are different signals
    T_I2 <= "010";
    T_I1 <= "101";
    T_I0 <= "111";

    -- case select equal "00"
    wait for 10 ns;
    T_S <= "00";
    wait for 1 ns;
    assert (T_O="111") report "Error Case 0" severity error;
    if (T_O/="111") then
      err_cnt := err_cnt+1;
    end if;
    -- case select equal "01"
    wait for 10 ns;
    T_S <= "01";
    wait for 1 ns;
    assert (T_O="101") report "Error Case 1" severity error;
    if (T_O/="101") then
      err_cnt := err_cnt+1;
    end if;
```

Test Bench of the multiplexer example...

```
-- case select equal "10"
    wait for 10 ns;
    T_S <= "10";
    wait for 1 ns;
    assert (T_O="010") report "Error Case 2" severity error;
    if (T_O/="010") then
        err_cnt := err_cnt+1;
    end if;
-- case select equal "11"
    wait for 10 ns;
    T_S <= "11";
    wait for 1 ns;
    assert (T_O="001") report "Error Case 3" severity error;

    if (T_O/="001") then
        err_cnt := err_cnt+1;
    end if;
-- case equal "11"
    wait for 10 ns;
    T_S <= "UU";

-- summary of all the tests
    if (err_cnt=0) then
        assert (false)
        report "Testbench of Mux completed sucessfully!"
        severity note;
    else
        assert (true)
        report "Something wrong, try again!"
        severity error;
    end if;

    wait;

end process;

end TB;


-----
configuration CFG_TB of Mux_TB is
    for TB
        end for;
end CFG_TB;
-----
```

Modeling the Structural way

- *Structural* architecture
 - implements the module as a composition of subsystems
 - contains
 - *signal declarations*, for internal interconnections
 - the entity ports are also treated as signals
 - *component instances*
 - instances of previously declared entity/architecture pairs
 - *port maps* in component instances
 - connect signals to component ports

Structural way Example

 Not complete example, just for concept justification ..



Structural way..

- First **declare D-latch** and **and-gate** entities and architectures

```
entity d_latch is  
    port ( d, clk : in bit; q : out bit );  
end entity d_latch;  
  
architecture basic of d_latch is  
begin  
    process (clk, d)  
    begin  
        if clk = '1' then  
            q <= d after 2 ns;  
        end if;  
    end process;  
end basic;
```

```
entity and2 is  
    port ( a, b : in bit; y : out bit );  
end entity and2;  
  
architecture basic of and2 is  
begin  
    process (a, b)  
    begin  
        y <= a and b after 2 ns;  
    end process ;  
end basic;
```


Structural way...

- **Declare** corresponding **components** in register architecture body

```
architecture struct of reg4 is  
  component d_latch  
    port ( d, clk : in bit; q : out bit );  
  end component;  
  component and2  
    port ( a, b : in bit; y : out bit );  
  end component;  
  signal int_clk : bit;  
  
  ...
```

Structural way....

 - Now **use them** to implement the register



```
...
begin
    bit0 : d_latch
        port map ( d0, int_clk, q0 );
    bit1 : d_latch
        port map ( d1, int_clk, q1 );
    bit2 : d_latch
        port map ( d2, int_clk, q2 );
    bit3 : d_latch
        port map ( d3, int_clk, q3 );
    gate : and2
        port map ( en, clk, int_clk );
end struct;
```

Trace the code & Draw the model structure

```
-----  
-- Combinational Logic Design  
-- (ESD book figure 2.4)  
-- by Weijun Zhang, 04/2001  
--  
-- A simple example of VHDL Structure Modeling  
-- we might define two components in two separate files,  
-- in main file, we use port map statement to instantiate  
-- the mapping relationship between each components  
-- and the entire circuit.  
-----
```

```
library ieee;                                -- component #1  
use ieee.std_logic_1164.all;  
  
entity OR_GATE is  
port( X:    in std_logic;  
      Y:    in std_logic;  
      F2:   out std_logic  
);  
end OR_GATE;  
  
architecture behv of OR_GATE is  
begin  
process(X,Y)  
begin  
    F2 <= X or Y;                            -- behavior des.  
end process;  
end behv;
```


```
-----  
library ieee;                                -- component #2  
use ieee.std_logic_1164.all;  
  
entity AND_GATE is  
port( A:    in std_logic;  
      B:    in std_logic;  
      F1:   out std_logic  
);  
end AND_GATE;  
  
architecture behv of AND_GATE is  
begin  
process(A,B)  
begin  
    F1 <= A and B;                            -- behavior des.  
end process;  
end behv;
```

Trace the code &
Draw the model
structure..


```
-----  
library ieee;                                -- top level circuit  
use ieee.std_logic_1164.all;  
use work.all;  
  
entity comb_ckt is  
port(   input1: in std_logic;  
        input2: in std_logic;  
        input3: in std_logic;  
        output: out std_logic  
);  
end comb_ckt;  
  
architecture struct of comb_ckt is  
  
    component AND_GATE is                    -- as entity of AND_GATE  
    port(   A: in std_logic;  
           B: in std_logic;  
           F1: out std_logic  
    );  
    end component;  
  
    component OR_GATE is                     -- as entity of OR_GATE  
    port(   X: in std_logic;  
           Y: in std_logic;  
           F2: out std_logic  
    );  
    end component;  
  
    signal wire: std_logic;                  -- signal just like wire  
  
begin  
  
    -- use sign "=>" to clarify the pin mapping  
  
    Gate1: AND_GATE port map (A=>input1, B=>input2, F1=>wire);  
    Gate2: OR_GATE port map (X=>wire, Y=>input3, F2=>output);  
  
end struct;  
-----
```

Trace the code & Draw the model structure..

- the model

 

- Simulation waveform

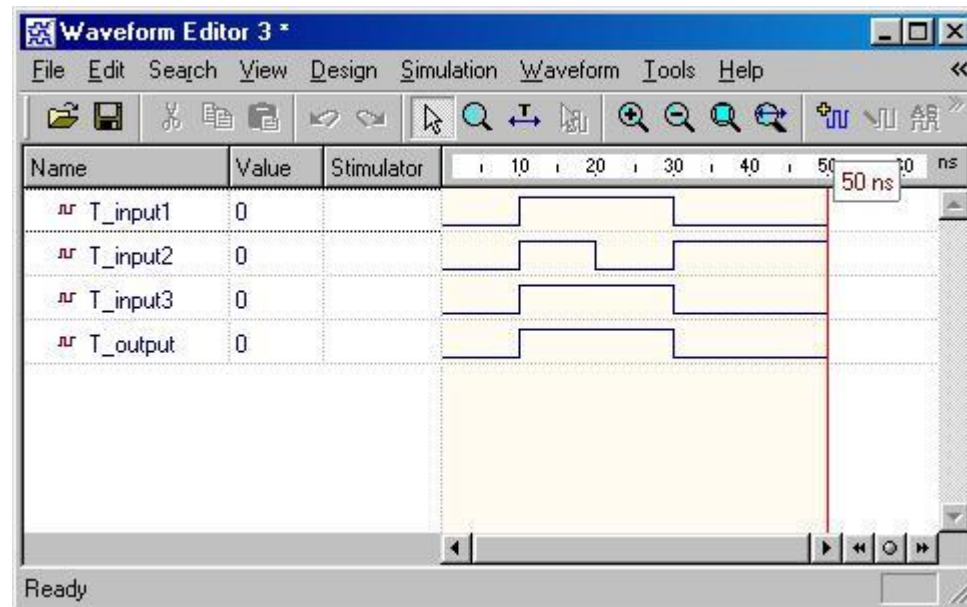


Mixed Behavior and Structure

- An architecture can contain both behavioral and structural parts
 - process statements and component instances
 - collectively called *concurrent statements*
 - processes can read and assign to signals
- Example: register-transfer-level (RTL) Model
 - data path described structurally
 - control section described behaviorally

Mixed Example

 Not complete example, just for concept justification ..



Mixed Example

```
entity multiplier is  
    port ( clk, reset : in bit;  
           multiplicand, multiplier : in integer;  
           product : out integer );  
end multiplier;  
  
architecture mixed of multiplier is  
    signal partial_product, full_product : integer;  
    signal arith_control, result_en, mult_bit, mult_load : bit;  
begin  
    arith_unit : entity work.shift_adder(behavior)  
        port map ( addend => multiplicand, augend => full_product,  
                  sum => partial_product,  
                  add_control => arith_control );  
    result : entity work.reg(behavior)  
        port map ( d => partial_product, q => full_product,  
                  en => result_en, reset => reset );  
  
    ...
```

Mixed Example..

```
...
multiplier_sr : entity work.shift_reg(behavior)
  port map ( d => multiplier, q => mult_bit,
            load => mult_load, clk => clk );
product <= full_product;

process (clk, reset)
  -- variable declarations for control_section
  -- ...
begin
  -- sequential statements to assign values to control signals
  -- ...
end process;
end mixed;
```

- For more details, refer to:
 - VHDL Tutorial: Learn by Example by Weijun Zhang
 - <http://esd.cs.ucr.edu/labs/tutorial/>
 - “**Introduction to VHDL**” presentation by Dr. Adnan Shaout, *The University of Michigan-Dearborn*
 - **The VHDL Cookbook**, Peter J. Ashenden, 1st edition, 1990.
- For inquires, send to:
 - ahmad.elbanna@feng.bu.edu.eg