

Designing with VHDL and FPGA

Instructor:

Dr. Ahmad El-Banna

LAB# 2
FALL 2016



(1)


Agenda

VHDL language constructs

Data flow and Behavioral Implementation


Remember!

3 ways to do the VHDL way

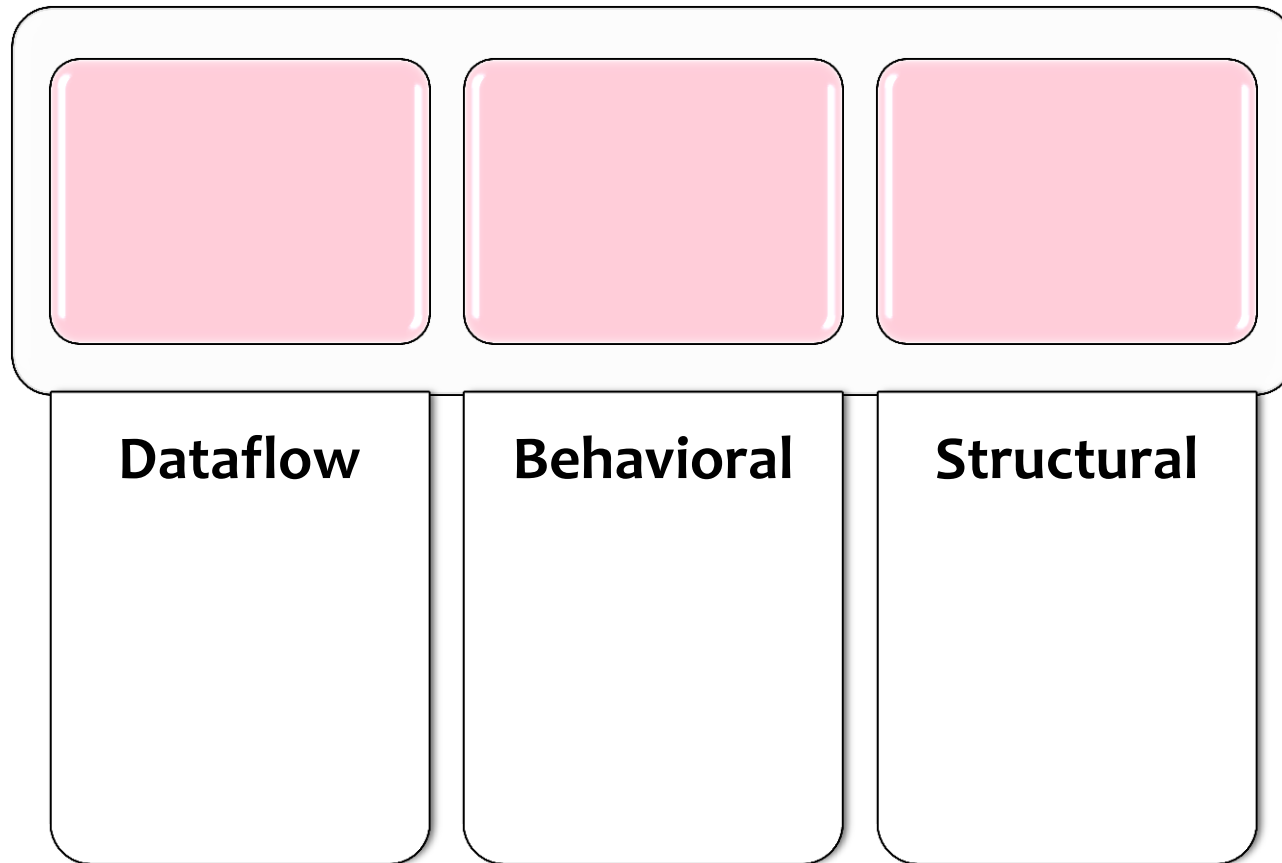

Jumping right in to a Model

 - lets look at a **SR latch** model -- doing it the dataflow way.....
ignore the extra junk for now –




```
entity latch is
  port (s,r : in bit;
        q,nq : out bit);
end latch;
```

```
architecture dataflow of latch is
begin
  q<=r nor nq;
  nq<=s nor q;
end dataflow;
```

Modeling Interfaces

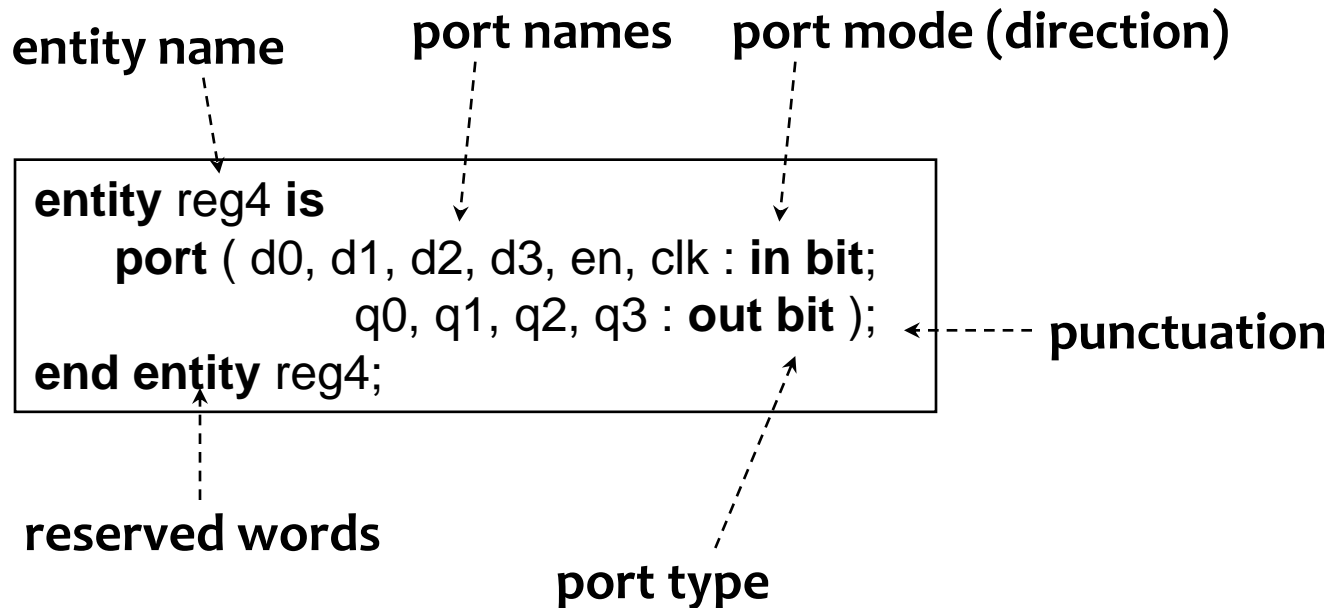- Entity declaration
 - describes the input/output ports of a module



Basic Constructs

- Comments
- Objects
 - Signals
 - Variables
 - Constants
 - Alias

```
-----  
-- example to show the caveat of the out mode  
-----  
architecture arch of mode_demo is  
    signal ab: std_logic; -- ab is the internal signal  
begin  
    ab <= a and b;  
    x <= ab;                -- ab connected to the x output  
    y <= not ab;  
end eg_arch ;
```

```
variable variable_name, variable_name, ... : data_type
```

```
constant BUS_WIDTH: integer := 32;  
constant BUS_BYTES: integer := BUS_WIDTH / 8;
```

```
signal word: std_logic_vector(15 downto 0);  
alias op: std_logic_vector(6 downto 0) is word(15 downto 9);  
alias reg1: std_logic_vector(2 downto 0) is word(8 downto 6);  
alias reg2: std_logic_vector(2 downto 0) is word(5 downto 3);  
alias reg3: std_logic_vector(2 downto 0) is word(2 downto 0);
```

Data Types in vhdl

- **IEEE1164_std_logic package** contains the basic standard logic.
- **IEEE numeric_std package** contains the arithmetic operations.
- Examples of data types :
 - integer: minimal range: $-(2^{31}-1)$ to $2^{31}-1$
 - boolean: (false, true)
 - bit: ('0', '1')
 - bit_vector: a one-dimensional array of bits

Data Types in vhdl..

IEEE std_logic_1164 package

- New data type: std_logic, std_logic_vector
- std_logic:
 - '0', '1': forcing logic '0' and forcing logic 1
 - 'Z': high-impedance, as in a tri-state buffer.
 - 'L' , 'H': weak logic 0 and weak logic 1, as in wired logic.
 - 'U': for uninitialized.
 - '-': don't-care.
- std_logic_vector
 - EX: signal a: std_logic_vector(7 downto 0);

Operators in vhdl

operator	description	data type of operand a	data type of operand b	data type of result
a ** b	exponentiation	integer	integer	integer
abs a	absolute value	integer		integer
not a	negation	boolean, bit, bit_vector		boolean, bit, bit_vector
a * b	multiplication	integer	integer	integer
a / b	division			
a mod b	modulo			
a rem b	remainder			
+ a	identity	integer		integer
- a	negation			
a + b	addition	integer	integer	integer
a - b	subtraction			
a & b	concatenation	1-D array, element	1-D array, element	1-D array

Operators in vhdl..

a sll b	shift left logical	bit_vector	integer	bit_vector
a srl b	shift right logical			
a sla b	shift left arithmetic			
a sra b	shift right arithmetic			
a rol b	rotate left			
a ror b	rotate right			

a = b	equal to	any	same as a	boolean
a /= b	not equal to			
a < b	less than	scalar or 1-D array	same as a	boolean
a <= b	less than or equal to			
a > b	greater than			
a >= b	greater than or equal to			

a and b	and	boolean, bit,	same as a	boolean, bit,
a or b	or	bit_vector		bit_vector
a xor b	xor			
a nand b	nand			
a nor b	nor			
a xnor b	xnor			

Precedence of the VHDL Operators

Table 3.2 Precedence of the VHDL operators

Precedence	Operators
Highest	** abs not
	* / mod rem
	+ - (identity and negation)
	& + - (addition and subtraction)
	sll srl sla sra rol ror
	= /= < <= > >=
Lowest	and or nand nor xor xnor

Precedence of the VHDL Operators

```
a + b > c or a < d
```

The **+** operator will be evaluated first, and then the **>** and **<** operators, and then the **or** operator.

```
a + b + c + d
```

The **a + b** expression will be evaluated first, and then **c** is added, and then **d** is added.

expression be evaluated from right to left:

```
a + (b + (c + d))
```

Unlike the logic expression used in Boolean algebra, the **and** and **or** operators have the same precedence in VHDL, and thus we must use parentheses to specify the desired order, as in

```
(a and b) or (c and d)
```

VHDL vs. Boolean

Table 3.3 VHDL operators versus conventional Boolean algebra notations

VHDL operator	Boolean algebra notation
not	'
and	.
or	+
xor	\oplus
+	+

$$y = a \cdot b + a' \cdot b'$$

When coded in VHDL, This expression becomes

```
y <= (a and b) or ((not a) and (not b));
```

Overloaded Operators in vhdl

There may exist multiple functions with the same name, each for a different data type.

This is known as overloading of a function or operator.

overloaded operator	data type of operand a	data type of operand b	data type of result
not a	std_logic_vector std_logic		same as a
a and b			
a or b			
a xor b	std_logic_vector	same as a	same as a
a nand b	std_logic		
a nor b			
a xnor b			

Concatenation operator

For example, we can shift the elements of the array to the right by two positions and append two 0's to the front:

```
y <= "00" & a(7 downto 2);
```

or append the MSB to the front (known as an arithmetic shift):

```
y <= a(7) & a(7) & a(7 downto 2);
```

or rotate the elements to the right by two positions:

```
y <= a(1 downto 0) & a(7 downto 2);
```

Array aggregate

```
a <= "10100000";
```

```
a <= ('1', '0', '1', '0', '0', '0', '0', '0');
```

```
a <= (7=>'1', 6=>'0', 0=>'0', 1=>'0', 5=>'1',  
      4=>'0', 3=>'0', 2=>'0');
```

```
a <= (7|5=>'1', 6|4|3|2|1|0=>'0');
```

```
a <= (7|5=>'1', others=>'0');
```

```
a <= (others=>'0');
```

It is more compact than

```
a <= "00000000";
```


Designing with VHDL and FPGA

Instructor:

Dr. Ahmad El-Banna

LAB# 3
FALL 2016



(17)

Agenda

Type conversions

Functions in std package

Process, Signals and Variables

Types Conversion

function	data type of operand a	data type of result
<code>to_bit(a)</code>	<code>std_logic</code>	<code>bit</code>
<code>to_stdlogic(a)</code>	<code>bit</code>	<code>std_logic</code>
<code>to_bit_vector(a)</code>	<code>std_logic_vector</code>	<code>bit_vector</code>
<code>to_stdlogicvector(a)</code>	<code>bit_vector</code>	<code>std_logic_vector</code>

Functions in std package

Table 3.7 Functions in the IEEE numeric_std package

Function	Description	Data type of operand a	Data type of operand b	Data type of result
shift_left(a,b)	shift left	unsigned, signed	natural	same as a
shift_right(a,b)	shift right			
rotate_left(a,b)	rotate left			
rotate_right(a,b)	rotate right			
resize(a,b)	resize array	unsigned, signed	natural	same as a
std_match(a,b)	compare '-'	unsigned, signed std_logic_vector, std_logic	same as a	boolean
to_integer(a)	data type	unsigned, signed		integer
to_unsigned(a,b)	conversion	natural	natural	unsigned
to_signed(a,b)		integer	natural	signed

Modeling the Behavior way

- *Architecture body*
 - describes an implementation of an entity
 - may be several per entity
- *Behavioral architecture*
 - describes the algorithm performed by the module
 - contains
 - *process statements*, each containing
 - *sequential statements*, including
 - *signal assignment statements* and
 - *wait statements*

VHDL Process

- Similar to *function* in C lang.
- Contains a set of sequential statements to be executed sequentially
- The whole process is a concurrent statement
- Can be interpreted as a circuit part enclosed inside of a black box
- May or may not be able to be mapped to physical hardware
- Two types of process
 - A process with a sensitivity list
 - A process with wait statement

A process with a sensitivity list

- A process is like a circuit part, which can be
 - active (known as *activated*)
 - inactive (known as *suspended*).
- A process is activated when a signal in the sensitivity list changes its value
- Its statements will be executed sequentially until the end of the process

```
• Syntax
  process(sensitivity_list)
    declarations;
  begin
    sequential statement;
    sequential statement;
    ...
  end process;
```

example

- E.g, 3-input and circuit

```
signal a,b,c,y: std_logic;  
process(a,b,c)  
begin  
    y <= a and b and c;  
end process;
```

- How to interpret this:

```
process(a)  
begin  
    y <= a and b and c;  
end process;
```

- For a combinational circuit, all input should be included in the sensitivity list

A process with wait statement

- Process has no sensitivity list
- Process continues the execution until a wait statement is reached and then suspended
- Forms of wait statement:
 - **wait on** signals;
 - **wait until** boolean_expression;
 - **wait for** time_expression;

```
E.g, 3-input and circuit
process
begin
    y <= a and b and c;
    wait on a, b, c;
end process;
```

- A process can has multiple wait statements
- Process with sensitivity list is preferred for synthesis

Sequential signal assignment

- Syntax

```
signal_name <= value_expression;
```

- Syntax is identical to the simple concurrent signal assignment

```
signal xtmp: bit;
```

- Caution:

- Inside a process, a signal can be assigned multiple times, but only the last assignment takes effect

- E.g.,

```
process(a,b,c,d)
begin
    y <= a or c;           -- yentry := y
    y <= a and b;         -- yexit := a or c;
    y <= c and d;         -- yexit := a and b;
    y <= c and d;         -- yexit := c and d;
end process;              -- y <= yexit
```
- It is same as


```
process(a,b,c,d)
begin
    y <= c and d;
end process;
```

Variables vs. signals

```
process(a,b,c)
  variable tmp: std_logic;
begin
  tmp := '0';
  tmp := tmp or a;
  tmp := tmp or b;
  y <= tmp;
end process;
```

- interpretation:
 
```
process(a,b,c)
  variable tmp0, tmp1, tmp2: std_logic;
begin
  tmp0 := '0';
  tmp1 := tmp0 or a;
  tmp2 := tmp1 or b;
  y <= tmp2;
end process;
```



Variables vs. signals ..

- What happens if signal is used?

```
process(a,b,c,tmp)
begin
    tmp <= '0';
    tmp <= tmp or a;
    tmp <= tmp or b;
end process;
```

-- tmp_{entry} := tmp
-- tmp_{exit} := '0';
-- tmp_{exit} := tmp_{entry} **or** a;
-- tmp_{exit} := tmp_{entry} **or** b;
-- tmp <= tmp_{exit}

- Same as:

```
process(a,b,c,tmp)
begin
    tmp <= tmp or b;
end process;
```

Designing with VHDL and FPGA

Instructor:

Dr. Ahmad El-Banna

LAB# 4
FALL 2016

Agenda

Sequential Statements

if, case, for loop, ... etc

Examples

If statement

Syntax

```
if boolean_expr_1 then
    sequential_statements;
elsif boolean_expr_2 then
    sequential_statements;
elsif boolean_expr_3 then
    sequential_statements;
...
else
    sequential_statements;
end if;
```

E.g., 4-to-1 mux

```
architecture if_arch of mux4 is
begin
    process (a,b,c,d,s)
    begin
        if (s="00") then
            x <= a;
        elsif (s="01") then
            x <= b;
        elsif (s="10") then
            x <= c;
        else
            x <= d;
        end if;
    end process;
end if_arch;
```

<hr/>	
input	output
s	x
<hr/>	
00	a
01	b
10	c
11	d

Example 2

E.g., 2-to- 2^2 binary decoder

```
architecture if_arch of decoder4 is
begin
  process (s)
  begin
    if (s="00") then
      x <= "0001";
    elsif (s="01") then
      x <= "0010";
    elsif (s="10") then
      x <= "0100";
    else
      x <= "1000";
    end if;
  end process;
end if_arch;
```

<hr/>	
input	output
s	x
<hr/>	
0 0	0001
0 1	0010
1 0	0100
1 1	1000
<hr/>	

Example 3

E.g., 4-to-2 priority encoder

```
architecture if_arch of prio_encoder42 is
begin
```

```
  process (r)
```

```
  begin
```

```
    if (r(3)='1') then
```

```
      code <= "11";
```

```
    elsif (r(2)='1') then
```

```
      code <= "10";
```

```
    elsif (r(1)='1') then
```

```
      code <= "01";
```

```
    else
```

```
      code <= "00";
```

```
    end if;
```

```
  end process;
```

```
  active <= r(3) or r(2) or r(1) or r(0);
```

```
end if_arch;
```

input			output	
r	code	active		
1---	11	1		
01--	10	1		
001-	01	1		
0001	00	1		
0000	00	0		

Comparison to conditional signal assignment

- Two statements are the same if there is only one output signal in if statement
- If statement is more flexible
- Sequential statements can be used in then, elsif and else branches:
 - Multiple statements
 - Nested if statements

Note:

According to VHDL definition:

- Only the “then” branch is required; “elsif” and “else” branches are optional
- Signals do not need to be assigned in all branch
- When a signal is unassigned due to omission, it keeps the “previous value” (implying “memory”)

example

```
sig <= value_expr_1 when boolean_expr_1 else
      value_expr_2 when boolean_expr_2 else
      value_expr_3 when boolean_expr_3 else
      . . .
      value_expr_n;
```

It can be written as

```
process (...)
  if boolean_expr_1 then
    sig <= value_expr_1;
  elsif boolean_expr_2 then
    sig <= value_expr_2;
  elsif boolean_expr_3 then
    sig <= value_expr_3;
  . . .
  else
    sig <= value_expr_n;
  end if;
end process
```

e.g., find the max of a, b, c

```
if (a > b) then
  if (a > c) then
    max <= a;  — a > b and a > c
  else
    max <= c;  — a > b and c >= a
  end if;
else
  if (b > c) then
    max <= b;  — b >= a and b > c
  else
    max <= c;  — b >= a and c >= b
  end if;
end if;
```

Case statement

Syntax

```
case case_expression is  
  when choice_1 =>  
    sequential statements;  
  when choice_2 =>  
    sequential statements;  
  ...  
  when choice_n =>  
    sequential statements;  
end case;
```

E.g., 4-to-1 mux

```
architecture case_arch of mux4 is  
begin  
  process(a,b,c,d,s)  
  begin  
    case s is  
      when "00" =>  
        x <= a;  
      when "01" =>  
        x <= b;  
      when "10" =>  
        x <= c;  
      when others =>  
        x <= d;  
    end case;  
  end process;  
end case_arch;
```

input	output
s	x
00	a
01	b
10	c
11	d

Example 2

E.g., 2-to- 2^2 binary decoder

```
architecture case_arch of decoder4 is
begin
  proc1:
  process (s)
  begin
    case s is
      when "00" =>
        x <= "0001";
      when "01" =>
        x <= "0010";
      when "10" =>
        x <= "0100";
      when others =>
        x <= "1000";
    end case;
  end process;
END case_arch;
```

input		output	
s		x	
0	0	0	0001
0	1	0	0010
1	0	0	0100
1	1	1	0000

Example 3

E.g., 4-to-2 priority encoder

architecture case_arch of prio_encoder42 is
begin

 process (r)

 begin

 case r is

 when "1000" | "1001" | "1010" | "1011" |
 "1100" | "1101" | "1110" | "1111" =>
 code <= "11";

 when "0100" | "0101" | "0110" | "0111" =>
 code <= "10";

 when "0010" | "0011" =>
 code <= "01";

 when others =>
 code <= "00";

 end case;

 end process;

 active <= r(3) or r(2) or r(1) or r(0);

end case_arch;

input	output	
r	code	active
1---	11	1
01--	10	1
001-	01	1
0001	00	1
0000	00	0

Case versus if choices

- Note
 - Choice values can NOT be duplicated in **case** statements
 - However, expressions can be duplicated in **if** statement.

```
begin
  process(s)
  begin
    case s is
      when "000" | "001" => y <= (7=>'1' , others
      when "001" => y <= (6=>'1' , others =>'0');
      when "010" => y <= (5=>'1' , others =>'0');
      when "011" => y <= (4=>'1' , others =>'0');
      when "100" => y <= (3=>'1' , others =>'0');
      when "101" => y <= (2=>'1' , others =>'0');
      when "110" => y <= (1=>'1' , others =>'0');
      when others => y <= (0=>'1' , others =>'0');
    end case;
  end process;
end;
```

syntax Error

```
process(r)
begin
  if(r(3)='1') or (r(2)='1') then
    cod<="11";

  elsif(r(2)='1') then
    cod<="10";

  elsif(r(1)='1') then
    cod<="01";
  end if;
end process;
```

syntax OK

Comparison to selected signal assignment

- Two statements are the same if there is only one output signal in case statement
- Case statement is more flexible
- Sequential statements can be used in choice branches

Note:

- According to VHDL definition:
 - Signals do not need to be assigned in all choice branch
 - When a signal is unassigned, it keeps the “previous value” (implying “memory”)

Comparison to selected signal assignment ..

```
with sel_exp select
  sig <= value_expr_1 when choice_1,
        value_expr_2 when choice_2,
        value_expr_3 when choice_3,
        . . .
        value_expr_n when choice_n;
```

It can be rewritten as:

```
case sel_exp is
  when choice_1 =>
    sig <= value_expr_1;
  when choice_2 =>
    sig <= value_expr_2;
  when choice_3 =>
    sig <= value_expr_3;
  . . .

  when choice_n =>
    sig <= value_expr_n;
end case;
```

Designing with VHDL and FPGA

Instructor:

Dr. Ahmad El-Banna

LAB# 5
FALL 2016



Simple for loop statement

- VHDL provides a variety of loop constructs
- Only a restricted form of loop can be synthesized
- Syntax of simple for loop:
for index **in** loop_range **loop**
 sequential statements;
end loop;
- loop_range must be static
- Index assumes value of loop_range from left to right

Example

- E.g., bit-wide xor

```
library ieee;
use ieee.std_logic_1164.all;

entity wide_xor is
  port(
    a, b: in std_logic_vector(3 downto 0);
    y: out std_logic_vector(3 downto 0)
  );
end wide_xor;

architecture demo_arch of wide_xor is
  constant WIDTH: integer := 4;
begin
  process(a, b)
  begin
    for i in (WIDTH-1) downto 0 loop
      y(i) <= a(i) xor b(i);
    end loop;
  end process;
end demo_arch;
```

Example 2


- E.g., reduced-xor

```
library ieee;
use ieee.std_logic_1164.all;

entity reduced_xor_demo is
  port(
    a: in std_logic_vector(3 downto 0);
    y: out std_logic
  );
end reduced_xor_demo;

architecture demo_arch of reduced_xor_demo is
  constant WIDTH: integer := 4;
  signal tmp: std_logic_vector(WIDTH-1 downto 0);
begin
  process(a, tmp)
  begin
    tmp(0) <= a(0);  — boundary bit
    for i in 1 to (WIDTH-1) loop
      tmp(i) <= a(i) xor tmp(i-1);
    end loop;
  end process;
  y <= tmp(WIDTH-1);
end demo_arch;
```

Example

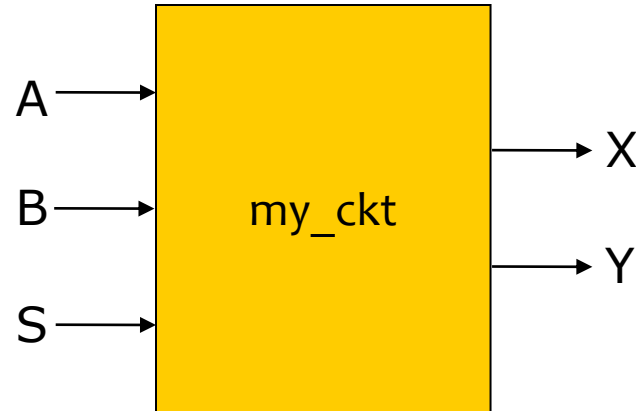

- Example: my_ckt
 - Inputs: A, B, C
 - Outputs: X, Y
- VHDL description:

```
entity my_ckt is
port (
    A: in bit;
    B: in bit;
    S: in bit;
    X: out bit;
    Y: out bit);
end my_ckt ;
```

- Functional Spec.
 - Behavior for output X:
 - When S = 0
X <= A
 - When S = 1
X <= B
 - Behavior for output Y:
 - When X = 0 and S = 0
Y <= '1'
 - Else
Y <= '0'

VHDL Architecture

- VHDL description (sequential behavior):

```
architecture arch_name of my_ckt is
begin
  p1: process (A,B,S)
  begin
    if (S='0') then
      X <= A;
    else
      X <= B;
    end if;

    if ((X = '0') and (S = '0')) then
      Y <= '1';
    else
      Y <= '0';
    end if;

  end process p1;
end;
```

Error: Signals defined as output ports can only be driven and not read

VHDL Architecture..

```
architecture behav_seq of my_ckt is
```

```
signal Xtmp: bit;
```

```
begin
```

```
  p1: process (A,B,S,Xtmp)
```

```
    begin
```

```
      if (S='0') then
```

```
        Xtmp <= A;
```

```
      else
```

```
        Xtmp <= B;
```

```
      end if;
```

```
      if ((Xtmp = '0') and (S = '0')) then
```

```
        Y <= '1';
```

```
      else
```

```
        Y <= '0';
```

```
      end if;
```

```
      X <= Xtmp;
```

```
    end process p1;
```

```
end;
```

Signals can only be defined in this place before the **begin** keyword

General rule: Include all signals in the sensitivity list of the process which either appear in relational comparisons or on the right side of the assignment operator inside the process construct.

In our example:

Xtmp and **S** occur in relational comparisons
A, **B** and **Xtmp** occur on the right side of the assignment operators

Example:

VHDL Architecture...

- VHDL description (concurrent behavior):

```
architecture behav_conc of my_ckt is
```

```
    signal Xtmp: bit;
```

```
begin
```

```
    Xtmp <= A when (S='0') else  
           B;
```

```
    Y <= '1' when ((Xtmp = '0') and (S = '0')) else  
           '0';
```

```
    X <= Xtmp;
```

```
end ;
```

EXAMPLES

Comparator Example

Behavior Code

```
-----  
-- n-bit Comparator (ESD book figure 2.5) by Weijun Zhang, 04/2001  
-- this simple comparator has two n-bit inputs & three 1-bit outputs  
-----
```

```
library ieee;  
use ieee.std_logic_1164.all;  
-----  
entity Comparator is  
  generic(n: natural :=2);  
  port(   A:      in std_logic_vector(n-1 downto 0);  
         B:      in std_logic_vector(n-1 downto 0);  
        less:    out std_logic;  
        equal:   out std_logic;  
        greater: out std_logic  
  );  
end Comparator;  
-----
```

Comparator Example..

Behavior Code & Simulation Waveforms

architecture behv of Comparator is

begin

 process(A,B)

 begin

 if (A<B) then

 less <= '1';

 equal <= '0';

 greater <= '0';

 elsif (A=B) then

 less <= '0';

 equal <= '1';

 greater <= '0';

 else

 less <= '0';

 equal <= '0';


 greater <= '1';

 end if;

 end process;

end behv;

Simulation Waveforms

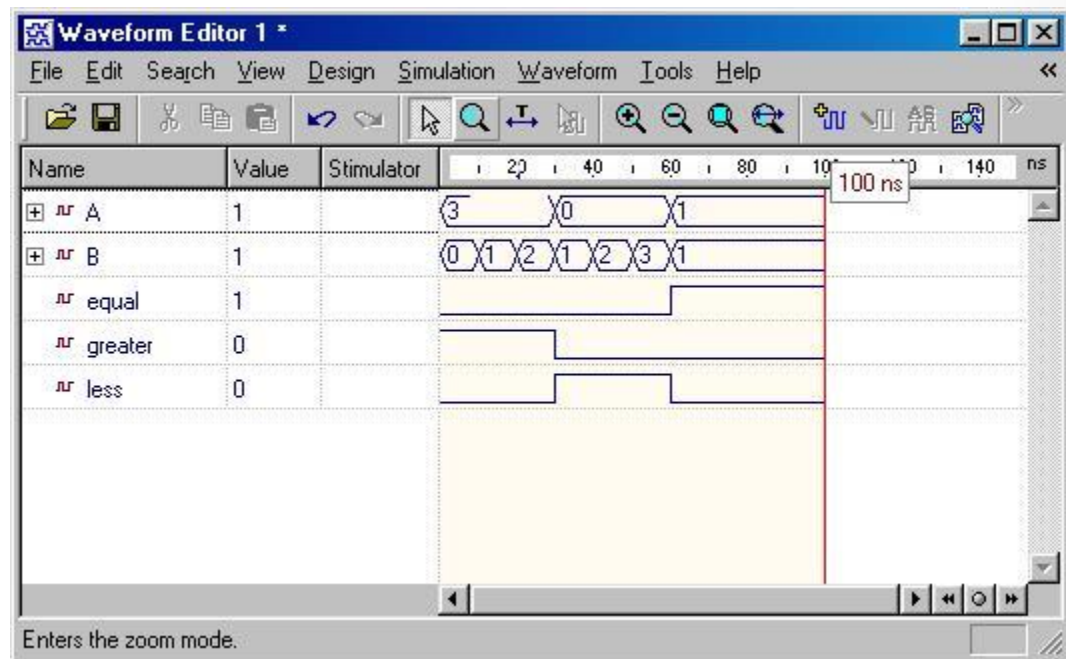

4x1 Multiplexer

-- VHDL code for 4:1 multiplexor-- (ESD book figure 2.5)-- by Weijun Zhang, 04/2001

---- Multiplexor is a device to select different inputs to outputs. we use 3 bits vector to -- describe its I/O ports

```
library ieee;  
use ieee.std_logic_1164.all;
```

```
entity Mux is  
port(  
    I3:      in std_logic_vector(2 downto 0);  
    I2:      in std_logic_vector(2 downto 0);  
    I1:      in std_logic_vector(2 downto 0);  
    I0:      in std_logic_vector(2 downto 0);  
    S:       in std_logic_vector(1 downto 0);  
    O:       out std_logic_vector(2 downto 0)  
);  
end Mux;
```

4x1 Multiplexer ..

architecture behv1 of Mux is

begin

process(l3,l2,l1,l0,S)

begin

-- use case statement

case S is

when "00" => O <= l0;

when "01" => O <= l1;

when "10" => O <= l2;

when "11" => O <= l3;

when others => O <= "ZZZ";

end case;

end process;

end behv1;

architecture behv2 of Mux is

begin

-- use when.. else statement

O <= l0 when S="00" else

l1 when S="01" else


l2 when S="10" else

l3 when S="11" else

"ZZZ";

end behv2;

Simulation Waveforms

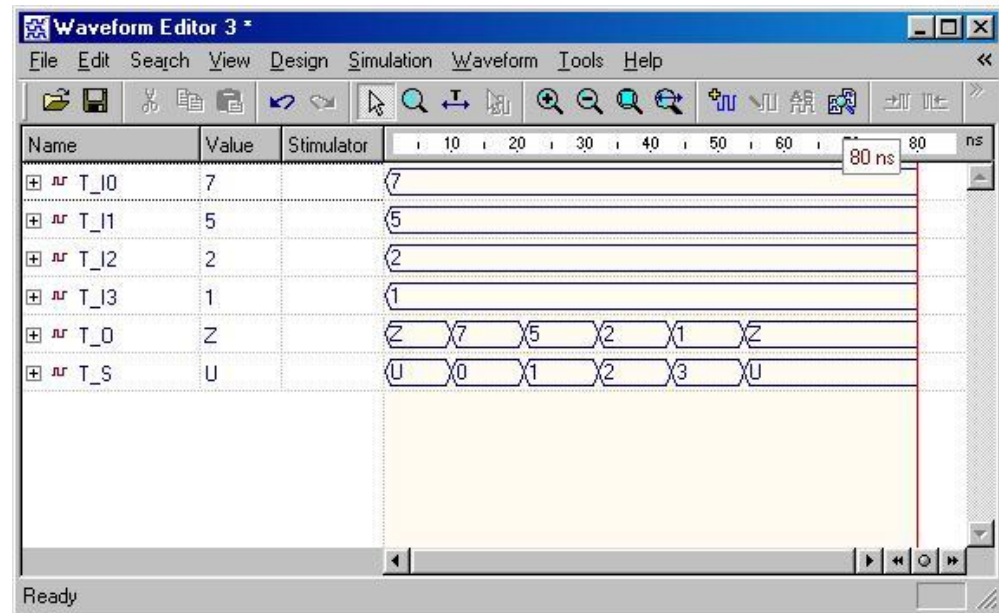

Decoder

```
-----  
-- 2:4 Decoder (ESD figure 2.5)-- by Weijun Zhang, 04/2001  
-- decoder is a kind of inverse process-- of multiplexor  
-----
```

```
library ieee;  
use ieee.std_logic_1164.all;  
-----
```

```
entity DECODER is  
port(   I:      in std_logic_vector(1 downto 0);  
       O:      out std_logic_vector(3 downto 0)  
);  
end DECODER;  
-----
```

architecture behv of DECODER is

begin

 -- process statement

 process (I)

 begin

 -- use case statement

 case I is

 when "00" => O <= "0001";

 when "01" => O <= "0010";

 when "10" => O <= "0100";

 when "11" => O <= "1000";

 when others => O <= "XXXX";

 end case;

 end process;

end behv;

architecture when_else of DECODER is

begin

 -- use when..else statement

 O <= "0001" when I = "00" else


 "0010" when I = "01" else

 "0100" when I = "10" else

 "1000" when I = "11" else

 "XXXX";

end when_else;

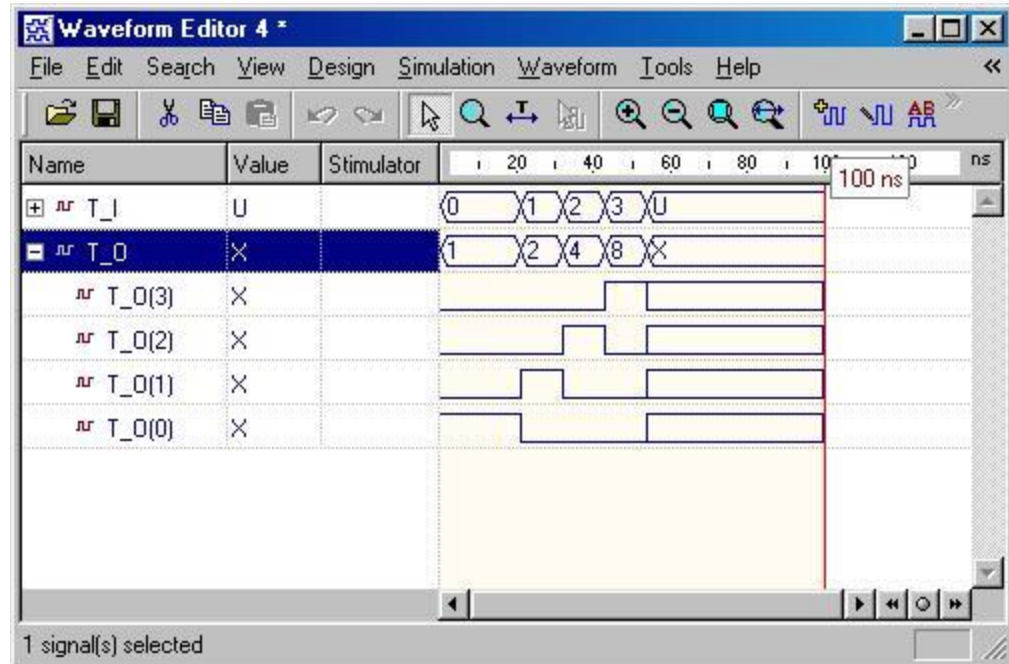

- For more details, refer to:
 - VHDL Tutorial: Learn by Example by Weijun Zhang
 - <http://esd.cs.ucr.edu/labs/tutorial/>
 - “**Introduction to VHDL**” presentation by Dr. Adnan Shaout, *The University of Michigan-Dearborn*
 - **The VHDL Cookbook**, Peter J. Ashenden, 1st edition, 1990.
- For inquires, send to:
 - ahmad.elbanna@feng.bu.edu.eg